

# Using the bq2954 to Charge the LiFePO<sub>4</sub> Battery

Mao Ye

PMP - Portable Power

## ABSTRACT

This application report describes how to use the bq2954 charge controller device to provide a high-efficiency switching-mode charging solution for multi-cell LiFePO<sub>4</sub> battery.

## 1 Introduction

The bq2954 was designed to charge Li-ion and Li-polymer battery packs. Its regulation voltage set point can be easily adjusted by two external resistors, which give an opportunity to support new developed LiFePO<sub>4</sub> battery. This application report shows how to use the bq2954 to provide a high-efficiency switching-mode charging solution for the multi-cell LiFePO<sub>4</sub> battery.

The LiFePO<sub>4</sub> battery has many unique features such as very high thermal runaway temperature, very high discharge current capability and high charge current. These special features make it very attractive in many applications such as power tools. Figure 1 shows a typical open circuit voltage (OCV) curve versus depth of discharge (DOD) of ANR26650M1 LiFePO<sub>4</sub> from A123Systems. Figure 2 shows the typical discharge characteristics at 25°C<sup>[1]</sup> and it is able to support very high discharge rate. The recommended charge voltage is 3.6 V and termination current is 50 mA.

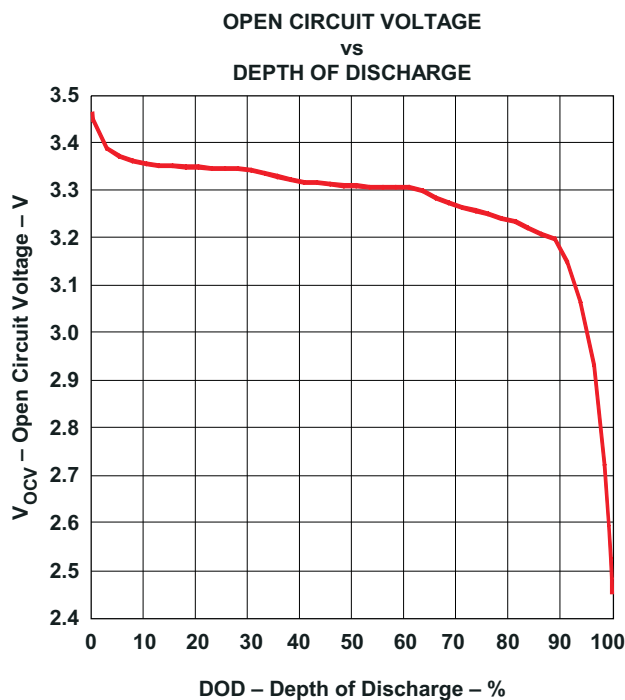


Figure 1.

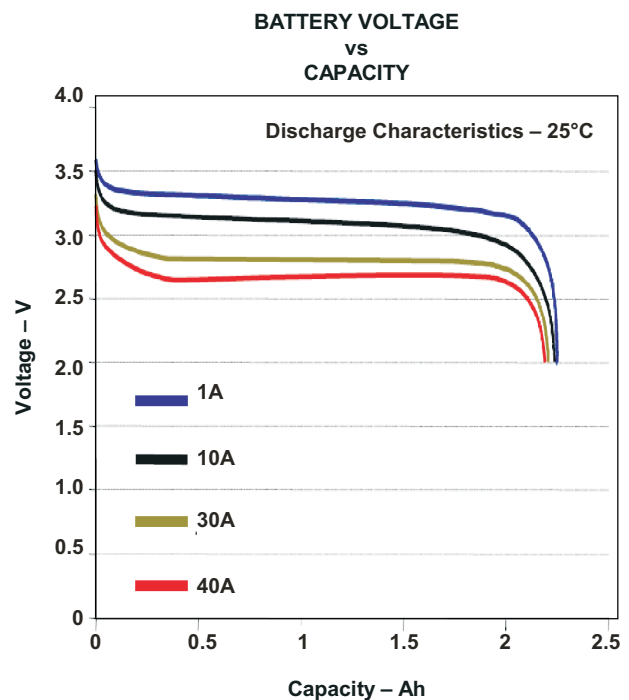


Figure 2.

This bq2954 prototype for a 6-cell application was developed to evaluate the performance for charging the LiFePO<sub>4</sub> battery and demonstrating its multi-cell application capability. The maximum charge voltage for each cell is 3.6 V, therefore 6-cells yield 21.6 V of maximum output voltage. Given the maximum 80% duty cycle limit of bq2954 and estimating 90% power conversion efficiency, the input voltage should be 30 V. To fast charge the LiFePO<sub>4</sub> battery, the prototype was designed to provide 5 A (for a 30-minute charge) charge current. The power stage design is straightforward. [Figure 3](#) shows the schematic.

The output inductor (L1) is a key component. Its value is determined by the specified charge current ripple. 20% of ripple current is typically selected in a practical design. To reduce the size of the output inductor, a 200-kHz frequency (the maximum frequency of bq2954) is selected. Below is the design procedure.

## 2 Step-By-Step Design Procedure

### 2.1 System Design Specification

- $V_{IN} = 30\text{ V}$
- $V_{BAT} = 21.6\text{ V}$  (6-cell, 3.6-V per cell)
- $I_{CHARGE} = 5\text{ A}$
- Inductor ripple current  $\Delta I_L = 20\%$  of fast charge current
- Frequency  $f = 200\text{ kHz}$

### 2.2 Inductor Design

The inductance is given by [Equation 1](#).

$$L_1 = \frac{V_{BAT} \times (V_{IN} - V_{BAT})}{V_{IN} \times f \times \Delta I_L} \quad (1)$$

The highest inductor ripple current occurs when the battery voltage equals half of the input voltage. Here  $V_{BAT} = 15\text{ V}$  (6-Cell, 2.5-V per cell) generates highest inductor ripple current.

$$L_1 = \frac{15 \times (30 - 15)}{30 \times (200 \times 10^3) \times 5 \times 0.2} \quad (2)$$

$$L_1 = 37.5\ \mu\text{H}.$$

Select 33- $\mu\text{H}$  standard value for output inductor.

Calculate the total ripple current with the 33- $\mu\text{H}$  inductor.

$$\Delta I_L = \frac{V_{BAT} \times (V_{IN} - V_{BAT})}{V_{IN} \times f \times L_1} \quad (3)$$

$$\Delta I_L = \frac{15 \times (30 - 15)}{30 \times (200 \times 10^3) \times (33 \times 10^{-6})} \quad (4)$$

$$\Delta I_L = 1.14\text{ A}$$

Calculate the maximum output current.

$$I_{LPK} = I_{OUT} + \frac{\Delta I_L}{2} \quad (5)$$

$$I_{LPK} = 5 + \frac{1.14}{2} \quad (6)$$

$$I_{LPK} = 5.57\text{ A}$$

A 33- $\mu\text{H}$ , 7-A inductor SER2817H-333KL from Coilcraft is selected.

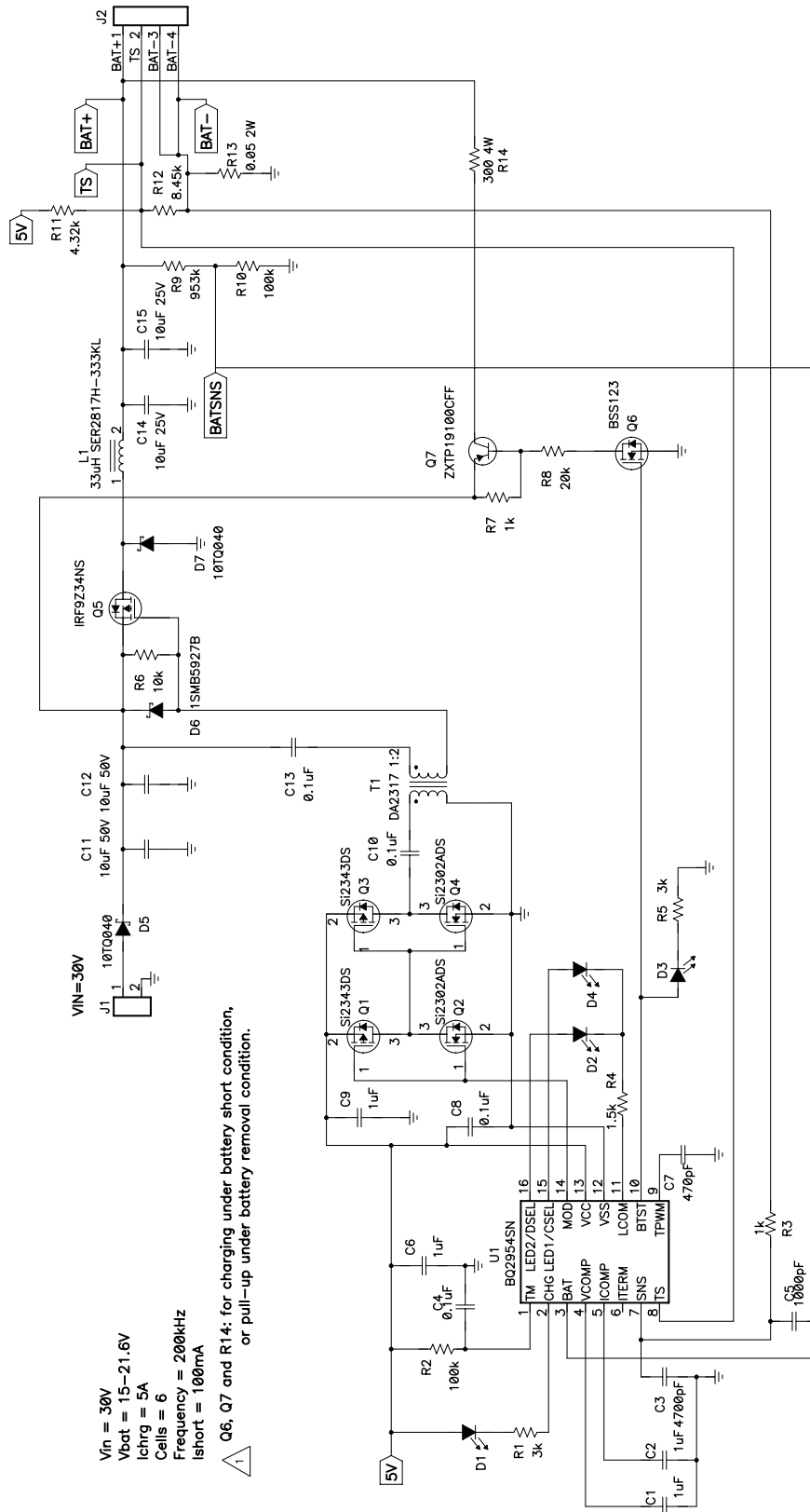


Figure 3. bq2954 Schematic For a 6-Cell, 5-A LiFePO<sub>4</sub> Battery Application

### 2.3 Input and Output Capacitor Design

The input capacitor voltage ripple should be small enough to maintain a DC voltage at the input stage. Assume the input current is DC and ignore output current ripple and power loss. Equation 7 calculates the input voltage ripple.

$$\Delta V_{IN} = \frac{I_{CHG} \times (V_{IN} - V_{BAT}) \times V_{BAT}}{V_{IN}^2 \times f \times C_{IN}} \quad (7)$$

The highest input ripple voltage occurs when the battery voltage equals half of the input voltage. Here  $V_{BAT}=15$  V (6-cell, 2.5-V per cell) generates highest input ripple voltage. Select two 10- $\mu$ F ceramic capacitors in parallel as the input capacitor.

$$\Delta V_{IN} = \frac{5 \times (30 - 15) \times 15}{30^2 \times (200 \times 10^3) \times (20 \times 10^{-6})} \quad (8)$$

$\Delta V_{IN} = 0.3125$  V, which is approximately 1% of input voltage.

Also select two 10- $\mu$ F ceramic capacitors in parallel as output capacitor. The output voltage ripple is given by Equation 9.

$$\Delta V_{OUT} = \frac{\Delta I_L}{8 \times f \times C_{OUT}} \quad (9)$$

$$\Delta V_{OUT} = \frac{1.14}{8 \times (200 \times 10^3) \times (20 \times 10^{-6})} \quad (10)$$

$\Delta V_{OUT} = 35.625$  mV, which is very small compared to output voltage.

### 2.4 Voltage Divider Design

R9 and R10 voltage divider determine the final voltage regulation point. According to the datasheet Equation 11 is used for calculation.

$$\frac{R_9}{R_{10}} = \frac{N \times V_{CELL}}{V_{REG}} - 1 \quad (11)$$

where

- Number of cells in series  $N = 6$
- Charging cell voltage  $V_{CELL} = 3.6$  V
- Internal reference  $V_{REG} = 2.05$  V

$$\frac{R_9}{R_{10}} = \frac{6 \times 3.6}{2.05} - 1 = 9.5366 \quad (12)$$

select

- $R_{10} = 100$  k $\Omega$
- $R_9 = 953.66$  k $\Omega$
- $R_9 = 953$  k $\Omega$  standard value

### 2.5 Current Sense Resistor

R13 is the current sensing resistor. A 5-A charge current should generate a 250-mV voltage drop according to datasheet. Therefore, a 50-m $\Omega$ , 2-W current sensing resistor is selected.

## 2.6 Control Circuit Design

The control circuit is similar to the datasheet typical application circuit in the evaluation module (EVM) schematic. bq2954 was configured as Mode 3 so that BTST pin can be used to drive Q6 and Q7 for pre-charge battery. The maximum pre-charge current is limited to 100 mA by R14. The ITERM pin is left floating so that the termination current is 250 mA with a 5-A fast charge current.

This controller requires a 5-V bias power supply which can be easily generated by a wide-input-range, step-down SWIFT™ converter such as the TPS5410.

## 2.7 Gate Drive Circuit and Power Stage Design

Q1 to Q4 are two inverter buffers that provide correct logic and drive an isolation transformer. These four MOSFETs can be replaced by one single-channel high-speed MOSFET driver such as the TPS2829. A DA2317 1:2 turns ratio gate drive transformer from Coilcraft is used. D6 is used to clamp the gate voltage to a safe level for the 55-V top-switch P-channel MOSFET Q5. A 40-V Schottky diode (D7) is selected as the bottom switch of the buck converter. The D5 diode prevents battery leakage current when the input voltage is removed and provides short circuit protection when the voltage input is shorted to ground.

## 2.8 Test Results

The P-channel MOSFET gate, drain and inductor current waveforms are shown in Figure 4. Figure 5 shows the measured power stage efficiency with battery voltage. The efficiency is between 92.5% and 93.5% when the battery voltage changes from 15 V to 21.6 V with a 5.28-A fast charge current. This represents a power stage loss between 6.4 W and 7.7 W. The test shows that this design is practical. It is easy to configure this circuit for charging any number of cells with different chemistries by selecting the external resistor divider R9 and R10.

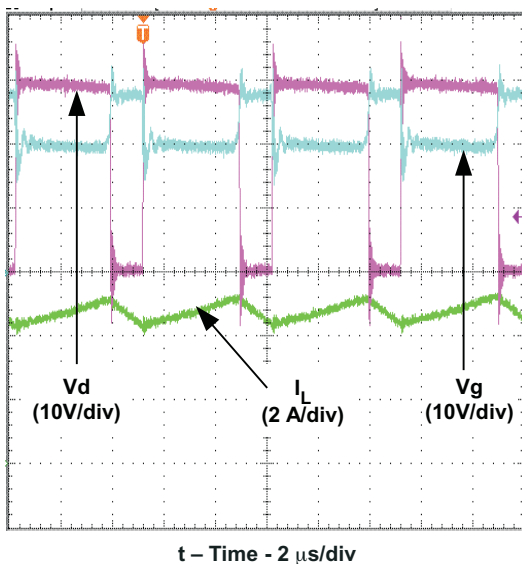


Figure 4.

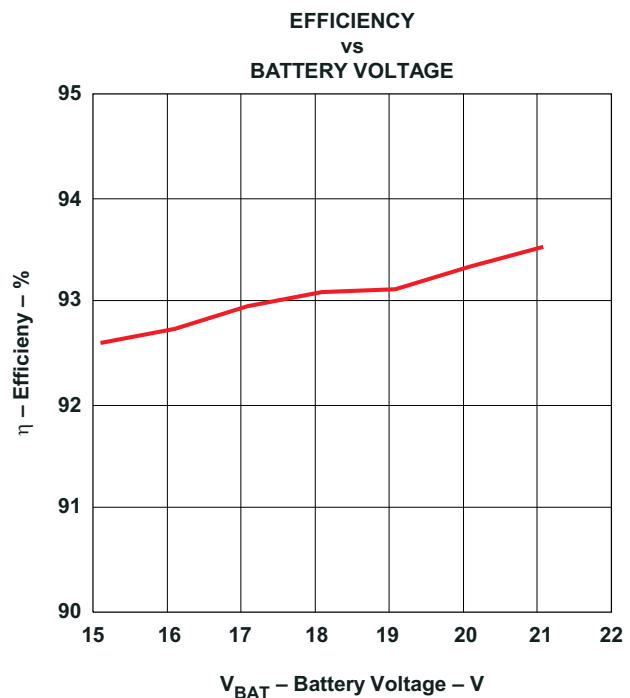


Figure 5.

## 2.9 References

1. ANR26650M1 LiFePO4 battery cell datasheet. ([http://a123systems.textdriven.com/product/pdf/1/ANR26650M1\\_Datasheet\\_NOV\\_2007.pdf](http://a123systems.textdriven.com/product/pdf/1/ANR26650M1_Datasheet_NOV_2007.pdf))
2. bq2954 datasheet (<http://focus.ti.com/lit/ds/symlink/bq2954.pdf>)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright 2008, Texas Instruments Incorporated