

***1U 51-0286 Debug
Waveform Capture***

Acumentrics Corporation

Sep 26, 2011

Test Conditions & Setup:

- PCB Level EUT: 51-0206 Unit#1 (with 51-0284, 51-0289, 51-0290)
- System Level EUT: NA
- Latest PCB Modification: Aug 22, 2011
- Vac_input: 90-250Vac
- Vacout= 120Vac Nules specified otherwise
- System set-up:
- Loading Condition:
 - As specified
- Ambient= 25C

Test Equipments:

- Tektronix DPO 4034, Scope (BW=350MHz unless specified otherwise) w/P6139A probes
- Differential Voltage Probe: TEK P5205
- Current Monitoring Instrument:
Tektronix TCPA400 base with TCP404XL Probe
Tektronix TCP0030 probe
- AC Source: California Instrument 3000iL and Variac
- DC Source: Agilent N5772A
- Load: 3000W resistive load bank
Chroma 63804 AC/DC Electronic Load

Objective:


The purpose is to record the critical operational waveforms and data during the process of debug and troubleshooting.

Summary:

Section I: AC/DC Front-End 51-0286-01 Unit#1 @25C

Unit #1 51-0286 w/T201 Gapped 5mil


Sep 21, 2011

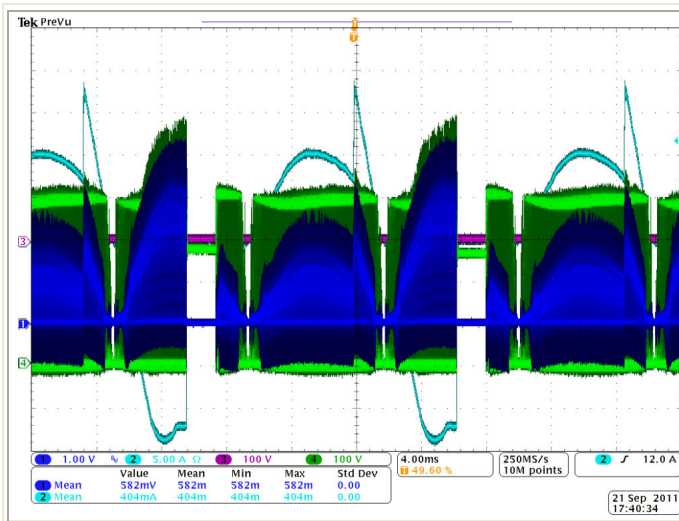

CH1: V_C202 (CT Xfmr #1)
 CH2: lac_input (5A/Div)
 CH3: NA
 CH4: V-Q102D-S (MOS#1)
 PFC_out: 1170W CC
 Vac = decrease from 120V

Result:
 AC Source: Variac
 Tek0098


Figure 1: AC Input Current Instability

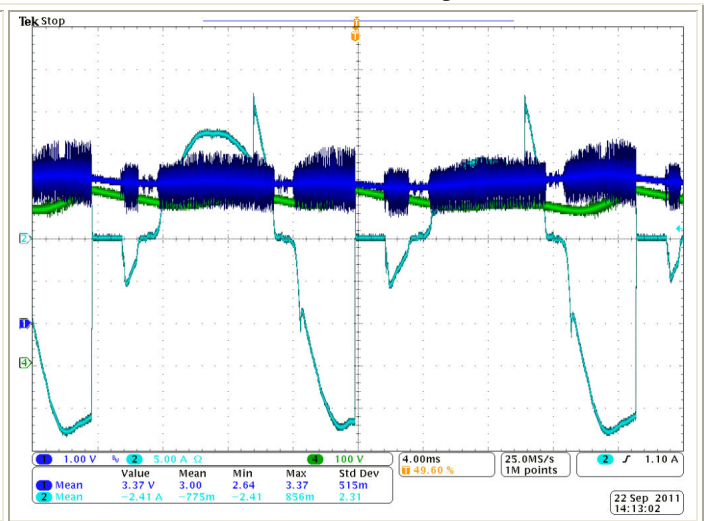

CH1: V_C221 (VEAO)
 CH2: lac_input (5A/Div)
 CH3: NA
 CH4: V_+400VDC
 PFC_out: 1170W CC
 Vac = decrease from 120V

Result:
 AC Source: Variac
 Tek0099


Figure 2: AC Input Current Instability

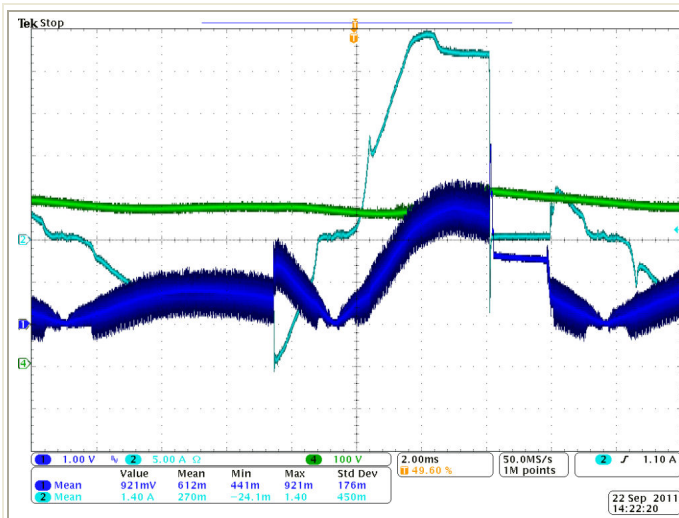

CH1: V_R251 (VIMO)
 CH2: lac_input (5A/Div)
 CH3: NA
 CH4: V_+400VDC
 PFC_out: 1170W CC
 Vac = decrease from 120V

Result:
 AC Source: Variac
 Tek0100


Figure 3: AC Input Current Instability

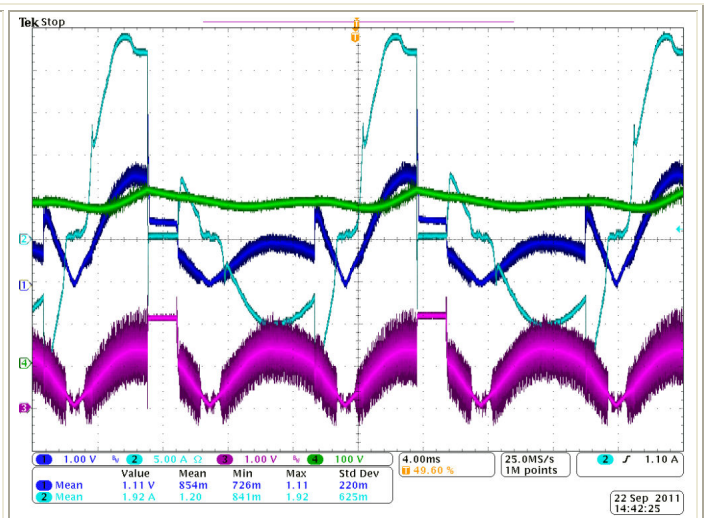

CH1: V_R251 (VIMO)
 CH2: lac_input (5A/Div)
 CH3: V_vinac
 CH4: V_+400VDC
 PFC_out: 1170W CC
 Vac = decrease from 120V

Result:
 AC Source: Variac
 Tek0101

Figure 4: AC Input Current Instability

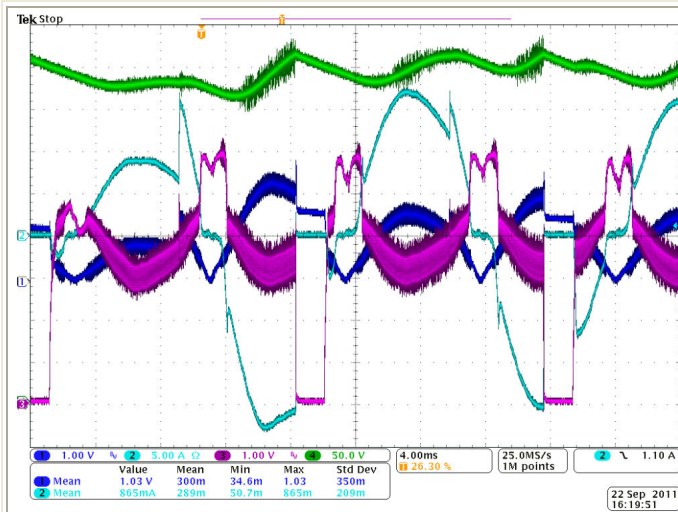

CH1: V_R251 (VIMO)
 CH2: lac_input (5A/Div)
 CH3: V_C229 (VCAOA)
 CH4: V_+400VDC
 PFC_out: 1170W CC


Result:

AC Source: Variac

Vac = decrease from 120V

Tek0102

Figure 5: AC Input Current Instability

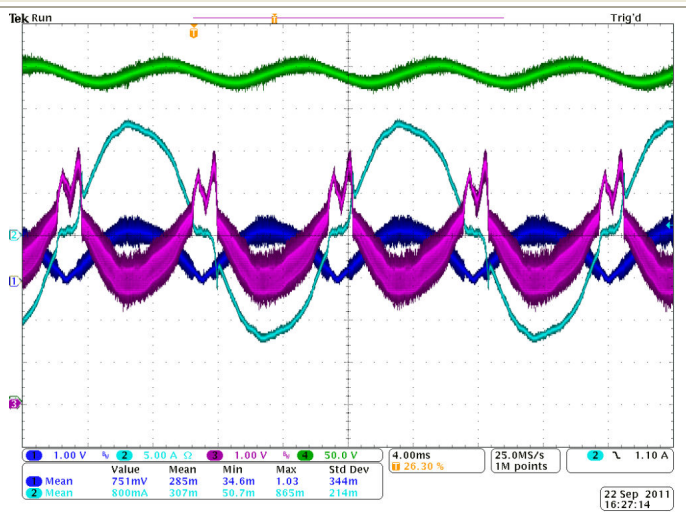

CH1: V_R251 (VIMO)
 CH2: lac_input (5A/Div)
 CH3: V_C229 (VCAOB)
 CH4: V_+400VDC
 PFC_out: 1170W CC


Result:

AC Source: Variac

Vac = 135V

Tek0103

Figure 6: AC Input Current Under Normal Operation

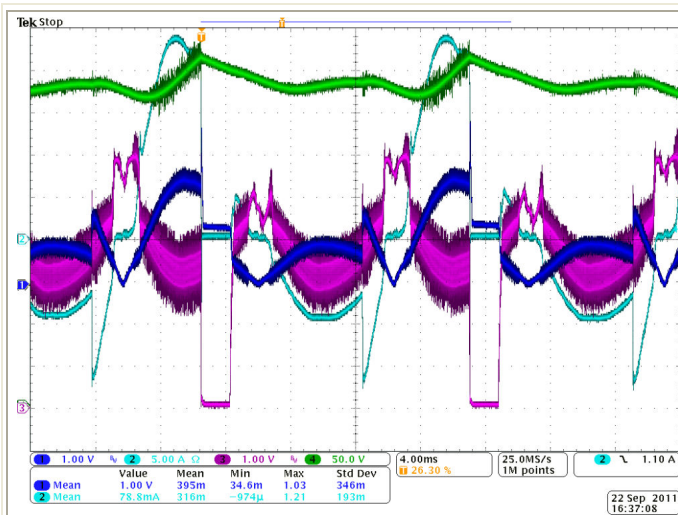

CH1: V_R251 (VIMO)
 CH2: lac_input (5A/Div)
 CH3: V_C226 (VCAOB)
 CH4: V_+400VDC
 PFC_out: 1170W CC


Result:

AC Source: Variac

Vac = decrease from 120V

Tek0104

Figure 7: AC Input Current Instability

 


CH1: Vac_input
 CH2: lac_input (5A/Div)
 CH3: Vac_out
 CH4: lac_out
 Pac_out: 1000W

Result:

Tek0172

Figure 8: 1000W Load Steady State Input Waveforms

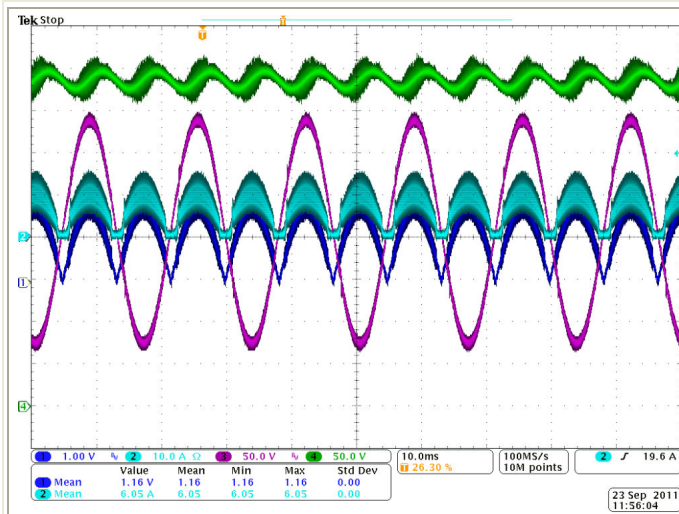

CH1: V_R251 (VIMO)
 CH2: I_L1 (5A/Div)
 CH3: Vac Input
 CH4: V_+400VDC
 PFC_out: 1170W CC


Vac = 95V

Result:

AC Source: California Instrument 3001i

Tek0105

Figure 9: AC Input Current Under Normal Operation

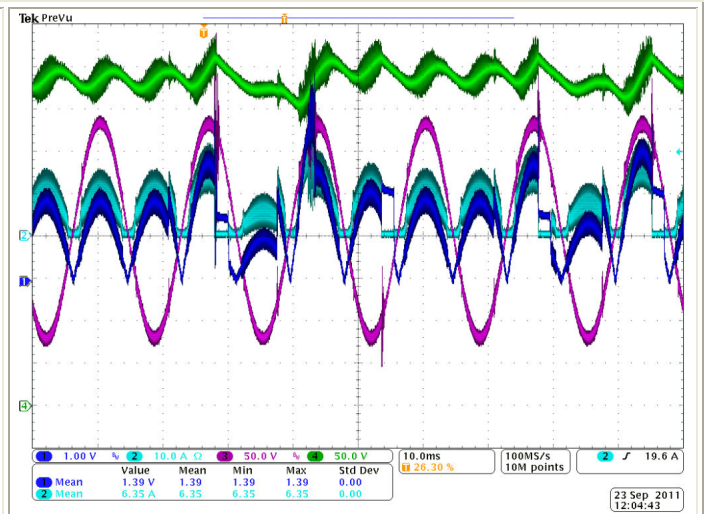

CH1: V_R251 (VIMO)
 CH2: I_L1 (5A/Div)
 CH3: Vac Input
 CH4: V_+400VDC
 PFC_out: 1170W CC


Vac = decrease from 95V

Result:

AC Source: California Instrument 3001i

Tek0105

Figure 10: AC Input current

 


CH1: Vac_input
 CH2: Iac_input (5A/Div)
 CH3: Vac_out
 CH4: Iac_out
 Pac_out: 0W

Vac = 250V

Result:

Tek0176

Figure 11: No Load Steady State Input Waveforms

 

CH1: Vac_input
 CH2: Iac_input (5A/Div)
 CH3: Vac_out
 CH4: Iac_out
 Pac_out: 1000W

Vac = 250V

Result:

Tek0175

Figure 12: 1000W Load Steady State Input Waveforms