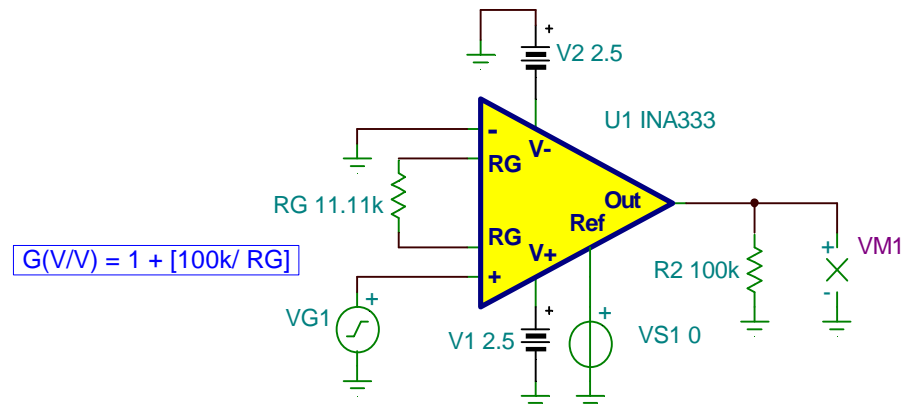


INA333 TINA-TI Reference Design



Circuit configurations altered as needed for each particular test

