

$$V_{\text{ref}} := 4.096\text{V} \quad R_{\text{pot}} := 100\text{k}\Omega$$

$$I_{\text{inmin}} := \frac{4\text{mA}}{100} \quad I_{\text{inmin}} = 40 \times 10^{-6} \text{ A}$$

$$I_{\text{inmax}} := \frac{20\text{mA}}{100} \quad I_{\text{inmax}} = 200 \times 10^{-6} \text{ A}$$

$$I_{\text{inspan}} := \frac{16\text{mA}}{100} \quad I_{\text{inspan}} = 160 \times 10^{-6} \text{ A}$$

$$I_{\text{inspan}} = \left(\frac{V_{\text{ref}}}{R_Z} - \frac{V_{\text{ref}}}{R_Z + R_{\text{pot}}} \right)$$

$$R_Z := \frac{\frac{\sqrt{I_{\text{inspan}} \cdot R_{\text{pot}} \cdot (4 \cdot V_{\text{ref}} + I_{\text{inspan}} \cdot R_{\text{pot}})}}{2} - \frac{I_{\text{inspan}} \cdot R_{\text{pot}}}{2}}{I_{\text{inspan}}}$$

$$R_Z = 21.134 \times 10^3 \Omega$$

$$I_{\text{inmin}} = \left(\frac{V_{\text{ref}}}{R_Z + R_{\text{pot}}} + \frac{V_{\text{ref}}}{R_{\text{sh}}} \right)$$

$$R_{\text{sh}} := \frac{V_{\text{ref}}}{I_{\text{inmin}} - \frac{V_{\text{ref}}}{R_Z + R_{\text{pot}}}} = 662.128 \times 10^3 \Omega$$

$$I_{\text{outmin}} := \left(\frac{V_{\text{ref}}}{R_Z + R_{\text{pot}}} + \frac{V_{\text{ref}}}{R_{\text{sh}}} \right) \cdot 100 = 4 \times 10^{-3} \text{ A}$$

$$I_{\text{outmax}} := \left(\frac{V_{\text{ref}}}{R_Z + 0} + \frac{V_{\text{ref}}}{R_{\text{sh}}} \right) \cdot 100 = 20 \times 10^{-3} \text{ A}$$

We'll choose the XTR116 which has a V_{ref} of 4.096V, and we'll also select a 0-100k Ω potentiometer.

The XTR116 has a current gain of 100A/A. Therefore, in order to achieve I_{out} of 4-20mA, we must provide I_{in} of 40-200 μ A.

We use a known value (I_{inspan}) to calculate our first unknown value (R_Z).

Solve the I_{inspan} equation for R_Z .

Since we started the calculations with the value of R_{pot} already chosen, we add a shunt resistor to better control the current in.

Correct current values are achieved with our calculated resistors.