

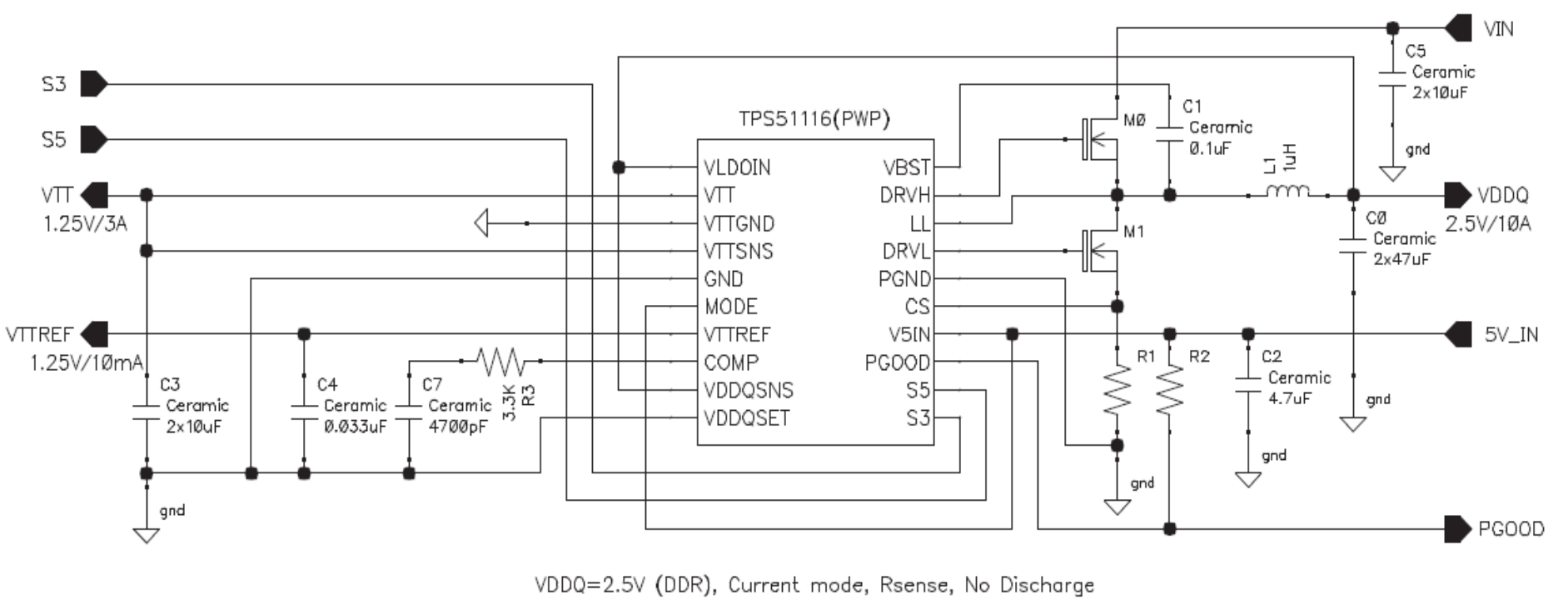


Figure 6. Current Mode, PWP Package

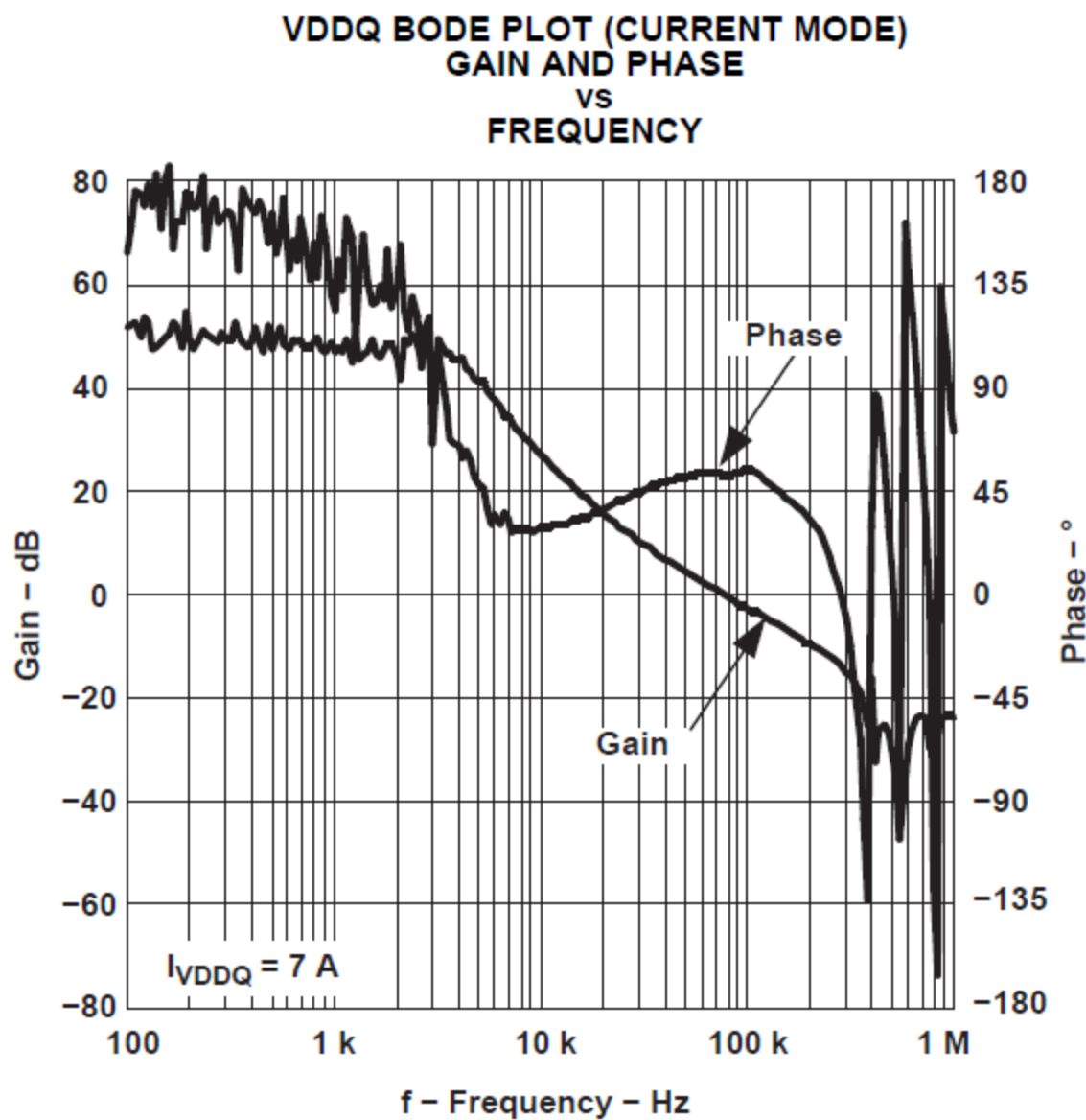


Figure 34.

Total open loop transfer function of the whole system is given by [Equation 6](#).

$$H(s) = H_1(s) \times H_2(s) \times H_3(s) \quad (6)$$



Assuming $RL \gg ESR$, $R_O \gg R_C$ and $C_C \gg C_{C2}$, each transfer function of the three blocks is shown starting with [Equation 7](#).

$$H_1(s) = \frac{R_2}{(R_2 + R_1)} \quad (7)$$



$$H_2(s) = -gm \times \frac{R_O (1 + s \times C_C \times R_C)}{(1 + s \times C_C \times R_O)(1 + s \times C_{C2} \times R_C)} \quad (8)$$

$$H_3(s) = \frac{(1 + s \times C_O \times ESR)}{(1 + s \times C_O \times RL)} \times \frac{RL}{R_S} \quad (9)$$

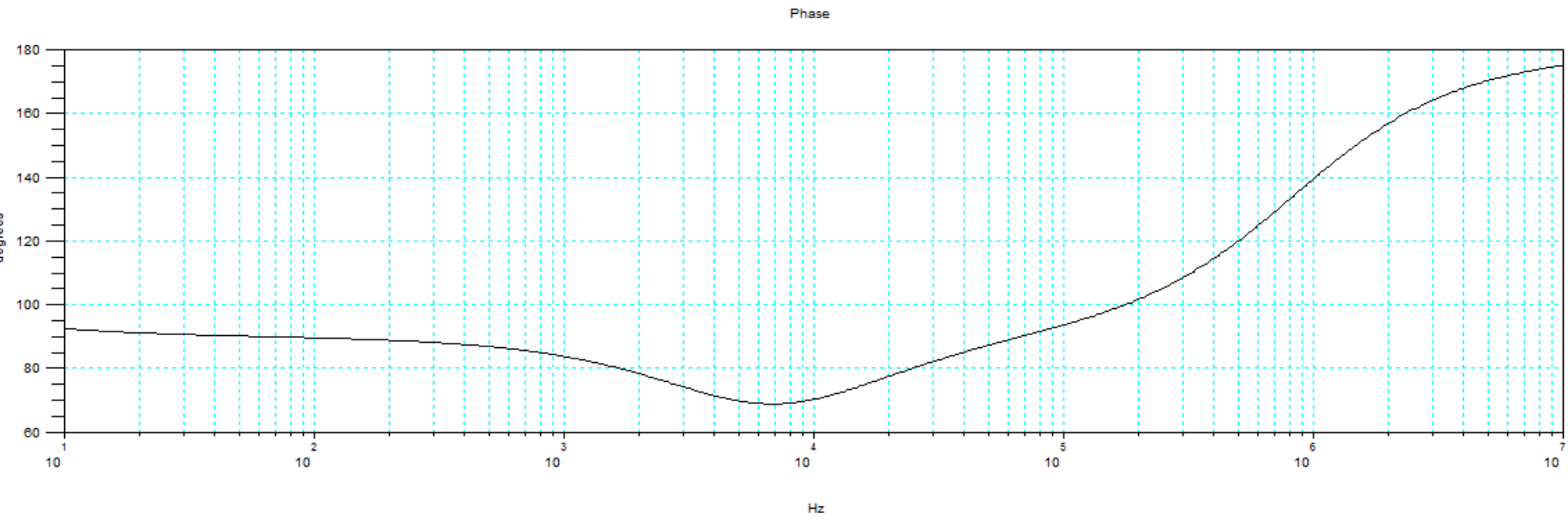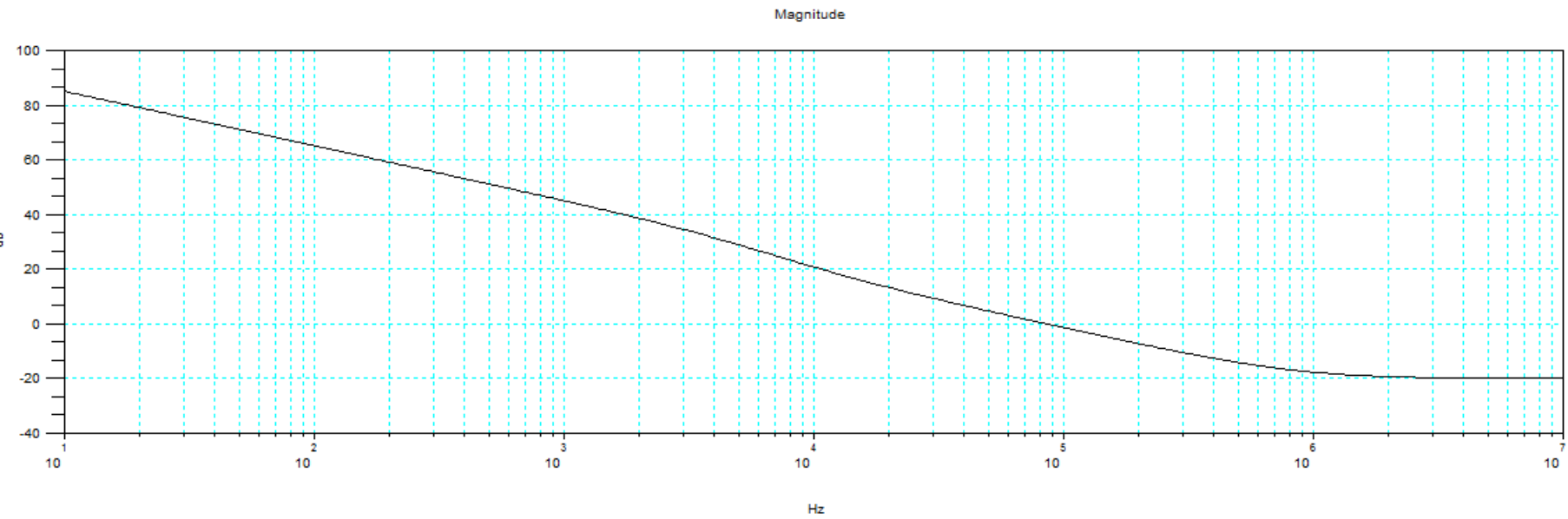Calculated by inputting the transfer function of the data sheet Equation 6.
Vin=12V、Vout=2.5V、Iout=7A、fsw=400kHz
L=1 μH、Cout=94 μF、ESR=2mΩ、R3=3.3kΩ、C7=4700pF



Calculated by inputting the transfer function of the data sheet Equation 6 multiply $H(4) = \exp^{-sT}$ $T=0.7\ \mu s$
Vin=12V、Vout=2.5V、Iout=7A、fsw=400kHz
L=1 μH 、Cout=94 μF 、ESR=2m Ω 、R3=3.3k Ω 、C7=4700pF

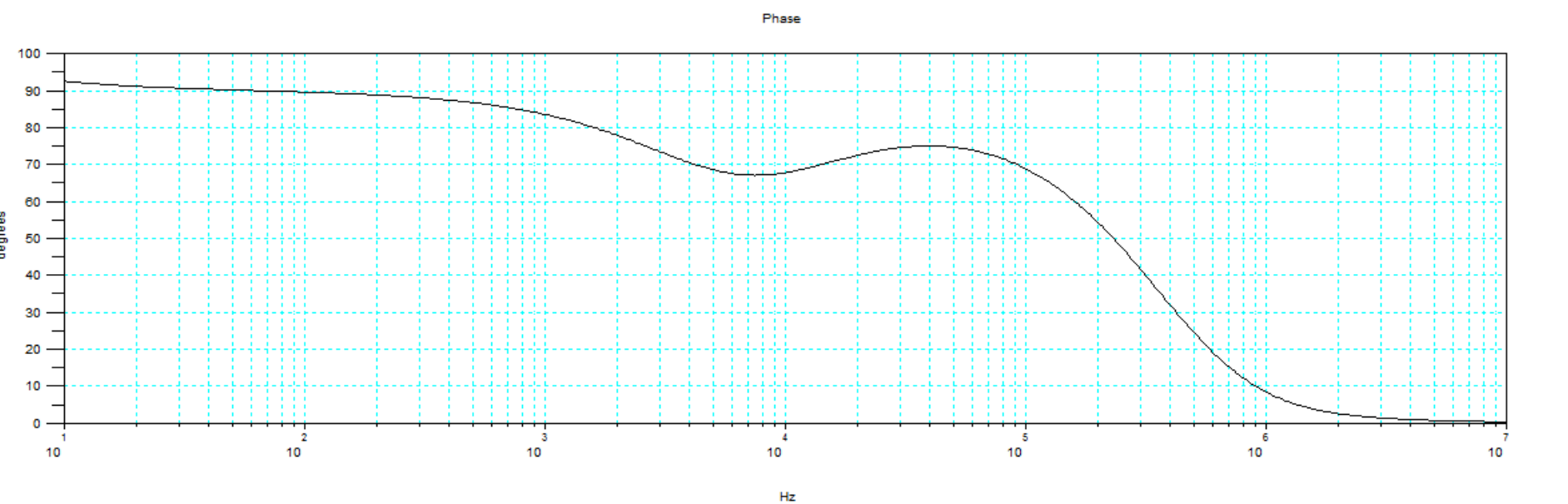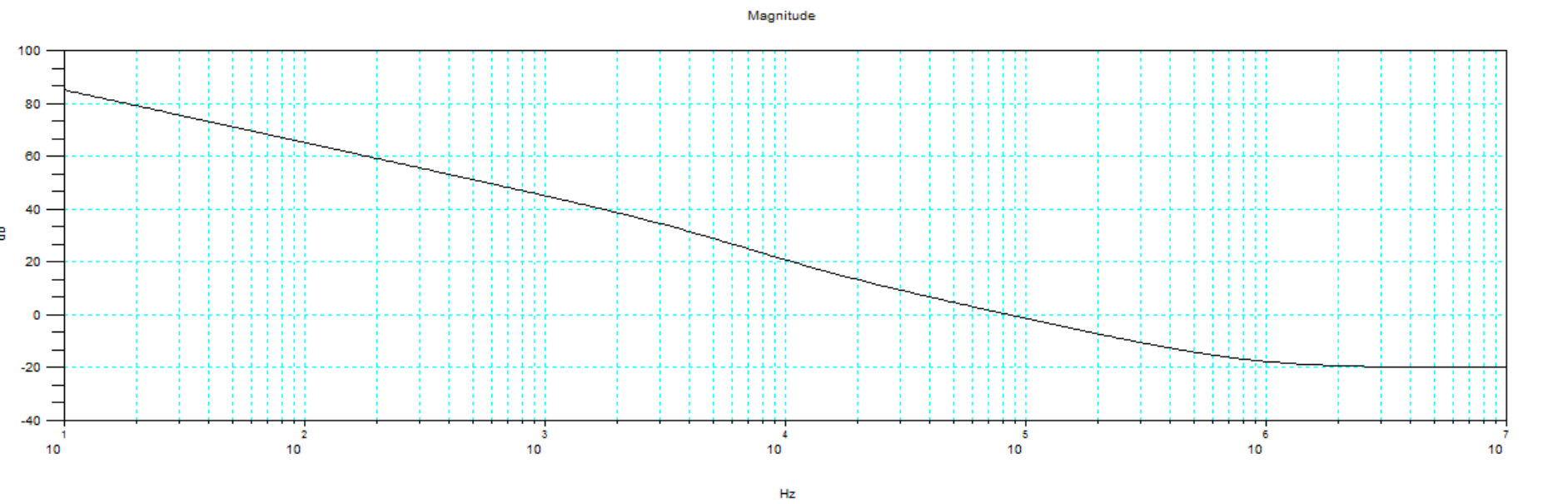

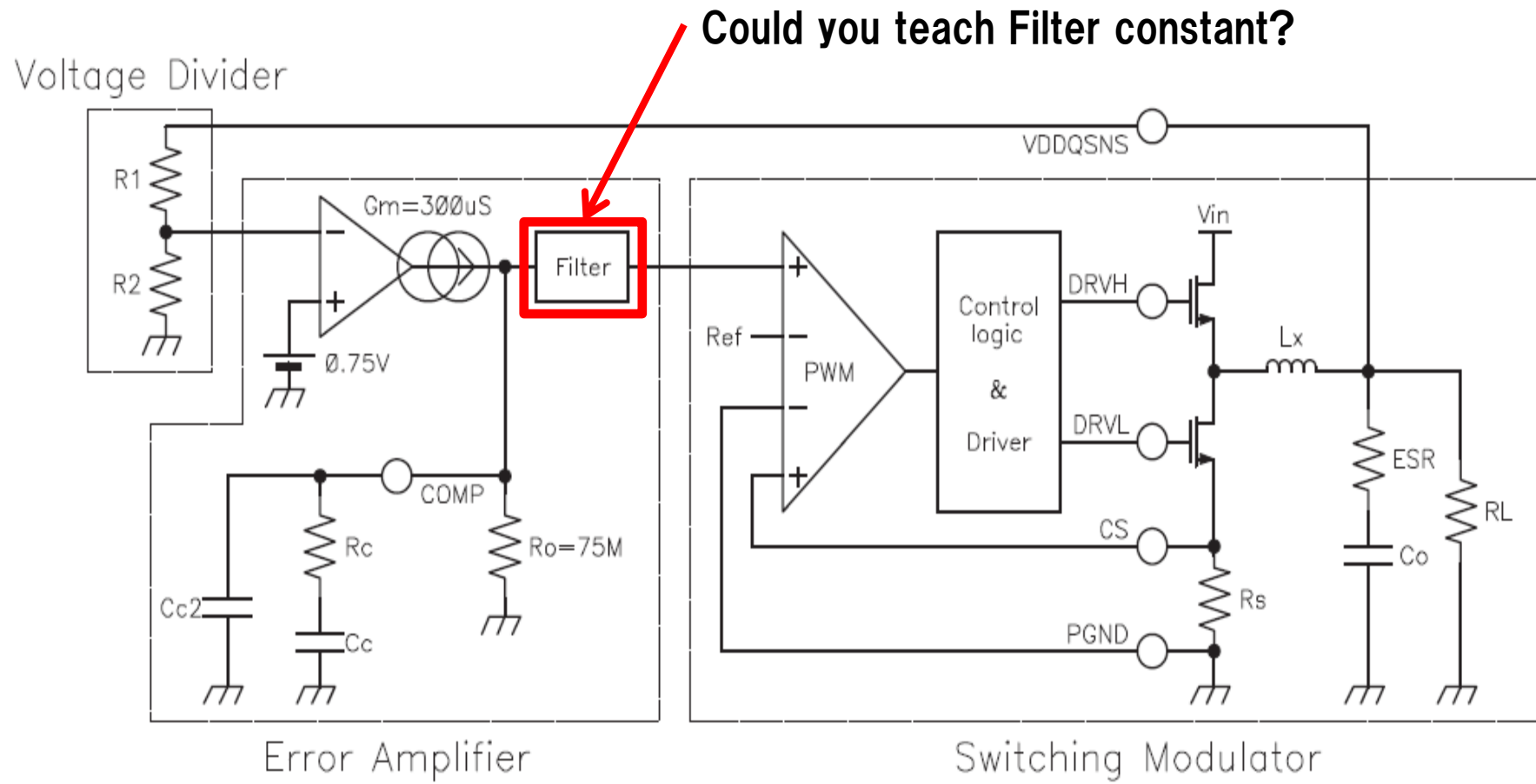


Figure 2. Linearizing the Modulator

Calculated by inputting the transfer function of the data sheet Equation 6 multiply $H4(s) = \exp^{-sT}$ $T=0.7\ \mu s$
multiply $H5(s) = \frac{1}{(Rf \times Cf \times s + 1)}$ Filter $Rf=10k\ \Omega$ 、 $Cf=5pF$
 $Vin=12V$ 、 $Vout=2.5V$ 、 $Iout=7A$ 、 $fsw=400kHz$ 、 $L=1\ \mu H$ 、 $Cout=94\ \mu F$ 、 $ESR=2m\ \Omega$ 、 $R3=3.3k\ \Omega$ 、 $C7=4700pF$

