



SP2T SWITCH WITH IMPEDANCE DETECTION MICRO-USB SWITCH TO SUPPORT USB, UART

This application note describes the operation of TSU6111. This is a differential high performance automated SP2T switch that will automatically detect accessories plugged via the mini/micro USB 5 pin connector. This document contains an application diagram with external critical components as well as PCB routing guidelines.

For detailed pin configuration and register properties, consult the TSU6111 datasheet.

Contents

1	Introduction	. 2
	Micro-USB Switch Flowchart	
	Application Schematic	
	Recommended Operating Conditions	
	PCB Routing Guidelines	
	Accessory ID Table	





Introduction

TSU6111 is a differential high performance automated SP2T switch with Battery Charger Detection BCDv1.1. Each of the dual SP2T switches supports USB 2.0 High Speed. The device features impedance detection of accessories that are attached through DP, DM and ID. Accessory detection includes plug-in/un-plug detection, USB charger detection (BCDv1.1). The switch is controlled automatically via detection logic or manually through I2C. JIG and BOOT pins are available to support USB and UART JIG cable testing during development and manufacturing.

Micro-USB Switch Flowchart

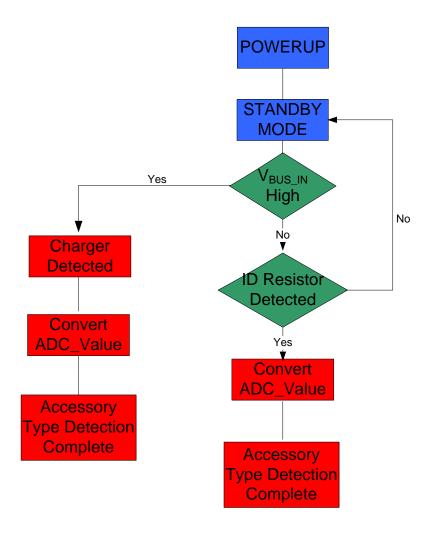


Figure 1: Micro-USB Switch Flow Diagram

www.ti.com

Application Schematic

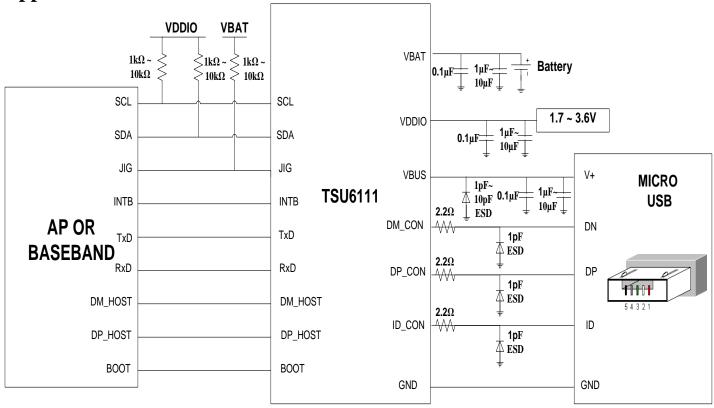


Figure 2: TSU6111 Application Schematic

Table 1: Critical Components

Pin Name	Pin Number	Critical Component		
		1μF~10μF		
V_{BUS_IN}	13	ESD Protection Diode		
		0.1μF		
V	8	1μF~10μF		
$V_{ m DDIO}$	O	0.1μF		
		1μF~10μF		
V_{BAT}	5	Battery		
		0.1μF		
Jig	7	1kΩ		
SCL	10	1kΩ		
SDA	11	1kΩ		
DM_CON	14	2.2Ω		
DM_CON	14	ESD Protection Diode		
DP_CON	15	2.2Ω		
DF_CON	13	ESD Protection Diode		
ID_CON	16	2.2Ω*		
ID_CON	16	ESD Protection Diode		

*Optional Components



Schematic Guidelines

- a) V_{BUS_IN} , V_{DDIO} , & V_{BAT} require $1\mu F\sim 10\mu F$ and $0.1\mu F$ decoupling capacitors to reduce noise from circuit elements. The capacitors act as a shunt to block off the noise. The $0.1\mu F$ capacitor smoothes out high frequencies and has a lower series inductance. The $1\mu F\sim 10\mu F$ capacitor smoothes out the lower frequencies and has a much higher series inductance. Placing both capacitors will provide better load regulation across the frequency spectrum.
- b) JIG is an open-drain output and therefore requires a $1k\Omega \sim 10k\Omega$ pull-up resistor to VBAT
- c) SCL and SDA require $1k\Omega \sim 10k\Omega$ pull-up resistors to VDDIO to prevent floating inputs
- d) V_{BUS_IN} , DM_CON and DP_CON are recommended to have an external resistor 2.2 Ω to provide extra ballasting to protect the chip and internal circuitry
 - a. For ID CON, if there is less stress on the ID pin then the external 2.2Ω resistor is optional
- e) DM_CON, DP_CON, and ID_CON are recommended to have a 1pF external ESD Protection Diode rated for 8kV IEC protection to prevent failure in case of an 8kV IEC contact discharge
- f) V_{BUS_IN} is recommended to have a 1pF ~ 10pF external ESD Protection Diode rated for 8kV IEC protection to prevent failure in case of an 8kV IEC contact discharge

Recommended Operating Conditions

Table 3: Recommended Operating Conditions


Condition	Min	Max	Units
$V_{ m BUS_IN}$	4.5	6.5	V
V_{BAT}	3.5	4.4	V
V_{DDIO}	1.7	3.3	V
Temperature	-40	85	°C


www.ti.com


PCB Routing Guidelines

Routing Guidelines for USB Signal Integrity

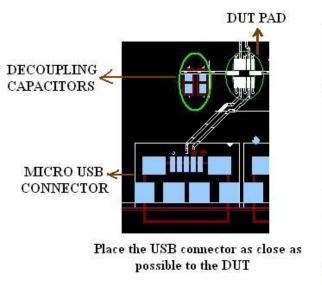- a) All the USB lines DP_CON, DM_CON, DP_HT, DM_HT, TxD & RxD
 - Must have 45Ω single ended characteristic impedance
 - Must have 90Ω differential ended impedance
 - To fulfill USB 2.0 requirements
- b) TSU6111 location
 - a. Close to the USB connector as possible
 - b. The distance between the USB controller and the device less than 1 inch
 - c. Shorter length of the trace will reduce effect of stray noise and radiate less EMI
- c) Minimize use of VIAs for USB related signals
 - a. Differential transmission lines should be matched as close as possible
 - b. No VIAs for optimum USB2.0 performance



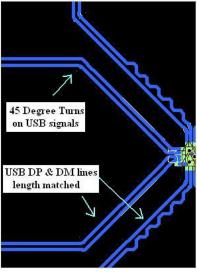

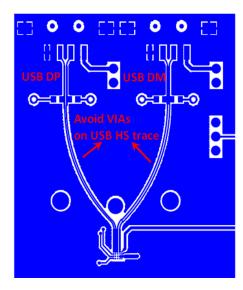





Accessory ID Table

If V_{BUS_IN} is high and the attachment is not a charger, then determine the impedance on the ID pin. If V_{BUS_IN} is low and an accessory is attached, then use an ADC for impedance sensing on the ID pin to identify which accessory is attached.

IMPEDANCE BUCKETS FOR EACH ACCESSORY

In order to implement ID detection, each accessory should contain below ID impedance resistor value which is 5% tolerance accuracy.

Table 2: Accessory ID Table

Accessory ID & Switch States							
	Detected Impedance on ID	Resistor Tolerance (%)		Switch	State	Factory	/ Cable
Accessory			ADC Value	DP/DM		IIC	воот
				USB	UART	JIG	ВООТ
OTG	0	-	00000	ON	OFF	OFF	OFF
Reserved Accessory #1	34K	5%	01111	OFF	OFF	OFF	OFF
Reserved Accessory #2	40.2K	5%	10000	OFF	OFF	OFF	OFF
Reserved Accessory #3	49.9K	5%	10001	OFF	OFF	OFF	OFF
Reserved Accessory #4	64.9K	5%	10010	OFF	OFF	OFF	OFF
Phone Powered Device	102K	5%	10100	OFF	ON	OFF	OFF
UART Cable	150K	5%	10110	OFF	ON	OFF	OFF
Factory Mode Cable - Boot Off USB	255K	5%	11000	ON	OFF	ON	OFF
Factory Mode Cable - Boot On USB	301K	5%	11001	ON	OFF	ON	ON
Factory Mode Cable - Boot Off UART	523K	5%	11100	OFF	ON	ON	OFF
Factory Mode Cable - Boot On UART	619K	5%	11101	OFF	ON	ON	ON
No ID	-	-	11111	OFF	OFF	OFF	OFF
USB Standard Downstream Port	-	-	11111	ON	OFF	OFF	OFF
USB Charging Downstream Port	-	-	11111	ON	OFF	OFF	OFF
Dedicated Charging Port	-	-	11111	OFF	OFF	OFF	OFF



www.ti.com

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2007, Texas Instruments Incorporated