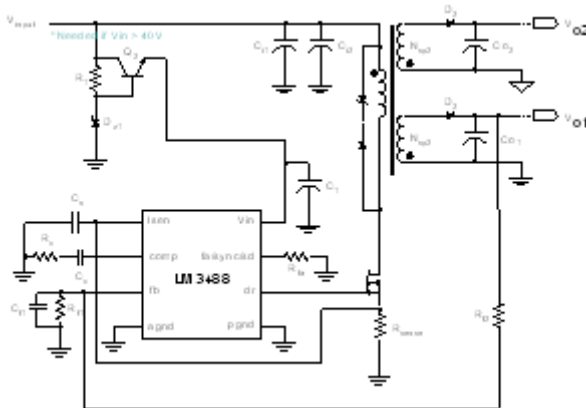




SWITCHING POWER SUPPLY DESIGN: CONTINUOUS MODE FLYBACK CONVERTER

Written by Michele Sclocchi
michele.sclocchi@nsc.com
Application Engineer
National Semiconductor

Typical Flyback power supply:



Notes:

Write down the power supply requirements on :

$X_{xx} :=$

Get the results on:

Results_{xx} :=

This Mathcad file helps the calculation of the external components of a typical continuous mode switching power supply.

Input voltage:

- Minimum input voltage: $V_{i_{min}} := 90 \cdot \text{volt}$ $\mu\text{sec} := 10^{-6} \cdot \text{sec}$

- Maximum input voltage: $V_{i_{max}} := 460 \cdot \text{volt}$

- Nominal input voltage: $V_{i_{nom}} := 300 \cdot \text{volt}$

Output:

- Nominal output voltage, maximum output ripple, minimum output current, maximum output current

$V_{o1} := 108 \cdot \text{volt}$ $V_{rp1} := 1000 \cdot \text{mV}$ $I_{o1_{min}} := 0.1 \cdot \text{amp}$ $I_{o1_{max}} := 1 \cdot \text{amp}$

$V_{o2} := 0 \cdot \text{volt}$ $V_{rp2} := 120 \cdot \text{mV}$ $I_{o2_{min}} := 0.000 \cdot \text{amp}$ $I_{o2_{max}} := 0.000 \cdot \text{amp}$

$V_{d_{fw}} := 0.7 \cdot \text{volt}$ (diode's forward drop voltage)

$$P_{o_{min}} := (V_{o1} + V_{d_{fw}}) \cdot I_{o1_{min}} + (V_{o2} + V_{d_{fw}}) \cdot I_{o2_{min}}$$

$$P_{o_{max}} := (V_{o1} + V_{d_{fw}}) \cdot I_{o1_{max}} + (V_{o2} + V_{d_{fw}}) \cdot I_{o2_{max}}$$

$$P_{o_{min}} = 10.87 \cdot \text{watt}$$

$$P_{o_{max}} = 108.7 \cdot \text{watt}$$

- **Switching Frequency:** $f_{sw} := 100 \cdot \text{kHz}$ $T := \frac{1}{f_{sw}}$ $T = 10 \cdot \mu\text{sec}$

- **Transformer's Efficiency:** $\eta := 0.90$ (Guessed value)

- **Maximum drop voltage across the switching mosfet during the on time:**

- **On resistance of the Mosfet:** $R_{ds_{on}} := 0.180 \cdot \text{ohm}$

$$V_{ds_{on}} := \frac{P_{o_{max}}}{\eta \cdot V_{i_{min}}} \cdot R_{ds_{on}} \quad V_{ds_{on}} = 0.24 \cdot \text{volt}$$

1) Define Primary/secondary turns ratio: Nps1

Primary/secondary turns ratio can be selected as compromise between maximum voltage across the switching mosfet and desired max.-min. duty cycle.

- **Nominal desired on Duty Cycle:** $D_{nom} := 0.24$

$$N_{ps1} := \left(\frac{V_{i_{nom}} - V_{ds_{on}}}{V_{o1} + V_{d_{fw}}} \right) \cdot \frac{D_{nom}}{1 - D_{nom}} \quad N_{ps1} = 0.9$$

The calculated turns ratio can be modified to optimise the windings

- **Flyback voltage across the mutual inductance during the off time: Vfm**

$$V_{fm} := N_{ps1} \cdot (V_{o1} + V_{d_{fw}}) \quad V_{fm} = 94.66 \cdot \text{volt}$$

- **Maximum voltage across the switching-mosfet:**

$$F_{spike} := 0.15$$

$$V_{ds_{max}} := (F_{spike} + 1) \cdot (V_{i_{max}} + V_{fm}) \quad V_{ds_{max}} = 637.86 \cdot \text{volt}$$

Safe factor (assume spikes of 20-30% of Vdc)

To reduce the maximum voltage across the switching mosfet reduce Nps turns ratio by reducing the desired on-duty cycle

- **Slave output turns ratio:** $N_{ps2} := \frac{V_{fm}}{V_{o2} + V_{d_{fw}}} \quad N_{ps2} = 135.2$

2) Maximum and minimum duty cycle : Dmax and Dmin

To maintain the continuous mode of operation the dead time has to be equal zero ($T_{on} + T_{off} = T$), and to reset the core every cycle, the average voltage on the primary inductance must be equal zero: $(V_i - V_{ds}) \cdot T_{on} = (V_o + V_d) \cdot N_{ps} \cdot T_{off}$, where T_{off} is equal to $(T - T_{on})$

$$T_{on_{max}} := \frac{V_{fm} \cdot T}{(V_{i_{min}} - V_{ds_{on}}) + V_{fm}} \quad T_{on_{max}} = 5.13 \cdot \mu\text{sec}$$

$$T_{on_{min}} := \frac{V_{fm} \cdot T}{(V_{i_{max}} - V_{ds_{on}}) + V_{fm}} \quad T_{on_{min}} = 1.71 \cdot \mu\text{sec}$$

$$D_{\max} := \frac{T_{\text{on}_{\max}}}{T}$$

Maximum duty cycle

$$D_{\max} = 0.51$$


$$D_{\min} := \frac{T_{\text{on}_{\min}}}{T}$$

Minimum duty cycle

$$D_{\min} = 0.17$$

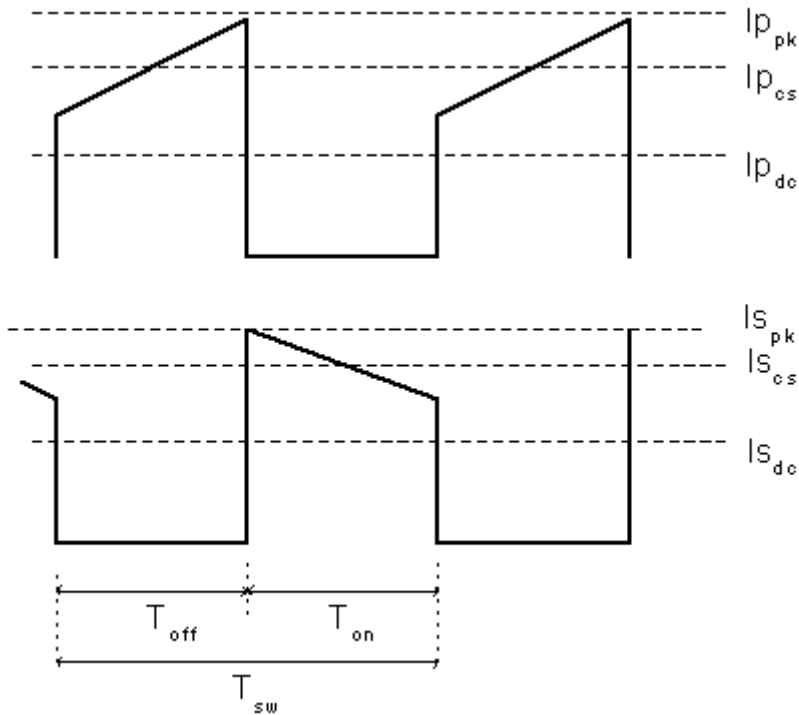3) Primary winding: Inductance, peak, AC, RMS current

In continuous mode the duty cycle changes with a change of input voltage. An increase of output current, will temporary increase the duty cycle until the average primary and secondary currents increase.



- Primary average current:

$$I_{p_{cs}} := \frac{P_{o_{\max}}}{(V_{i_{\min}} - V_{ds_{on}}) \cdot \eta \cdot D_{\max}}$$

$$I_{p_{cs}} = 2.62 \cdot \text{amp}$$

There are several criterias to select the primary and secondary inductances, following are explained two different solutions: the first one is to select the primary inductance in order to insure continuous mode of operation from full load to minimum load. (about 1/10-1/20 of the maximum load). **(3-a)**, The second alternative criteria, is to calculate primary and secondary inductances by defining maximum secondary ripple current. **(3-b)**

3-a) Select primary inductance for continuous mode of operation at minimum load:

During the transition from discontinuous to continuous mode, the peak primary current it's about double the central average current $I_{p_{cs}(\min)}$. In order to maintain continuous mode at minimum load the maximum ramp amplitude has to be twice the minimum average current.

- Ramp amplitude:

$$\Delta I_{p_a} := \frac{2 \cdot P_{o_{\min}}}{(V_{i_{\min}} - V_{ds_{on}}) \cdot \eta \cdot D_{\max}}$$

$$\Delta I_{p_a} = 0.52 \cdot \text{amp}$$

- Primary inductance: $\Delta I_p = (V_i - V_{ds}) \cdot T_{on} / L_p$

$$L_{p_a} := \frac{(V_{i_{min}} - V_{ds_{on}}) \cdot T_{on_{max}}}{\Delta I_{p_a}}$$

$$L_{p_a} = 878.74 \cdot \mu H$$

3-b) Primary and secondary inductance for a maximum defined secondary peak to peak ripple current:

AC core losses, AC winding losses, and output ripple current are directly proportional to the current ramp amplitude of the primary and secondaries windings. Therefore in high current application, AC ripple currents could have a predominant role on the overall performance of the converter, a good compromise between transformer's size and AC currents can be obtained by selecting the most appropriate secondary ripple current:

- Desired secondary ripple current:

$$\Delta I_{s\%} := 23\% \quad (\text{maximum value / average})$$

$$I_{s1_{cs}} := \frac{I_{o1_{max}}}{(1 - D_{max})}$$

$$I_{s1_{cs}} = 2.05 \cdot \text{amp}$$

- Ramp amplitude:

$$\Delta I_{s1_b} := I_{s1_{cs}} \cdot \Delta I_{s\%}$$

$$\Delta I_{s1_b} = 0.47 \cdot \text{amp}$$

- Secondary inductance :

$$L_{s1_b} := \frac{(V_{o1} + V_{d_{fw}}) \cdot (T - T_{on_{max}})}{\Delta I_{s1_b}}$$

$$L_{s1_b} = 1.12 \times 10^3 \cdot \mu H$$

- Primary inductance:

$$L_{p_b} := L_{s1_b} \cdot N_{ps1}^2$$

$$L_{p_b} = 849.02 \cdot \mu H$$

- Ramp amplitude:

$$\Delta I_{p_b} := \frac{(V_{i_{min}} - V_{ds_{on}}) \cdot T_{on_{max}}}{L_{p_b}}$$

$$\Delta I_{p_b} = 0.54 \cdot \text{amp}$$

Select primary inductance (3-a) or (3-b):---->

$$L_p := L_{p_b}$$

$$L_p = 849.02 \cdot \mu H$$

$$\Delta I_p := \frac{(V_{i_{min}} - V_{ds_{on}}) \cdot T_{on_{max}}}{L_p}$$

$$\Delta I_p = 0.54 \cdot \text{amp}$$

- Primary average current:

$$I_{p_{cs}} := \frac{P_{o_{max}}}{(V_{i_{min}} - V_{ds_{on}}) \cdot \eta \cdot D_{max}}$$

$$I_{p_{cs}} = 2.62 \cdot \text{amp}$$

- Primary peak current:

$$I_{p_{pk}} := I_{p_{cs}} + \frac{\Delta I_p}{2}$$

$$I_{p_{pk}} = 2.89 \cdot \text{amp}$$

- Primary RMS current:

$$I_{p_{rms}} := \sqrt{D_{max} \cdot \left[I_{p_{pk}} \cdot \left(I_{p_{cs}} - \frac{\Delta I_p}{2} \right) + \frac{1}{3} \cdot \left[I_{p_{pk}} - \left(I_{p_{cs}} - \frac{\Delta I_p}{2} \right) \right]^2 \right]}$$

$$I_{p_{rms}} = 1.88 \cdot \text{amp}$$

- Primary DC current: $I_{p_{dc}} := \frac{P_{o_{max}}}{\eta \cdot (V_{i_{min}} - V_{d_{s_{on}}})}$ $I_{p_{dc}} = 1.35 \cdot \text{amp}$

- Primary AC(rms) current: $I_{p_{ac}} := \sqrt{I_{p_{rms}}^2 - I_{p_{dc}}^2}$ $I_{p_{ac}} = 1.32 \cdot \text{amp}$

$E_{dt} := V_{i_{min}} \cdot T_{on_{max}}$ $E_{dt} = 4.62 \times 10^{-4} \cdot \text{volt} \cdot \text{sec}$

4) Secondary winding: Inductance, peak, AC, RMS current

-Master output:

- Primary average current: $I_{s1_{cs}} := \frac{I_{o1_{max}}}{(1 - D_{max})}$ $I_{s1_{cs}} = 2.05 \cdot \text{amp}$

- Secondary inductance : $L_{s1} := \frac{L_p}{N_{ps1}^2}$ $L_{s1} = 1.12 \times 10^3 \cdot \mu\text{H}$

- Ramp amplitude: $\Delta I_{s1} := \frac{(V_{o1} + V_{d_{fw}}) \cdot (T - T_{on_{max}})}{L_{s1}}$ $\Delta I_{s1} = 0.47 \cdot \text{amp}$

- Secondary peak current: $I_{s1_{pk}} := I_{s1_{cs}} + \frac{\Delta I_{s1}}{2}$ $I_{s1_{pk}} = 2.29 \cdot \text{amp}$

- Secondary RMS current:

$$I_{s1_{rms}} := \sqrt{(1 - D_{max}) \cdot \left[I_{s1_{pk}} \cdot \left(I_{s1_{cs}} - \frac{\Delta I_{s1}}{2} \right) + \frac{1}{3} \cdot \left[I_{s1_{pk}} - \left(I_{s1_{cs}} - \frac{\Delta I_{s1}}{2} \right) \right]^2 \right]}$$

$I_{s1_{rms}} = 1.44 \cdot \text{amp}$

- Secondary AC current: $I_{s1_{ac}} := \sqrt{I_{s1_{rms}}^2 - I_{o1_{max}}^2}$ $I_{s1_{ac}} = 1.03 \cdot \text{amp}$

-First slave output:

- Primary average current: $I_{s2_{cs}} := \frac{I_{o2_{max}}}{(1 - D_{max})}$ $I_{s2_{cs}} = 0 \cdot \text{amp}$

- Secondary inductance : $L_{s2} := \frac{L_p}{N_{ps2}^2}$ $L_{s2} = 0.05 \cdot \mu\text{H}$

- Ramp amplitude: $\Delta I_{s2} := \frac{(V_{o2} + V_{d_{fw}}) \cdot (T - T_{on_{max}})}{L_{s2}}$ $\Delta I_{s2} = 73.38 \cdot \text{amp}$

- Secondary peak current: $I_{s2_{pk}} := I_{s2_{cs}} + \frac{\Delta I_{s2}}{2}$ $I_{s2_{pk}} = 36.69 \cdot \text{amp}$

- Secondary RMS current:

$$I_{s2_{rms}} := \sqrt{(1 - D_{max}) \cdot \left[I_{s2_{pk}} \cdot \left(I_{s2_{cs}} - \frac{\Delta I_{s2}}{2} \right) + \frac{1}{3} \cdot \left[I_{s2_{pk}} - \left(I_{s2_{cs}} - \frac{\Delta I_{s2}}{2} \right) \right]^2 \right]}$$

$$I_{s2_{rms}} = 14.78 \cdot \text{amp}$$

- **Secondary AC current:** $I_{s2_{ac}} := \sqrt{I_{s2_{rms}}^2 - I_{o2_{max}}^2}$

$$I_{s2_{ac}} = 14.78 \cdot \text{amp}$$

5) Maximum Stress across the output diodes: Vdiode

-**Maximum stress voltage on the cathode of diodes**

$$V_{diode1_{max}} := \frac{V_{i_{max}}}{N_{ps1}} + V_{o1} \quad V_{diode1_{max}} = 636.22 \cdot \text{volt}$$

$$V_{diode2_{max}} := \frac{V_{i_{max}}}{N_{ps2}} + V_{o2} \quad V_{diode2_{max}} = 3.4 \cdot \text{volt}$$

Select a diode with $V_{a-c} \gg V_{diode_{max}}$, and ultra-fast switching diode

$$P_{diode1_{max}} := I_{s1_{rms}} \cdot V_{d_{fw}} \cdot (1 - D_{max}) \quad P_{diode1_{max}} = 0.49 \cdot \text{watt}$$

$$P_{diode2_{max}} := I_{s2_{rms}} \cdot V_{d_{fw}} \cdot (1 - D_{max}) \quad P_{diode2_{max}} = 5.04 \cdot \text{watt}$$

$$P_{diode_{tot}} := P_{diode1_{max}} + P_{diode2_{max}} \quad P_{diode_{tot}} = 5.52 \cdot \text{watt}$$

6) Output ripple Specifications and Output Capacitors

To meet the output ripple specifications the output capacitors have to meet two criterias:

- satisfy the standard capacitance definition: $I = C \cdot dV/dt$ where t is the Toff time, V is 25% of the allowable output ripple.
- The Equivalent Series Resistance (ESR) of the capacitor has to provide less than 75% of the maximum output ripple. ($V_{ripple} = dI \cdot ESR$)

-**Maximum outputs ripple:** $V_{rp1} = 1 \times 10^3 \cdot \text{mV}$ $V_{rp2} = 120 \cdot \text{mV}$

-**Minimum output capacitance:** $C_{o1} := \Delta I_{s1} \cdot \frac{(T_{on_{max}})}{V_{rp1} \cdot 0.25}$ $C_{o1} = 9.7 \cdot \mu\text{F}$

-**Maximum ESR value:** $ESR1 := \frac{V_{rp1} \cdot 0.75}{\Delta I_{s1}}$ $ESR1 = 1.59 \cdot \text{ohm}$

-**Minimum output capacitance:** $C_{o2} := \Delta I_{s2} \cdot \frac{(T_{on_{max}})}{V_{rp2} \cdot 0.25}$ $C_{o2} = 1.26 \times 10^4 \cdot \mu\text{F}$

-**Maximum ESR value:** $ESR2 := \frac{0.75 \cdot V_{rp2}}{\Delta I_{s2}}$ $ESR2 = 1.23 \times 10^{-3} \cdot \text{ohm}$

7) Input capacitor:

The input capacitor has to meet the maximum ripple current rating $I_p(\text{rms})$ and the maximum input voltage ripple ESR value.

8) Switching Mosfet: Power Dissipation

The Mosfet is chosen based on maximum Stress voltage (section1), maximum peak input current

(section 3), total power losses, maximum allowed operating temperature, and driver capability of the LM3488.

-The drain to source Breakdown of the mosfet (V_{dss}) has to be greater than: $V_{ds_{max}} = 637.86 \cdot \text{volt}$

-Continuous Drain current of the mosfet (I_d) has to be greater than: $I_{pk} = 2.89 \cdot \text{amp}$

- Maximum drive voltage:

The voltage on the drive pin of the LM3488, V_{dr} is equal to the input voltage when input voltage is less than 7.2V, and V_{dr} is equal to 7.2V when the input voltage is greater than 7.2V

$$V_{dr} := 7.2 \cdot \text{volt}$$

$$R_{dr_{on}} := 7 \cdot \text{ohm}$$

-Total Mosfet's losses and maximum junction temperature:

The goal in selecting a Mosfet is to minimize junction temperature rise by minimizing the power loss while being cost effective. Besides maximum voltage rating, and maximum current rating, the others three important parameters of a Mosfet are $R_{ds(on)}$, gate threshold voltage, and gate capacitance. The switching Mosfet has three types of losses, conduction loss and switching loss, and gate charge losses:

-**Conduction losses** are equal to: $I^2 \cdot R$ losses, therefore the total resistance between the source and drain during the on state, $R_{ds(on)}$ has to be as low as possible.

-**Switching losses** are equal to: $\text{Switching-time} \cdot V_{ds} \cdot I \cdot \text{frequency}$. The switching time, rise time and fall time is a function of the gate to drain Miller-charge of the Mosfet, Q_{gd} , the internal resistance of the driver and the Threshold Voltage, $V_{gs(th)}$ the minimum gate voltage which enables the current through drain source of the Mosfet.

-**Gate charge losses** are caused by charging up the gate capacitance and then dumping the charge to ground every cycle. The gate charge losses are equal to: $\text{frequency} \cdot Q_{g(tot)} \cdot V_{dr}$

Unfortunately, the lowest on resistance devices tend to have higher gate capacitance. Because this loss is frequency dependent, in very high current supplies with very large FETs, with large gate capacitance, a more optimal design may result from reducing operating frequency.

Switching losses are also effected by gate capacitance. If the gate driver has to charge a larger capacitance, then the time the Mosfet spends in the linear region increases and the losses increase. The faster the rise time, the lower the switching loss. Unfortunately this causes high frequency noise.

Mosfet: _____

$$n := 10^{-9}$$

$R_{ds_{on}} := 0.200 \cdot \text{ohm}$ (Total resistance between the source and drain during the on state)

$C_{oss} := 95 \cdot \text{pF}$ (Output capacitance)

$Q_{g_{tot}} := 13 \cdot n \cdot \text{coul}$ (Total gate charge)

$Q_{gd_{miller}} := 6.1 \cdot n \cdot \text{coul}$ (Gate drain Miller charge)

$V_{gs_{th}} := 2 \cdot \text{volt}$ (Threshold voltage)

- Conduction losses: P_{cond}

$$P_{cond} := R_{ds_{on}} \cdot I_{prms}^2 \cdot D_{max} \quad P_{cond} = 0.36 \cdot \text{watt}$$

- Switching losses: $P_{sw(max)}$

Turn On time:

$$t_{sw} := Q_{gd_{miller}} \cdot \frac{R_{dr_{on}}}{V_{dr} - V_{gs_{th}}} \quad t_{sw} = 8.21 \times 10^{-9} \text{ s}$$

$$P_{sw_{max}} := (t_{sw} \cdot V_{ds_{max}} \cdot I_{pk} \cdot f_{sw}) + \frac{C_{oss} \cdot V_{ds_{max}}^2 \cdot f_{sw}}{2} \quad P_{sw_{max}} = 3.45 \cdot \text{watt}$$

- Gate charge losses: P_{gate}

Average current required to drive the gate capacitor of the Mosfet:

$$I_{gate_avg} := f_{sw} \cdot Q_{g_{tot}} \qquad I_{gate_avg} = 1.3 \times 10^{-3} \cdot \text{amp}$$

$$P_{gate} := I_{gate_avg} \cdot V_{dr} \qquad P_{gate} = 9.36 \times 10^{-3} \cdot \text{watt}$$

-Total losses: P_{tot(max)}

$$P_{mosfet_{tot}} := P_{cond} + P_{sw_{max}} + P_{gate} \qquad P_{mosfet_{tot}} = 3.82 \cdot \text{watt}$$

-Maximum junction temperature and heat sink requirement:

Maximum junction temperature desired: $T_{j_{max}} := 140$ Celsius


Maximum ambient temperature: $T_{a_{max}} := 70$ Celsius

-Thermal resistance junction to ambient temperature:

$$\theta_{ja} := \frac{T_{j_{max}} - T_{a_{max}}}{P_{mosfet_{tot}}} \qquad \theta_{ja} = 18.32 \cdot \frac{1}{\text{watt}} \text{ Celsius}$$

If the thermal resistance calculated is lower than that one specified on the Mosfet's data sheet a heat sink or higher copper area is needed.

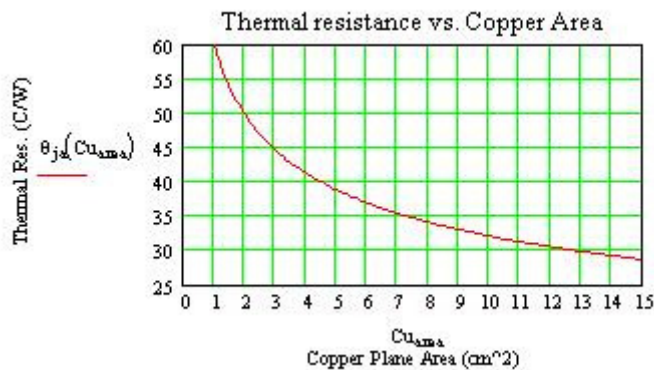For Example for a T0-263 (D2pak) package the T_{ja} of the Mosfet versus copper plane area is:



10) Current limit:

The LM3488 uses a current mode control scheme. The main advantages of current mode control are inherent cycle-by-cycle current limit for the switch, and simple control loop characteristics.

Since the LM3488 has a maximum duty cycle of 100%, the current limit should be designed to have current limit just above the maximum primary peak current plus 20-30%


$$R_{sense} := \frac{160 \cdot \text{mV}}{I_{p_{pk}} \cdot 1.2} \qquad R_{sense} = 0.05 \cdot \Omega$$

11) Transformer Design:

The inductor- transformer should be designed to minimize the leakage inductance, ac winding losses, and core losses.

In continuous mode of operation, the total amper-turns never goes to zero, therefore the transformer will have lower core losses, and high AC winding losses.

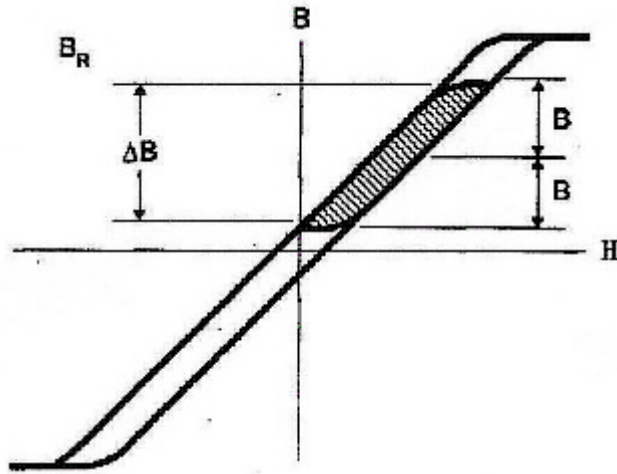Unipolar pulses cause dc current to flow through the core winding, moving the flux in the core from Br towards saturation. When pulses goes to zero, the flux travels back to Br. The transformer in Flyback power supply acts as an energy storage device, therefore to do not saturate is used a air-gapped ferrite core or Molypermalloy Powder cores with distributed air-gap.



The power handling capacity of the transformer core can be determined by its $WaAc$ product area, where Wa is the available core window area, and Ac is the effective core cross-sectional area. The $WaAc$ power output relationship is obtained with the Faraday's law:

$$E = 4 B A_c N f 10^{-8}$$

Where:

E = applied voltage

J = current density amp/cm²

B = flux density in gauss

K = winding factor

A_c = core area in cm²

I = current (rms)

N = number of turns

P_o = output power

f = frequency

Wa = window area in cm²

-Select maximum current density of the windings:C (280- 390 amp/cm², or 400-500 circular-mils/amp)

$$J := 390 \cdot \frac{\text{amp}}{\text{cm}^2}$$

$$\text{cir_mil} := 5.07 \cdot 10^{-6} \cdot \text{cm}^2$$

$$\frac{1}{J} = 505.74 \cdot \frac{\text{cir_mil}}{\text{amp}}$$

- winding factor: $K_w := 0.2$ (0.2-0.3 for flyback continuous mode)

-Select core material and maximum flux density:

It is assumed that at high switching frequency ($f_{sw} \gg 25\text{kHz}$) the limitation factor is the core losses, and temperature rise of the transformer

The type of ferrite material chosen will influence the core losses at the given operating conditions:

- F material has its lowest losses at room temperature to 40°C.
- P material has lowest losses at 70°C-80°C.
- R material has lowest losses at 100°C-110°C.
- K material has lowest losses at 40°C-60°C at elevated frequencies.

At high switching frequency it is necessary to adjust the flux density in order to limit core temperature rise: limiting core losses density to 100mW/cm³ would keep the temperature rise at approximately 40°C.

Use the following formula to select the most appropriate maximum flux density:

-Maximum core losses density: $P_{cored} := 250 \text{ mW/cm}^3$

for P material:

$a = 0.158$ $b = 1.36$ $c = 2.86$ for frequency $f < 100\text{kHz}$
 $a = 0.0434$ $b = 1.63$ $c = 2.62$ for frequency $100\text{kHz} < f < 500\text{kHz}$
 $a = 7.36 \cdot 10^{-7}$ $b = 3.47$ $c = 2.54$ for frequency $f > 500\text{kHz}$

for K material:

$a = 0.0530$ $b = 1.60$ $c = 3.15$ for frequency $f < 500\text{kHz}$
 $a = 0.00113$ $b = 2.19$ $c = 3.10$ for frequency $500\text{kHz} < f < 1 \text{ MHz}$
 $a = 1.77 \cdot 10^{-9}$ $b = 4.13$ $c = 2.98$ for frequency $f > 1\text{MHz}$

$$a1 := 0.0434$$

$$b1 := 1.63$$

$$c1 := 2.62$$

$$B := \left[\frac{P_{\text{cored}}}{a_1 \cdot \left(\frac{f_{\text{sw}}}{\text{kHz}} \right)^{b_1}} \right]^{\frac{1}{c_1}} \cdot 10^3 \cdot \text{gauss} \quad B = 1.55 \times 10^3 \cdot \text{gauss}$$

$$B = 1.55 \times 10^3 \cdot \text{gauss} \quad \implies \quad \Delta B := B \cdot 2 \quad \Delta B = 3.1 \times 10^3 \cdot \text{gauss}$$

-Topology constant: $K_t := \frac{0.00025}{1.97} \cdot 10^3$

$$W_a A_c := \frac{P_{o_{\text{max}}}}{K_t \cdot \Delta B \cdot f_{\text{sw}} \cdot J}$$

$$W_a A_c = 0.71 \cdot \text{cm}^4$$

- Select a core with Area Product larger than : --->

$$W_a A_c = 0.71 \cdot \text{cm}^4$$

Core selected:

- Manufacture: EPCOS
- Material: N87
- Shape: ETD core
- Part number: ETD34
- Core Area: Ae
- Bobbin area: Wa
- Core volume: Ve
- Window length lw
- Area product: Used ----->
- Inductance per 1000 turns without airgap :
- first length of turn:

$$A_e := 0.97 \cdot \text{cm}^2$$


$$W_a := 1.22 \cdot \text{cm}^2$$

$$l_w := 2.09 \cdot \text{cm}$$

$$V_e := 7.63 \cdot \text{cm}^3$$

$$A_e \cdot W_a = 1.18 \cdot \text{cm}^4$$

$$L_t := 6.05 \cdot \text{cm}$$

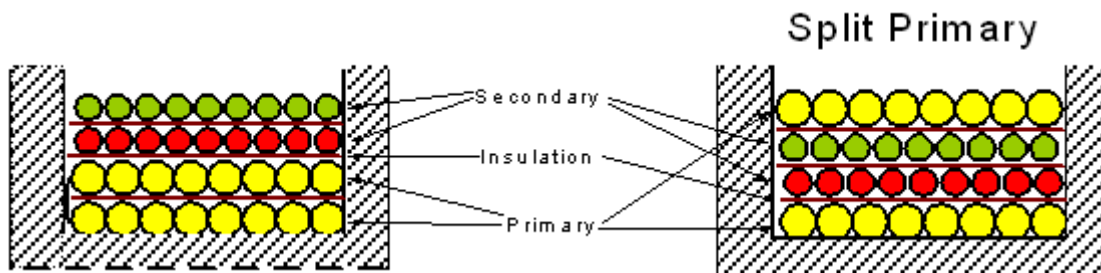

- Primary inductance: Primary turns

$$N_{p_c} := \frac{L_p \cdot I_{p_{pk}}}{\Delta B \cdot A_e}$$

$$N_{p_c} = 81.55$$

The number of turns has to be rounded to the higher or lower integer value: $N_p := 82$

$$\frac{N_p \cdot A_e \cdot \Delta B}{I_{p_{pk}}} = 853.7 \cdot \mu\text{H}$$

- Secondary inductance: Secondary turns

$$N_{s1_c} := \left(\frac{N_p}{N_{ps1}} \right)$$

$$N_{s1_c} = 94.16$$

$$N_{s1} := 94$$

$$Ns2_c := \left(\frac{Np}{Nps2} \right)$$

$$Ns2_c = 0.61$$

$$Ns2 := 0$$

-Air-gap length

The air-gap length is proportional to the effective gap section area (A_g).
 A_g is equal to the core section times the finging coefficient, that take in consideration the finging flux in the air-gap. Since A_g depends on the air-gap length itself, the air-gap length (L_g) can be calculated with few iterations of a loop cycle.

$$\mu_o := 4 \cdot \pi \cdot 10^{-7} \cdot \frac{\text{henry}}{\text{m}}$$

$$L_g := \left| \begin{array}{l} A_g \leftarrow \frac{A_e}{\text{cm}^2} \\ \text{for } i \in 0..4 \\ \quad \left| \begin{array}{l} l_{\text{gap}} \leftarrow \mu_o \cdot \frac{\text{cm}}{\text{henry}} \cdot Np^2 \cdot \left(\frac{A_g}{\frac{L_p}{\text{henry}}} \right) \\ A_g \leftarrow \frac{A_e}{\text{cm}^2} \cdot \left(1 + \frac{l_{\text{gap}}}{\sqrt{\frac{A_e}{\text{cm}^2}}} \cdot \log \left(\frac{2 \cdot \frac{l_w}{\text{cm}}}{l_{\text{gap}}} \right) \right) \end{array} \right. \\ (l_{\text{gap}}) \cdot \text{cm} \end{array} \right.$$

$$L_g = 1.14 \cdot \text{mm}$$

(Air-gap length)

$$L_g = 0.04 \cdot \text{in}$$

- Primary and secondary wire size:

Maximum current density: $J = 390 \cdot \frac{\text{amp}}{\text{cm}^2}$

Primary rms current: $I_{p_{\text{rms}}} = 1.88 \cdot \text{amp}$

Primary:

by wire area: $W_{p_{\text{cu}}} := \frac{I_{p_{\text{rms}}}}{J}$ $W_{p_{\text{cu}}} = 4.82 \cdot 10^{-3} \cdot \text{cm}^2$

or by wire size: $AWG_p := -4.2 \cdot \ln \left(\frac{W_{p_{\text{cu}}}}{\text{cm}^2} \right)$ $AWG_p = 22.4$ (Approximated AWG wire size, for more precision refer to wire size table)

Primary Wire selected:

Wire size

$$AWG_{L_p} := 25$$

Bare area (copper plus insulation)

$$W_{a_{L_p}} := 2 \cdot 10^{-3} \cdot \text{cm}^2$$

Copper area:

$$W_{cu_{L_p}} := 2.514 \cdot 10^{-3} \cdot \text{cm}^2$$

Diameter

$$D_{cu_{L_p}} := 0.0505 \cdot \text{cm}$$

Number of strands:

$$N_{st_{L_p}} := 2$$

- Number of primary turns per layer: $Nt_{LP} := \text{floor}\left(\frac{l_w}{D_{CuLP}}\right)$ $Nt_{LP} = 41$

- Number of primary layers: $Nly_{LP} := \text{ceil}\left(\frac{N_p \cdot Nst_{LP}}{Nt_{LP}}\right)$ $Nly_{LP} = 4$

Secondary: Master

by wire area: $Ws_{1cu} := \frac{Is_{1rms}}{J}$ $Ws_{1cu} = 3.68 \cdot 10^{-3} \cdot \text{cm}^2$

or by wire size: $AWGs_1 := -4.2 \cdot \ln\left(\frac{Ws_{1cu}}{\text{cm}^2}\right)$ $AWGs_1 = 23.54$

Secondary Wire selected: Wire size $AWG_{LS1} := 25$

Bare area (copper plus insulation) $Wa_{LS1} := 2 \cdot 10^{-3} \cdot \text{cm}^2$

Copper area: $Wcu_{LS1} := 2.514 \cdot 10^{-3} \cdot \text{cm}^2$

Diameter $Dcu_{LS1} := 0.0505 \cdot \text{cm}$

Number of strands: $Nst_{LS1} := 2$

- Number of secondary turns per layer: $Nt_{LS1} := \text{floor}\left(\frac{l_w}{Dcu_{LS1}}\right)$ $Nt_{LS1} = 41$

- Number of secondary layers: $Nly_{LS1} := \text{ceil}\left(\frac{Ns_1 \cdot Nst_{LS1}}{Nt_{LS1}}\right)$ $Nly_{LS1} = 5$

by wire area: $Ws_{2cu} := \frac{Is_{2rms}}{J}$ $Ws_{2cu} = 37.89 \cdot 10^{-3} \cdot \text{cm}^2$

or by wire size: $AWGs_2 := -4.2 \cdot \ln\left(\frac{Ws_{2cu}}{\text{cm}^2}\right)$ $AWGs_2 = 13.75$

Secondary: Slave

Secondary Wire selected: Wire size $AWG_{LS2} := 26$

Bare area (copper plus insulation) $Wa_{LS2} := 1.63 \cdot 10^{-3} \cdot \text{cm}^2$

Copper area: $Wcu_{LS2} := 1.28 \cdot 10^{-3} \cdot \text{cm}^2$

Diameter $Dcu_{LS2} := 0.0452 \cdot \text{cm}$

Number of strands: $Nst_{LS2} := 1$

- Number of secondary turns per layer: $Nt_{LS2} := \text{floor}\left(\frac{l_w}{Dcu_{LS2}}\right)$ $Nt_{LS2} = 46$

- Number of secondary layers:
$$Nly_{Ls2} := \text{ceil} \left(\frac{Ns2 \cdot Nst_{Ls2}}{Ntl_{Ls2}} \right) \quad Nly_{Ls2} = 0$$

- Copper area:
$$Wcu_{tot} := (Dcu_{Lp} \cdot Nly_{Lp} + Dcu_{Ls1} \cdot Nly_{Ls1} + Dcu_{Ls2} \cdot Nly_{Ls2}) \cdot 1.15 \cdot lw$$

$$Wcu_{tot} = 1.09 \cdot \text{cm}^2$$

- Window utilization:
$$Wu := \frac{Wcu_{tot}}{Wa} \quad Wu = 89.54\%$$

Important: if Window utilisation is greater than 90%, (Copper area >> than bobbin area) a core with larger window area, or smaller wire sizes must be selected.

- Core losses:

$$P_{core} := Ve \cdot \left[\left(\frac{B}{10^3 \cdot \text{gauss}} \right)^{c1} \cdot a1 \cdot \left(\frac{fsw}{\text{kHz}} \right)^{b1} \right] \cdot \frac{10^{-3} \cdot \text{watt}}{\text{cm}^3} \quad P_{core} = 1.91 \cdot \text{watt}$$

- Winding copper losses:

There are two effects, which can cause the winding losses to be significantly greater than ($I^2 \cdot R_{cu}$): skin and proximity effects.

Skin effect causes current in a wire to flow only in a thin skin of the wire.

Skin depth: distance below the surface where the current density has fallen to 1/e of its value at the surface: (Sd)

$$Sd := \frac{6.61}{\sqrt{\frac{fsw}{\text{Hz}}}} \cdot \text{cm} \quad Sd = 0.02 \cdot \text{cm}$$

$$Lt = 6.05 \cdot \text{cm} \quad Nly_{Lp} = 4$$

To minimize the AC copper losses in a transformer, if the wire diameter is greater than two times the skin depth, a multi strands winding or litz wires should be considered

If $Dcu_{Lp} = 0.05 \cdot \text{cm}$ is greater than $Sd \cdot 2 = 0.04 \cdot \text{cm}$

Primary winding length:

$$Lcu_{Lp} := \begin{cases} L1 \leftarrow Lt \\ L \leftarrow 0 \cdot \text{cm} \\ \text{for } i \in 1 \dots (Nly_{Lp} - 1) \\ \quad \begin{cases} L \leftarrow L + L1 \cdot Ntl_{Lp} \\ L1 \leftarrow L1 + 4 \cdot Dcu_{Lp} \end{cases} \\ [L + L1 \cdot [Np - (Nly_{Lp} - 1) \cdot Ntl_{Lp}]] \end{cases} \quad Ldf_{Lp} := \begin{cases} L1 \leftarrow Lt \\ \text{for } i \in 1 \dots (Nly_{Lp} - 1) \\ \quad L1 \leftarrow L1 + 4 \cdot Dcu_{Lp} \\ L1 \end{cases}$$

$$Np = 82$$

$$L_{cu_{Lp}} = 496.1 \cdot \text{cm}$$

$$L_{df_{Lp}} = 6.66 \cdot \text{cm}$$

Copper resistivity: (20C)

$$\rho_{20} := 1.724 \cdot 10^{-6} \cdot \text{ohm} \cdot \text{cm}$$

$$7.15 \cdot N_p = 586.3$$

-Maximum temperature of the winding:

$$T_{\text{max}_{cu}} := 80$$

$$\rho := \rho_{20} \cdot [1 + 0.0042 \cdot (T_{\text{max}_{cu}} - 20)]$$

$$R_{dc_{Lp}} := \rho \cdot \frac{L_{cu_{Lp}}}{W_{cu_{Lp}} \cdot N_{st_{Lp}}}$$

$$R_{dc_{Lp}} = 0.21 \cdot \text{ohm}$$

$$R_{ac_{Lp}} := \frac{R_{dc_{Lp}} \cdot \left(\frac{D_{cu_{Lp}}}{2 \cdot S_d} \right)^2}{\left(\frac{D_{cu_{Lp}}}{2 \cdot S_d} \right)^2 - \left(\frac{D_{cu_{Lp}}}{2 \cdot S_d} - 1 \right)^2}$$

$$R_{ac_{Lp}} = 0.22 \cdot \text{ohm}$$

$$\frac{R_{ac_{Lp}}}{R_{dc_{Lp}}} = 1.03$$

$$P_{cu_{Lp}} := R_{dc_{Lp}} \cdot I_{p_{dc}}^2 + R_{ac_{Lp}} \cdot I_{p_{ac}}^2$$

$$P_{cu_{Lp}} = 0.77 \cdot \text{watt}$$

Secondary winding length:

$$L_{cu_{Ls1}} := \left[\begin{array}{l} L1 \leftarrow L_{df_{Lp}} \\ L \leftarrow 0 \cdot \text{cm} \\ \text{for } i \in 1..(N_{ly_{Ls1}} - 1) \\ \quad \left[\begin{array}{l} L \leftarrow L + L1 \cdot N_{tl_{Ls1}} \\ L1 \leftarrow L1 + 4 \cdot D_{cu_{Ls1}} \end{array} \right. \\ L \leftarrow 0 \text{ if } N_{ly_{Ls1}} \leftarrow 1 \\ \left[L + L1 \cdot [N_{s1} - (N_{ly_{Ls1}} - 1) \cdot N_{tl_{Ls1}}] \right] \end{array} \right.$$

$$L_{df_{Ls1}} := \left[\begin{array}{l} L1 \leftarrow L_{df_{Lp}} \\ \text{for } i \in 1..(N_{ly_{Ls2}} - 1) \\ \quad L1 \leftarrow L1 + 4 \cdot D_{cu_{Ls1}} \\ L1 \end{array} \right.$$

$$L_{cu_{Ls1}} = 701.62 \cdot \text{cm}$$

$$R_{dc_{Ls1}} := \rho \cdot \frac{L_{cu_{Ls1}}}{W_{cu_{Ls1}} \cdot N_{st_{Ls1}}}$$

$$R_{dc_{Ls1}} = 0.3 \cdot \text{ohm}$$

$$R_{ac_{Ls1}} := \frac{R_{dc_{Ls1}} \cdot \left(\frac{D_{cu_{Ls1}}}{2 \cdot S_d} \right)^2}{\left(\frac{D_{cu_{Ls1}}}{2 \cdot S_d} \right)^2 - \left(\frac{D_{cu_{Ls1}}}{2 \cdot S_d} - 1 \right)^2}$$

$$R_{ac_{Ls1}} = 0.31 \cdot \text{ohm}$$

$$\frac{R_{ac_{Ls1}}}{R_{dc_{Ls1}}} = 1.03$$

$$P_{cu_{Ls1}} := R_{dc_{Ls1}} \cdot I_{o1_{\text{max}}}^2 + R_{ac_{Ls1}} \cdot I_{s1_{ac}}^2$$

$$P_{cu_{Ls1}} = 0.63 \cdot \text{watt}$$

$$L_{cu_{Ls2}} := \begin{cases} L1 \leftarrow L_{df_{Ls1}} \\ L \leftarrow 0 \cdot \text{cm} \\ \text{for } i \in 1 \dots (Nly_{Ls2} - 1) \\ \quad \begin{cases} L \leftarrow L + L1 \cdot Ntl_{Ls2} \\ L1 \leftarrow L1 + 4 \cdot Dcu_{Ls2} \end{cases} \\ L \leftarrow 0 \text{ if } Nly_{Ls2} \leftarrow 1 \\ \left[L + L1 \cdot [Ns2 - (Nly_{Ls2} - 1) \cdot Ntl_{Ls2}] \right] \end{cases}$$

$$L_{cu_{Ls2}} = 0 \cdot \text{cm}$$

$$R_{dc_{Ls2}} := \rho \cdot \frac{L_{cu_{Ls2}}}{W_{cu_{Ls2}} \cdot Nst_{Ls2}}$$

$$R_{dc_{Ls2}} = 0 \cdot \text{ohm}$$

$$R_{ac_{Ls2}} := \frac{R_{dc_{Ls2}} \cdot \left(\frac{Dcu_{Ls2}}{2 \cdot Sd} \right)^2}{\left(\frac{Dcu_{Ls2}}{2 \cdot Sd} \right)^2 - \left(\frac{Dcu_{Ls2}}{2 \cdot Sd} - 1 \right)^2}$$

$$R_{ac_{Ls2}} = 0 \cdot \text{ohm}$$

$$\frac{R_{ac_{Ls2}}}{R_{dc_{Ls2}}} = 0$$

$$P_{cu_{Ls2}} := R_{dc_{Ls2}} \cdot I_{o2_{\max}}^2 + R_{ac_{Ls2}} \cdot I_{s2_{ac}}^2$$

$$P_{cu_{Ls2}} = 0 \cdot \text{watt}$$

$$P_{cu_{\text{tot}}} := P_{cu_{Lp}} + P_{cu_{Ls1}} + P_{cu_{Ls2}}$$

$$P_{cu_{\text{tot}}} = 1.4 \cdot \text{watt}$$

$$P_{\text{core}} = 1.91 \cdot \text{watt}$$

-Total transformer's losses:

$$P_{\text{trans}_{\text{tot}}} := P_{cu_{\text{tot}}} + P_{\text{core}}$$

$$P_{\text{trans}_{\text{tot}}} = 3.3 \cdot \text{watt}$$

-Transformer's efficiency:

$$\eta_{\text{Tra}} := \frac{P_{o_{\max}}}{P_{o_{\max}} + P_{\text{trans}_{\text{tot}}}}$$

$$\eta_{\text{Tra}} = 97.05 \cdot \%$$

12) Total Power Supply Efficiency:

$$P_{\text{out}} := V_{o1} \cdot I_{o1_{\max}} + V_{o2} \cdot I_{o2_{\max}}$$

$$P_{\text{trans}_{\text{tot}}} = 3.3 \cdot \text{watt}$$

$$P_{\text{diode}_{\text{tot}}} = 5.52 \cdot \text{watt}$$

$$P_{\text{mosfet}_{\text{tot}}} = 3.82 \cdot \text{watt}$$

$$\eta_{\text{tot}} := \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{trans}_{\text{tot}}} + P_{\text{diode}_{\text{tot}}} + P_{\text{mosfet}_{\text{tot}}}}$$

$$\eta_{\text{tot}} = 89.52 \cdot \%$$

13) Select the proper switching frequency:

The operating frequency of the power supply should be selected to obtain the best balance between switching losses, total transformer losses, size and cost of magnetic components and output capacitors. High switching frequency reduces the output capacitor value and the inductance of the primary and secondary windings, and therefore the total size of the transformer.

In the same manner, higher switching frequency increases the transformer losses and the switching losses of the switching transistor. High losses reduce the overall efficiency of the power supply, and increase the

size of the heat-sink required to dissipate the heat.

Notes:

Wire table:

AWG Wire Size	Bare Area cm ² 10 ⁻³	Area cm ² 10 ⁻³	Diameter cm
10	52,61	55,9	0,267
11	41,68	44,5	0,238
12	33,08	35,64	0,213
13	26,36	28,36	0,19
14	20,82	22,95	0,171
15	16,51	18,37	0,153
16	13,07	14,73	0,137
17	10,39	11,68	0,122
18	8,23	9,32	0,109
19	6,53	7,54	0,098
20	5,19	6,06	0,0879
21	4,12	4,84	0,0785
22	3,24	3,86	0,0701
23	2,59	3,13	0,0632
24	2,05	2,514	0,0566
25	1,62	2	0,0505
26	1,28	1,603	0,0452
27	1,02	1,313	0,0409
28	0,8	1,05	0,0366
29	0,647	0,854	0,033
30	0,506	0,678	0,0294

References:

1. Rudolf P. Severns, Gordon E. Bloom "Modern DC to DC switchmode power converter circuits".
2. Magnetics application notes.
3. Colonel Wm. T. McLyman "Transformer and Inductor Design Handbook"
4. Pressman "Switching Power Supply Design"
5. R. Martinelli, C. Hymowitz, Intusoft "Designing a 12.5W 50kHz Flyback Transformer"