

# LM5046,SM72295

***Application Note 2116 SolarMagic ICs in Micro-inverter Applications***



Literature Number: SNVA471A

# SolarMagic™ ICs in Microinverter Applications

National Semiconductor  
Application Note 2116  
Perry Tsao  
May 4, 2011



## Introduction

Microinverters are a growing and rapidly evolving part of the photovoltaic (PV) system. Modern microinverters are designed to convert the DC power from one PV module (solar panel) to the AC grid, and are designed for a max output power in the range of 180W to 300W. Compared to conventional string or central inverters, microinverters have advantages in ease of installation, localized max power point tracking, and redundancy that provides robustness to failure. Since this area of power electronics is seeing such rapid innovation, there are many different topologies and variations being developed. This article explores some of the prevalent topologies used in microinverters today, and the use of SolarMagic™ ICs in these demanding applications. In particular, the use of the SM72295 Photovoltaic Full-Bridge Driver will be highlighted.

## SolarMagic Renewable Energy Grade Components


The environment for electronics in PV systems is a very demanding one due to the extremes in temperatures and requirements for long-lifetime. The ambient temperature behind a photovoltaic module can range from below freezing in the winter to over 90°C on a summer day. With this in mind National Semiconductor created the Renewable Energy Grade line of SolarMagic ICs that are all rated for operation from -40° C to +125° C and have all been screened and tested to standards appropriate for products that are designed for a 25 year

lifetime. This line of products includes MOSFET gate drives, PWM controllers with integrated switches, LDO regulators, amplifiers, and many other ICs necessary for photovoltaic electronics. All of the ICs recommended in this article are being made available as Renewable Energy Grade components.


## Single-Stage Microinverters

There have been a multitude of microinverter topologies developed [1], and these topologies can be broken up into two broad categories. The first category depicted in the block diagram of *Figure 1* employs a DC/DC converter and controls the converter output voltage to have the shape of a rectified sinusoid. This rectified sinusoid waveform is then inverted into a full sinusoidal waveform using an “unfolding bridge” that interfaces to the grid voltage. Though perhaps not the most accurate name, this category of microinverter topologies is often referred to as a “single-stage microinverter” because the boosting of the panel voltage and shaping of the AC waveform is accomplished in a single stage.

A more formal categorization of microinverter topologies [2] refers to this as a PV-side decoupled topology because the input capacitors decouple the AC power variation. The most widespread topology of this category is a quasi-resonant interleaved flyback, however, there are other variants such as interleaved flyback (not quasi-resonant) and interleaved forward converter. The unfolding inverter is generally implemented with 4 SCR's (silicon controlled rectifiers) that switch at the grid frequency.

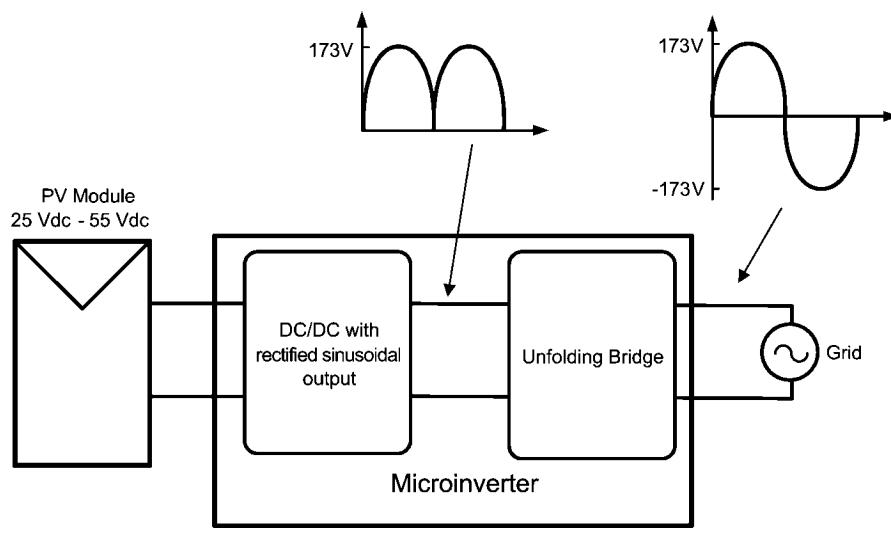

**FIGURE 1. Block diagram of a microinverter using a single-stage topology. The DC/DC stage can be implemented as a quasi-resonant interleaved flyback or another topology.**

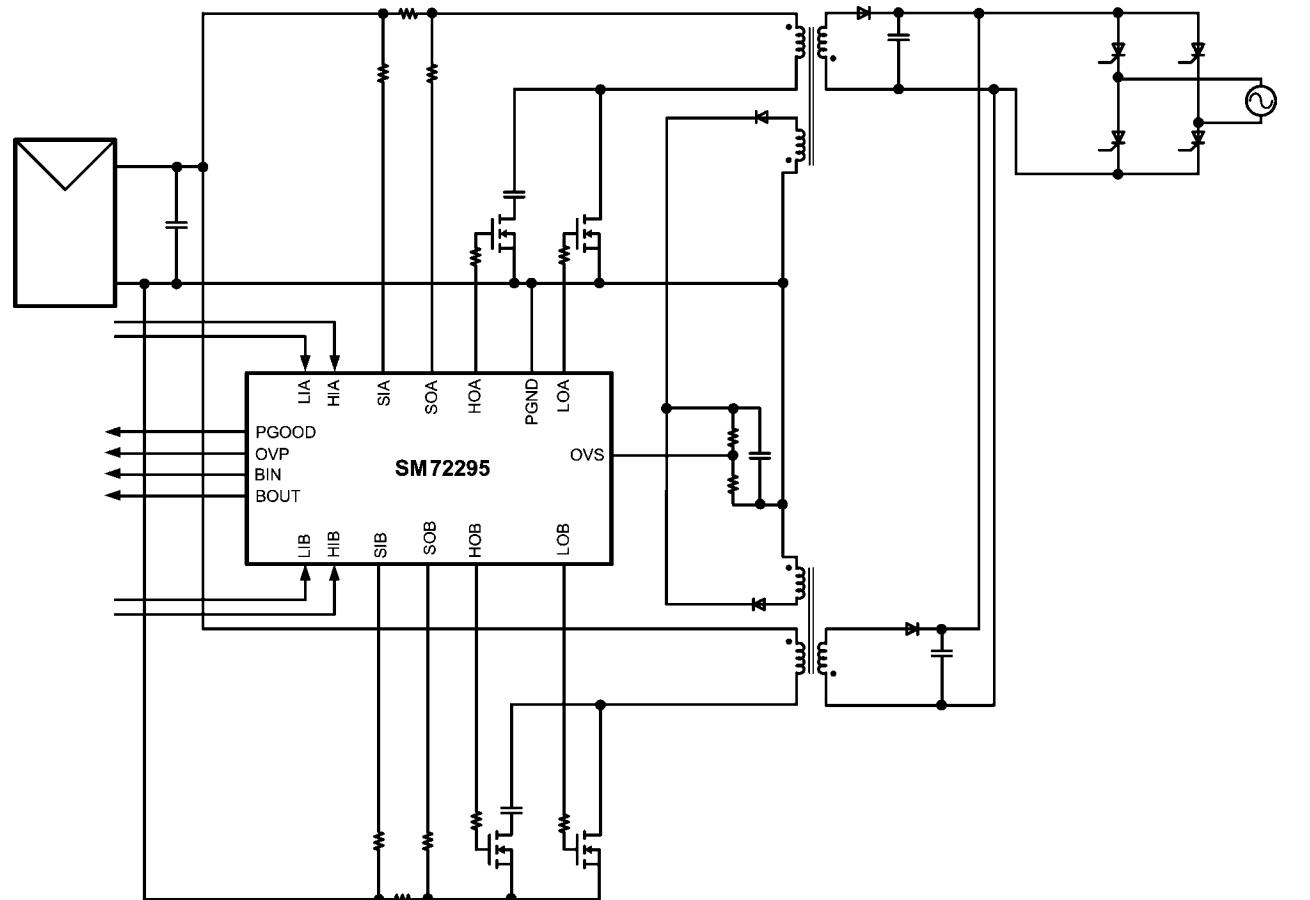

30150102

**FIGURE 2. Simplified schematic of a quasi-resonant interleaved flyback using the SM72295. Current sensing is implemented with high-side current sense resistors, and output overvoltage shutdown is implemented using voltage sense windings and the OVS pin.**

*Figure 2* depicts a simplified schematic of a single-stage microinverter using a quasi-resonant interleaved flyback for the DC-DC stage. In the quasi-resonant interleaved flyback, the SM72295 provides the microinverter designer with a high level of integration and enables maximized power density, reduced component count, and reduced PCB space. The SM72295 combines four independent 3A MOSFET gate drives with signal conditioning, power good, and overvoltage sensing functionality. Gate drive signal inputs are compatible with both 3.3V and 5V logic.

The integrated signal conditioning provides two channels optimized for using high-side current sense resistors with common-mode voltages up to 100V. A transconductance amplifier provides gain and is followed by a low-impedance buffer suitable for interfacing into an analog to digital converter (ADC). The use of current sense resistors is a lower cost alternative to commonly used current-sense transformers. In addition, the ability to put the current sense resistors on the high-side (positive voltage) current path as opposed to the low-side (ground) return path can ease layout because it does not require segmenting the ground plane and also eliminates the need for a negative rail voltage in cases where the sense resistor voltage goes below ground.

The advantages of the single-stage topology microinverters are their lower component count, low switching frequencies of the unfolding bridge, and ease of implementing isolation. Disadvantages include high voltage ratings on both the primary side switches and the secondary side diode, and high amplitude 120Hz ripple current at the input. This input ripple current must be controlled to maintain an acceptable efficiency level due to the nature of the photovoltaic module.

A photovoltaic module has a load curve with a specific maximum power point  $P_{mp}$  that occurs when its output voltage equals  $V_{mp}$  and output current equals  $I_{mp}$ . To maximize energy harvest, the microinverter maintains the module output voltage and current as closely as possible to  $V_{mp}$  and  $I_{mp}$  using a max power point tracking algorithm. Deviations from  $V_{mp}$  or  $I_{mp}$ , such as those caused by input ripple current, would cause power loss. Therefore the input ripple current of the single-stage inverters must be reduced to minimize the power loss, and this necessitates large capacitors at the input of the microinverter. For practical cost and size purposes these capacitors can only be implemented with electrolytic capacitors.

## Two-Stage Microinverters

The second category of microinverter topologies depicted in the block diagram of *Figure 3* employ an intermediate high voltage DC-bus. These topologies use a DC/DC converter with a high boost ratio to boost from the PV module voltage to the intermediate DC-bus voltage, and then use a conventional PWM controlled MOSFET or IGBT full-bridge to invert the waveform to the grid. This type of microinverter is also referred to as a DC-link topology [2].


There are many different options being implemented for the DC/DC stage in the designs being developed today. Possibilities include:

1. Interleaved flyback
2. Push-pull converter (current-fed or voltage-fed, with passive or active clamp)
3. Full-bridge converter (voltage-fed, current-fed, or resonant)


From a high-level perspective, all of these topologies are more complex and costly than the single-stage microinverter

due to the additional high-frequency switching components. At first it may not be obvious why these topologies are being developed. However, for applications in microinverters, there's an overriding focus on maximizing reliability, which puts emphasis on choosing a topology that enables the selection of the highest reliability components. All of the these topologies have much lower input ripple current at the PV input side, and therefore use lower capacitance values that make it practical to use higher reliability film capacitors in the place of electrolytic capacitors.

Another benefit of the two-stage topologies is that it makes it possible to provide reactive power to the grid, whereas it is not possible with single-stage inverters with an SCR unfolding bridge. The ability to provide reactive power is a highly desirable feature for some commercial installations, and it is already a requirement for larger photovoltaic installations in some countries.

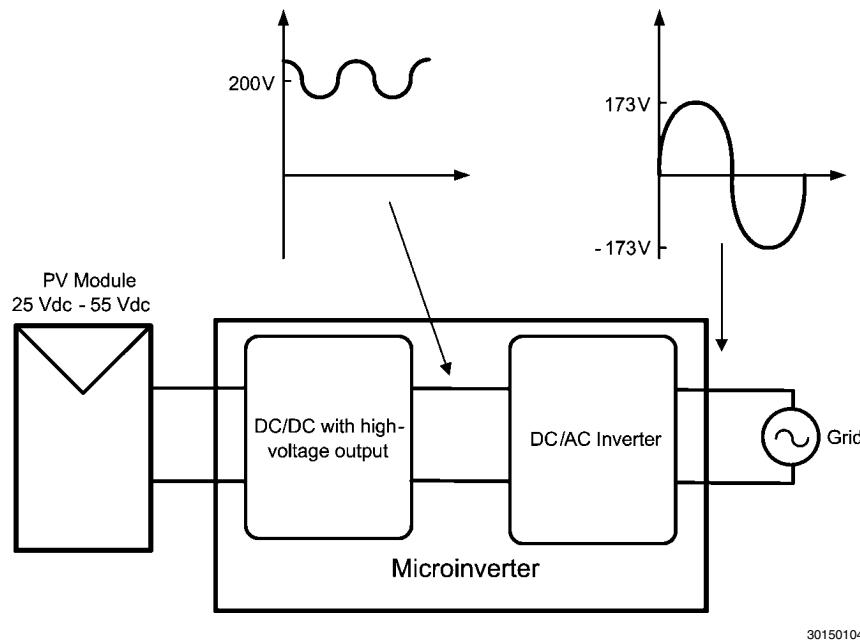

**FIGURE 3. Block Diagram Of Two-Stage Inverter With A DC Bus.**

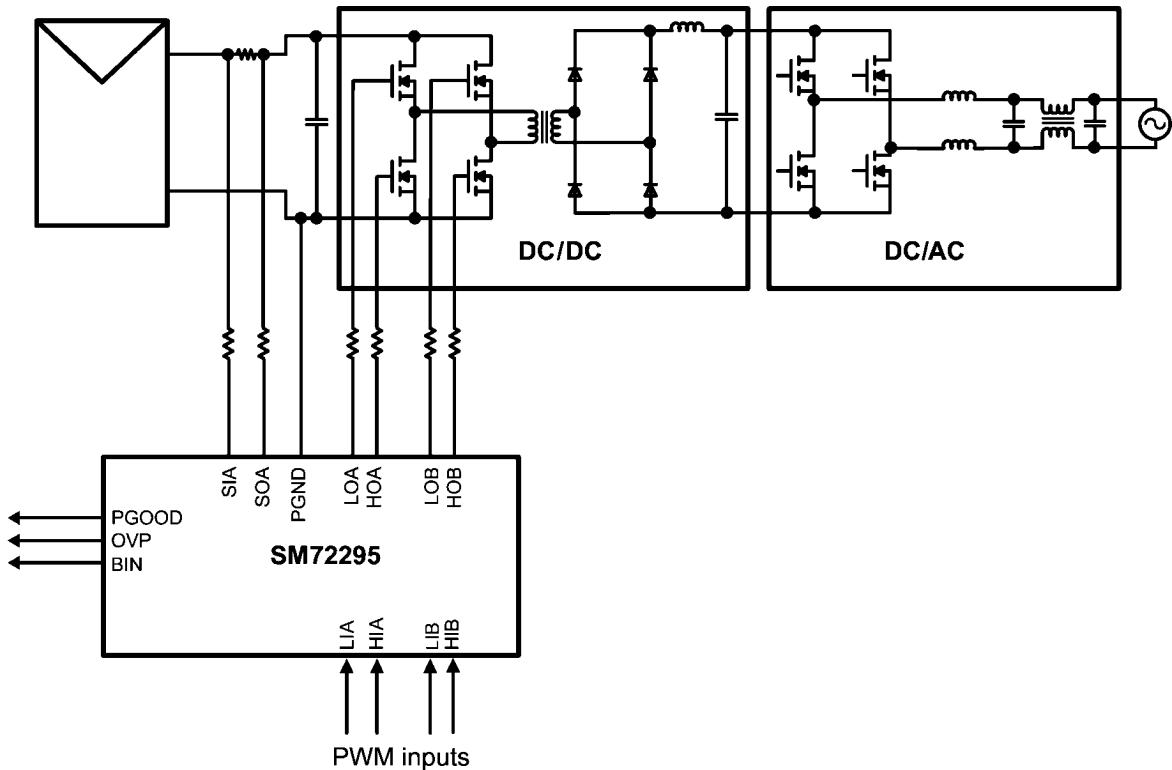

30150105

**FIGURE 4. Simplified schematic of a two stage microinverter using the SM72295. The DC/DC stage is implemented as a voltage-fed full-bridge converter, and the DC/AC stage is implemented as a MOSFET Full-bridge.**

Shown in *Figure 4* is a simplified schematic of a two-stage microinverter implemented with a voltage-fed full-bridge for the DC/DC stage and a MOSFET full-bridge for the DC/AC stage. In this application, the SM72295 provides gate drives for the four primary side MOSFETs. The SM72295 is ideally suited as a gate driver in many of these two-stage topologies, several of which use a MOSFET full-bridge on their primary side.

As shown in *Figure 4*, the SM72295 is capable of driving all 4 MOSFETs in the primary side full-bridge. It provides 2 high-side and 2 low-side gate drives, integrated bootstrap diodes, and is suitable for input voltages up to 100V. The additional integration of signal conditioning, undervoltage lockout, and overvoltage shutdown further reduce part count and conserve valuable PCB real-estate.

## Housekeeping Power and Other Applications


In addition to the SM72295, there is a broad range of SolarMagic ICs suitable for application in other areas of the microinverter. As shown in *Figure 5* and *Table 1*, this includes temperature sensors, voltage references, precision amplifiers for current and voltage sensing, and switchers and LDOs for housekeeping power. These ICs have application in both single-stage and two-stage microinverters of all topologies.

## Conclusion

Microinverters are an exciting and growing application area for power electronics. This article gave a brief overview of some of the topologies being used in microinverters today, and described the SM72295 Photovoltaic Full-bridge Driver which integrates the key functions of MOSFET gate drives, signal conditioning, undervoltage lockout, and overvoltage shutdown. The SM72295 and other SolarMagic ICs support the most prevalent topologies used in microinverters today, and help microinverter designers maximize reliability, minimize complexity, minimize size, and minimize cost.

## References

- [1] B. Burger, B. Goeldi, S. Rogalla, H. Schmidt. "Module integrated electronics – an overview" 25<sup>th</sup> European Photovoltaic Solar Energy Conference and Exhibition. 6-10 Sept. 2010. pp. 3700 – 3707.
- [2] Haibing Hu; Harb, S.; Kutkut, N.; Batarseh, I.; Shen, Z.J. "Power decoupling techniques for micro-inverters in PV systems-a review" Energy Conversion Congress and Exposition (ECCE), 2010. pp. 3235 – 3240.

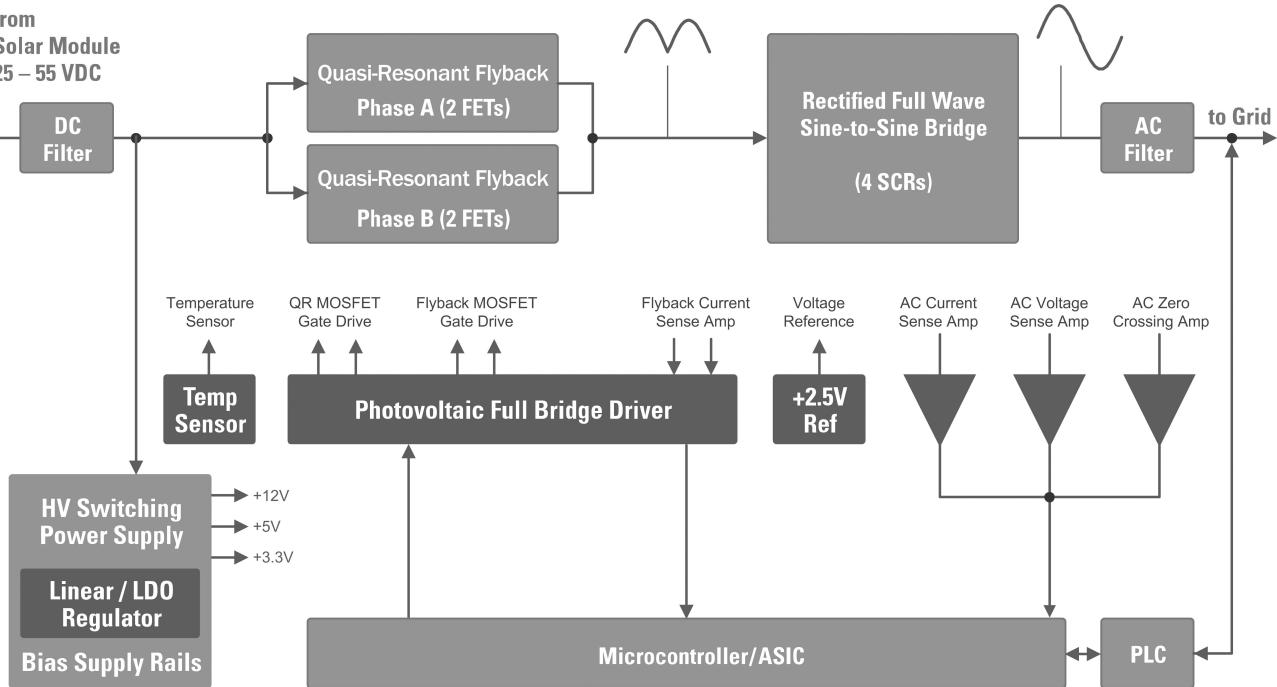

**FIGURE 5. Block Diagram Of SolarMagic Ics In A Microinverter Application**

**TABLE 1.**

<b>Gate Drives</b>	<b>Description</b>
SM72295	Photovoltaic Full-Bridge Driver
SM72482	Dual 5A Compound Gate Driver
SM74101	Tiny 7A MOSFET Gate Driver (LLP-6 package)
SM74104	High Voltage Half-Bridge Gate Driver with Adaptive Delay
<hr/>	
<b>High Voltage Switching Regulators with Integrated Switch</b>	<b>Description</b>
SM72485	100V, 150mA Step-Down (Buck) Converter
SM74301	100V, 350 mA Constant On-Time Buck Switching Regulator
SM74304	80V, 500mA Step Down Swithching Regulator
<hr/>	
<b>Low Dropout Voltage Regulators</b>	<b>Description</b>
SM74501	50mA Low Dropout Voltage Regulator (3.3V, 5.0V), max Vin 40V
SM72238	100mA Low Dropout Voltage Regulator (3.3V, 5.0V), max Vin 30V
SM74503	800mA Low-Dropout Regulator (3.3V, 5.0V), max Vin 15V
<hr/>	
<b>Amplifiers for current sensing, voltage sensing, and buffering</b>	<b>Description</b>
SM72501	Precision, CMOS Input, Rail-to-Rail Input Output, Wide Supply Range Amplifier
SM73301	Rail-to-Rail Input Output, High Output Current & Unlimited Cap Load Op Amp
SM73302	88 MHz, Precision, Low Noise, 1.8V CMOS Input, Op Amp
SM73303	5 MHz, Low Noise, Rail-to-Rail Output, Dual Operational Amplifier with CMOS Input
SM73304	Dual 17 MHz, Low Noise, CMOS Input Amplifier
SM73305	17 MHz, Low Noise, CMOS Input Amplifier
SM73306	Dual CMOS Rail to Rail Input and Output Operational Amplifier
<hr/>	
<b>Comparators</b>	<b>Description</b>
SM72375	Dual Micro-Power CMOS Comparator
SM73402	Low Power Low Offset Quad Comparators
SM73403	Single General Purpose Voltage Comparator
<hr/>	
<b>Reset and Supervisory</b>	<b>Description</b>
SM72240	5-Pin Microprocessor Reset Circuit (3.08V, 4.63V thresholds)
SM74601	Precision Micropower Series Voltage Reference (2.5V)
<hr/>	
<b>Thermostats and Temperature Sensors</b>	<b>Description</b>
SM72480	125°C, 120°C, and 105°C Thermostat
SM73710	±4°C Accurate, Temperature Sensor



## Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:  
[www.national.com](http://www.national.com)

Products		Design Support	
Amplifiers	<a href="http://www.national.com/amplifiers">www.national.com/amplifiers</a>	WEBENCH® Tools	<a href="http://www.national.com/webench">www.national.com/webench</a>
Audio	<a href="http://www.national.com/audio">www.national.com/audio</a>	App Notes	<a href="http://www.national.com/appnotes">www.national.com/appnotes</a>
Clock and Timing	<a href="http://www.national.com/timing">www.national.com/timing</a>	Reference Designs	<a href="http://www.national.com/refdesigns">www.national.com/refdesigns</a>
Data Converters	<a href="http://www.national.com/adc">www.national.com/adc</a>	Samples	<a href="http://www.national.com/samples">www.national.com/samples</a>
Interface	<a href="http://www.national.com/interface">www.national.com/interface</a>	Eval Boards	<a href="http://www.national.com/evalboards">www.national.com/evalboards</a>
LVDS	<a href="http://www.national.com/lvds">www.national.com/lvds</a>	Packaging	<a href="http://www.national.com/packaging">www.national.com/packaging</a>
Power Management	<a href="http://www.national.com/power">www.national.com/power</a>	Green Compliance	<a href="http://www.national.com/quality/green">www.national.com/quality/green</a>
Switching Regulators	<a href="http://www.national.com/switchers">www.national.com/switchers</a>	Distributors	<a href="http://www.national.com/contacts">www.national.com/contacts</a>
LDOs	<a href="http://www.national.com/ldo">www.national.com/ldo</a>	Quality and Reliability	<a href="http://www.national.com/quality">www.national.com/quality</a>
LED Lighting	<a href="http://www.national.com/led">www.national.com/led</a>	Feedback/Support	<a href="http://www.national.com/feedback">www.national.com/feedback</a>
Voltage References	<a href="http://www.national.com/vref">www.national.com/vref</a>	Design Made Easy	<a href="http://www.national.com/easy">www.national.com/easy</a>
PowerWise® Solutions	<a href="http://www.national.com/powerwise">www.national.com/powerwise</a>	Applications & Markets	<a href="http://www.national.com/solutions">www.national.com/solutions</a>
Serial Digital Interface (SDI)	<a href="http://www.national.com/sdi">www.national.com/sdi</a>	Mil/Aero	<a href="http://www.national.com/milaero">www.national.com/milaero</a>
Temperature Sensors	<a href="http://www.national.com/tempssensors">www.national.com/tempssensors</a>	SolarMagic™	<a href="http://www.national.com/solarmagic">www.national.com/solarmagic</a>
PLL/VCO	<a href="http://www.national.com/wireless">www.national.com/wireless</a>	PowerWise® Design University	<a href="http://www.national.com/training">www.national.com/training</a>

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

### LIFE SUPPORT POLICY

**NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION.** As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2011 National Semiconductor Corporation

For the most current product information visit us at [www.national.com](http://www.national.com)



National Semiconductor  
 Americas Technical  
 Support Center  
 Email: [support@nsc.com](mailto:support@nsc.com)  
 Tel: 1-800-272-9959

National Semiconductor Europe  
 Technical Support Center  
 Email: [europe.support@nsc.com](mailto:europe.support@nsc.com)

National Semiconductor Asia  
 Pacific Technical Support Center  
 Email: [ap.support@nsc.com](mailto:ap.support@nsc.com)

National Semiconductor Japan  
 Technical Support Center  
 Email: [jpn.feedback@nsc.com](mailto:jpn.feedback@nsc.com)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

[TI E2E Community Home Page](#)

[e2e.ti.com](#)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated