

CMRR

TIPL 1231

TI Precision Labs – Op Amps


Presented by Collin Wells

Prepared by Collin Wells, Art Kay, Ian Williams, and Tim Green

Prerequisites: Op Amp Bandwidth 1 – 3

(TIPL1221 – TIPL1223)

Referring Error to Input (RTI)

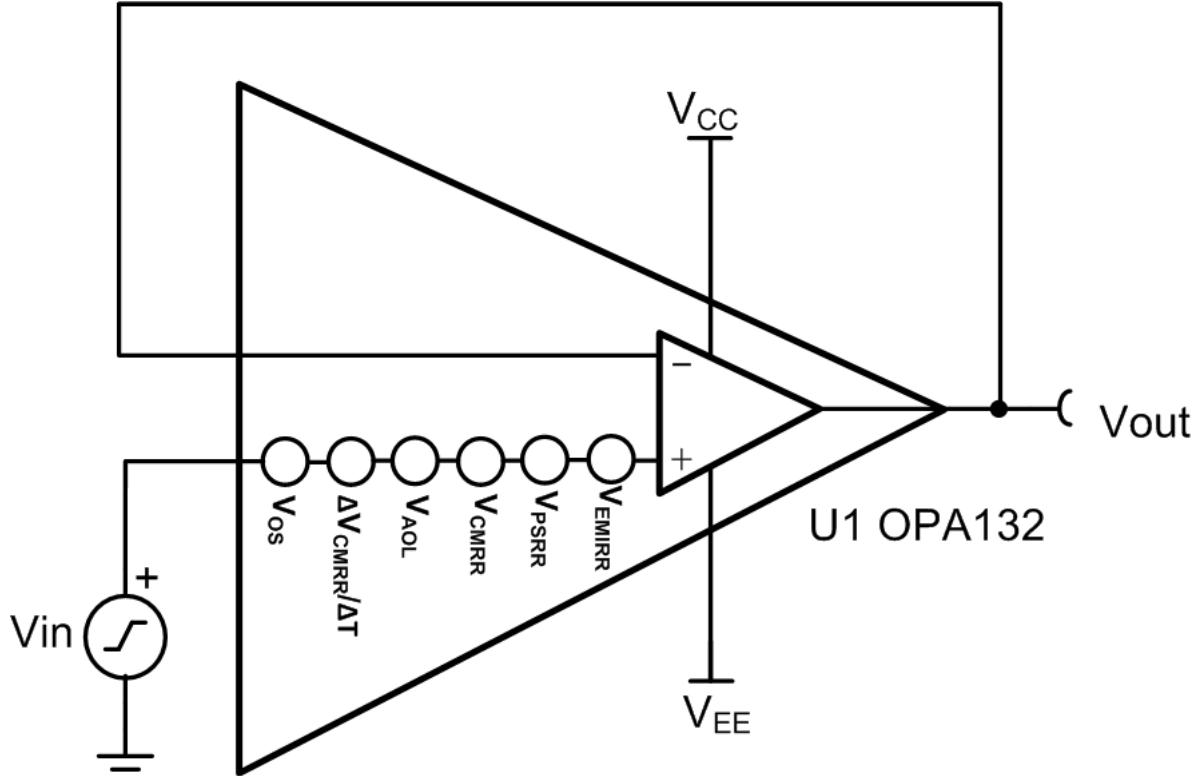

CMRR and A_{OL} Combined

| | Typical | Unit |
|----------|---------|------|
| A_{OL} | 136 | dB |
| CMRR | 134 | dB |



Combined Effects of A_{OL} and CMRR

$$V_{osAol} = \frac{\Delta V_{out}}{A_{OL}} = \frac{10V}{10^{\frac{136}{20}}} = 1.6\mu V$$


$$V_{osCMRR} = \frac{\Delta V_{out}}{CMRR} = \frac{10V}{10^{\frac{134}{20}}} = 2\mu V$$

$$\Delta V_{osTotal} = V_{osAol} + V_{osCMRR} = 3.6\mu V$$
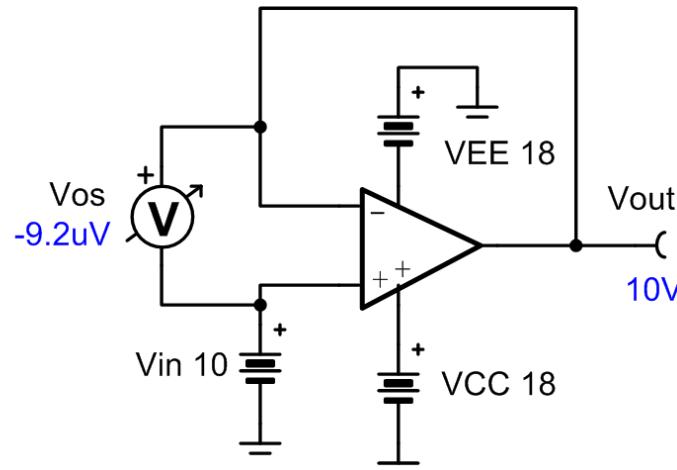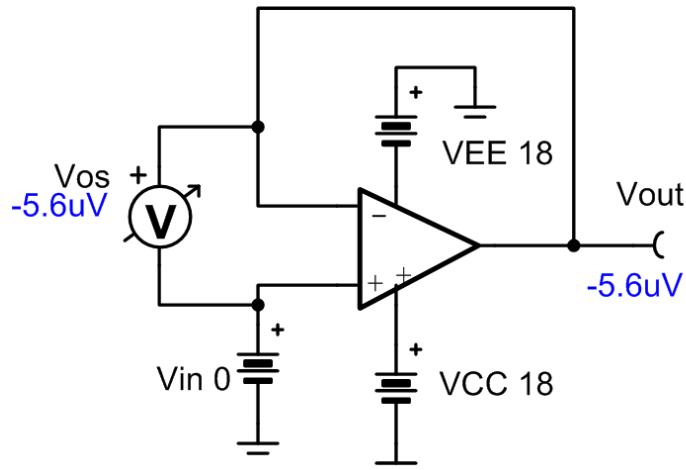
$$\Delta V_{osSim} = V_{os10V} - V_{os0V} = 3.6\mu V$$



Introducing the Dif Amp for testing CMRR

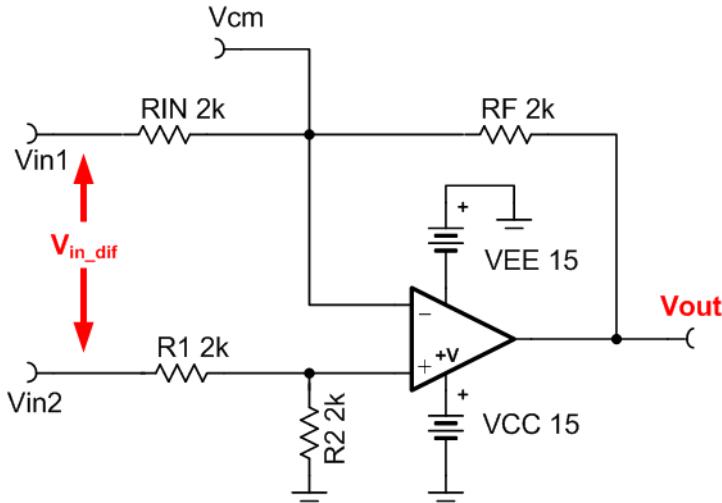


Gain of a Dif-Amp

$$R_f = R_2 \text{ and } R_{in} = R_1$$

$$G_{dif} = \frac{R_F}{R_{IN}} = 1 \text{ V/V}$$

$$V_{out} = G_{dif} \cdot V_{in_dif}$$

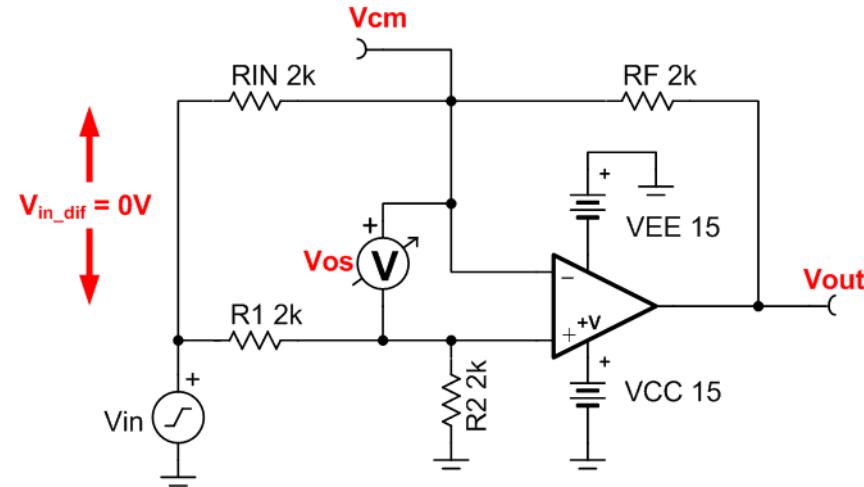

CMRR of a Dif-Amp

$$V_{out} = (0V) \cdot (1 \text{ V/V}) = 0V$$

$$V_{cm} = V_{in} \cdot \left(\frac{R_2}{R_1 + R_2} \right) = \frac{V_{in}}{2}$$



$$\text{CMRR(V/V)} = \frac{\Delta V_{os}}{\Delta V_{cm}}$$

Ideal output.

Common Mode Voltage

Common Mode Rejection

DC CMRR Test

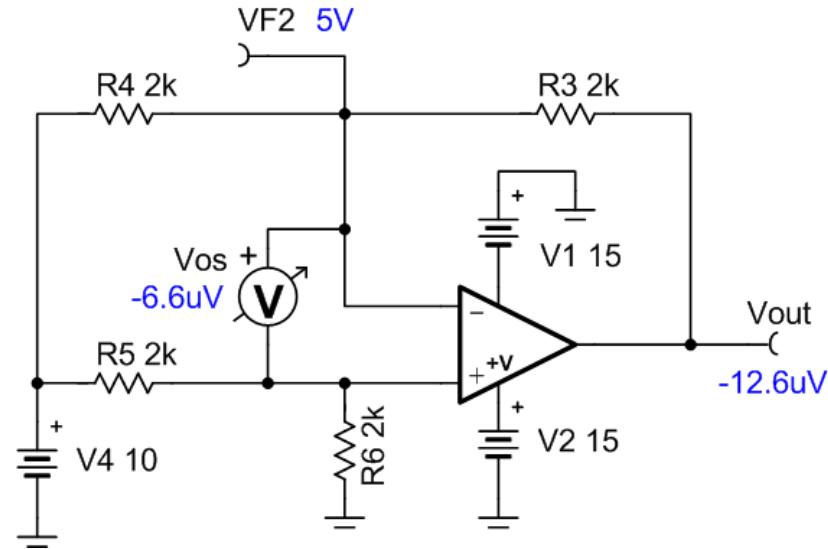
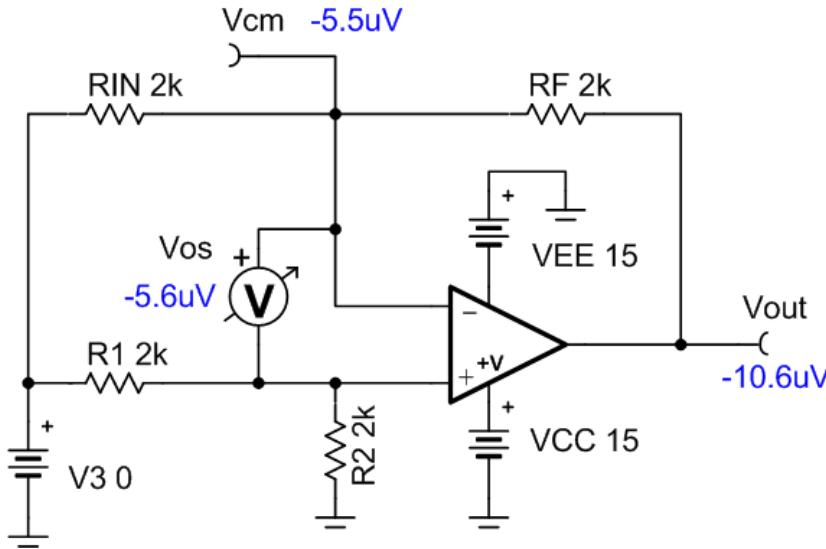


CMRR of a Dif-Amp

$$CMRR(V/V) = \frac{\Delta V_{os}}{\Delta V_{cm}} = \frac{|-6.6\mu V - (-5.6\mu V)|}{|5V - 0V|} = 0.2 \cdot 10^{-6} V/V$$

$$CMRR(dB) = -20 \cdot \log[CMRR(V/V)] = 134dB$$

AC CMRR Test

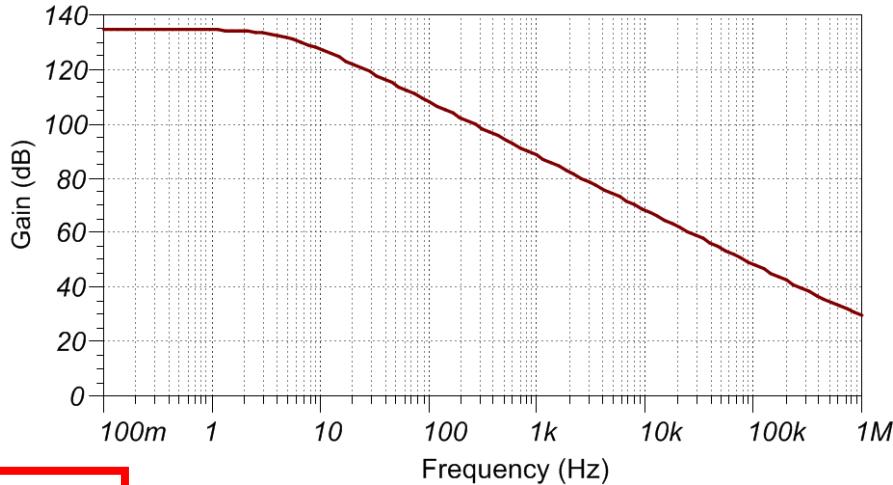
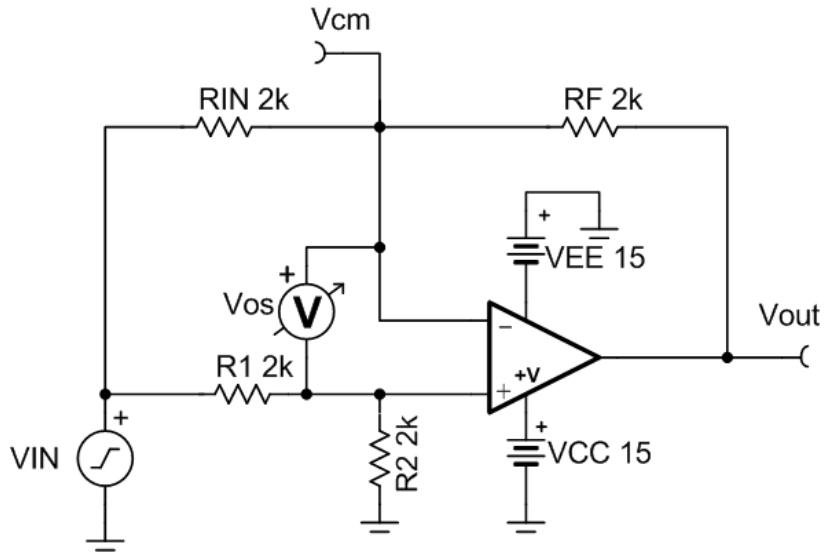


CMRR of a Dif-Amp



$$CMRR(V/V) = \frac{\Delta V_{os}}{\Delta V_{cm}}$$

$$CMRR(dB) = -20 \cdot \log[CMRR(V/V)]$$

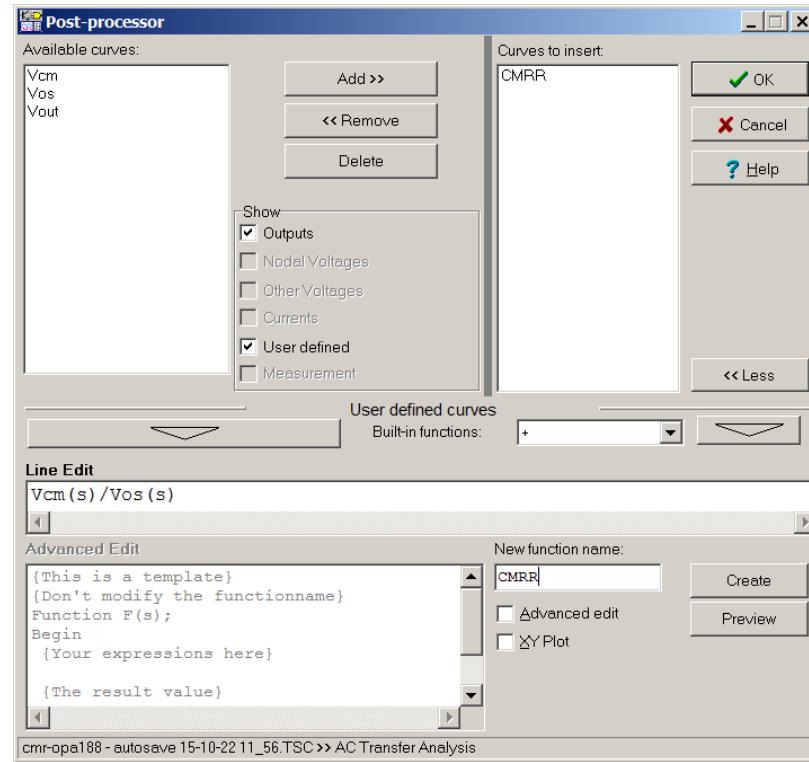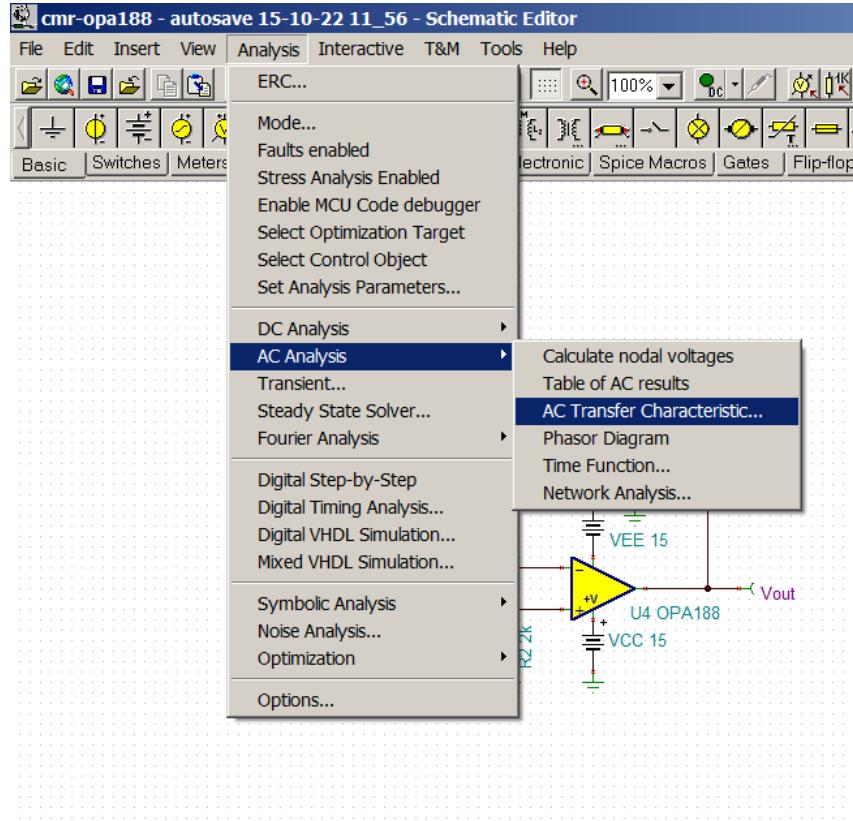Post Processor – Generating the Curve in Tina



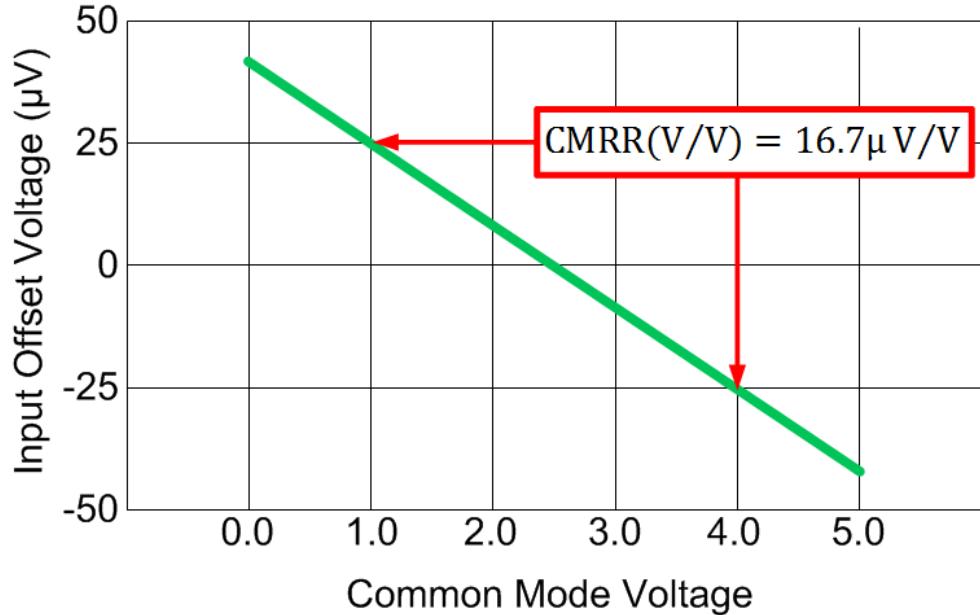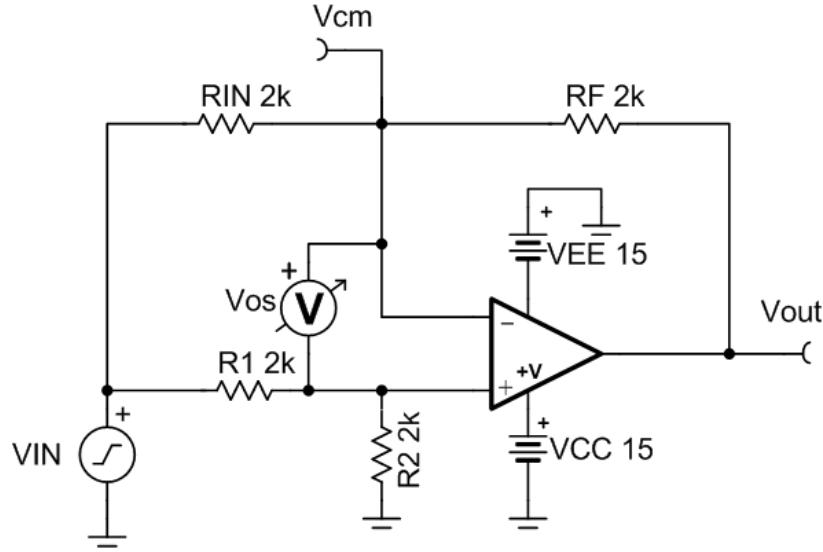
Offset (V_{os}) vs. Common Mode Voltage (V_{cm})



$$CMRR(V/V) = \frac{\Delta V_{os}}{\Delta V_{cm}} = \frac{|25\mu V - (-25\mu V)|}{|1V - 4V|} = 16.7 \cdot 10^{-6} V/V$$
$$CMRR(dB) = -20 \cdot \log[CMRR(V/V)] = 96dB$$


Distribution of CMRR

| PARAMETER | TEST CONDITION | MIN | TYP | MAX | UNIT |
|-----------------------|------------------------------|-----|-----|-----|------|
| Common-Mode Rejection | $V_{CM} = -12.5V$ to $12.5V$ | 87 | 100 | | dB |



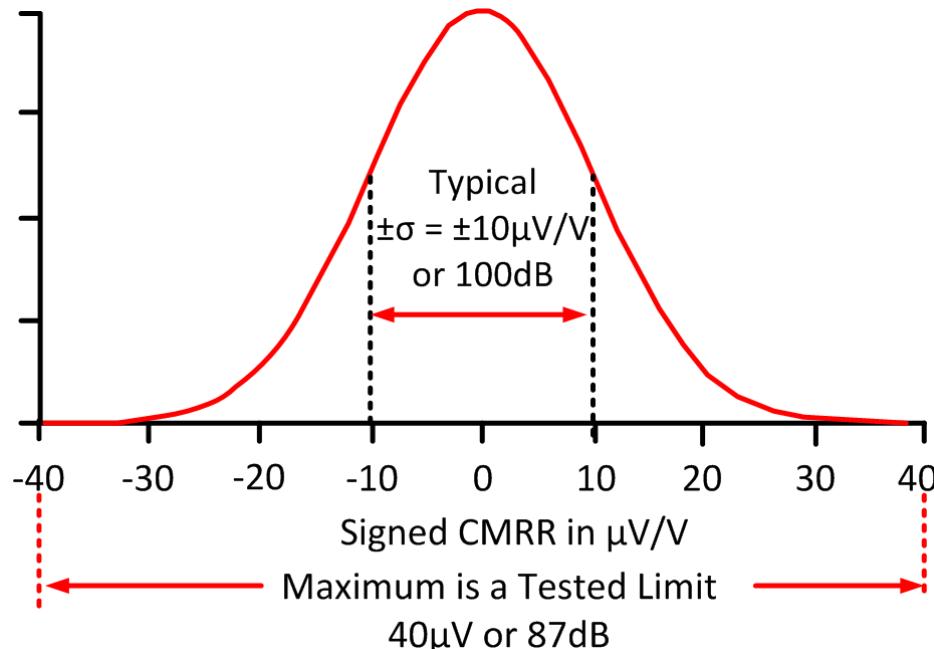


Crossover Distortion Caused by CMRR

Vout vs. Time (Crossover Distortion)


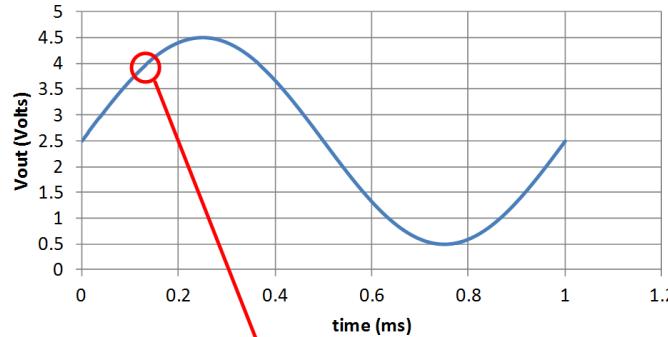


Zoom in on Crossover Distortion

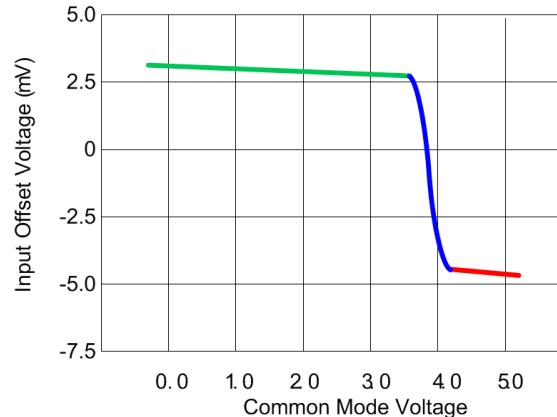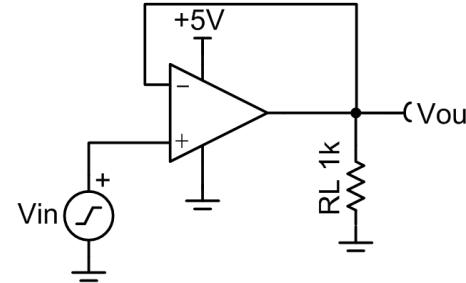
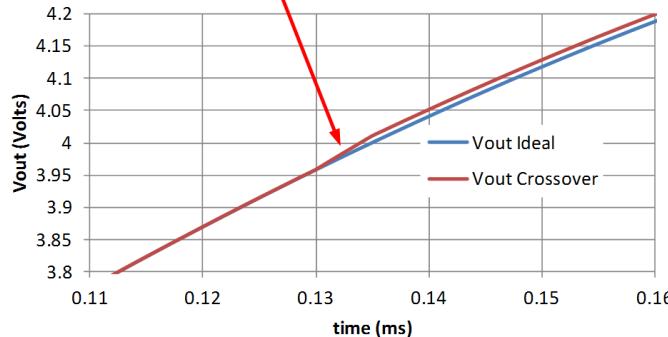


CMRR for Amplifiers with Crossover Distortion

| PARAMETER | TEST CONDITIONS | OPA192 | | | UNIT |
|-------------------------------------|--|-----------------------------|-----|-----|------|
| | | MIN | TYP | MAX | |
| CMRR Common-mode rejection ratio | $(V-) - 0.1 \text{ V} < V_{CM} < (V+) - 3 \text{ V}$ | 120 | 140 | | dB |
| | $(V+) - 3 \text{ V} < V_{CM} < (V+) - 1.5 \text{ V}$ | See Typical Characteristics | | | |
| | $(V+) - 1.5 \text{ V} < V_{CM} < (V+) + 0.1 \text{ V}$ | 100 | 120 | | dB |

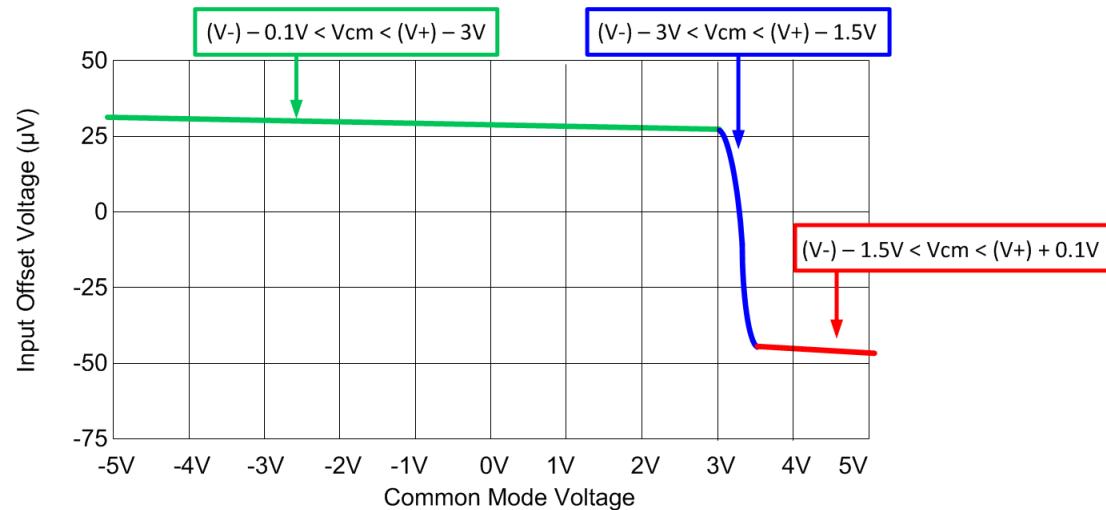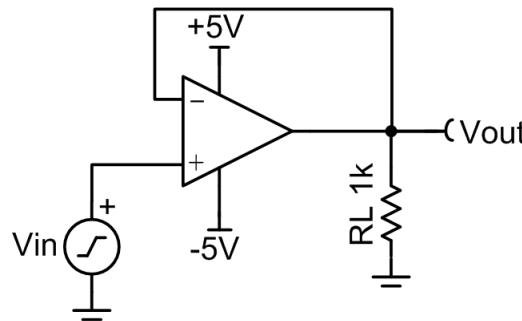

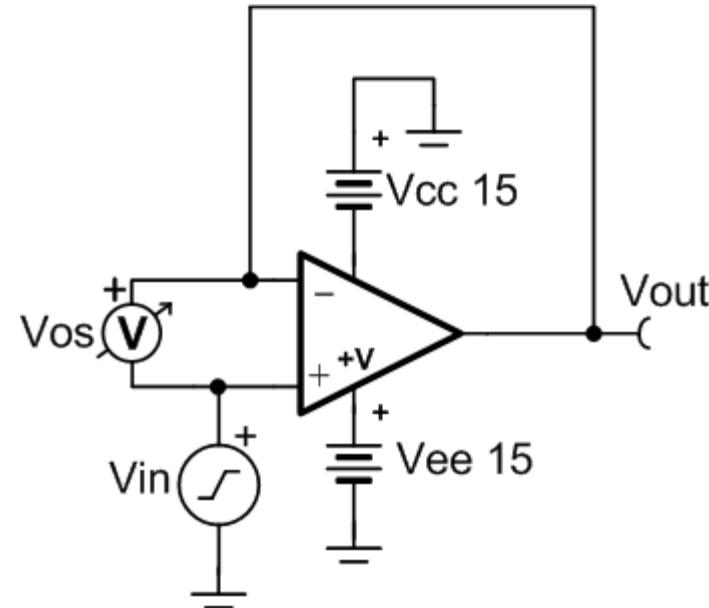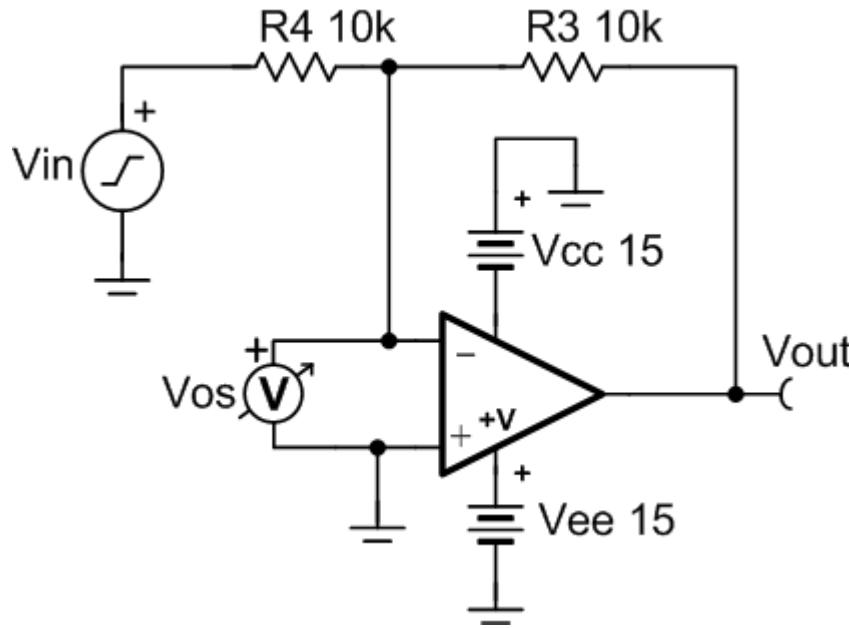Inverting vs. Non-inverting (Impact on CMRR)



**Thanks for your time!
Please try the quiz.**