

Noise In Photodiode Applications

By Art Kay and Bryan Zhao (赵伟)

June 1, 2011

Contents

- Photodiode Review
- Photodiode Noise Theory
- Bandwidth and Stability
- OPA827 Hand Calculation
- OPA827 Tina Spice Analysis
- OPA827 Measurement Example

Photodiode Basics

Why Photodiode Noise?

- Noise is a key parameter in photodiode design
 - Wide bandwidth (integrate more noise)
 - Low signal levels (noise more critical)
- Photodiode amplifier noise is more complex
 - Parasitic capacitance and sensor capacitance
 - Poles and zeros
 - Gain peaking

Photodiode Basics



- **Introduction**

- Photodiodes convert light into current or voltage.


- **Photodiode type**

- PIN photodiode – wide spectral range (less selective), PIN = p-doping, intrinsic material, n-doping
- PN photodiode – more wavelength selective
- APD (Avalanche photodiode) – sensitive to low light, fast

SPECTRAL RESPONSE

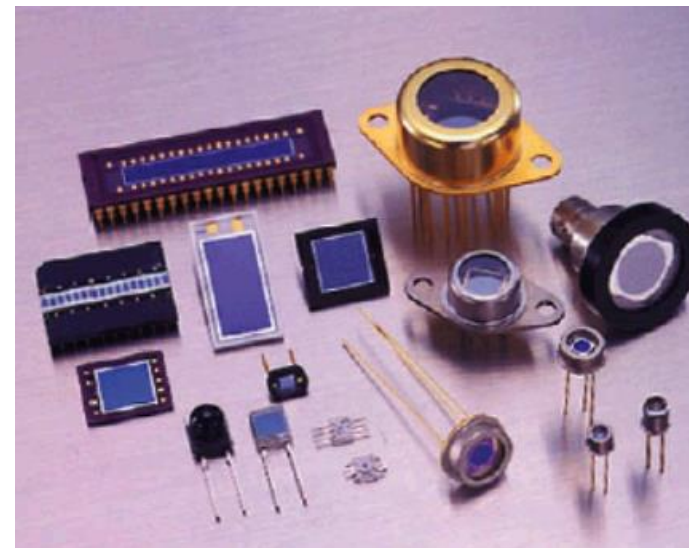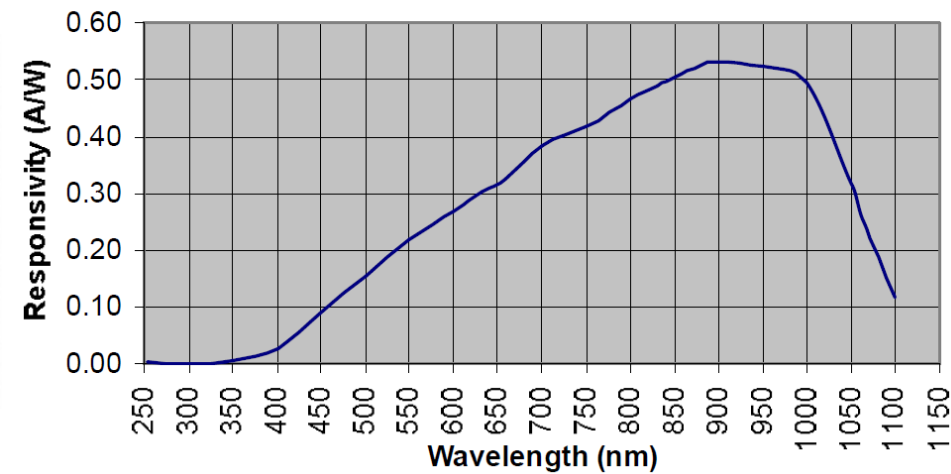

Basic Photodiode Physics

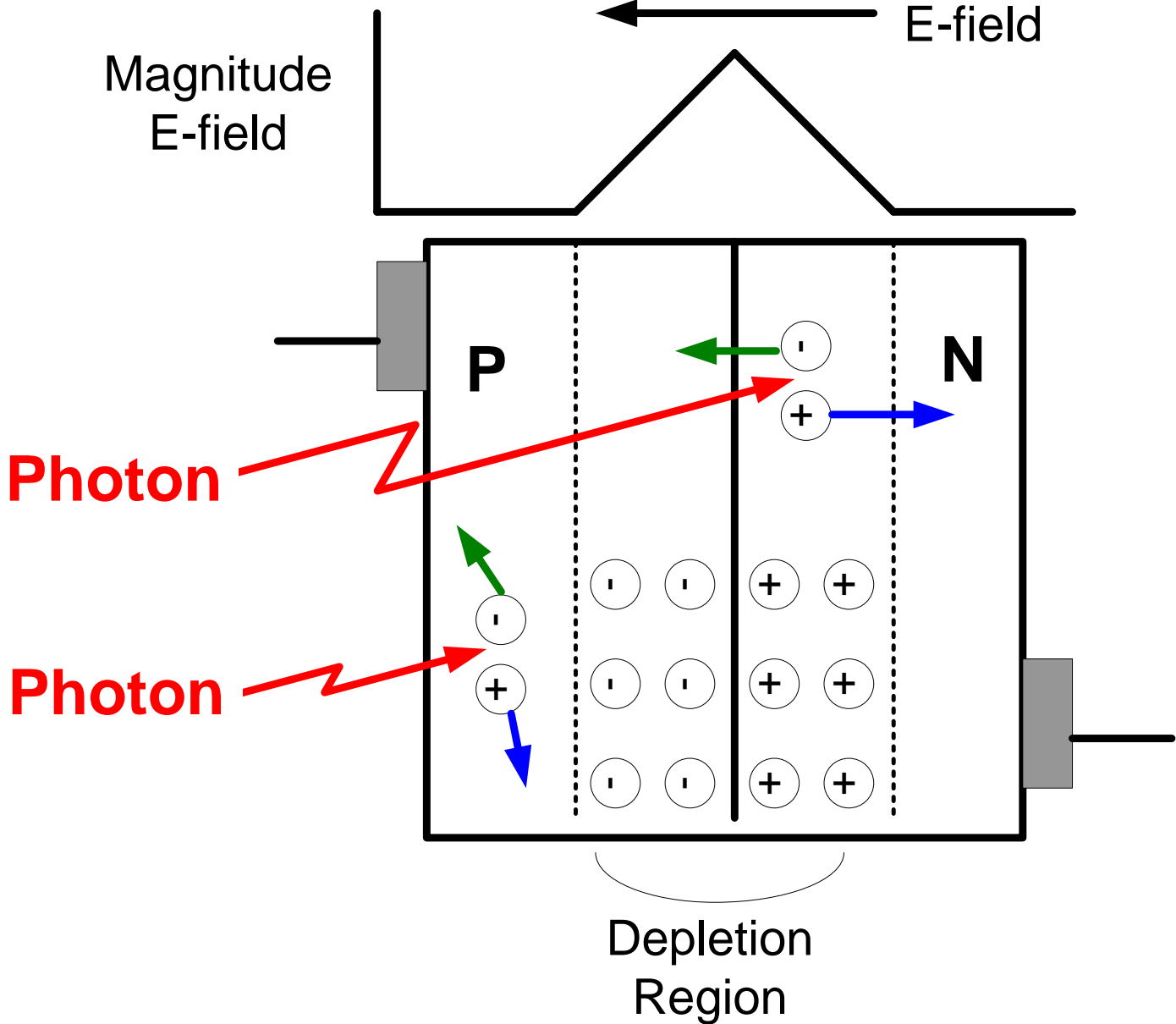

Photodiode model

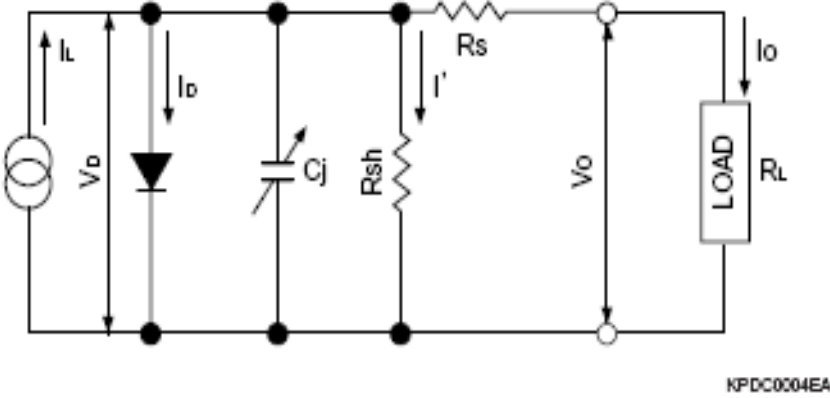


Figure 1.4 Photodiode Equivalent Circuit

KPDC0004EA

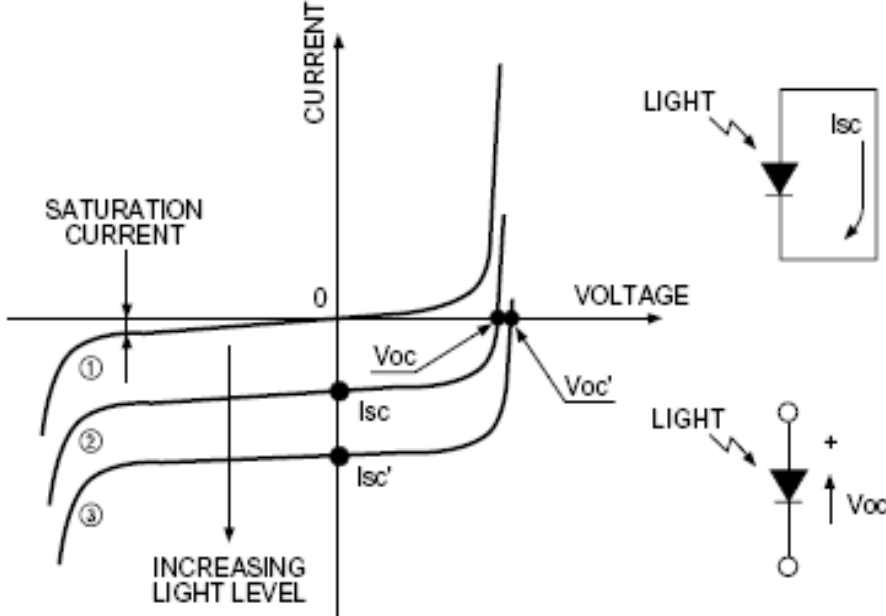


Figure 1.5 Current VS. Voltage Characteristics

KPDC0005EA

Output current is given as :

$$I_o := I_L - I_D - I' = I_L - I_S \left(e^{\frac{eV_D}{kT}} - 1 \right) - I'$$

I_S : Photodiode reverse saturation current

e : electron charge

k : Boltzmann's constant

T : Absolute temperature of the photodiode

I_L = light current


I_D = dark current

I' = leakage current

The open circuit voltage V_{oc} is the output voltage when I_o equals 0. Thus V_{oc} becomes:

$$V_{oc} := \frac{kT}{c} \ln \left(\frac{I_L - I'}{I_S} + 1 \right)$$

Photodiode and Control Source TINA model

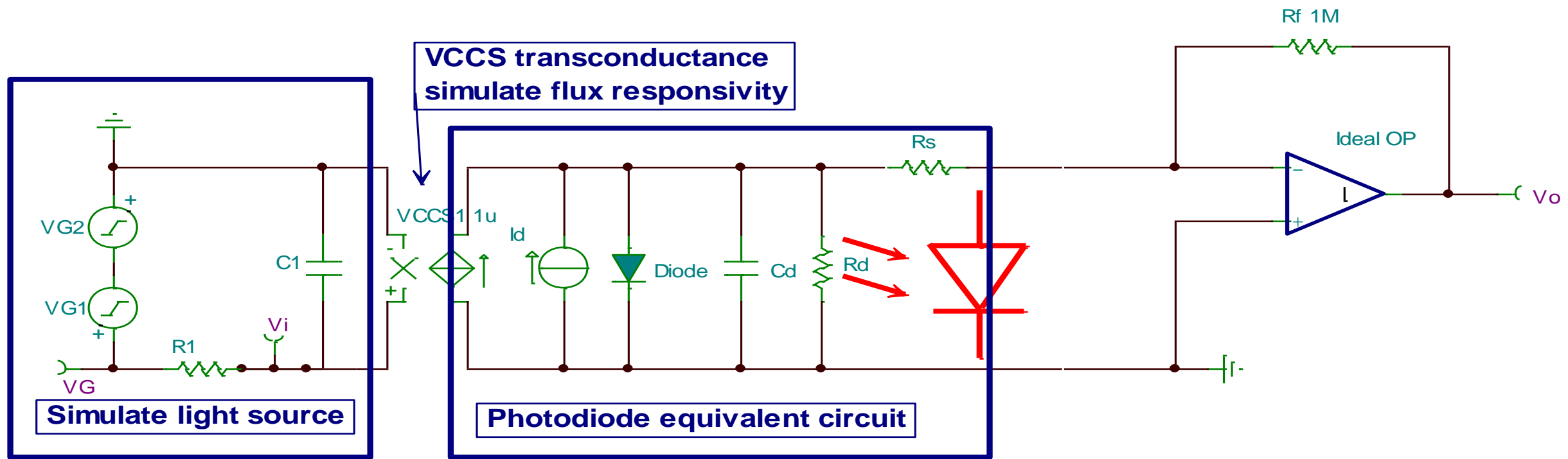

Light exciting source:


- 1) Use VG1 and VG2 voltage sources to simulate light power wave.
- 2) Use R1 and C1 shape light signal
- 3) The Voltage Control Current Source (VCCS1) simulates photodiode sensitivity.

Photodiode Equivalent Circuit:

- 1), Current Source I_d simulates Dark current
- 2), Diode is a ideal diode
- 3), Cd and Rd simulate photodiode's junction capacitor and dark Resistance.
- 4), Rs is series resistor, which is far smaller than Rd.

Photodiode Noise Theory

Photo-Diode Amp Noise Model

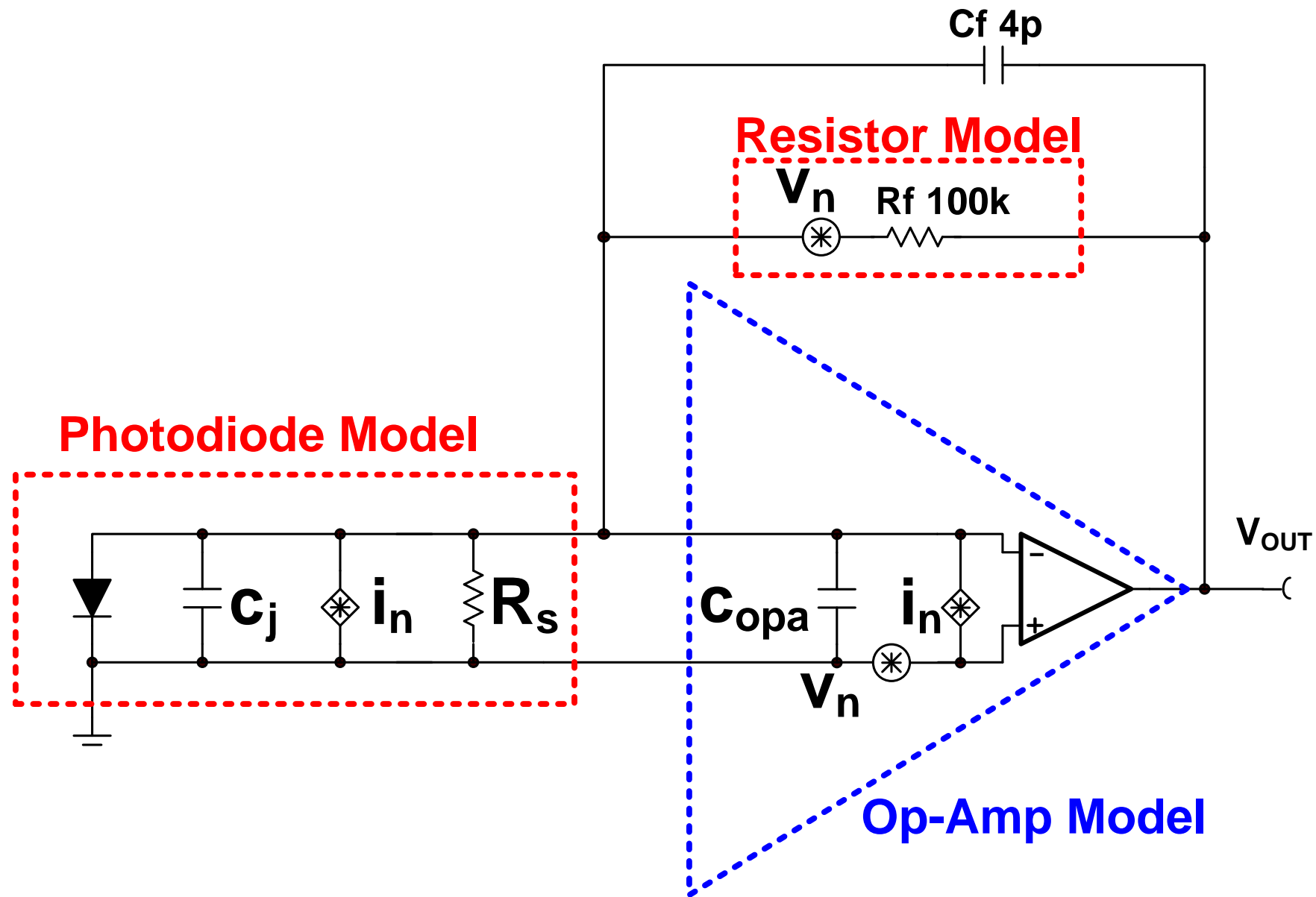

Photodiode noise

Thermal (Johnson Noise)

$$i_j = \sqrt{\frac{4k_b \cdot T_n}{R_{sh}}}$$

k_b Boltzmann constant $1.38 \cdot 10^{-23} \text{ J/K}$

q Electron Charge $1.6 \cdot 10^{-19} \text{ C}$

T_n Temperature in Kelvin (25C)

f_p Transconductance bandwidth

R_{sh} Shunt Resistance in photodiode

I_D Dark Current in photodiode

I_L Photo current in photodiode

Shot noise (dark)


$$i_{sD} = \sqrt{2q \cdot I_D}$$

Shot noise (w . Light)

$$i_{sL} = \sqrt{2q \cdot I_L}$$

Total Diode Current Noise
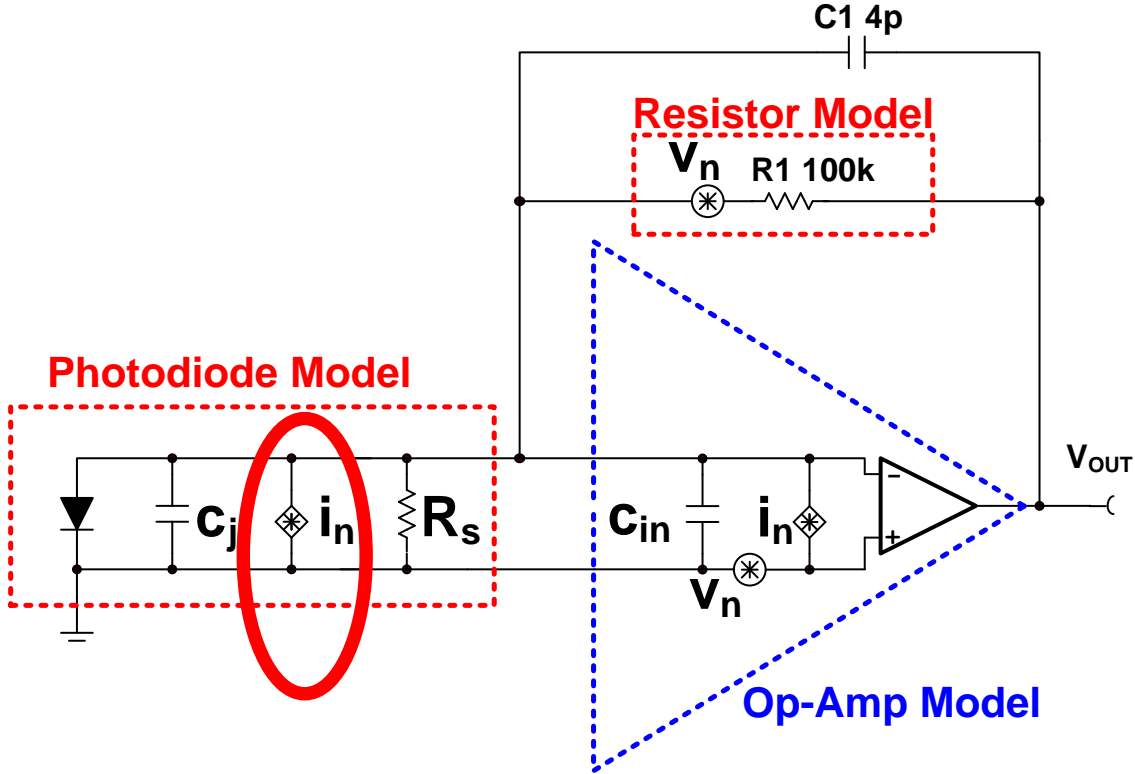
$$i_n = \sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2}$$






Noise Gain

Simplify the model to compute Noise Gain

$$\text{Noise_Gain} = \frac{V_{\text{out}}}{V_n}$$

Gain seen by the noise voltage source.

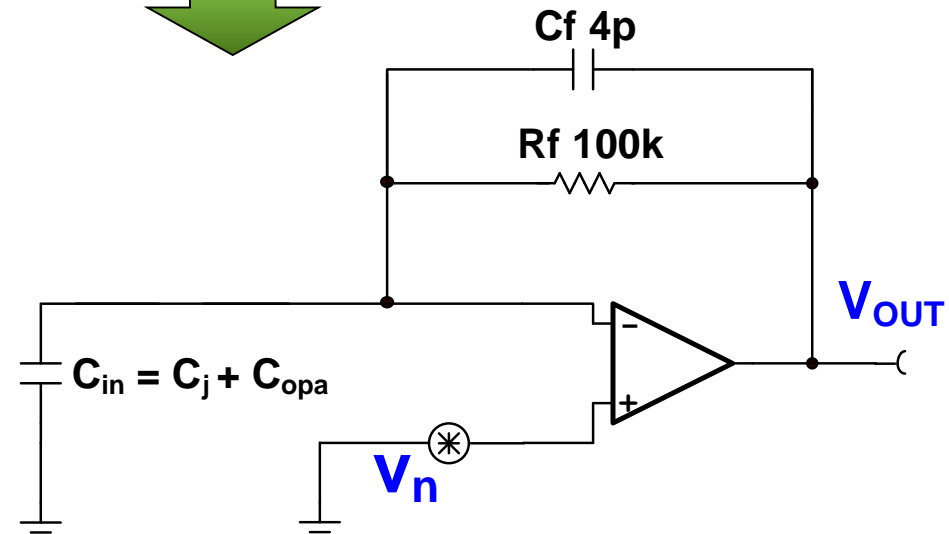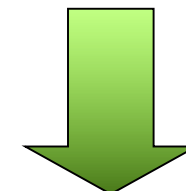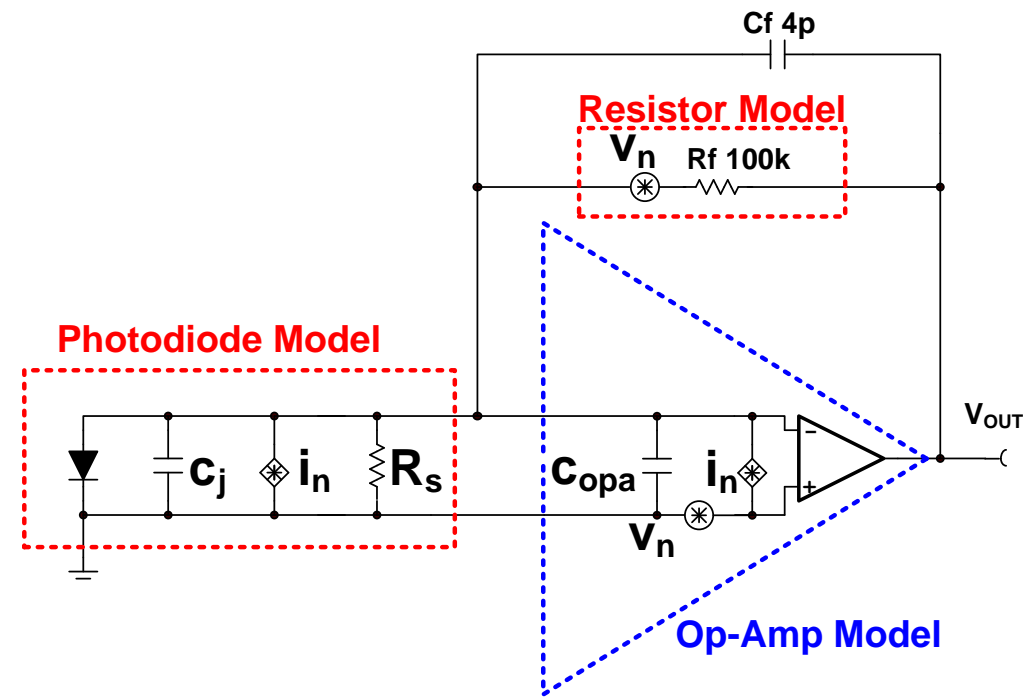

Noise Gain

Nodal Analysis on transimpedance amp

$$\frac{V_n}{\frac{1}{s \cdot C_{in}}} + \frac{(V_n - V_{out})}{R_f} + \frac{V_n - V_{out}}{\frac{1}{s \cdot C_f}} = 0$$

Solve for noise gain V_{out} / V_n



$$\frac{V_{out}}{V_n} = \frac{R_f \cdot (C_f + C_{in}) \cdot s + 1}{C_f \cdot R_f \cdot s + 1}$$

The numerator contains a **Zero**


$$f_z = \frac{1}{2\pi R_f \cdot (C_f + C_{in})}$$

The denominator contains a **Pole**

$$f_p = \frac{1}{2\pi R_f \cdot C_f}$$

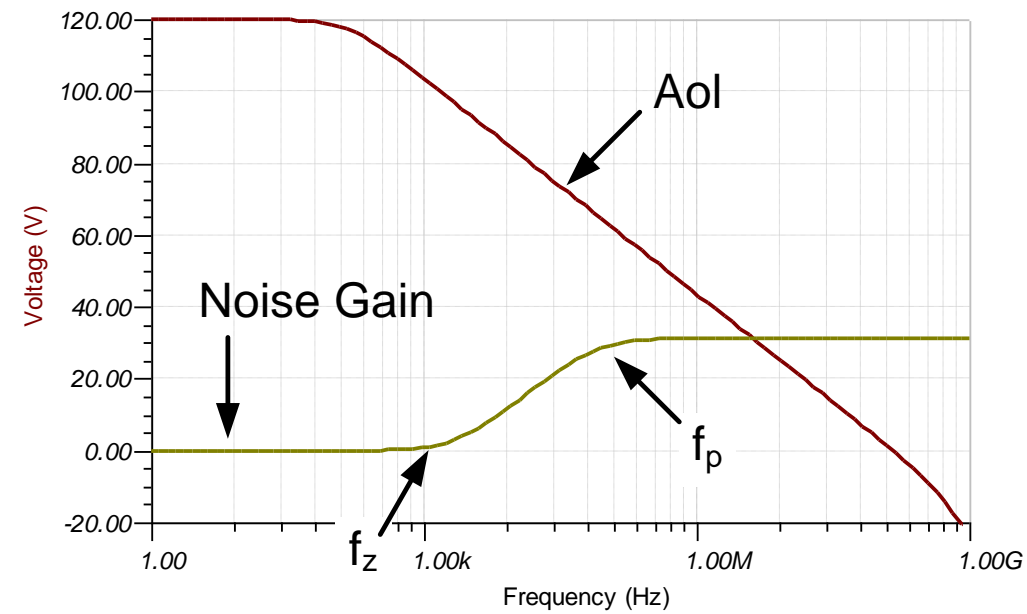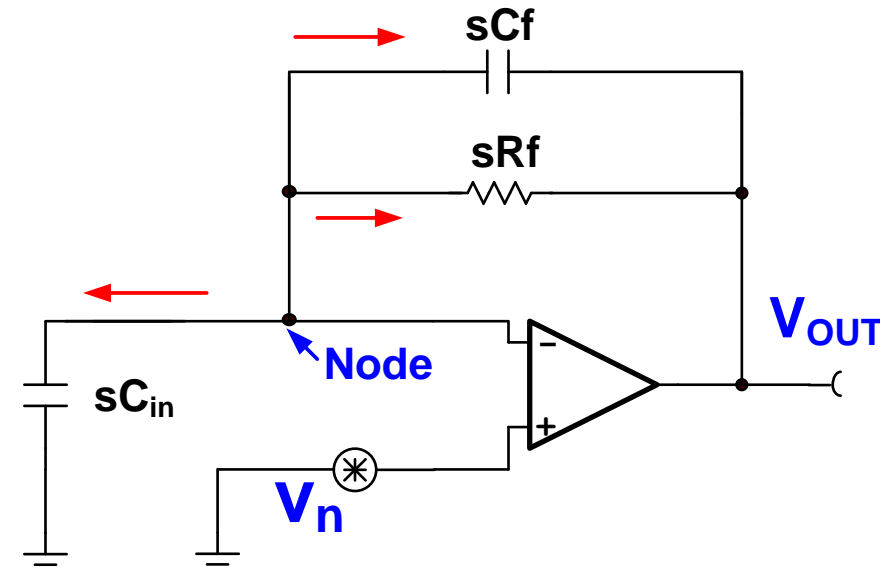

Noise Gain

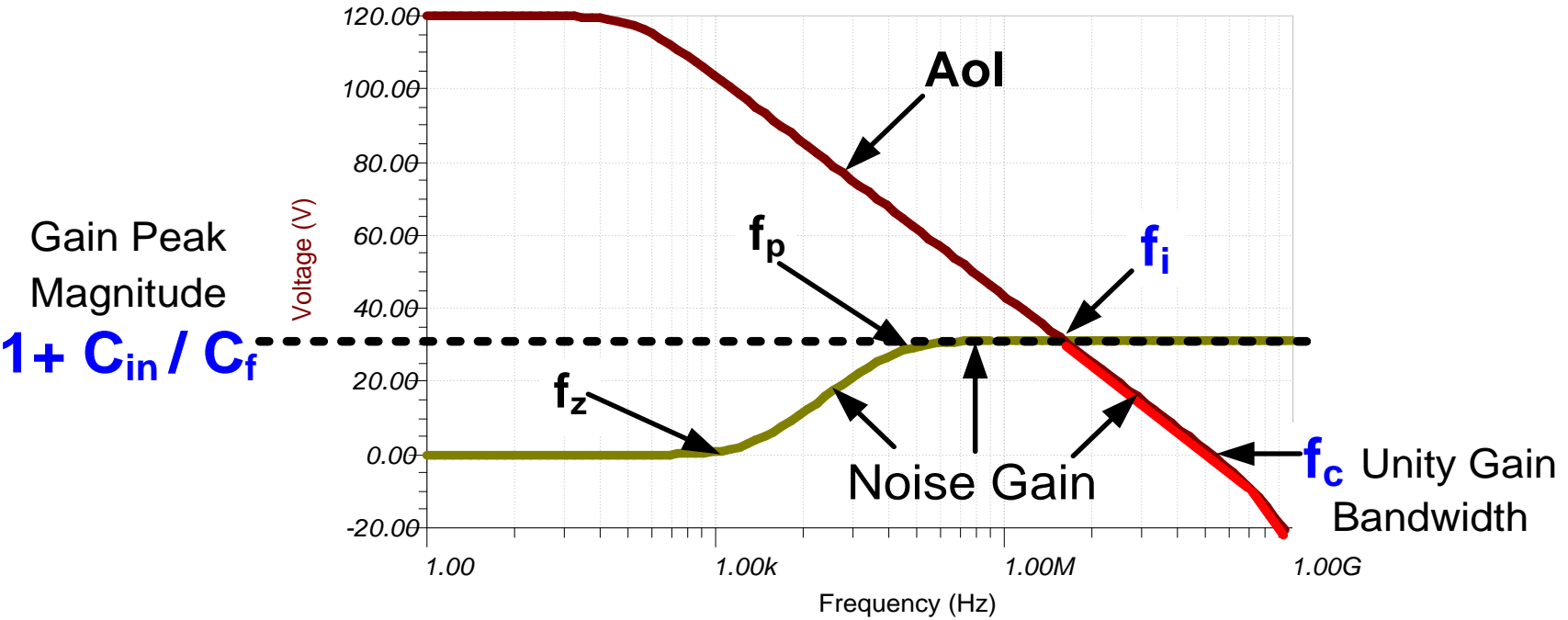

$$f_i = \frac{C_f}{C_i + C_f} \cdot f_c$$

Intersection of the noise gain curve with the Aol Curve

$$f_c$$





Unity Gain Bandwidth from Op-Amp Data Sheet

$$GPM = 1 + \frac{C_{in}}{C_f}$$


Gain Peak Magnitude

Noise Gain

Op-Amp
Voltage Noise
(Data Sheet)

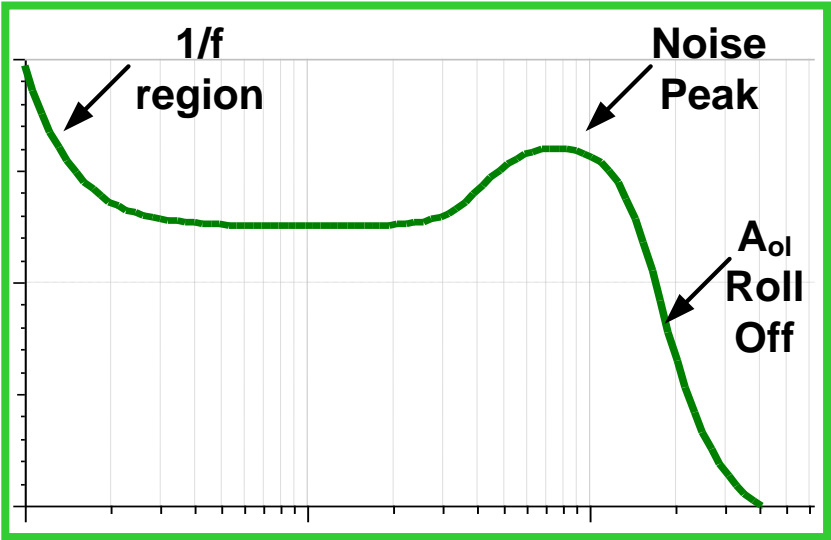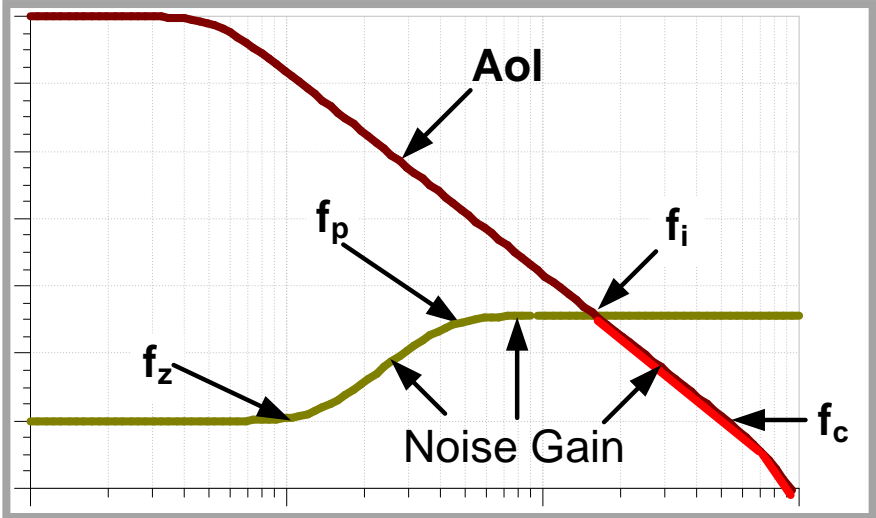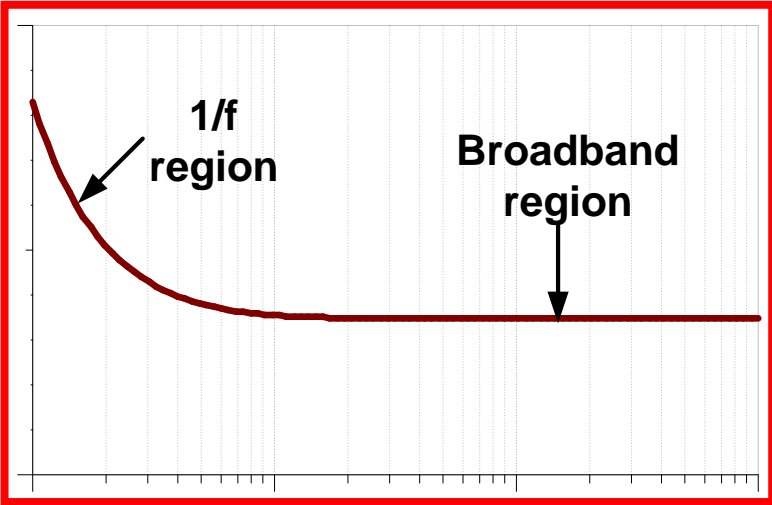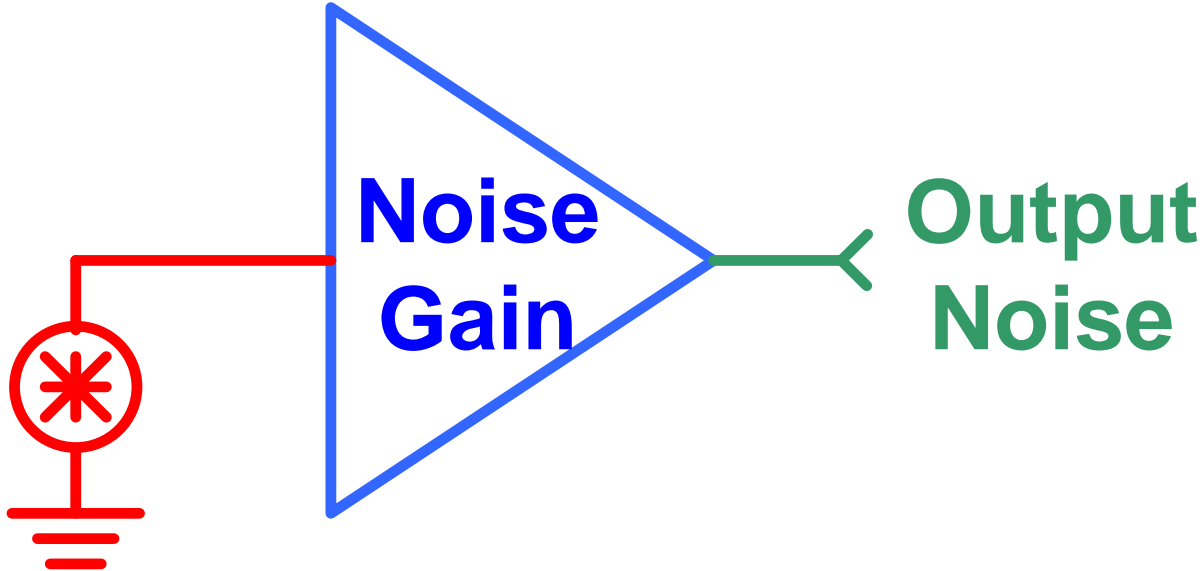

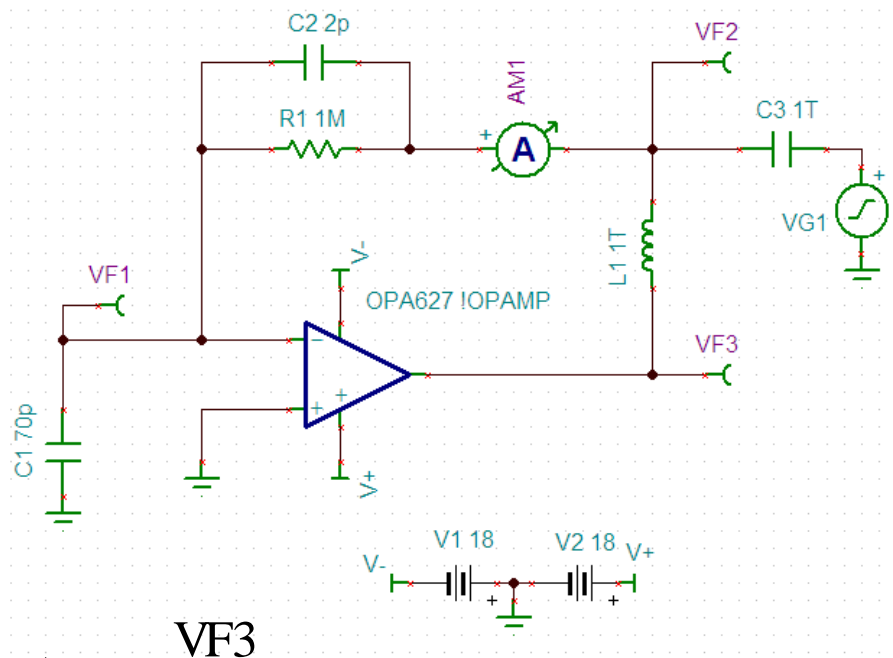Simulating Noise gain and noise bandwidth




- Break the loop to measure Aol, 1/B, and I to V Gain

$$A_{ol} = \frac{VF3}{VF1}$$


$$\text{Noise_Gain} = \frac{1}{\beta} = \frac{VF2}{VF1}$$

$$I_to_V_Gain = \frac{VF3}{AM1}$$

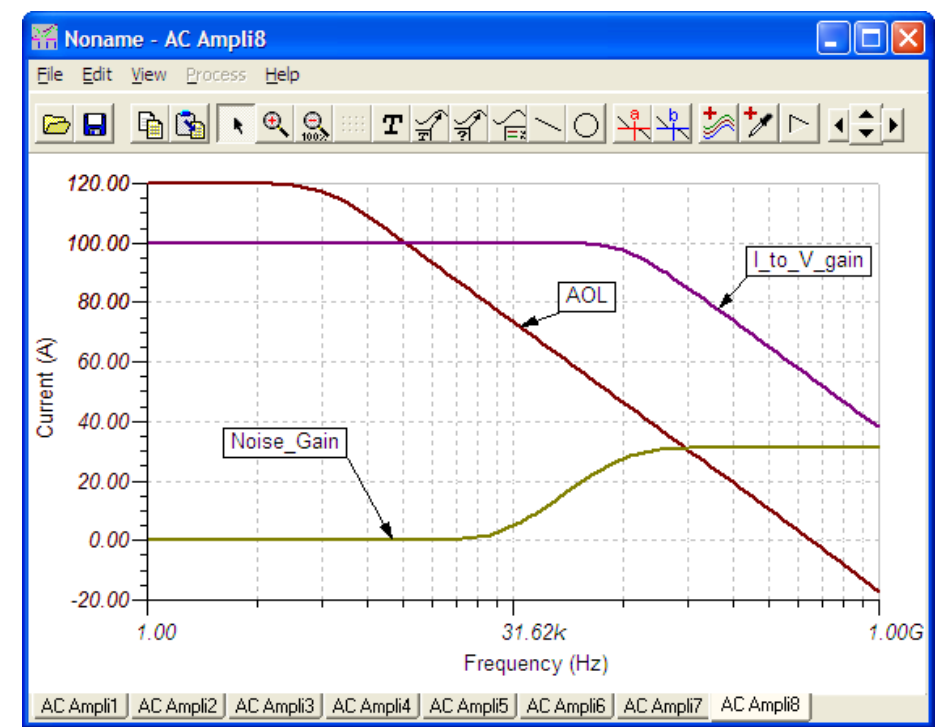

Voltage Noise e_{ni} , e_{no} and E_n
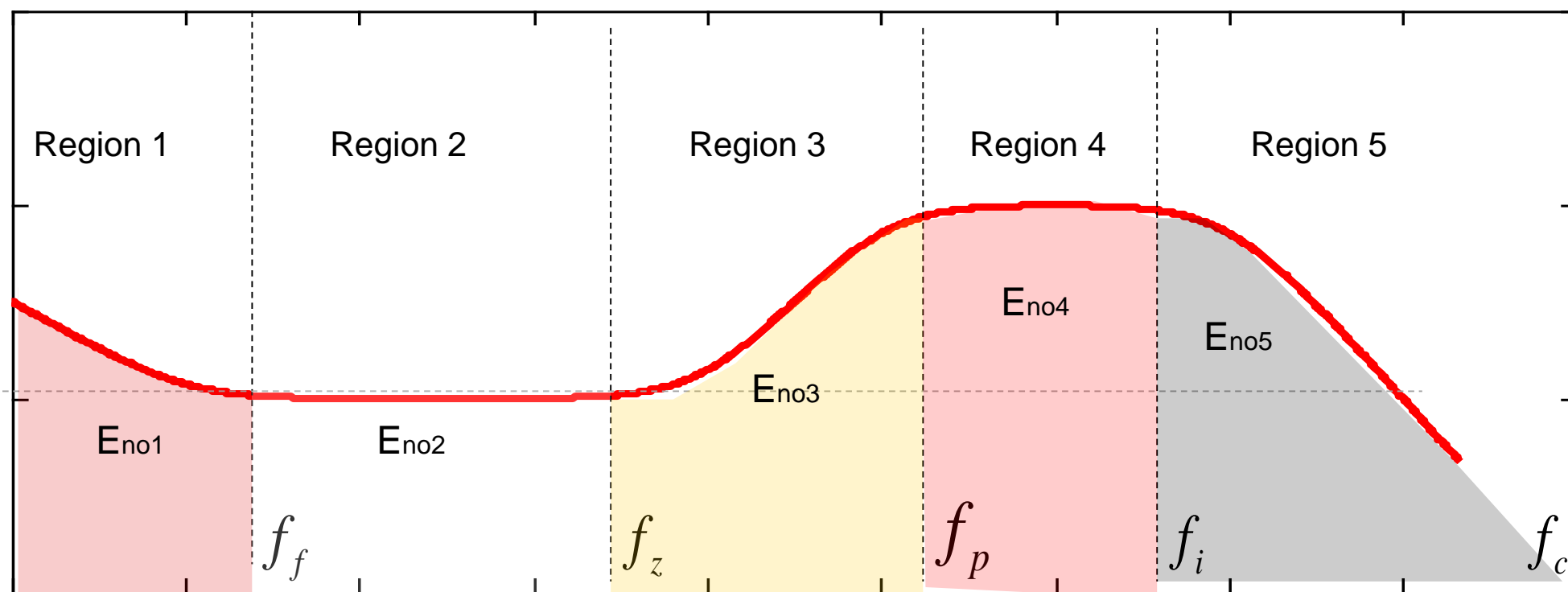
$$e_{no} = A_n \cdot e_{ni} = \frac{\left(1 + \frac{s}{\omega_z}\right) \cdot \sqrt{1 + \frac{\omega_f}{s}}}{\left(1 + \frac{s}{\omega_p}\right) \cdot \left(1 + \frac{s}{\omega_i}\right)}$$



Voltage Noise e_{ni} , e_{no} and E_{no}

Region 1 noise:
$$E_{noe1}^2 = \int_{f_L}^{f_f} \frac{e_{nif}^2 \cdot f_f}{f} d_f = e_{nif}^2 f_f \ln \frac{f_f}{f_L}$$

Region 2 noise:
$$E_{noe2}^2 = \int_{f_f}^{f_z} e_{nif}^2 d_f = e_{nif}^2 (f_z - f_f)$$


Region 3 noise:
$$E_{noe3}^2 = \int_{f_z}^{f_p} \frac{e_{nif}^2 \cdot f^2}{f_z^2} d_f = \left(\frac{e_{nif}}{f_z} \right)^2 \frac{f_p^3 - f_z^3}{3}$$

Region 4 noise:
$$E_{noe4}^2 = \int_{f_p}^{f_i} \left(\frac{e_{nif}}{\beta} \right)^2 d_f = \left(e_{nif} \cdot \frac{C_i + C_f}{C_f} \right)^2 (f_i - f_p)$$


Region 5 noise:
$$E_{noe5}^2 = \int_{f_i}^{\infty} \left(\frac{e_{nif} f_c}{f} \right)^2 d_f = \frac{(e_{nif} f_c)^2}{f_i}$$

Total voltage noise:
$$E_{noe}^2 = E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2$$

Voltage Noise e_{ni} , e_{no} and E_{no}

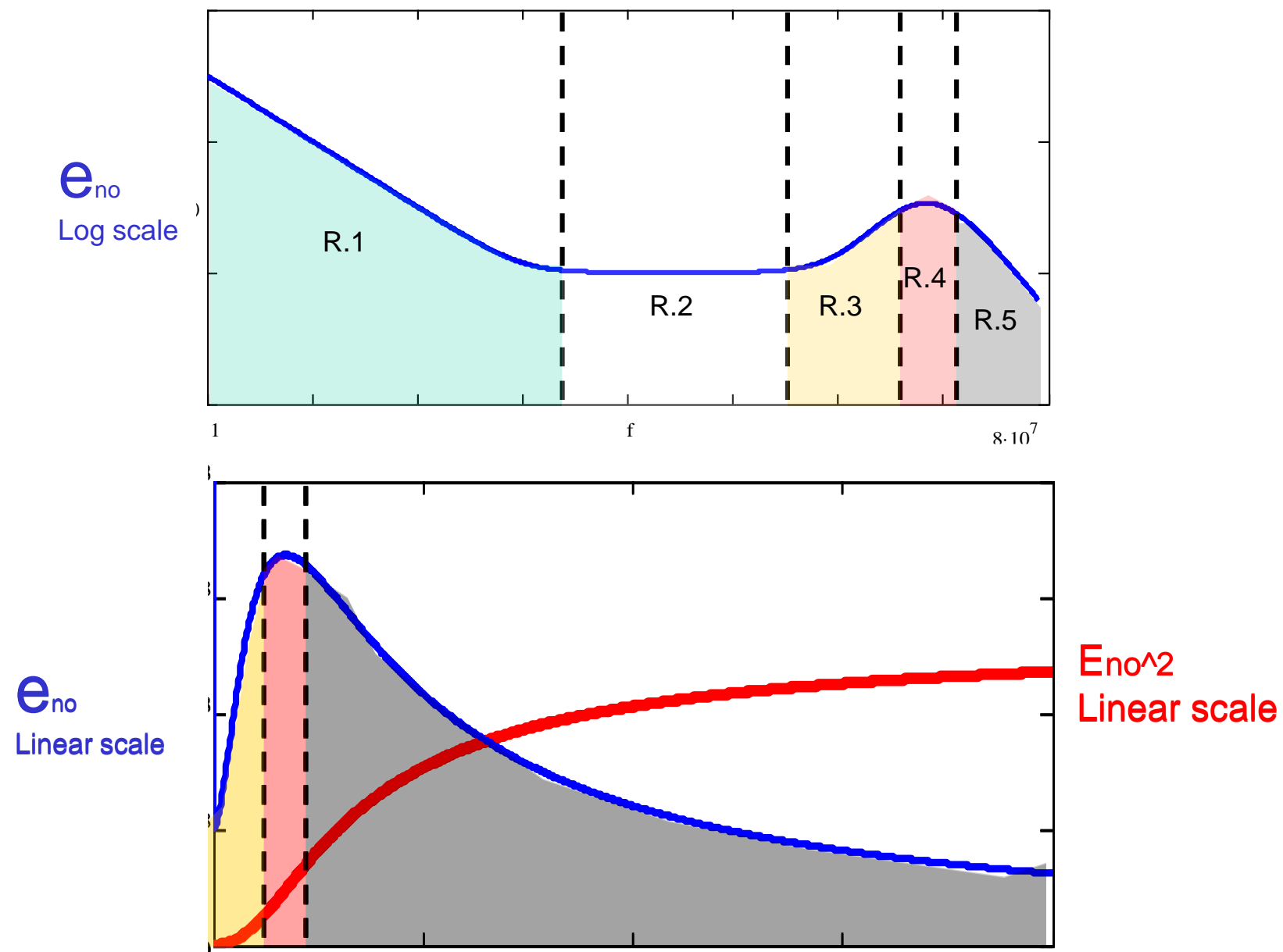


Resistor Noise and Current Noise

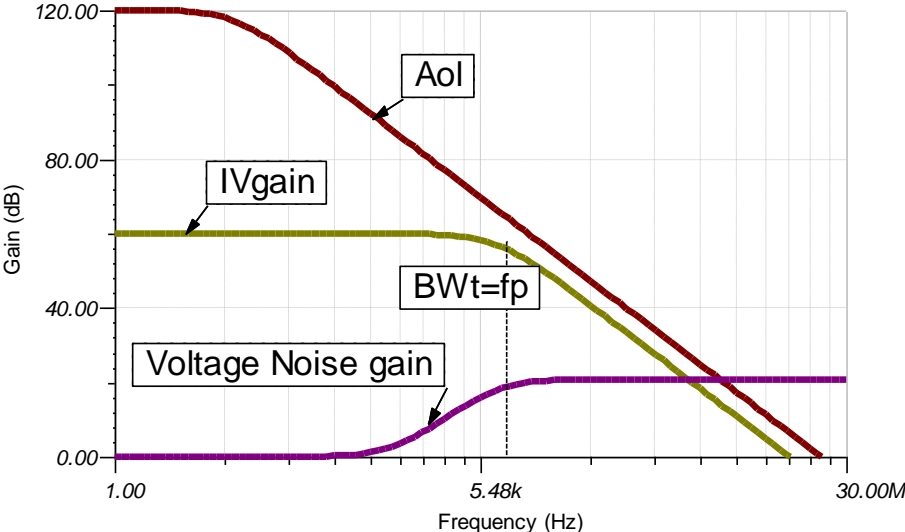

Current noise and resistor noise are limited by the transimpedance (I-V gain) bandwidth

Poles	Kn
1	1.57
2	1.22
3	1.16

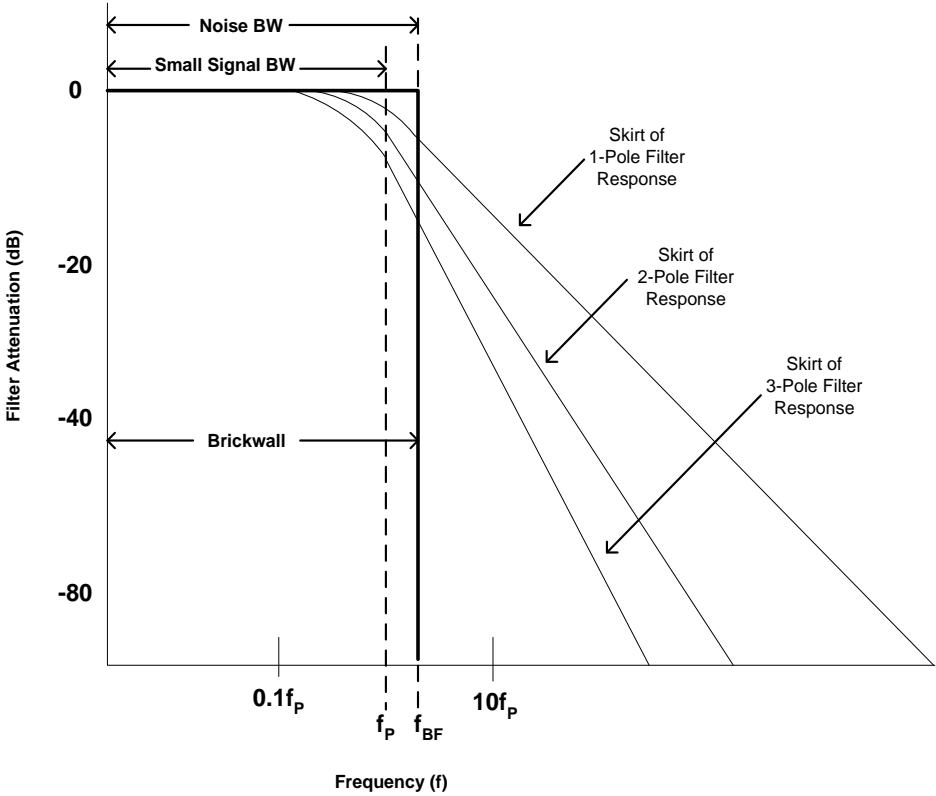


$$BW_n = K_n \cdot f_p$$

$$E_{noR} = \sqrt{4K \cdot T \cdot R_f \cdot BW_n}$$


$$E_{noI} = i_{ni} \cdot R_f \cdot BW_n$$

Bandwidth and Stability

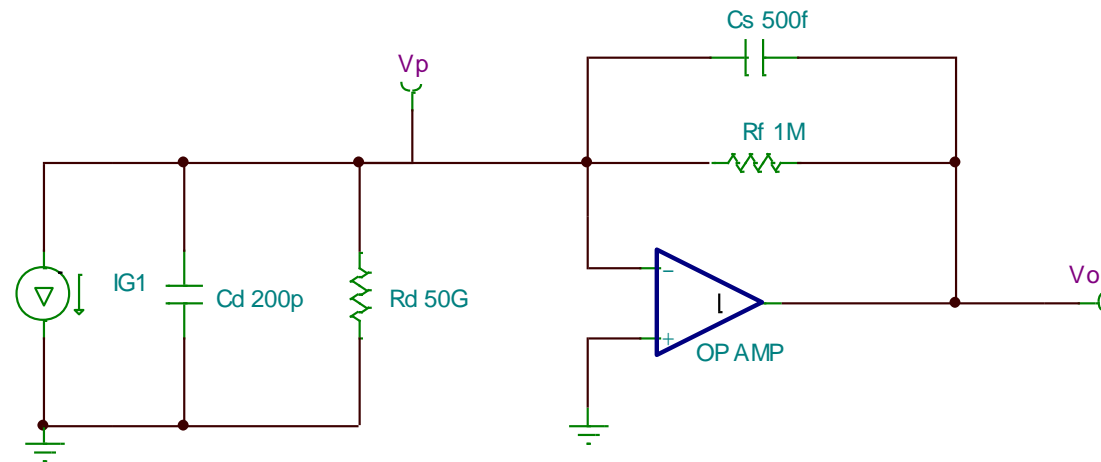Parasitic Capacitance Limits the Bandwidth



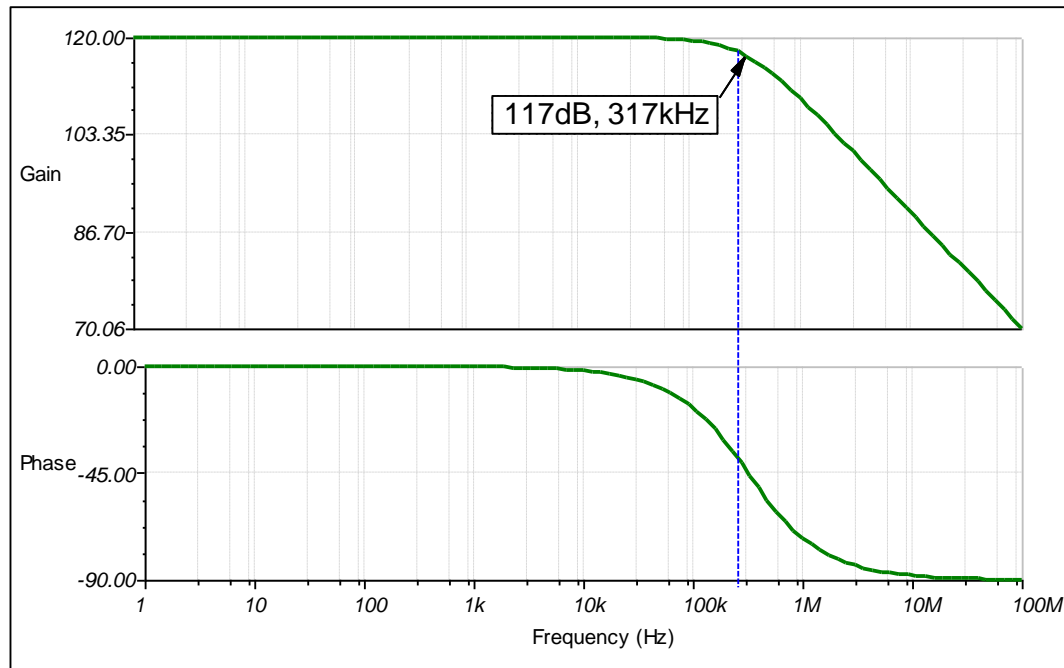
$$f_p = \frac{1}{2\pi R_f \cdot C_f} = 318\text{kHz}$$




- Max bandwidth with Min C_f
- Low C_f may be unstable
- Wide BW increases noise
- As shown $C_f=C_s$ (stray cap)


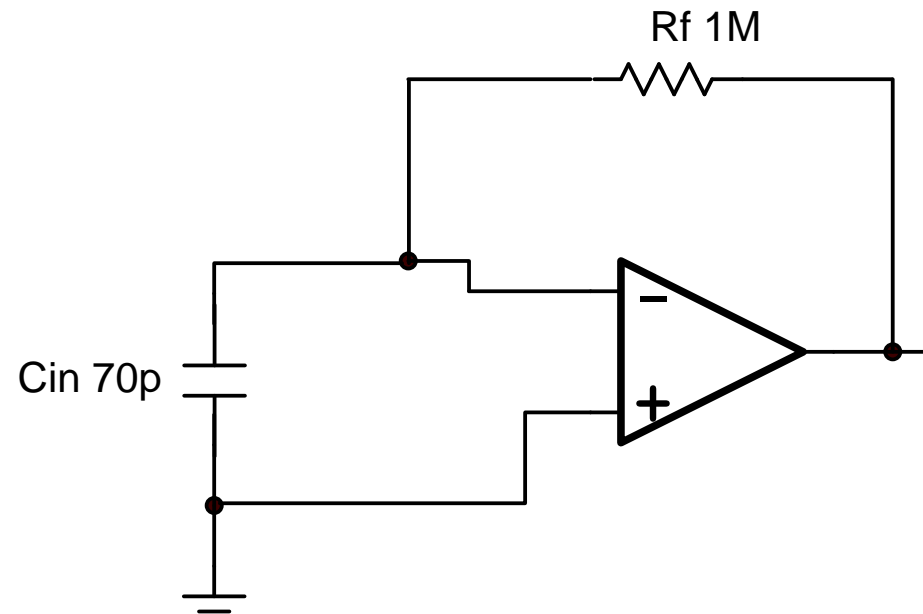
Feedback Capacitance Required for Stability



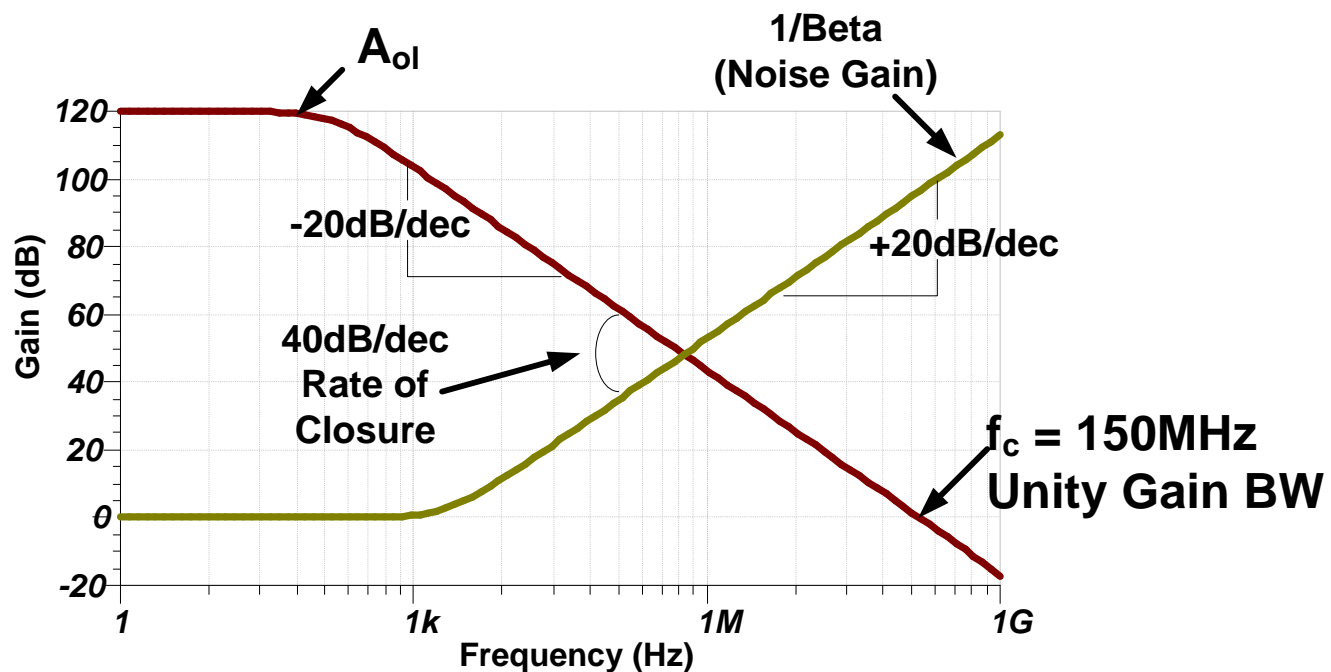- Noise Gain is key to stability
- Also called $1/\text{Beta}$ (in stability analysis)
- ROC = Rate of Closure
- $\text{ROC} = (\text{Aol slope}) - (1/\text{Beta slope})$
- Unstable when $\text{ROC} > 20\text{dB/decade}$





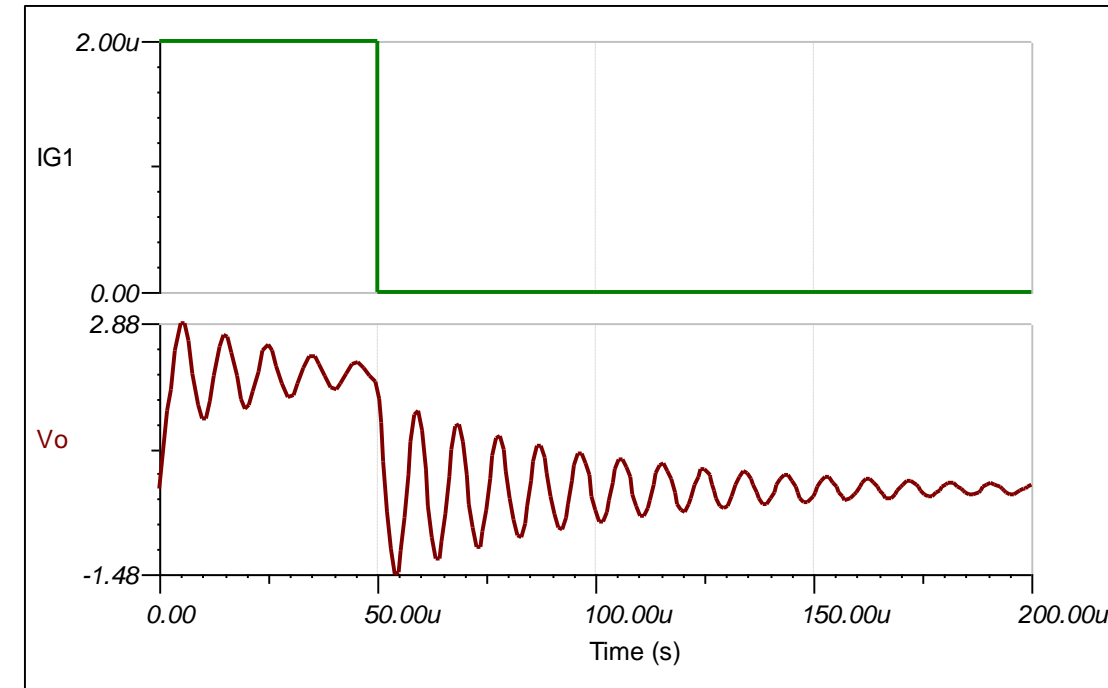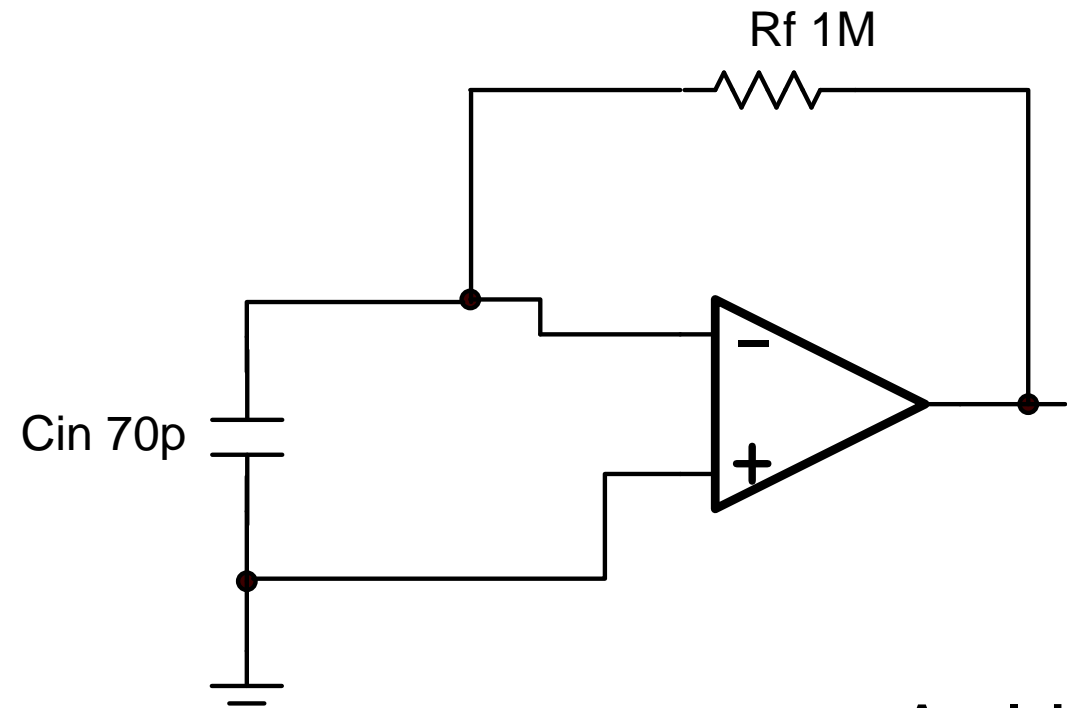Feedback Capacitance Required for Stability



Applying a Step Input shows instability at output

Choosing a Minimum Cf for Stability

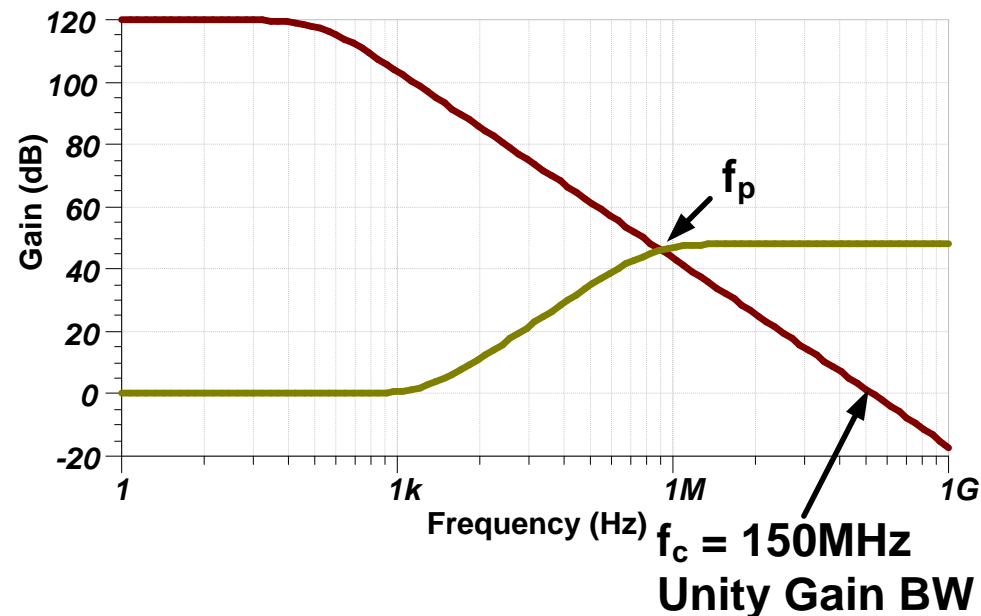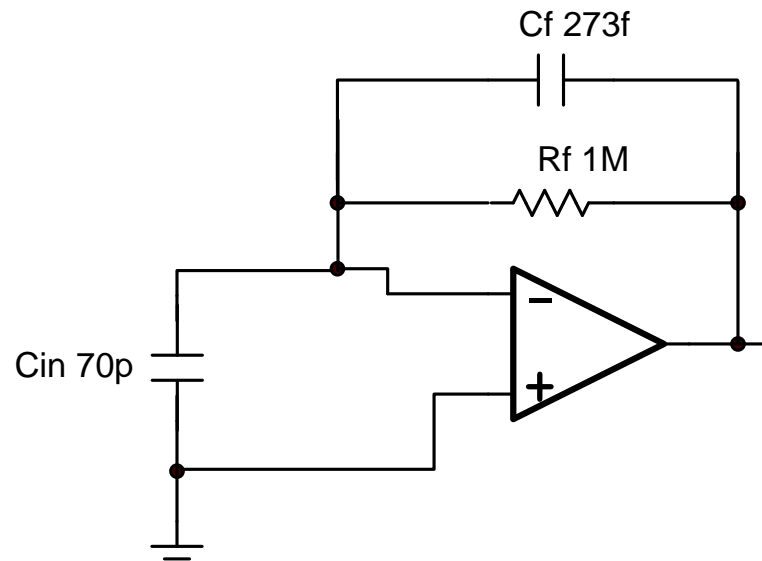

$$f_c = 150MHz$$

Op-amp Unity Gain Bandwidth

$$C_{in} = 70pF$$

Total input capacitance

$$R_f = 1M\Omega$$

Feedback resistance

$$C_f = \sqrt{\frac{C_{in}}{2\pi \cdot R_f \cdot f_c}} = 272.5fF$$

Simplified equation for minimum feedback cap
Assumes $C_{in} \gg C_f$

$$C_c = \frac{1}{2\pi \cdot R_f \cdot f_c}$$


Intermediate calculation used in more exact formula

$$C_{fe} = \frac{C_c}{2} \cdot \left(1 + \sqrt{1 + \frac{4C_{in}}{C_c}} \right) = 273.1fF$$

More exact formula for feedback capacitance

OPA827 Hand Calculation

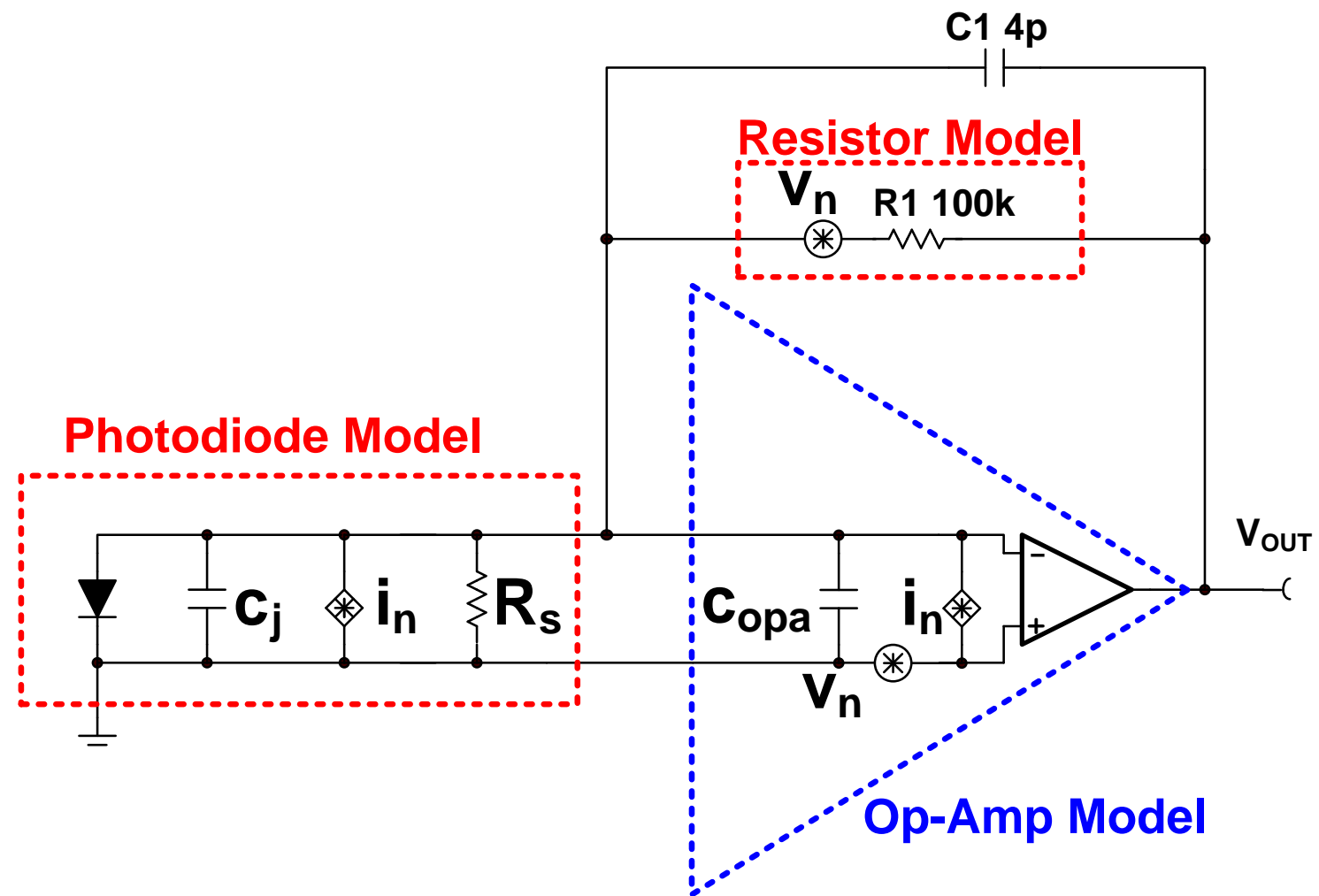Noise Model for Simple Transimpedance Amp




Example Photodiode: PDB-C158

ABSOLUTE MAXIMUM RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	PARAMETER	MIN	MAX	UNITS
V_{BR}	Reverse Voltage		50	V
T_{STG}	Storage Temperature	-40	+100	°C
T_O	Operating Temperature	-40	+80	°C
T_S	Soldering Temperature*		+260	°C

* 1/16 inch from case for 3 seconds max.

SPECTRAL RESPONSE

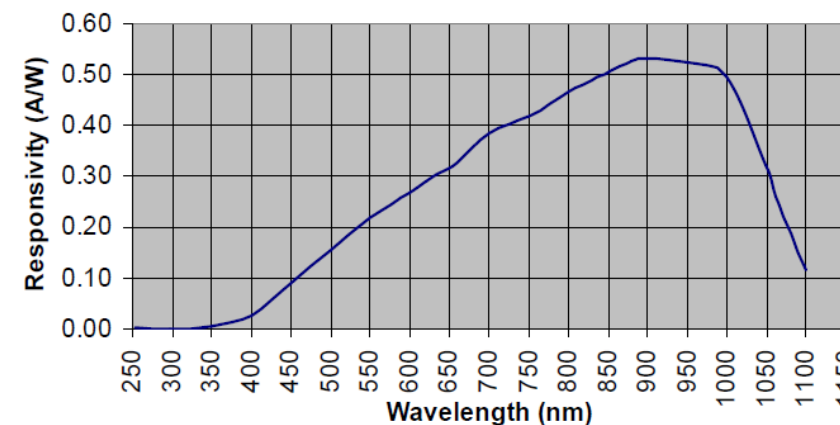

ELECTRO-OPTICAL CHARACTERISTICS RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	CHARACTERISTIC	TEST CONDITIONS	MIN	TYP	MAX	UNITS
I_{SC}	Short Circuit Current	$H = 100 \text{ fc}, 2850 \text{ K}$	100	145		μA
I_D	Dark Current	$V_R = 10 \text{ V}$		2	30	nA
R_{SH}	Shunt Resistance	$V_R = 10 \text{ mV}$	100	150		$\text{M}\Omega$
C_J	Junction Capacitance	$V_R = 10 \text{ V}, f = 1 \text{ MHz}$		10	25	pF
λ_{range}	Spectral Application Range	Spot Scan	400		1100	nm
V_{BR}	Breakdown Voltage	$I = 10 \mu\text{A}$	30	75		V
NEP	Noise Equivalent Power	$V_R = 10 \text{ V} @ \lambda = \text{Peak}$		4.4×10^{-14}		$\text{W}/\sqrt{\text{Hz}}$
t_r	Response Time	$R_L = 1 \text{ K}\Omega, V_R = 10 \text{ V}$		50		nS

Unfortunately C_j is not specified at $V_r=0\text{V}$.

We called the manufacturer for this info $C_j=70\text{pF}$ for $V_r=0\text{V}$

Calculate Diode Current Noise

Thermal (Johnson Noise)

$$\sqrt{\frac{4k_b \cdot T_n}{R_{sh}}} = 10.472 \times 10^{-15} \frac{A}{\sqrt{Hz}}$$

Shot noise (dark)

$$\sqrt{2q \cdot I_D} = 25.314 \times 10^{-15} \cdot \frac{A}{\sqrt{Hz}}$$

Shot noise (w . Light)

$$i_{sL} := \sqrt{2q \cdot I_L} = 0$$

Total Diode Current Noise

$$\sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2} = 27.395 \times 10^{-15} \cdot \frac{A}{\sqrt{Hz}}$$

$$k_b := 1.3810^{-23} \frac{J}{K}$$

$$q := 1.60210^{-19} C$$

$$T_n := 298K$$

$$f_p := 397.887 \times 10^3 Hz$$

$$R_{sh} := 150 \cdot 10^6 \Omega$$

$$I_D := 2 \cdot 10^{-9} A$$

$$I_L := 0A$$

Boltzmann constant

One electron Charge


Temperature in Kelvin (25C)

Transconductance bandwidth


Shunt Resistance in photodiode

Dark Current in photodiode

Photo current in photodiode
(our measurements are dark)

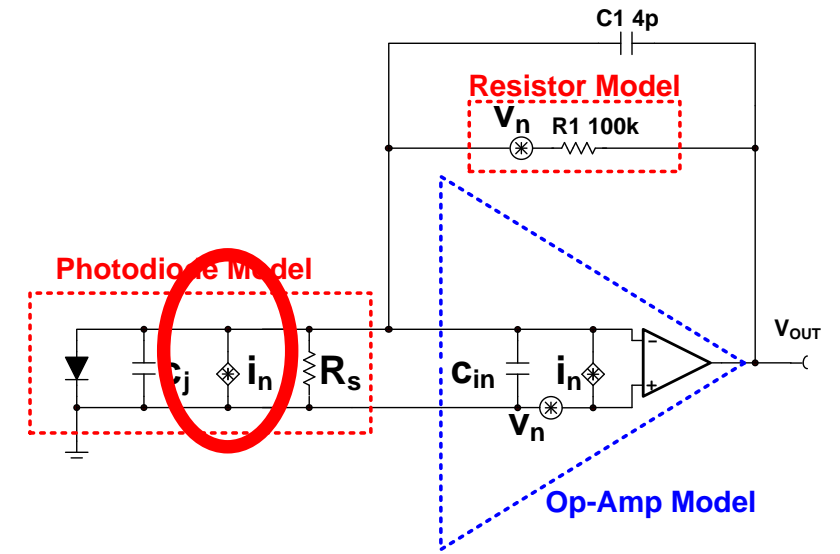

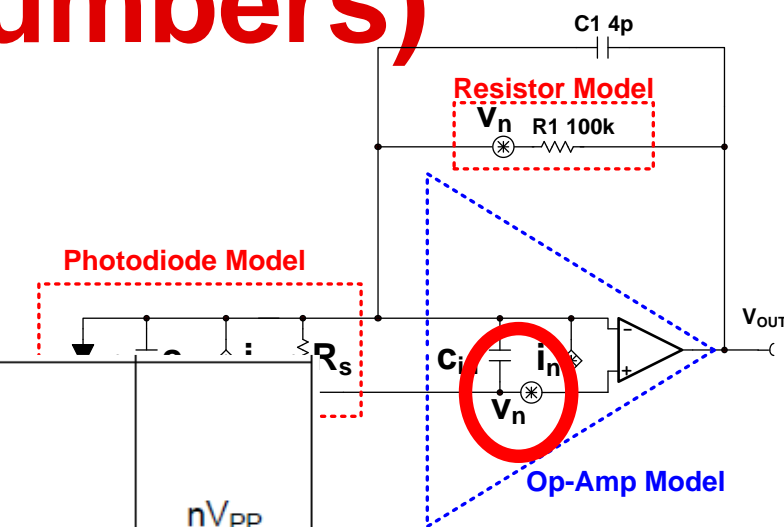OPA827 Noise Hand Calculation (key numbers)



NOISE								
Input Voltage Noise:								
f = 0.1Hz to 10Hz	e_n	$V_S = \pm 18V, V_{CM} = 0V$		250		250	nV _{PP}	
Input Voltage Noise Density:								
f = 1kHz	e_n	$V_S = \pm 18V, V_{CM} = 0V$		4		4	nV/ \sqrt{Hz}	
f = 10kHz	e_n	$V_S = \pm 18V, V_{CM} = 0V$		3.8		3.8	nV/ \sqrt{Hz}	
Input Current Noise Density:								
f = 1kHz	i_n	$V_S = \pm 18V, V_{CM} = 0V$		2.2		2.2	fA/ \sqrt{Hz}	
INPUT IMPEDANCE								
Differential				$10^{13} \parallel 9$		$10^{13} \parallel 9$	$\Omega \parallel pF$	
Common-Mode				$10^{13} \parallel 9$		$10^{13} \parallel 9$	$\Omega \parallel pF$	
OPEN-LOOP GAIN								
Open-Loop Voltage Gain	A_{OL}	$(V-)+3V \leq V_O \leq (V+)-3V, R_L = 1k\Omega$	120	126		120	126	dB
Over Temperature		$(V-)+3V \leq V_O \leq (V+)-3V, R_L = 1k\Omega$	114			114		dB
FREQUENCY RESPONSE								
Gain-Bandwidth Product	GBW	G = +1		22		22		MHz

OPA827 Noise Hand Calculation

$C_j := 70\text{pF}$ Photodiode Junction Capacitance
(from photodiode manufacturer)

$C_{\text{opa}} := 18\text{pF}$ Opamp input capacitance
(OPA827 Data Sheet)

$C_i := C_j + C_{\text{opa}}$ Total input capacitance

$f_c := 22\text{MHz}$ Unity Gain Bandwidth
(OPA827 Data Sheet)



$R_f := 100\text{k}\Omega$ Feedback resistance

$C_f := 4\text{pF}$ Feedback capacitor

$e_{\text{nif}} := 3.8 \frac{\text{nV}}{\sqrt{\text{Hz}}}$ Broadband Noise Spectral Density
(OPA827 Data Sheet)

$f_L := .1\text{Hz}$ Lower bound on frequency (1/f region)
(arbitrary lower bound of frequency)

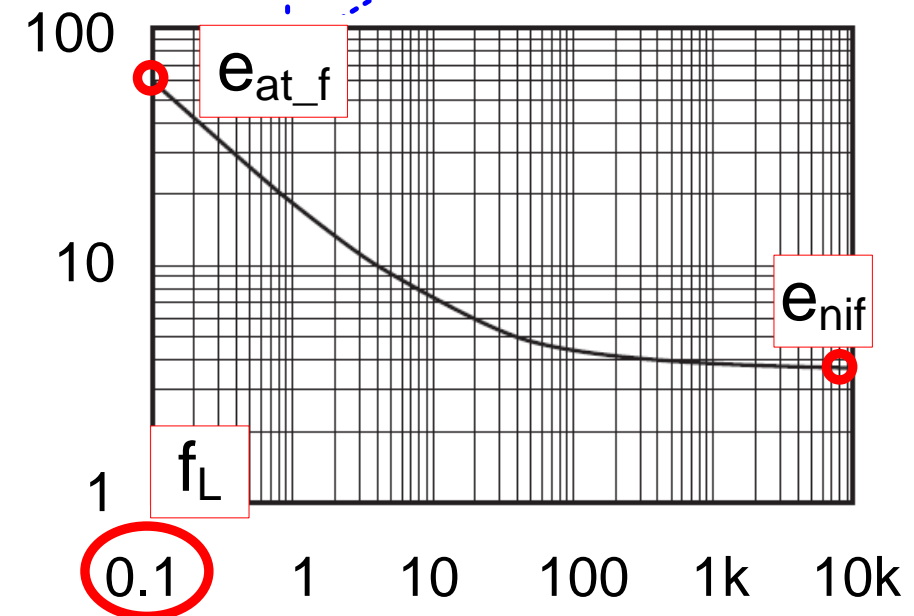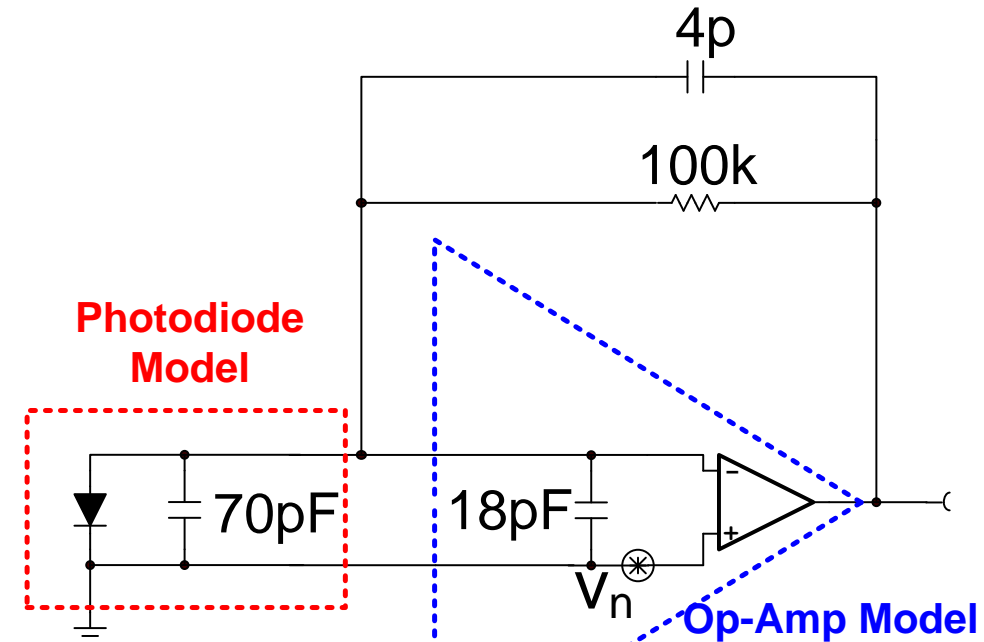
$e_{\text{at}_f} := 60 \frac{\text{nV}}{\sqrt{\text{Hz}}}$ Flicker noise measured at f_L
(OPA827 Data Sheet Noise Curve)



1/f (flicker) Noise Corner

$$e_{\text{fnorm}} := e_{\text{at_f}} \sqrt{f_L} = 18.974 \times 10^{-9} \text{ V}$$
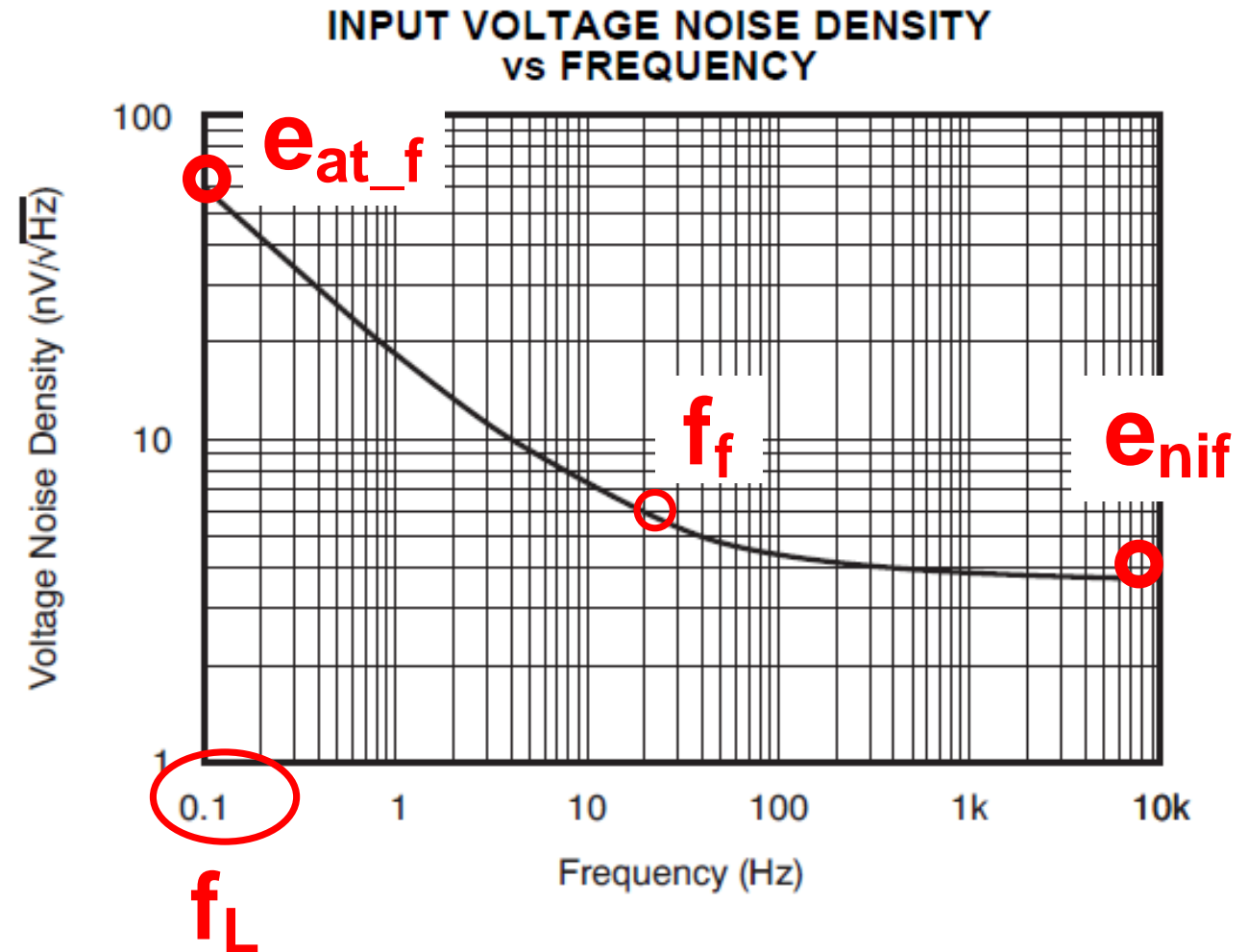
$$f_f := \frac{e_{\text{fnorm}}^2}{e_{\text{nif}}^2} = 24.93 \text{ Hz}$$



Output Noise from OPA Noise Voltage

$$E_{noe1} := \sqrt{e_{nif}^2 \cdot f_f \cdot \ln\left(\frac{f_f}{f_L}\right)} = 44.573 \times 10^{-9} \text{ V}$$


$$E_{noe2} := \sqrt{e_{nif}^2 \cdot (f_z - f_f)} = 499.444 \times 10^{-9} \text{ V}$$

$$E_{noe3} := \sqrt{\left(\frac{e_{nif}}{f_z}\right)^2 \cdot \frac{f_p^3 - f_z^3}{3}} = 31.828 \times 10^{-6} \text{ V}$$

$$E_{noe4} := \sqrt{\left(e_{nif} \frac{C_i + C_f}{C_f}\right)^2 (f_i - f_p)} = 65.324 \times 10^{-6} \text{ V}$$

$$E_{noe5} := \sqrt{\frac{(e_{nif} f_c)^2}{f_i}} = 85.479 \times 10^{-6} \text{ V}$$
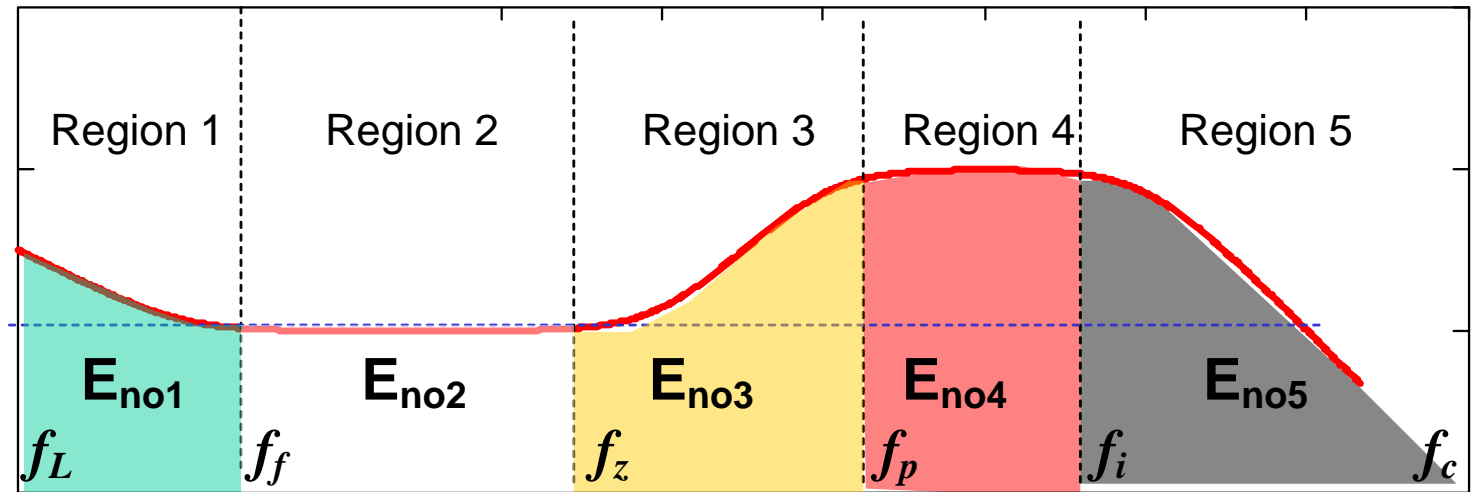
$$E_{noe} := \sqrt{E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2} = 112.193 \times 10^{-6} \text{ V}$$



Thermal (Resistor) Noise at Output

$$R_f := 100 \cdot 10^3 \Omega$$

Feedback Resistance

$$k_b := 1.38 \cdot 10^{-23} \frac{\text{J}}{\text{K}}$$

Boltzmann constant

$$T_n := 298 \text{K}$$

Temperature in Kelvin (25C)

$$f_p := 397.887 \times 10^3 \text{ Hz}$$

Transconductance bandwidth

$$K_n := 1.57$$


Noise Current from OPA827 data sheet

$$BW_n := K_n \cdot f_p$$

Noise bandwidth (brick w all filter)


$$e_{n_r} := \sqrt{4k_b \cdot T_n \cdot R_f \cdot BW_n} = 32.056 \times 10^{-6} \text{ V}$$

Thermal noise at output

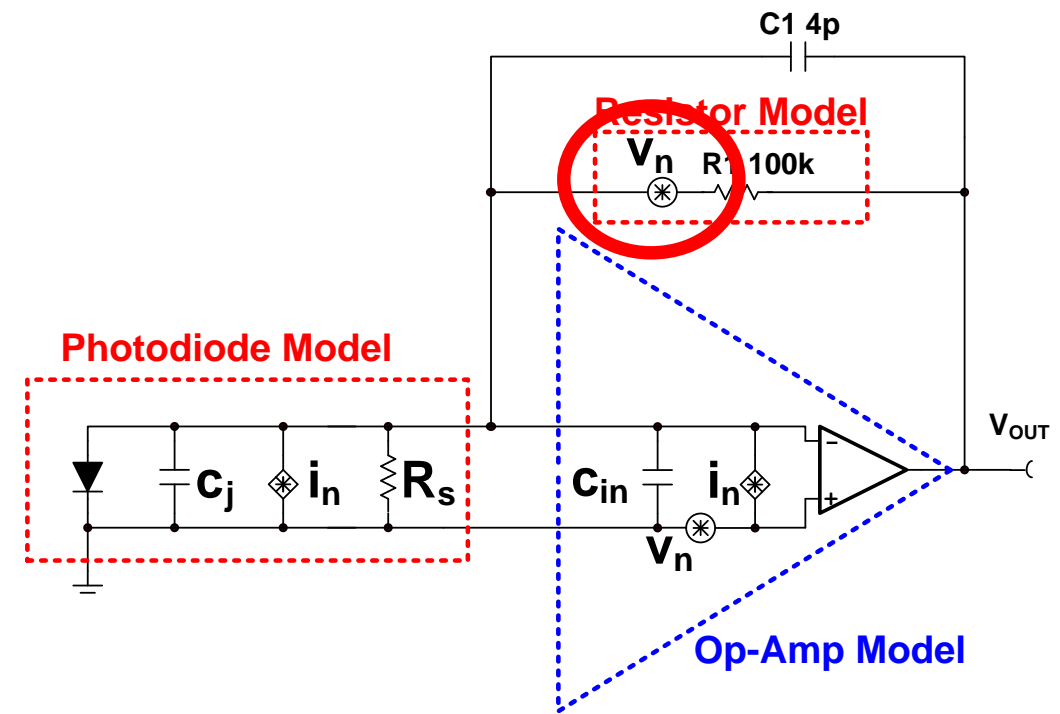

Current Noise to Voltage Noise at Output

EQUATION	DESCRIPTION
$R_f = 100 \times 10^3 \Omega$	Feedback resistance
$f_p = 397.887 \times 10^3 \text{ Hz}$	Transconductance bandwidth
$i_{n_opa} = 2.2 \times 10^{-15} \frac{\text{A}}{\sqrt{\text{Hz}}}$	Noise current from OPA827 data sheet
$i_{n_diode} = 27.395 \times 10^{-15} \frac{\text{A}}{\sqrt{\text{Hz}}}$	Noise current from diode (calculated)
$i_{n_total} = \sqrt{i_{n_opa}^2 + i_{n_diode}^2}$	Total noise current
$K_n = 1.57$	Noise bandwidth factor first order filter
$BW_n = K_n \times f_p = 624 \text{ kHz}$	Noise bandwidth (brick wall filter)
$E_{nol} = i_{n_total} \times R_f \times \sqrt{BW_n} = 2.17 \mu\text{V}$	Current noise at output

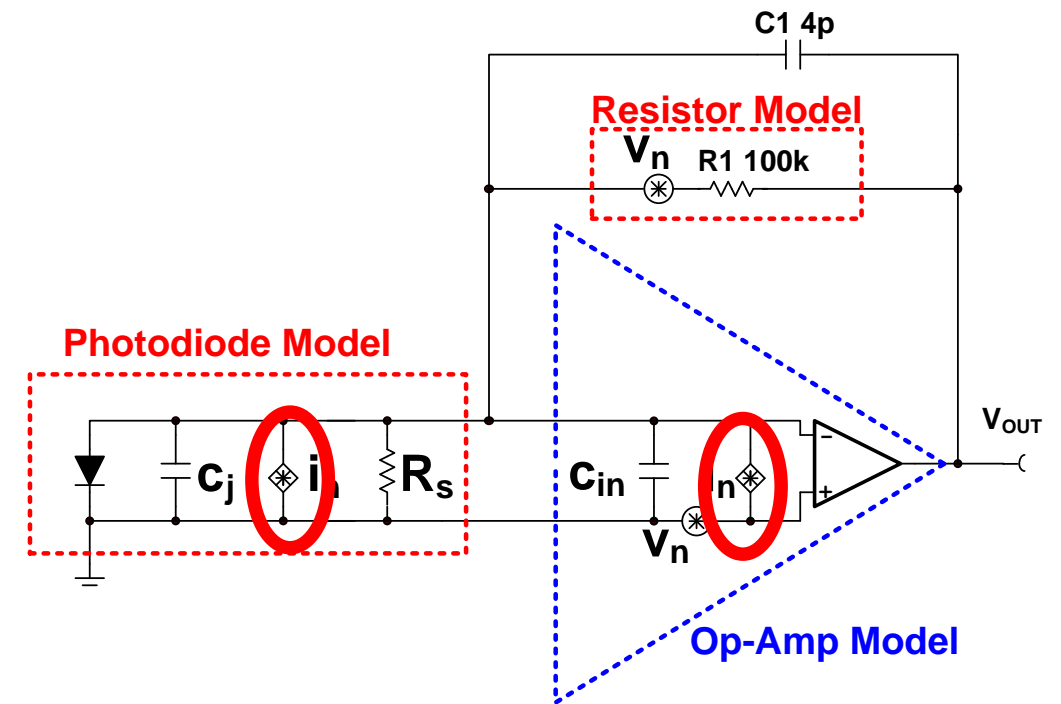

The Final Total Noise


$$E_{noe} := 112.193 \times 10^{-6} \text{ V} \quad \text{Op-Amp Voltage Noise}$$

$$E_{noR} := 32.056 \times 10^{-6} \text{ V} \quad \text{Resistor Noise}$$



$$E_{noI} := 2.172 \times 10^{-6} \text{ V} \quad \text{Op-Amp Current Noise}$$

$$E_{no} := \sqrt{E_{noR}^2 + E_{noI}^2 + E_{noe}^2} = 116.703 \times 10^{-6} \text{ V} \quad \text{Total Output Noise for OPA827 Transimpedance Amp}$$


Calculation vs Simulation

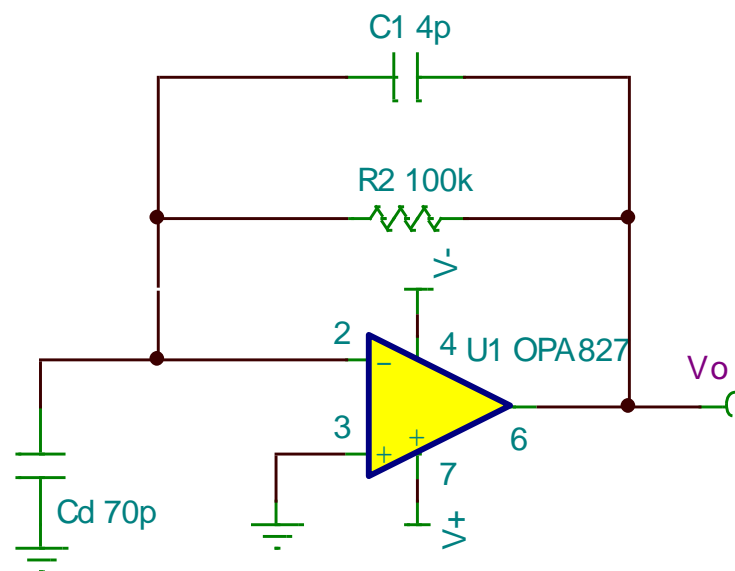

Calculated (rms)	Simulated (rms)
116.7uV	109.1uV

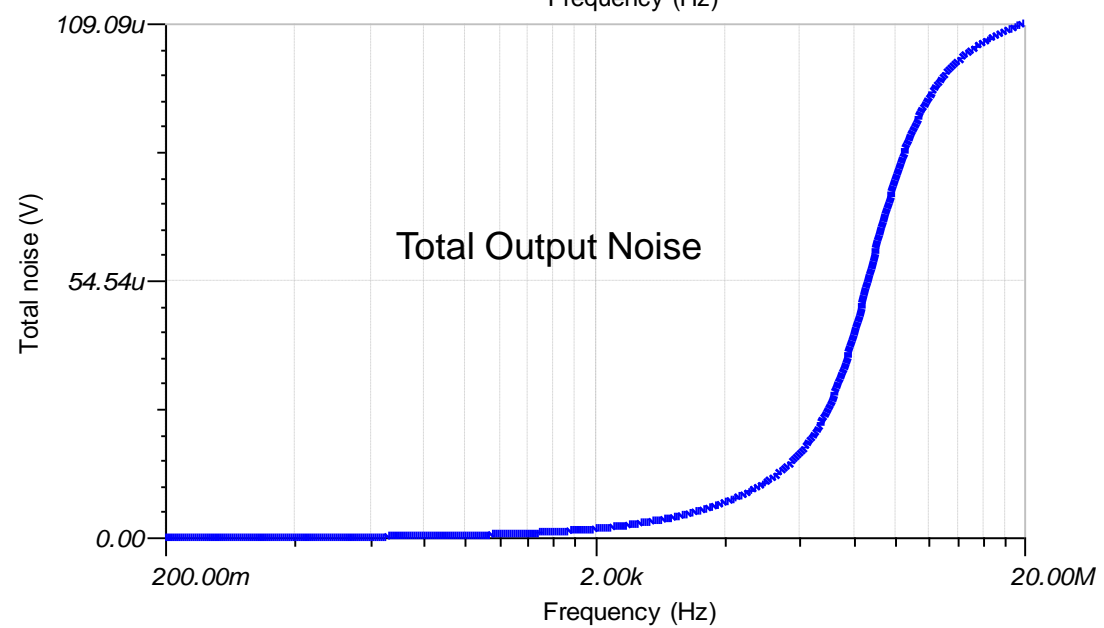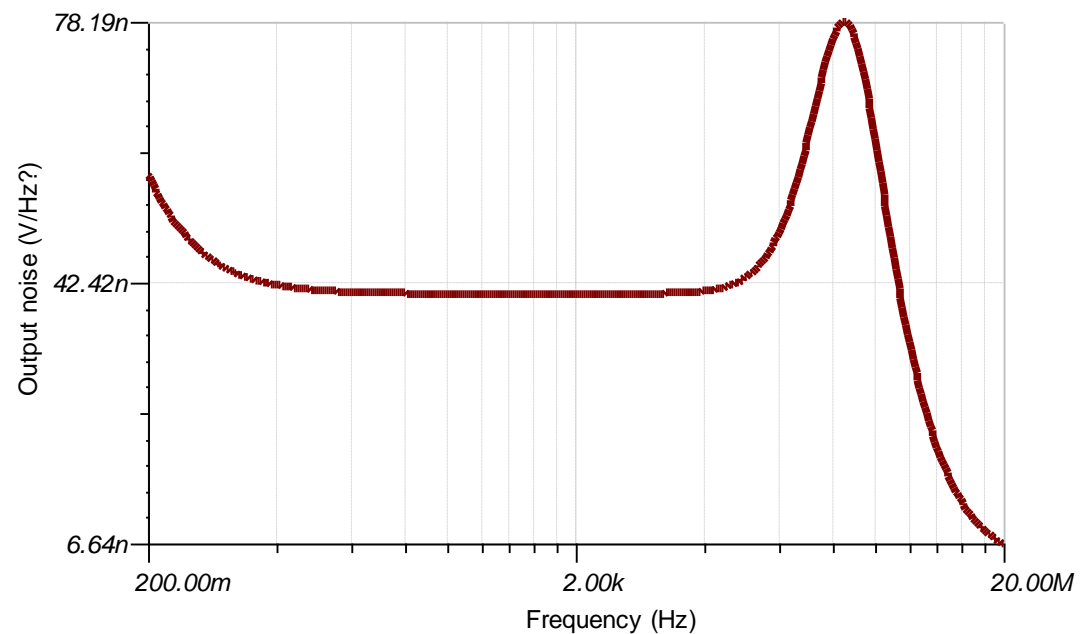

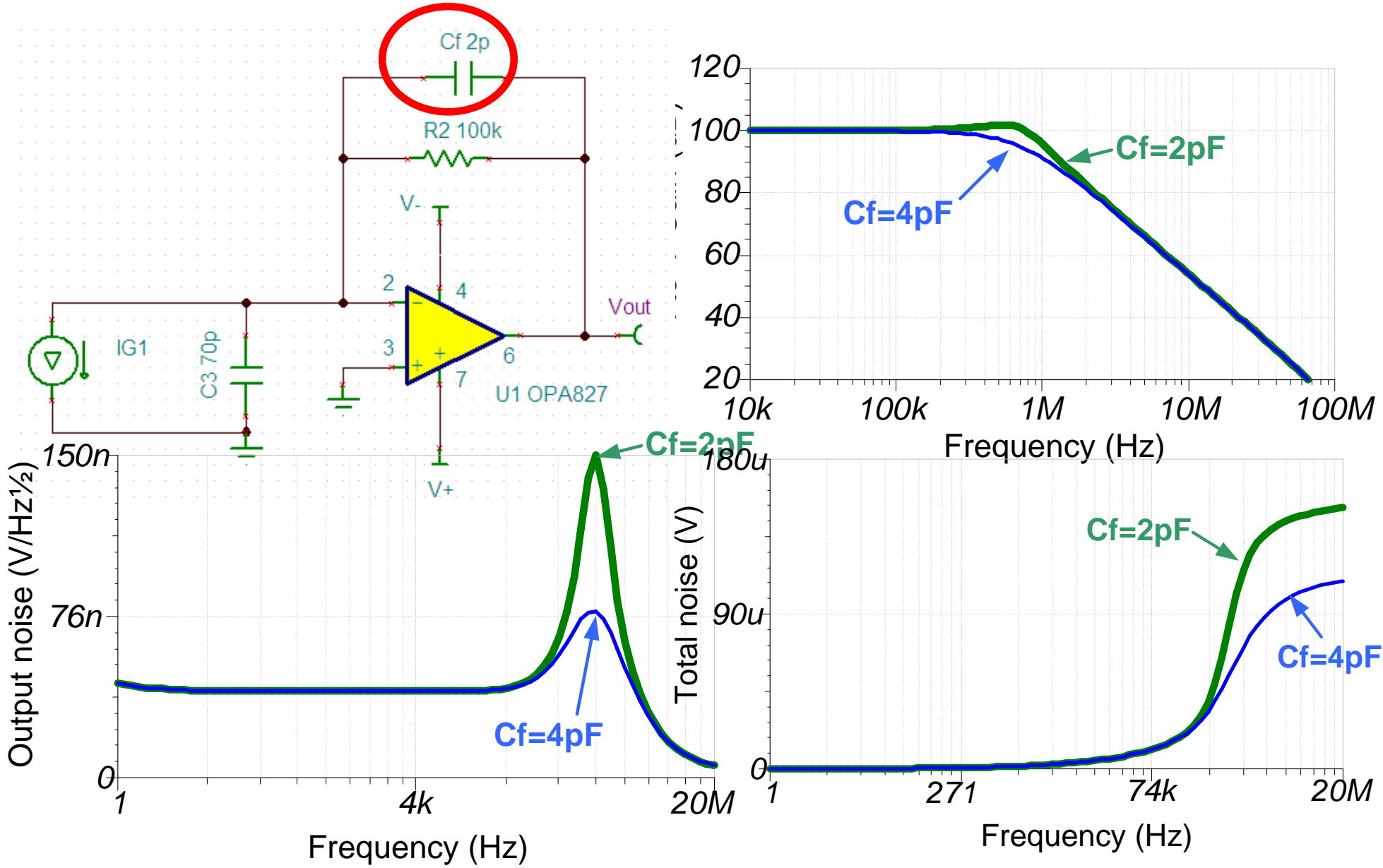
Reducing Noise (Higher Cf = Lower BW & Noise)



OPA827 Measurement Example

Validating Test Equipment Capability

**What is the
noise floor?**

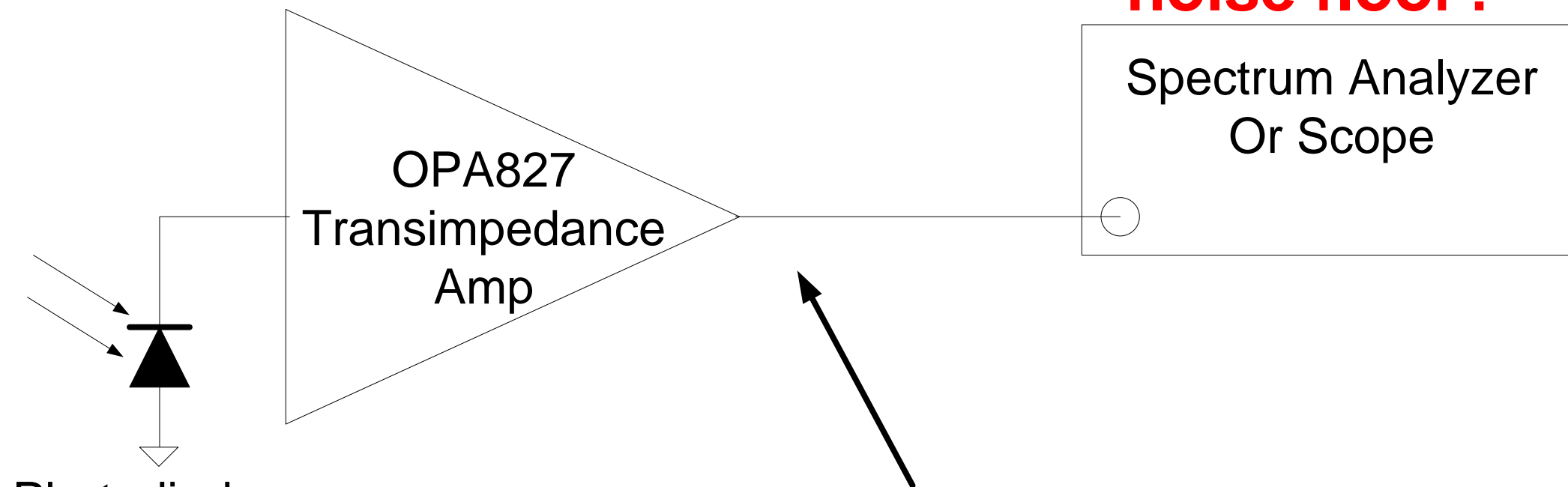


Noise Spectral Density = $3.8\text{nV}/\sqrt{\text{Hz}}$
Total Noise = $109.1\text{uV}_{\text{rms}}$
= $654.6\text{uV}_{\text{p-p}}$

Tektronix DPO 4034 Oscilloscope



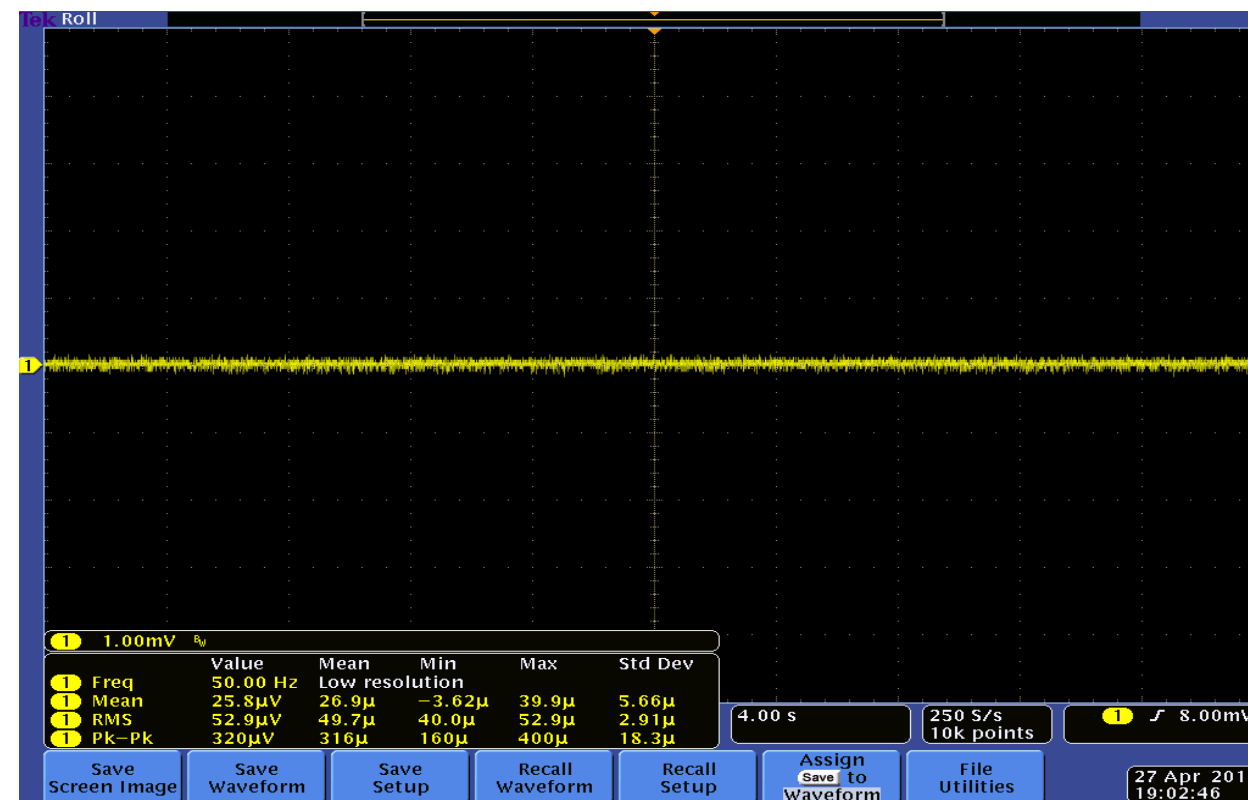- 1) Set DC couple, 20MHz bandwidth limit
- 2) Short input channel to measure noise floor




STDEV: 48uV (same as RMS)

P-P: 6.6*STDEV=319uV

40s P-P: 320uV

Agilent 4395A Spectrum Analyzer

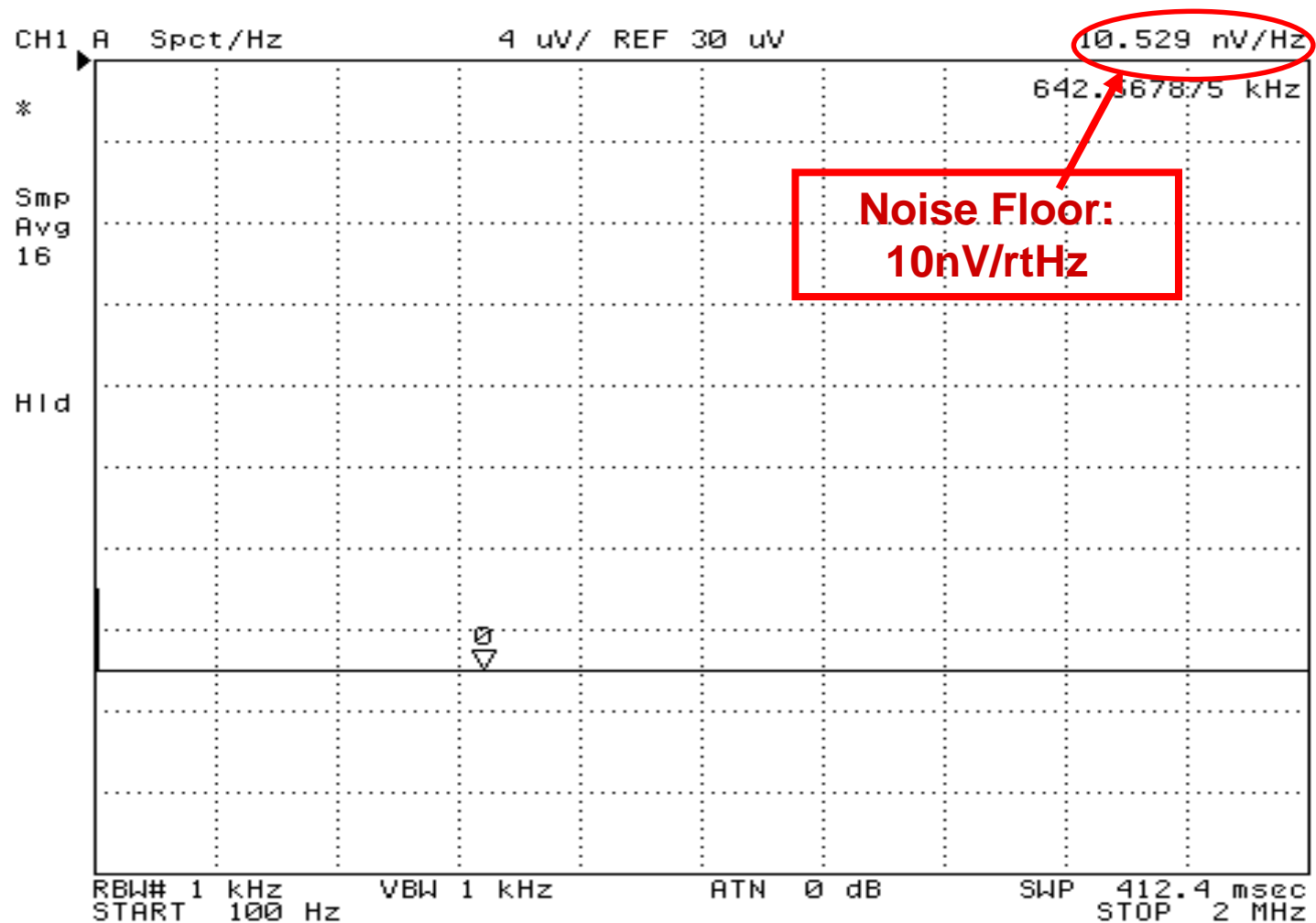1. Frequency Range: 10Hz~500MHz
2. Noise floor: 10nV/rtHz
3. Input Impedance: 50Ω




The Noise Floors are Not Good Enough


Noise Floors:

Scope (1mV range)= 48uV rms =320uVpp

4395A Spect. Analyzer = 10nV/rtHz



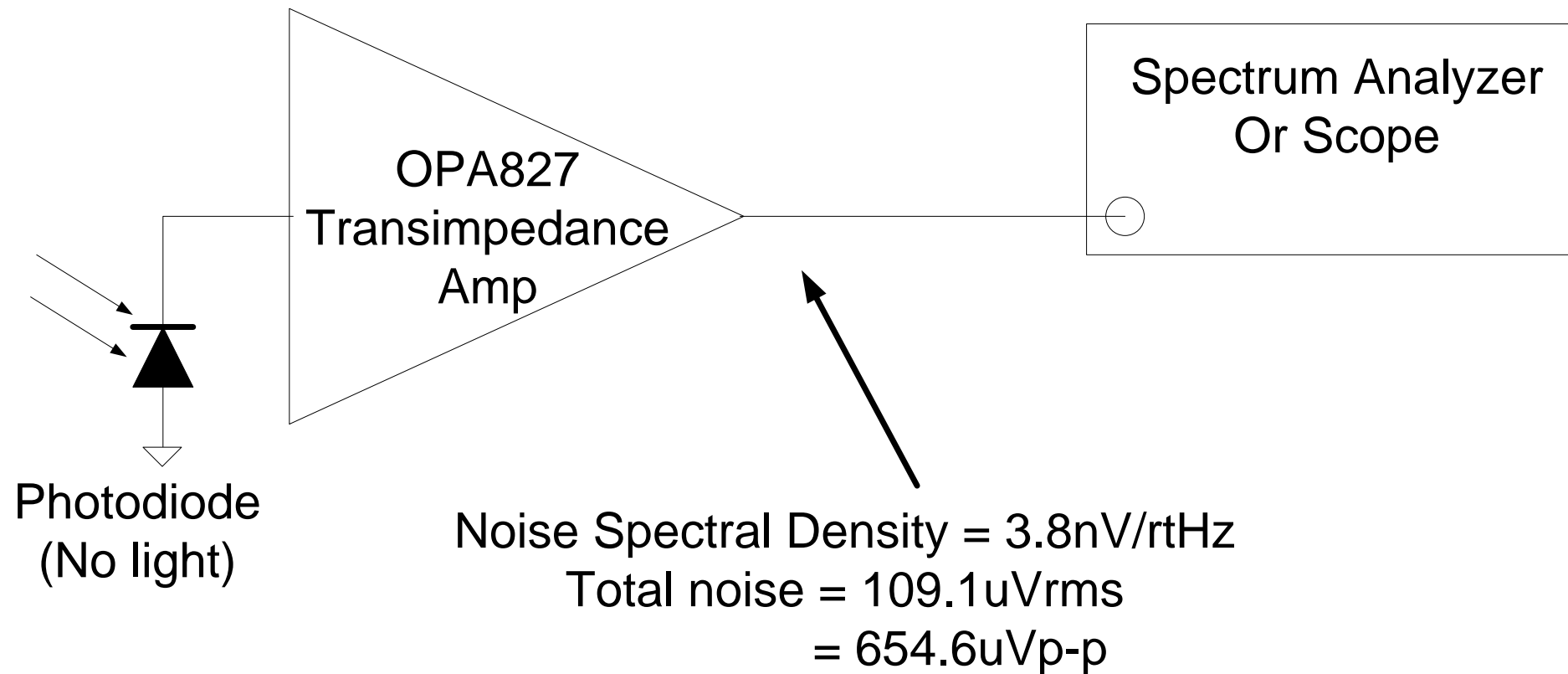


Solution: Use A Post Amp, Which one?

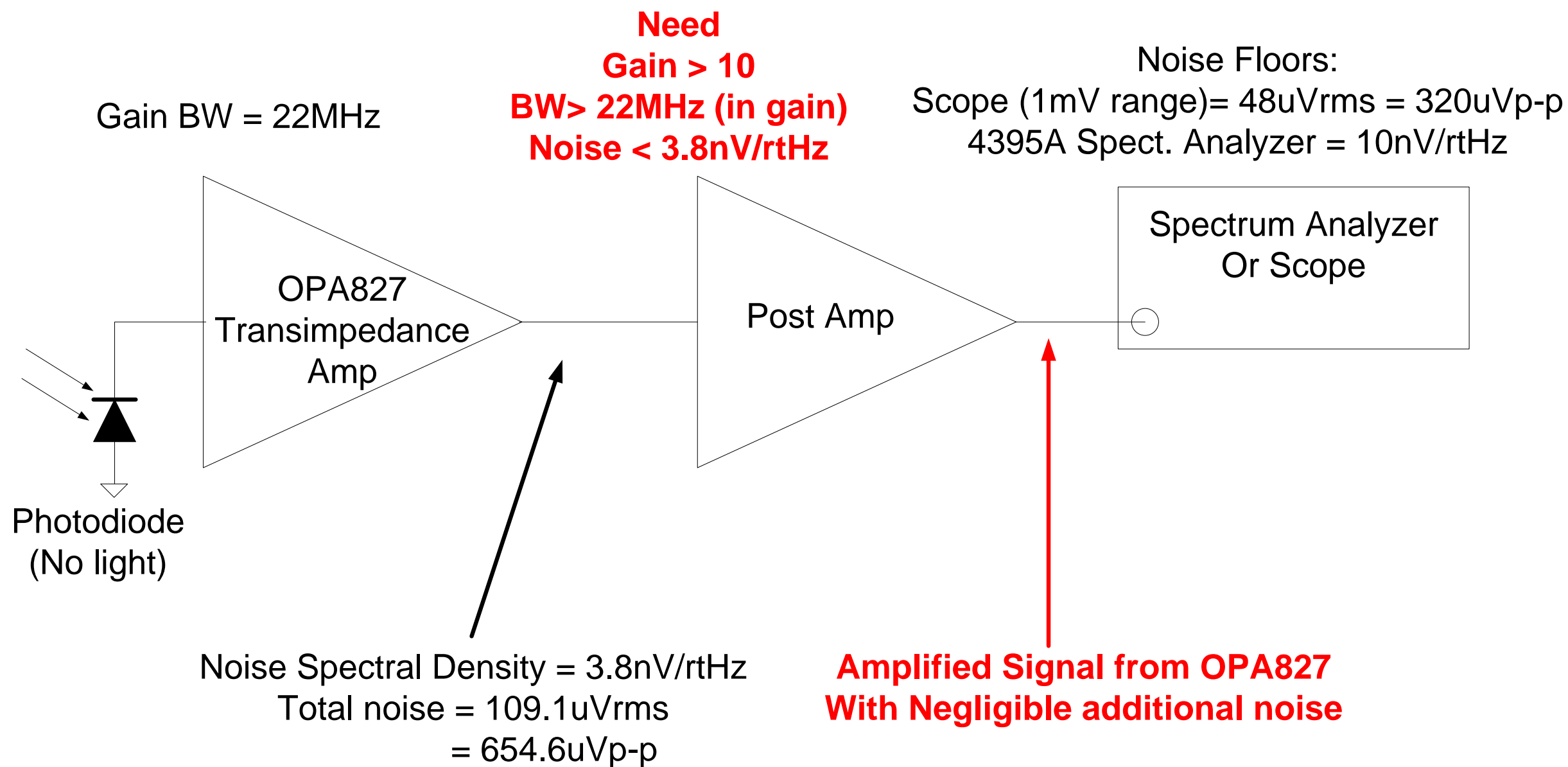


Use OPA847 as post amplifier

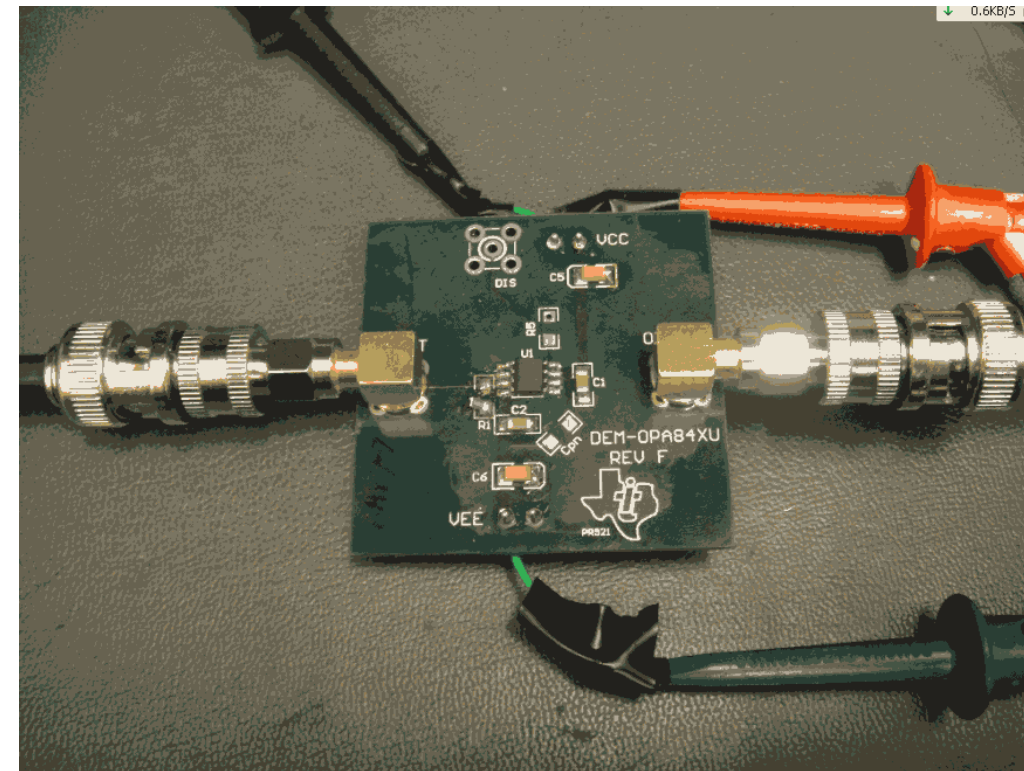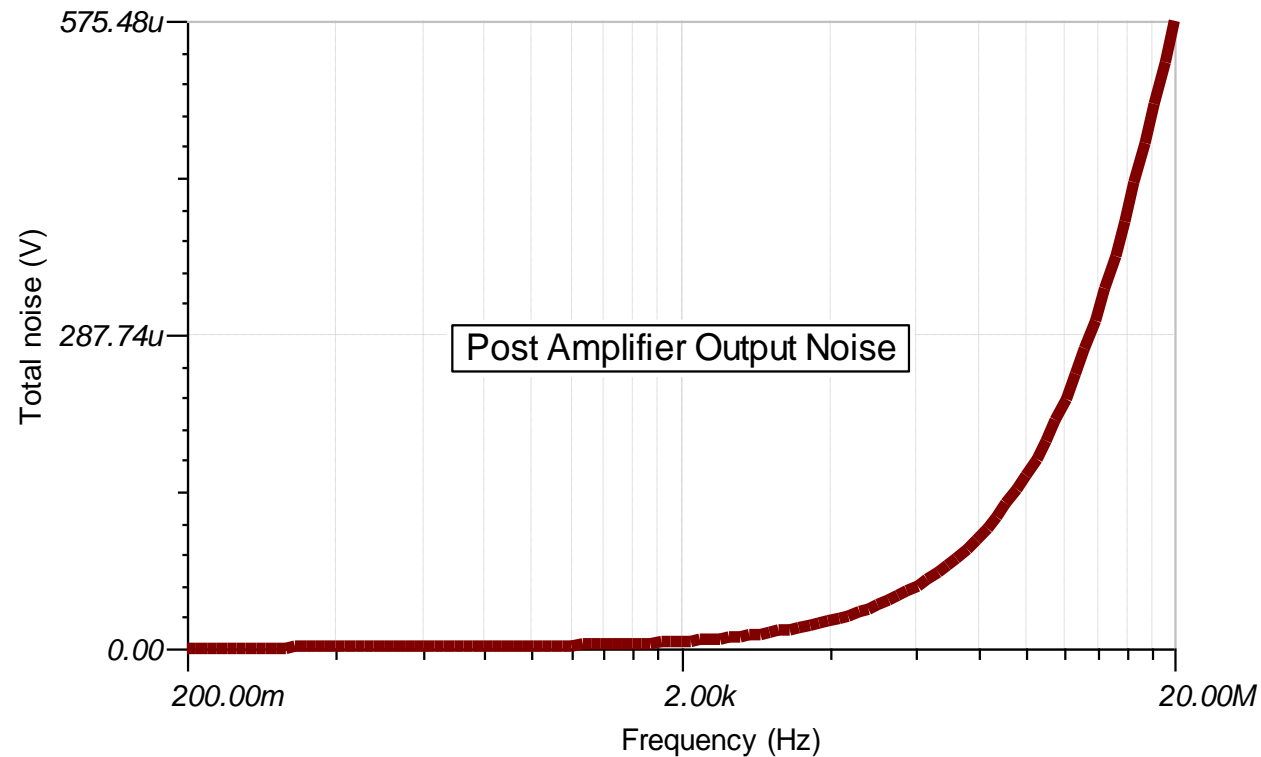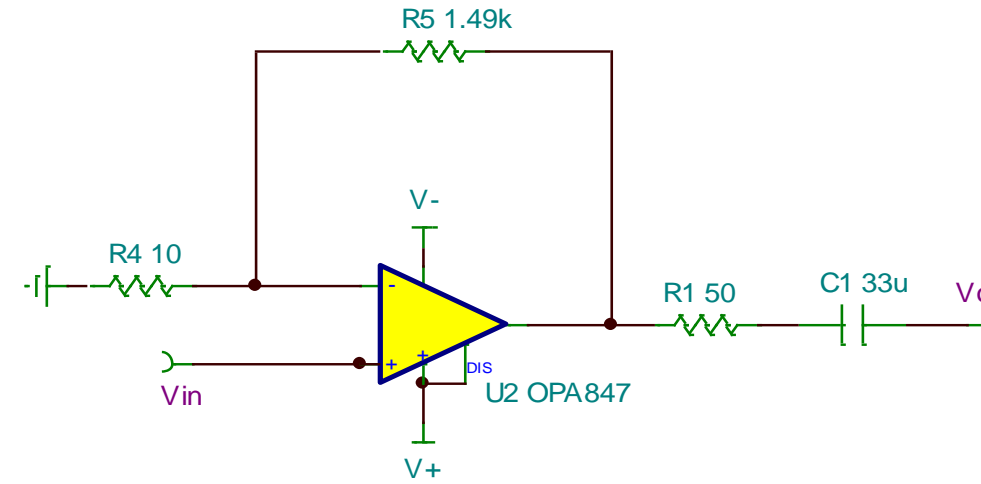
- At the gain of 150, the bandwidth is 26MHz
- $0.85\text{nV}/\sqrt{\text{Hz}}$ Input Voltage Noise
- $2.5\text{pA}/\sqrt{\text{Hz}}$ Input Current Noise
- $\pm 100\mu\text{V}$ Input Offset Voltage (Typical))



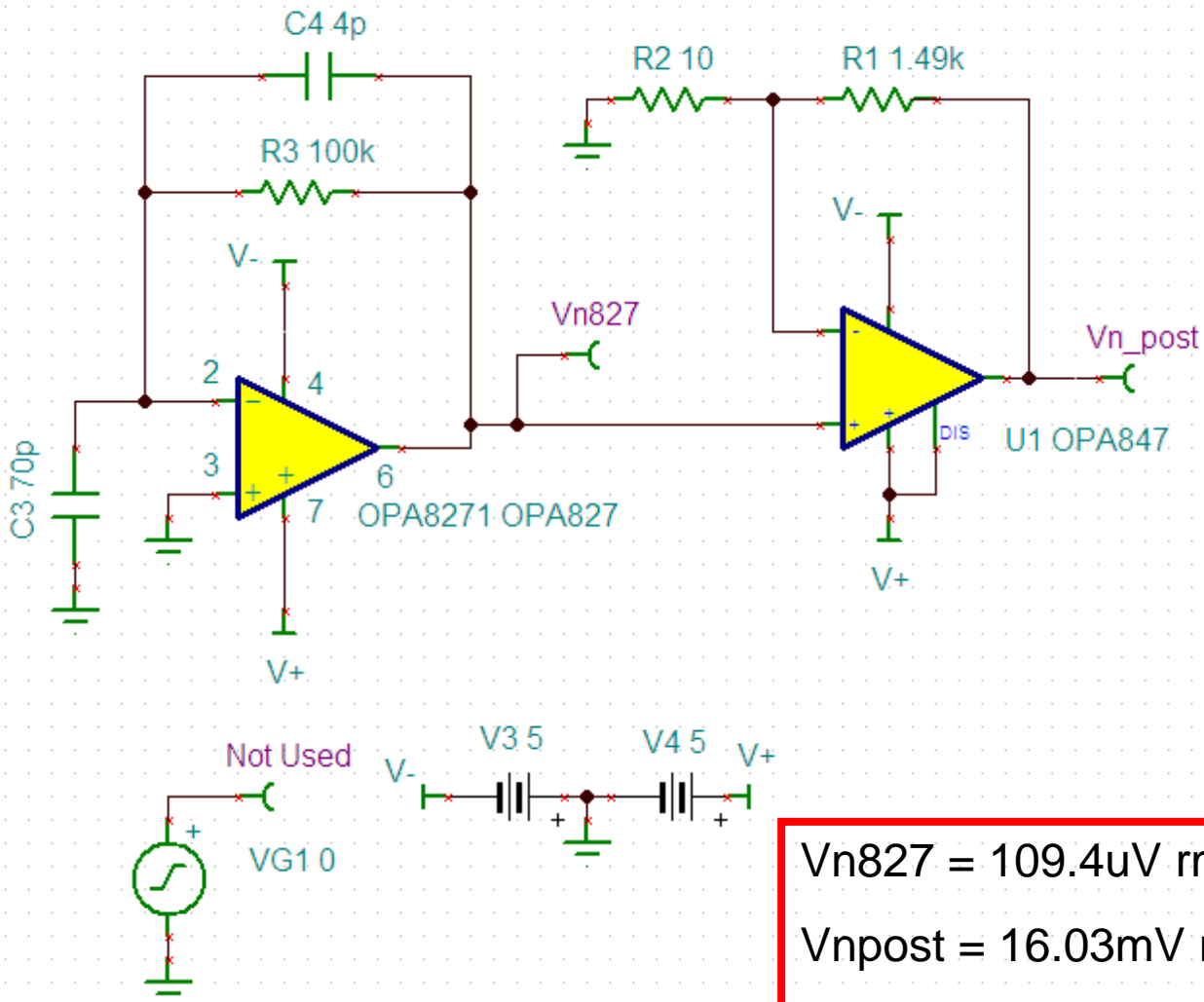
Post Amplifier adds relatively small error!



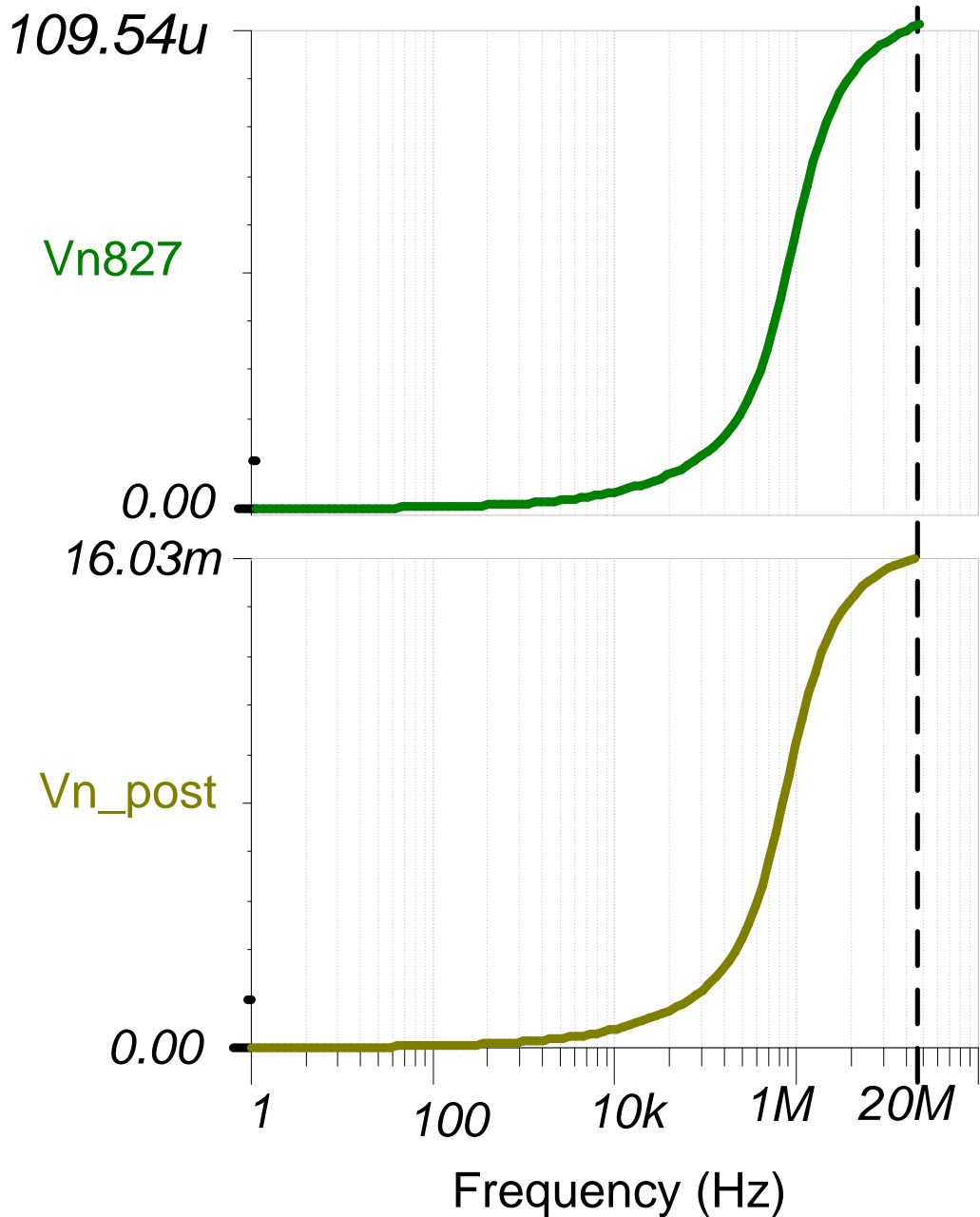
$Vn_{827} = 109.4\mu\text{V rms}$
 $Vn_{post} = 16.03\text{mV rms}$
 $Vn_{post}/\text{Gain} = 16.03\text{mV}/150 = 106.8\mu\text{V rms}$



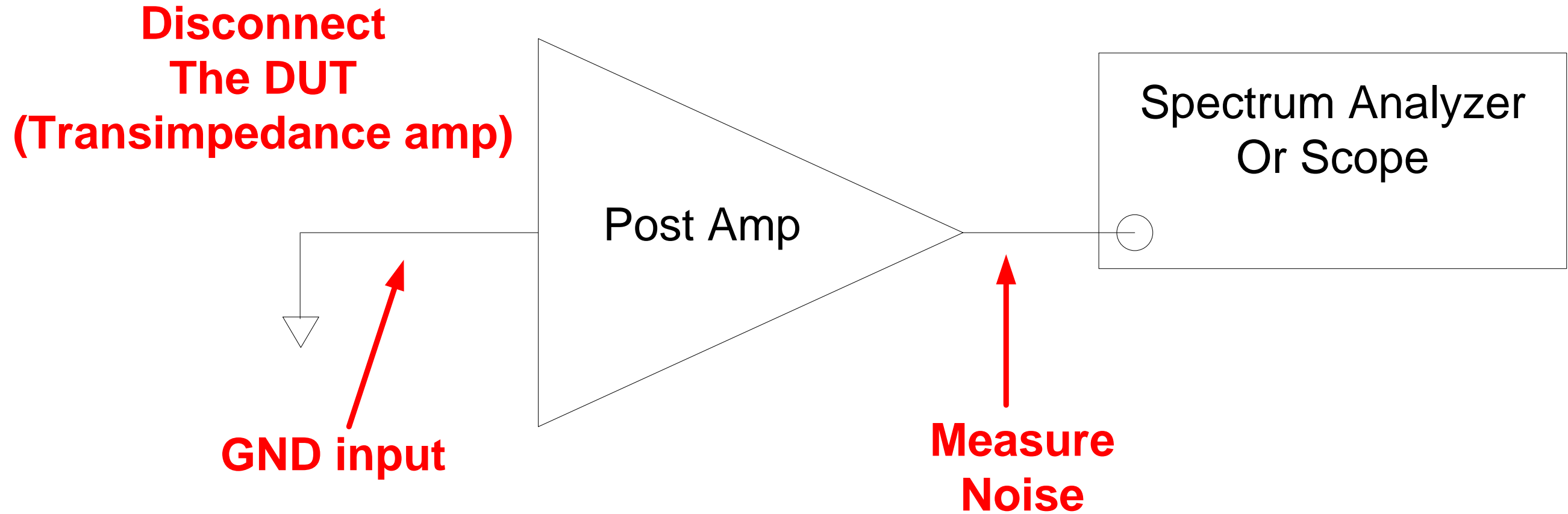Test the Noise Floor of post amp + instrument





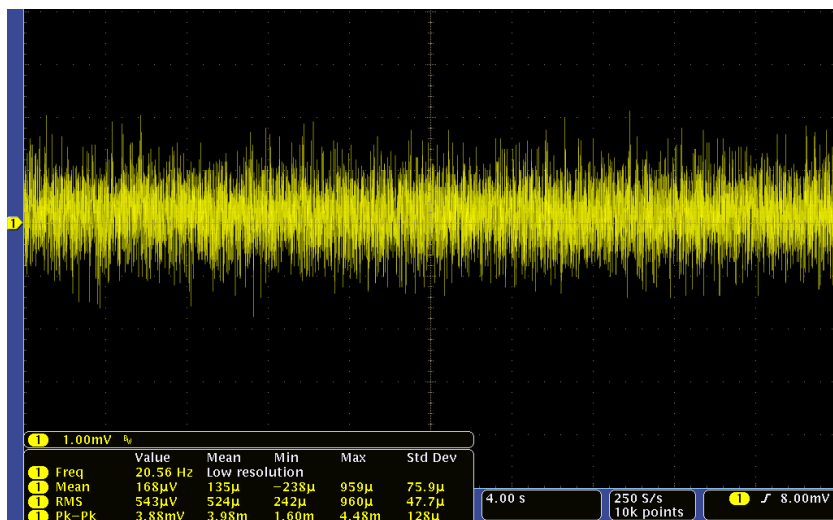Test The Noise Floor – Post Amp Noise Scope




Simulated (rms)	Measured (rms)
575uV	518uV


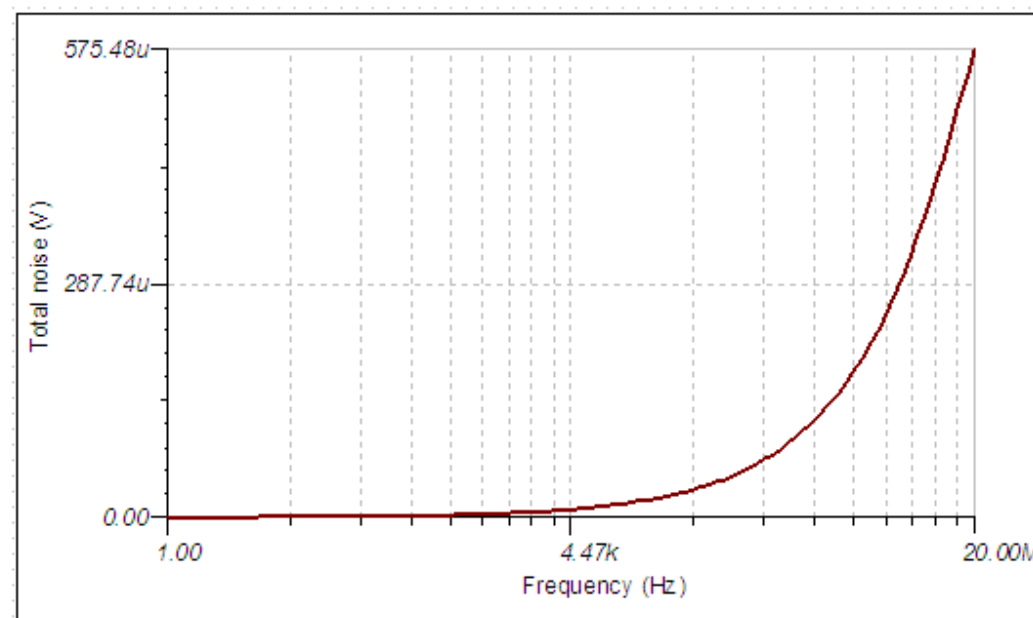
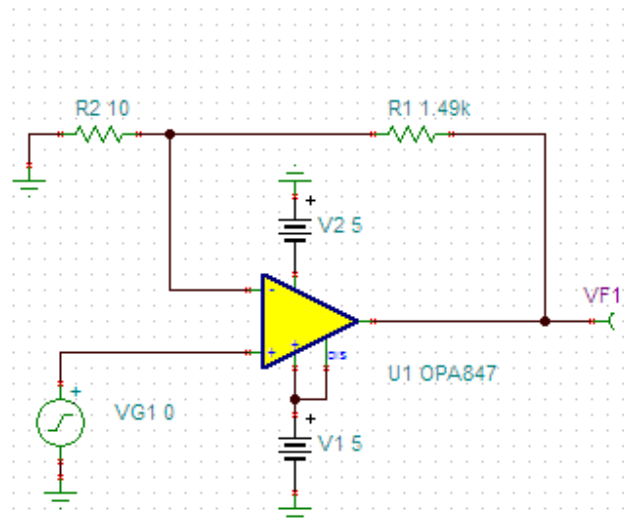
STDEV: 518uV
P-P: 6.6*STDEV=3.4mV
40s P-P: 3.88mV



Hardware Connections

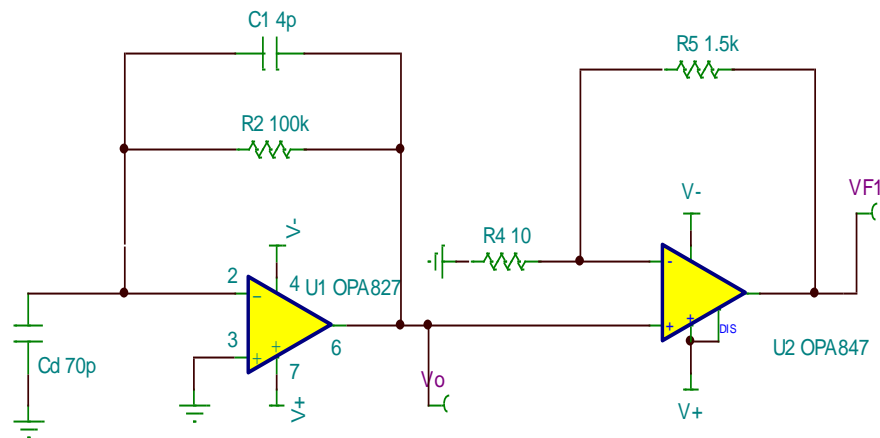

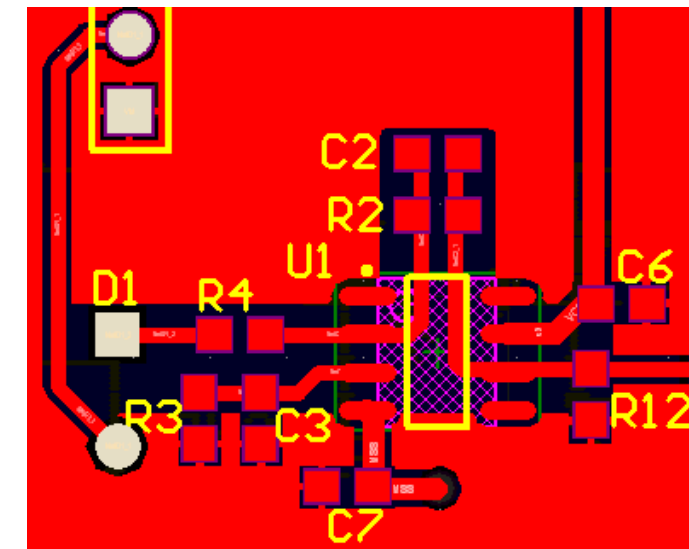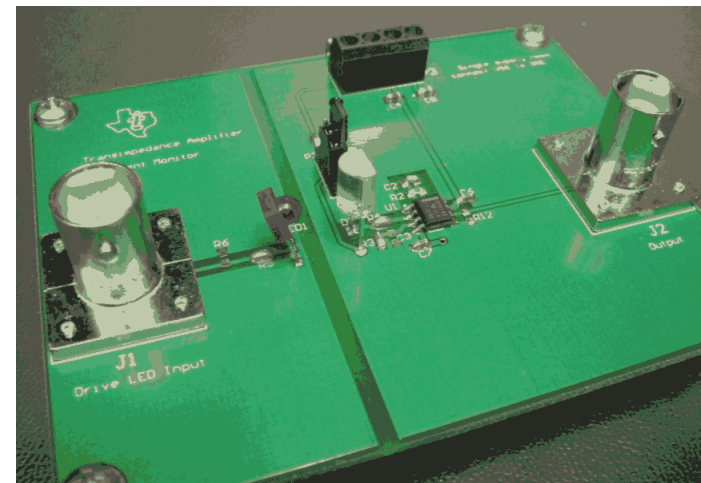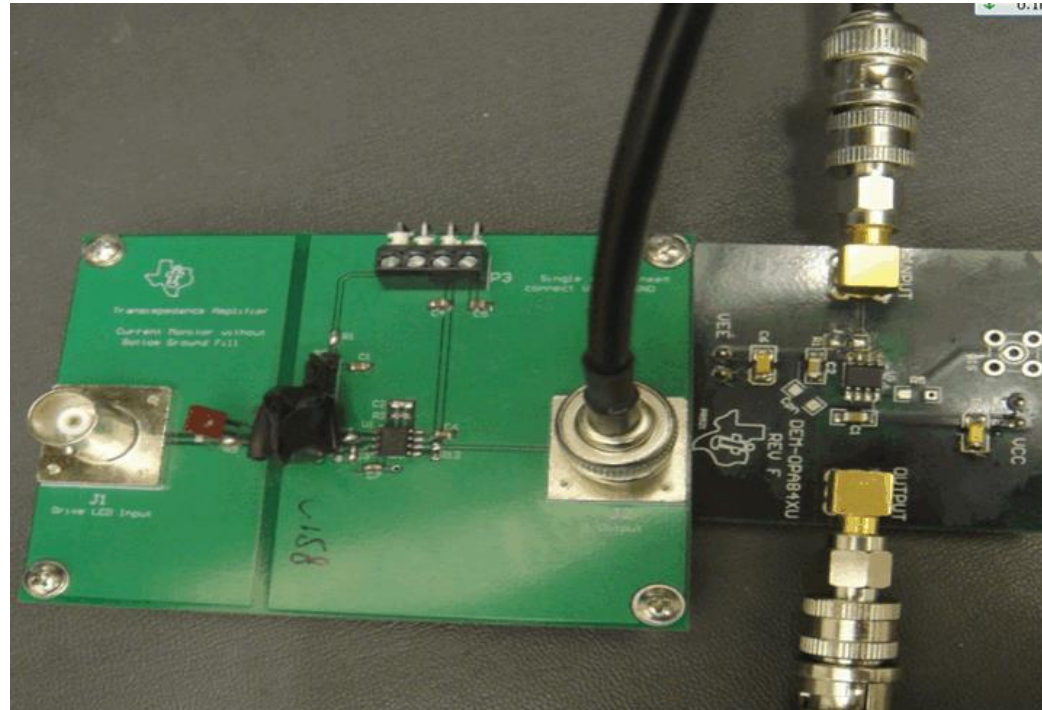1. PDB-C158-ND photodiode
2. 70pF junction capacitance at $V_r=0$ V
3. 100dB I-V gain
4. 4pF compensation capacitor
5. ± 5 V power supply.



Shield the Circuit





Power Supply
Vcc, Vss, GND


Input & Output BNC
connectors

Shield

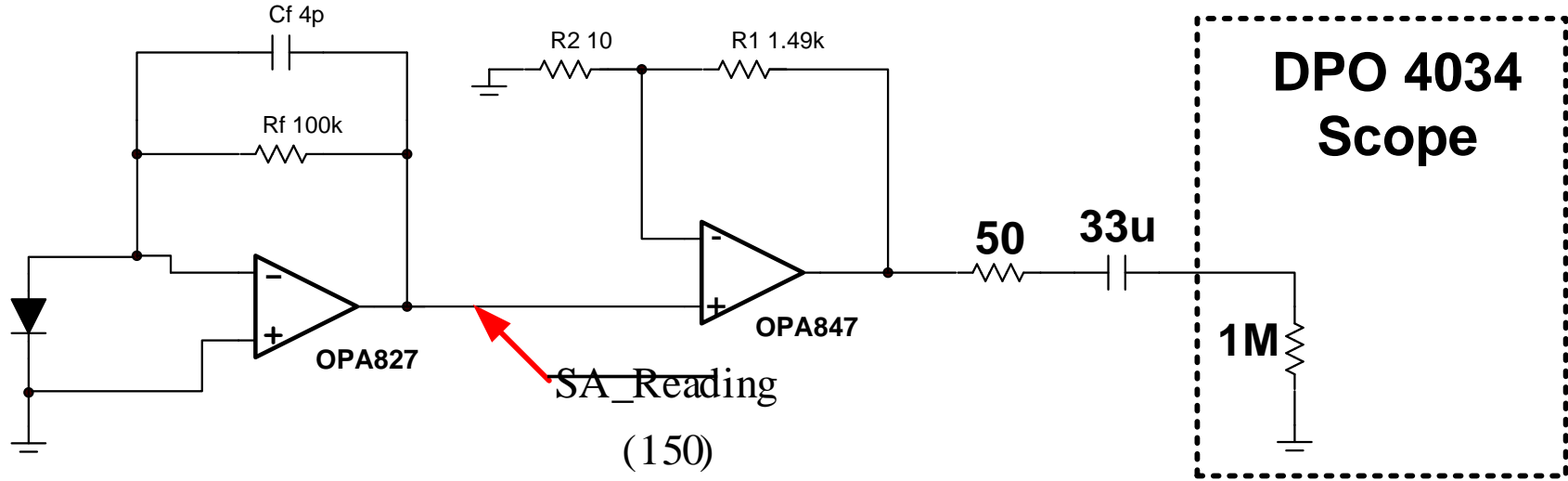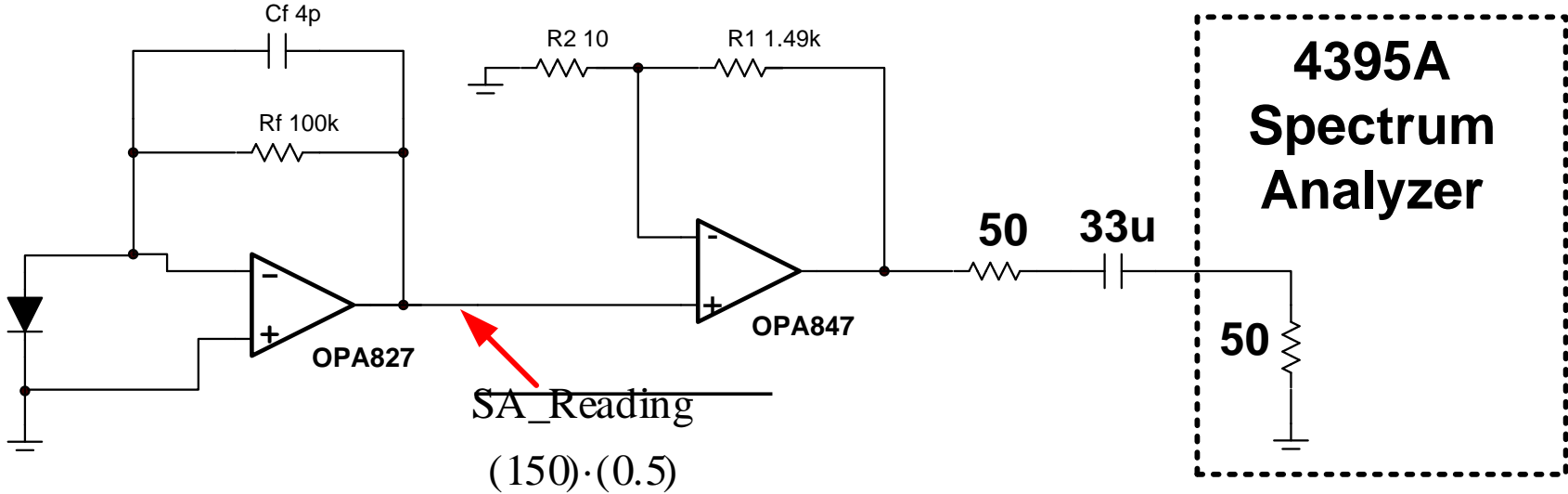Divide by post amp gain for OPA827 Output Noise



Measured vs Simulated (DPO 4034 Scope)

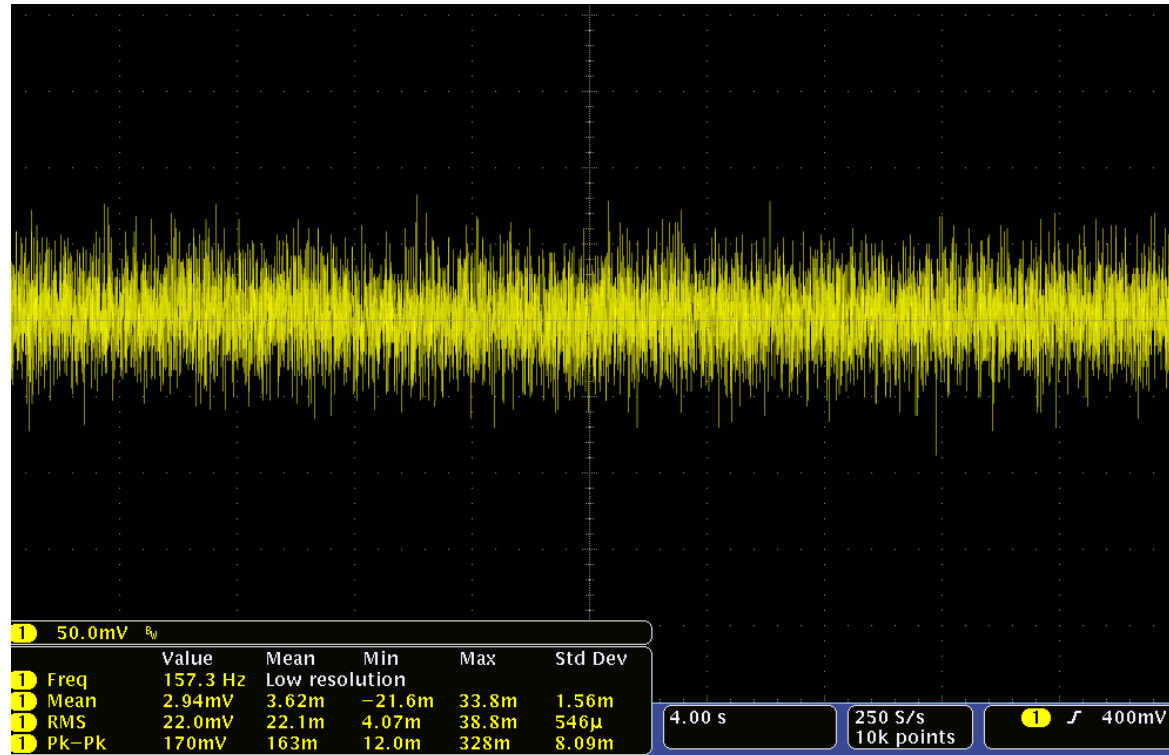

OPA847 Measured at Scope:

STDEV: 21.7mV

P-P: 6.6*STDEV=143mV

40s P-P: 170mV


At OPA827 (DUT) Output:

Divide by gain



$V_{n827} = 21.7\text{mV}/150 = 144.6\mu\text{V}$

Calculated (rms)	Simulated (rms)	Measured (rms)
116.7uV	109.1uV	144.6uV

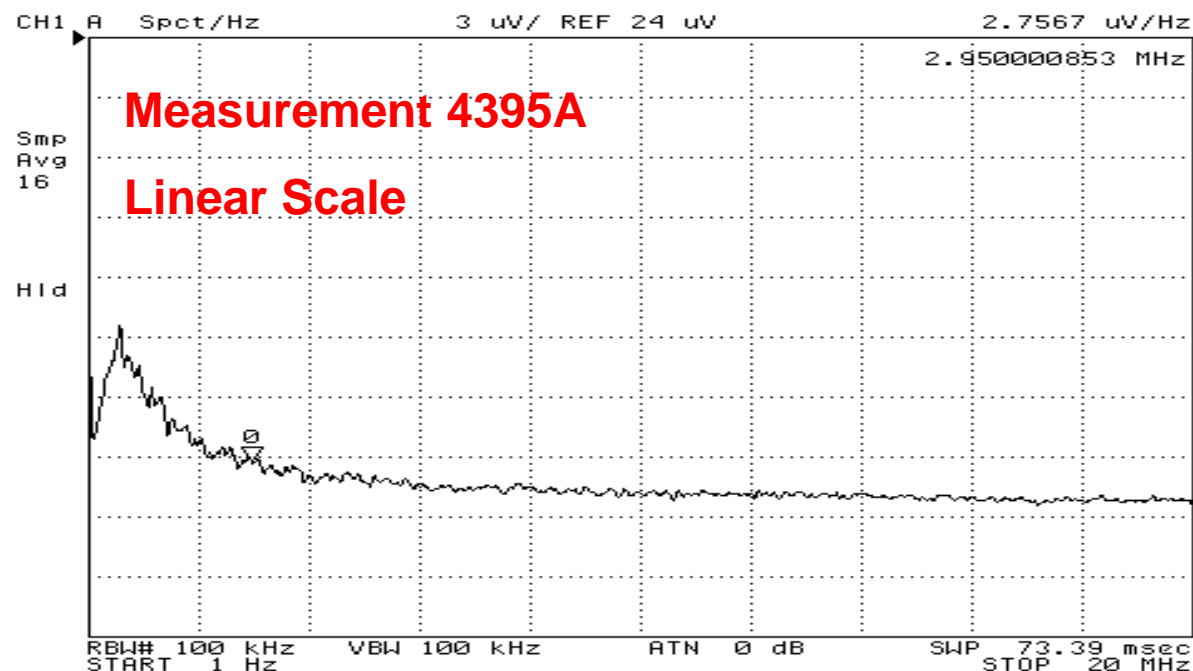
Measured Spectral Density Spectrum Analyzer



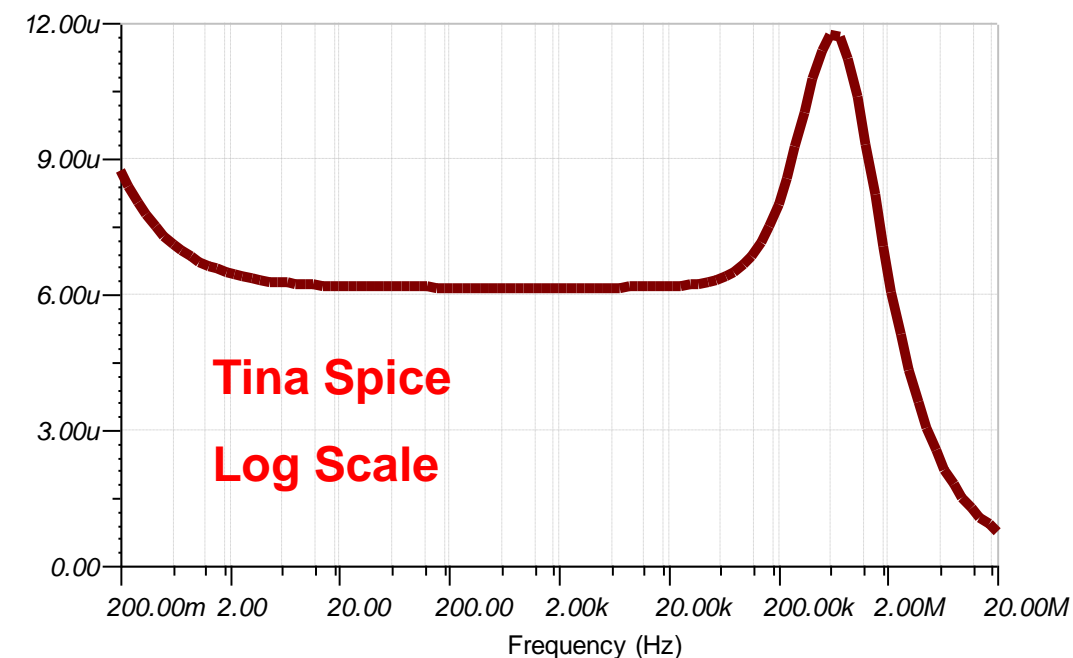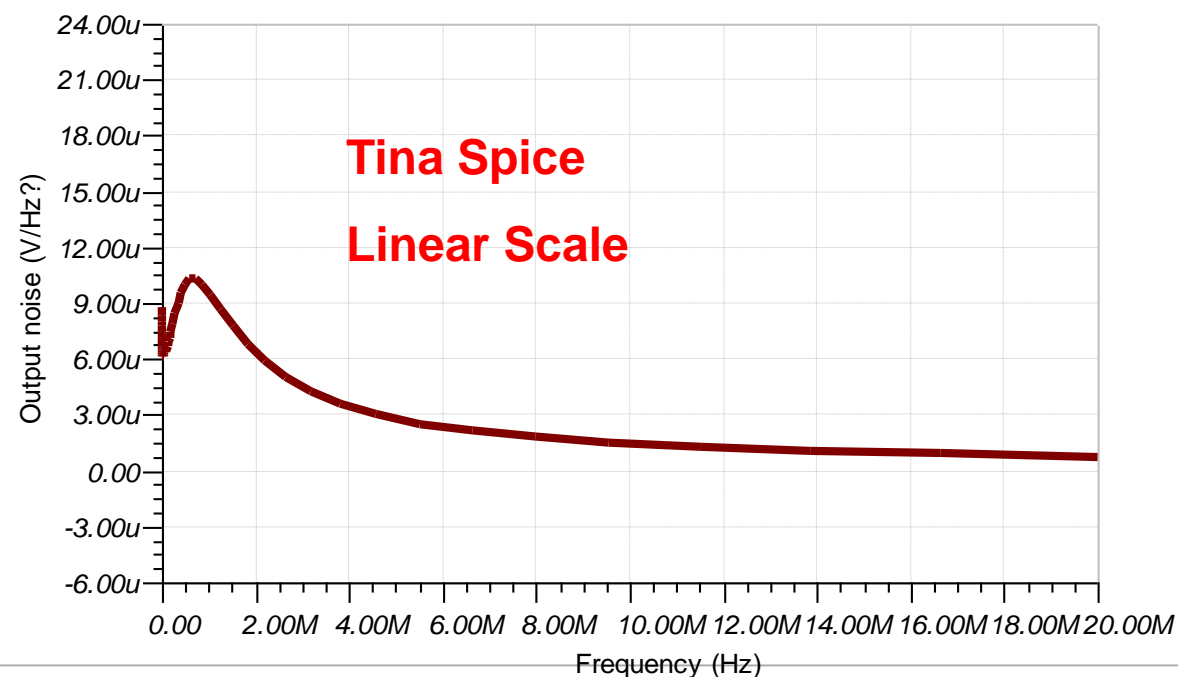1. Agilent 4395A Spectrum Analyzer test 1Hz~20MHz span, 3uV/div, REF=24uV.
2. The tested noise density curve shape is the same as simulation.



Measured vs Simulated

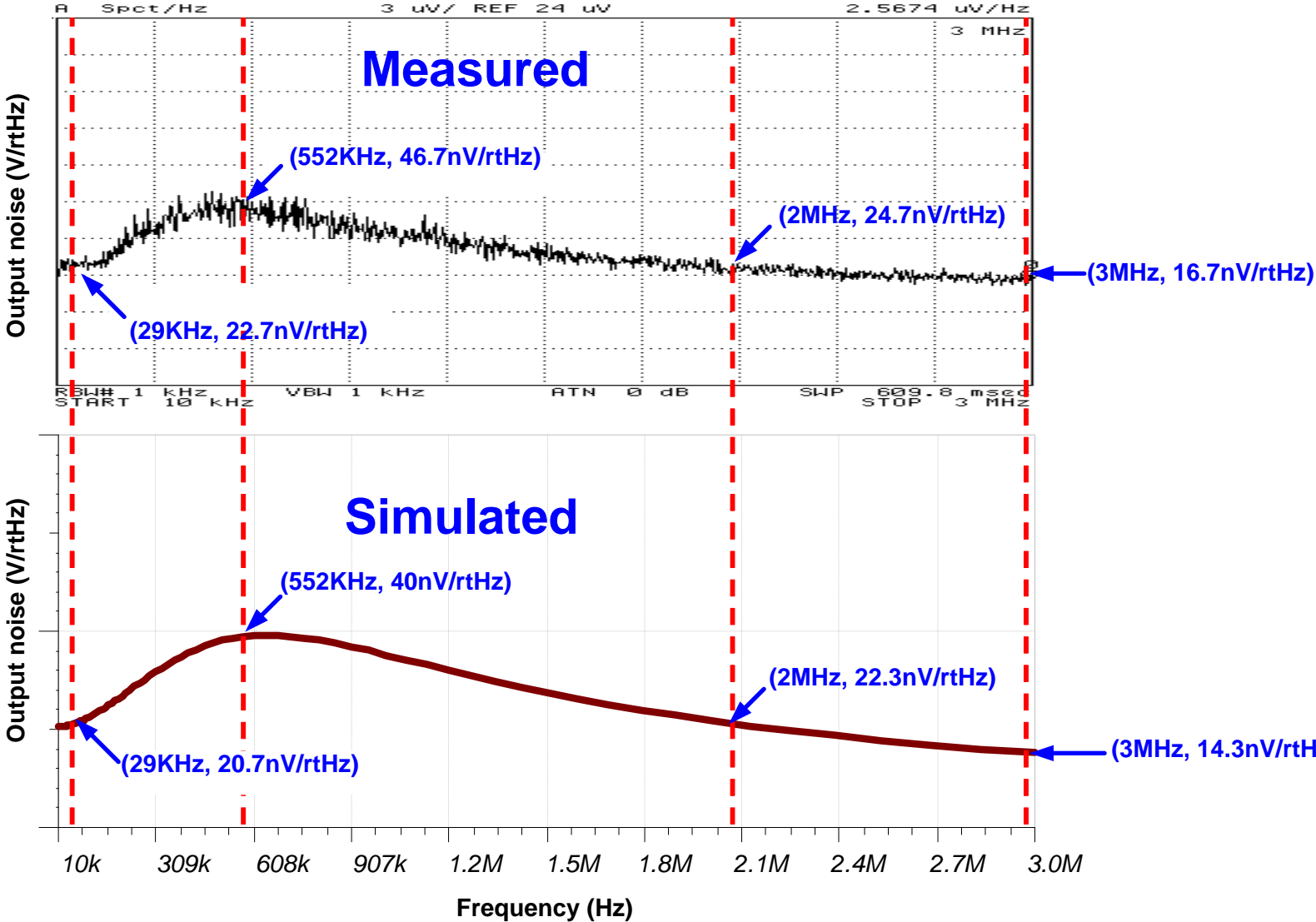

Thanks for your time

- Bryan Zhao (赵伟)
- Matt Hann
- Collin Wells, Peter Semig, Curtis Mayberry

References

- Jerald Graeme <Photodiode Amplifiers>
- Art Kay < Op-Amp Noise Calculation and Measurement >
- HAMAMATSU <Photodiode Technical Information>
- Tim Green <Operational amp stability>