

Noise In Photodiode Applications

By Art Kay and Bryan Zhao (赵 伟)

June 1, 2011

Contents

- Photodiode Review
- Photodiode Noise Theory
- Bandwidth and Stability
- OPA827 Hand Calculation
- OPA827 Tina Spice Analysis
- OPA827 Measurement Example

Photodiode Basics

Why Photodiode Noise?

- Noise is a key parameter in photodiode design
 - Wide bandwidth (integrate more noise)
 - Low signal levels (noise more critical)
- Photodiode amplifier noise is more complex
 - Parasitic capacitance and sensor capacitance
 - Poles and zeros
 - Gain peaking

Photodiode Basics



- **Introduction**

- Photodiodes convert light into current or voltage.


- **Photodiode type**

- PIN photodiode – wide spectral range (less selective), PIN = p-doping, intrinsic material, n-doping (most popular)
- PN photodiode – more wavelength selective
- APD (Avalanche photodiode) – sensitive to low light, fast

SPECTRAL RESPONSE

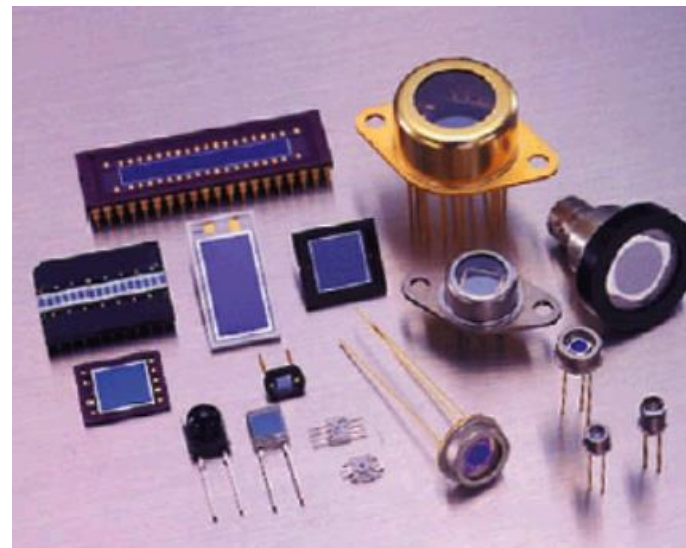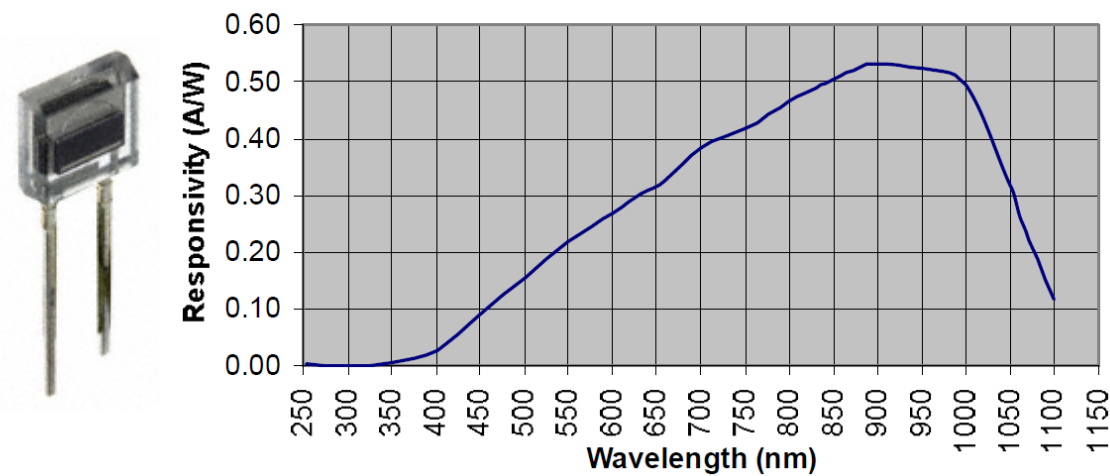

Basic Photodiode Physics

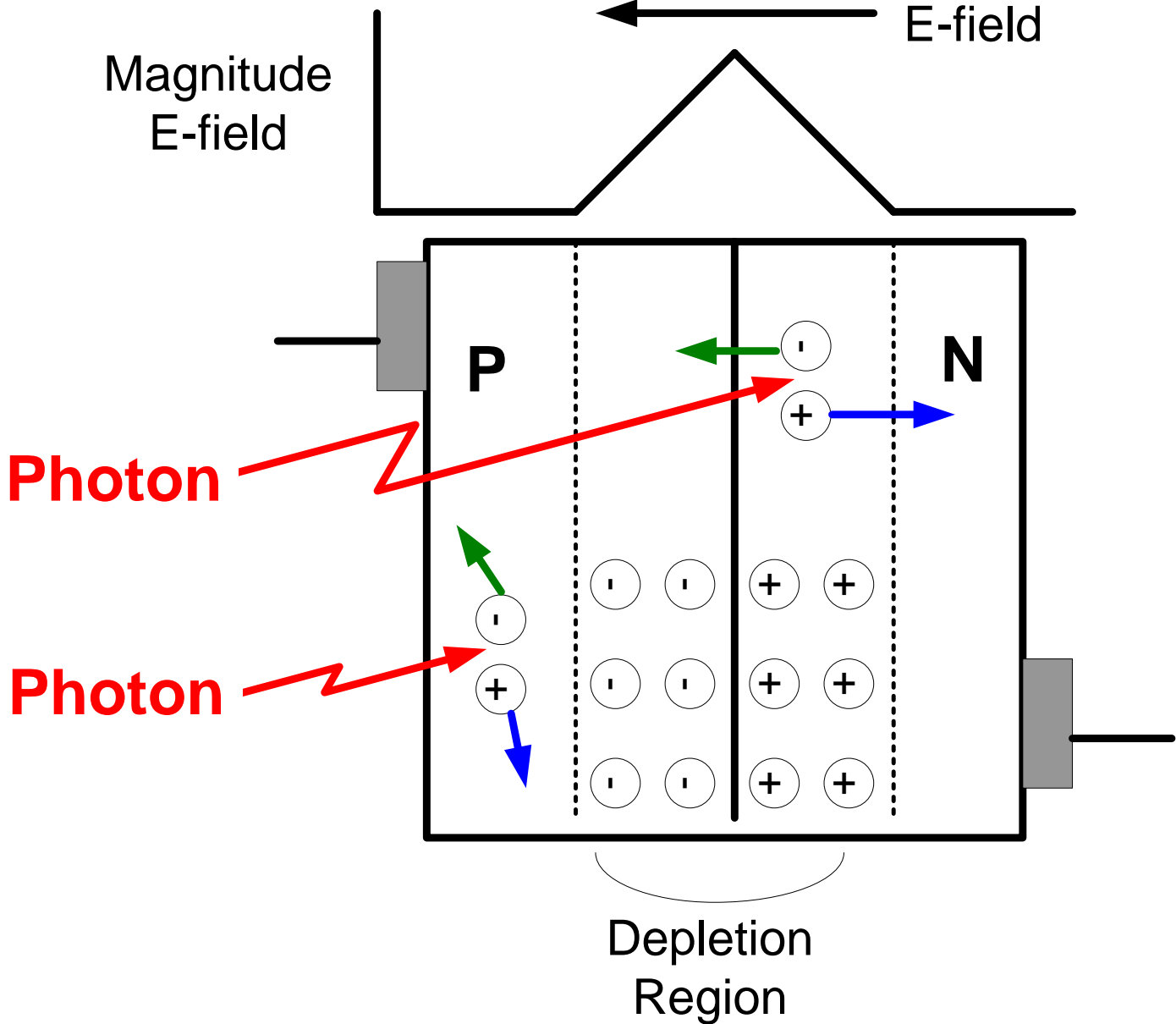

Photodiode model

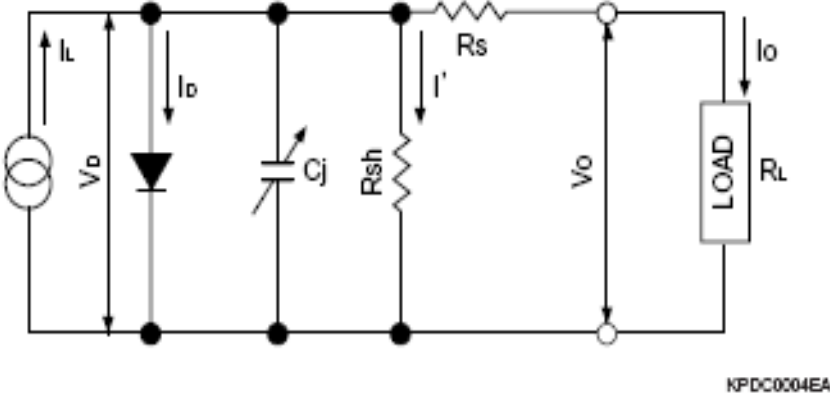


Figure 1.4 Photodiode Equivalent Circuit

KPDC0004EA

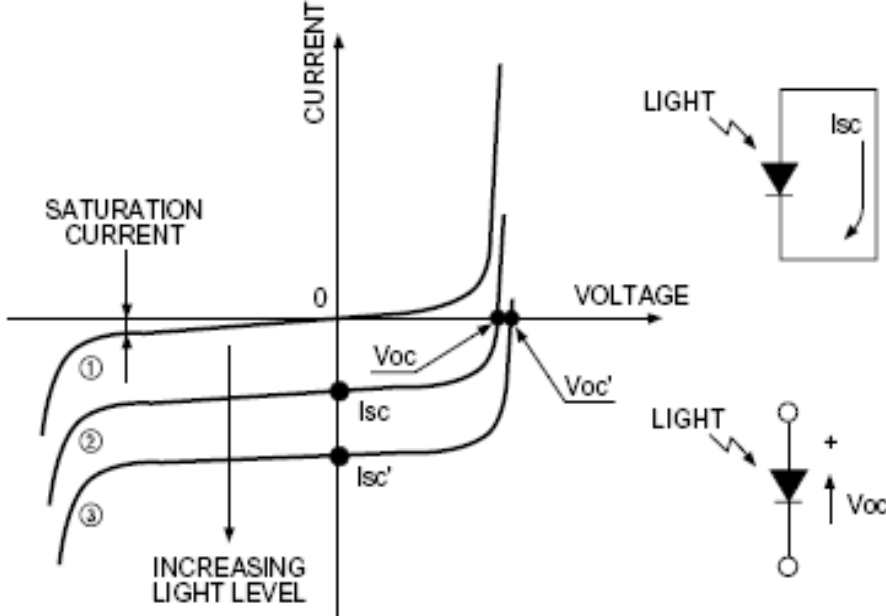


Figure 1.5 Current VS. Voltage Characteristics

KPDC0005EA

Output current is given as :

$$I_o := I_L - I_D - I' = I_L - I_S \left(e^{\frac{eV_D}{kT}} - 1 \right) - I'$$

I_S : Photodiode reverse saturation current

e : electron charge

k : Boltzmann's constant

T : Absolute temperature of the photodiode

I_L = light current


I_D = dark current

I' = leakage current

The open circuit voltage V_{oc} is the output voltage when I_o equals 0. Thus V_{oc} becomes:

$$V_{oc} := \frac{kT}{c} \ln \left(\frac{I_L - I'}{I_S} + 1 \right)$$

Photodiode and Control Source TINA model

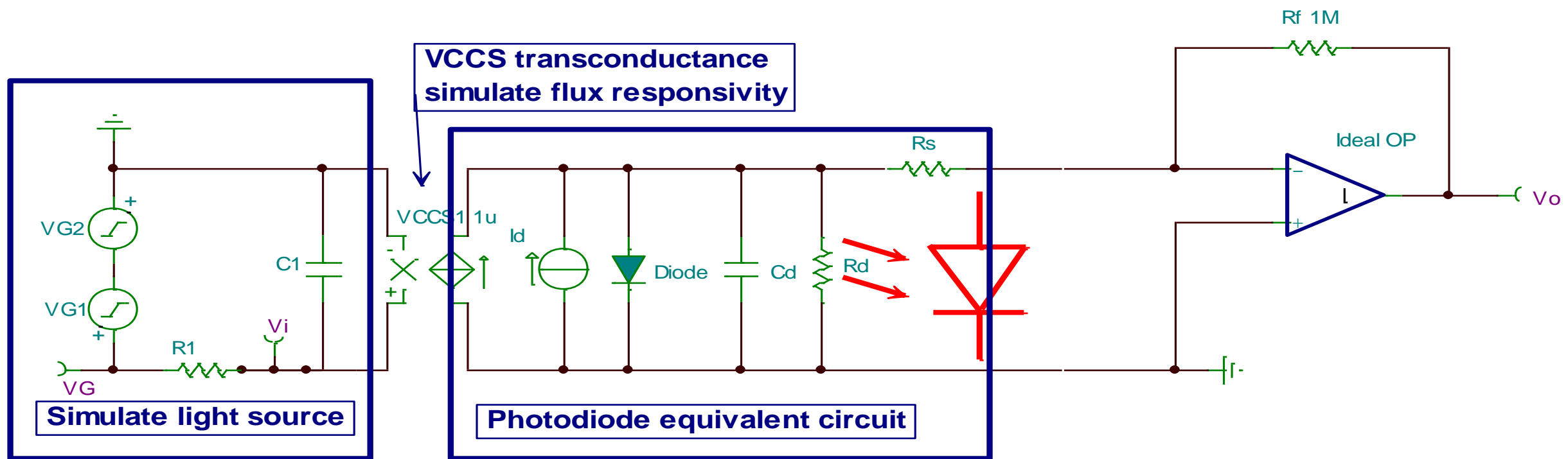

Light exciting source:


- 1) Use VG1 and VG2 voltage sources to simulate light power wave.
- 2) Use R1 and C1 shape light signal
- 3) The Voltage Control Current Source (VCCS1) simulates photodiode sensitivity.

Photodiode Equivalent Circuit:

- 1), Current Source Id simulates Dark current
- 2), Diode is a ideal diode
- 3), Cd and Rd simulate photodiode's junction capacitor and dark Resistance.
- 4), Rs is series resistor, which is far smaller than Rd.

Photodiode Noise Theory

Photo-Diode Amp Noise Model

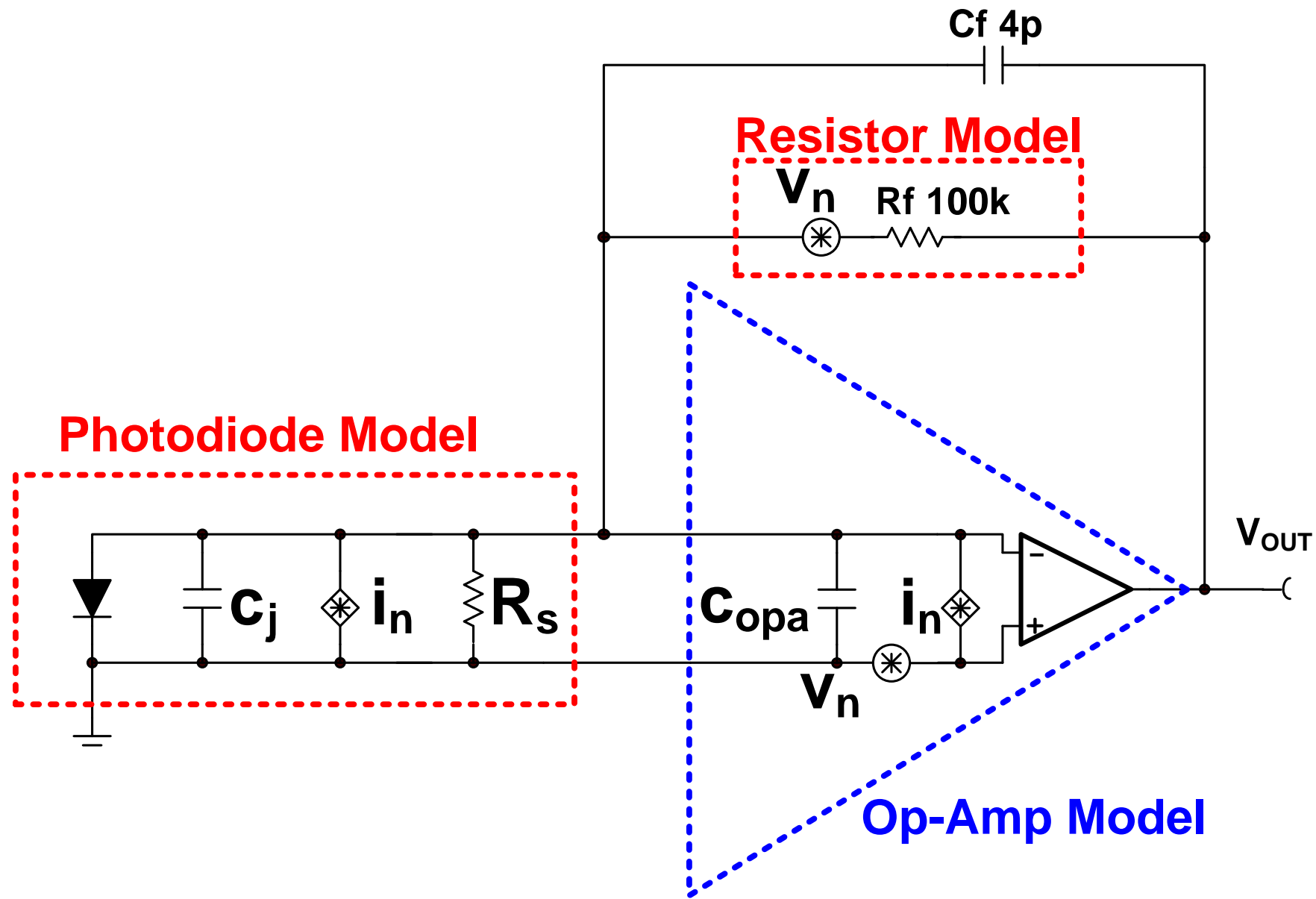

Photodiode noise

Thermal (Johnson Noise)

$$i_j = \sqrt{\frac{4k_b \cdot T_n}{R_{sh}}}$$

k_b Boltzmann constant $1.38 \cdot 10^{-23} \text{ J/K}$

q Electron Charge $1.6 \cdot 10^{-19} \text{ C}$

T_n Temperature in Kelvin (25C)

f_p Transconductance bandwidth

R_{sh} Shunt Resistance in photodiode

I_D Dark Current in photodiode

I_L Photo current in photodiode

Shot noise (dark)


$$i_{sD} = \sqrt{2q \cdot I_D}$$

Shot noise (w . Light)

$$i_{sL} = \sqrt{2q \cdot I_L}$$

Total Diode Current Noise
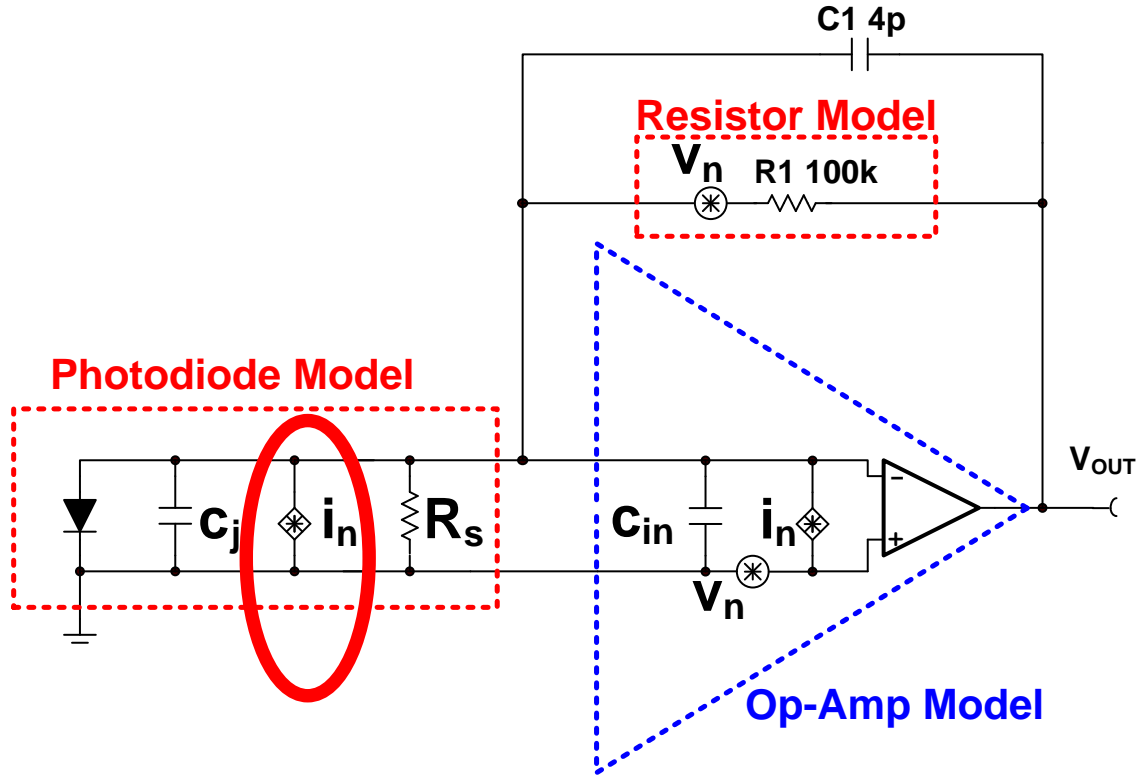
$$i_n = \sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2}$$






Noise Gain

Simplify the model to compute Noise Gain

$$\text{Noise_Gain} = \frac{V_{\text{out}}}{V_n}$$

Gain seen by the noise voltage source.

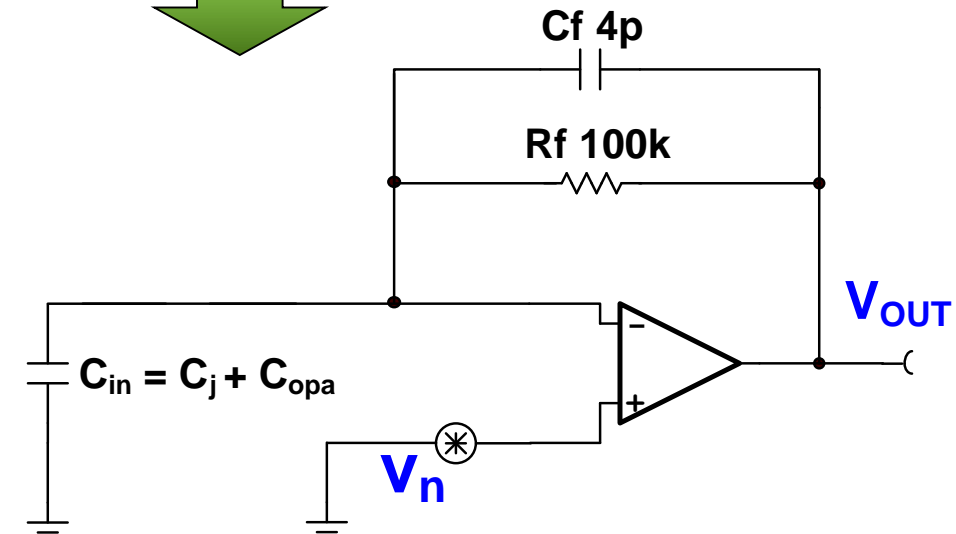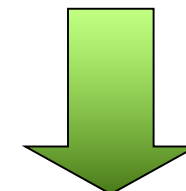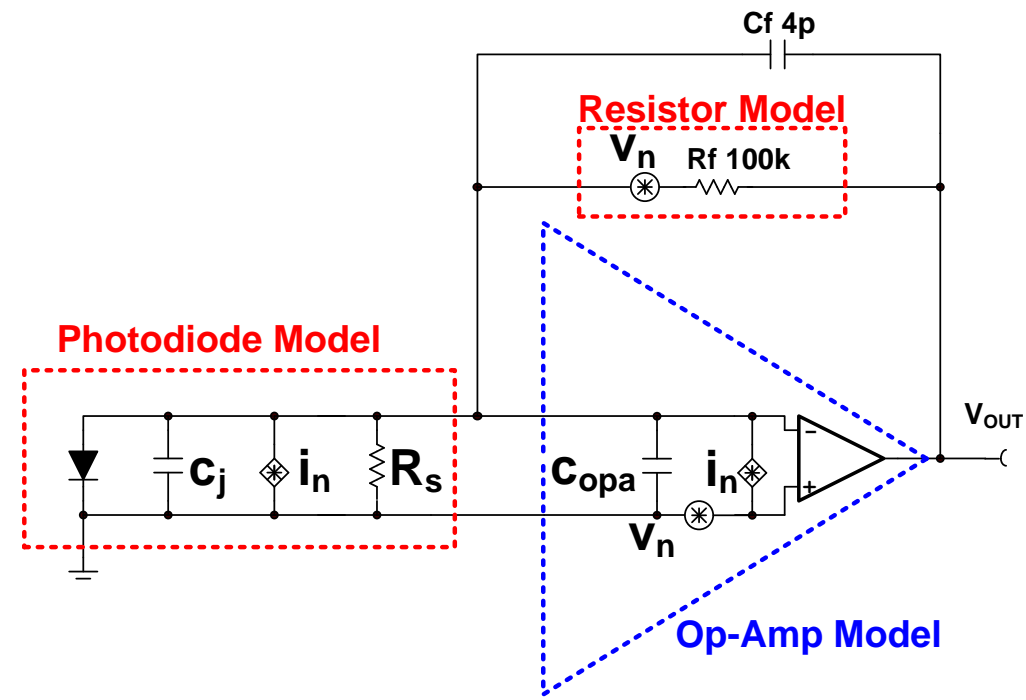

Noise Gain

Nodal Analysis on transimpedance amp

$$\frac{V_n}{\frac{1}{s \cdot C_{in}}} + \frac{(V_n - V_{out})}{R_f} + \frac{V_n - V_{out}}{\frac{1}{s \cdot C_f}} = 0$$

Solve for noise gain V_{out} / V_n



$$\frac{V_{out}}{V_n} = \frac{R_f \cdot (C_f + C_{in}) \cdot s + 1}{C_f \cdot R_f \cdot s + 1}$$

The numerator contains a **Zero**


$$f_z = \frac{1}{2\pi R_f (C_f + C_{in})}$$

The denominator contains a **Pole**

$$f_p = \frac{1}{2\pi R_f \cdot C_f}$$

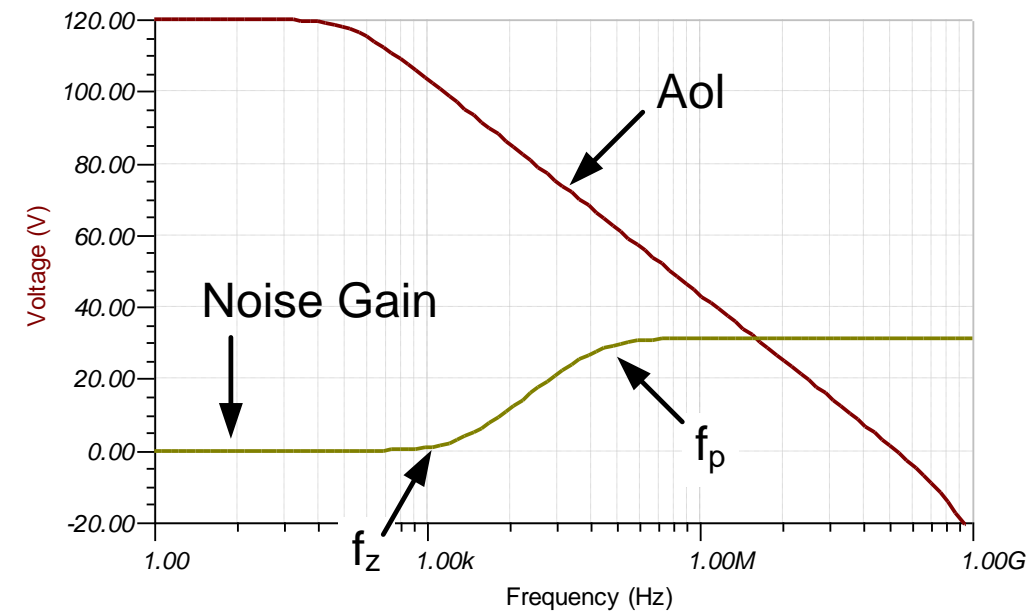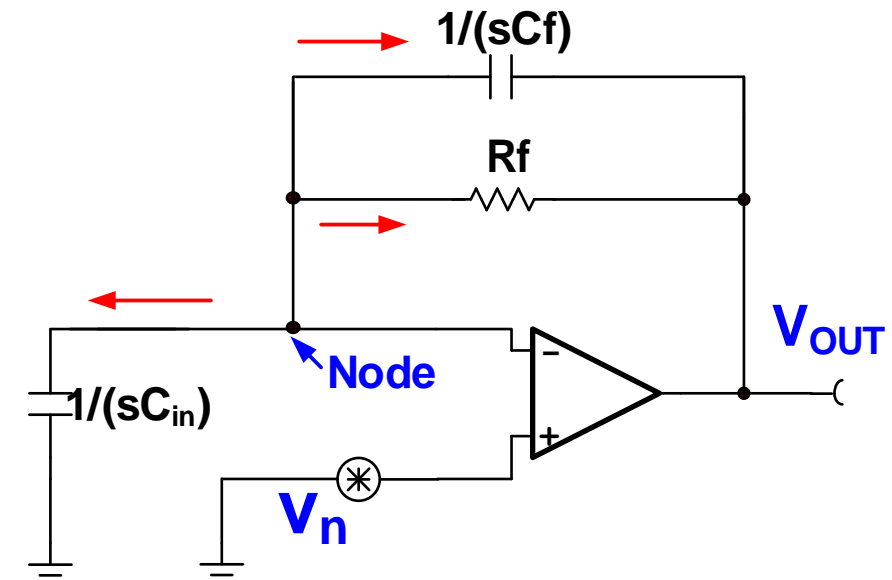

Noise Gain

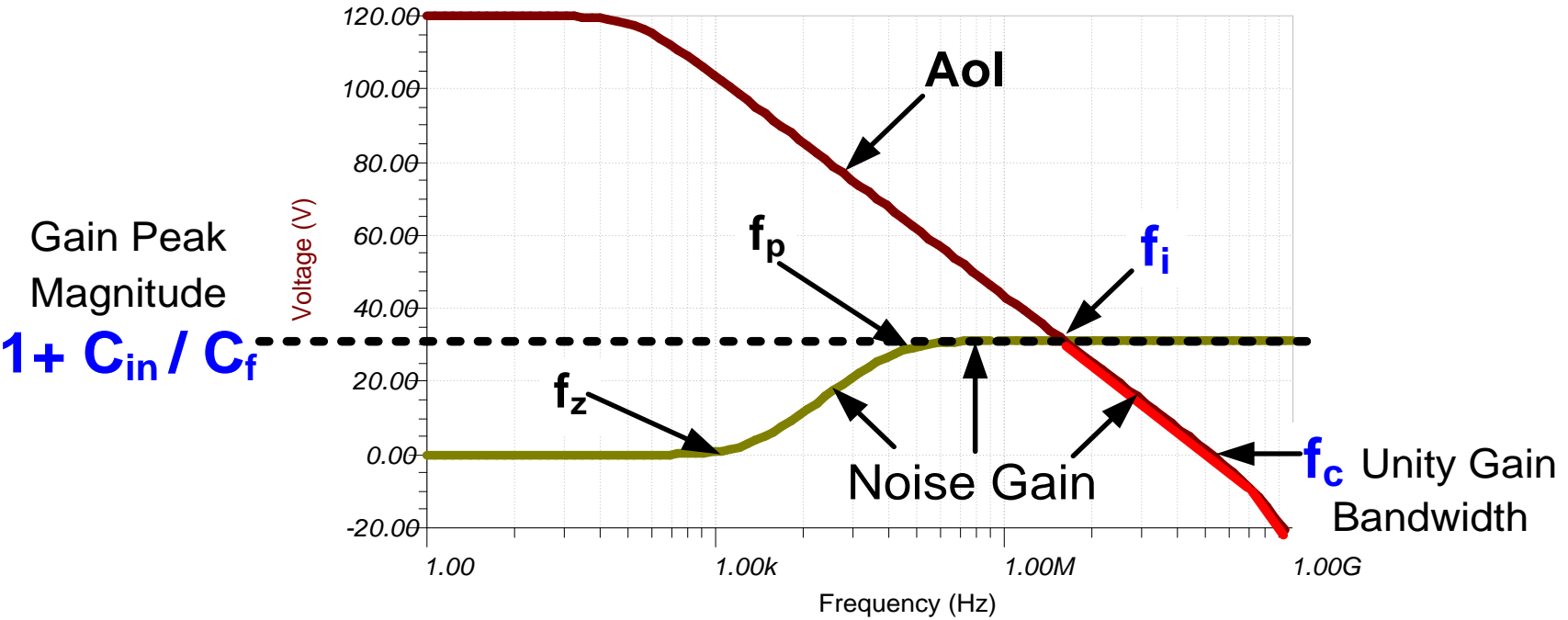

$$f_i = \frac{C_f}{C_i + C_f} \cdot f_c$$

Intersection of the noise gain curve with the Aol Curve

$$f_c$$





Unity Gain Bandwidth from Op-Amp Data Sheet

$$GPM = 1 + \frac{C_{in}}{C_f}$$


Gain Peak Magnitude

Noise Gain

Op-Amp
Voltage Noise
(Data Sheet)

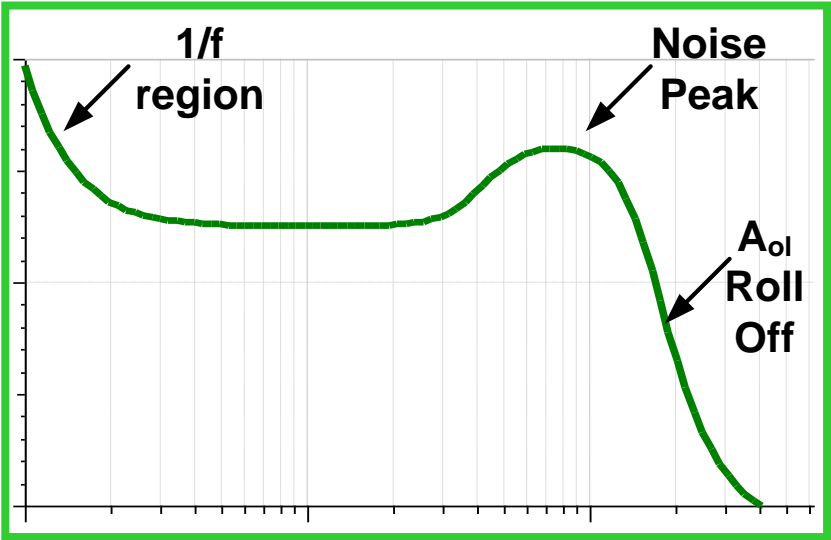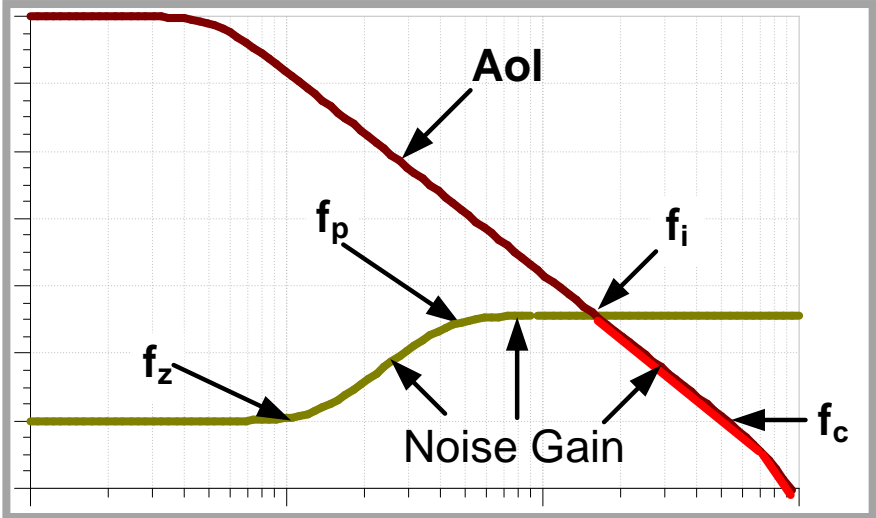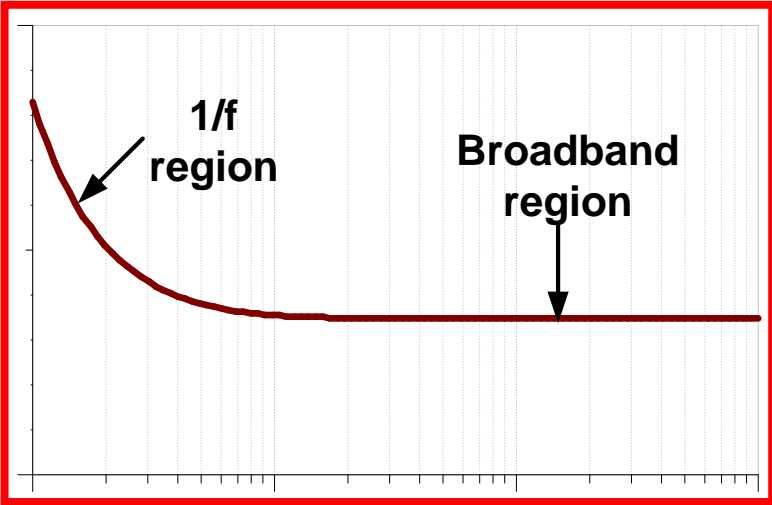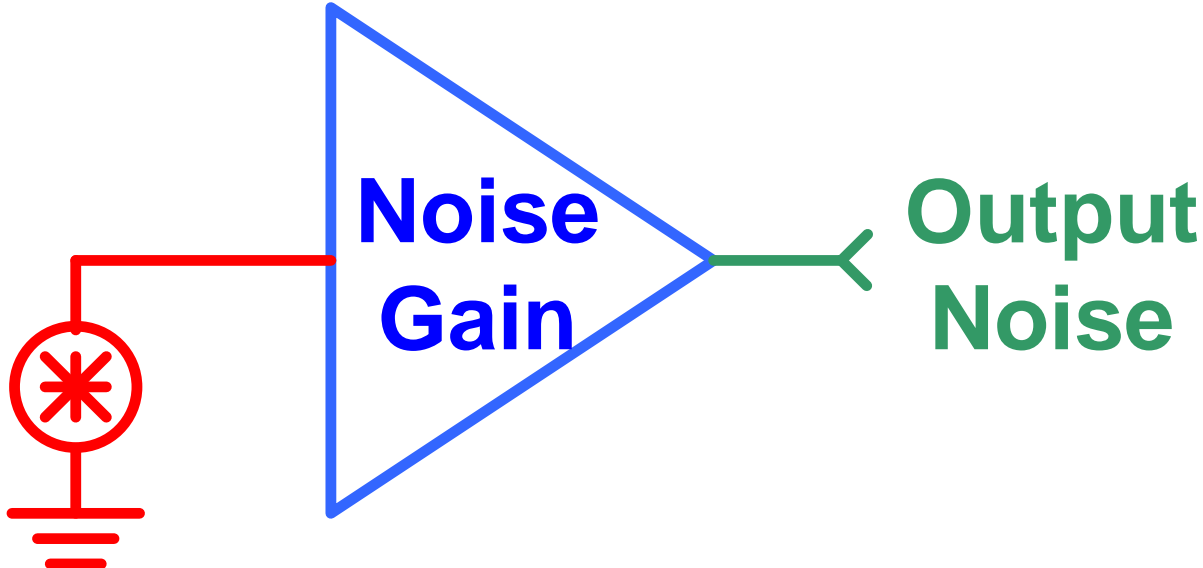

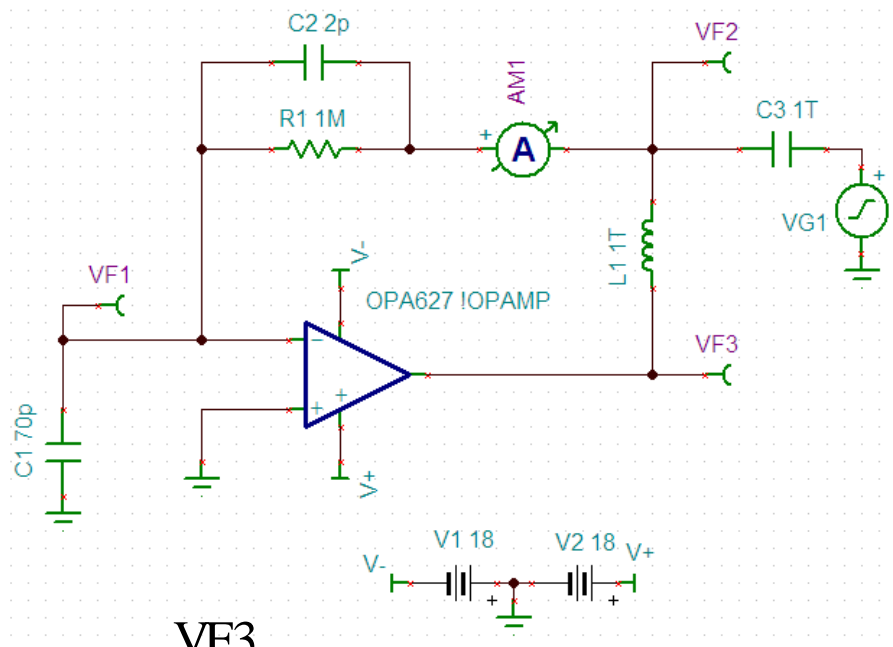Simulating Noise gain and noise bandwidth




- Break the loop to measure Aol, 1/B, and I to V Gain

$$A_{ol} = \frac{VF3}{VF1}$$


$$\text{Noise_Gain} = \frac{1}{\beta} = \frac{VF2}{VF1}$$

$$I_to_V_Gain = \frac{VF3}{AM1}$$

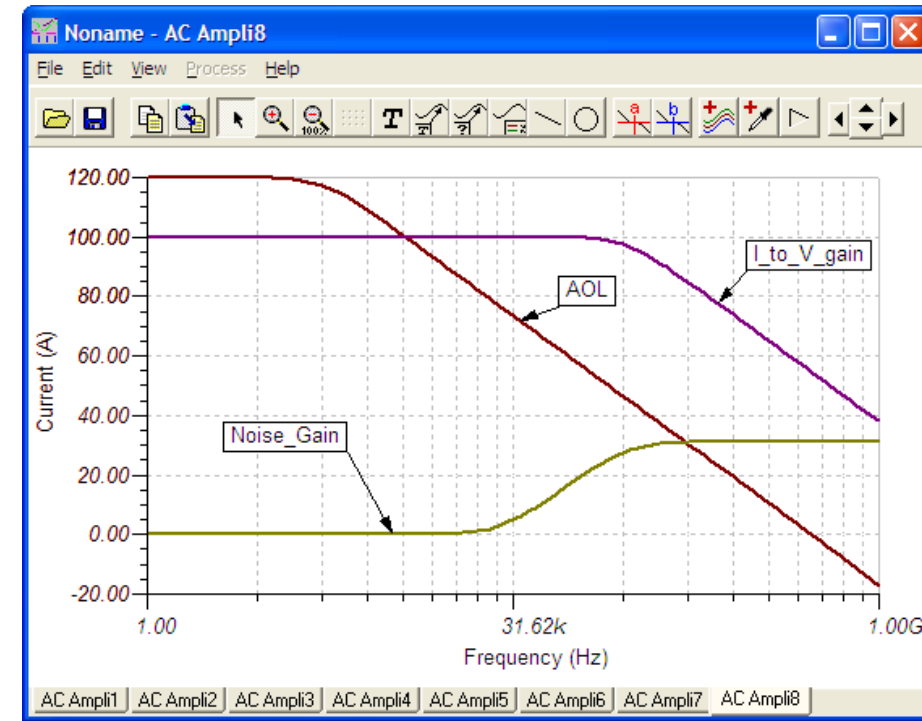

Voltage Noise e_{ni} , e_{no} and E_n
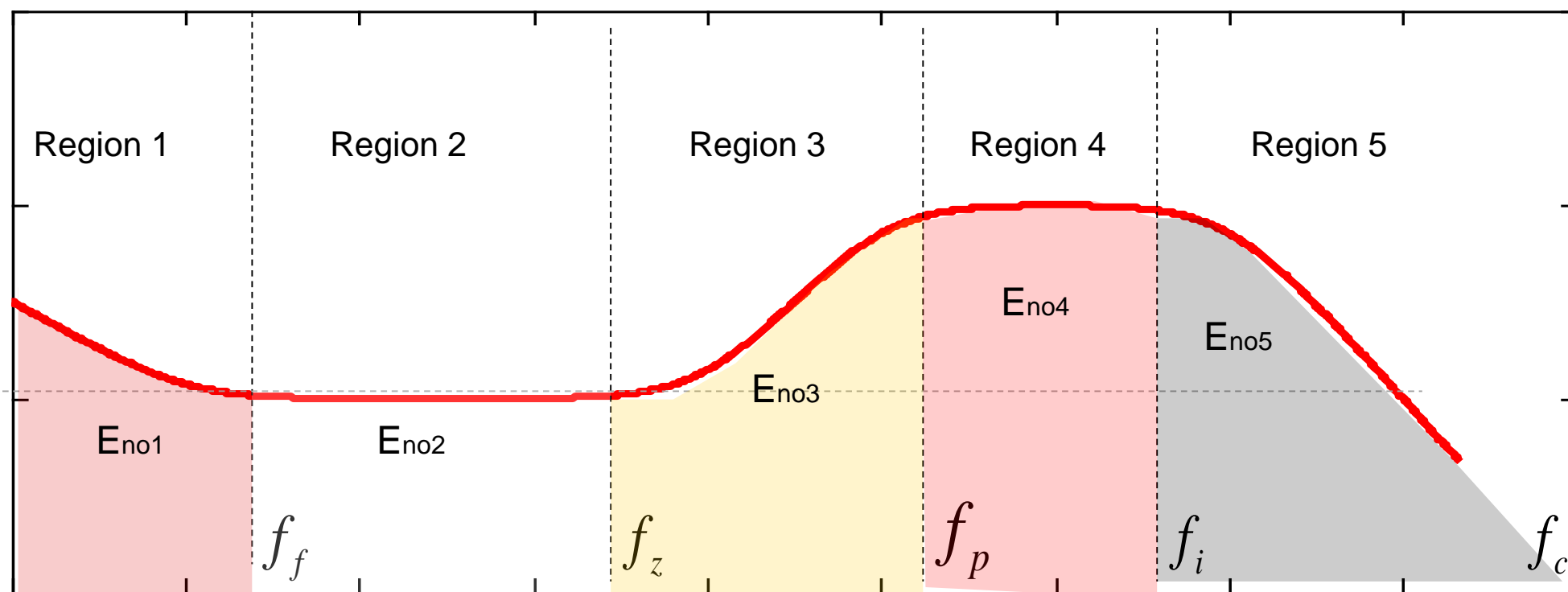
$$e_{no} = A_n \cdot e_{ni} = \frac{\left(1 + \frac{s}{\omega_z}\right) \cdot \sqrt{1 + \frac{\omega_f}{s}}}{\left(1 + \frac{s}{\omega_p}\right) \cdot \left(1 + \frac{s}{\omega_i}\right)}$$



Voltage Noise e_{ni} , e_{no} and E_{no}

Region 1 noise:
$$E_{noe1}^2 = \int_{f_L}^{f_f} \frac{e_{nif}^2 \cdot f_f}{f} d_f = e_{nif}^2 f_f \ln \frac{f_f}{f_L}$$

Region 2 noise:
$$E_{noe2}^2 = \int_{f_f}^{f_z} e_{nif}^2 d_f = e_{nif}^2 (f_z - f_f)$$


Region 3 noise:
$$E_{noe3}^2 = \int_{f_z}^{f_p} \frac{e_{nif}^2 \cdot f^2}{f_z^2} d_f = \left(\frac{e_{nif}}{f_z} \right)^2 \frac{f_p^3 - f_z^3}{3}$$

Region 4 noise:
$$E_{noe4}^2 = \int_{f_p}^{f_i} \left(\frac{e_{nif}}{\beta} \right)^2 d_f = \left(e_{nif} \cdot \frac{C_i + C_f}{C_f} \right)^2 (f_i - f_p)$$


Region 5 noise:
$$E_{noe5}^2 = \int_{f_i}^{\infty} \left(\frac{e_{nif} f_c}{f} \right)^2 d_f = \frac{(e_{nif} f_c)^2}{f_i}$$

Total voltage noise:
$$E_{noe}^2 = E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2$$

Voltage Noise e_{ni} , e_{no} and E_{no}

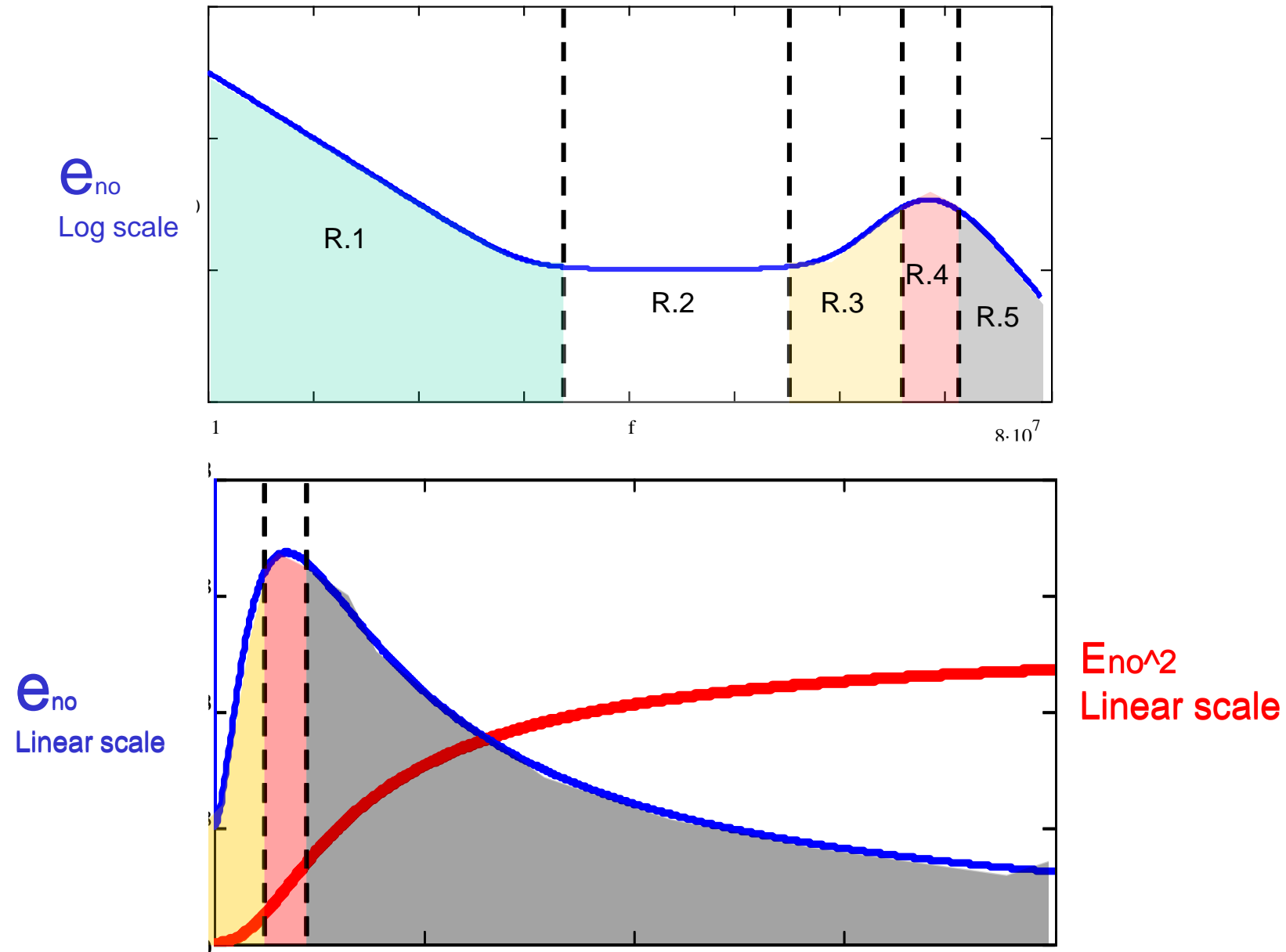


Resistor Noise and Current Noise

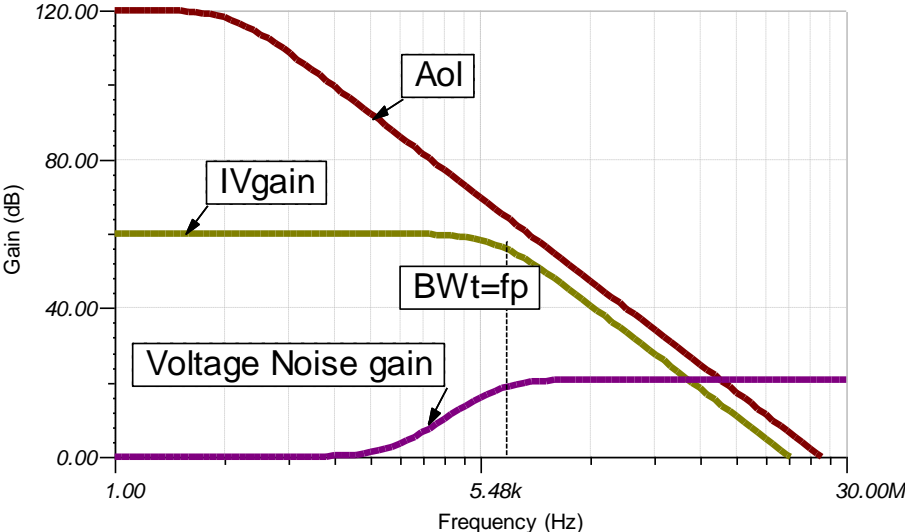

Current noise and resistor noise are limited by the transimpedance (I-V gain) bandwidth

Poles	Kn
1	1.57
2	1.22
3	1.16

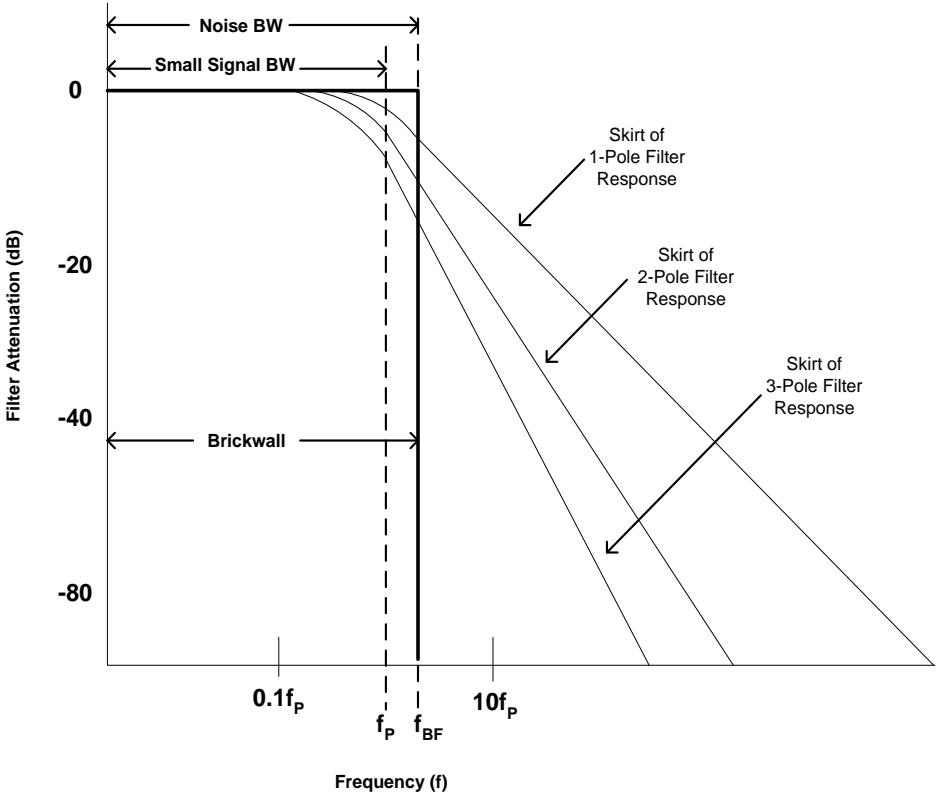


$$BW_n = K_n \cdot f_p$$

$$E_{noR} = \sqrt{4K \cdot T \cdot R_f \cdot BW_n}$$


$$E_{noI} = i_{ni} \cdot R_f \cdot BW_n$$

Bandwidth and Stability

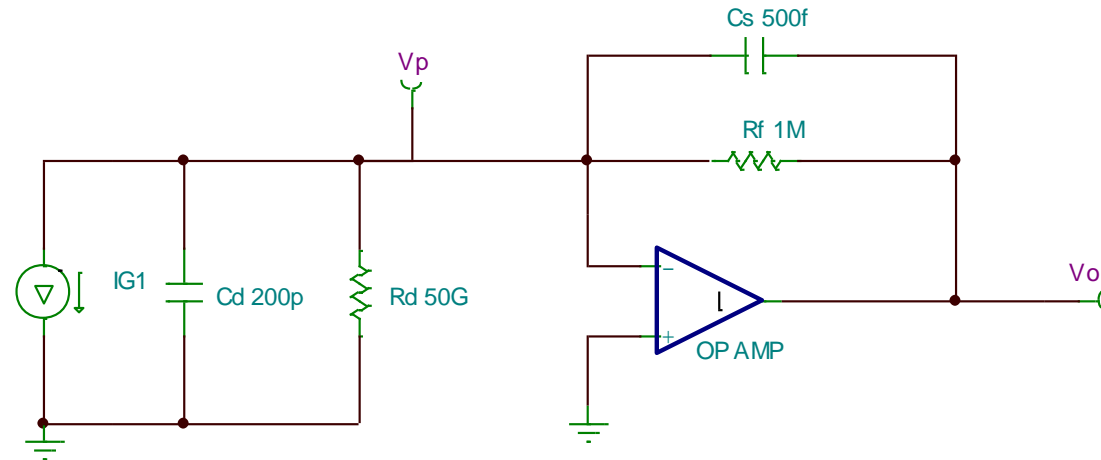Parasitic Capacitance Limits the Bandwidth



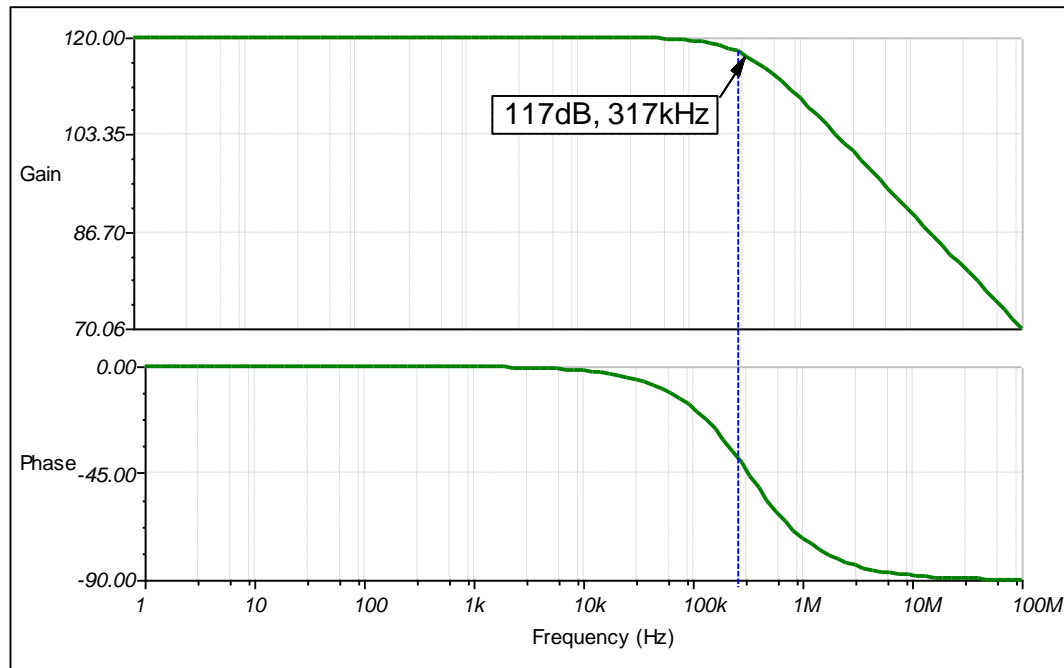
$$f_p = \frac{1}{2\pi R_f \cdot C_f} = 318\text{kHz}$$




- Max bandwidth with Min C_f
- Low C_f may be unstable
- Wide BW increases noise
- As shown $C_f=C_s$ (stray cap)


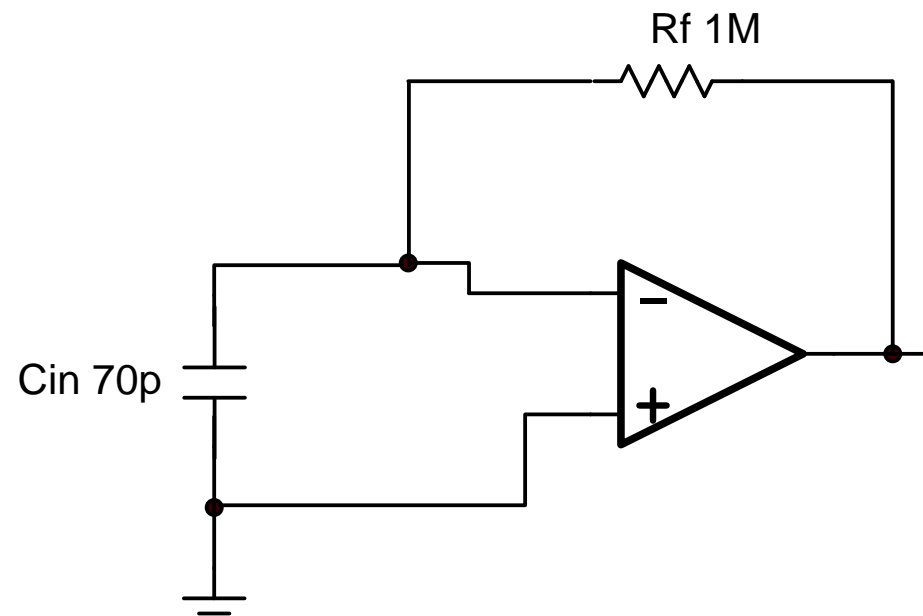
Feedback Capacitance Required for Stability



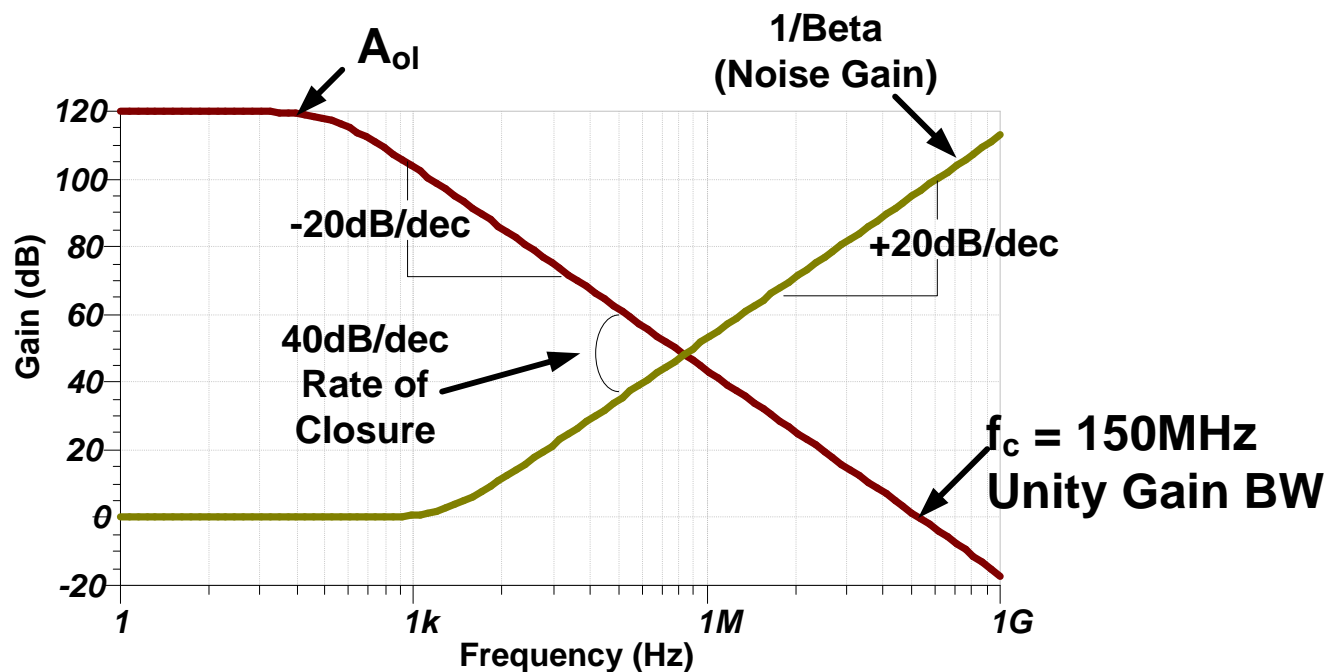- Noise Gain is key to stability
- Also called 1/Beta (in stability analysis)
- ROC = Rate of Closure
- $ROC = (A_{ol} \text{ slope}) - (1/\text{Beta slope})$
- Unstable when $ROC > 20\text{dB/decade}$





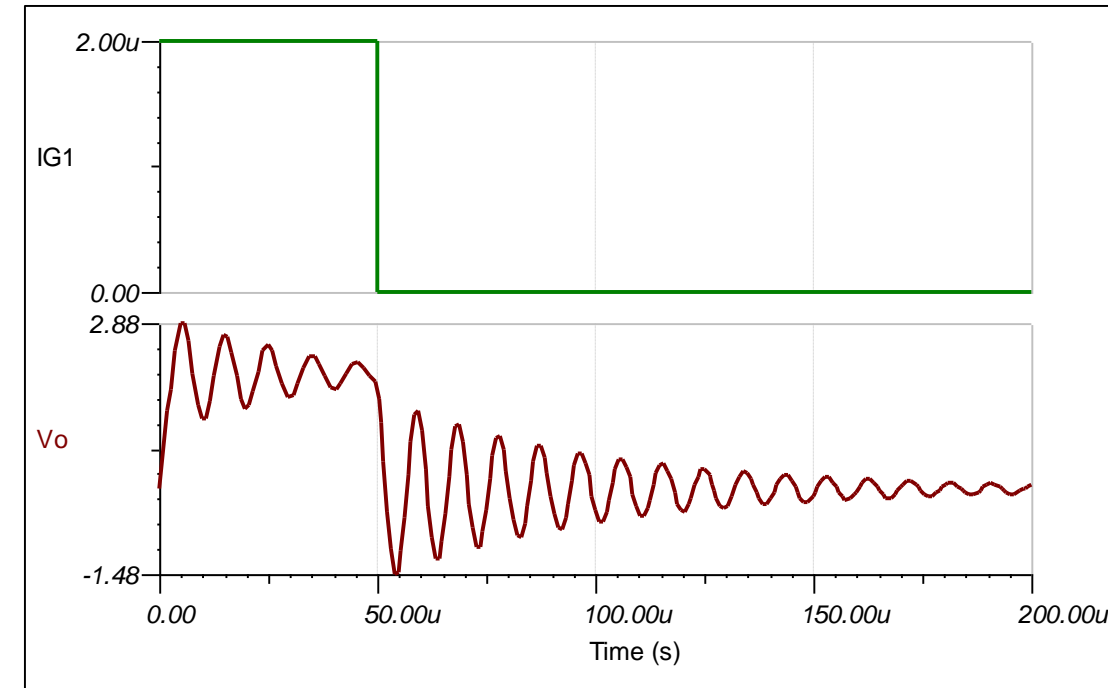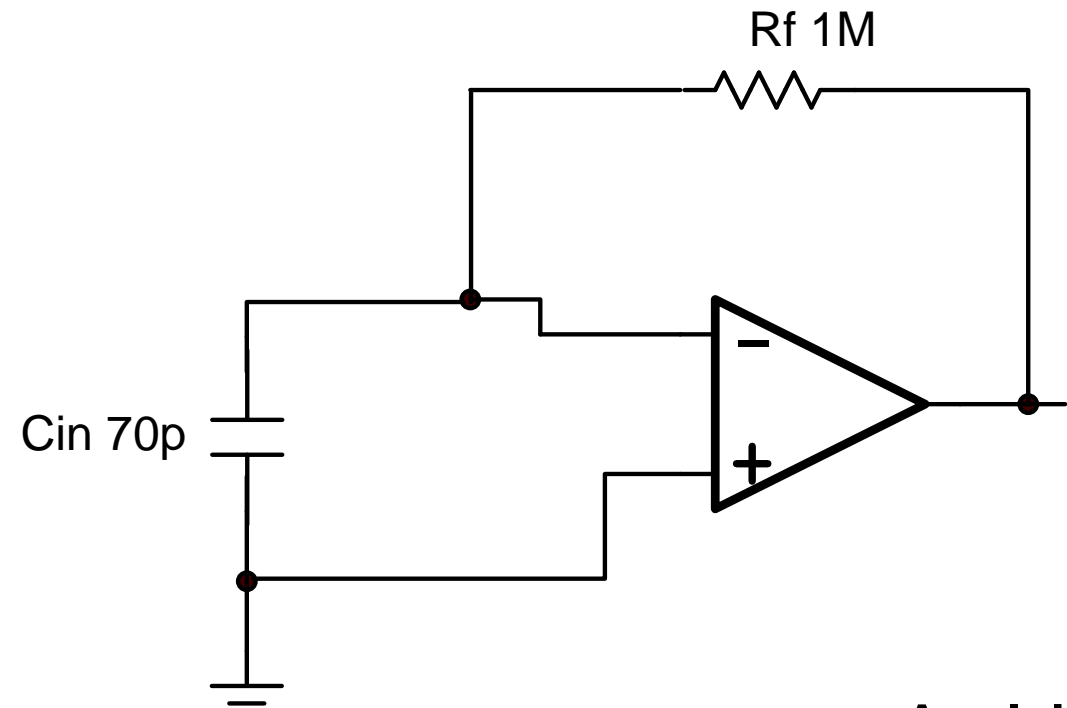Feedback Capacitance Required for Stability



Applying a Step Input shows instability at output

Choosing a Minimum Cf for Stability

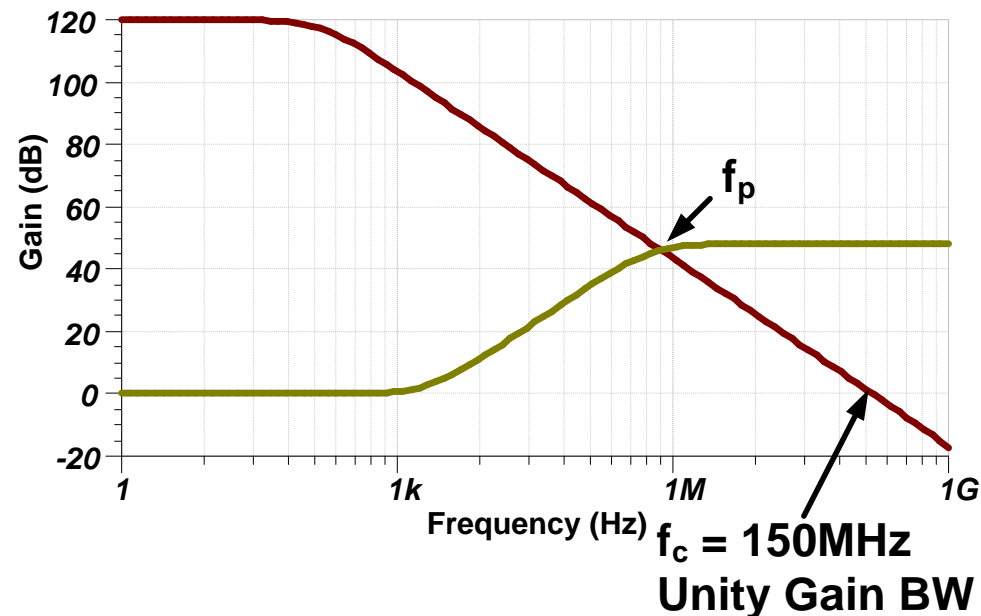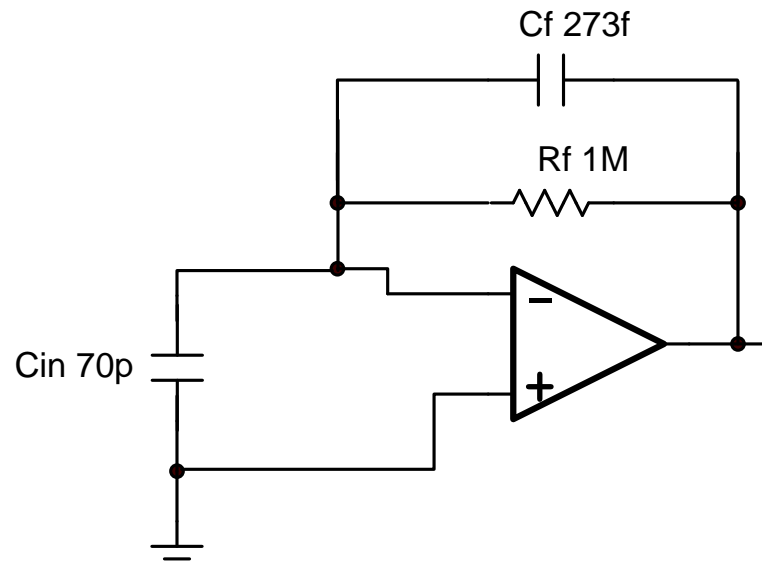

$$f_c = 150MHz$$

Op-amp Unity Gain Bandwidth

$$C_{in} = 70pF$$

Total input capacitance

$$R_f = 1M\Omega$$

Feedback resistance

$$C_f = \sqrt{\frac{C_{in}}{2\pi \cdot R_f \cdot f_c}} = 272.5fF$$

Simplified equation for minimum feedback cap
Assumes $C_{in} \gg C_f$

$$C_c = \frac{1}{2\pi \cdot R_f \cdot f_c}$$


Intermediate calculation used in more exact formula

$$C_{fe} = \frac{C_c}{2} \cdot \left(1 + \sqrt{1 + \frac{4C_{in}}{C_c}} \right) = 273.1fF$$

More exact formula for feedback capacitance

OPA827 Hand Calculation

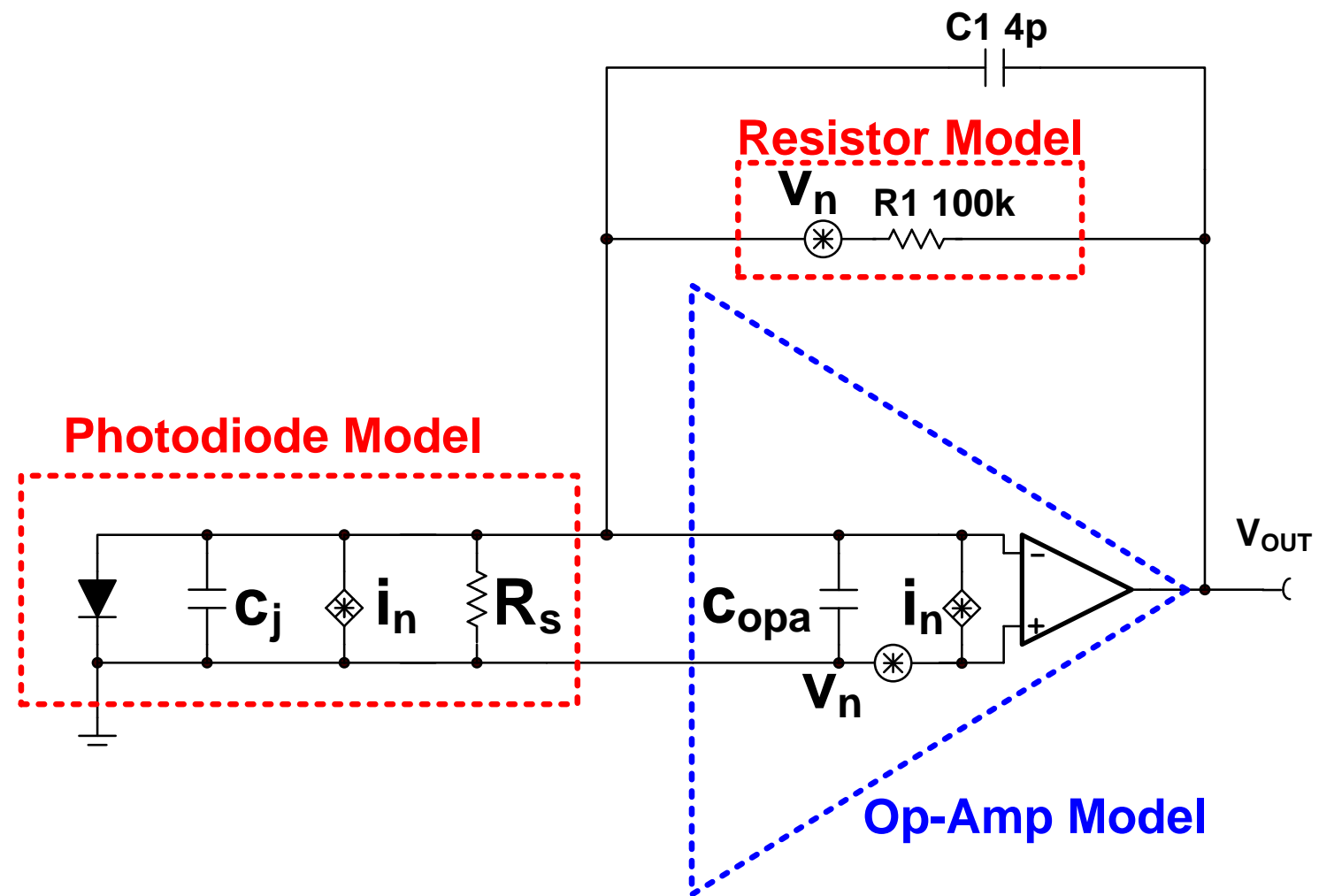Noise Model for Simple Transimpedance Amp




Example Photodiode: PDB-C158

ABSOLUTE MAXIMUM RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	PARAMETER	MIN	MAX	UNITS
V_{BR}	Reverse Voltage		50	V
T_{STG}	Storage Temperature	-40	+100	°C
T_O	Operating Temperature	-40	+80	°C
T_S	Soldering Temperature*		+260	°C

* 1/16 inch from case for 3 seconds max.

SPECTRAL RESPONSE

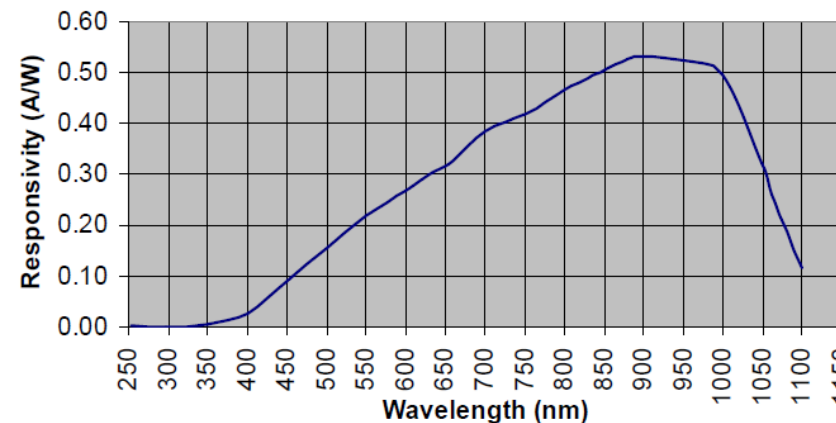

ELECTRO-OPTICAL CHARACTERISTICS RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	CHARACTERISTIC	TEST CONDITIONS	MIN	TYP	MAX	UNITS
I_{SC}	Short Circuit Current	$H = 100 \text{ fc}, 2850 \text{ K}$	100	145		μA
I_D	Dark Current	$V_R = 10 \text{ V}$		2	30	nA
R_{SH}	Shunt Resistance	$V_R = 10 \text{ mV}$	100	150		$\text{M}\Omega$
C_J	Junction Capacitance	$V_R = 10 \text{ V}, f = 1 \text{ MHz}$		10	25	pF
λ_{range}	Spectral Application Range	Spot Scan	400		1100	nm
V_{BR}	Breakdown Voltage	$I = 10 \mu\text{A}$	30	75		V
NEP	Noise Equivalent Power	$V_R = 10 \text{ V} @ \lambda = \text{Peak}$		4.4×10^{-14}		$\text{W}/\sqrt{\text{Hz}}$
t_r	Response Time	$R_L = 1 \text{ K}\Omega, V_R = 10 \text{ V}$		50		nS

Unfortunately C_j is not specified at $V_r=0\text{V}$.

We called the manufacturer for this info $C_j=70\text{pF}$ for $V_r=0\text{V}$

Calculate Diode Current Noise

Thermal (Johnson Noise)

$$\sqrt{\frac{4k_b \cdot T_n}{R_{sh}}} = 10.472 \times 10^{-15} \frac{A}{\sqrt{Hz}}$$

Shot noise (dark)

$$\sqrt{2q \cdot I_D} = 25.314 \times 10^{-15} \cdot \frac{A}{\sqrt{Hz}}$$

Shot noise (w . Light)

$$i_{sL} := \sqrt{2q \cdot I_L} = 0$$

Total Diode Current Noise

$$\sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2} = 27.395 \times 10^{-15} \cdot \frac{A}{\sqrt{Hz}}$$

$$k_b := 1.3810^{-23} \frac{J}{K}$$

Boltzmann constant

$$q := 1.60210^{-19} C$$

One electron Charge

$$T_n := 298K$$

Temperature in Kelvin (25C)

$$f_p := 397.887 \times 10^3 Hz$$

Transconductance bandwidth

$$R_{sh} := 150 \cdot 10^6 \Omega$$


Shunt Resistance in photodiode

$$I_D := 2 \cdot 10^{-9} A$$


Dark Current in photodiode

$$I_L := 0A$$

Photo current in photodiode
(our measurements are dark)

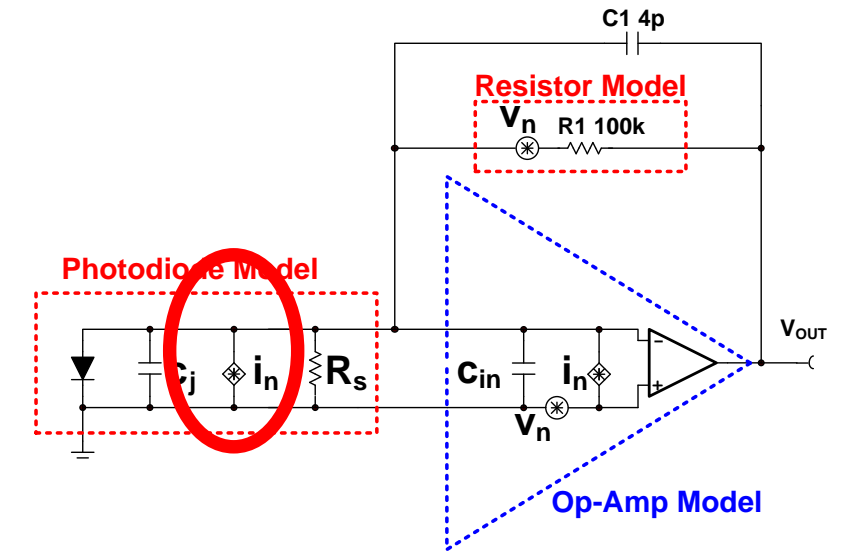

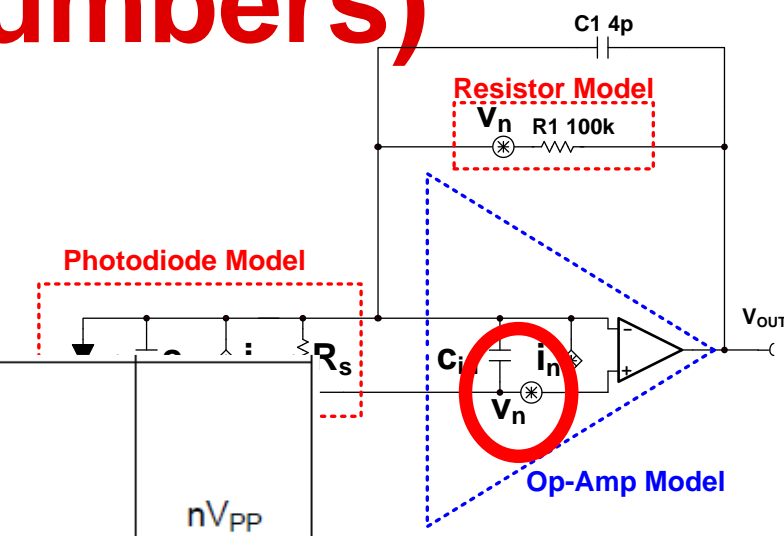OPA827 Noise Hand Calculation (key numbers)



NOISE								
Input Voltage Noise:								
f = 0.1Hz to 10Hz	e_n	$V_S = \pm 18V, V_{CM} = 0V$		250		250	nV _{PP}	
Input Voltage Noise Density:								
f = 1kHz	e_n	$V_S = \pm 18V, V_{CM} = 0V$		4		4	nV/ \sqrt{Hz}	
f = 10kHz	e_n	$V_S = \pm 18V, V_{CM} = 0V$		3.8		3.8	nV/ \sqrt{Hz}	
Input Current Noise Density:								
f = 1kHz	i_n	$V_S = \pm 18V, V_{CM} = 0V$		2.2		2.2	fA/ \sqrt{Hz}	
INPUT IMPEDANCE								
Differential				$10^{13} \parallel 9$		$10^{13} \parallel 9$	$\Omega \parallel pF$	
Common-Mode				$10^{13} \parallel 9$		$10^{13} \parallel 9$	$\Omega \parallel pF$	
OPEN-LOOP GAIN								
Open-Loop Voltage Gain	A_{OL}	$(V-)+3V \leq V_O \leq (V+)-3V, R_L = 1k\Omega$	120	126		120	126	dB
Over Temperature		$(V-)+3V \leq V_O \leq (V+)-3V, R_L = 1k\Omega$	114			114		dB
FREQUENCY RESPONSE								
Gain-Bandwidth Product	GBW	G = +1		22		22		MHz

OPA827 Noise Hand Calculation

$C_j := 70\text{pF}$ Photodiode Junction Capacitance
(from photodiode manufacturer)

$C_{opa} := 18\text{pF}$ Opamp input capacitance
(OPA827 Data Sheet)

$C_i := C_j + C_{opa}$ Total input capacitance

$f_c := 22\text{MHz}$ Unity Gain Bandwidth
(OPA827 Data Sheet)



$R_f := 100\text{k}\Omega$ Feedback resistance

$C_f := 4\text{pF}$ Feedback capacitor

$e_{nif} := 3.8 \frac{\text{nV}}{\sqrt{\text{Hz}}}$ Broadband Noise Spectral Density
(OPA827 Data Sheet)

$f_L := .1\text{Hz}$ Lower bound on frequency (1/f region)
(arbitrary lower bound of frequency)

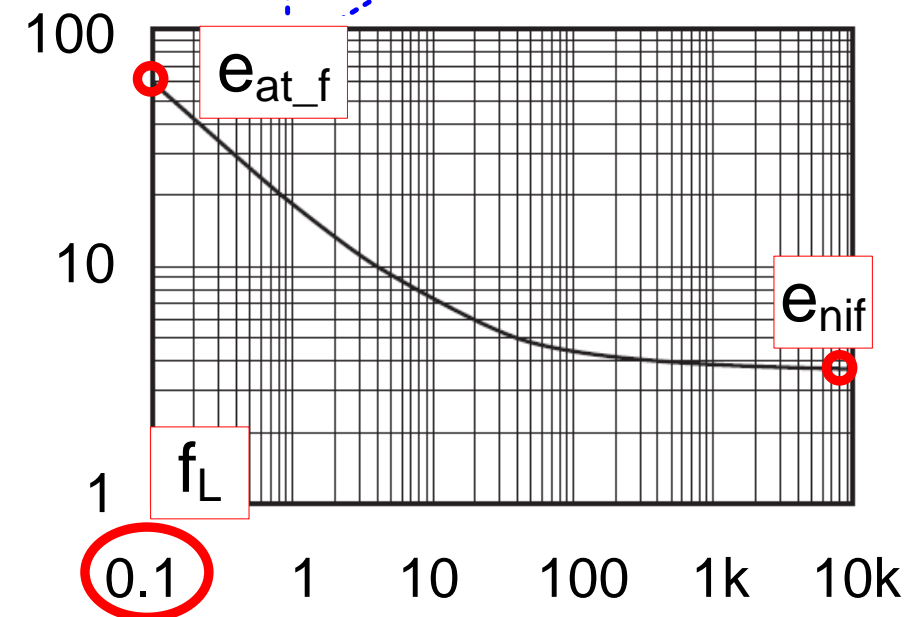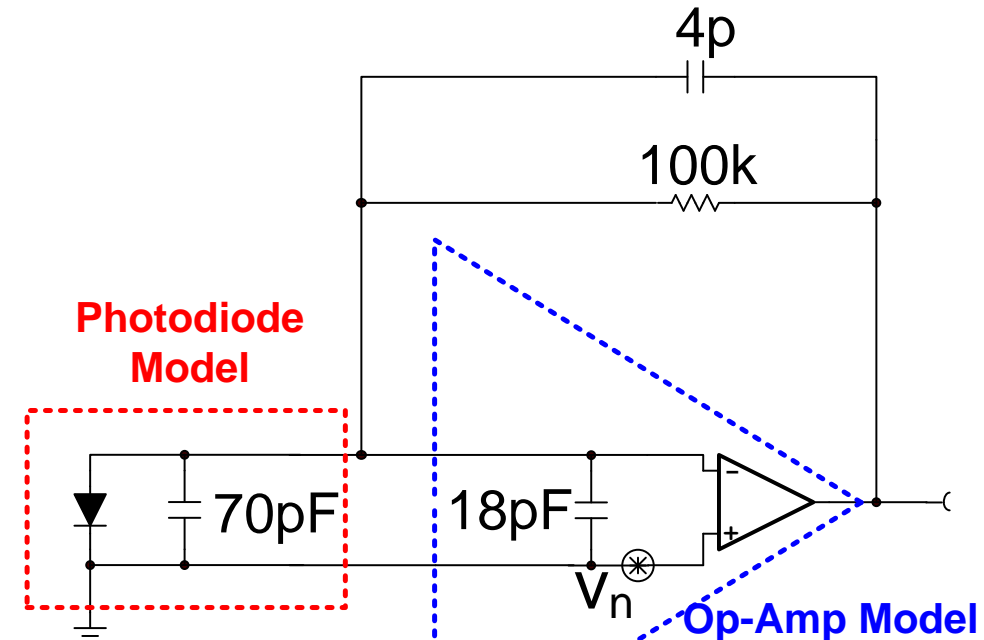$e_{at_f} := 60 \frac{\text{nV}}{\sqrt{\text{Hz}}}$ Flicker noise measured at f_L
(OPA827 Data Sheet Noise Curve)




Poles and Zeros in Noise Gain Curve

$$f_z := \frac{1}{2\pi R_f \cdot (C_i + C_f)} = 17.299 \times 10^3 \text{ Hz}$$

$$f_p := \frac{1}{2\pi R_f \cdot C_f} = 397.887 \times 10^3 \text{ Hz}$$

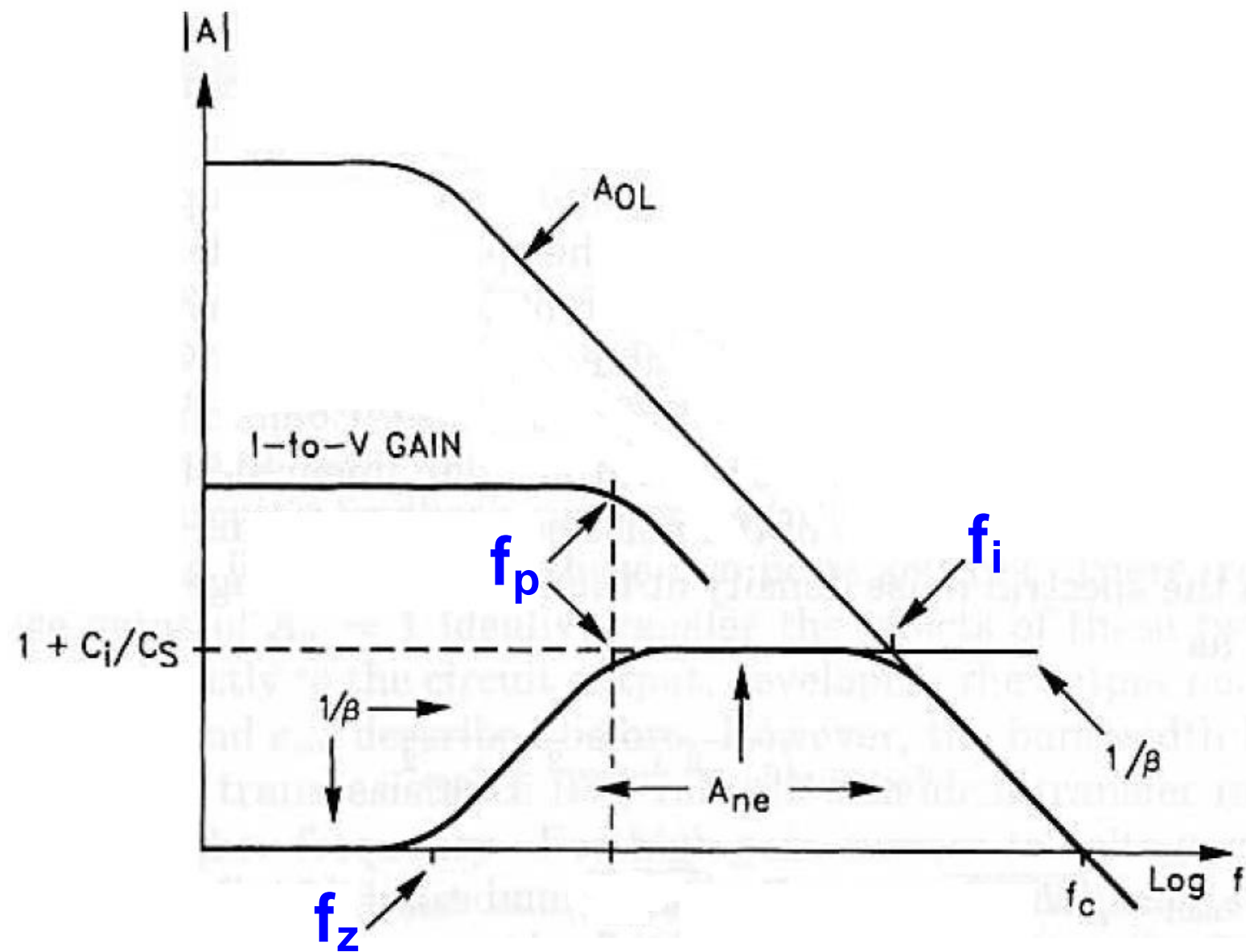
$$f_i := \frac{C_f}{C_i + C_f} \cdot f_c = 956.522 \times 10^3 \text{ Hz}$$



1/f (flicker) Noise Corner

$$e_{\text{fnorm}} := e_{\text{at_f}} \sqrt{f_L} = 18.974 \times 10^{-9} \text{ V}$$
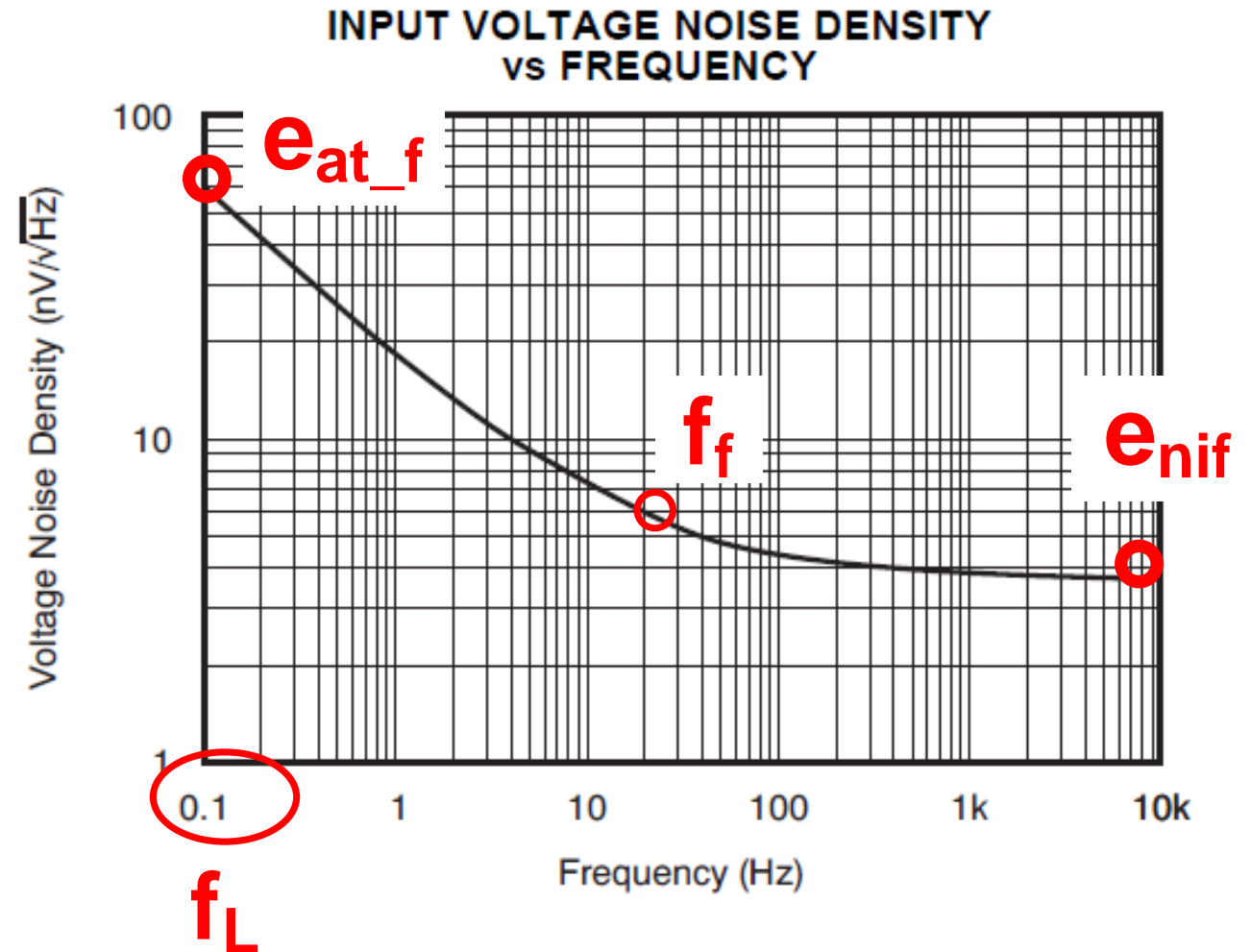
$$f_f := \frac{e_{\text{fnorm}}^2}{e_{\text{nif}}^2} = 24.93 \text{ Hz}$$



Output Noise from OPA Noise Voltage

$$E_{noe1} := \sqrt{e_{nif}^2 \cdot f_f \cdot \ln\left(\frac{f_f}{f_L}\right)} = 44.573 \times 10^{-9} \text{ V}$$


$$E_{noe2} := \sqrt{e_{nif}^2 \cdot (f_z - f_f)} = 499.444 \times 10^{-9} \text{ V}$$

$$E_{noe3} := \sqrt{\left(\frac{e_{nif}}{f_z}\right)^2 \cdot \frac{f_p^3 - f_z^3}{3}} = 31.828 \times 10^{-6} \text{ V}$$

$$E_{noe4} := \sqrt{\left(e_{nif} \frac{C_i + C_f}{C_f}\right)^2 (f_i - f_p)} = 65.324 \times 10^{-6} \text{ V}$$

$$E_{noe5} := \sqrt{\frac{(e_{nif} f_c)^2}{f_i}} = 85.479 \times 10^{-6} \text{ V}$$
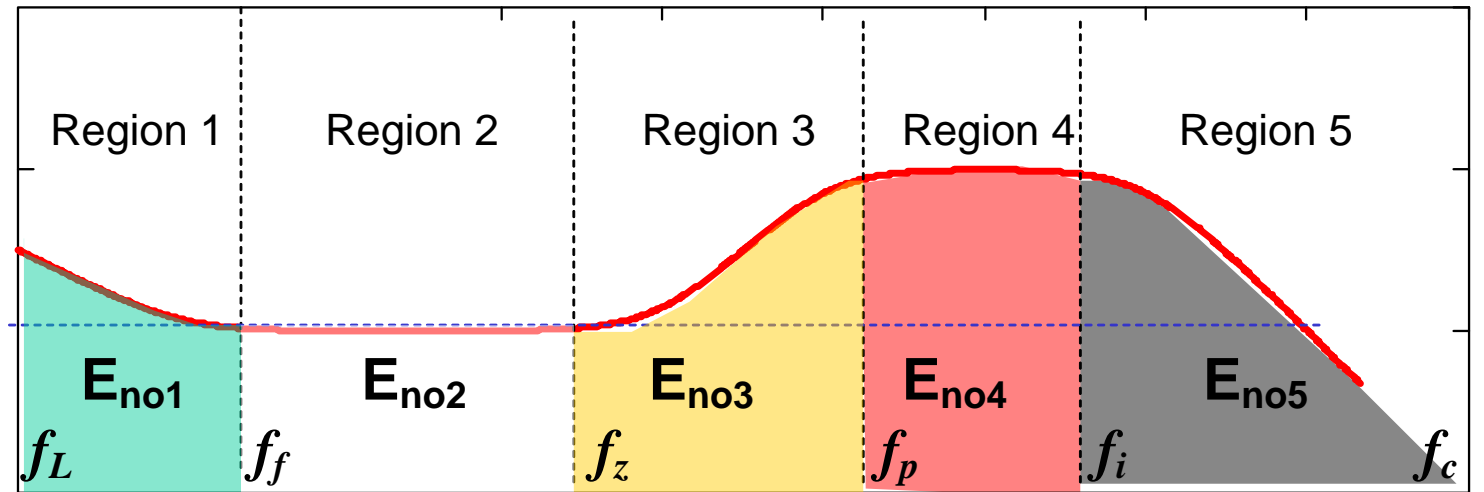
$$E_{noe} := \sqrt{E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2} = 112.193 \times 10^{-6} \text{ V}$$



Thermal (Resistor) Noise at Output

$$R_f := 100 \cdot 10^3 \Omega$$

Feedback Resistance

$$k_b := 1.38 \cdot 10^{-23} \frac{\text{J}}{\text{K}}$$

Boltzmann constant

$$T_n := 298 \text{K}$$

Temperature in Kelvin (25C)

$$f_p := 397.887 \times 10^3 \text{ Hz}$$

Transconductance bandwidth

$$K_n := 1.57$$


Noise Current from OPA827 data sheet

$$BW_n := K_n \cdot f_p$$

Noise bandwidth (brick w all filter)


$$e_{n_r} := \sqrt{4k_b \cdot T_n \cdot R_f \cdot BW_n} = 32.056 \times 10^{-6} \text{ V}$$

Thermal noise at output

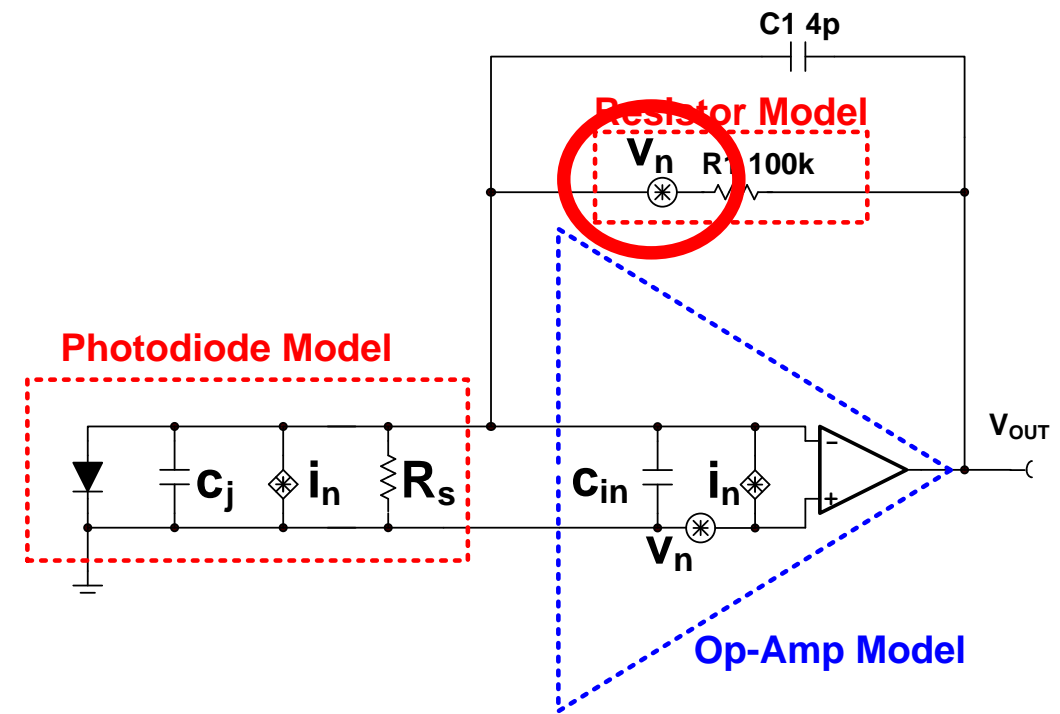

Current Noise to Voltage Noise at Output

EQUATION	DESCRIPTION
$R_f = 100 \times 10^3 \Omega$	Feedback resistance
$f_p = 397.887 \times 10^3 \text{ Hz}$	Transconductance bandwidth
$i_{n_opa} = 2.2 \times 10^{-15} \frac{\text{A}}{\sqrt{\text{Hz}}}$	Noise current from OPA827 data sheet
$i_{n_diode} = 27.395 \times 10^{-15} \frac{\text{A}}{\sqrt{\text{Hz}}}$	Noise current from diode (calculated)
$i_{n_total} = \sqrt{i_{n_opa}^2 + i_{n_diode}^2}$	Total noise current
$K_n = 1.57$	Noise bandwidth factor first order filter
$BW_n = K_n \times f_p = 624 \text{ kHz}$	Noise bandwidth (brick wall filter)
$E_{nol} = i_{n_total} \times R_f \times \sqrt{BW_n} = 2.17 \mu\text{V}$	Current noise at output

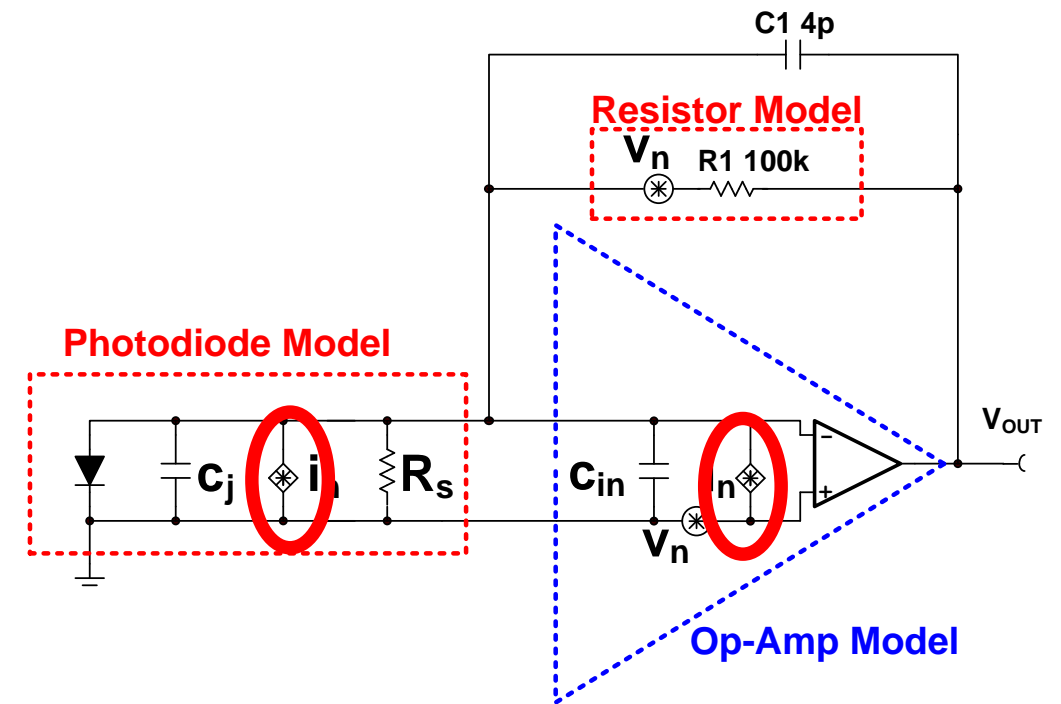

The Final Total Noise


$$E_{noe} := 112.193 \times 10^{-6} \text{ V} \quad \text{Op-Amp Voltage Noise}$$

$$E_{noR} := 32.056 \times 10^{-6} \text{ V} \quad \text{Resistor Noise}$$



$$E_{noI} := 2.172 \times 10^{-6} \text{ V} \quad \text{Op-Amp Current Noise}$$

$$E_{no} := \sqrt{E_{noR}^2 + E_{noI}^2 + E_{noe}^2} = 116.703 \times 10^{-6} \text{ V} \quad \text{Total Output Noise for OPA827 Transimpedance Amp}$$


Calculation vs Simulation

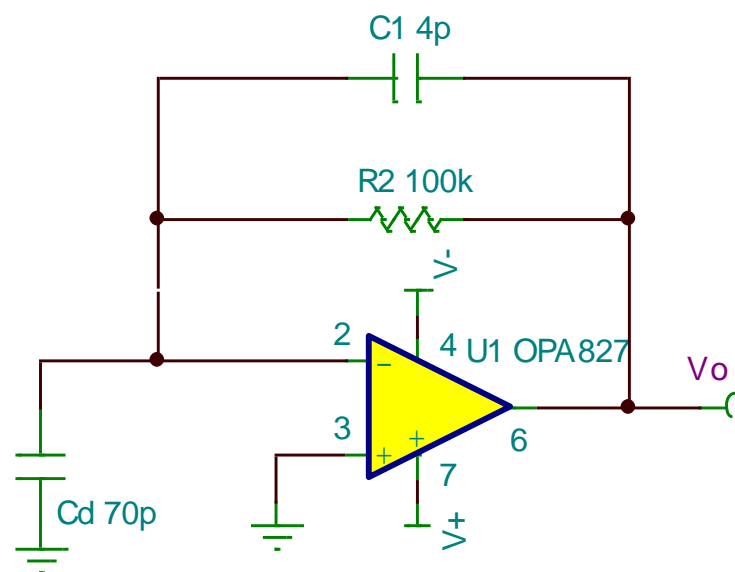

Calculated (rms)	Simulated (rms)
116.7uV	109.1uV

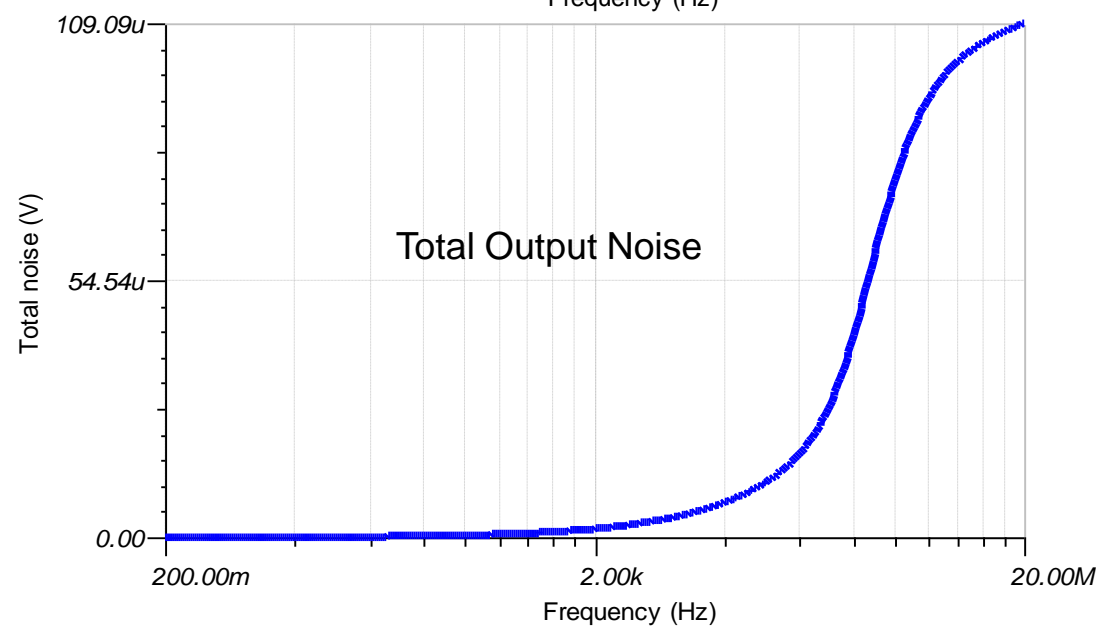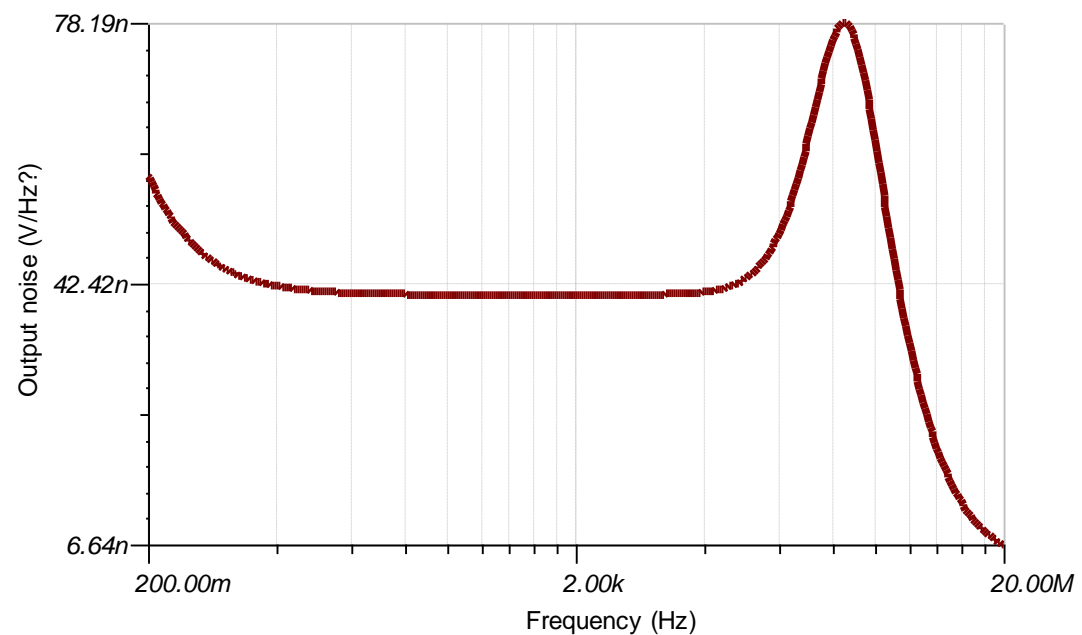

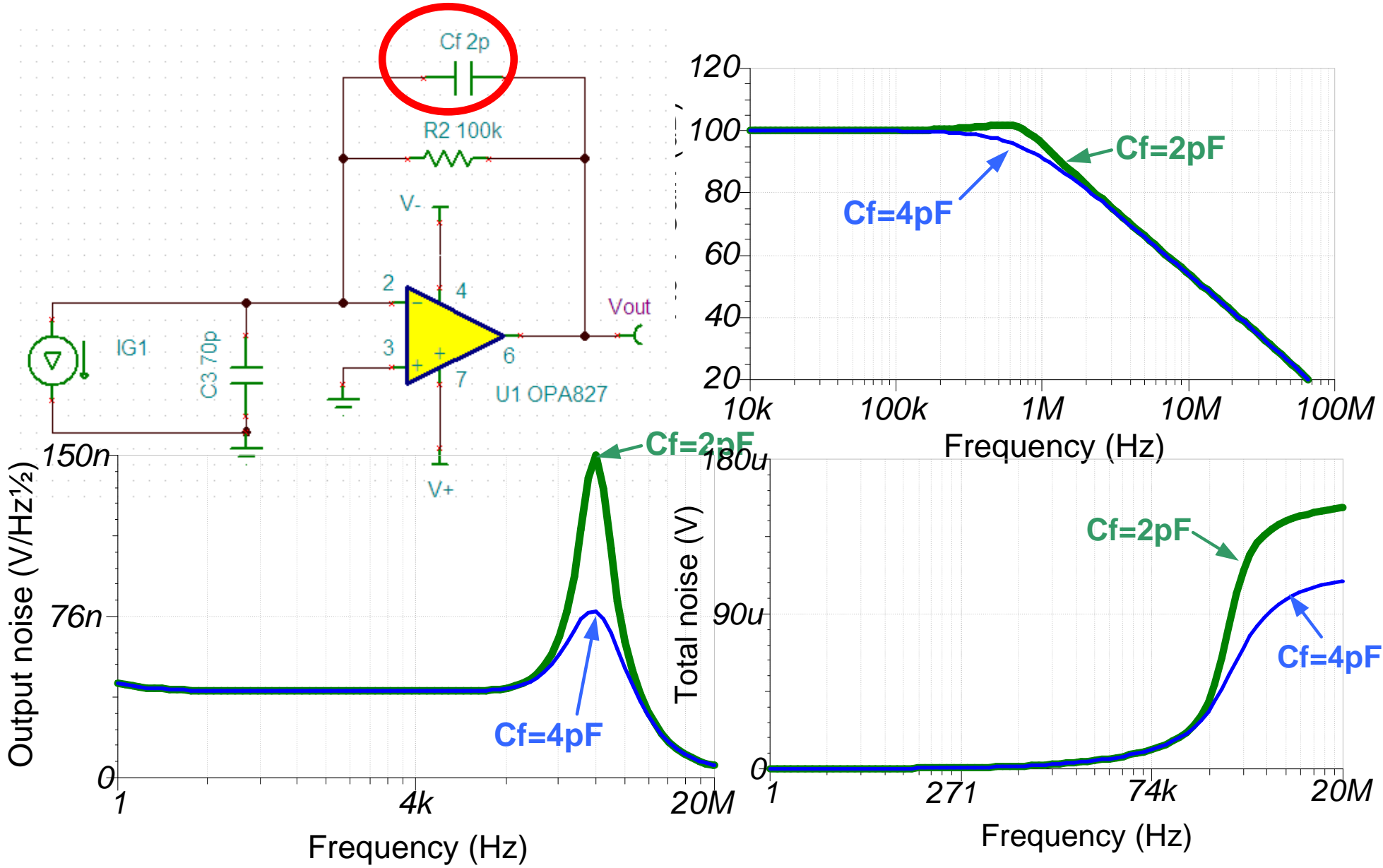
Reducing Noise (Higher Cf = Lower BW & Noise)



OPA827 Measurement Example

Validating Test Equipment Capability


**What is the
noise floor?**

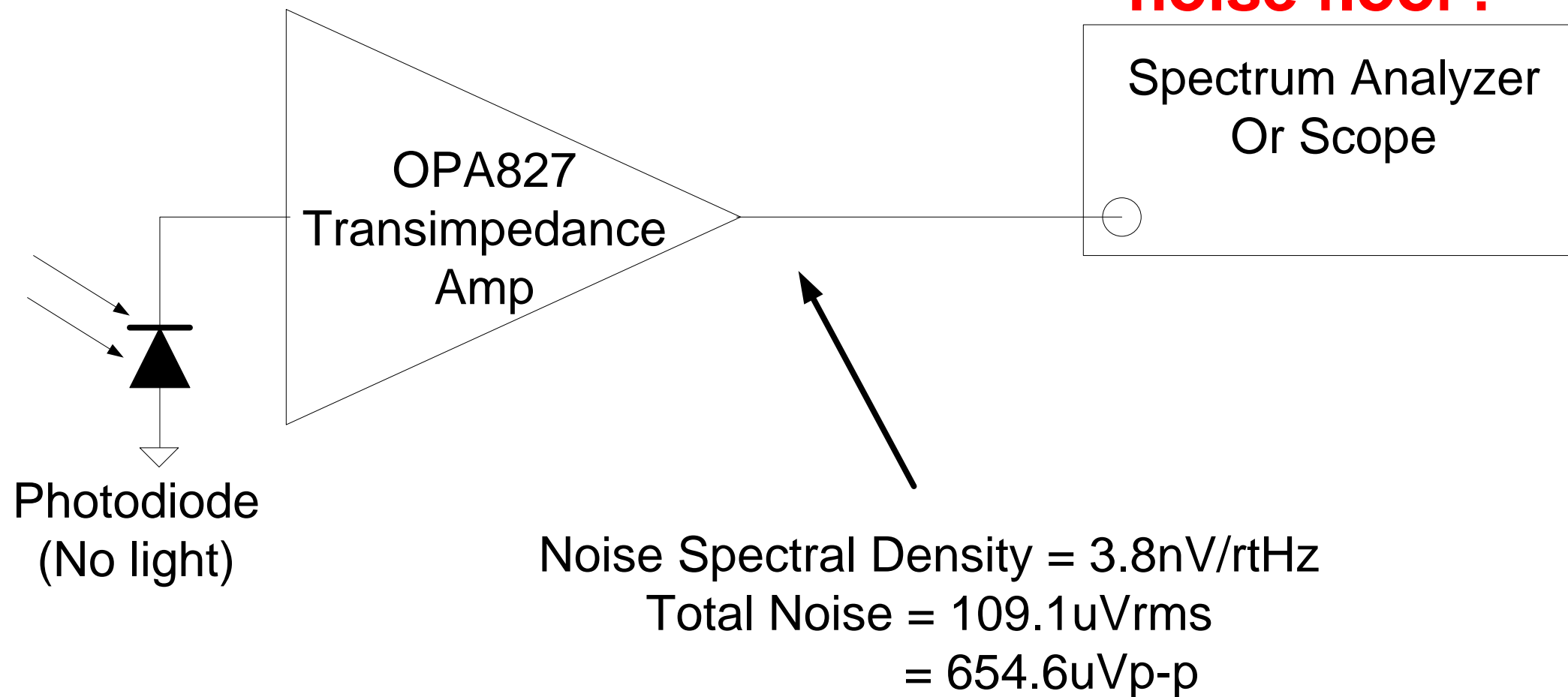

Tektronix DPO 4034 Oscilloscope



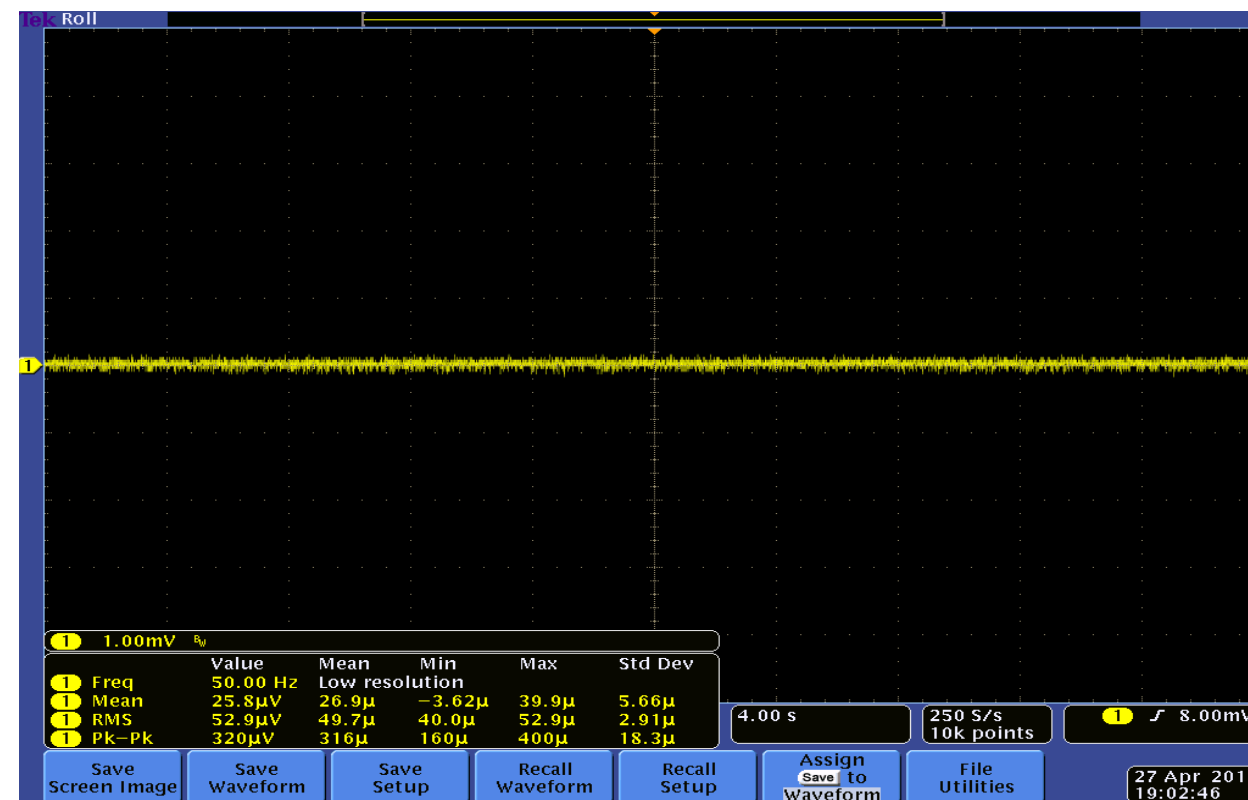- 1) Set DC couple, 20MHz bandwidth limit
- 2) Short input channel to measure noise floor




STDEV: 48uV (same as RMS)

P-P: 6.6*STDEV=319uV

40s P-P: 320uV

Agilent 4395A Spectrum Analyzer

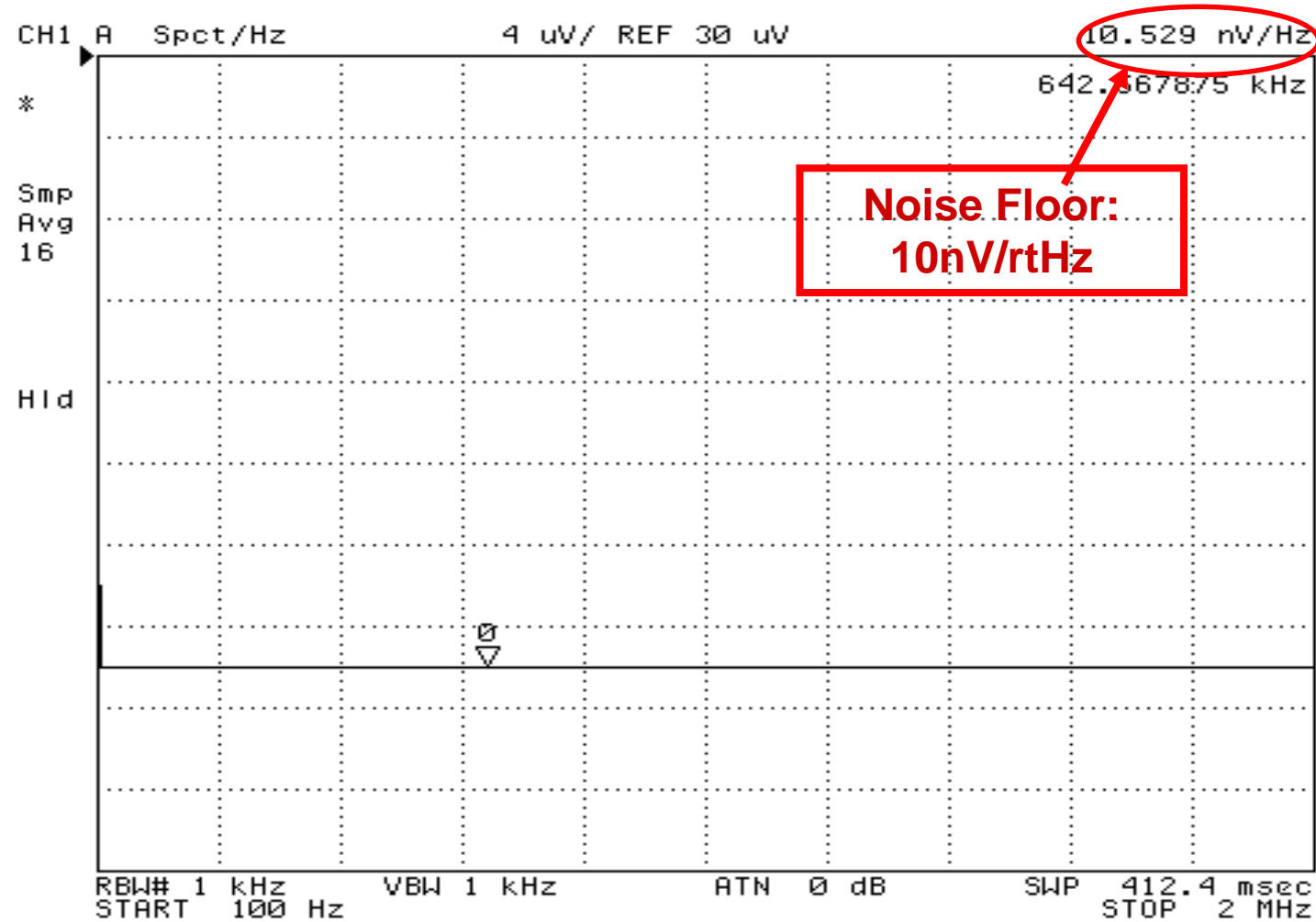
1. Frequency Range: 10Hz~500MHz
2. Noise floor: 10nV/rtHz
3. Input Impedance: 50Ω




The Noise Floors are Not Good Enough

Noise Floors:

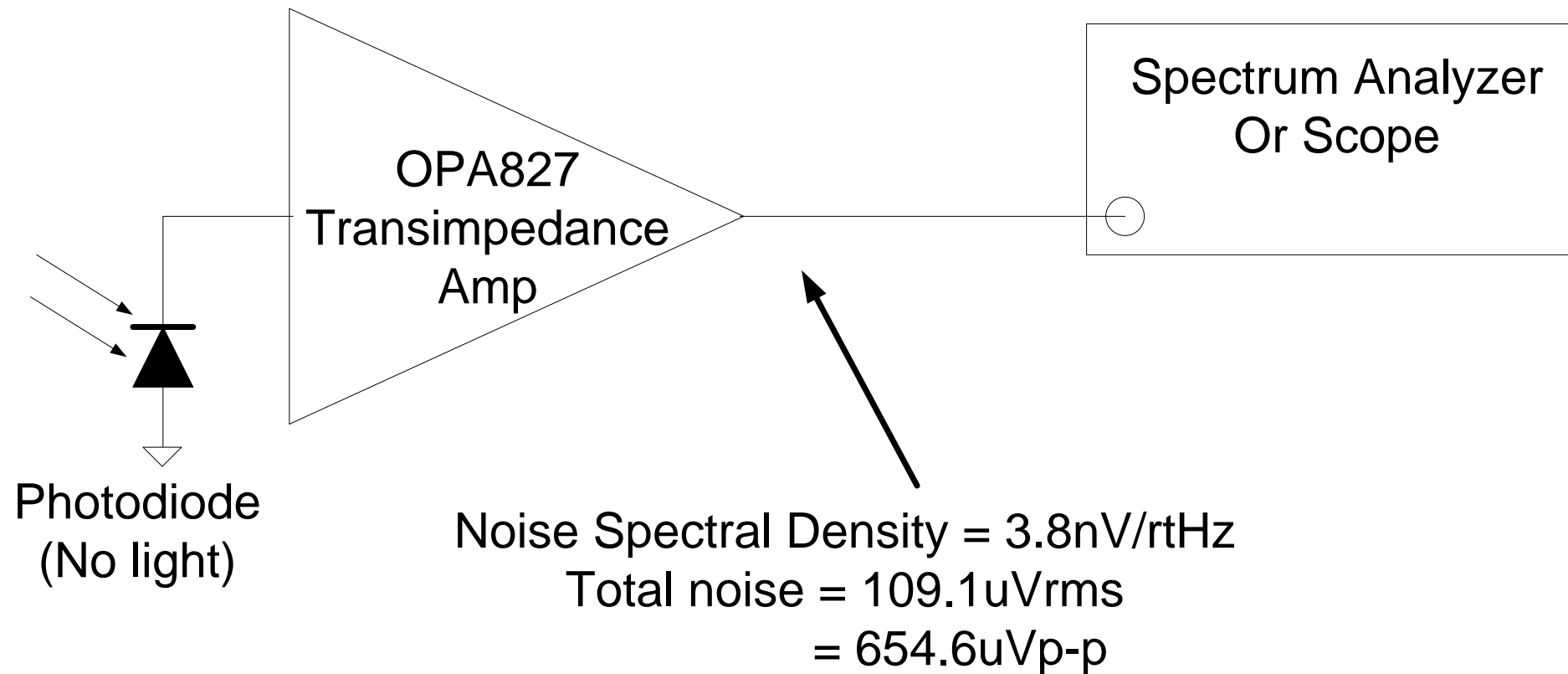Scope (1mV range) = 48uV rms = 320uVpp
4395A Spect. Analyzer = 10nV/rtHz






Solution: Use A Post Amp, Which one?

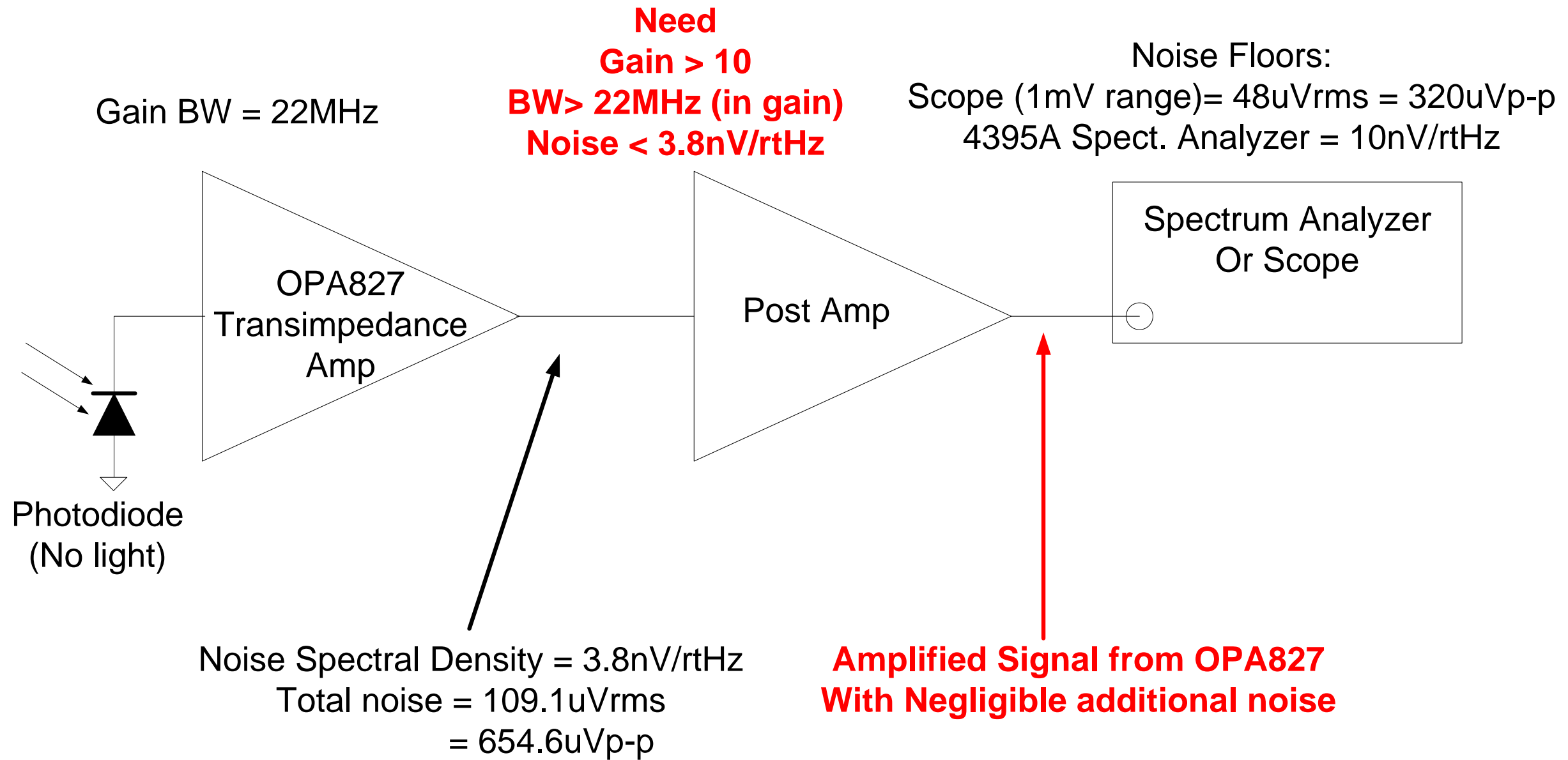


Use OPA847 as post amplifier

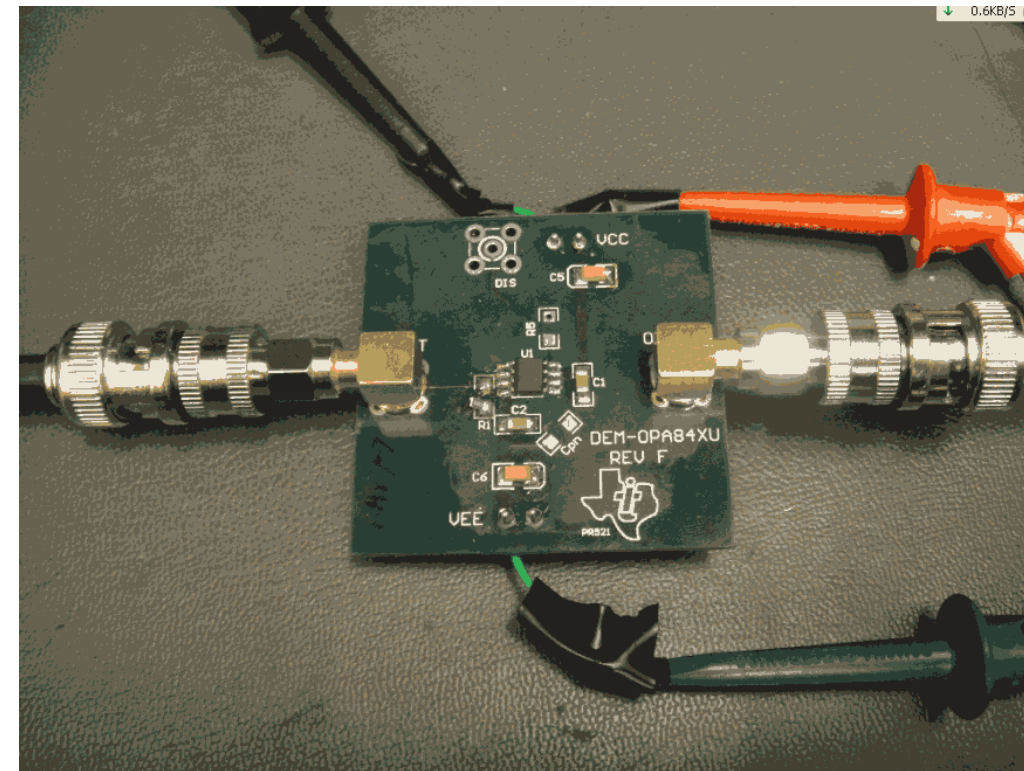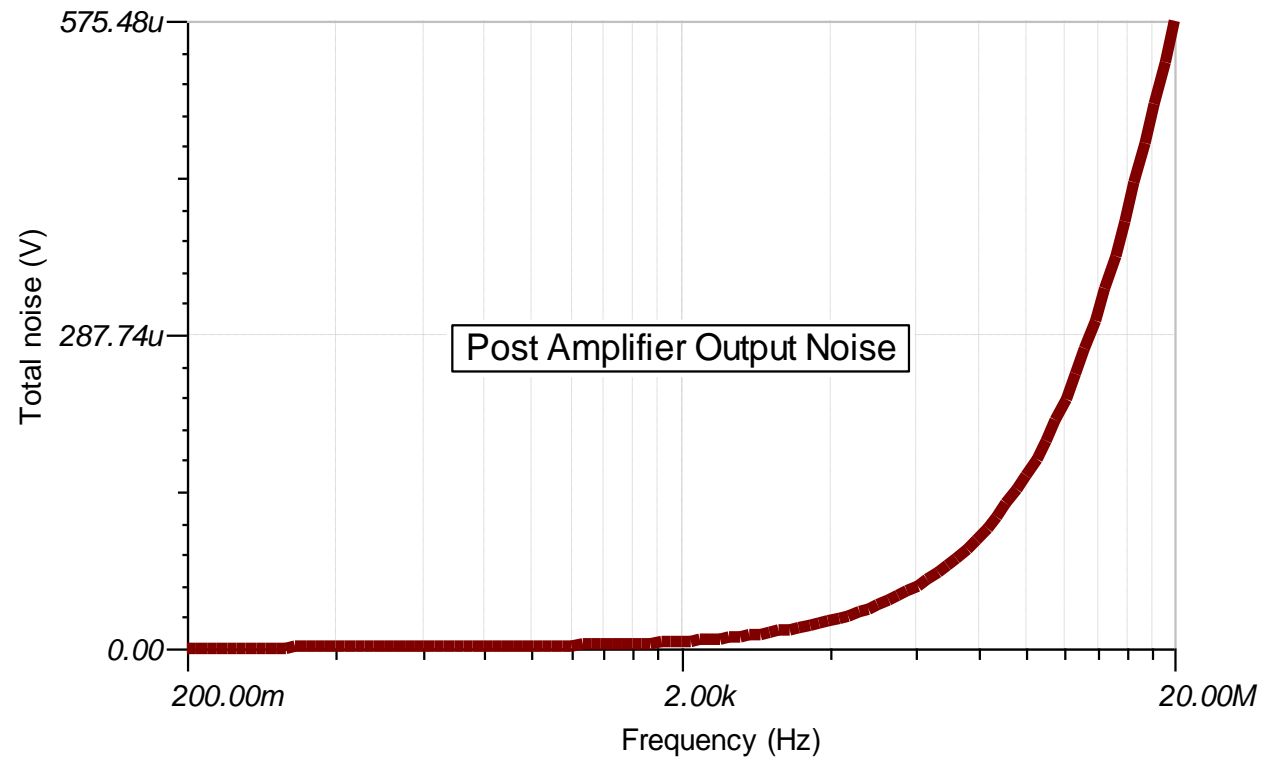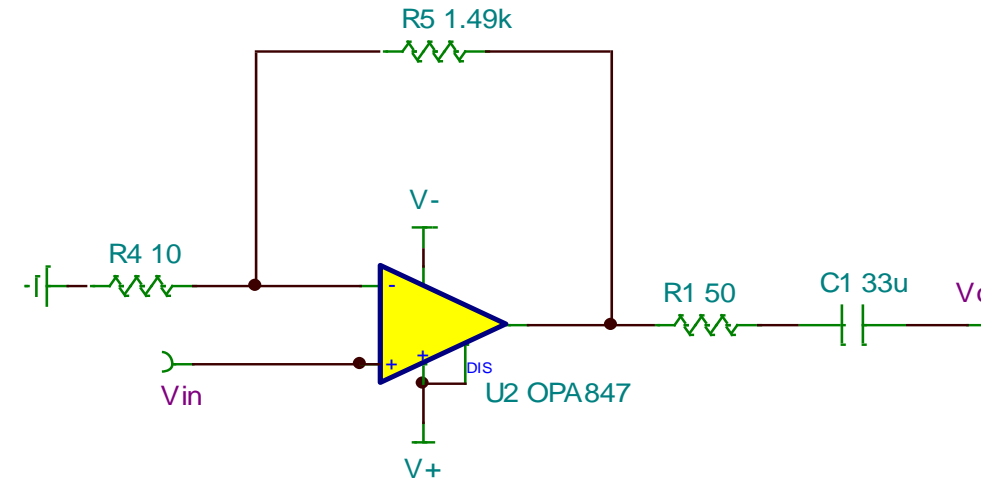
- At the gain of 150, the bandwidth is 26MHz
- $0.85\text{nV}/\sqrt{\text{Hz}}$ Input Voltage Noise
- $2.5\text{pA}/\sqrt{\text{Hz}}$ Input Current Noise
- $\pm 100\mu\text{V}$ Input Offset Voltage (Typical))



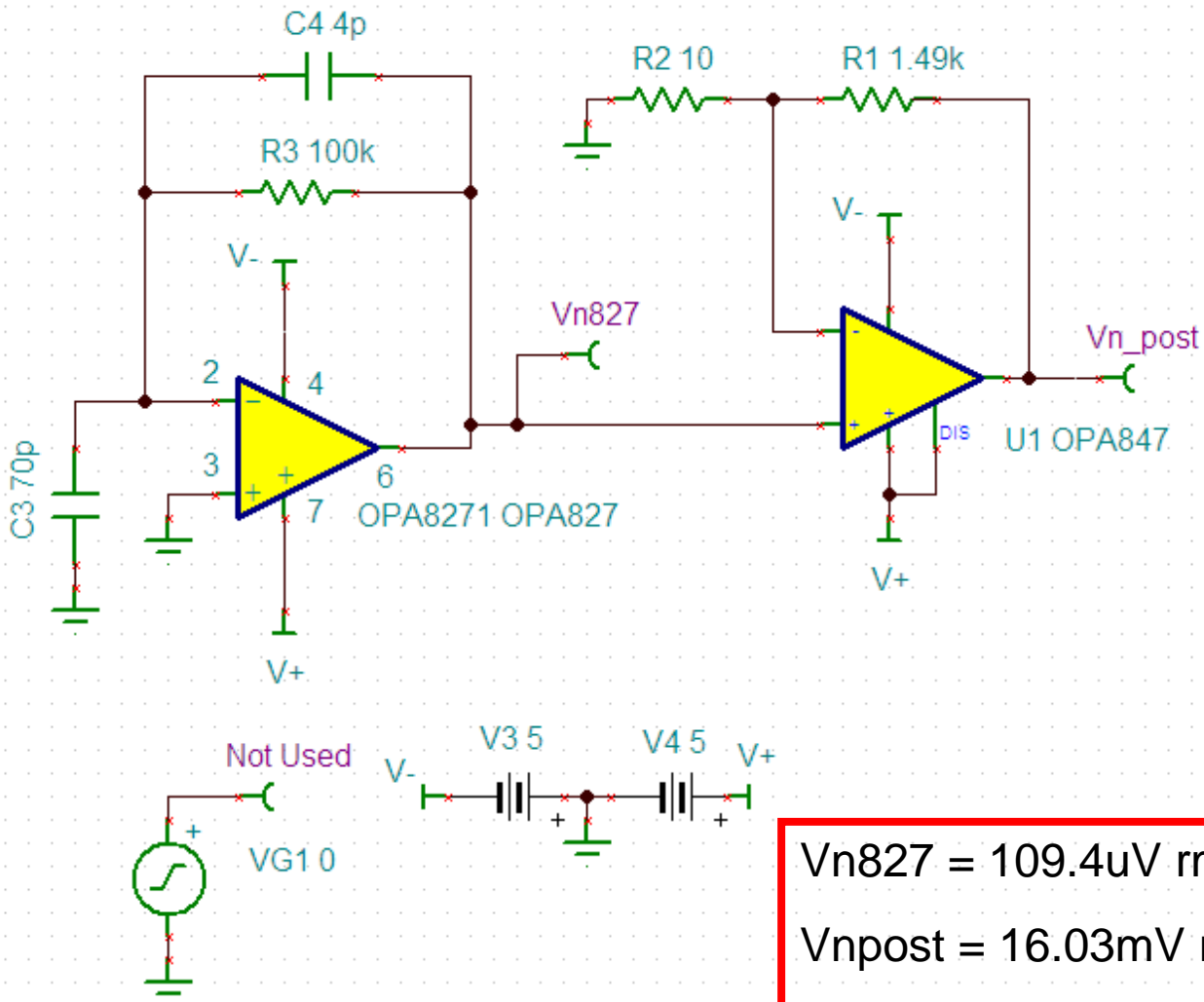
Post Amplifier adds relatively small error!



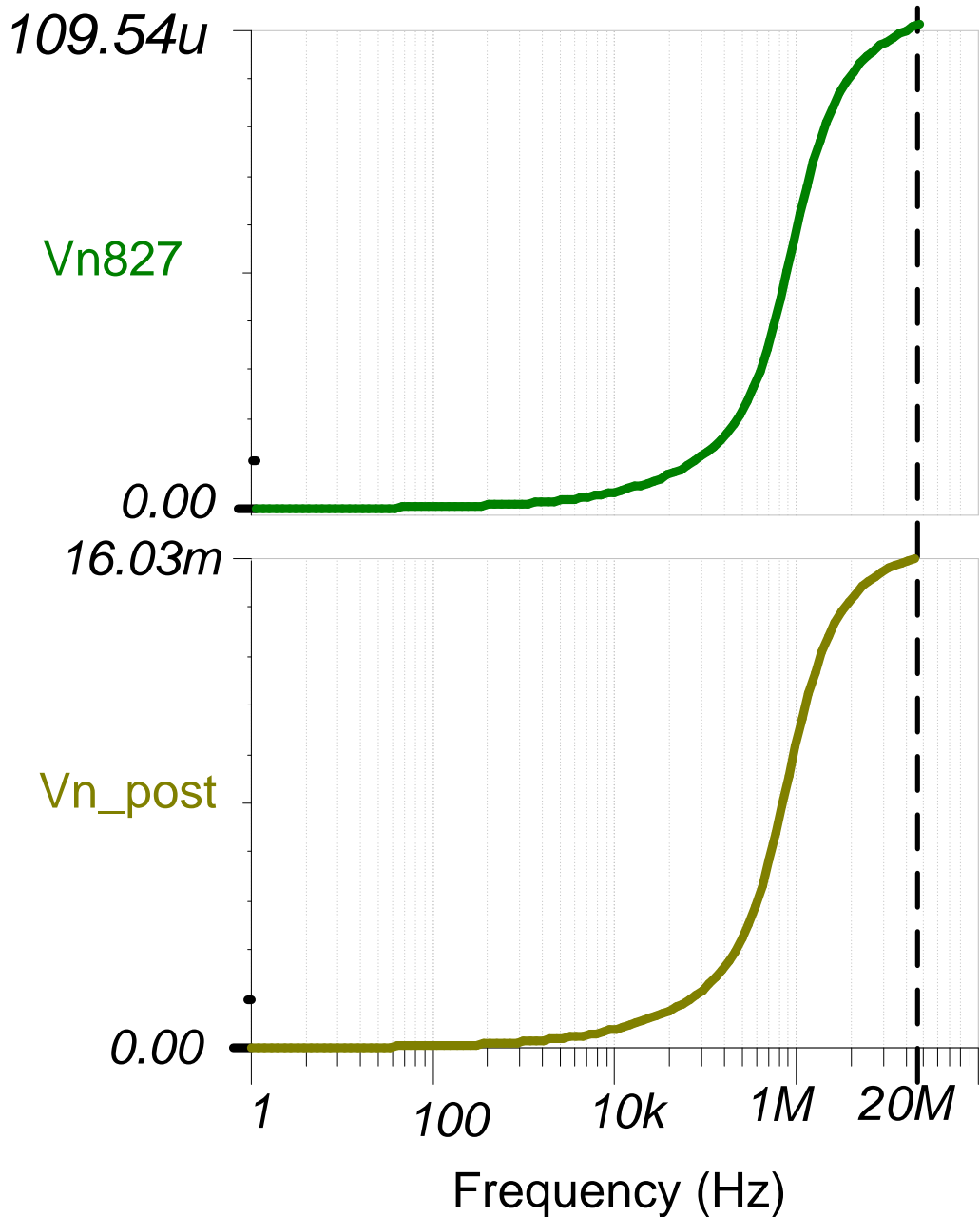
$Vn_{827} = 109.4\mu V \text{ rms}$
 $Vn_{post} = 16.03mV \text{ rms}$
 $Vn_{post}/Gain = 16.03mV/150 = 106.8\mu V \text{ rms}$



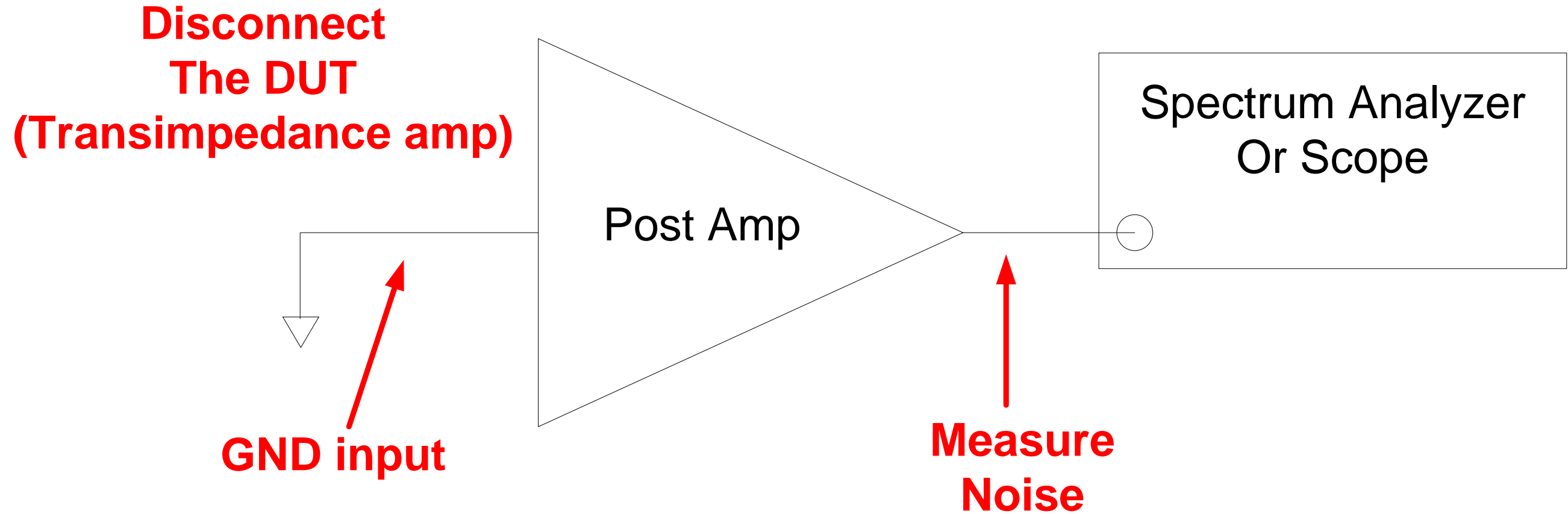Test the Noise Floor of post amp + instrument




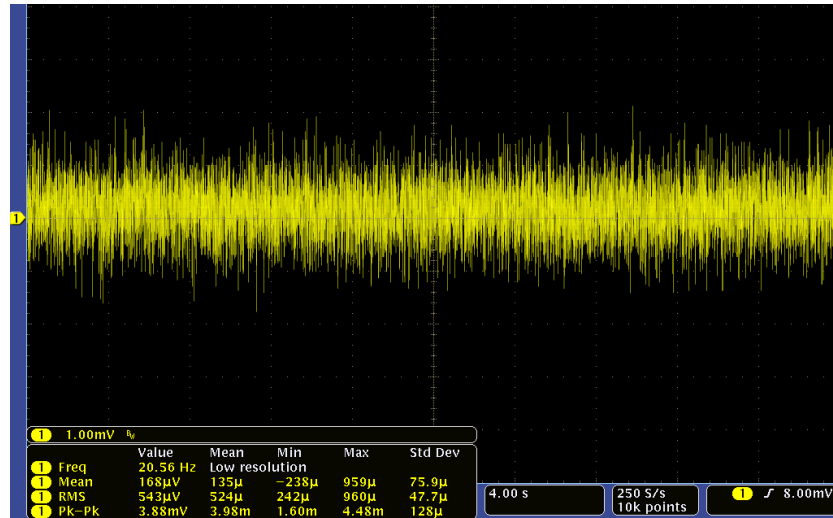Test The Noise Floor – Post Amp Noise Scope




Simulated (rms)	Measured (rms)
575uV	518uV



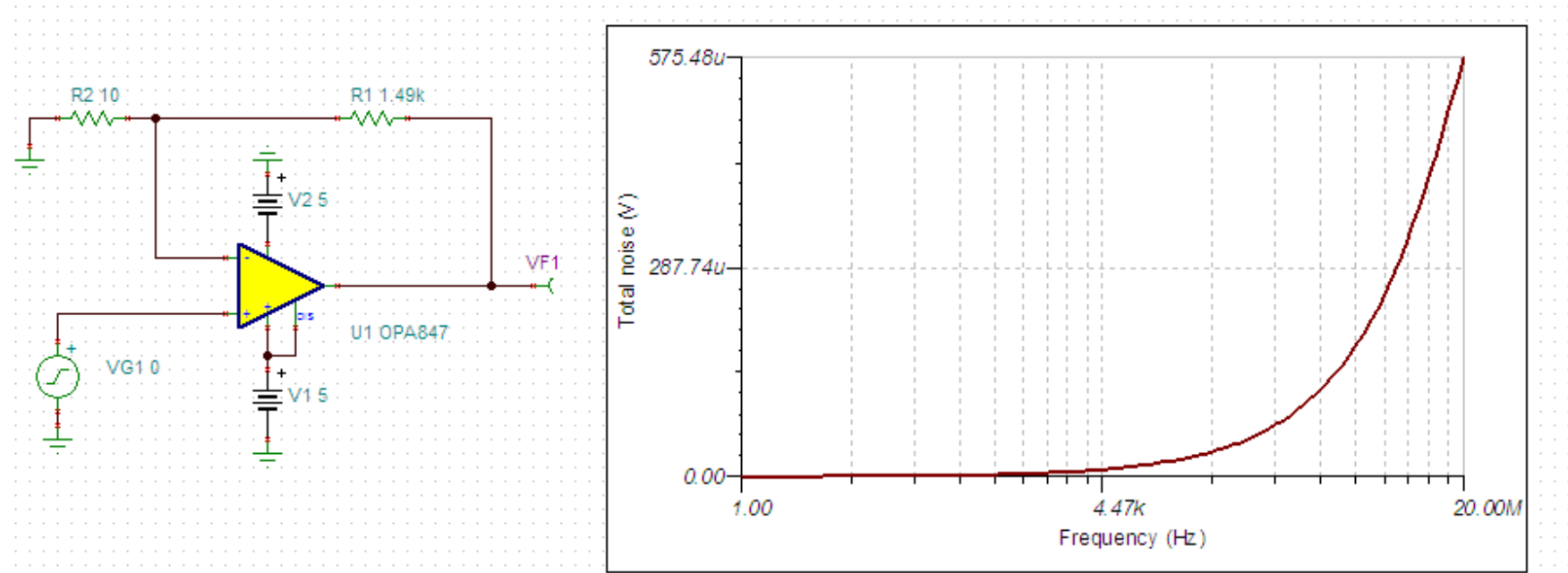
STDEV: 518uV
P-P: 6.6*STDEV=3.4mV
40s P-P: 3.88mV



Hardware Connections

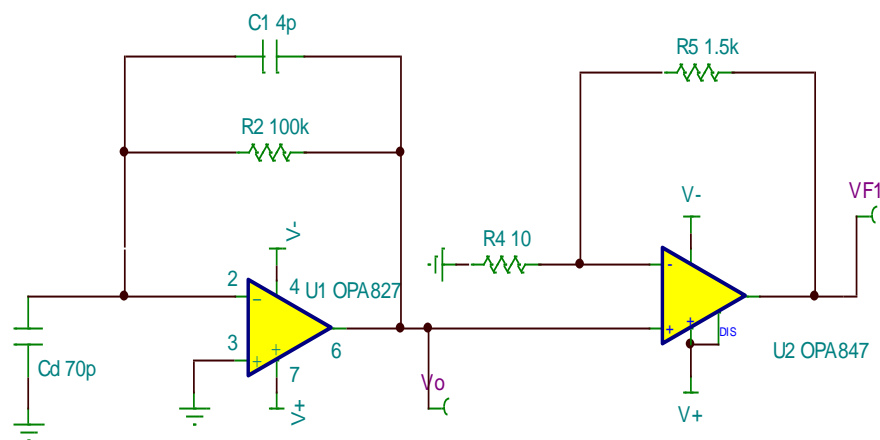

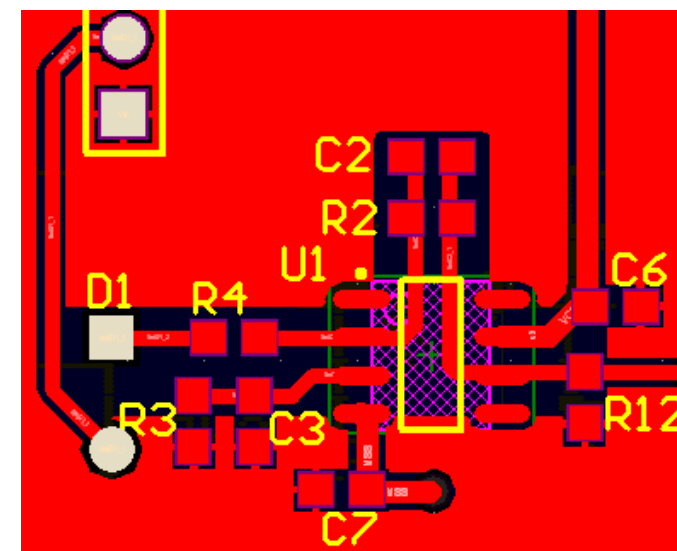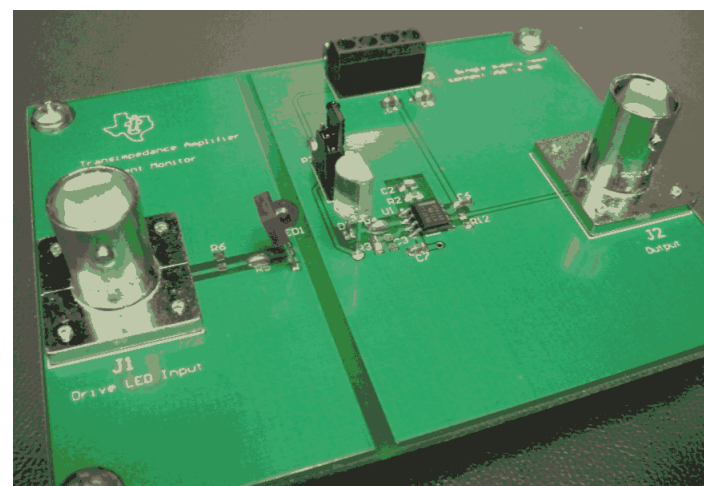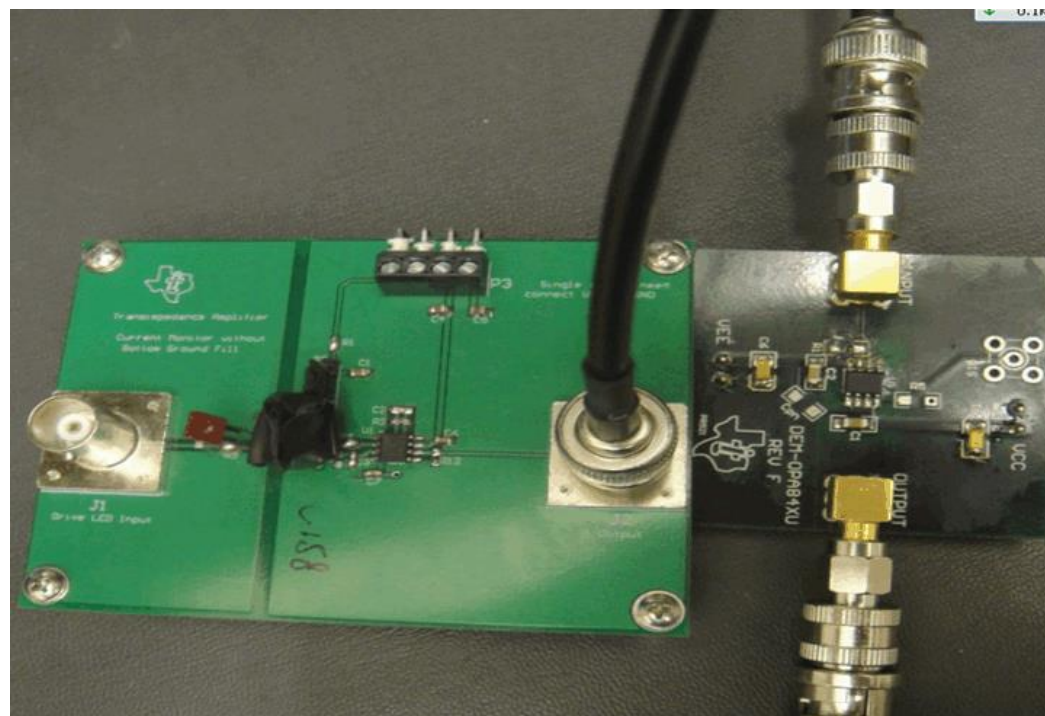1. PDB-C158-ND photodiode
2. 70pF junction capacitance at $V_r=0$ V
3. 100dB I-V gain
4. 4pF compensation capacitor
5. ± 5 V power supply.



Shield the Circuit





Power Supply
Vcc, Vss, GND


Input & Output BNC
connectors

Shield

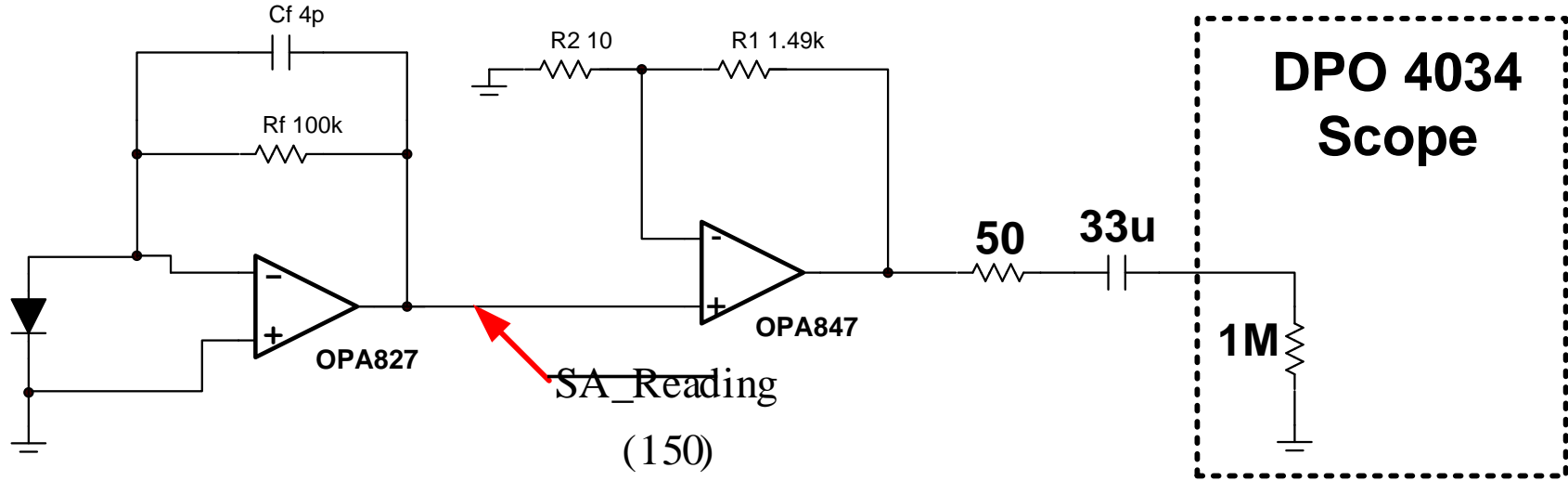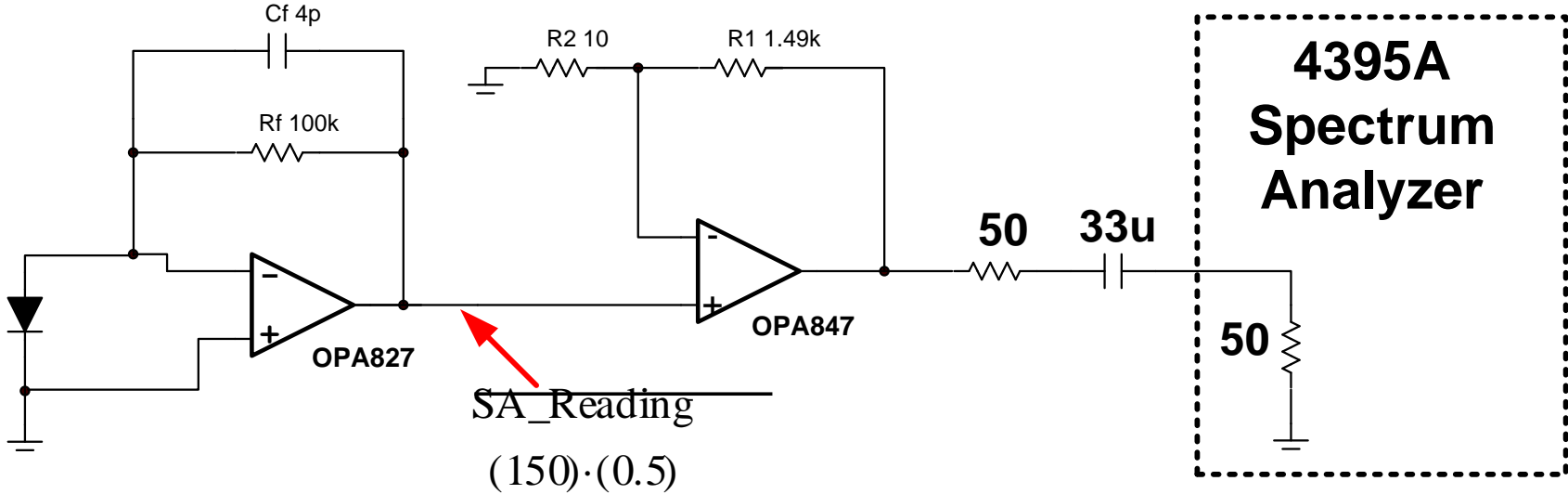Divide by post amp gain for OPA827 Output Noise



Measured vs Simulated (DPO 4034 Scope)

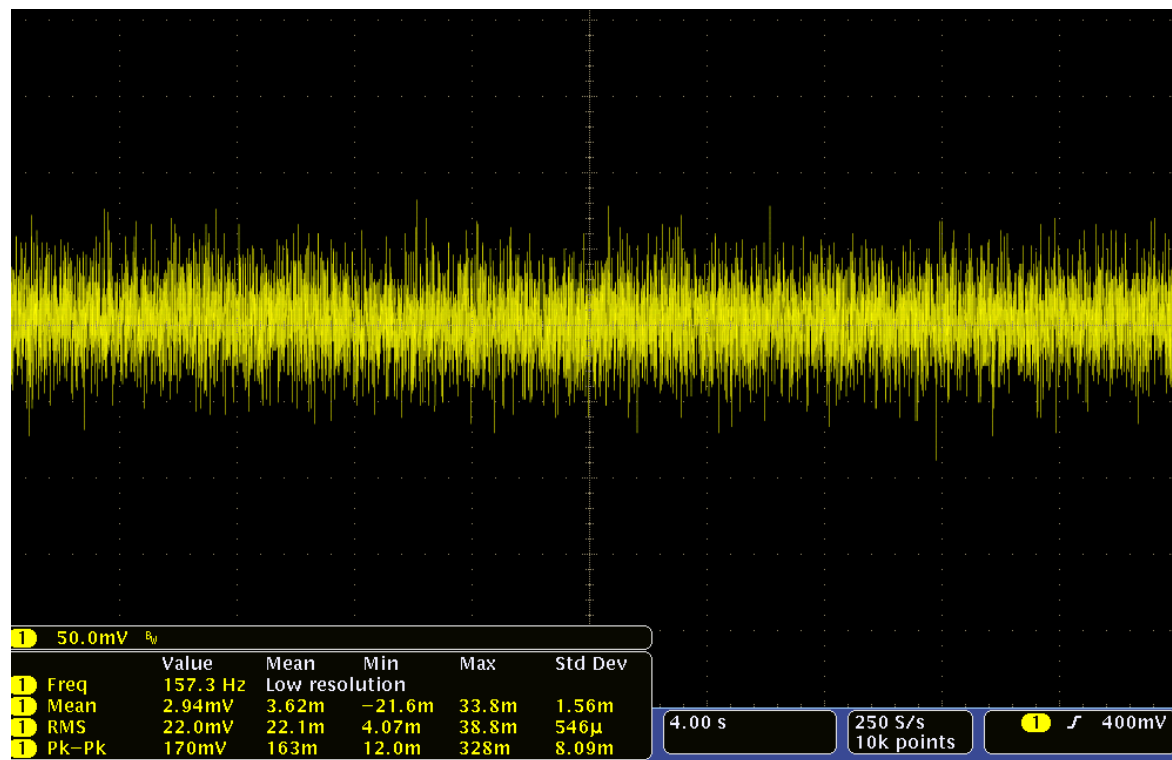

OPA847 Measured at Scope:

STDEV: 21.7mV

P-P: 6.6*STDEV=143mV

40s P-P: 170mV


At OPA827 (DUT) Output:

Divide by gain



$V_{n827} = 21.7\text{mV}/150 = 144.6\mu\text{V}$

Calculated (rms)	Simulated (rms)	Measured (rms)
116.7uV	109.1uV	144.6uV

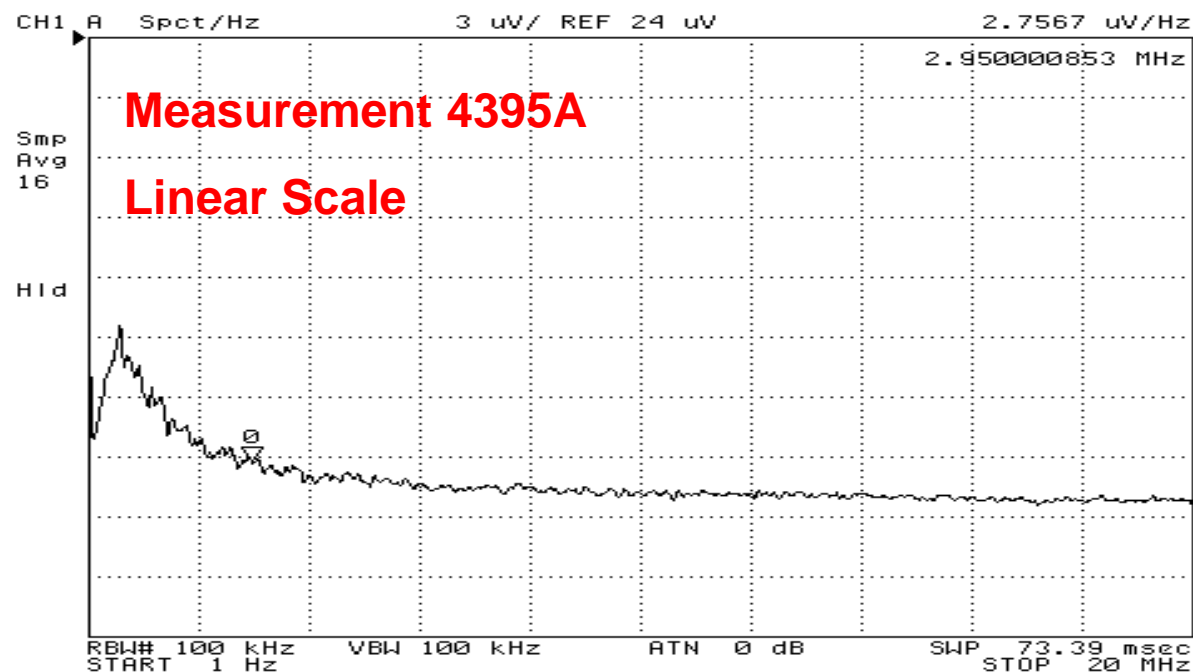
Measured Spectral Density Spectrum Analyzer



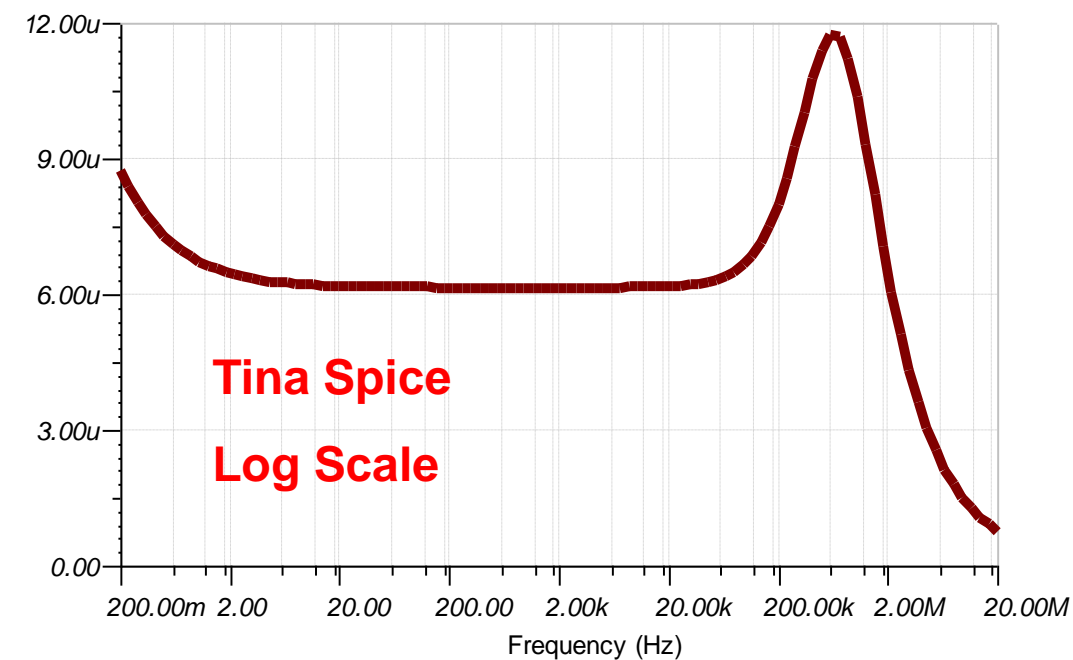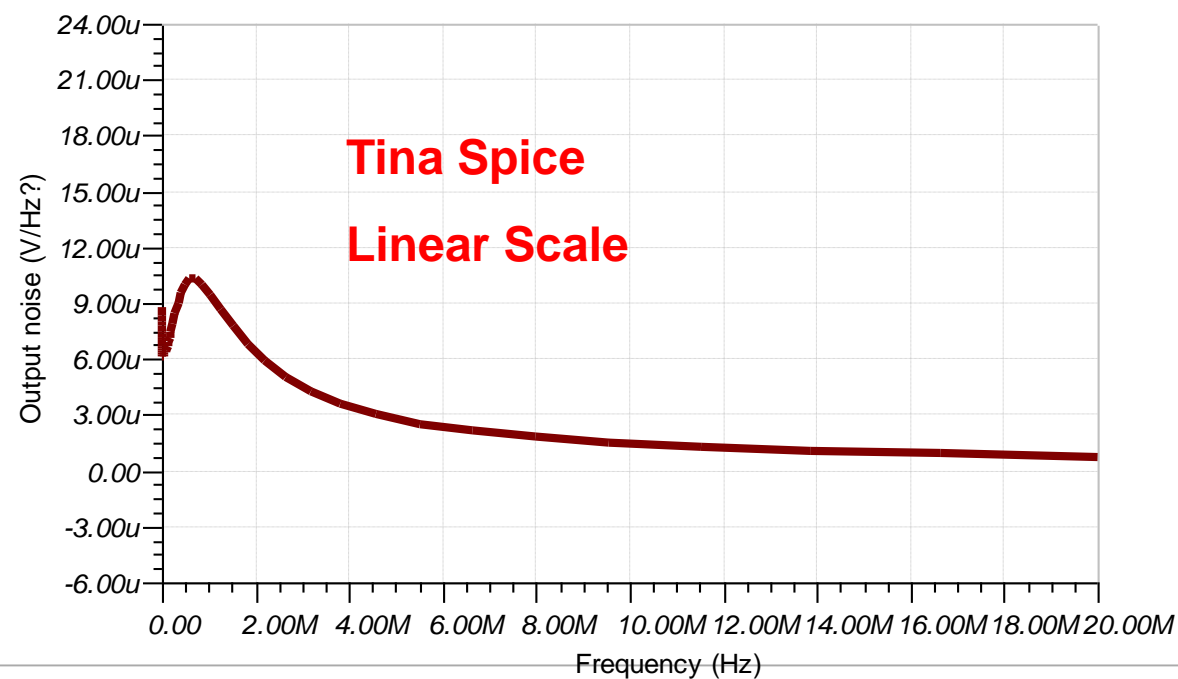1. Agilent 4395A Spectrum Analyzer test 1Hz~20MHz span, 3uV/div, REF=24uV.
2. The tested noise density curve shape is the same as simulation.



Measured vs Simulated

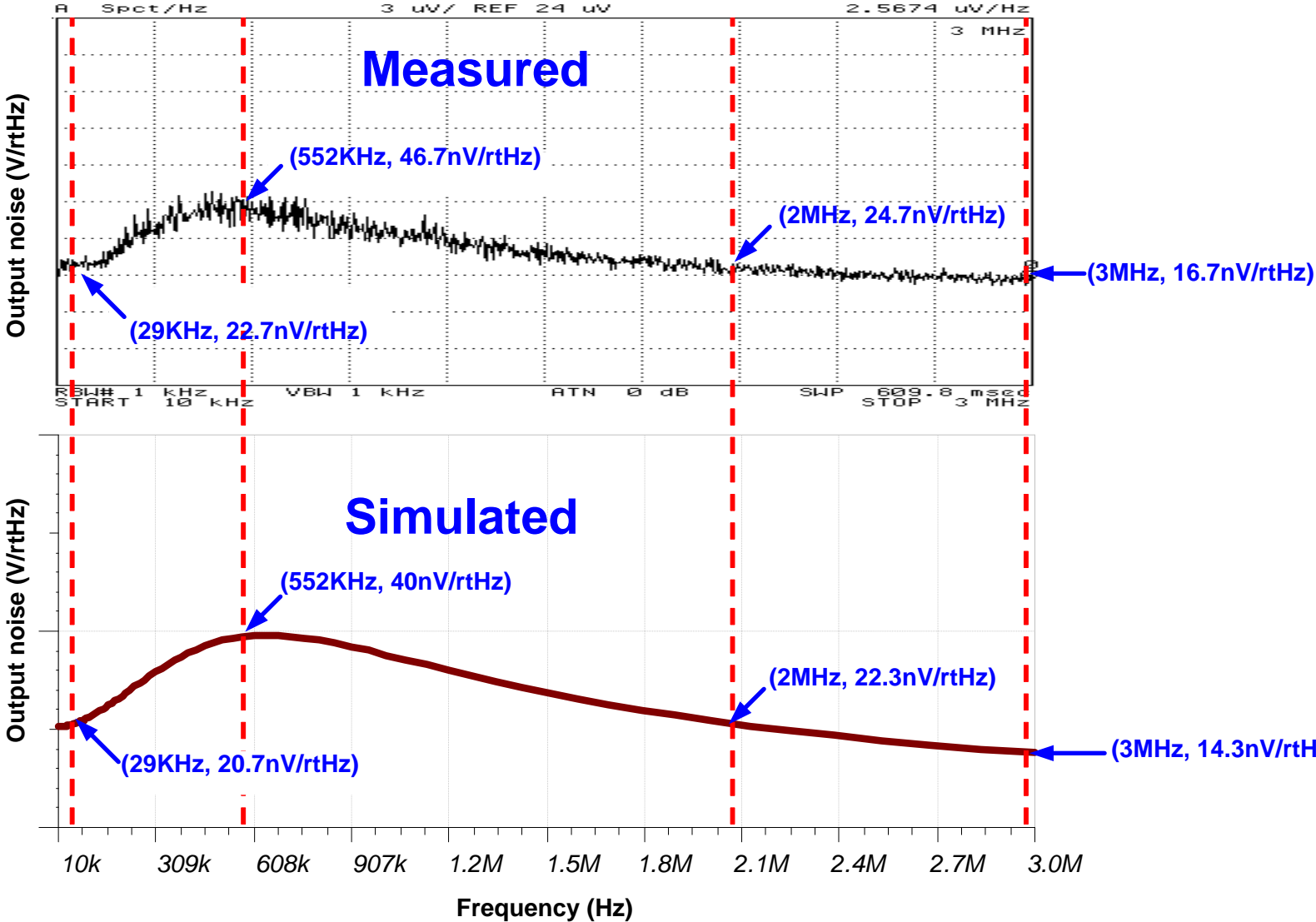

Thanks for your time

- Bryan Zhao (赵伟)
- Matt Hann
- Collin Wells, Peter Semig, Curtis Mayberry

References

- Jerald Graeme <Photodiode Amplifiers>
- Art Kay < Op-Amp Noise Calculation and Measurement >
- HAMAMATSU <Photodiode Technical Information>
- Tim Green <Operational amp stability>