

Instrumentation amplifiers are composed of multiple op amps. This figure shows the simplified INA851 configuration. Each amplifier inside the INA has it's own input and output swing limitations. These limitations combine into an overall common mode versus output swing range limitation for the instrumentation amplifier.

The output swing limitation of the first stage internal amplifiers is a function of the input front-end gain, input common-mode voltage, input stage supplies (VS+/VS-). The output range limitations of the second stage is a function of the VOCM voltage, the gain of the output stage, the power supplies (VS+/VS-), and the clamp voltages (VCLAMP+ and VCLAMP-). This relationship can be complex and generally cannot be determined with a simple equation or data sheet parameter. In some cases a data sheet diagram graphing common mode versus output swing can be used to understand this limitation.

INA851	Input and Output Range Design Calculator
	INA851 Input and Output Range Design Calculator: (excel file) <u>ti.com/tool/download/INA851-INPUT-OUTPUT-RANGE-DESIGN-CALC</u>
Home / Design resources	T-OUTPUT-RANGE-DESIGN-CALC
Select a version Filter by version or date REV-1 (21 Oct 2022)	Latest version Version: REV-1 Release date: 21 Oct 2022
	Downloads Supported products & hardware INA851-Input-and-Output-Range-Calc-revA.xtex - 490 K MD5 checksum 08fe3a07d827041745c278e57684cfce Image: Calc-revA.xtex - 490 K
	Requires export approval (1 minute) Texas Instruments


Download INA851 Input and Output Range Design Calculator: (excel file)

INA851 Input and Output Range Design Calculator

The excel tool consists of two sheets:

First sheet: "INA851_Vin_Vout_tool"


- User fills the highlighted cells in blue with required voltages.
- <u>Required:</u> VS+, VS-, Front-End Gain, Back-End Gain, Input differential/input common-mode Voltage, VOCM, VCLAMP+ and VCLAMP- (if Clamps Enabled).
- Excel provides resulting VOUT+, VOUT-, and VOUT-differential voltages, and the RG resistor for a given front-end gain.
- The tool highlights in red any voltage out of range, and displays warnings in red if the device is outside of linear range.

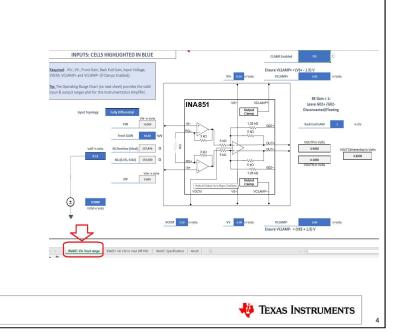

The excel tool consists of two sheets, select the sheet at the bottom:


First sheet: "INA851_Vin_Vout_tool"

- User fills the highlighted cells in blue with required voltages.
- <u>Required:</u> VS+, VS-, Front-End Gain, Back-End Gain, Input differential/input common-mode Voltage, VOCM, VCLAMP+ and VCLAMP- (if Clamps Enabled).
- Excel provides resulting VOUT+, VOUT-, and VOUT-differential voltages, and the RG resistor for a given front-end gain.
- The tool highlights in red any voltage out of range, and displays warnings in red if the device is outside of linear range.

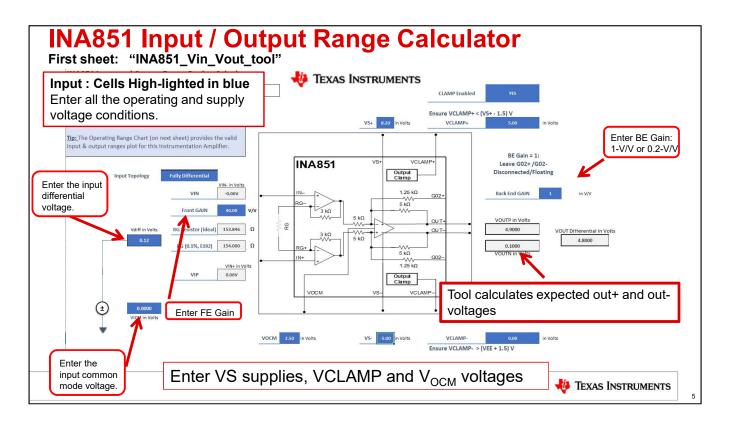


First sheet: "INA851_Vin_Vout_tool"

- User fills the highlighted cells in blue with required voltages.
- <u>Required:</u> VS+, VS-, Front-End Gain, Back-End Gain, Input differential/input common-mode Voltage, VOCM, VCLAMP+ and VCLAMP- (if Clamps Enabled).
- Excel provides resulting VOUT+, VOUT-, and VOUT-differential voltages, and the RG resistor for a given front-end gain.
- The tool highlights in red any voltage out of range, and displays warnings in red if the device is outside of linear range

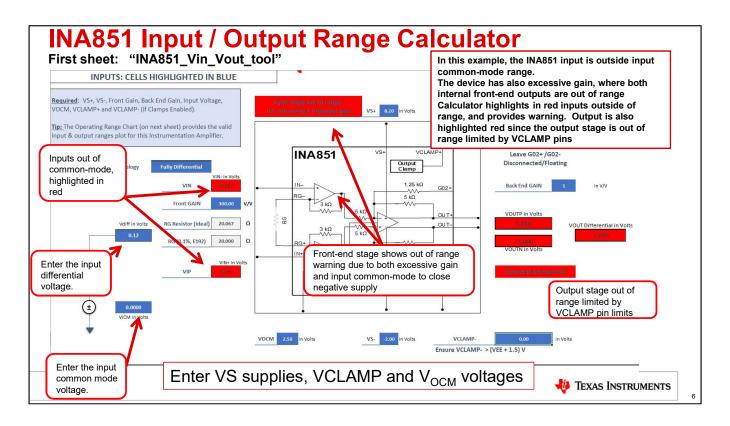

First sheet: "INA851_Vin_Vout_tool"

- User fills the highlighted cells in blue with required voltages.
- <u>Required:</u> VS+, VS-, Front-End Gain, Back-End Gain, Input differential/input common-mode Voltage, VOCM, VCLAMP+ and VCLAMP- (if Clamps Enabled).
- Excel provides resulting VOUT+, VOUT-, and VOUT-differential voltages, and the RG resistor for a given front-end gain.
- The tool highlights in red any voltage out of range, and displays warnings in red if the device is outside of linear range

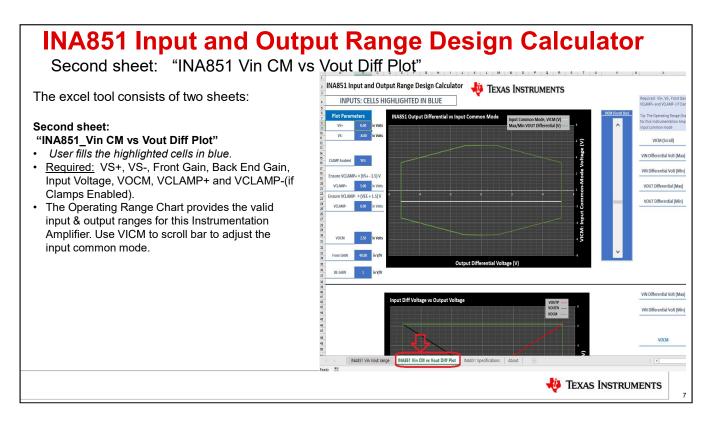


The excel tool consists of two sheets, select the sheet at the bottom:

Second sheet:

"INA851_VinCM_vs_VoutDiff_Plot"

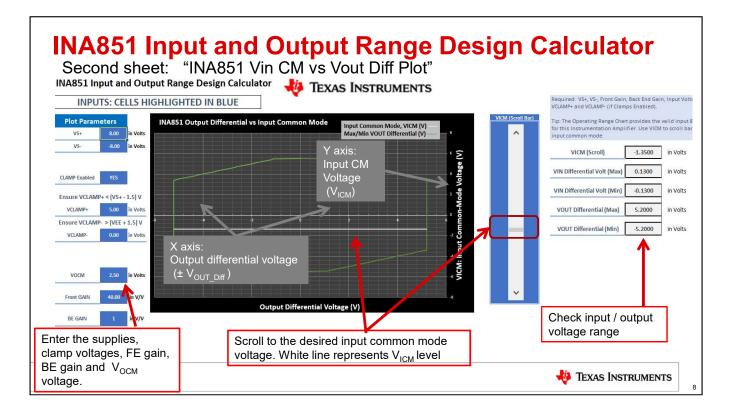- User fills the highlighted cells in blue.
- <u>Required:</u> VS+, VS-, Front Gain, Back End Gain, Input Voltage, VOCM, VCLAMP+ and VCLAMP- (if Clamps Enabled).
- The Operating Range Chart provides the valid input & output ranges for this Instrumentation Amplifier. Use VICM to scroll bar to adjust the input common mode.



"INA851_VinCM_vs_VoutDiff_Plot": User fills the highlighted cells in blue.

<u>Required:</u> VS+, VS-, Front Gain, Back End Gain, Input Voltage, VOCM, VCLAMP+ and VCLAMP- (if Clamps Enabled).

The Operating Range Chart provides the valid input & output ranges for this Instrumentation Amplifier. Use VICM to scroll bar to adjust the input common mode.

Here we show a calculator that allow you to confirm that the instrumentation amplifier will have a linear output swing for your configuration. Enter the supplies, front-end gain, back-end gain, VOCM voltage and VCLAMPs (if clamps enabled). Enter/Scroll the common mode voltage using VICM scroll voltage. Notice that the graph has common mode voltage on the vertical axis and Vout differential on the horizontal axis. The selected common mode voltage shows up as a white horizontal line. The output swing limitation are the points where the white line intersects with the green plot. The excel also displays the maximum differential input and max differential output on the right side of the screen.

Important notice and disclaimer

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to <u>TI's Terms of Sale</u> or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

