

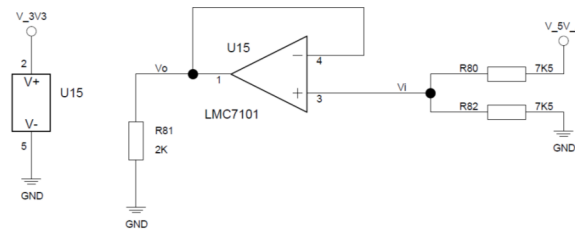


Schematic circuit :

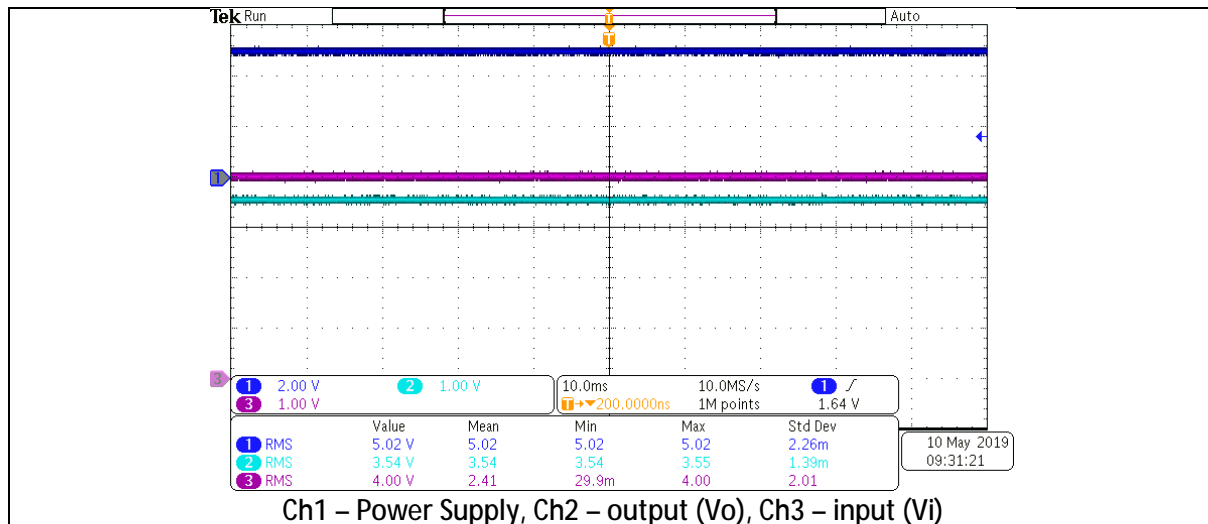


Power supply [V]	V input (Vi) [V]	Voutput (Vo) [V]
3.30	1.00	1.00
3.30	1.50	1.50
3.30	1.85	1.85
3.30	1.90	1.88
3.30	2.00	1.88
3.30	2.10	1.88
5.00	1.00	1.00
5.00	1.50	1.50
5.00	1.85	1.85
5.00	2.00	2.00
5.00	2.50	2.50
5.00	3.00	3.00
5.00	3.50	3.50
5.00	3.75	3.54
5.00	4.00	3.54

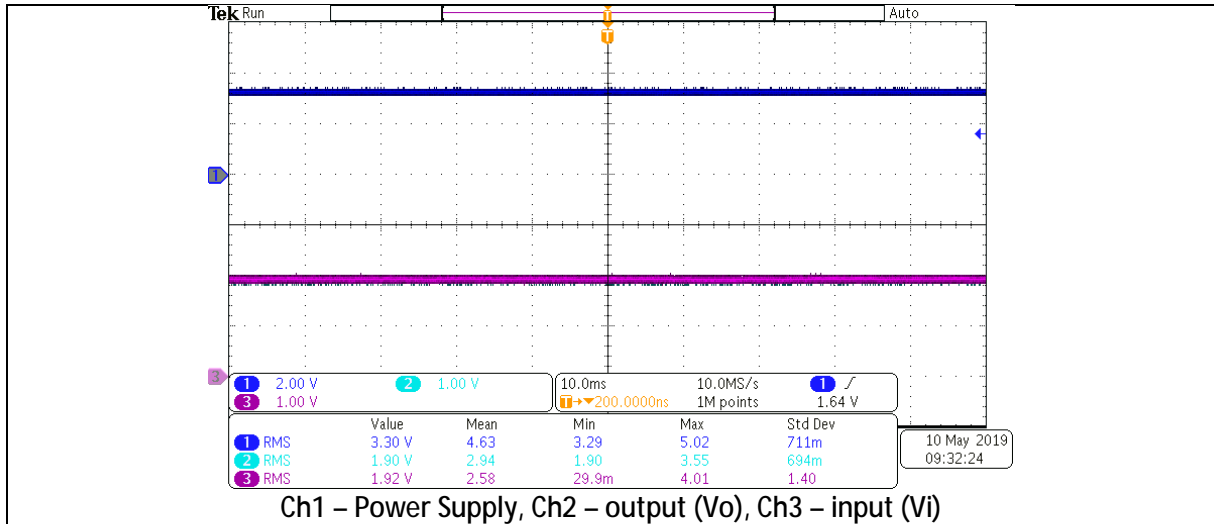



Ch1 – Power Supply, Ch2 – output (Vo), Ch3 – input (Vi)

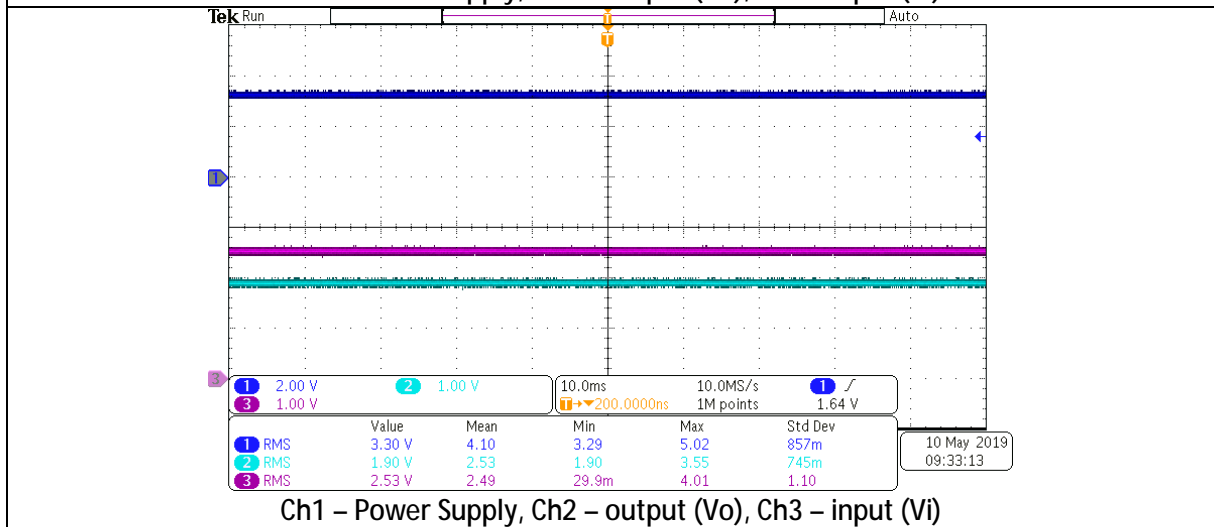

Ch1 – Power Supply, Ch2 – output (Vo), Ch3 – input (Vi)