

$$V_{in_min} = 0.25 \quad V_{O_MIN} = 1 \quad V_{REF} = 5$$

$$V_{in_max} = 0.8 \quad V_{O_MAX} = 4.95$$

Write the equations for the two cases in the system and solve for the gain and offset coefficients (m and b)

$$1 \quad 1 = m \cdot 0.25 + b$$

$$2 \quad 4.95 = m \cdot 0.8 + b$$

Solve Eqn 2 for b

$$b = 4.95 - 0.8 \cdot m$$

Plug b back into Eqn1 and solve for m

$$1 = m \cdot 0.25 + (4.95 - 0.8 \cdot m)$$

$$1 = 4.95 - 0.55 \cdot m$$

$$m = 7.181818181818182$$

Plug m back into Eqn 2 and solve for b

$$b = 4.95 - 0.8 \cdot (7.181818181818182)$$

$$b = -0.7954545454545456$$

Double Check the results for m and b

$$V_{o_min} := 7.181818181818182 \cdot 0.25 + -0.795 = 1$$

$$V_{o_max} := 7.181818181818182 \cdot 0.8 + -0.795 = 4.95$$

Solve for the circuit component values:

Assuming $R_1 \parallel R_2$ is $\ll R_G$, then

$$m = \frac{R_F + R_G}{R_G}$$

Plug in m and solve for R_F

$$7.181818181818182 = \frac{R_F + R_G}{R_G}$$

$$R_F = 6.181818181818182 \cdot R_G$$

R_1 and R_2 can be solved for once b, V_{REF} , and R_F/R_G are known

$$|b| = V_{REF} \cdot \left(\frac{R_F}{R_G} \right) \cdot \left(\frac{R_2}{R_1 + R_2} \right)$$

$$0.795 = 5 \cdot 6.181818181818182 \cdot \left(\frac{R_2}{R_1 + R_2} \right)$$

$$R_1 = 37.879359634076615209 \cdot R_2$$