
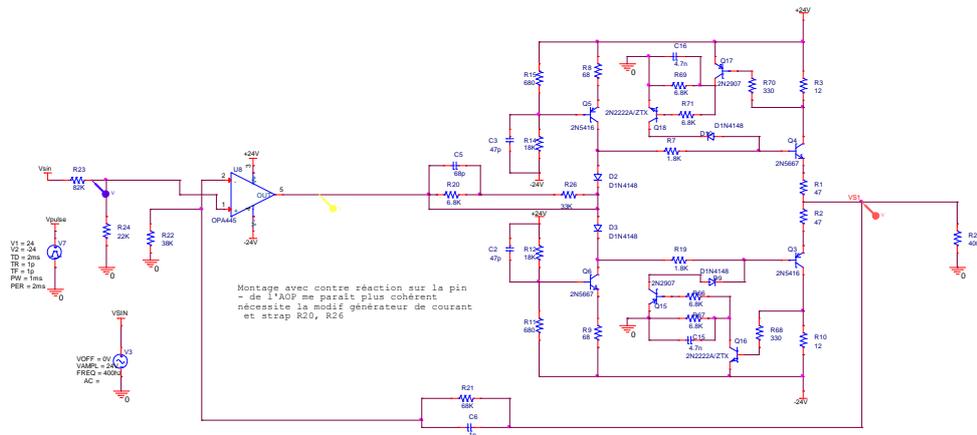


Amplifier schematic class AB with pin feedback -


Modification of current generators

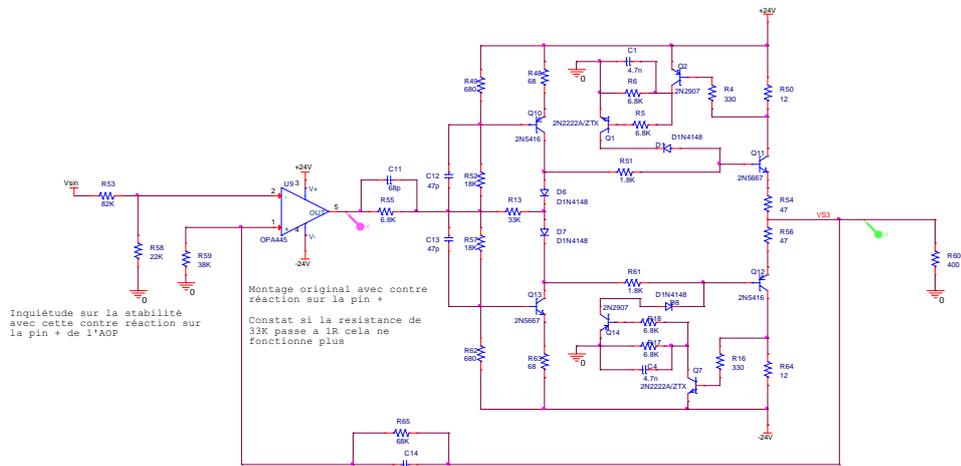

Amplifier schematic class AB with pin feedback +






Résultats

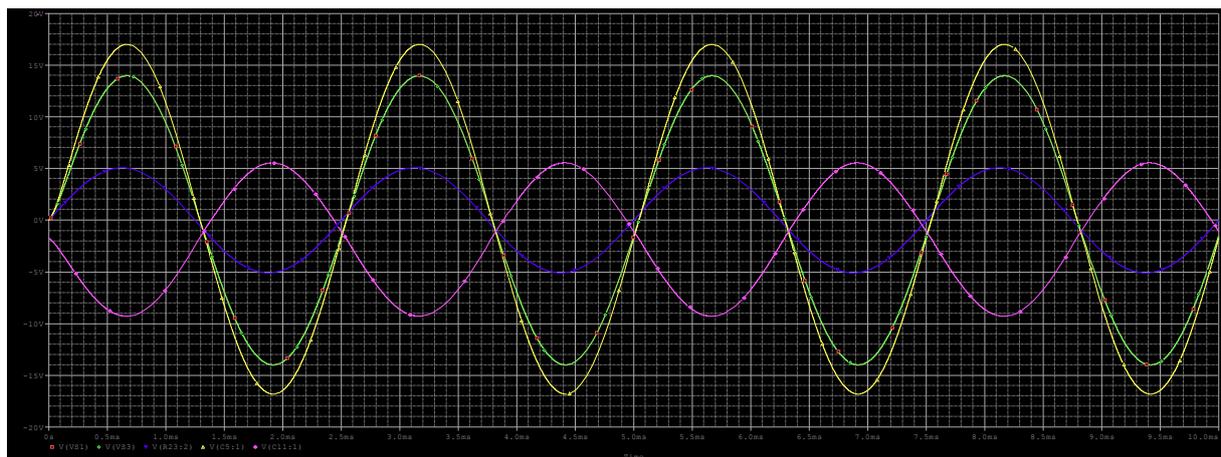



Identical result with both assemblies

Why does the amp with a feedback on the pin + it works?

Bode

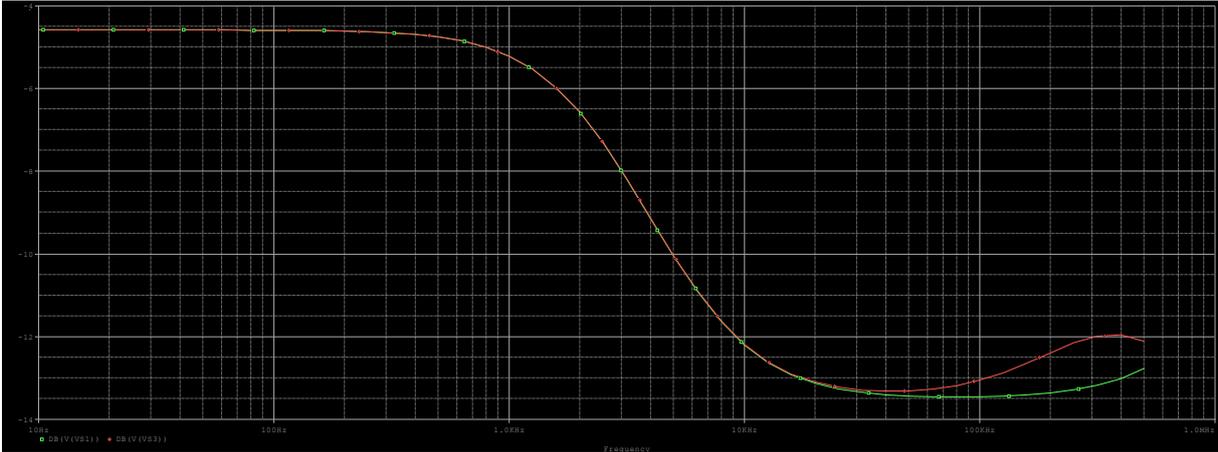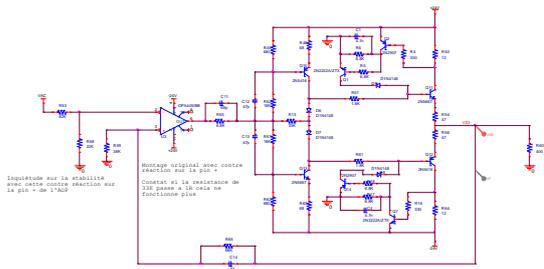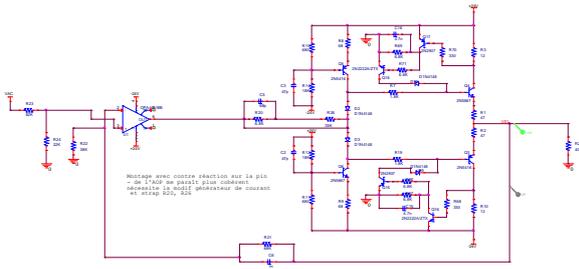

Square

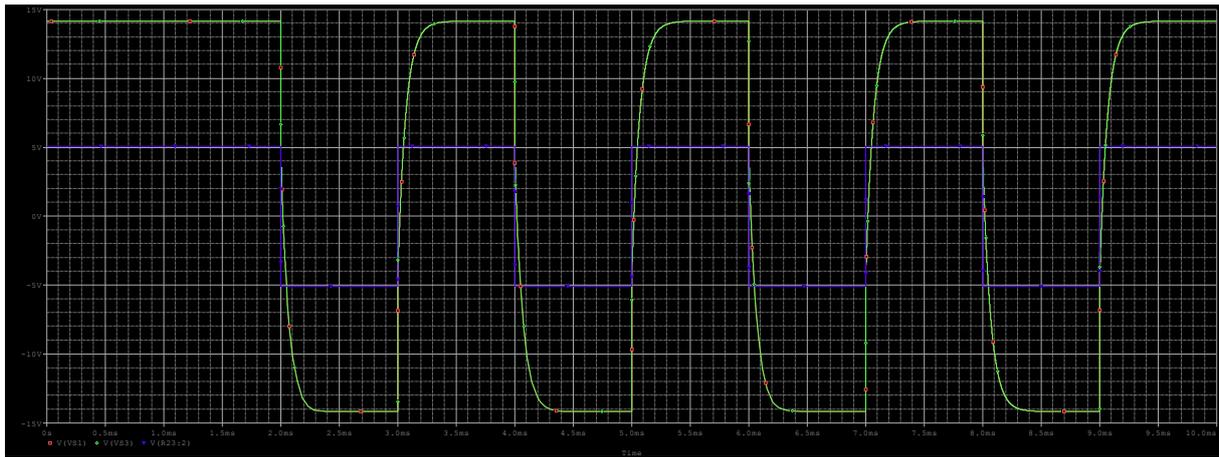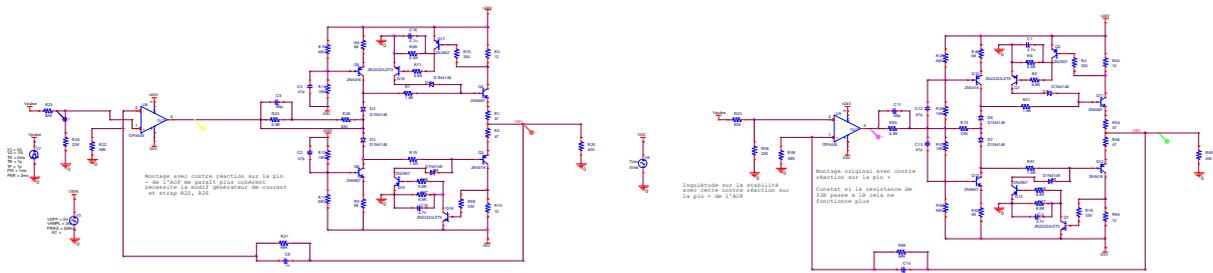

No différence