

Op Amp Aol vs Vout Swing Rules-of-Thumb

Tim Green, MGTS

9/29/2015

Precision Analog Linear Applications

Key TI Consultants:

Art Kay, MGTS

Marek Lis

Precision Analog Linear Applications

Slam Test vs Aol Test

Datasheet Specifications

OPA180 Specs for Discussion

- Output – Voltage Output Swing from Rail
- Aol – Open Loop Voltage Gain

Output Swing

ELECTRICAL CHARACTERISTICS: $V_S = \pm 2\text{ V}$ to $\pm 18\text{ V}$ ($V_S = +4\text{ V}$ to $+36\text{ V}$) (continued)

At $T_A = +25^\circ\text{C}$, $R_L = 10\text{ k}\Omega$ connected to $V_S/2$, and $V_{\text{COM}} = V_{\text{OUT}} = V_S/2$, unless otherwise noted.

PARAMETER	CONDITIONS	OPA2180, OPA4180			UNIT
		MIN	TYP	MAX	
OUTPUT					
Voltage output swing from rail	No load		8	18	mV
	$R_L = 10\text{ k}\Omega$		250	300	mV
	$T_A = -40^\circ\text{C}$ to $+105^\circ\text{C}$, $R_L = 10\text{ k}\Omega$		325	360	mV


This is “Slam Test” or “Saturation Test”.

This is a **NON-LINEAR** test.


The output is driven hard into output stage saturation.

Aol is **NOT** guaranteed closer than 500mV to either rail

OPEN-LOOP GAIN					
A _{OL}	Open-loop voltage gain	(V ₋) + 500 mV < V _O < (V ₊) - 500 mV, R _L = 10 kΩ	110	120	dB
		T _A = -40°C to +105°C, (V ₋) + 500 mV < V _O < (V ₊) - 500 mV, R _L = 10 kΩ	104	114	dB

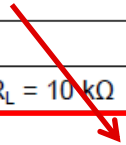

Line Chart

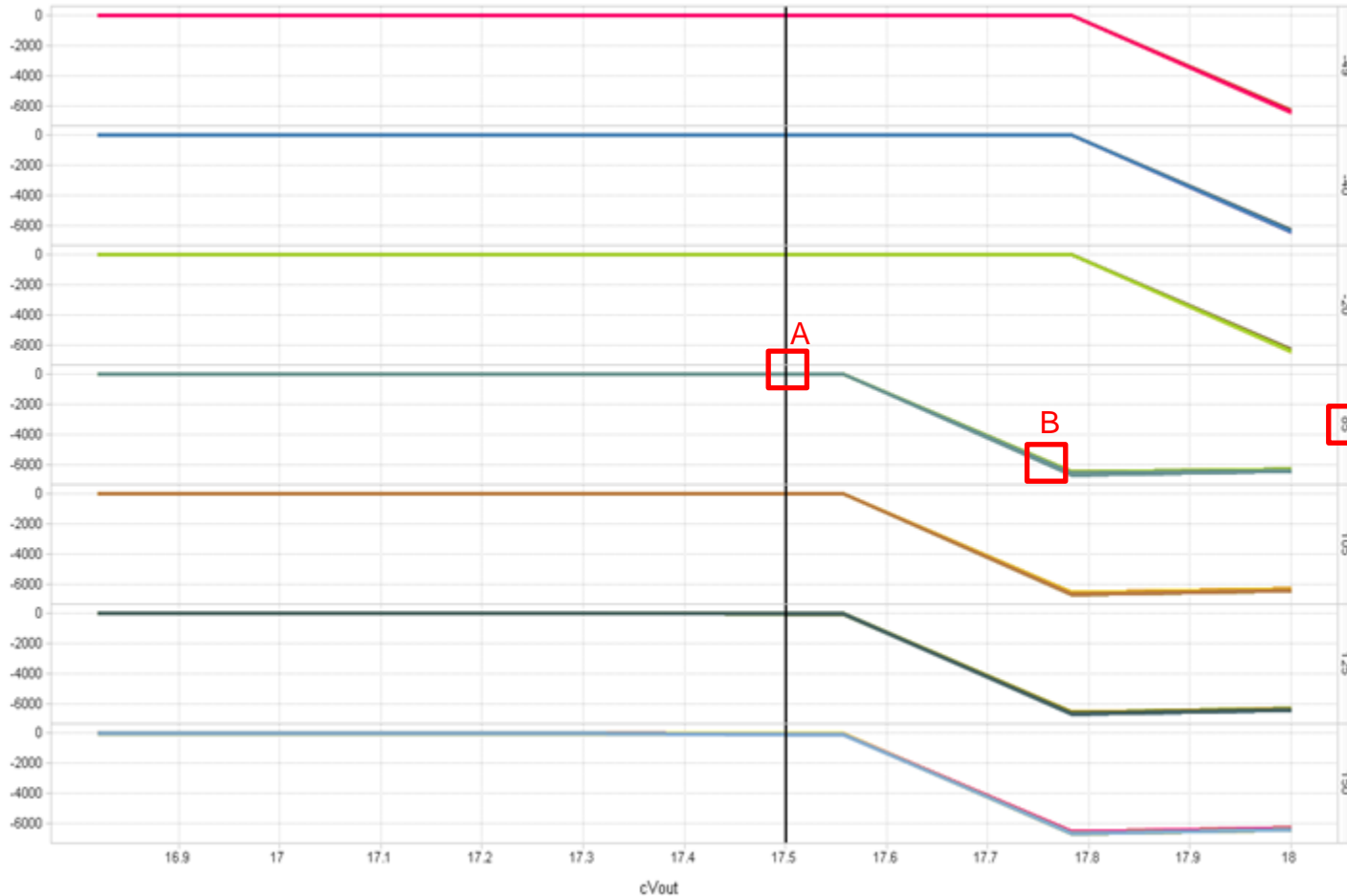

V₊ = +18V
V₋ = -18V

Point A:
V_{out} = (V₊) - 0.5V
V_{os} = 35μV
Aol = 114dB

Point B:
V_{out} = (V₊) - 0.25V
V_{os} = 6000μV
Aol = 69.42dB
Aol = x2958

Point B
Closed Loop Gain:
A_{cl} = Aol / (1 + Aolβ)
A_{cl} = 2958 / (1 + 2958 * 0.0065)
A_{cl} = 146
A_{cl} should be x154 !!

Gets WORSE Closer to the rail the output swings!

Note: Beyond point "B" is Test Equipment Range Limitation

Datasheet Specifications

Check Op Amp Datasheet for Op Amp used in application circuit as **ALL** Op Amps have this limitation!

- Output – Voltage Output Swing from Rail
 - Output **Saturation** Specification
 - Slam Test
 - Claw Curve
- Aol – Open Loop Voltage Gain
 - Measured in **Linear** Operating Range
 - Note Vout Swing where Aol is Tested

CMOS RRO Op Amps and Linear Vout Region

OPA188 – How do we know it is CMOS output?

ELECTRICAL CHARACTERISTICS:

High-Voltage Operation, $V_S = \pm 4 \text{ V}$ to $\pm 18 \text{ V}$ ($V_S = +8 \text{ V}$ to $+36 \text{ V}$) (continued)

At $T_A = +25^\circ\text{C}$, $R_L = 10 \text{ k}\Omega$ connected to $V_S / 2^{(1)}$, and $V_{CM} = V_{OUT} = V_S / 2^{(1)}$, unless otherwise noted.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNIT
OUTPUT					
Voltage output swing from rail	No load		6	15	mV
	$R_L = 10 \text{ k}\Omega$		220	250	mV
	$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$		310	350	mV

Output Saturation or Slam Test shows $< 300\text{mV}$ to the rail at light load ($10\text{k}\Omega$) and $\ll 100\text{mV}$ at no load.

OPA188 AoI Test

ELECTRICAL CHARACTERISTICS:

High-Voltage Operation, $V_S = \pm 4 \text{ V}$ to $\pm 18 \text{ V}$ ($V_S = +8 \text{ V}$ to $+36 \text{ V}$)

At $T_A = +25^\circ\text{C}$, $R_L = 10 \text{ k}\Omega$ connected to $V_S / 2^{(1)}$, and $V_{CM} = V_{OUT} = V_S / 2^{(1)}$, unless otherwise noted.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNIT
OPEN-LOOP GAIN					
A_{OL} Open-loop voltage gain	$(V-) + 0.5 \text{ V} < V_O < (V+) - 0.5 \text{ V}$	130	136		dB
	$(V-) + 0.5 \text{ V} < V_O < (V+) - 0.5 \text{ V}$, $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$	120	126		dB

$$V_{out} = (V+) - 0.5\text{V}$$

$$V_{out} = 18\text{V} - 0.5\text{V} = 17.5\text{V}$$

$$R_L = 10\text{k}\Omega$$

$$I_{out} = \frac{V_{out}}{R_L}$$

$$I_{out} = \frac{17.5\text{V}}{10\text{k}\Omega} = 1.75\text{mA}$$

$$R_{ds_on} = \frac{(V+) - V_{out}}{I_{out}} = \frac{18\text{V} - 17.5\text{V}}{1.75\text{mA}} = 285.7\Omega$$

OPA188 Claw Curves (they look like a Lobster Claw!)

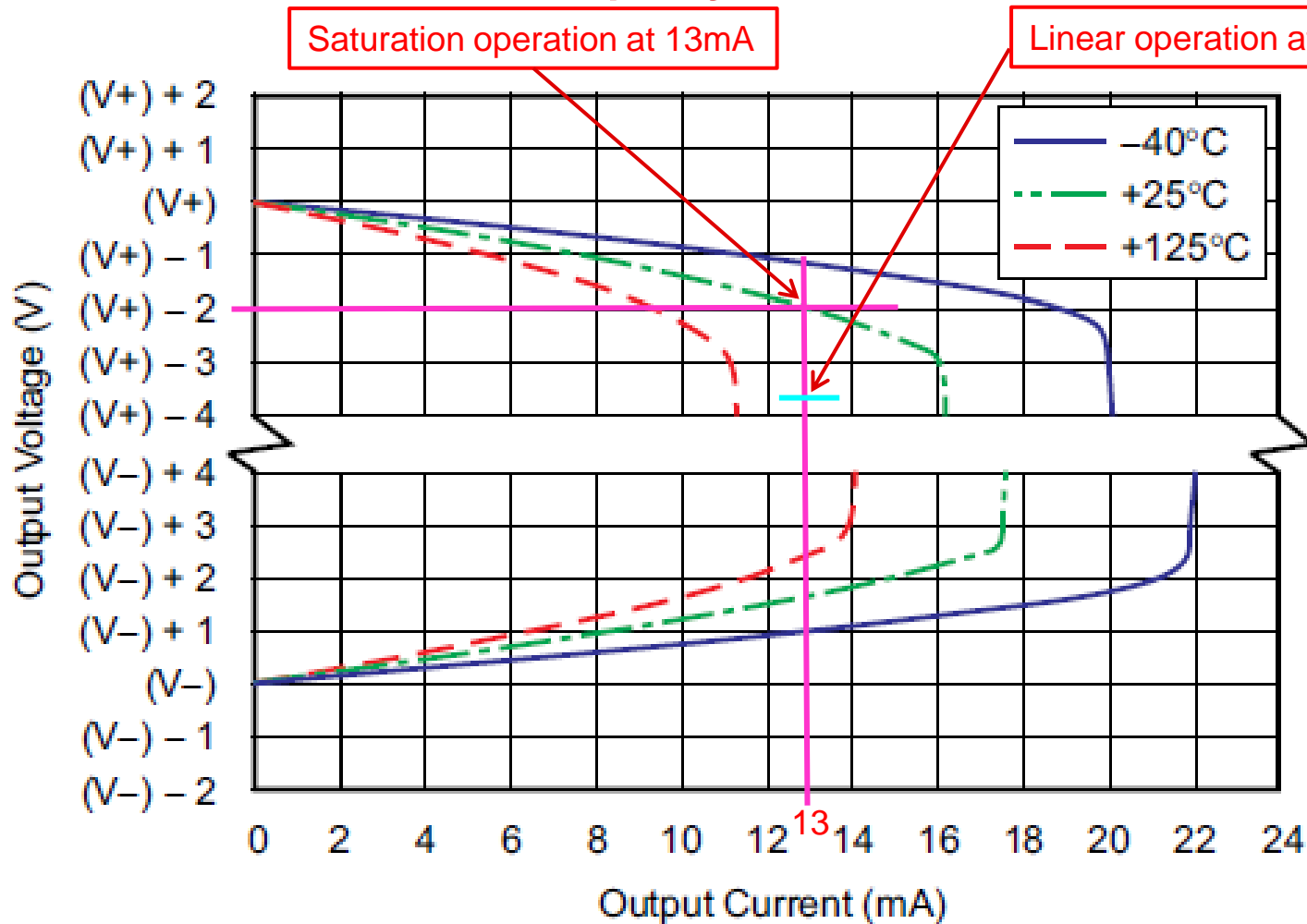


Figure 12. OUTPUT VOLTAGE SWING vs OUTPUT CURRENT (Maximum Supply)

OPA188 Claw Curve vs Linear Operation at 13mA

From Aol Test :

$$R_{ds_on} = 285.7\Omega$$

$$I_{out} = 13mA$$

$$V_{drop_rds} = I_{out} * R_{ds_on}$$

$$V_{drop_rds} = 13mA * 285.7\Omega = 3.7V$$

$$V_{drop_claw} = 2V @ 13mA$$

For Linear Operation at 13mA use $V_{drop_rds} = 3.7V$

Bipolar Emitter Follower Output Stage and Linear V_{out} Region

OPA227 –

How do we know it is Bipolar Emitter Follower output?

OUTPUT						
Voltage Output	$R_L = 10\text{ k}\Omega$	(V-)+2	(V+)-2	(V-)+2	(V+)-2	V
	$R_L = 10\text{ k}\Omega$	(V-)+2	(V+)-2	(V-)+2	(V+)-2	V
	$T_A = -40^\circ\text{C to } 85^\circ\text{C}$					
	$R_L = 600\ \Omega$	(V-)+3.5	(V+)-3.5	(V-)+3.5	(V+)-3.5	V
	$R_L = 600\ \Omega$	(V-)+3.5	(V+)-3.5	(V-)+3.5	(V+)-3.5	V
	$T_A = -40^\circ\text{C to } 85^\circ\text{C}$					

Output Saturation or Slam Test shows $>1.5\text{V}$ to the rail at light load ($10\text{k}\Omega$)

OPA227 AoI Test

6.6 Electrical Characteristics: OPAx227 Series ($V_S = \pm 5\text{ V}$ to $\pm 15\text{ V}$)

At $T_A = 25^\circ\text{C}$, and $R_L = 10\text{ k}\Omega$, unless otherwise noted.

PARAMETER	TEST CONDITIONS	OPA227P, U OPA2227P, U			OPA227PA, UA OPA2227PA, UA OPA4227PA, UA			UNIT
		MIN	TYP	MAX	MIN	TYP	MAX	
OPEN-LOOP GAIN								
A_{OL} Open-Loop Voltage Gain	$V_O = (V_-)+2\text{ V}$ to $(V_+)-2\text{ V}$, $R_L = 10\text{ k}\Omega$	132	160		132	160		dB
	$T_A = -40^\circ\text{C}$ to 85°C	132			132			dB
	$V_O = (V_-)+3.5\text{ V}$ to $(V_+)-3.5\text{ V}$, $R_L = 600\ \Omega$	132	160		132	160		dB
	$T_A = -40^\circ\text{C}$ to 85°C	132			132			dB

AoI Test ($10\text{k}\Omega$) :

$$V_{out} = (V_-) + 2V$$

$$V_{out} = -15V + 2V = -13V$$

$$R_L = 10\text{k}\Omega$$

$$I_{out} = \frac{V_{out}}{R_L}$$

$$I_{out} = \frac{-13V}{10\text{k}\Omega} = -1.3\text{mA}$$

AoI Test (600Ω) :

$$V_{out} = (V_-) + 3.5V$$


$$V_{out} = -15V + 3.5V = -11.5V$$

$$R_L = 600\Omega$$

$$I_{out} = \frac{V_{out}}{R_L}$$

$$I_{out} = \frac{-11.5V}{600\Omega} = -19.17\text{mA}$$

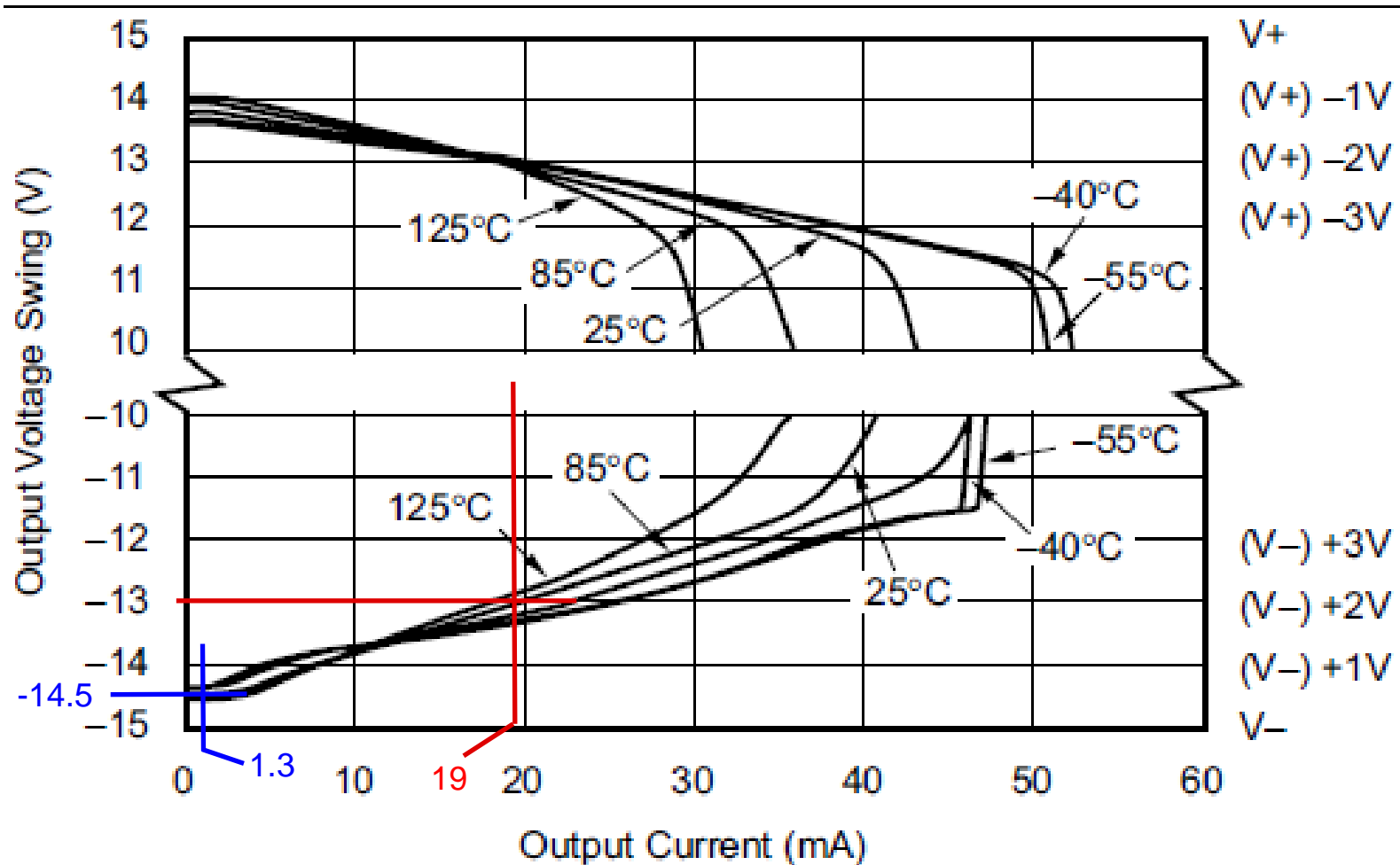OPA227 Claw Curves (they look like a Lobster Claw!)



OPA227 Claw Curve vs Linear Operation

OPA227	Vdrop	Vdrop
Iout	Aol	Claw
1.3mA	2V	0.5V
19mA	3.5V	2V

$$V_{\text{drop_Linear}} = V_{\text{drop_Claw}} + 1.5V$$

Bipolar Collector Output Stage and Linear Vout Region

OPA211 – How do we know it is Bipolar Emitter Follower output?

ELECTRICAL CHARACTERISTICS: $V_S = \pm 2.25V$ to $\pm 18V$ (continued)

BOLDFACE limits apply over the specified temperature range, $T_A = -40^\circ C$ to $+125^\circ C$.

At $T_A = +25^\circ C$, $R_L = 10k\Omega$ connected to midsupply, $V_{CM} = V_{OUT} =$ midsupply, unless otherwise noted.

PARAMETER	CONDITIONS	Standard Grade OPA211AI, OPA2211AI			High Grade OPA211I ⁽¹⁾			UNIT
		MIN	TYP	MAX	MIN	TYP	MAX	
OUTPUT								
Voltage Output	V_{OUT}	$R_L = 10k\Omega, A_{OL} \geq 114dB$			$(V-) + 0.2$			V
		$R_L = 600\Omega, A_{OL} \geq 110dB$			$(V-) + 0.6$			V
		$I_O < 15mA, A_{OL} \geq 110dB$			$(V-) + 0.6$			V

Output Saturation or Slam Test shows $<300mV$ to the rail at light load ($10k\Omega$). Not as small as CMOS RRO unloaded ($<100mV$) but not as large as Bipolar emitter follower output (2V).

OPA211 – How do we know it is Bipolar Collector output?

Also because of the simplified schematic in the datasheet !

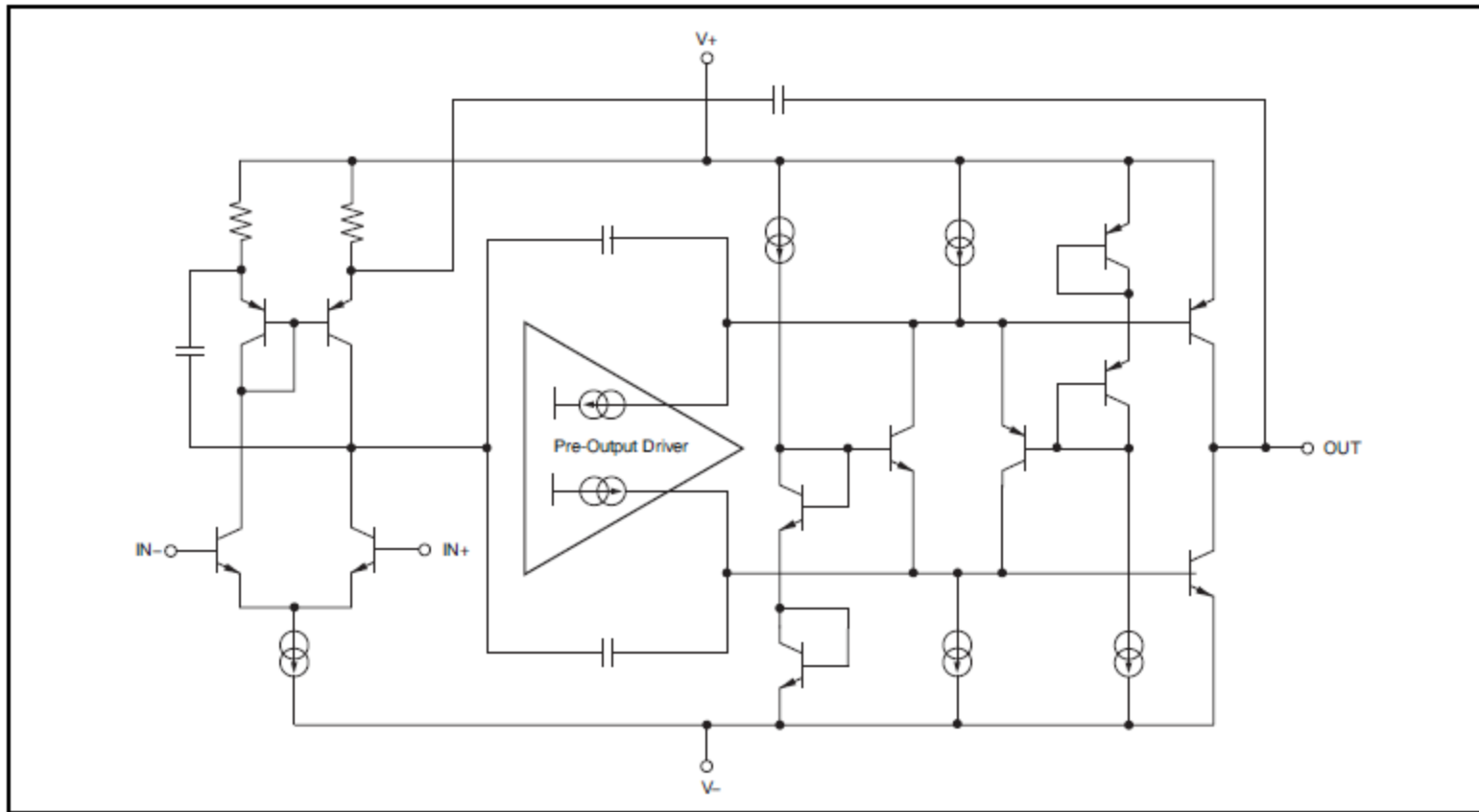


Figure 44. OPA211 Simplified Schematic

OPA211 Aol Test

ELECTRICAL CHARACTERISTICS: $V_S = \pm 2.25V$ to $\pm 18V$

BOLDFACE limits apply over the specified temperature range, $T_A = -40^\circ C$ to $+125^\circ C$.

At $T_A = +25^\circ C$, $R_L = 10k\Omega$ connected to midsupply, $V_{CM} = V_{OUT} =$ midsupply, unless otherwise noted.

OPEN-LOOP GAIN							
Open-Loop Voltage Gain	A_{OL}	$(V-) + 0.2V \leq V_O \leq (V+) - 0.2V,$ $R_L = 10k\Omega$	114	130	114	130	dB
	A_{OL}	$(V-) + 0.6V \leq V_O \leq (V+) - 0.6V,$ $R_L = 600\Omega$	110	114	110	114	dB
Over Temperature							
OPA211	A_{OL}	$(V-) + 0.6V \leq V_O \leq (V+) - 0.6V,$ $I_O \leq 15mA$	110		110		dB
OPA211	A_{OL}	$(V-) + 0.6V \leq V_O \leq (V+) - 0.6V,$ $15mA \leq I_O \leq 30mA$	103		103		dB
OPA2211 (per channel)	A_{OL}	$(V-) + 0.6V \leq V_O \leq (V+) - 0.6V,$ $I_O \leq 15mA$	100				dB

Aol Test (10k Ω):

$$V_{out} = (V+) - 0.2V$$

$$V_{out} = 18V - 0.2V = 17.8V$$

$$R_L = 10k\Omega$$

$$I_{out} = \frac{V_{out}}{R_L}$$

$$I_{out} = \frac{17.8V}{10k\Omega} = 1.78mA$$

Aol Test (600 Ω):

$$V_{out} = (V+) - 0.6V$$

$$V_{out} = 18V - 0.6V = 17.4V$$

$$R_L = 600\Omega$$

$$I_{out} = \frac{V_{out}}{R_L}$$

$$I_{out} = \frac{17.4V}{600\Omega} = 29mA$$

From OPA211 Aol Test

Aol Test (10k Ω) \rightarrow Vdrop_10k = 0.2V @ 1.78mA

Aol Test (600 Ω) \rightarrow Vdrop_600 = 0.6V @ 29mA

Rc (collector output resistance) :


$$R_c = \frac{V_{\text{drop_600}} - V_{\text{drop_10k}}}{I_{\text{out_600}}}$$

$$R_c = \frac{0.6\text{V} - 0.2\text{V}}{29\text{mA}} = 13.8\Omega$$

$$V_{\text{drop_Linear}} = I_{\text{out}} * R_c + 0.2\text{V}$$

OPA211 Claw Curves (they look like a Lobster Claw!)

OUTPUT VOLTAGE vs OUTPUT CURRENT

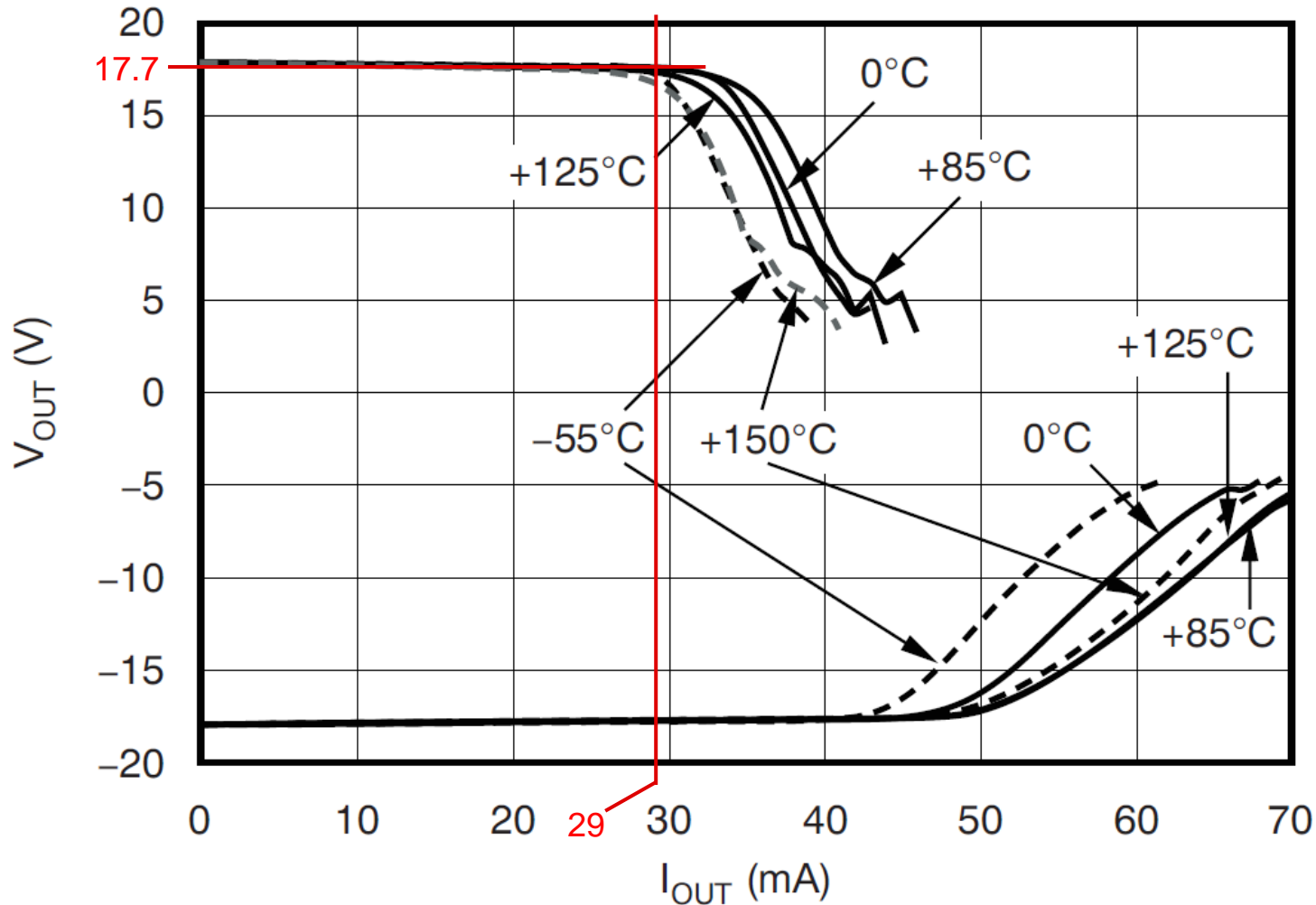

OPA211 Claw Curve vs Linear Operation

OPA211	Vdrop	Vdrop
Iout	Aol	Claw
29mA	0.6V	0.3V

$$\text{Vdrop_Linear} = (\text{Iout} * \text{Rc}) + 0.2\text{V}$$

Rc for OPA211 = 13.8Ω