

# Signal Conditioning and Linearization of RTD Sensors

Collin Wells

Texas Instruments

HPA Precision Linear Applications

9/24/11

# Introduction

- Primary Support
  - 4-20mA Loop Drivers (XTRXXX)
  - Gamma Buffers (BUFXXXXX)
- Other Support
  - Temperature Sensors (TMP)
  - IR Temperature Sensors (TMP006)
  - OPA Stability
  - Instrument Amplifiers
- Applications (Other)
  - Industrial – Programmable Logic Controllers (PLC)
  - RTD
  - Reference Designs





# Contents

- RTD Overview
- RTD Nonlinearity
- Analog Linearization
- Digital Acquisition and Linearization

# What is an RTD?

- Resistive Temperature Detector
- Sensor with a predictable resistance vs. temperature
- Measure the resistance and calculate temperature based on the Resistance vs. Temperature characteristics of the RTD material

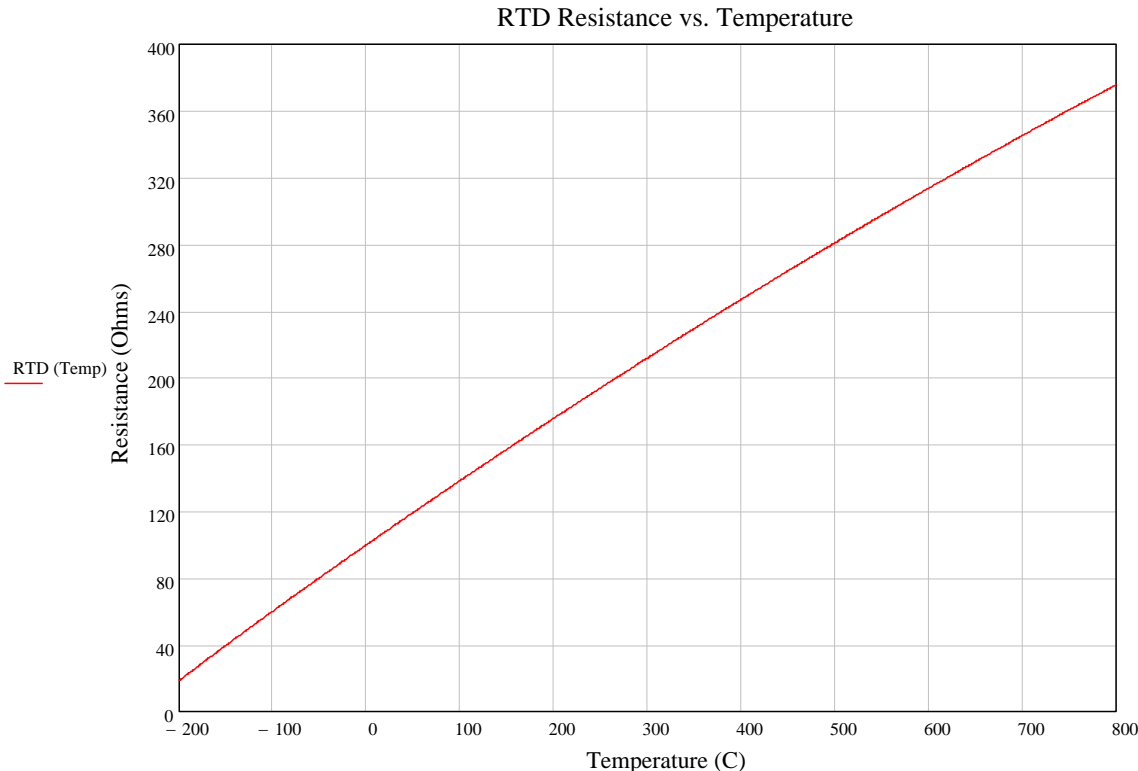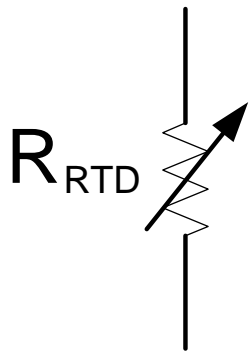

**PT100**  
 **$\alpha = 0.00385$**

# How does an RTD work?

$$\text{Resistance} = R = \frac{\rho \cdot L}{A}$$

$$\text{Resistivity} = \rho = \frac{1}{e \cdot n \cdot \mu}$$

- L = Wire Length
- A = Wire Area
- e = Electron Charge (1.6e-19 Coulombs)
- n = Electron Density
- u = Electron Mobility

- The product  $n \cdot u$  decreases over temperature, therefore resistance increases over temperature (PTC)
- Linear Model of Conductor Resistivity Change vs. Temperature

$$\rho(t) = \rho_0 \left( 1 + \alpha(t - t_0) \right)$$

# What is an RTD made of?

- Platinum (pt)
- Nickel (Ni)
- Copper (Cu)
- Have relatively linear change in resistance over temp
- Have high resistivity allowing for smaller dimensions
- Either Thin-Film or Wire-Wound

Metal	Resistivity (Ohm/CMF)
Gold (Au)	13
Silver (Ag)	8.8
Copper (Cu)	9.26
Platinum (Pt)	59
Tungsten (W)	30
Nickel (Ni)	36

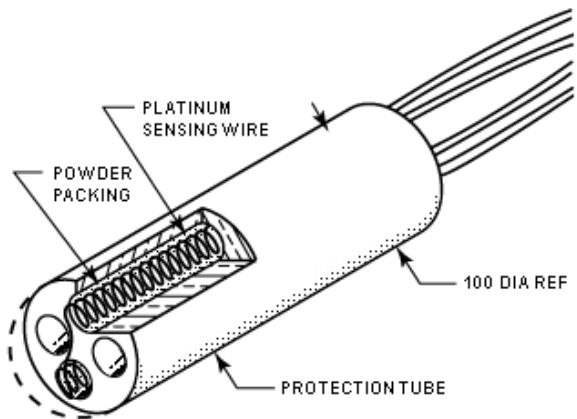


Figure 1. The coiled element sensor, made by inserting the helical sensing wires into a packed powder-filled insulating mandrel, provides a strain-free sensing element.

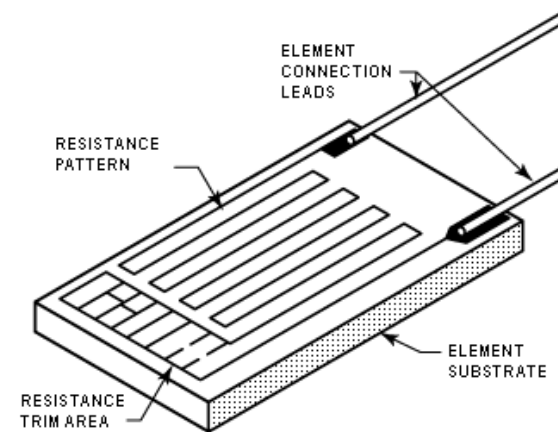


Figure 2. The thin film sensing element is made by depositing a thin layer of platinum in a resistance pattern on a ceramic substrate. A glassy layer is applied for seal and protection.

\*Images from RDF Corp

# How Accurate is an RTD?

- Absolute accuracy is “Class” dependant - defined by DIN-IEC 60751. Allows for easy interchangeability of field sensors

Tolerance Class (DIN-IEC 60751)	**Temperature Range of Validity		Tolerance Values (C)	Resistance at 0C (Ohms)	Error at 100C (C)	Error over Wire-Wound Range (C)
	Wire-Wound	Thin-Film				
*AAA (1/10 DIN)	0 - +100	0 - +100	+/- (0.03 + 0.0005*t)	100 +/- 0.012	0.08	0.08
AA (1/3DIN)	-50 - +250	0 - +150	+/- (0.1 + 0.0017*t)	100 +/- 0.04	0.27	0.525
A	-100 - +450	-30 - +300	+/- (0.15 + 0.002*t)	100 +/- 0.06	0.35	1.05
B	-196 - +600	-50 - +500	+/- (0.3 + 0.005*t)	100 +/- 0.12	0.8	3.3
C	-196 - +600	-50 - +600	+/- (0.6 + 0.01*t)	100 +/- 0.24	1.6	6.6


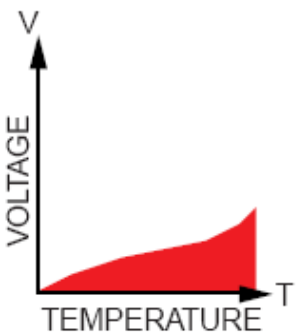

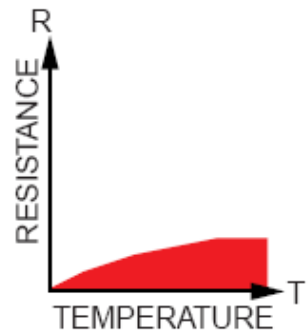

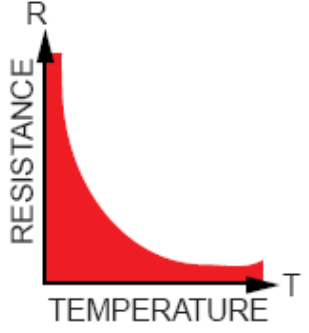

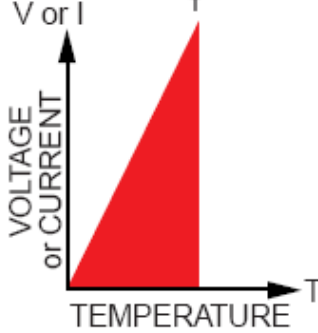
\*AAA (1/10DIN) is not included in the DIN-IEC-60751 spec but is an industry accepted tolerance class for high-performance measurements

\*\*Manufacturers may choose to guarantee operation over a wider temperature range than the DIN-IEC60751 provides

- Repeatability usually very good, allows for individual sensor calibration
- Long-Term Drift usually <0.1C/year, can get as low as 0.0025C/year

# Why use an RTD?

Table Comparing Advantages and Disadvantages of Temp Sensors

	<b>Thermocouple</b>  	<b>RTD</b>  	<b>Thermistor</b>  	<b>I. C. Sensor</b>  
<b>Advantages</b>	<input type="checkbox"/> Self-powered <input type="checkbox"/> Simple <input type="checkbox"/> Rugged <input type="checkbox"/> Inexpensive <input type="checkbox"/> Wide variety <input type="checkbox"/> Wide temperature range	<input type="checkbox"/> Most stable <input type="checkbox"/> Most accurate <input type="checkbox"/> More linear than thermocouple	<input type="checkbox"/> High output <input type="checkbox"/> Fast <input type="checkbox"/> Two-wire ohms measurement	<input type="checkbox"/> Most linear <input type="checkbox"/> Highest output <input type="checkbox"/> Inexpensive
<b>Disadvantages</b>	<input type="checkbox"/> Non-linear <input type="checkbox"/> Low voltage <input type="checkbox"/> Reference required <input type="checkbox"/> Least stable <input type="checkbox"/> Least sensitive	<input type="checkbox"/> Expensive <input type="checkbox"/> Current source required <input type="checkbox"/> Small $\Delta R$ <input type="checkbox"/> Low absolute resistance <input type="checkbox"/> Self-heating	<input type="checkbox"/> Non-linear <input type="checkbox"/> Limited temperature range <input type="checkbox"/> Fragile <input type="checkbox"/> Current source required <input type="checkbox"/> Self-heating	<input type="checkbox"/> $T < 200^\circ\text{C}$ <input type="checkbox"/> Power supply required <input type="checkbox"/> Slow <input type="checkbox"/> Self-heating <input type="checkbox"/> Limited configurations




# How to Measure an RTD Resistance?

- Use a.....

**Current Source**


or

**Wheatstone Bridge**

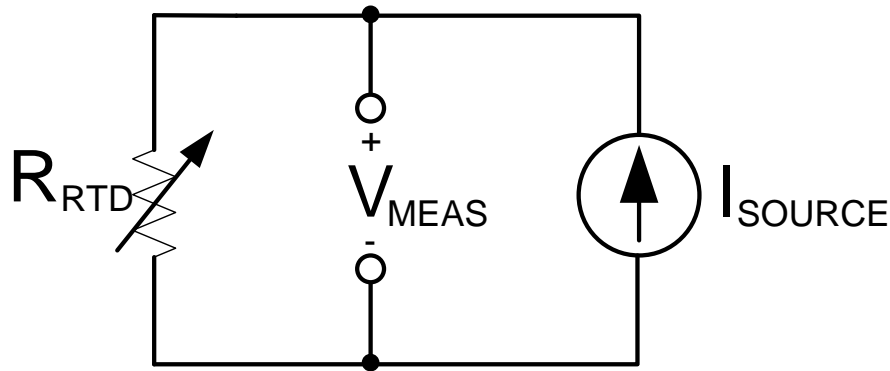

$$V_{meas} = I_{source} \cdot R_{RTD}$$
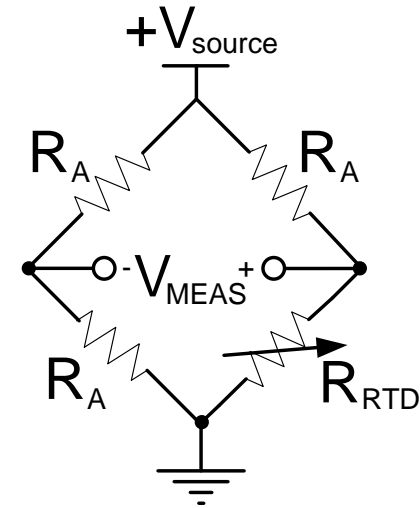
$$R_{RTD} = \frac{V_{meas}}{I_{source}}$$




$$V_{meas} = V_{source} \cdot \left[ \left( \frac{R_{RTD}}{R_A + R_{RTD}} \right) - \frac{1}{2} \right]$$

$$R_{RTD} = \frac{2 \cdot R_A \cdot V_{meas} + R_A \cdot V_{source}}{V_{source} - 2 \cdot V_{meas}}$$

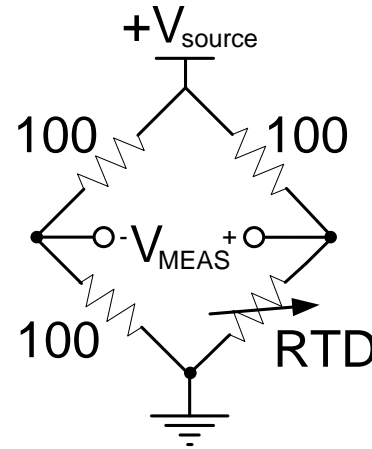
# Note on Non-Linear Output of Bridge

$$V_{\text{meas}} = V_{\text{source}} \cdot \left[ \left( \frac{R_{\text{RTD}}}{R_A + R_{\text{RTD}}} \right) - \frac{1}{2} \right]$$






Denominator causes a non-linear output even for a linear sensor



$\Delta\text{RTD} = 50\text{Ohms}$

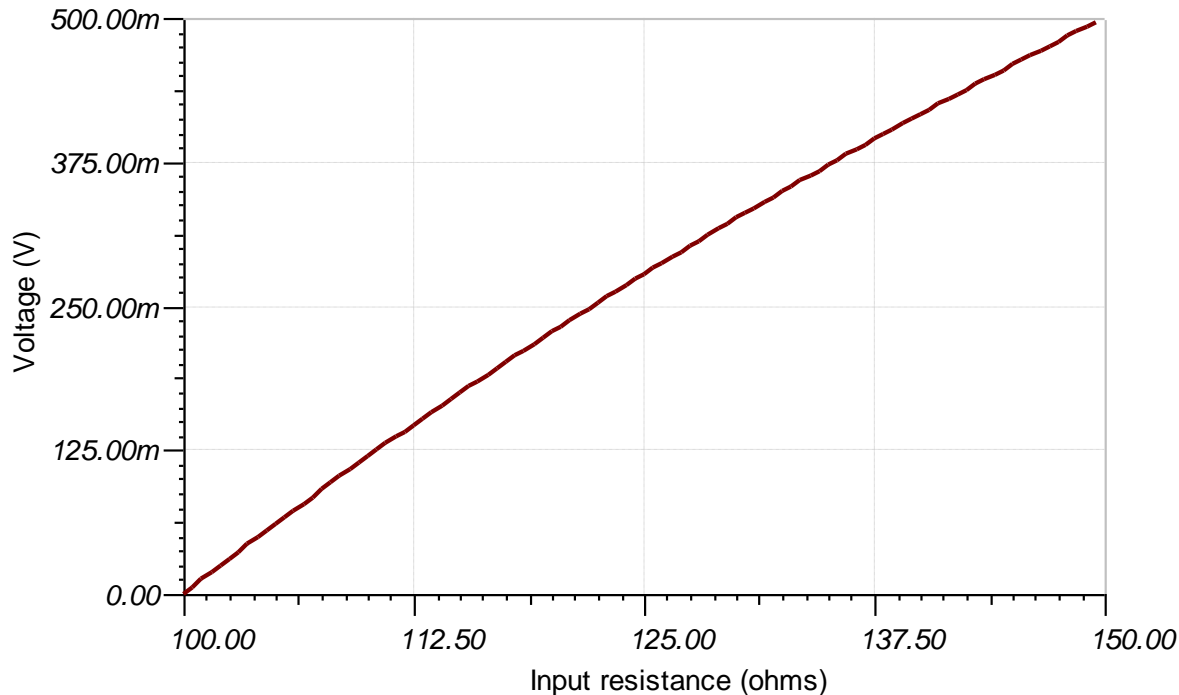


# Simple Current Source / Sink Circuits

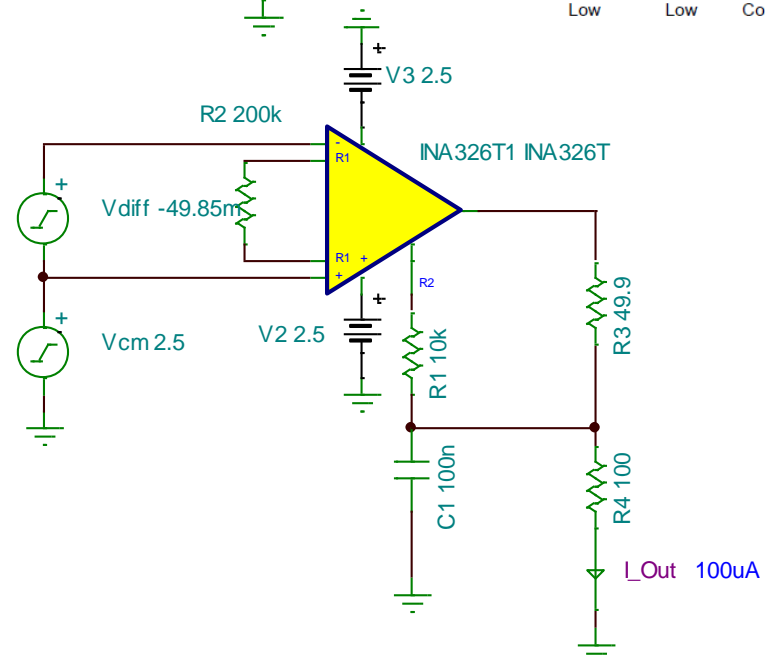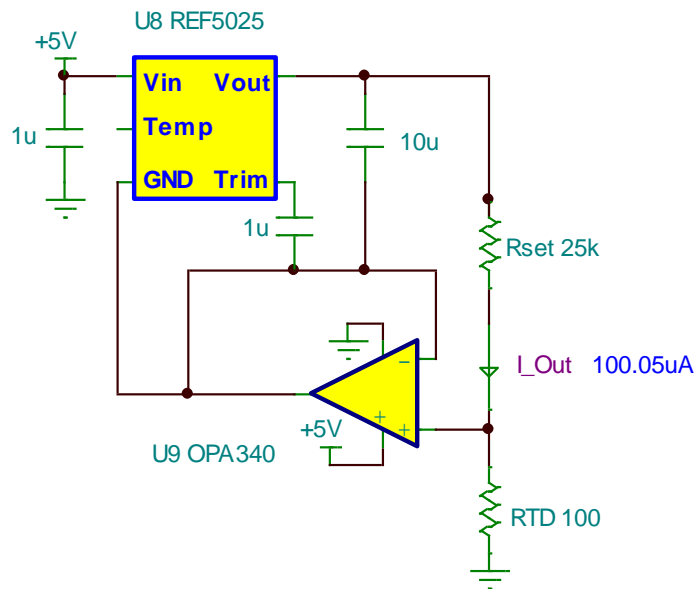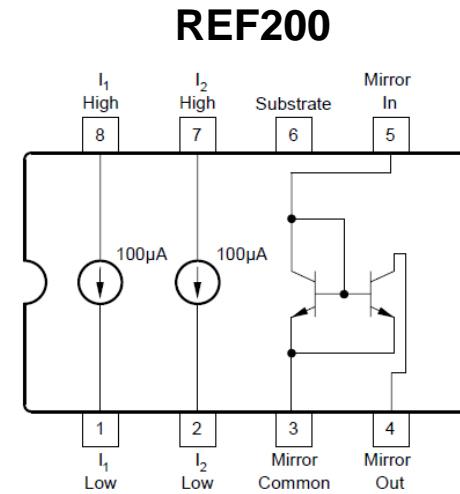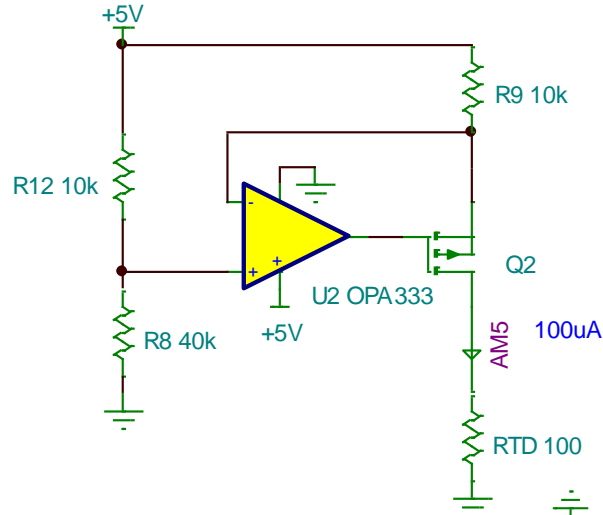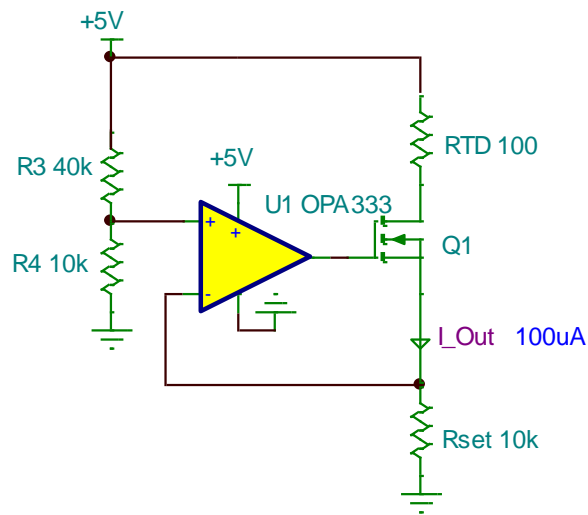


# RTD Types and Their Parasitic Lead Resistances


**2-Wire**

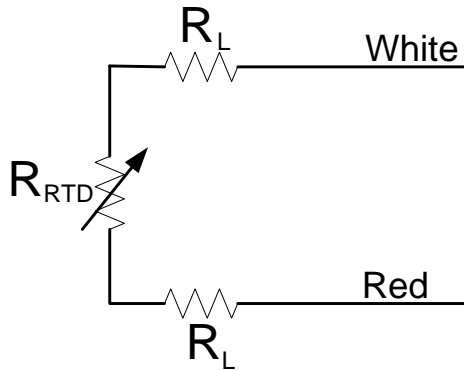


**3-Wire**

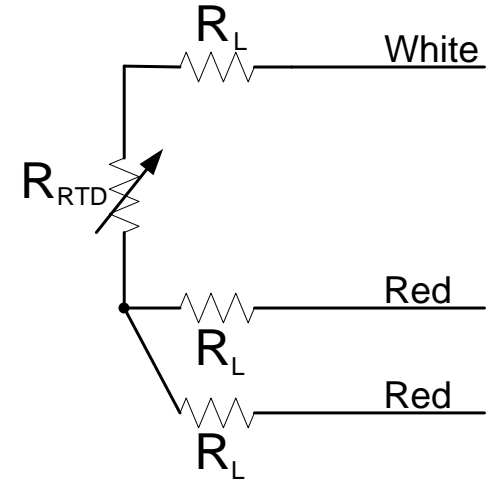


**4-Wire**

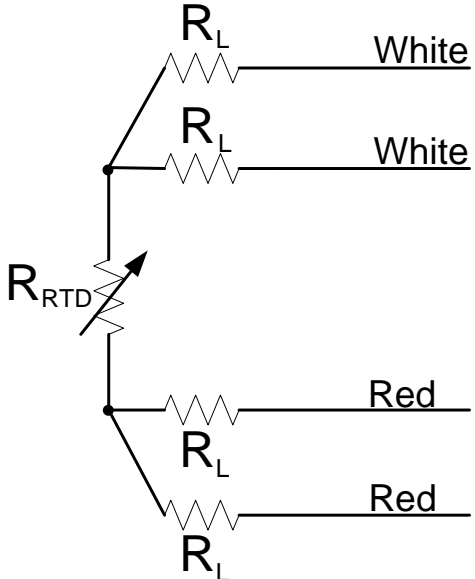

**2-Wire with  
Compensating  
Loop**

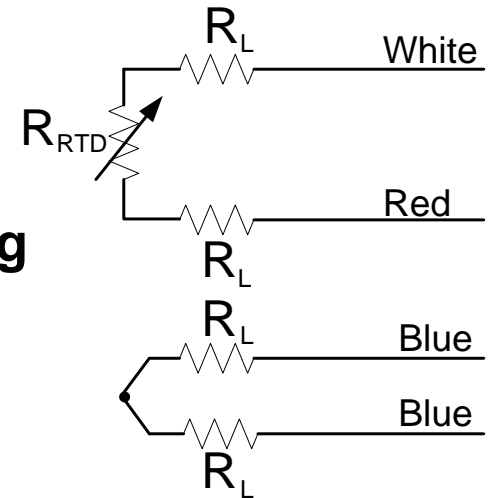


# 2-Wire Measurements

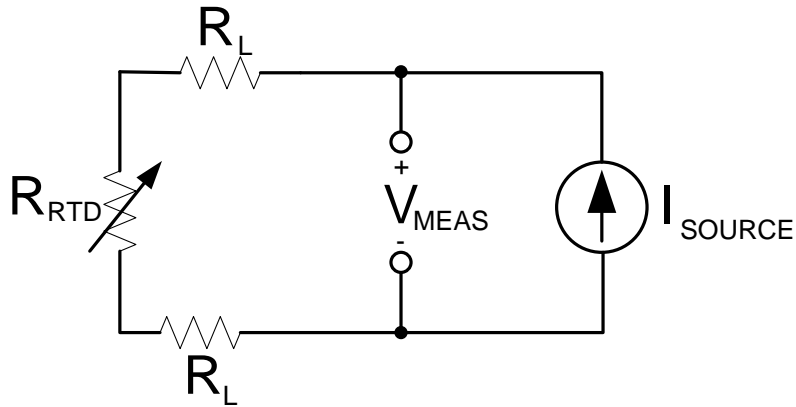

$$V_{meas} = I_{source} \cdot R_{RTD} + I_{source} \cdot 2 \cdot R_L$$



$$\text{Error} = I_{source} \cdot 2R_L$$

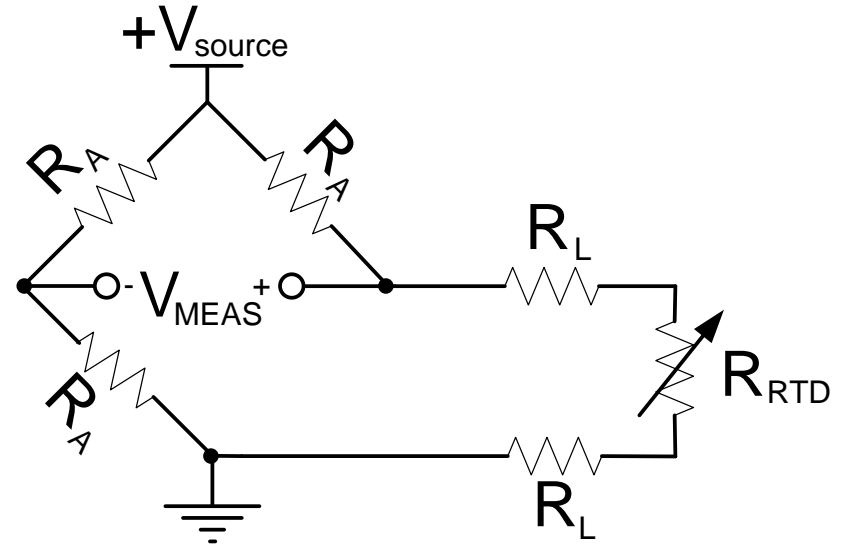

$$V_{meas} = V_{source} \cdot \left[ \left( \frac{R_{RTD} + 2R_L}{R_A + R_{RTD} + 2R_L} \right) - \frac{1}{2} \right]$$

$$\text{Error} = V_{source} \cdot \left[ \frac{2 \cdot R_A \cdot R_L}{(R_A + R_{RTD}) \cdot (R_A + 2 \cdot R_L + R_{RTD})} \right]$$

# 3-Wire Measurements

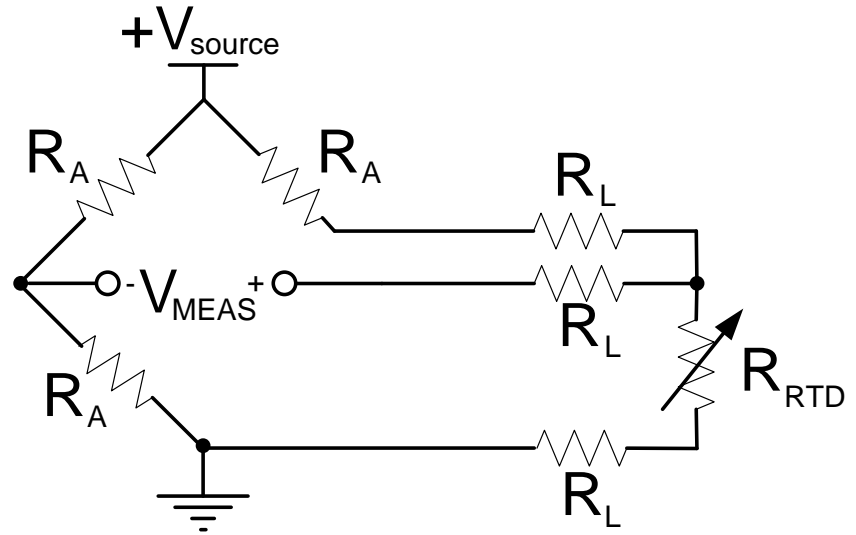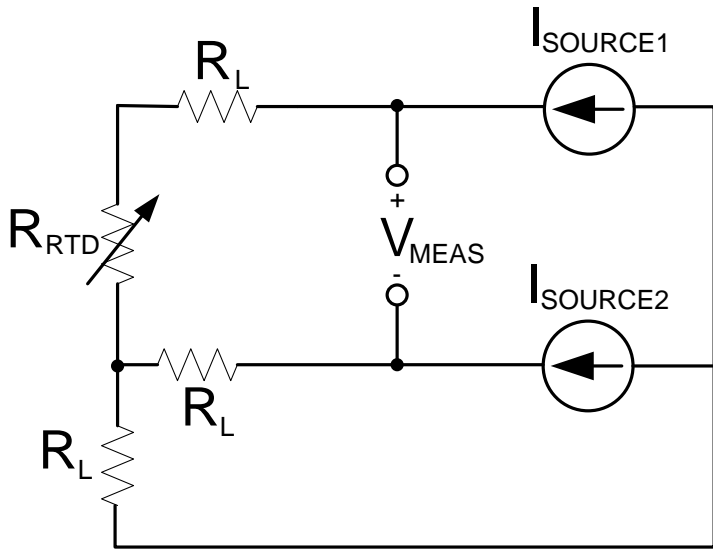

$$I_{\text{source1}} = I_{\text{source2}} = I$$

$$V_{\text{meas}_+} = I \cdot R_L + I \cdot R_{\text{RTD}} + (2 \cdot I) \cdot R_L = I \cdot R_{\text{RTD}} + 3 \cdot I \cdot R_L$$

$$V_{\text{meas}_-} = I \cdot R_L + (2 \cdot I) \cdot R_L = 3 \cdot I \cdot R_L$$


$$V_{\text{meas}_+} - V_{\text{meas}_-} = (I \cdot R_{\text{RTD}} + 3 \cdot I \cdot R_L) - (3 \cdot I \cdot R_L) = I \cdot R_{\text{RTD}}$$

**Error = 0 as long as Isource1 = Isource2 and RL are equal**

$$V_{\text{meas}} = V_{\text{source}} \left[ \left( \frac{R_{\text{RTD}} + R_L}{R_A + R_{\text{RTD}} + 2 \cdot R_L} \right) - \frac{1}{2} \right]$$


$$\text{Error} = V_{\text{source}} \cdot \left[ \frac{R_L \cdot (R_A - R_{\text{RTD}})}{(R_A + R_{\text{RTD}}) \cdot (R_A + 2 \cdot R_L + R_{\text{RTD}})} \right]$$

# 4-Wire Measurements

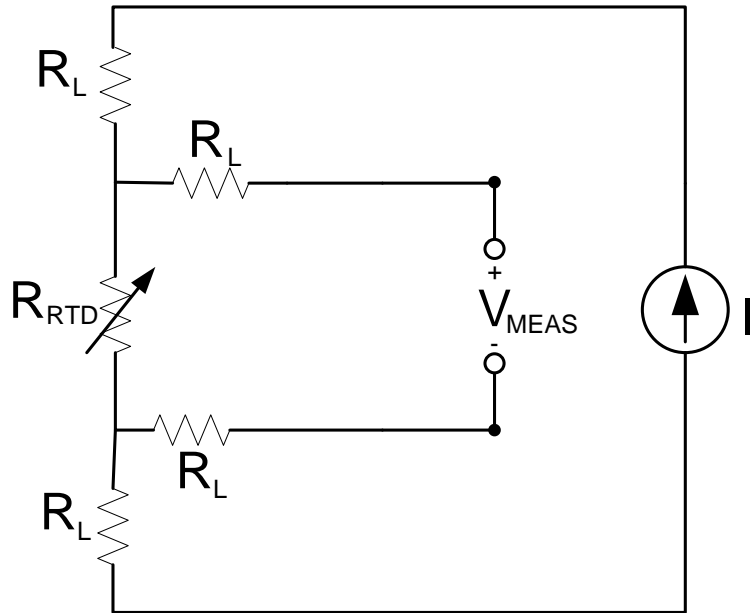

$$V_{\text{meas}} = I_{\text{source}} \cdot R_{\text{RTD}}$$

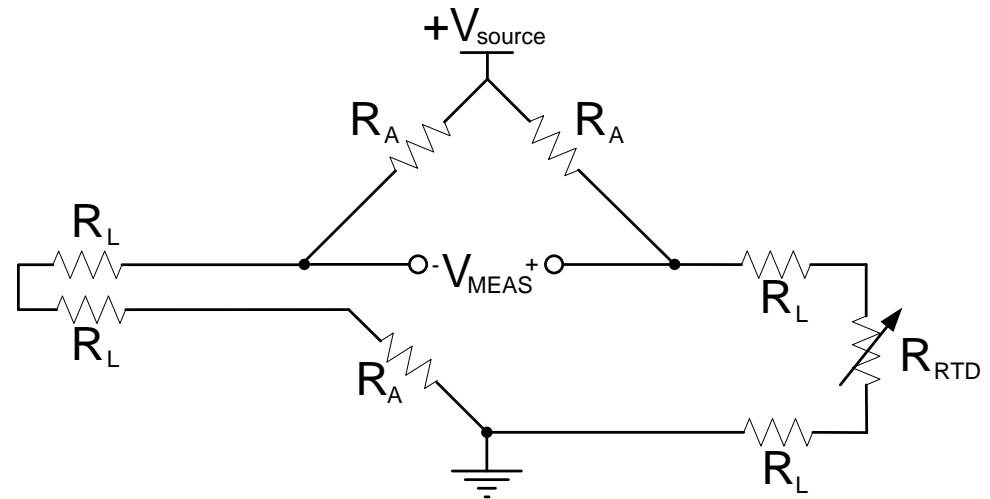**System Errors reduced to measurement circuit accuracy**




$$V_{\text{meas}} = \frac{R_A \cdot V_{\text{source}} \cdot (R_A - R_{\text{RTD}})}{2 \cdot R_A^2 + 6 \cdot R_A \cdot R_L + 2 \cdot R_{\text{RTD}} R_A + 4 \cdot R_L^2 + 2 \cdot R_{\text{RTD}} R_L}$$

$$\text{Error} = V_{\text{source}} \left[ \frac{R_L \cdot (2.0 R_A - 2.0 R_{\text{RTD}})}{(R_A + R_{\text{RTD}}) \cdot (R_A + 4.0 R_L + R_{\text{RTD}})} \right]$$
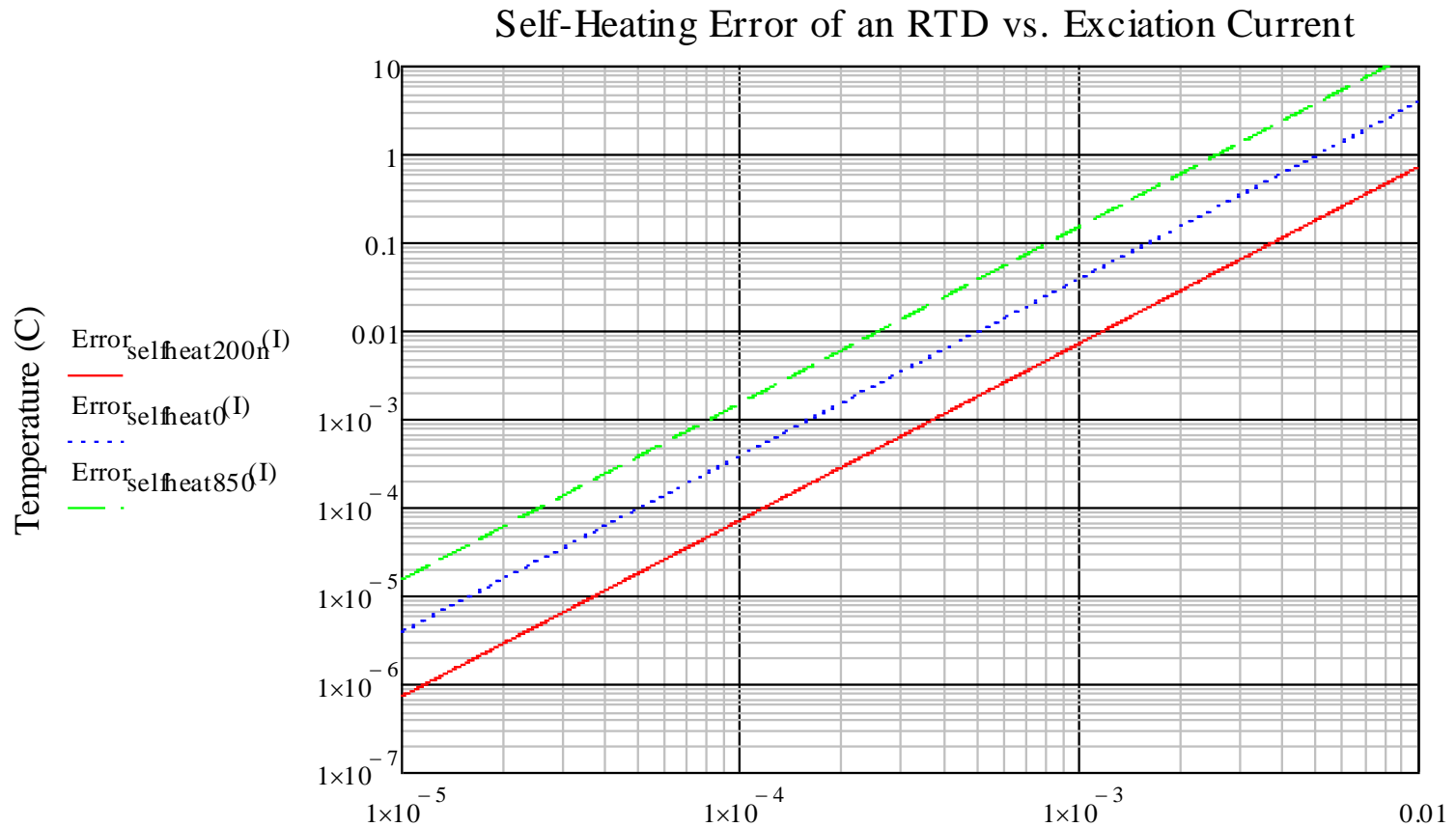
# Self-Heating Errors of RTD

- Typically 2.5mW/C – 60mW/C
- Set excitation level so self-heating error is <10% of the total error budget





# RTD Resistance vs Temperature

## Callendar-Van Dusen Equations

$$\text{For } (T > 0): \text{RTD}(T) := R_0 \cdot \left[ 1 + A \cdot T + B \cdot (T^2) \right]$$

$$\text{For } (T < 0): \text{RTD}(T) := R_0 \cdot \left[ 1 + A \cdot T + B \cdot (T^2) + C \cdot (T^3) \cdot (T - 100) \right]$$

## Equation Constants for

**IEC 60751 PT-100 RTD ( $\alpha = 0.00385$ )**


$$R_0 := 100$$

$$A := 3.908310^{-3}$$

$$B := -5.77510^{-7}$$

$$C := -4.18310^{-12}$$


RTD Resistance vs. Temperature

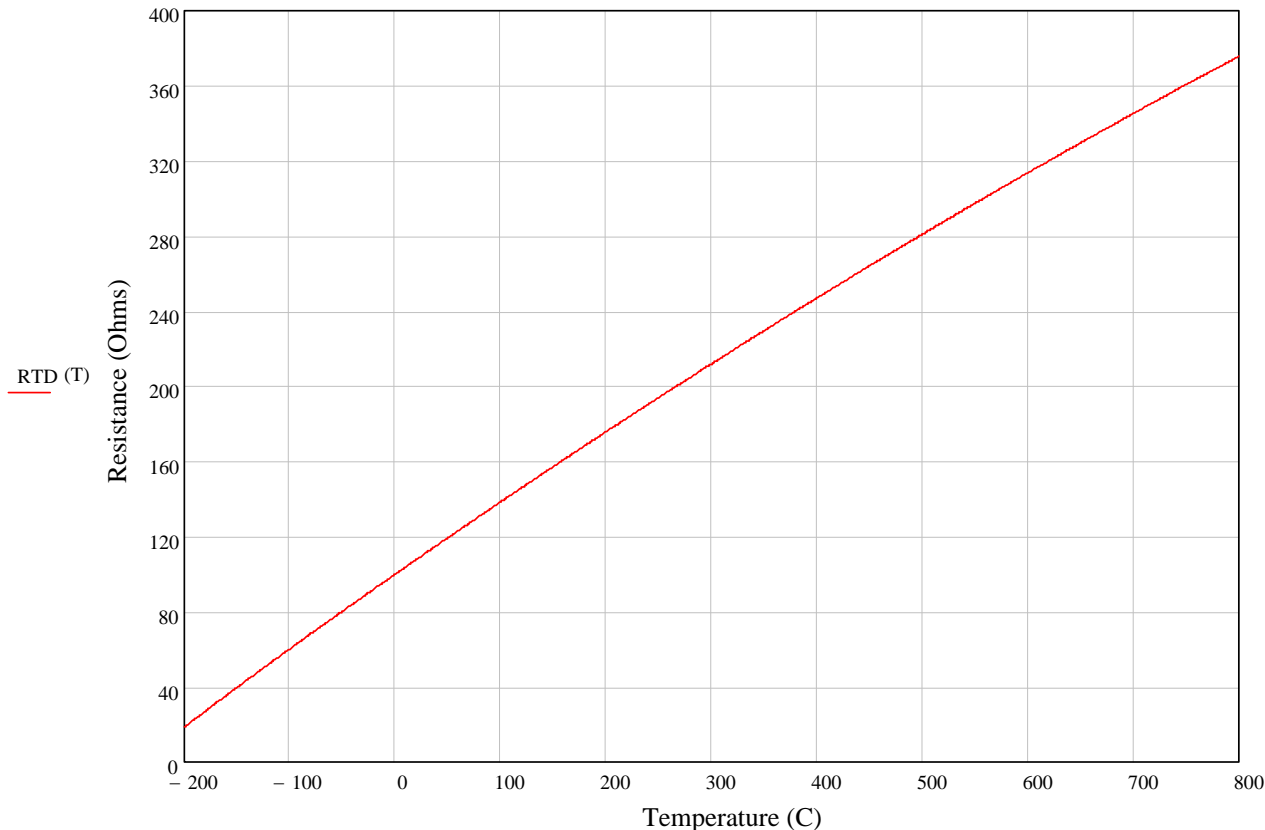


# RTD Nonlinearity

Linear fit between the two end-points shows the Full-Scale nonlinearity

RTD Resistance vs. Temperature

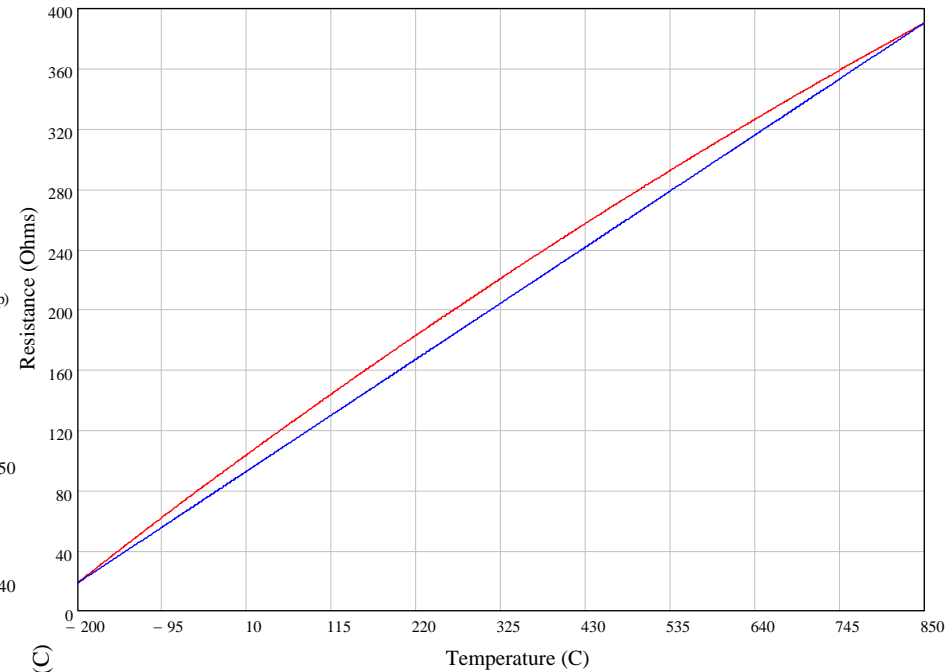

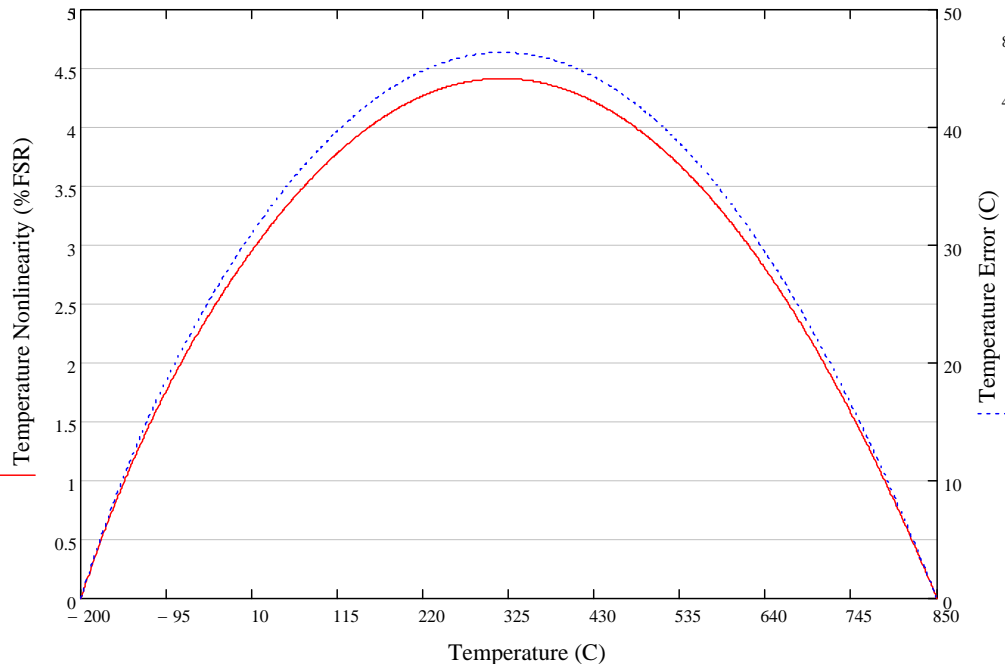Nonlinearity and Temperature Error vs. Temperature



**Nonlinearity = 4.5%**

**Temperature Error > 45C**

# RTD Nonlinearity

$$\text{For } (T > 0): \text{RTD}(T) := R_0 \cdot [1 + A \cdot T + B \cdot (T^2)]$$

$$\text{RTD}_{\text{linear}}(T) := R_0 \cdot (1 + A \cdot T)$$

$$\text{For } (T < 0): \text{RTD}(T) := R_0 \cdot [1 + A \cdot T + B \cdot (T^2) + C \cdot (T^3) \cdot (T - 100)]$$

$$R_0 := 100$$


$$A := 3.908310^{-3}$$

$$B := -5.77510^{-7}$$


$$C := -4.18310^{-12}$$

**B and C terms are negative so 2<sup>nd</sup> and 3<sup>rd</sup> order effects decrease the sensor output over the sensor span.**

RTD(Temp)  
RTD<sub>linear</sub>(Temp)

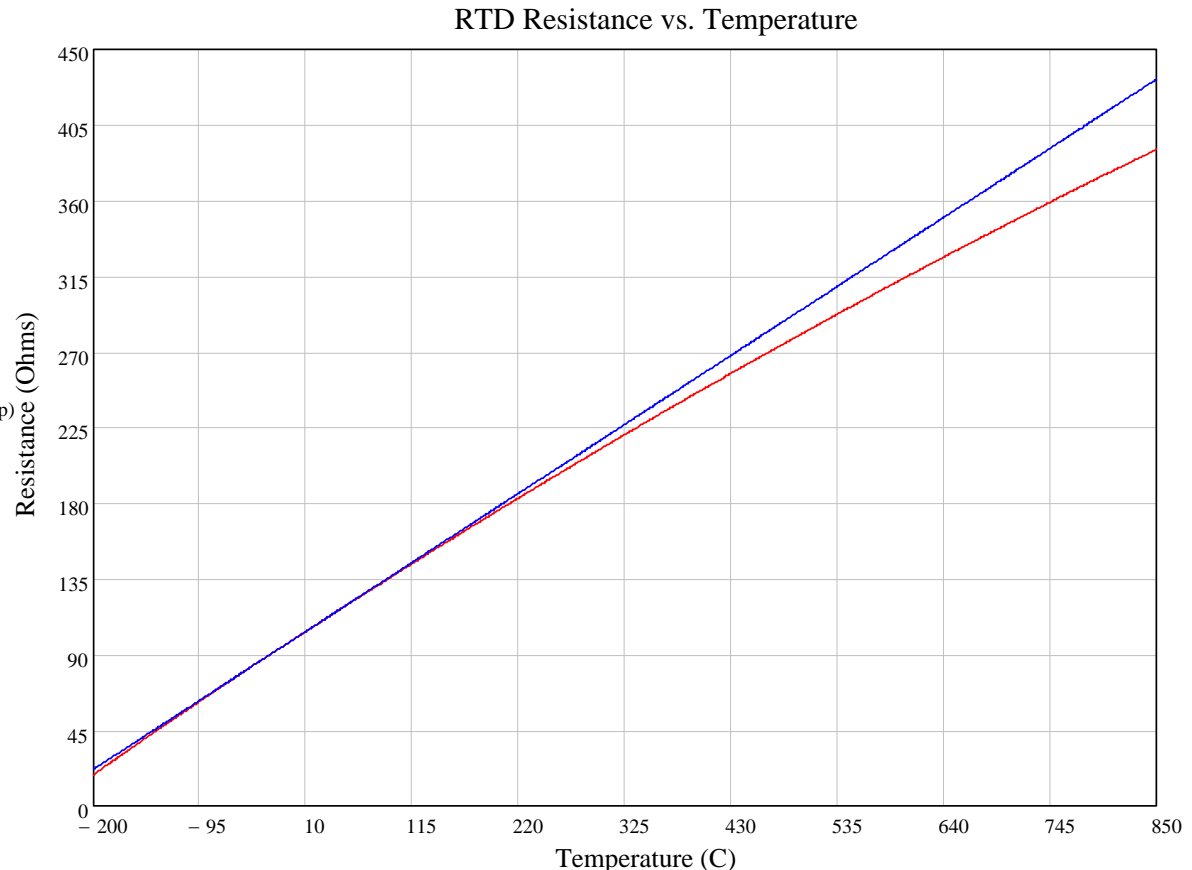


# Measurement Nonlinearity

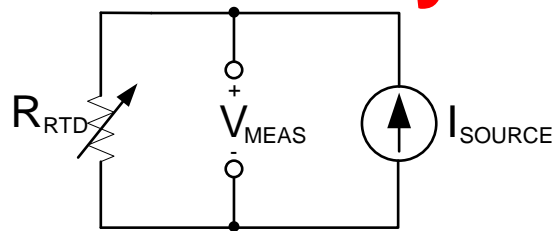


$$V_{meas} = I_{source} \cdot R_{RTD}$$

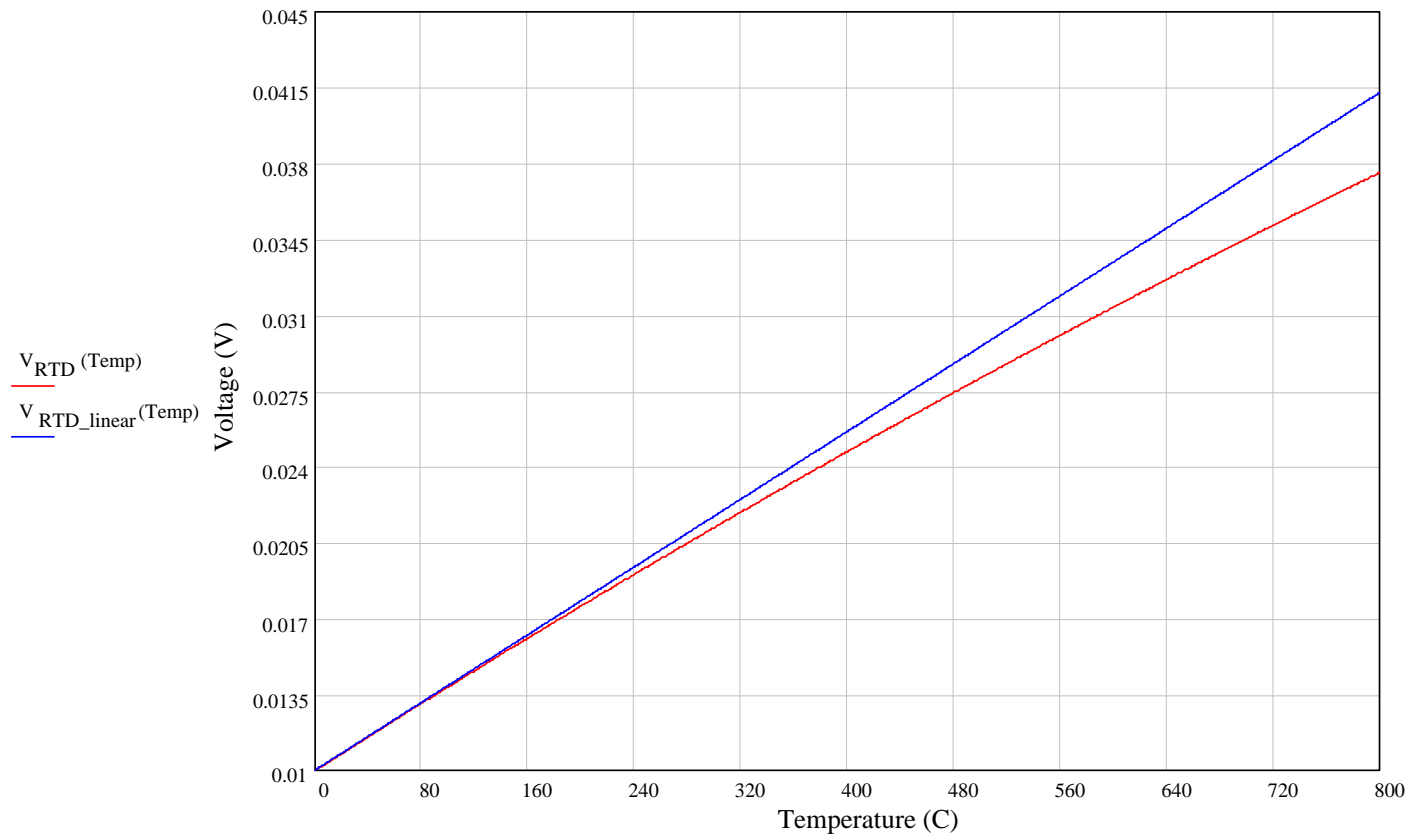RTD Sensor Output vs. Temperature (I<sub>source</sub> = 100uA)



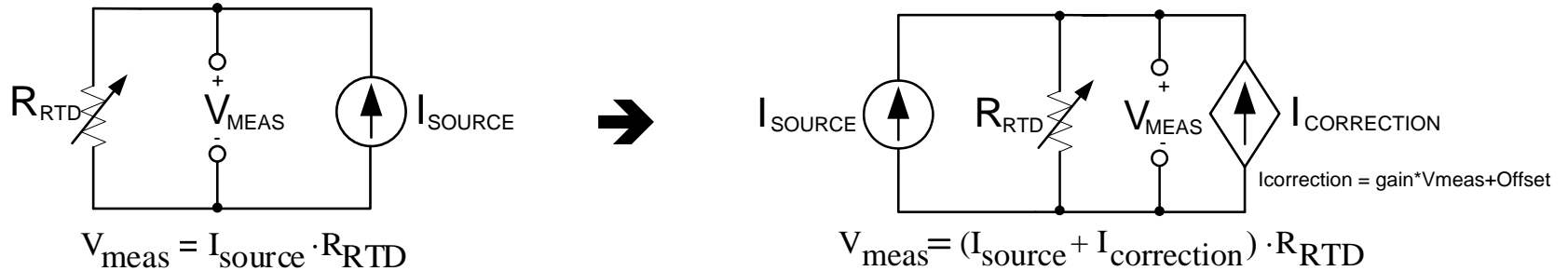
# Correcting for Non-Linearity

Sensor output decreases over span? Compensate by increasing excitation over span!



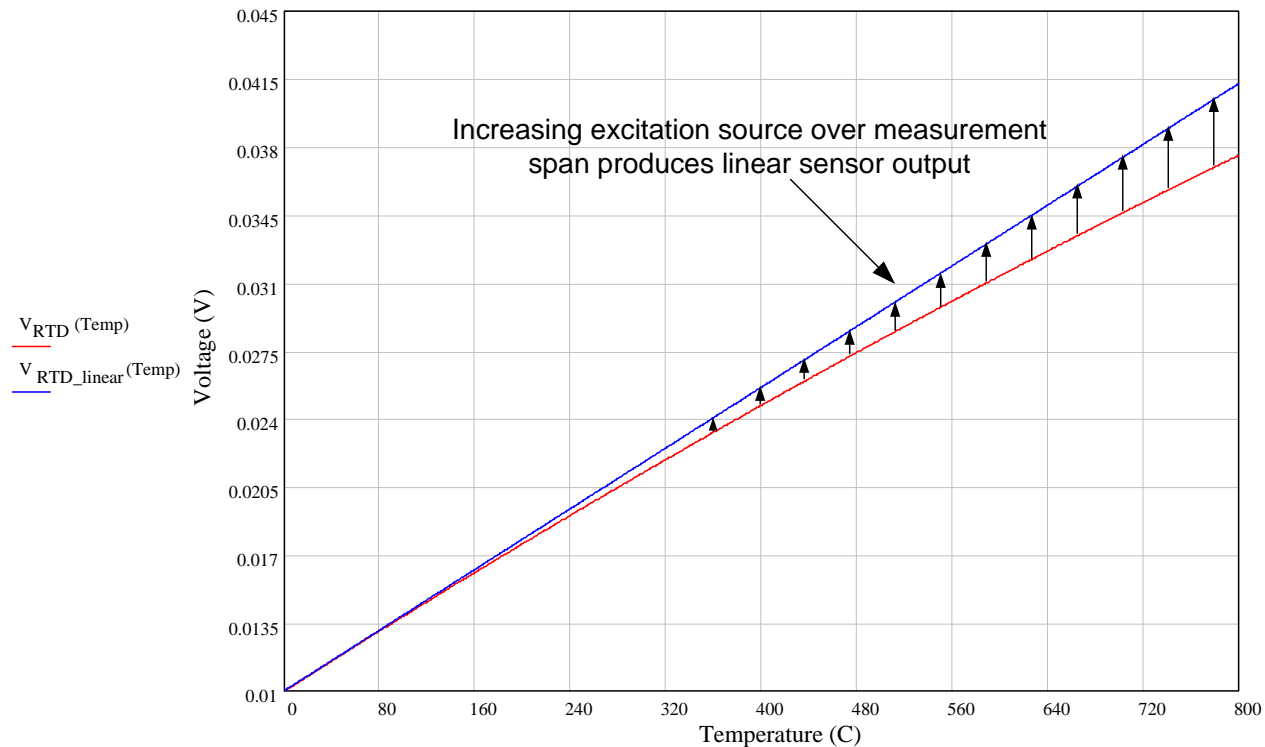RTD Sensor Output vs. Temperature ( $I_{source} = 100\mu A$ )



# Correcting for Non-linearity

$$I_{\text{source}} := 0.0005$$


$$V_{\text{RTD}}(T) := \text{RTD}(T) \cdot I_{\text{source}}$$

$$V_{\text{RTD\_linear}}(T) := \text{RTD}_{\text{linear}}(T) \cdot I_{\text{source}}$$

$$I_{\text{source\_correction}}(T) := I_{\text{source}} + \frac{(V_{\text{RTD\_linear}}(T) - V_{\text{RTD}}(T))}{\text{RTD}(T)}$$

$$V_{\text{RTD\_correction}}(T) := \text{RTD}_{\text{linear}}(T) \cdot I_{\text{source\_correction}}(T)$$

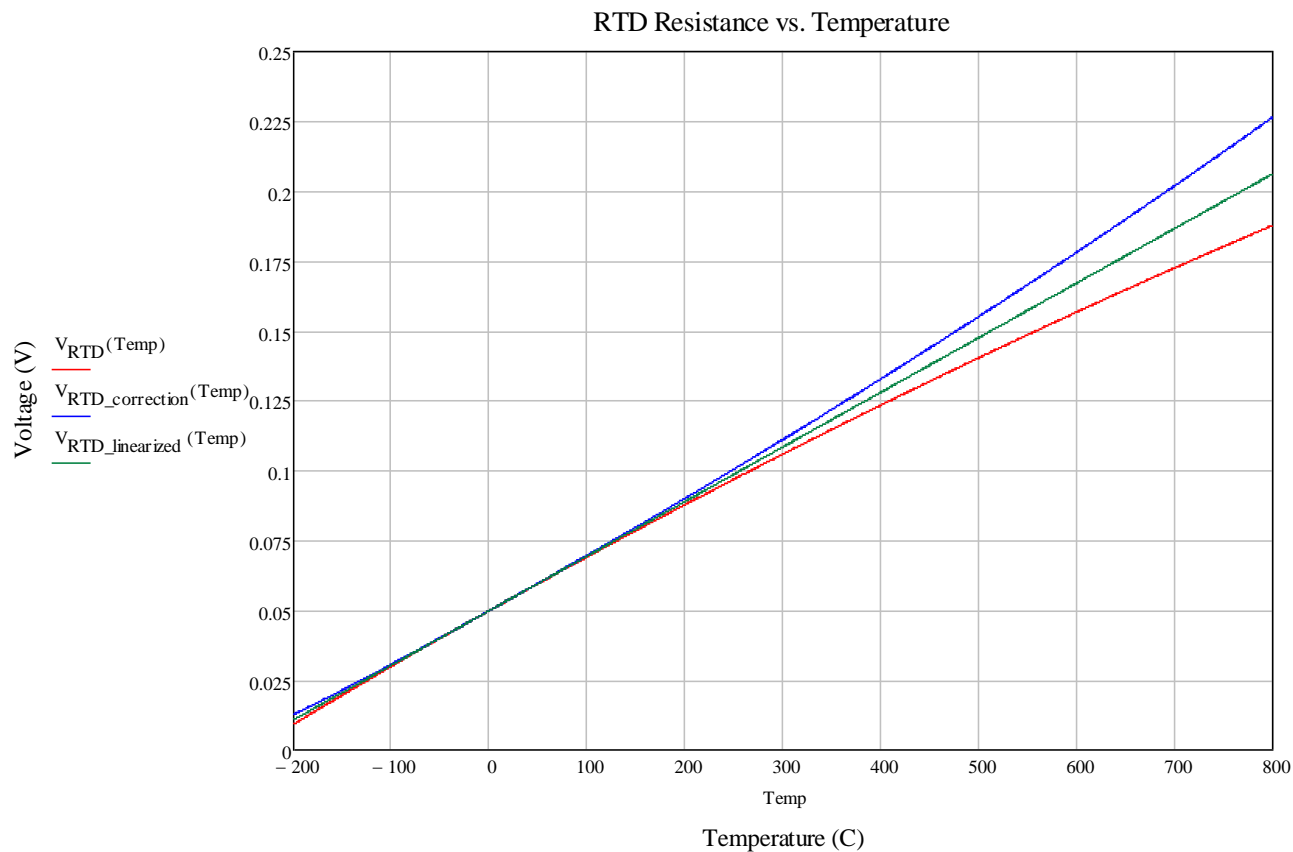
$$V_{\text{RTD\_linearized}}(T) := I_{\text{source\_correction}}(T) \cdot \text{RTD}(T)$$



# Analog Linearization Circuits

# Analog Linearization Circuits

## Two-Wire Single Op-Amp

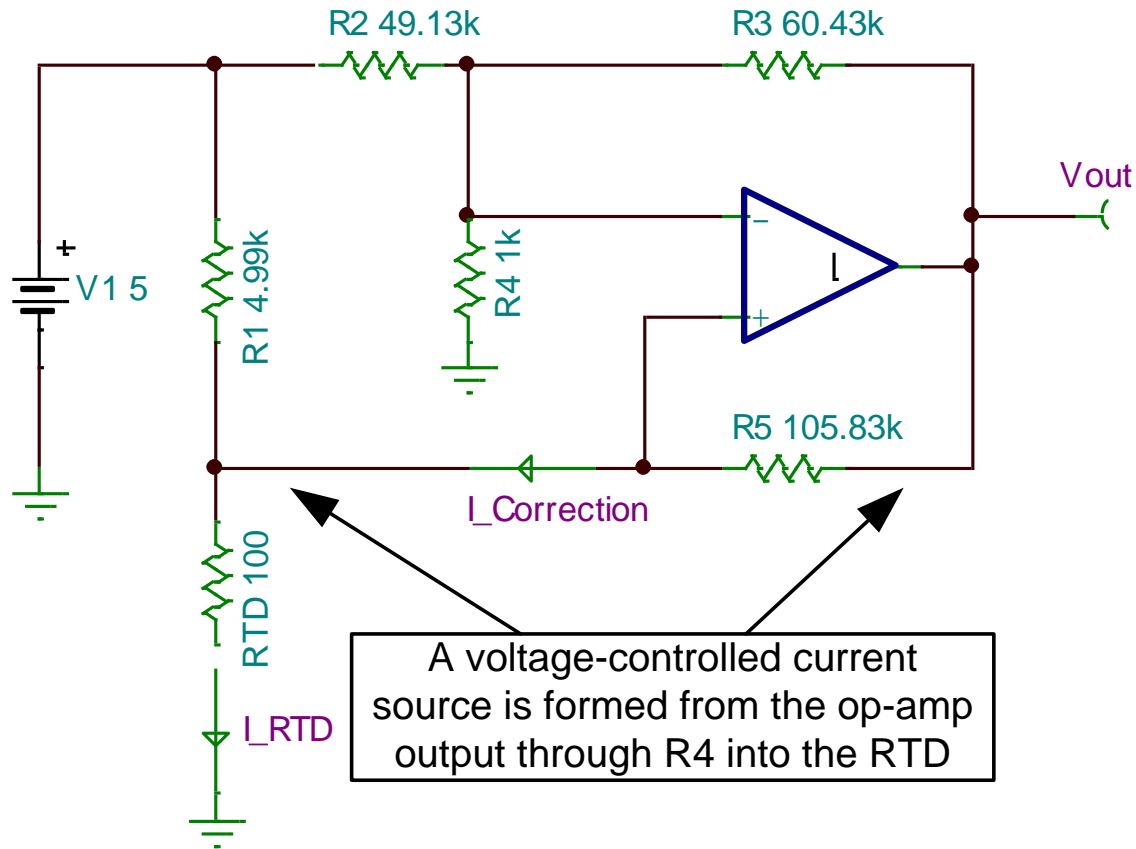

Example  
Amplifiers:

Low-Voltage:

OPA333  
OPA376

High Voltage:

OPA188  
OPA277



This circuit is designed for a 0-5V output for a 0-200C temperature span. Components R2, R3, R4, and R5 are adjusted to change the desired measurement temperature span and output.



# Analog Linearization Circuits
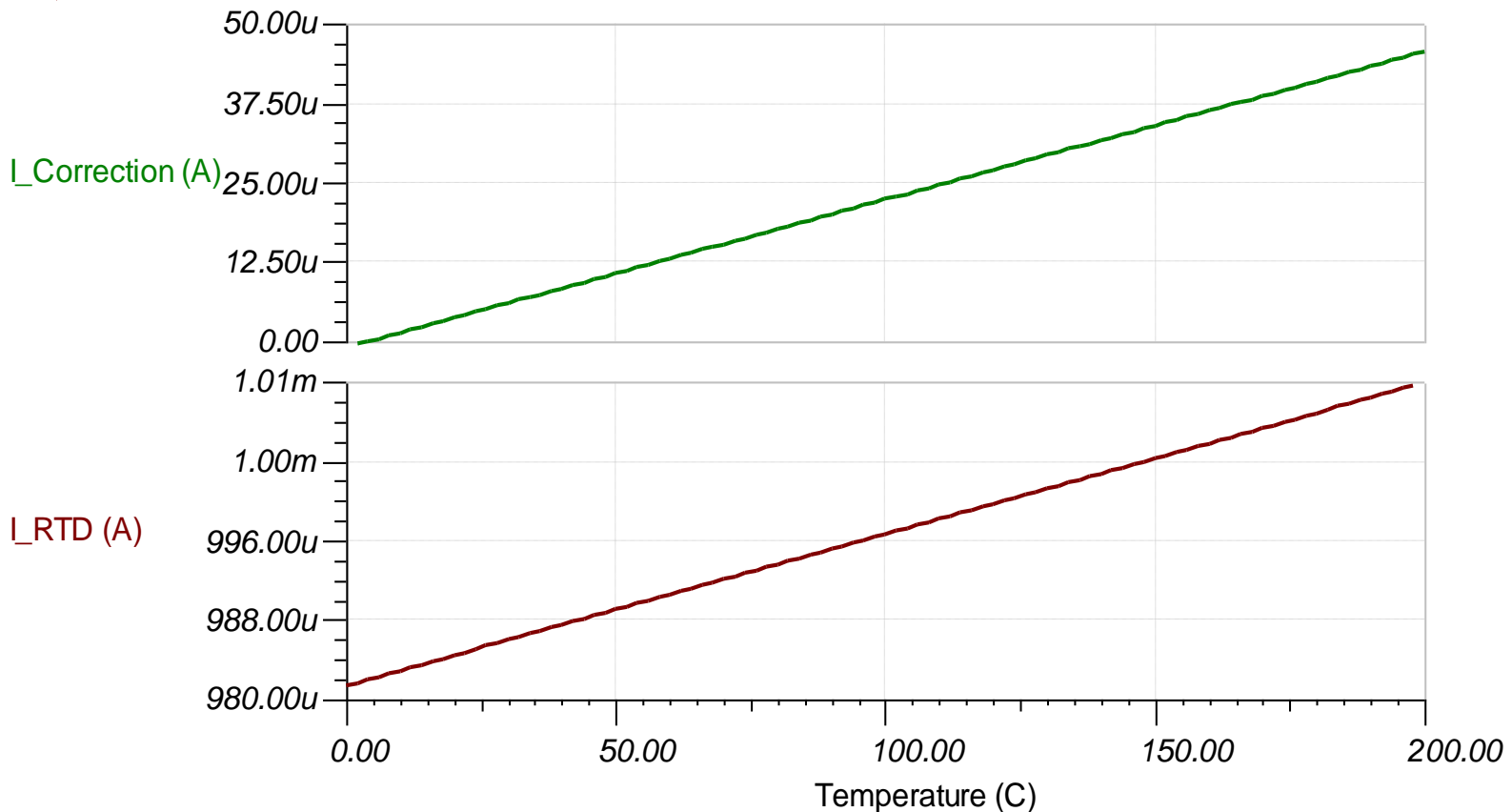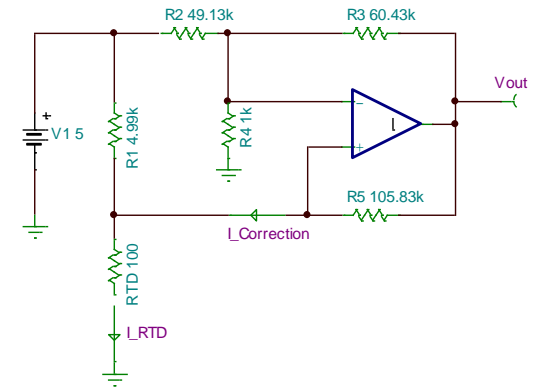
## Two-Wire Single Op-Amp



Non-linear increase in excitation current over temperature span will help correct non-linearity of RTD measurement



# Analog Linearization Circuits

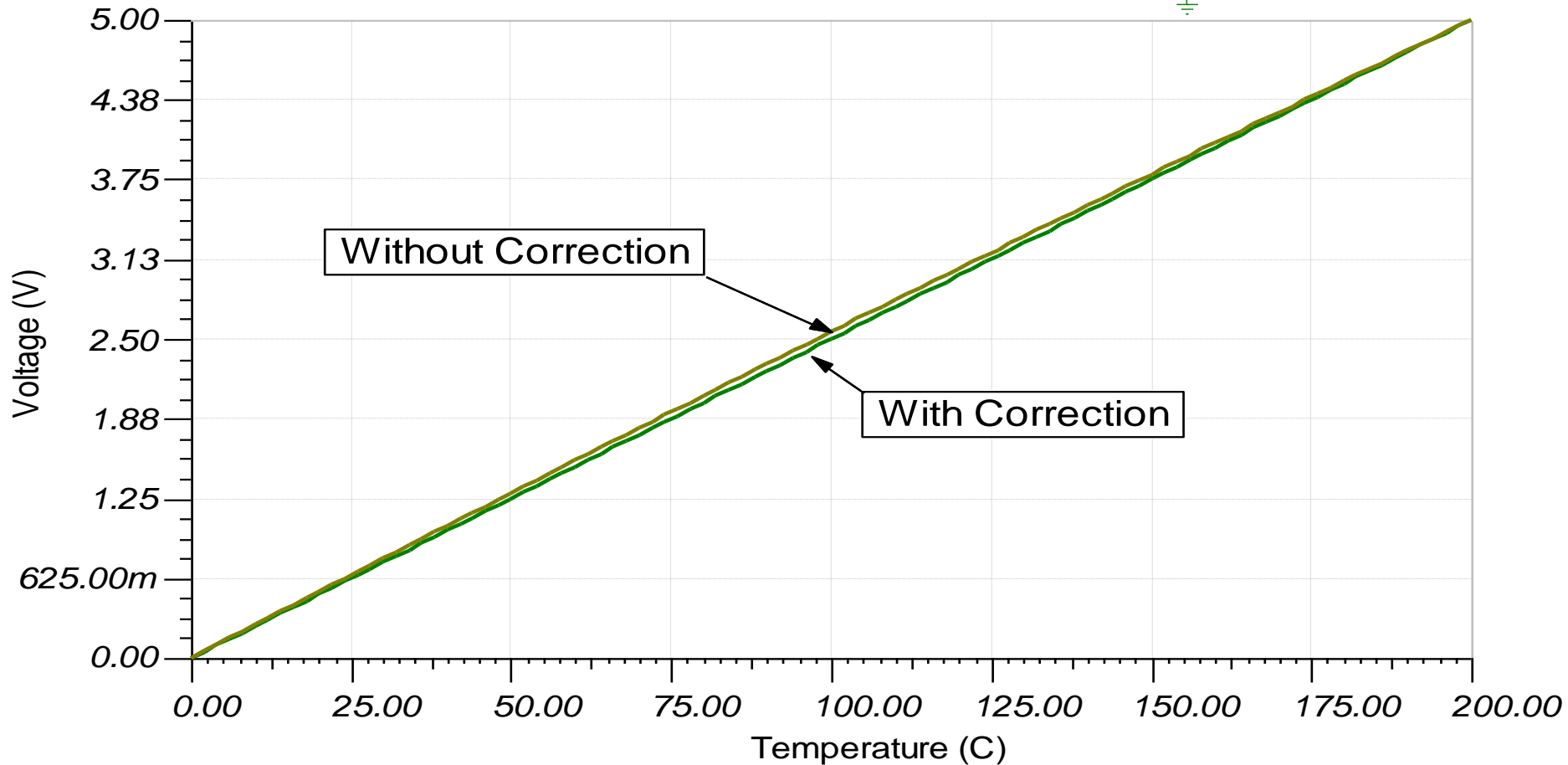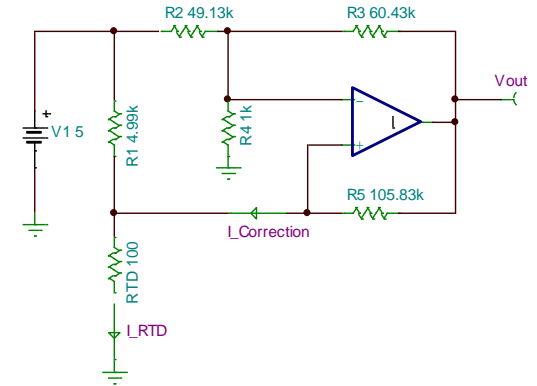
## Two-Wire Single Op-Amp

This type of linearization typically provides a 20X - 40X improvement in linearity



# Analog Linearization Circuits

## Three-Wire Single INA

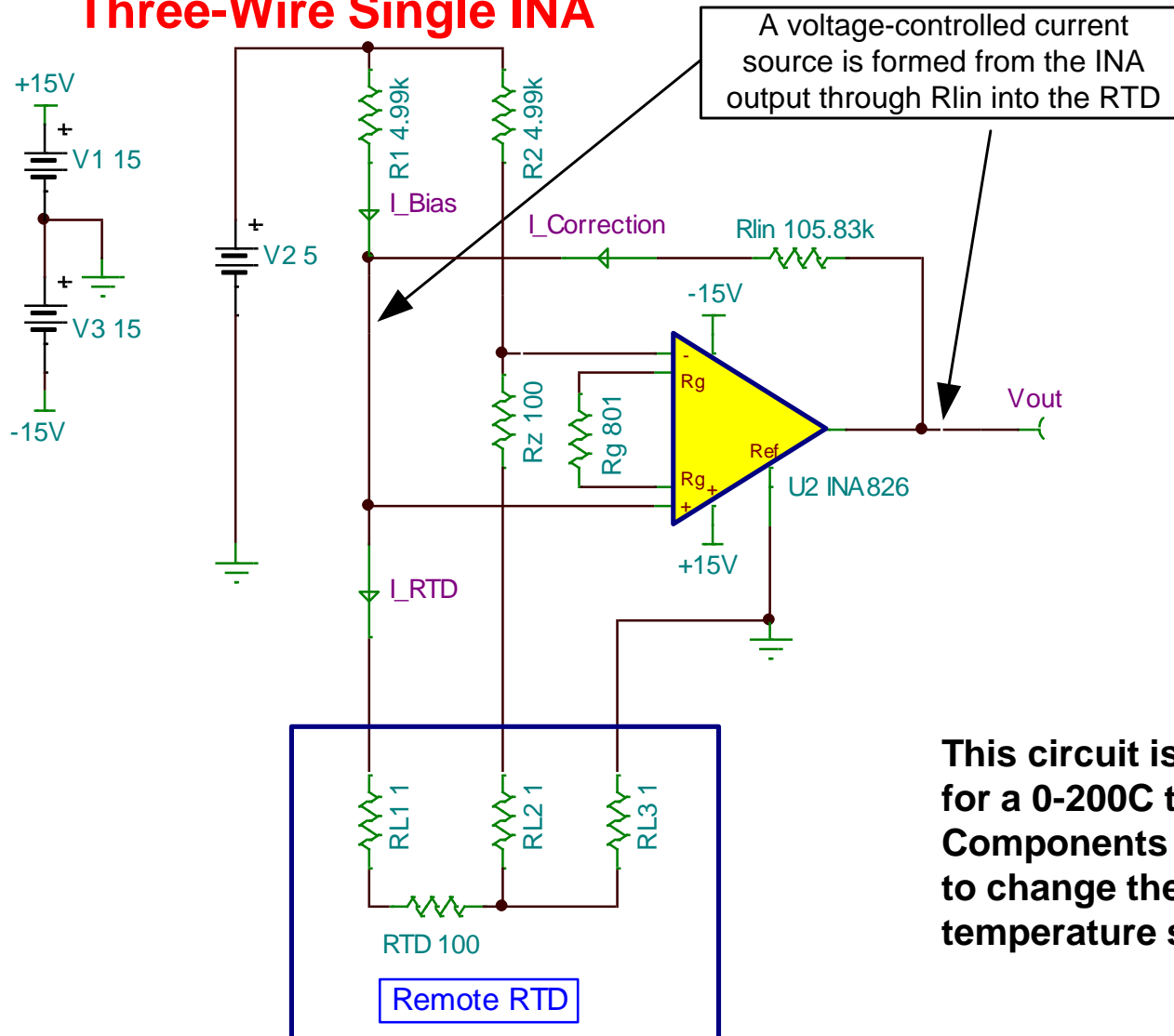

**Example Amplifiers:**

**Low-Voltage:**

INA333

INA114

**High Voltage**

INA826



INA114

This circuit is designed for a 0-5V output for a 0-200C temperature span. Components R<sub>Z</sub>, R<sub>g</sub>, and R<sub>lin</sub> are adjusted to change the desired measurement temperature span and output.

# Analog Linearization Circuits

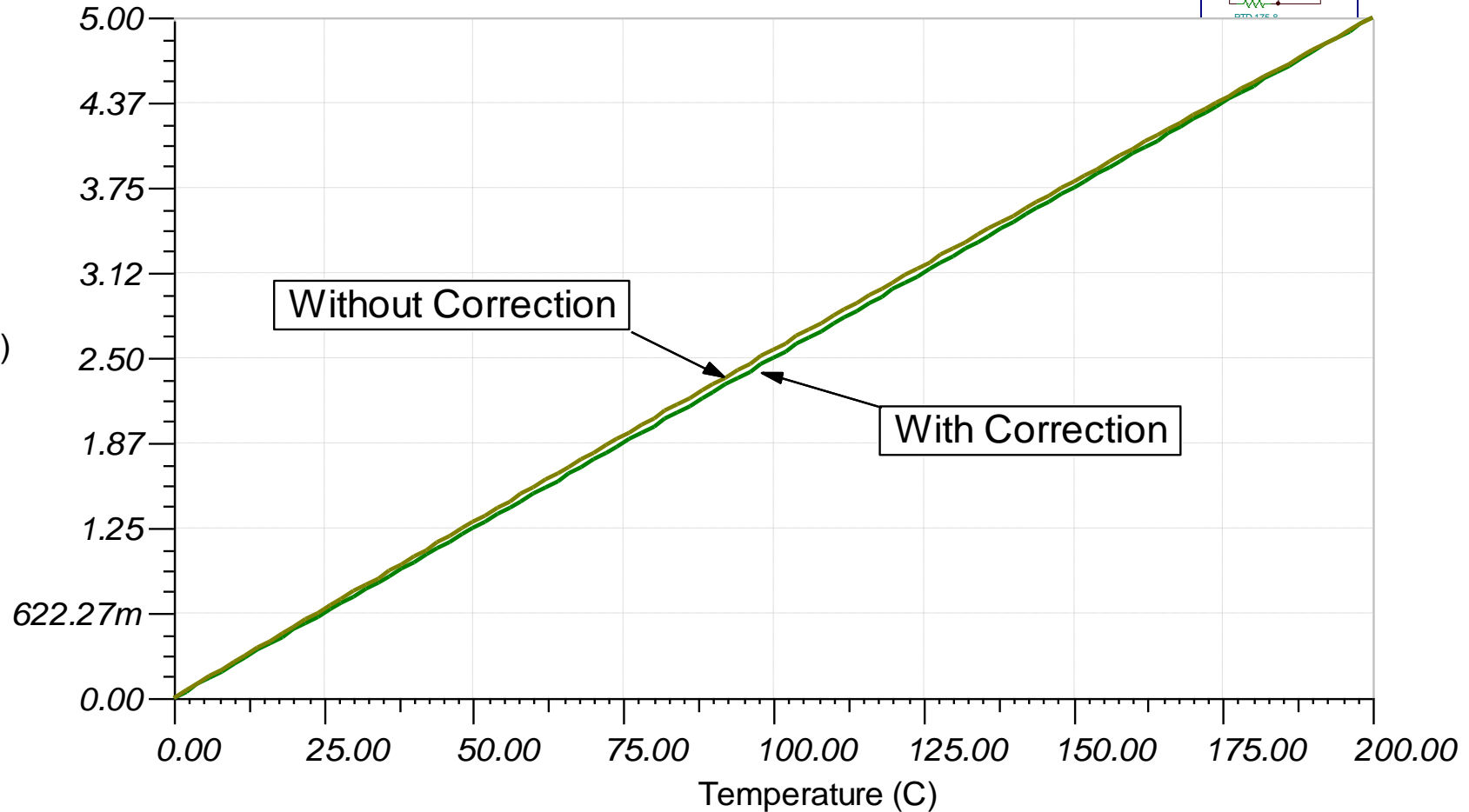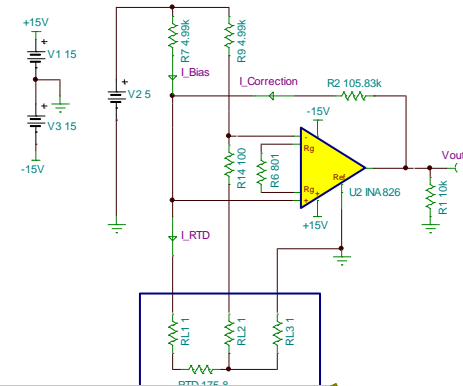
## Three-Wire Single INA

This type of linearization typically provides a 20X - 40X improvement in linearity and some lead resistance cancellation




# Analog Linearization Circuits

## XTR105 4-20mA Current Loop Output

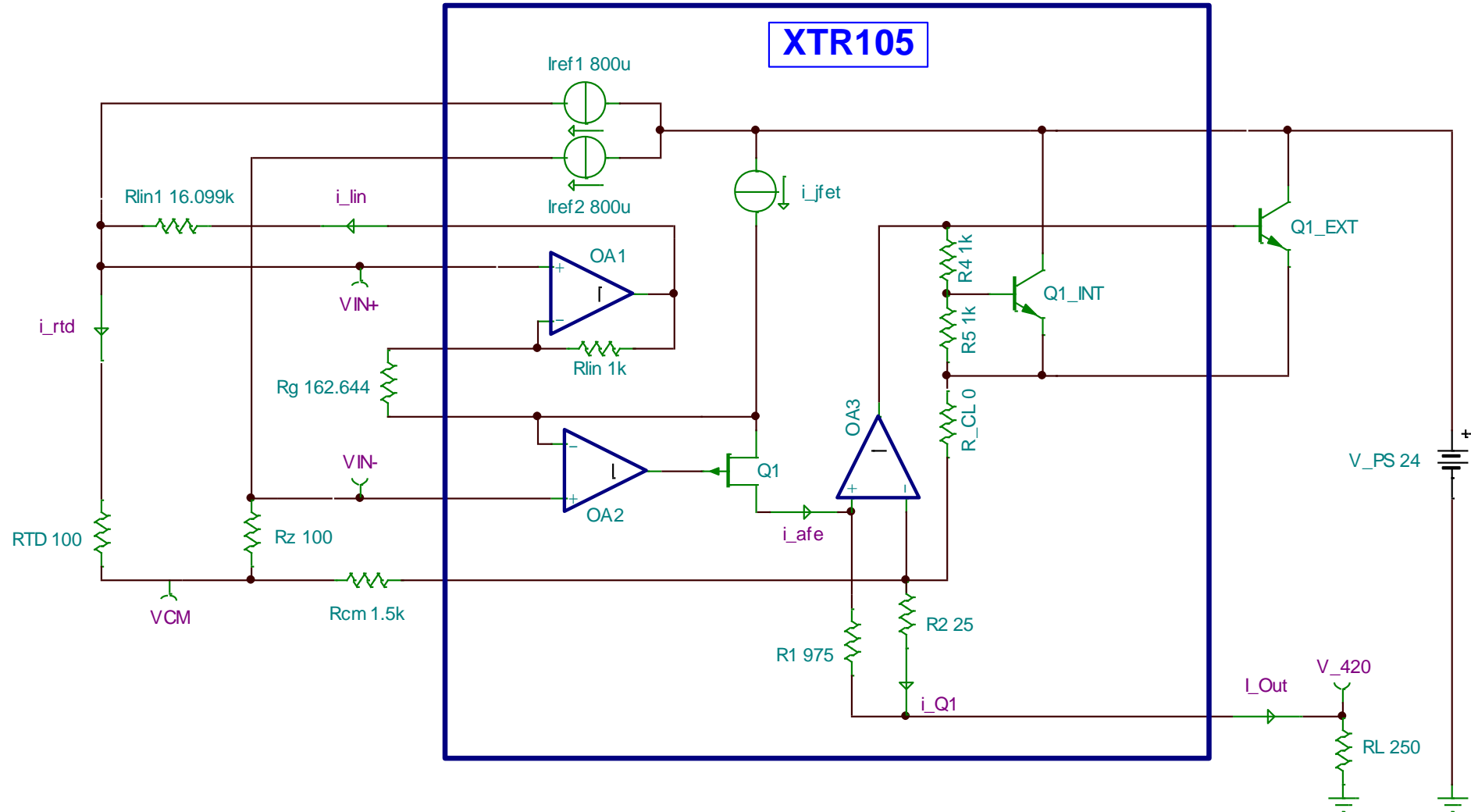



# Analog Linearization Circuits

## XTR105 4-20mA Current Loop Output

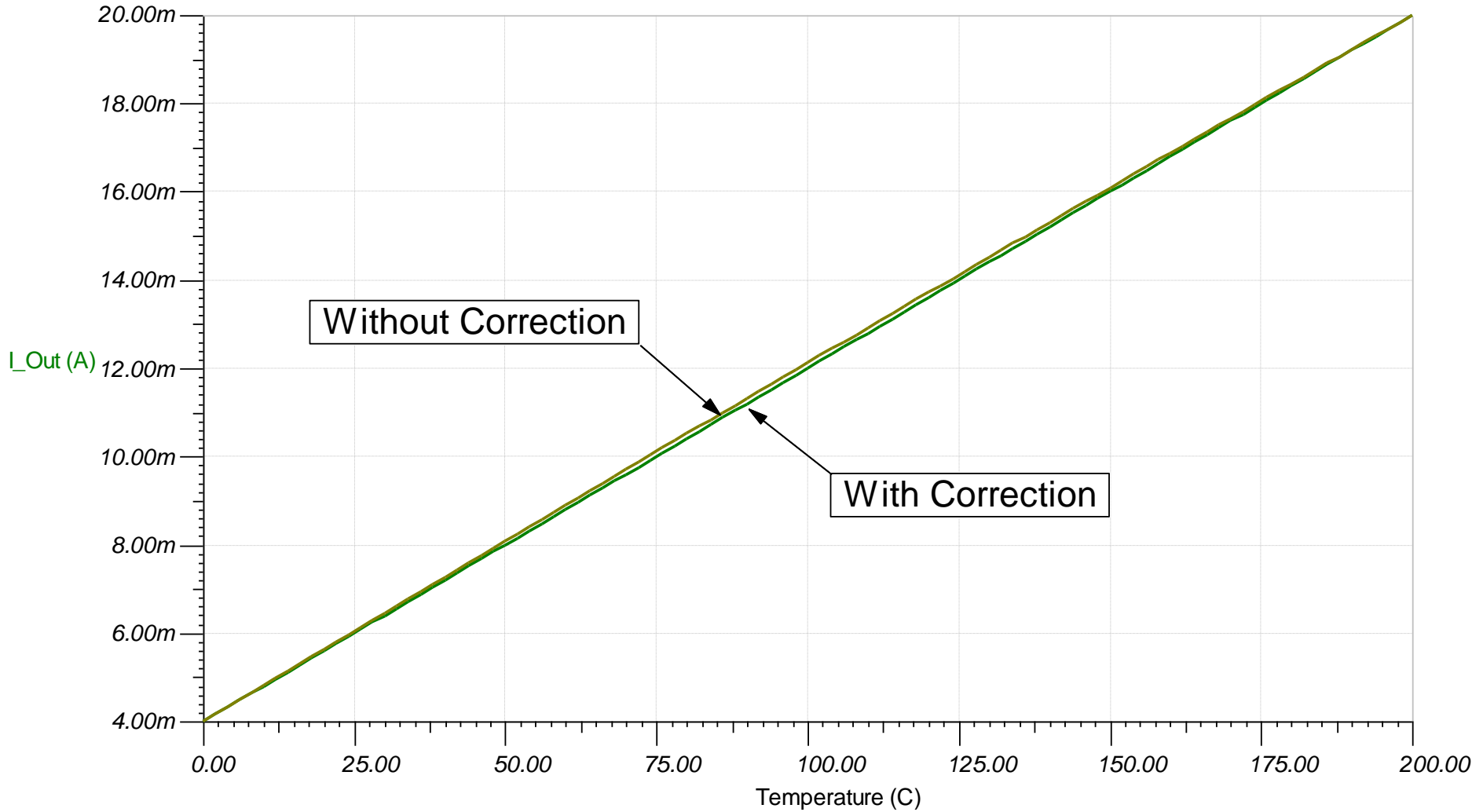

# Analog + Digital Linearization Circuits

## XTR108 4-20mA Current Loop Output

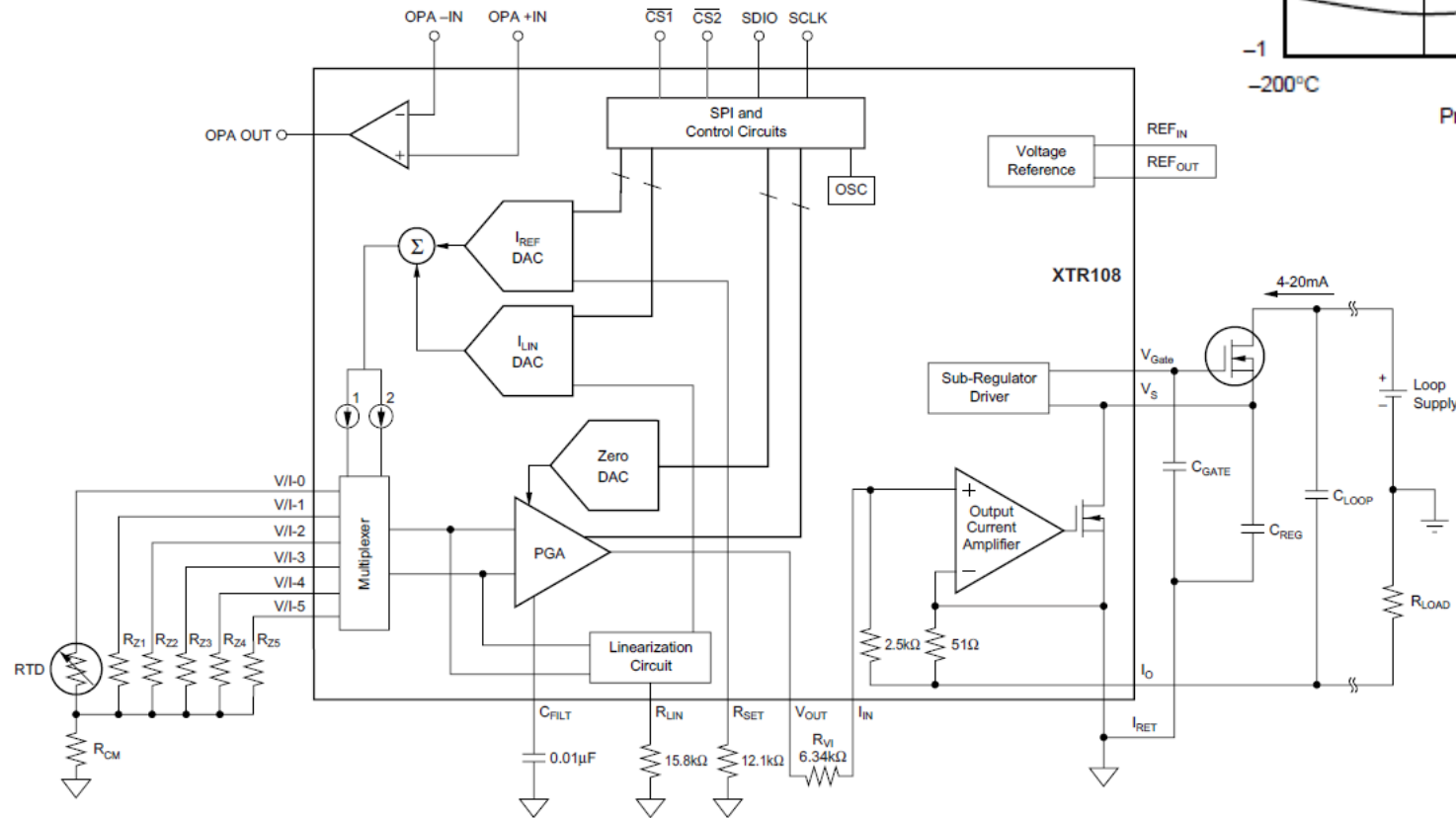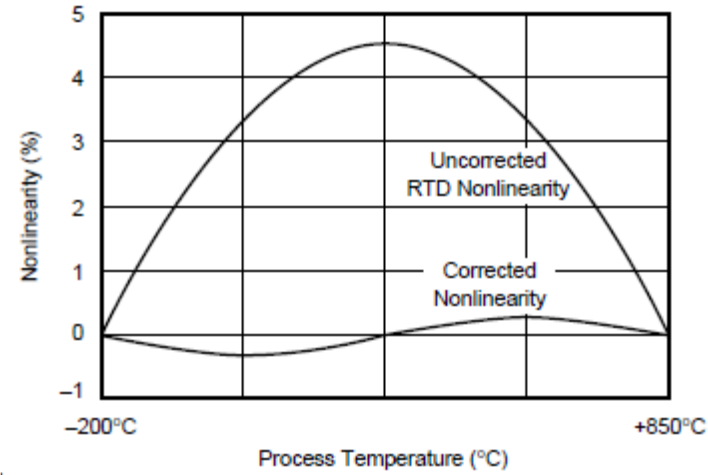


# Digital Acquisition Circuits and Linearization Methods




# Digital Acquisition Circuits
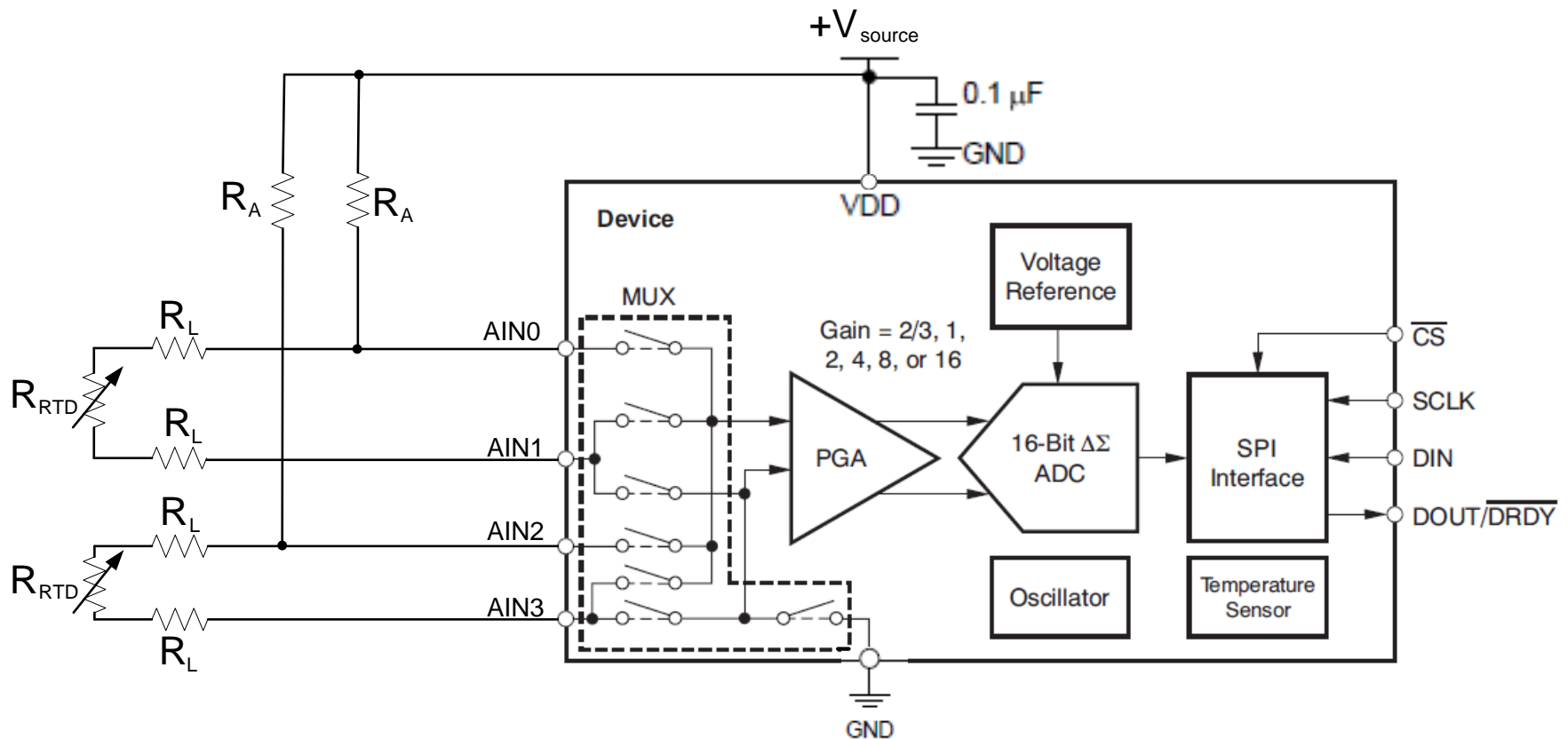
## ADS1118 16-bit Delta-Sigma 2-Wire Measurement with Half-Bridge



# Digital Acquisition Circuits

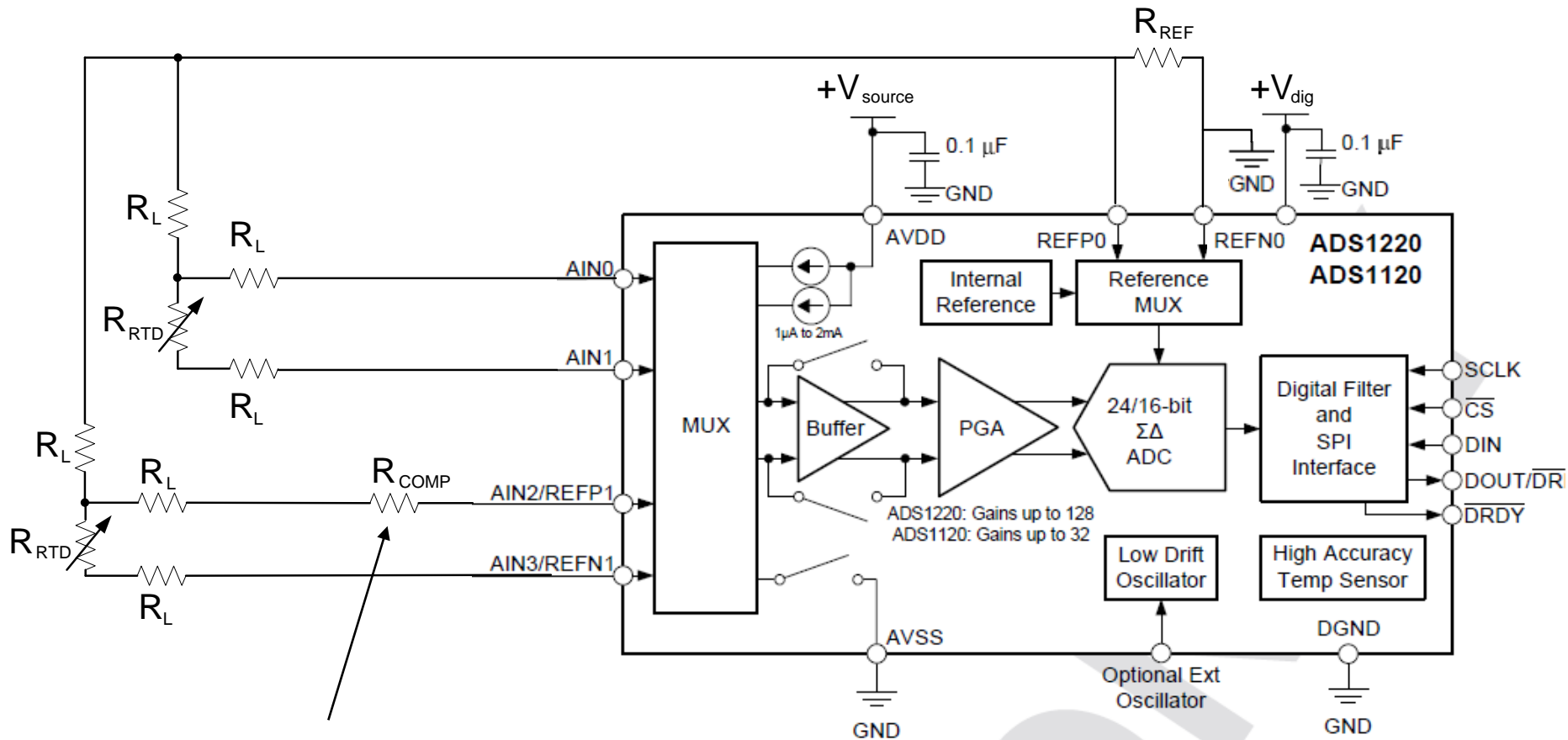
## ADS1220 24-bit Delta-Sigma Two 3-wire RTDs



3-wire + Rcomp shown for AIN2/AIN3


# Digital Acquisition Circuits
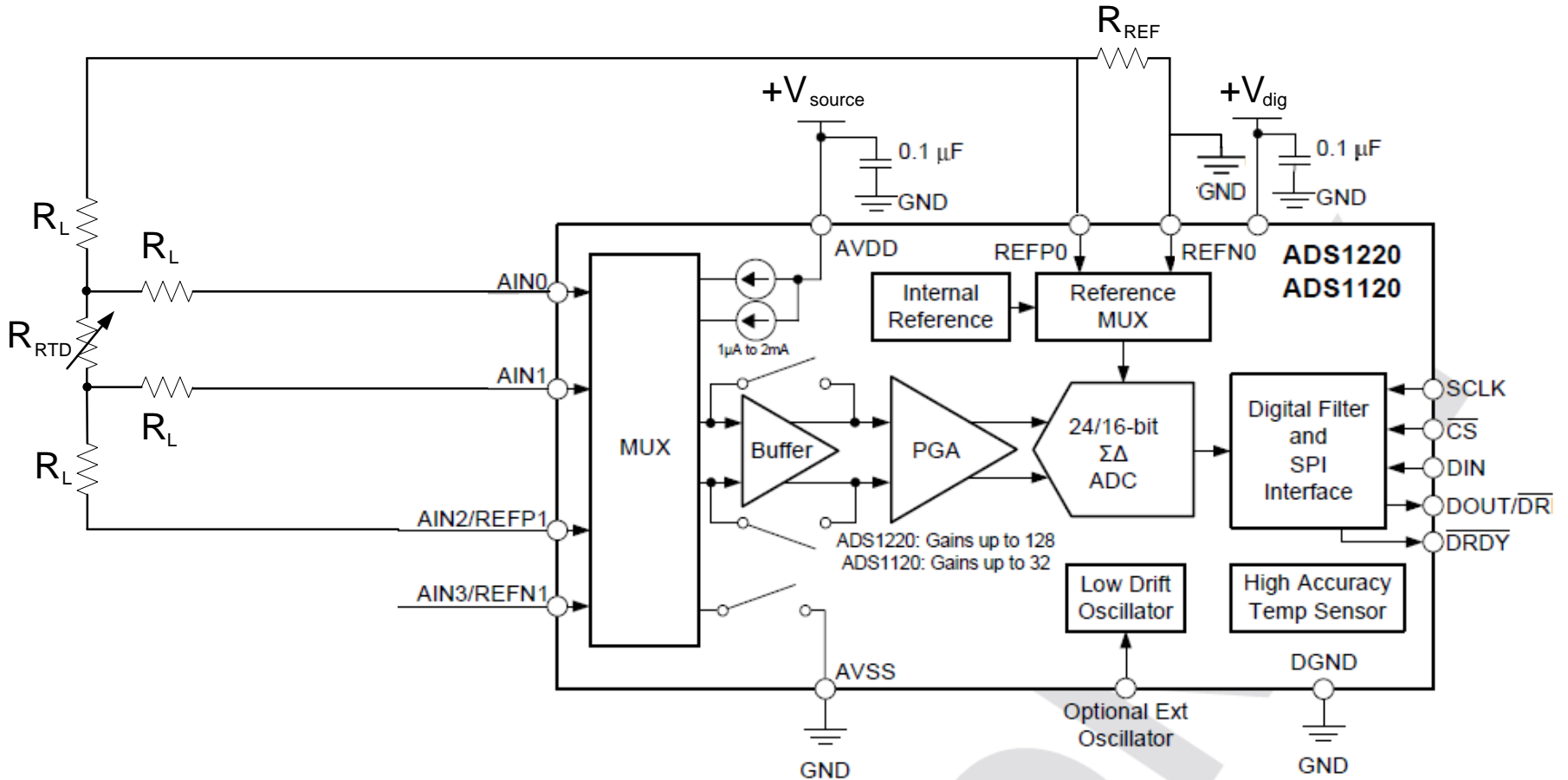
## ADS1220 24-bit Delta-Sigma One 4-Wire RTD



# Digital Acquisition Circuits

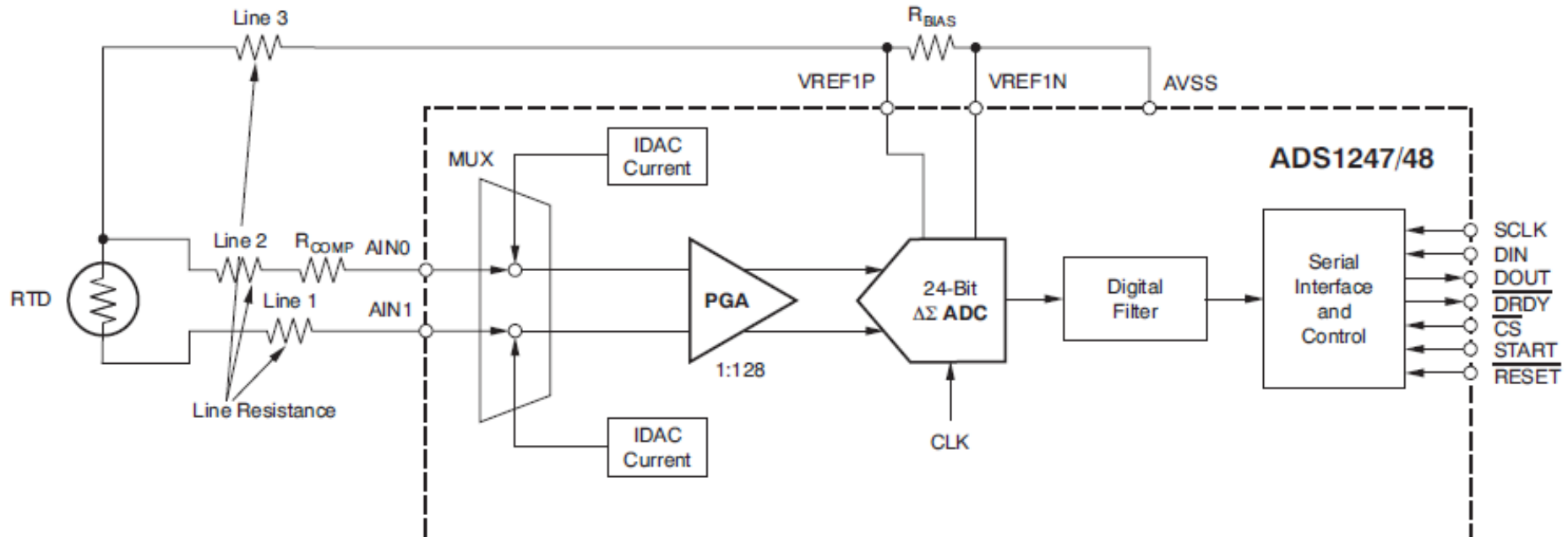
## ADS1247 24-bit Delta-Sigma Three-Wire + Rcomp



Note:  $R_{BIAS}$  and  $R_{COMP}$  should be as close to the ADC as possible.

# Digital Acquisition Circuits


## ADS1247 24-bit Delta-Sigma Four-Wire

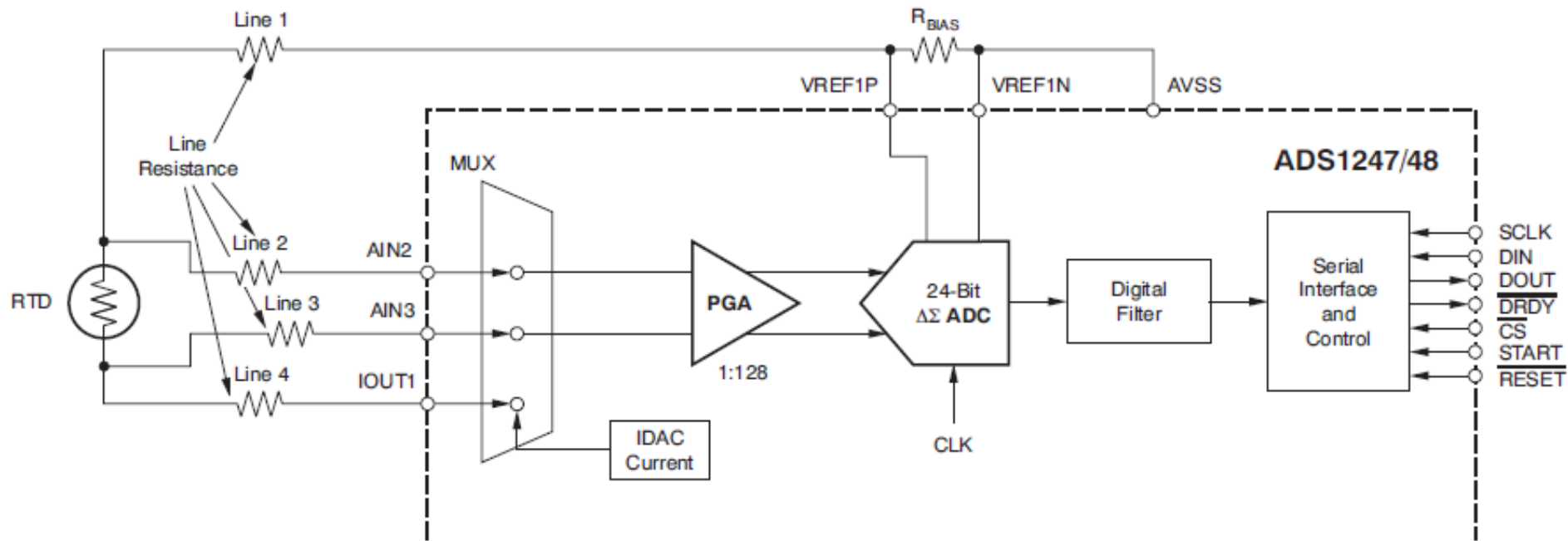

Note:  $R_{BIAS}$  should be as close to the ADC as possible.
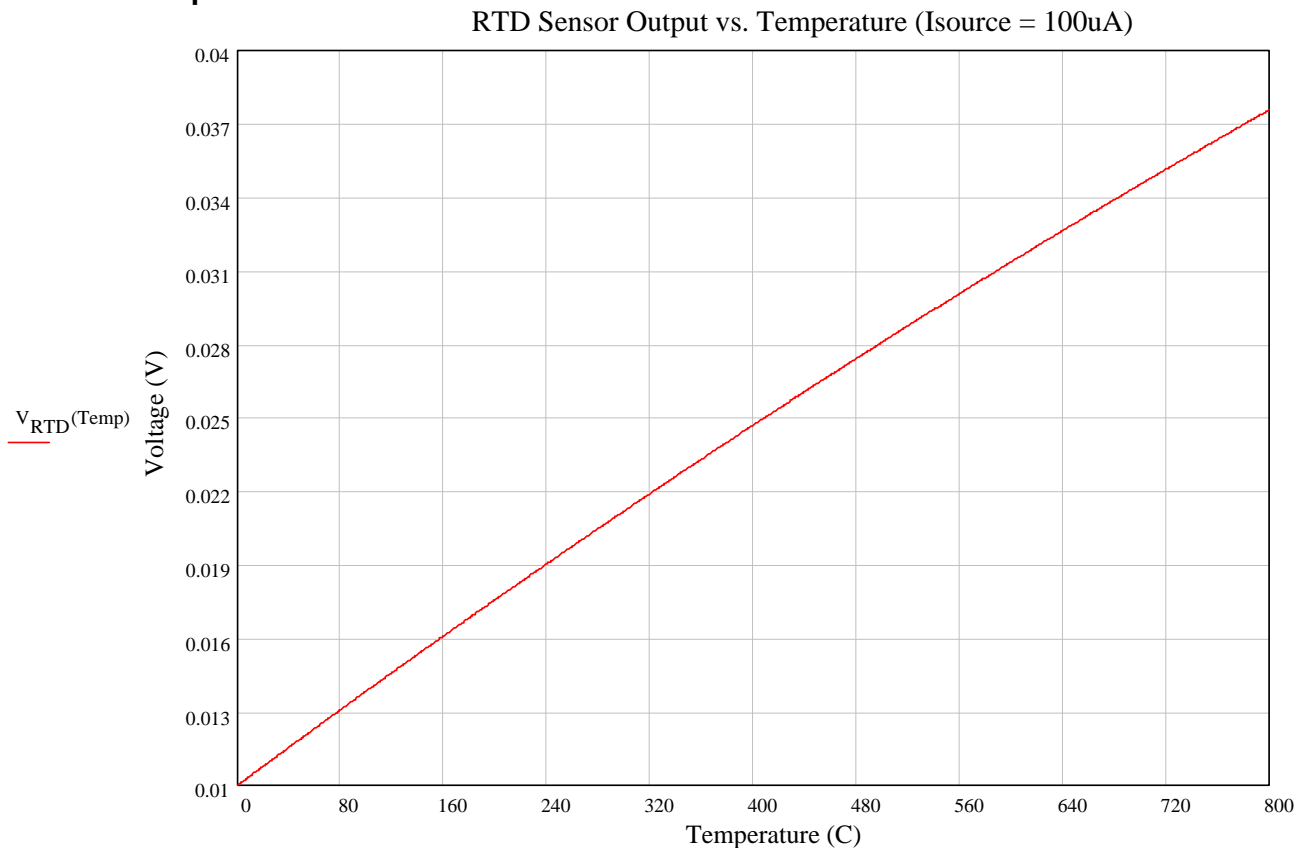
# Digital Linearization Methods

- Three main options
  - Linear-Fit
  - Piece-wise Linear Approximations
  - Direct Computations



# Digital Linearization Methods

## Linear Fit

Pro's:

- Easiest to implement
- Very Fast Processing Time
- Fairly accurate over small temp span


Con's:

Least Accurate

$$T_{\text{Linear}}(t) = A \cdot \text{RTD}(t) + B$$

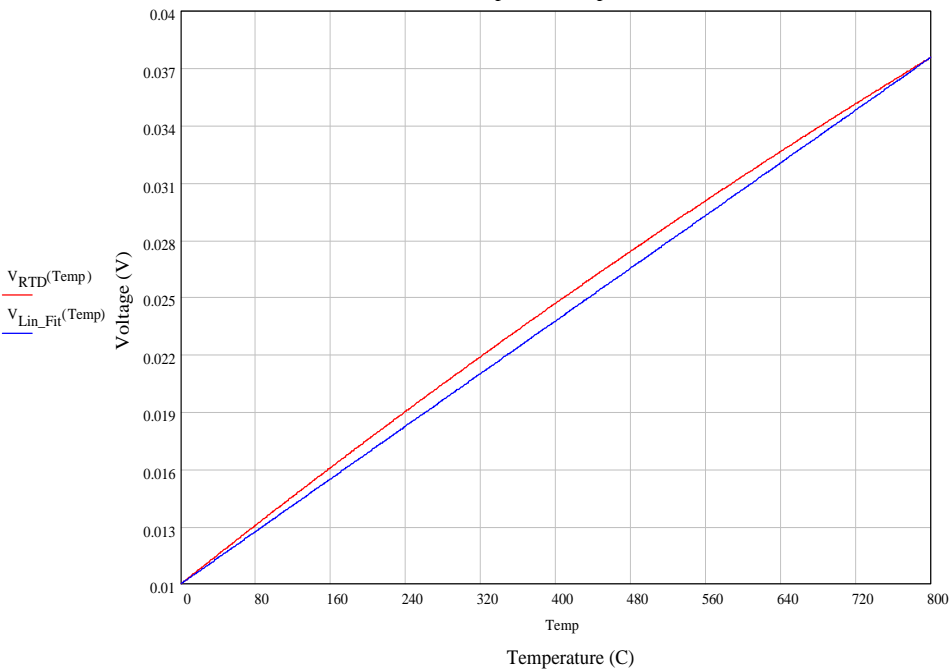
### End-point Fit

RTD Sensor Output vs. Temperature (Isource = 100uA)


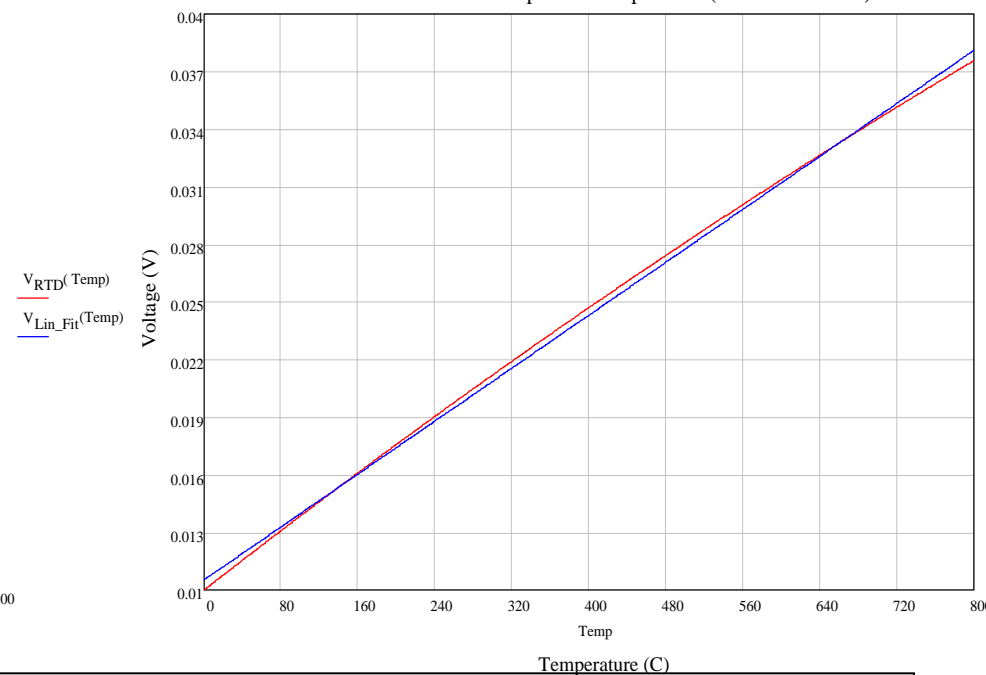
### Best-Fit

RTD Sensor Output vs. Temperature (Isource = 100uA)



# Digital Linearization Methods

## Piece-wise Linear Fit


### Pro's:

- Easy to implement
- Fast Processing Time
- Programmable accuracy
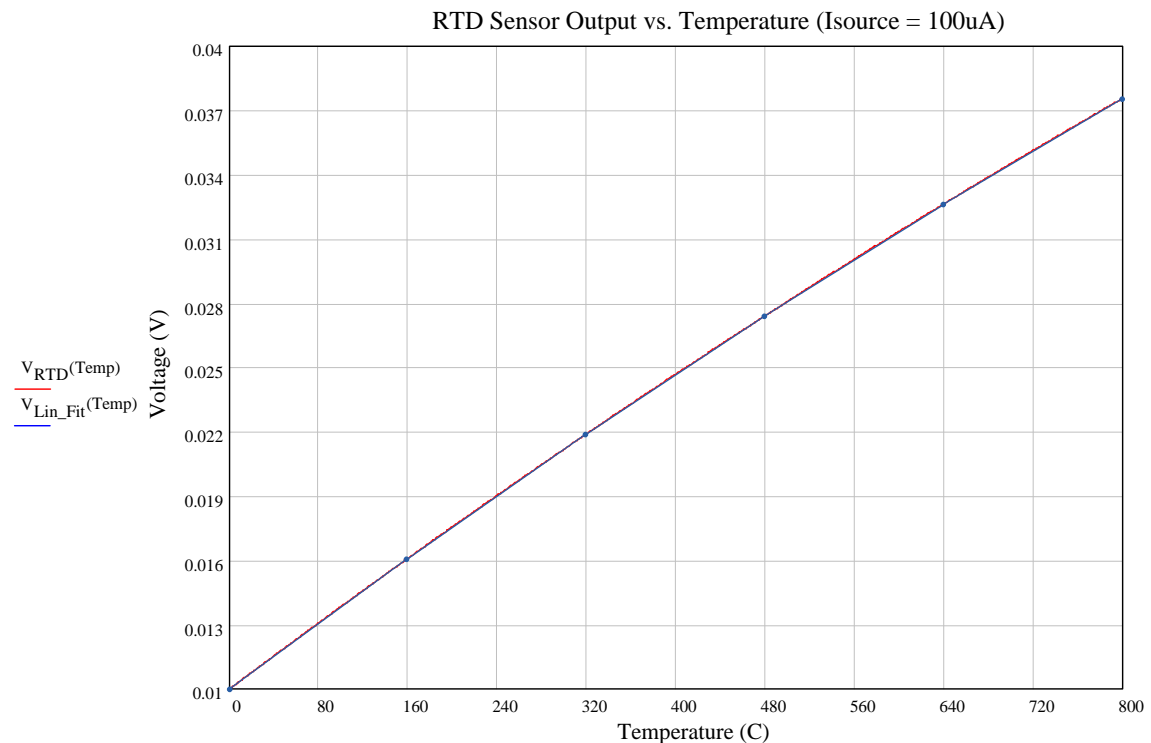
### Con's:

- Code size required for coefficients

$$T_{\text{Peicewise}} = T(n - 1) + (T(n) - T(n - 1)) \left( \frac{RTD - RTD(n - 1)}{RTD(n) - RTD(n - 1)} \right)$$





# Digital Linearization Methods

## Direct Computation

### Pro's:

- Almost Exact Answer, Least Error
- With 32-Bit Math Accuracy to +/-0.0001C

### Con's:

- Processor intensive
- Requires Math Libraries
- Negative Calculation Requires simplification or bi-sectional solving


### Positive Temperature Direct Calculation

$$T_{\text{Direct}}^{+}(t) = \frac{-A + \sqrt{A^2 - 4B \cdot \left(1 - \frac{\text{RTD}(t)}{R_0}\right)}}{2B}$$
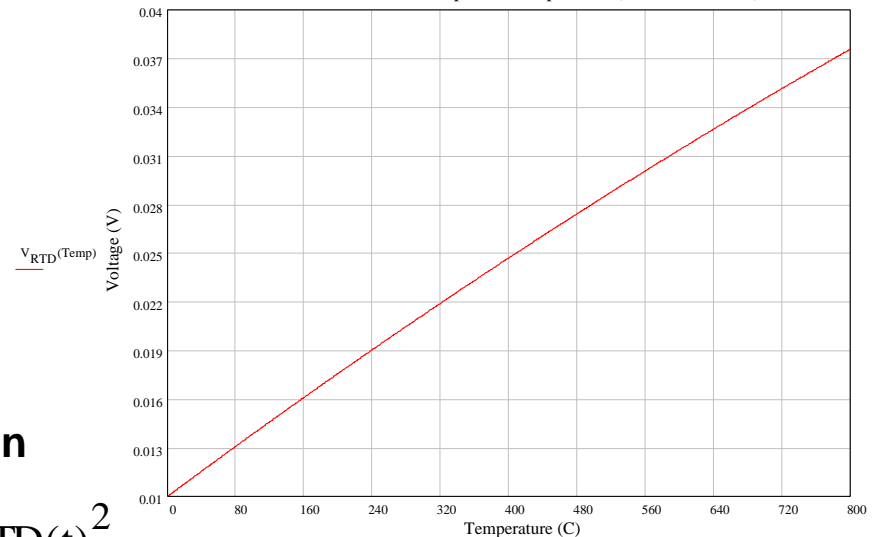
### Negative Temperature Simplified Approximation

$$T_{\text{Direct}}^{-}(t) = -241.96 + 2.2163 \text{RTD}(t) + 2.8541 \cdot 10^{-3} \cdot \text{RTD}(t)^2 - 9.9121 \cdot 10^{-6} \cdot \text{RTD}(t)^3 - 1.7052 \cdot 10^{-8} \cdot \text{RTD}(t)^4$$

RTD Sensor Output vs. Temperature (I<sub>source</sub> = 100uA)



# Digital Linearization Methods

## Direct Computation

### Bi-Section Method for Negative Temperatures

RTDError := 100    Res := 60.256    Tlow := -250    Thigh := 50

```
TBisection := | RTDTemp ← 0                                     = -99.999
                | while ( |RTDError| > 0.0001)
                |   | Tmid ←  $\frac{(Tlow + Thigh)}{2}$ 
                |   | Rcal ←  $100 \left[ 1 + A \cdot Tmid + B Tmid^2 + (Tmid - 100) \cdot C \cdot Tmid^3 \right]$  if Tmid < 0
                |   | Rcal ←  $100 \left( 1 + A \cdot Tmid + B \cdot Tmid^2 \right)$  if Tmid > 0
                |   | Rcal ← 0 if Rcal < 0
                |   | RTDError ← Res - Rcal
                |   | Tlow ← Tmid if RTDError > 0
                |   | Thigh ← Tmid if RTDError < 0
                |   | RTDTemp ← Tmid
                |   | return RTDTemp
```

T<sub>Bisection</sub> = -99.999

# Questions/Comments?

## Thank you!!

**Special Thanks to:**

**Art Kay**

**Bruce Trump**

**PA Apps Team**

**Mike Beckman**

**Omega Sensors**

**RDF Corp**

## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.