

Getting Started with Current Sense Amplifiers Video Series

Session 4: How To Choose An Appropriate Shunt Resistor


How To Choose An Appropriate Shunt Resistor

Overview

- Definition of Shunt Resistor
- Primary factors that influence the choice of the shunt resistor
- Calculating a maximum value of the shunt resistor for an application
- Shunt resistor tolerance error

How To Choose An Appropriate Shunt Resistor

What is a Shunt Resistor?

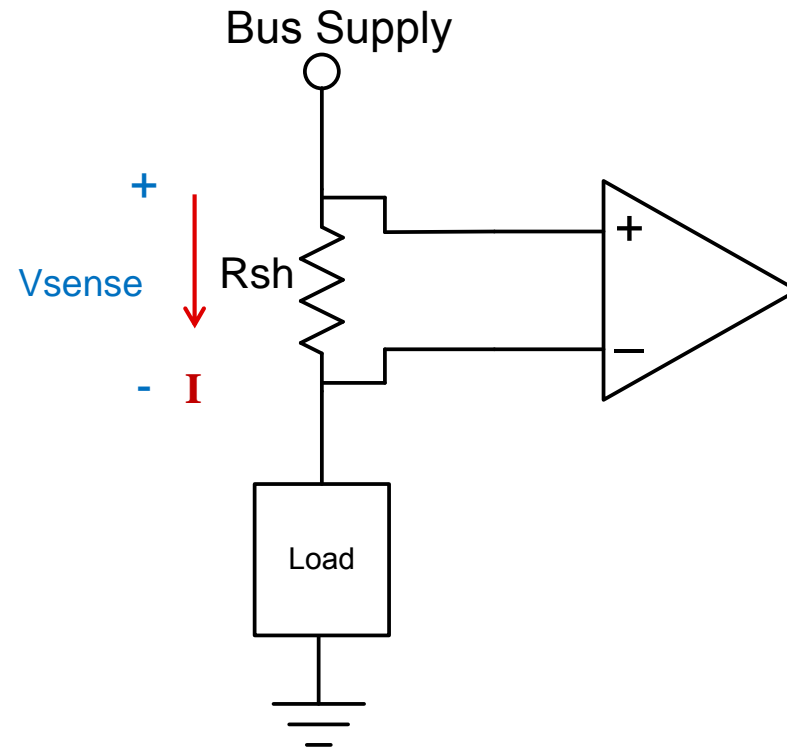

How To Choose An Appropriate Shunt Resistor


Primary Factors for choosing a Shunt

1. Minimum Current Accuracy
2. Maximum Current Power dissipation (Size and Cost)




How To Choose An Appropriate Shunt Resistor

Minimum Current Accuracy

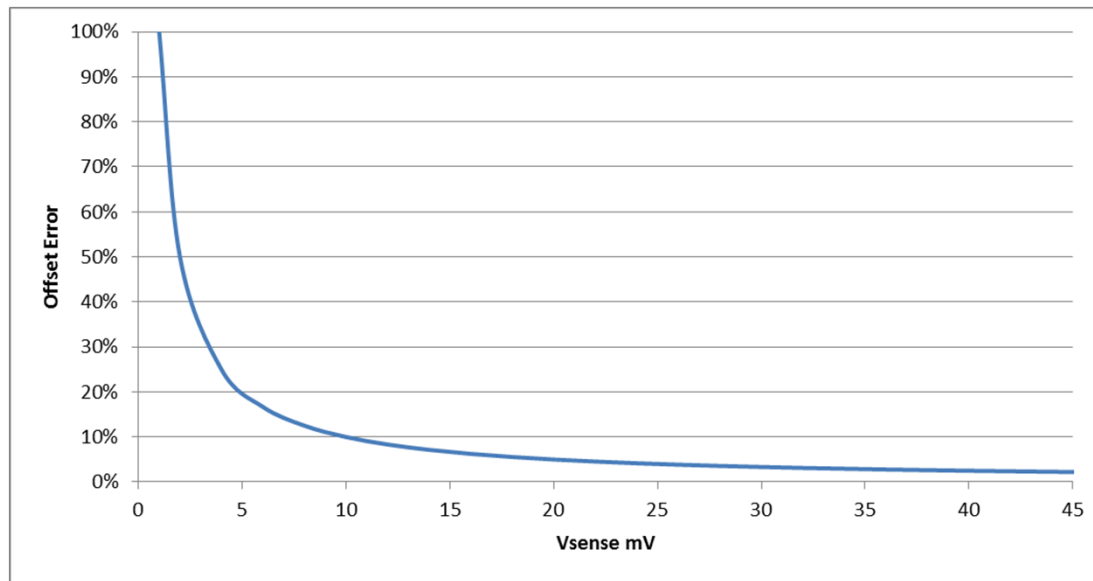


$$\text{Offset Error (in percent)} = \left(\frac{V_{os}}{V_{sense}} \right) * 100$$

$$V_{sense} = R_{sh} * I_{load}$$

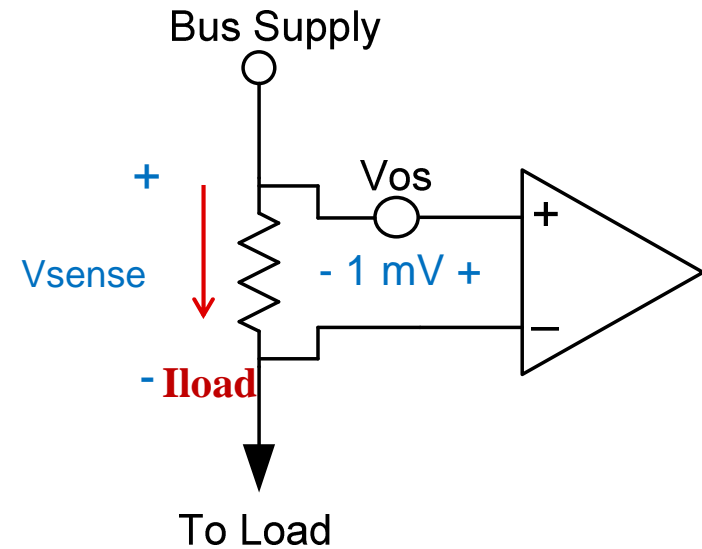


How To Choose An Appropriate Shunt Resistor

Minimum Current Accuracy

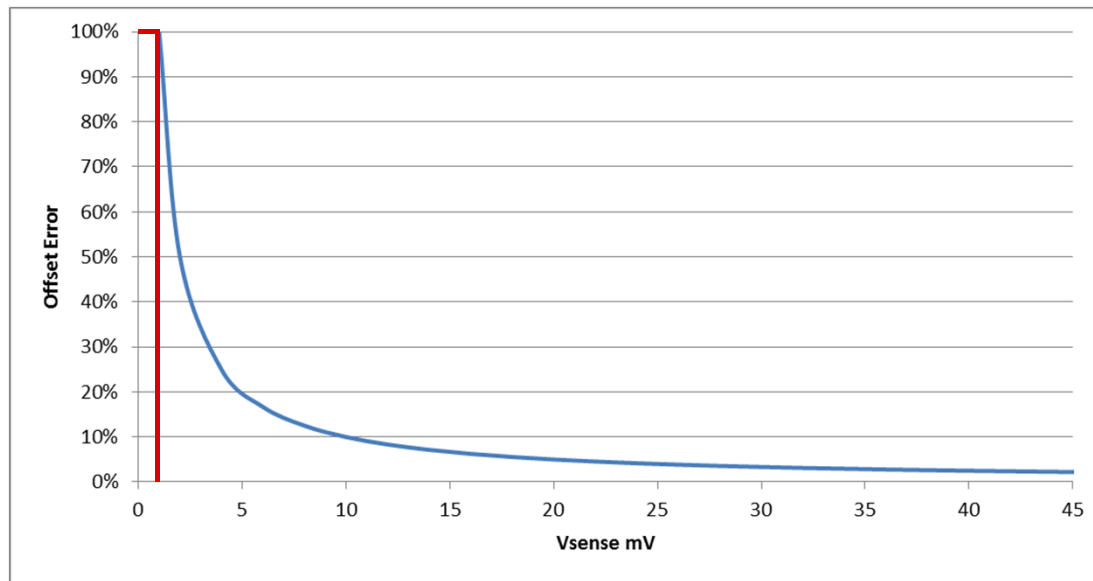

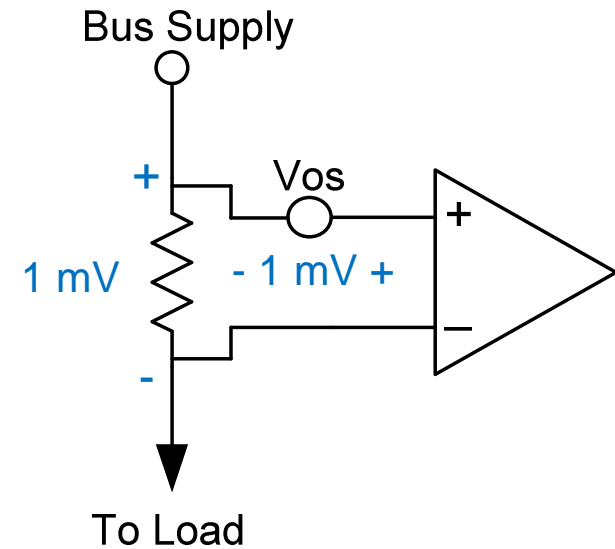
$$\text{Offset Error} = \frac{1 \text{ mV}}{1 \text{ mV}} * 100 = 100 \%$$




How To Choose An Appropriate Shunt Resistor

Minimum Current Accuracy

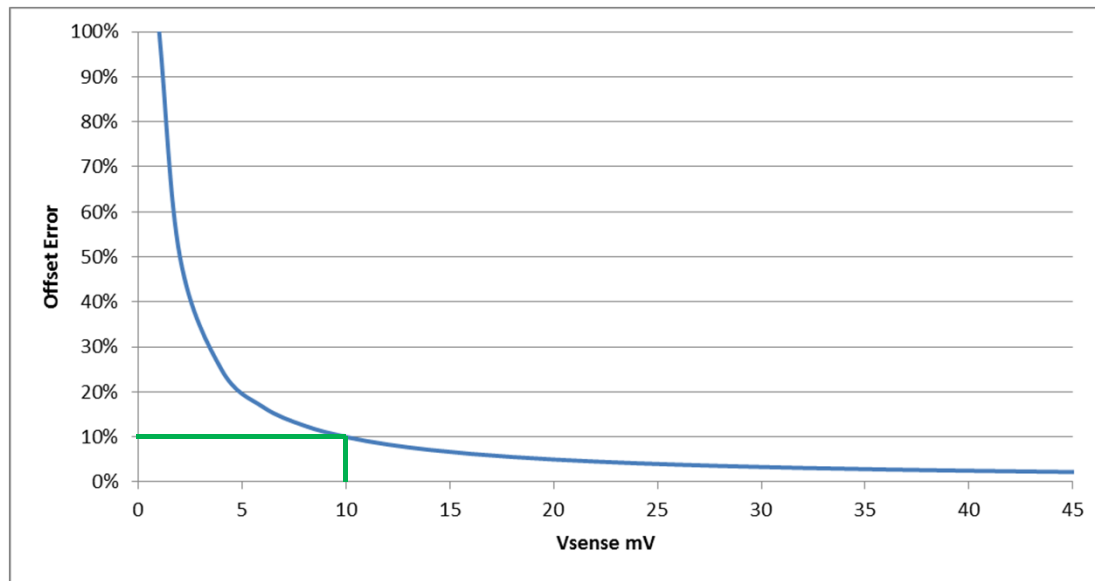

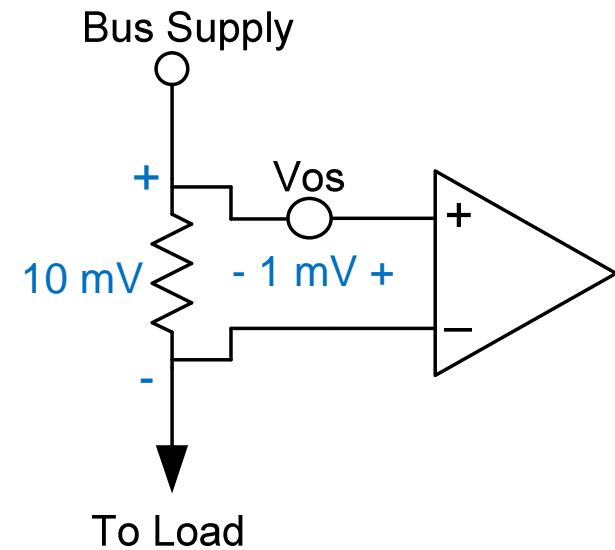
$$\text{Offset Error} = \frac{1 \text{ mV}}{10 \text{ mV}} * 100 = 10 \%$$




How To Choose An Appropriate Shunt Resistor

Maximum Current Power Dissipation


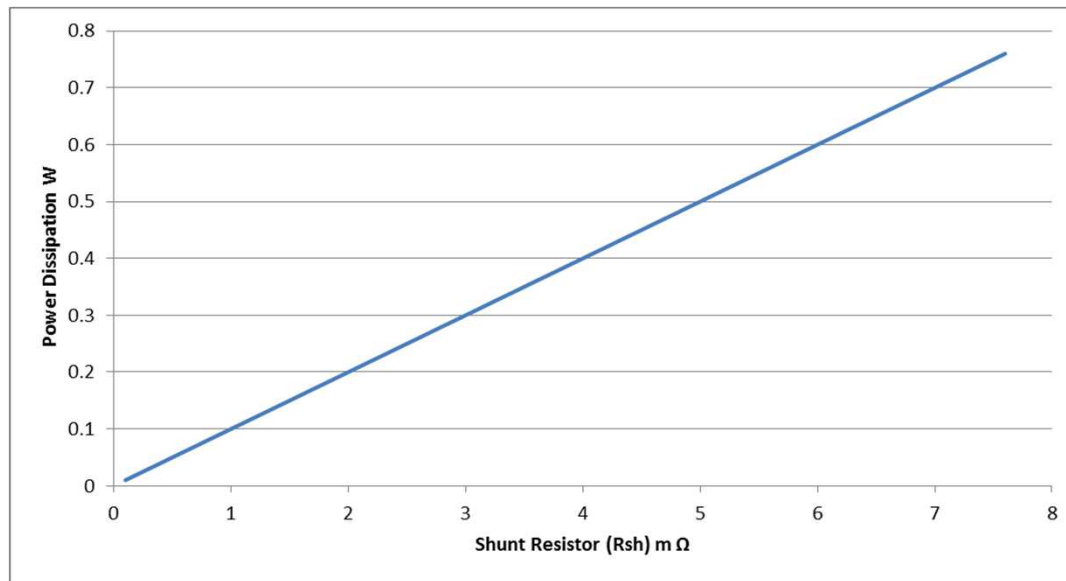


$$Power\ Dissipation = Rsh * Iload^2$$

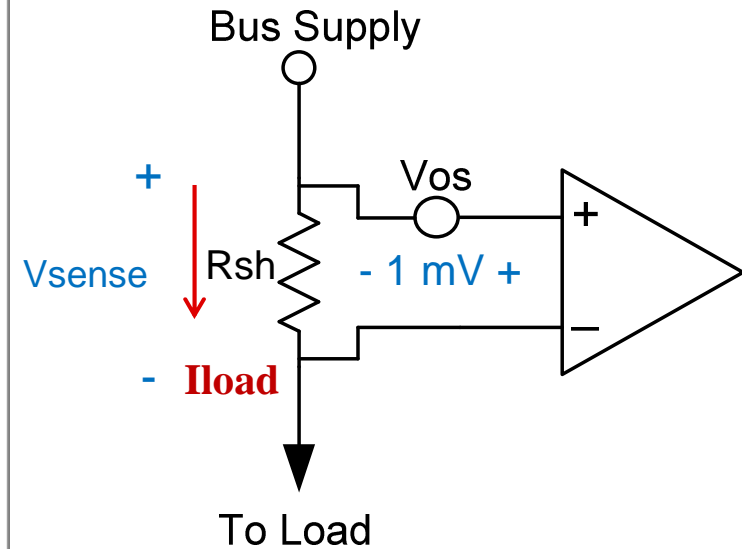

How To Choose An Appropriate Shunt Resistor

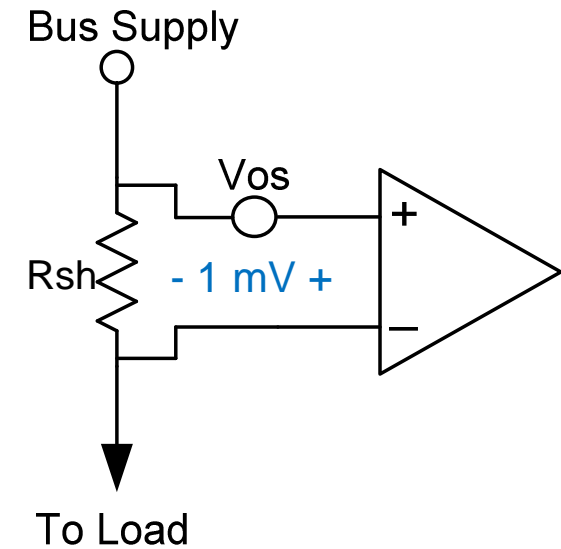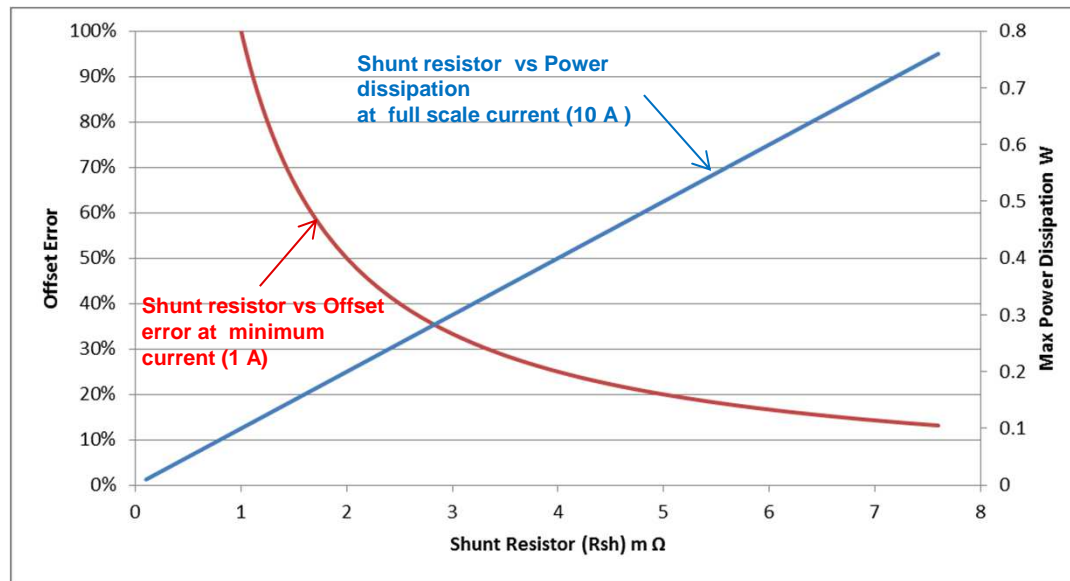Power Dissipation vs Minimum Current Accuracy tradeoff





$$\text{Offset Error (in percent)} = \frac{V_{os}}{R_{sh} * I_{load_min}} * 100$$

$$\text{Max Power Dissipation (W)} = R_{sh} * I_{load_max}^2$$

Iload_min = 1 A; Iload_max = 10 A

How To Choose An Appropriate Shunt Resistor

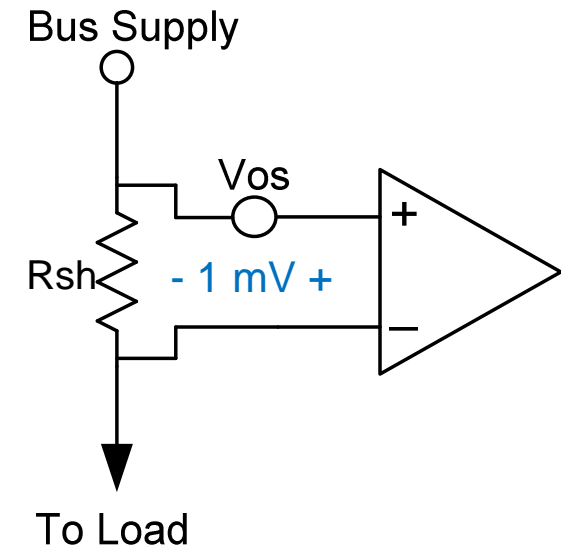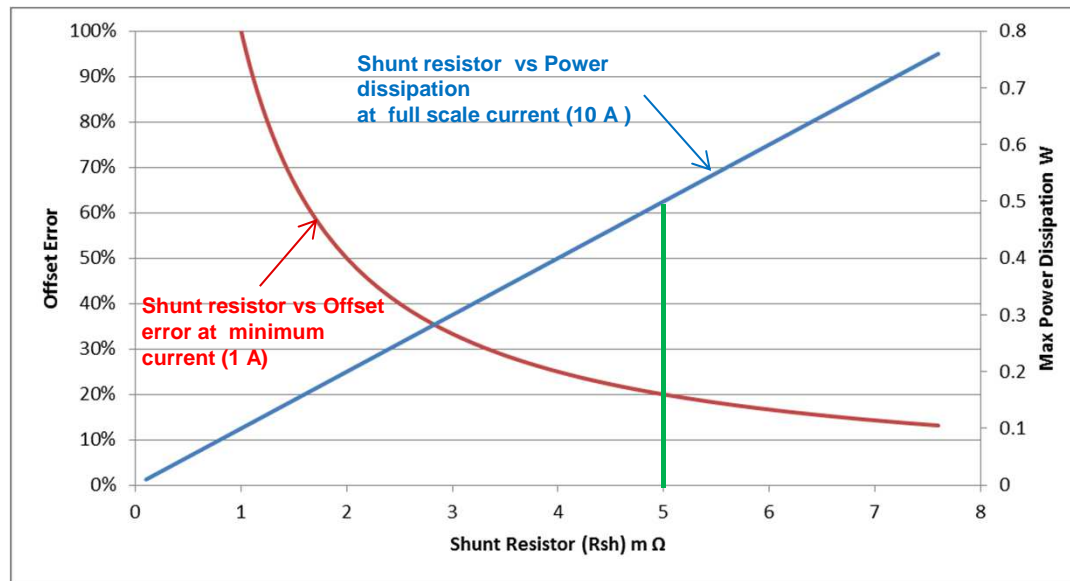Power Dissipation vs Minimum Current Accuracy tradeoff





$$\text{Offset Error (in percent)} = \frac{1 \text{ mV}}{5 \text{ m}\Omega * 1 \text{ A}} * 100 = 20 \%$$

$$\text{Max Power Dissipation (W)} = 5 \text{ m}\Omega * 10 \text{ A}^2 = 0.5 \text{ W}$$

Iload_min = 1 A; Iload_max = 10 A

How To Choose An Appropriate Shunt Resistor

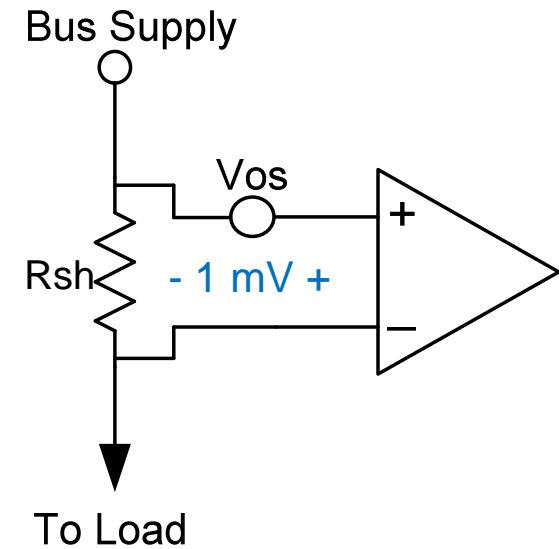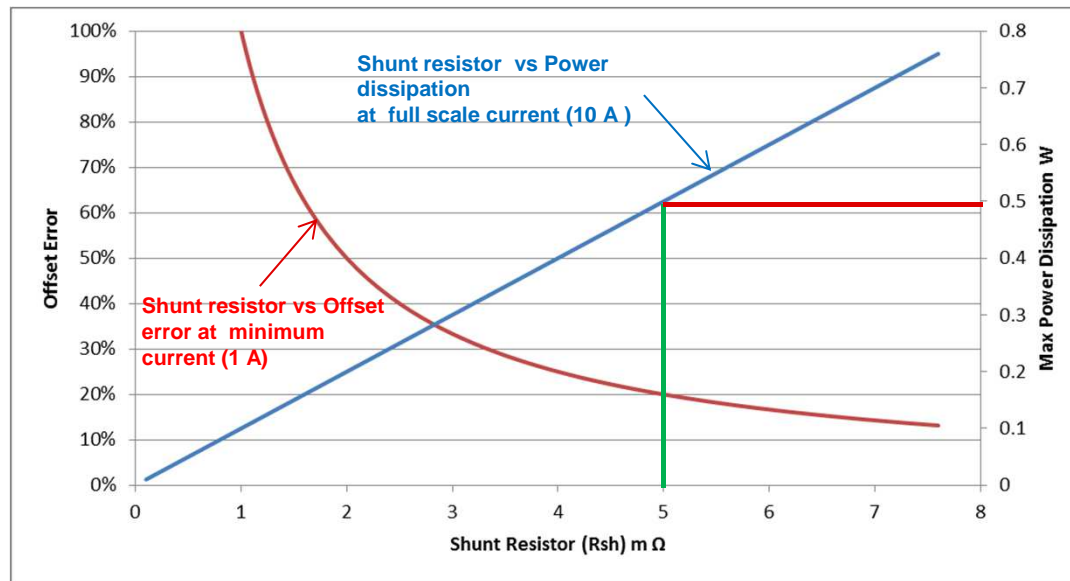Power Dissipation vs Minimum Current Accuracy tradeoff





$$\text{Offset Error (in percent)} = \frac{1 \text{ mV}}{5 \text{ m}\Omega * 1 \text{ A}} * 100 = 20 \%$$

$$\text{Max Power Dissipation (W)} = 5 \text{ m}\Omega * 10 \text{ A}^2 = 0.5 \text{ W}$$

Iload_min = 1 A; Iload_max = 10 A

How To Choose An Appropriate Shunt Resistor

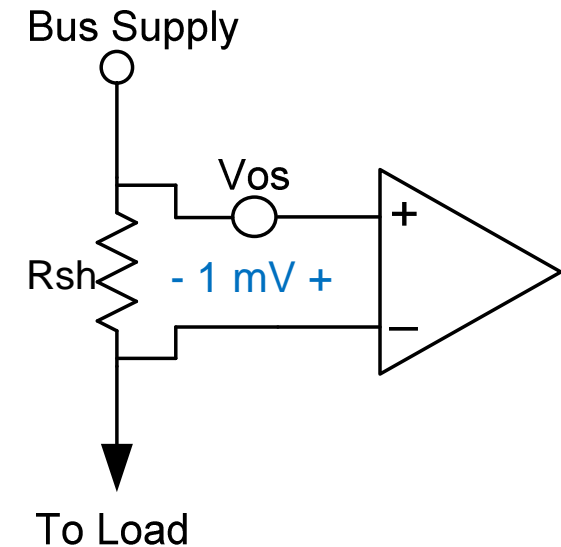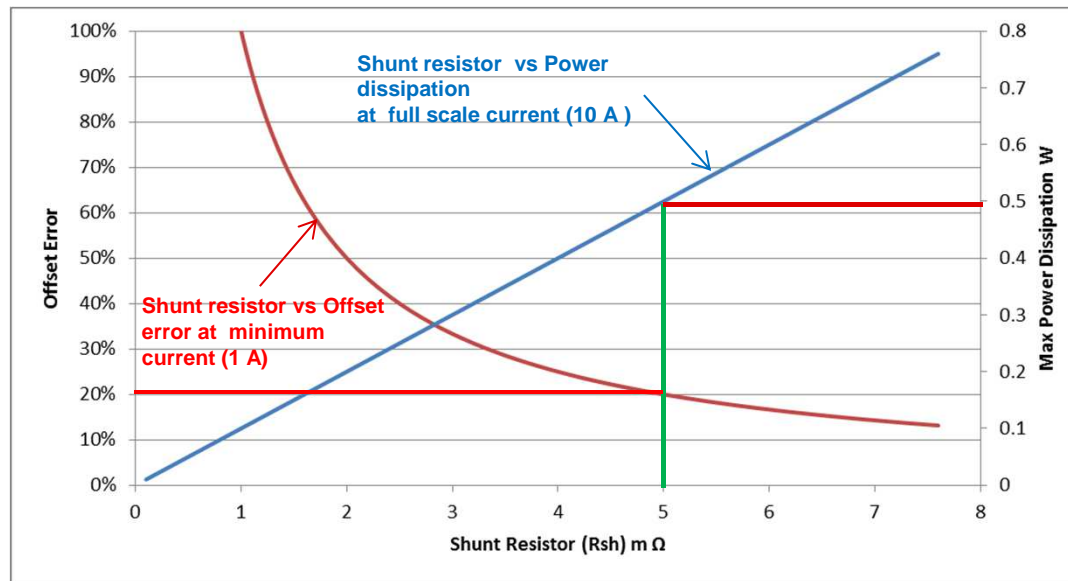Power Dissipation vs Minimum Current Accuracy tradeoff





$$\text{Offset Error (in percent)} = \frac{1 \text{ mV}}{5 \text{ m}\Omega * 1 \text{ A}} * 100 = 20 \%$$

$$\text{Max Power Dissipation (W)} = 5 \text{ m}\Omega * 10 \text{ A}^2 = 0.5 \text{ W}$$

$$I_{\text{load_min}} = 1 \text{ A}; I_{\text{load_max}} = 10 \text{ A}$$

How To Choose An Appropriate Shunt Resistor

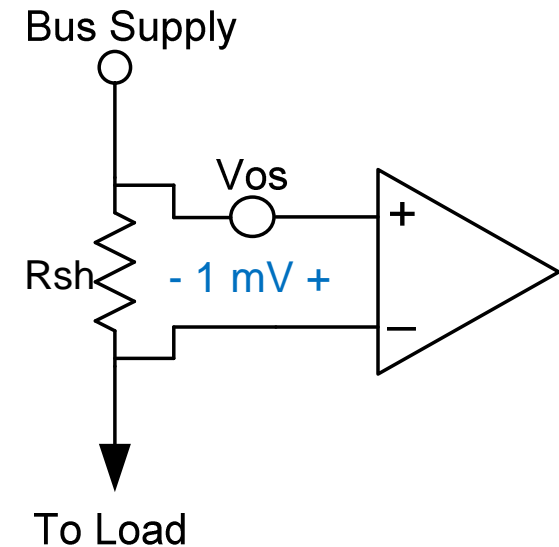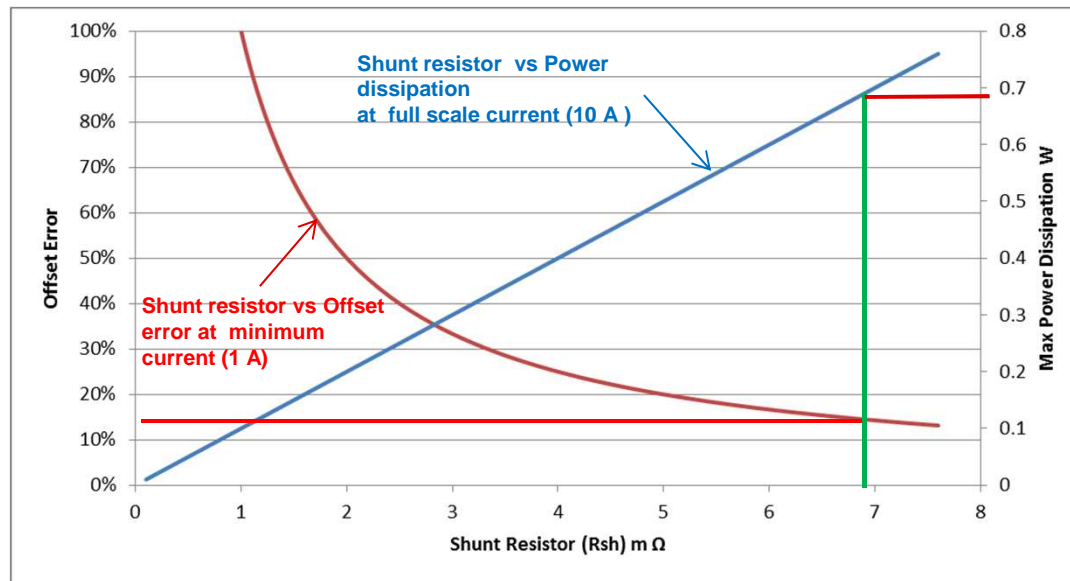Power Dissipation vs Minimum Current Accuracy tradeoff



$$\text{Offset Error (in percent)} = \frac{1 \text{ mV}}{6.66 \text{ m}\Omega * 1 \text{ A}} * 100 = 15 \%$$

$$\text{Max Power Dissipation (W)} = 6.66 \text{ m}\Omega * 10 \text{ A}^2 = 0.66 \text{ W}$$

$$I_{\text{load_min}} = 1 \text{ A}; I_{\text{load_max}} = 10 \text{ A}$$

How To Choose An Appropriate Shunt Resistor

Maximum value of Sense resistor

1. Maximum load current
2. Full-scale output range of the sensing device (V_{out})
3. Gain

$$\text{Maximum value of shunt resistor} = \frac{V_{out} \div \text{Gain}}{\text{Maximum load current}}$$

How To Choose An Appropriate Shunt Resistor

Shunt Resistor Tolerance Error

- Maximum deviation from the ideal value, expressed as a percentage.

$$\text{Actual Resistance} = \text{Ideal Resistance} \pm \frac{\text{Tolerance}}{100} * \text{Ideal Resistance}$$

$$\text{Actual Resistance} = 10 \text{ m}\Omega \pm \frac{1}{100} * 10\text{m}\Omega = 10 \text{ m}\Omega \pm 0.1 \text{ m}\Omega$$

9.9 m Ω \longrightarrow 10.1 m Ω

How To Choose An Appropriate Shunt Resistor

Example

PARAMETER	VALUES	PARAMETER	EQUATION	RESULT (INA199A1)
Iload_min	100 mA	Rsh_Max (Max Current-shunt resistor value)	$Rsh_{max} = \frac{Vout \div Gain}{Iload_{max}} = \frac{5 V \div 50 V/V}{10 A}$	10 mΩ
Iload_max	10 A	Psh (Current-sense resistor power dissipation at Full-scale current)	$Psh = Rsh * Iload_{max}^2 = 10 m\Omega * 10 A * 10 A$	1 W
Vout	5 V	Error due to offset at minimum load current	$Offset Error = \frac{Vos}{Rsh * Iload_{min}} * 100 = \frac{150 \mu V}{10 m\Omega * 100 mA} * 100$	15 %
Gain (INA199 A1)	50 V/V	Total Error at minimum load current		~15%
Gain Error (INA199 A1)	1.5 %	Error due to offset at maximum load current	$Offset Error = \frac{Vos}{Rsh * Iload_{min}} * 100 = \frac{150 \mu V}{10 m\Omega * 10 A} * 100$	0.15 %
Vos (INA199A1)	150 μV	Total Error at maximum load current	Rsh tolerance = 1%	~ 1.8 %

How To Choose An Appropriate Shunt Resistor

Shunt Resistor Pricing

Package	Tolerance (%)	Resistance (mΩ)	Power Rating (W)	Unit Price (\$)
805	1	10	0.5	0.53
1206	1	10	1	0.64
2512	1	10	2	0.65
1206	0.5	10	0.5	0.74
2512	0.5	10	1	1.66
Wide 2512	0.5	10	2	2.16

How To Choose An Appropriate Shunt Resistor

- Shunt Resistor definition
- Primary factors for choosing a Shunt Resistor
 - ✓ Accuracy at minimum current
 - ✓ Power dissipation at maximum current

- Calculating maximum value of the shunt resistor :

$$\text{Maximum value of shunt resistor} = \frac{V_{out} \div \text{Gain}}{\text{Maximum load current}}$$

ti.com/sensing ti.com/currentsense

Getting Started with Current Sense Amplifiers Video Series

Session 1: When to choose a Current Sense Amp

Session 2: Current Sense Amp Design Considerations

Session 3: Implementation options for both high-side and low-side monitoring

Session 4: How to choose an appropriate Shunt Resistor

Session 5: Understanding different types of error in current shunt monitor designs

Session 6: Understanding gain errors

Session 7: Understanding offset errors

Session 8: Understanding filter related error

Session 9: Understanding common mode voltage error

Session 10: Understanding temperature related error

Session 11: Understanding power supply rejection error

Session 12: Understanding shunt resistor tolerance error

Session 13: Layout considerations for a Current Shunt Monitor circuit

Session 14: Debugging a Current Shunt Monitor circuit - where to probe

Session 15: Programming Power Settings