

The slewing-rate limitation will not only cause distortion of the output for square-wave inputs, but also distort the output for sine-wave inputs of sufficiently high frequency. The slew rate limits the maximum slope of the sinusoidal output, and by equating the sine wave's maximum slope to the slew-rate limit, the full-power bandwidth is found:

$$\begin{aligned}
 e &= E_p \sin 2\pi f t \\
 \left| \frac{de}{dt} \right| &= 2\pi f E_p \cos 2\pi f t \\
 S_R &= \left| \frac{de}{dt} \right|_{\max} = 2\pi f_p E_p \\
 f_p &= \frac{S_R}{2\pi E_p}
 \end{aligned}
 \quad (1-24)$$

where  $E_p$  is the peak amplitude of the sine wave. Generally, the full-power bandwidth is specified for rated output, which is typically  $\pm 10$  V.

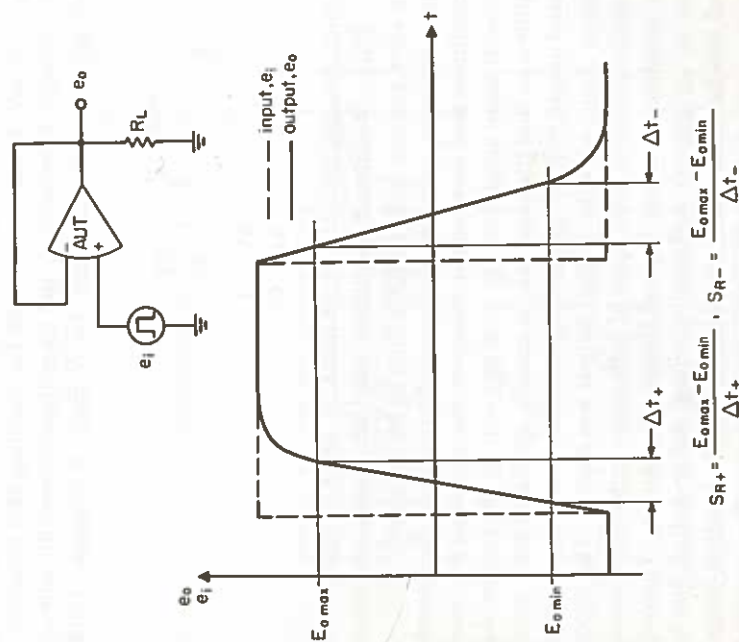


Fig. 1.24 The slew rate of practical operational amplifiers is frequently unsymmetrical, requiring testing for both positive and negative transitions.

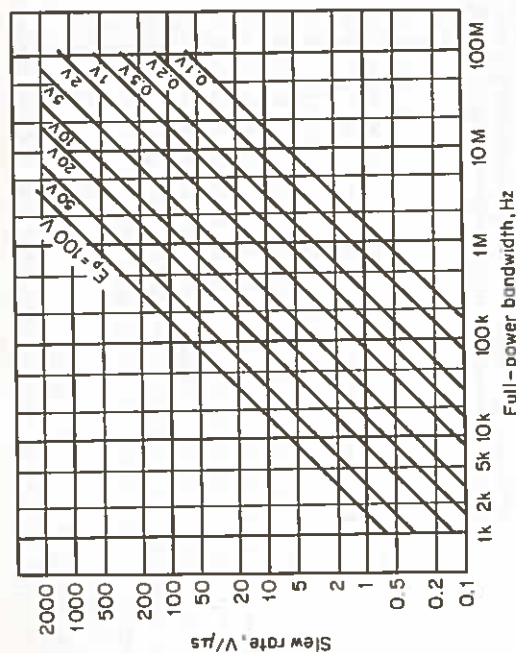


Fig. 1.25 Full-power bandwidth is theoretically related to slew rate, and is the primary frequency limitation when the output swing is large.

However, the full-power bandwidth for reduced output swing is frequently of most interest, and it can be found from Eq. (1-24), or from the graph in Fig. 1.25.

With the graphs in Figs. 1.23 and 1.25, the upper frequency limit of an operational amplifier circuit can be found. With the amplifier's slew-rate specification and the sine-wave amplitude required, the full-power bandwidth is determined from Fig. 1.25 or Eq. (1-24). Then, if the frequency of interest is less than the full-power bandwidth, the magnitude and vector errors can be found from Fig. 1.23. Note that if the frequency of interest is above the full-power bandwidth of the amplifier, the graph in Figure 1.23 does not apply, since it is generated for linear frequency response.

**1.3.3 Settling time** Settling time is the time required following application of an input step for the output to settle to within a specified error band of its final value. A complex output step response, containing overshoot and ring, is shown in Fig. 1.26. The settling time  $t_s$  is a strong function of the error-band  $\eta$  specified, particularly when there is output ring following a step input.

General-purpose amplifiers are usually phase-compensated to have a single-pole frequency response, as discussed previously in Sec. 1.3.1. Such an amplifier's output response to a step input  $E_i(t)$  can be found from the inverse Laplace transform of Eq. (1-23):

$$e_o(t) = A_{CL} (1 - e^{-t/\theta_{CL}}) E_i$$