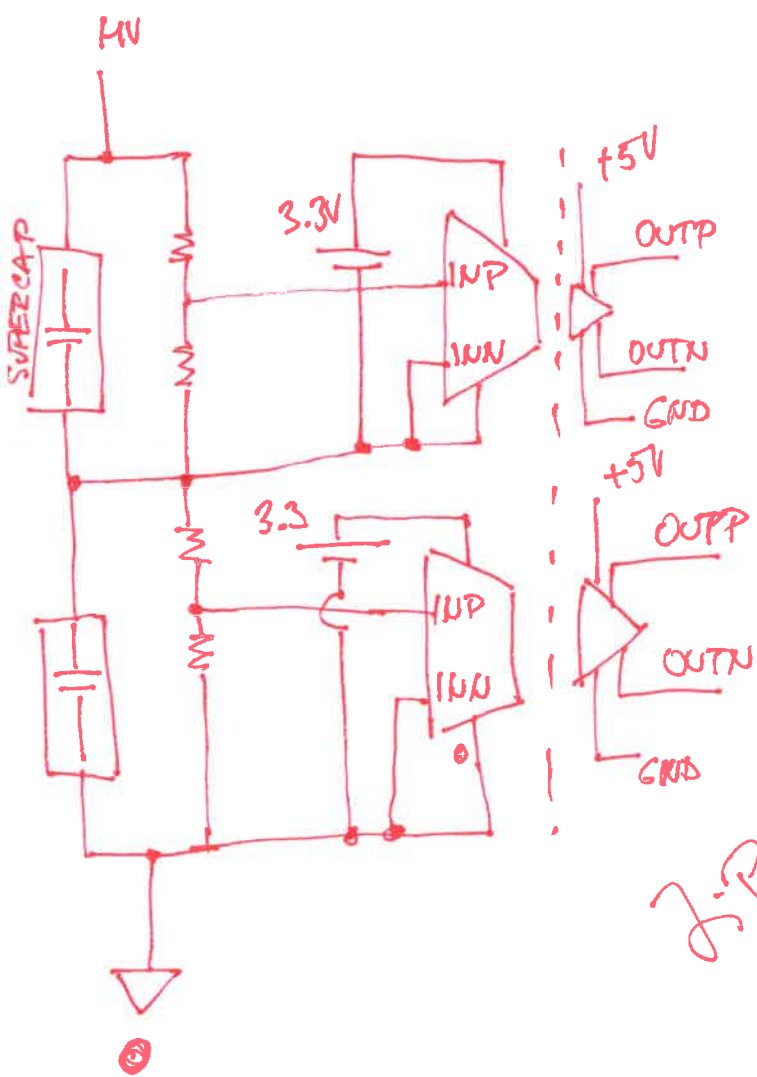




J.P 2025
:-)

Calculate the resistors
such it matches the input
range of the ADC device