



# Transimpedance Amplifier Circuit Design Consideration

**Bryan Zhao ( 赵伟 )**

Texas Instruments Signal Chain FAE

[Bryan-Zhao@ti.com](mailto:Bryan-Zhao@ti.com)



# Photodiode Basic





# Photodiode Basic

- **Introduction**

Photodiodes are semiconductor light sensors that generate a current or voltage when the P-N junction in the semiconductor is illuminated by light. The term photodiode can be broadly defined to include even solar batteries, but it usually refers to sensors used to detect the intensity of light.

- **Photodiode type**

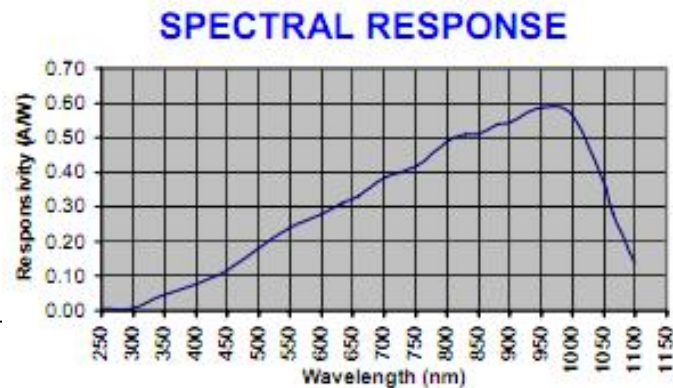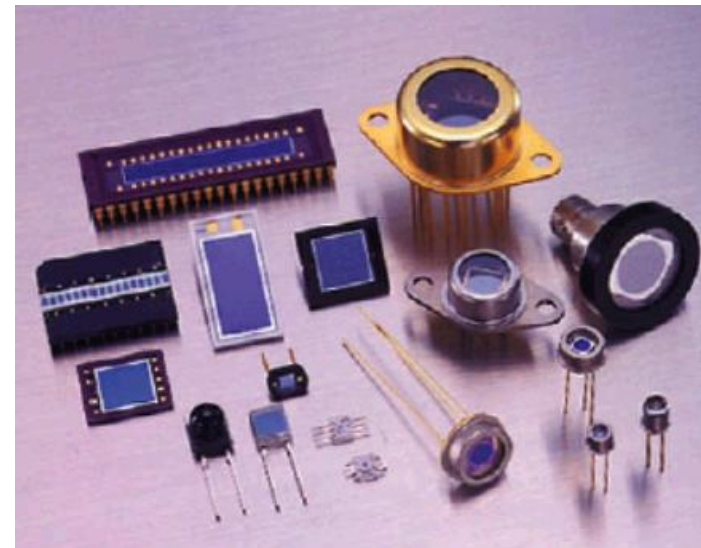- PN photodiode
- PIN photodiode
- Schottky type photodiode
- APD (Avalanche photodiode)





# Photodiode Basic


## Principle of Operation:

. - The P-layer material at the active surface and the N material at the substrate form a PN junction which operates as a photoelectric converter.

- When light strikes a photodiode, the electron within the crystal structure becomes stimulated. If the light energy is greater than the band gap energy  $E_g$ , the electrons are pulled up into the conduction band, leaving holes in their place in the valence band.


- These electron-hole pairs occur throughout the P-layer, depletion layer and N-layer materials. In the depletion layer the electric field accelerates these electrons toward the N-layer and the holes toward the P-layer.

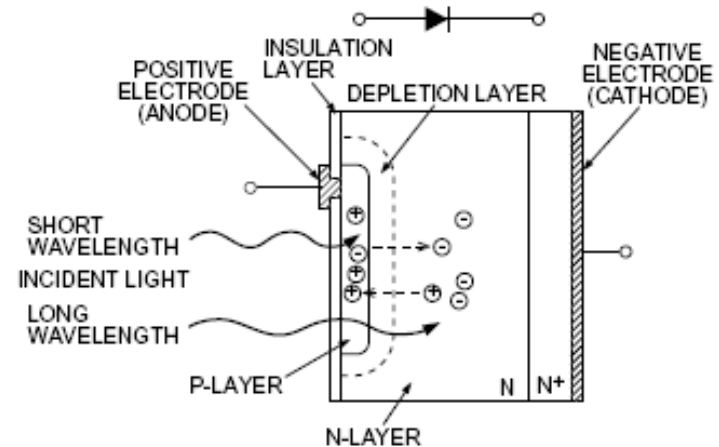- This results in a positive charge in the P-layer and a negative charge in the N-layer. If an external circuit is connected between the P- and N-layers, electrons will flow away from the N-layer, and holes will flow away from the P-layer toward the opposite respective electrodes.



KPDC0002EA

Figure1.1 Photodiode cross section

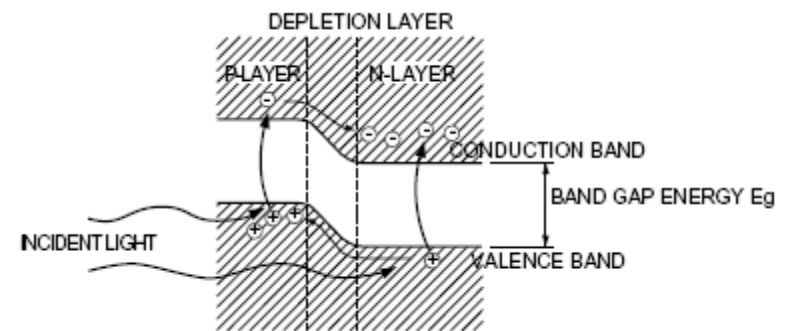

KPDC0003EA

Figure1.2 PN junction State



# Photodiode Basic

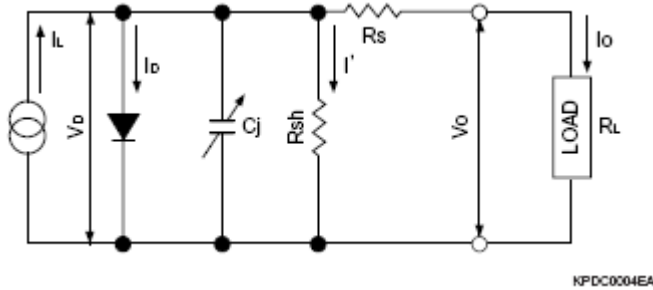


Figure 1.3 Photodiode Equivalent Circuit

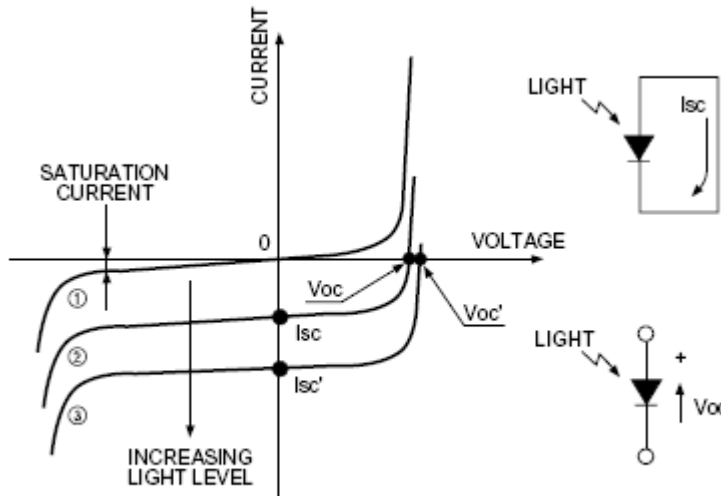


Figure 1.4 Current VS. Voltage characters

**$I_L$  : Current generated by the incident light**

$$I_L := r_\phi \phi_e$$

$r_\phi$  is the diode's flux responsivity

$\phi_e$  is the radiant flux energy in watts

**$I_D$  : Diode Current**

**$C_j$  : Junction capacitance**

$$C_j := \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{\phi_B}}}$$

$C_{j0}$  is the photodiode capacitance at zero bias

$\phi_B$  is the built-in voltage of the diode junction

$V_R$  is the reverse bias voltage

**$R_{sh}$  : Shunt resistance**

**$R_s$  : Series resistance**

**$I'$  : Shunt resistance current**

**$V_D$  : Output current**

**$I_o$  : Output current**

**$V_o$  : Output voltage**



# Photodiode Basic

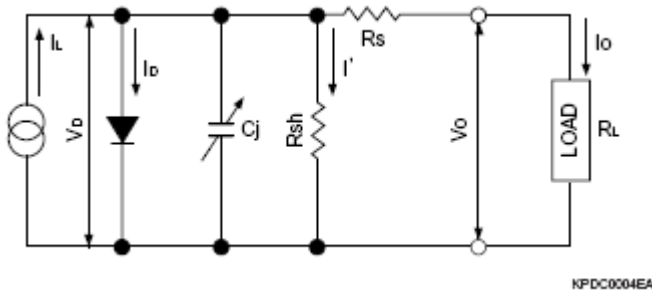


Figure1.4 Photodiode Equivalent Circuit

Use left equivalent circuit, the output current is given as :

$$I_o := I_L - I_D - I' = I_L - I_S \left( e^{\frac{eV_D}{kT}} - 1 \right) - I'$$

$I_S$  : Photodiode reverse saturation current

$e$ : electron charge

$k$ : Boltzmann's constant

$T$ : Absolute temperature of the photodiode

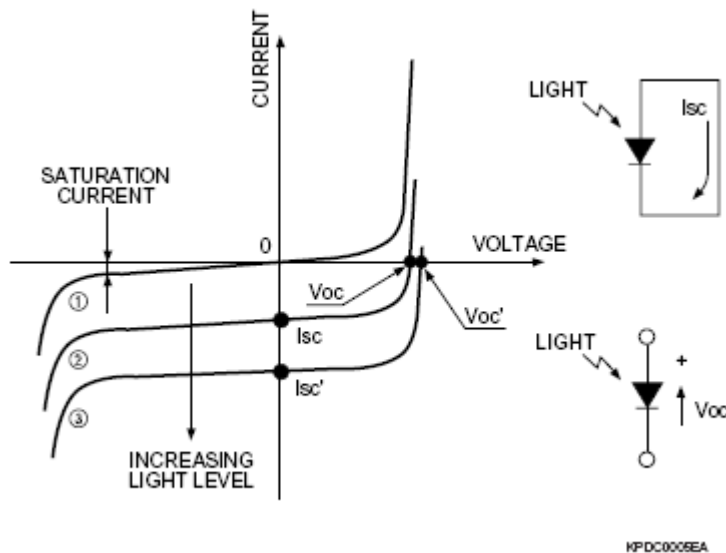


Figure1.5 Current VS. Voltage characters

The open circuit voltage  $V_{oc}$  is the output voltage when  $I_o$  equals 0. Thus  $V_{oc}$  becomes:

$$V_{oc} := \frac{kT}{c} \ln \left( \frac{I_L - I'}{I_S} + 1 \right)$$


If  $I'$  is negligible, since  $I_s$  increases exponentially with respect to ambient temperature,  $V_{oc}$  is inversely proportional to the ambient temperature and proportional to the log of  $I_L$ . However, this relationship does not hold for very low light levels.



- ∅ The ac response of  $I_L$  displays a dual time constant due to the two carries travel mechanisms that account for photodiode current. Carries generated both within and outside the depletion region travel under the accelerating influence of the region's electric field and proceed rapidly to the diode's terminals. This produces a fast or drift component of  $I_L$ ,  $I_{dr}$  as controlled by the drift time of the depletion region.
- ∅ The carries generated outside the region initially travel slower. So the interim diffusion time produces a slow component of  $I_L$ ,  $I_{di}$ .
- ∅ The combination of the two components produces a time domain current of  $I_L$ .


$$I_L(t) = I_L(\infty) \left( 1 - \alpha_{dr} e^{-\frac{t}{\tau_{dr}}} - \alpha_{di} e^{-\frac{t}{\tau_{di}}} \right)$$

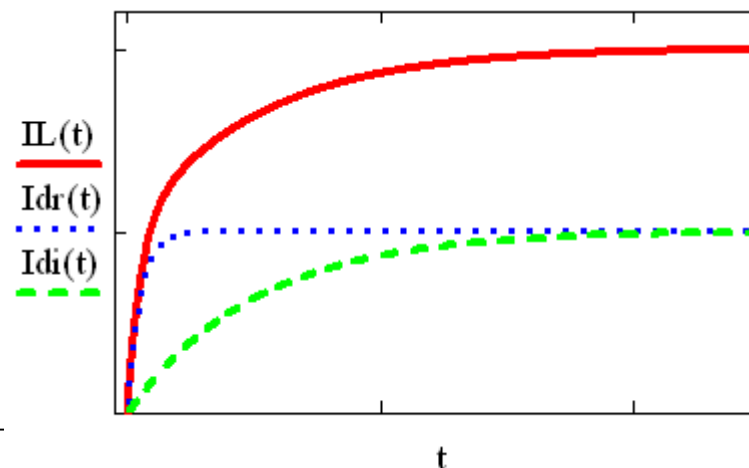$\alpha_{dr}$  and  $\alpha_{di}$  represent the fractions of  $I_L$  supplied by the drift and diffusion components.




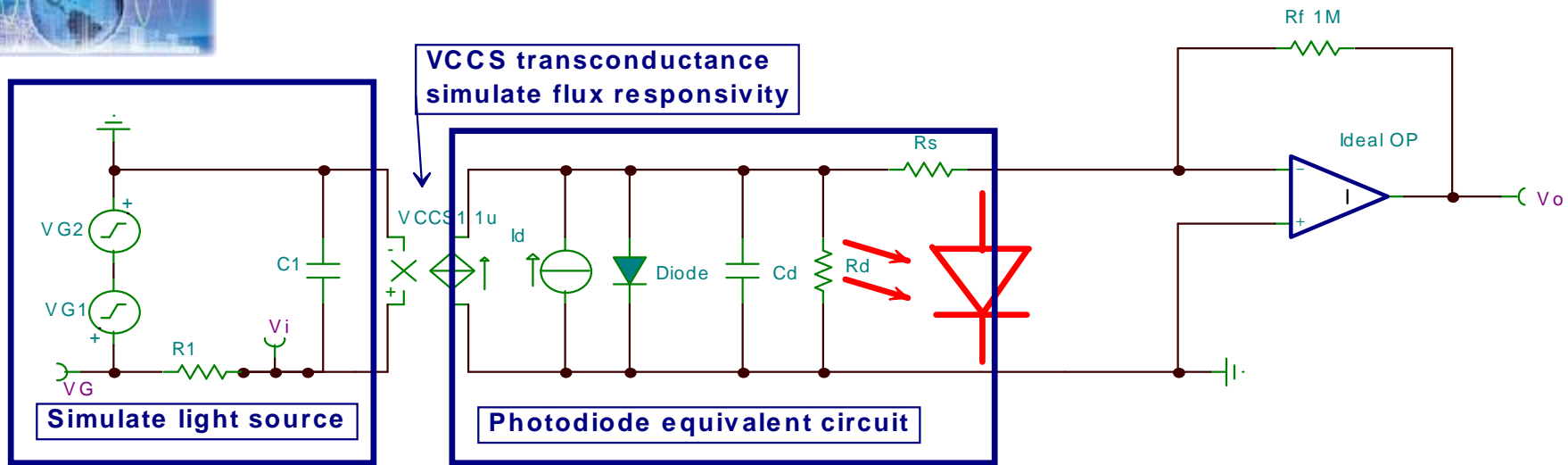
# Photodiode and Control Source TINA model



## Light exciting source:

- 1) Use VG1 and VG2 voltage sources to simulate light power wave.
- 2) Use R1 and C1 to control voltage signal's rise edge and fall edge, to simulate photodiode's current response. The time constant  $\tau$  equals to  $R1 \cdot C1$ , change R1 and C1 can set different rise/fall edge times. Usually we need select a very small R1 to prevent voltage attenuation.
- 3) The signal is converted to current by Voltage Control Current Source (VCCS1), we control the transconductance to simulate photodiode's sensitivity.

## photodiode equivalent circuit:

- 1), Current Source  $I_d$  simulate Dark current
- 2), Diode is a ideal diode
- 3), Cd and Rd simulate photodiode's junction capacitor and dark Resistance.
- 4), Rs is series resistor, which is far smaller than Rd.







# Photodiode TINA model- Exciting Source

If we need a 1nA peak, 40ns width, 5ns rise/fall time photodiode output current.

- 1), Set VG1 and VG2 as 1V, unit step with 20ns and 60ns delay.
- 2), Set VCCS1 trans conductance equals to 1u
- 3), Set R1=1mΩ, C1=3uF.
- 4), Time constant equals to  $R1 * C1 = 3ns$

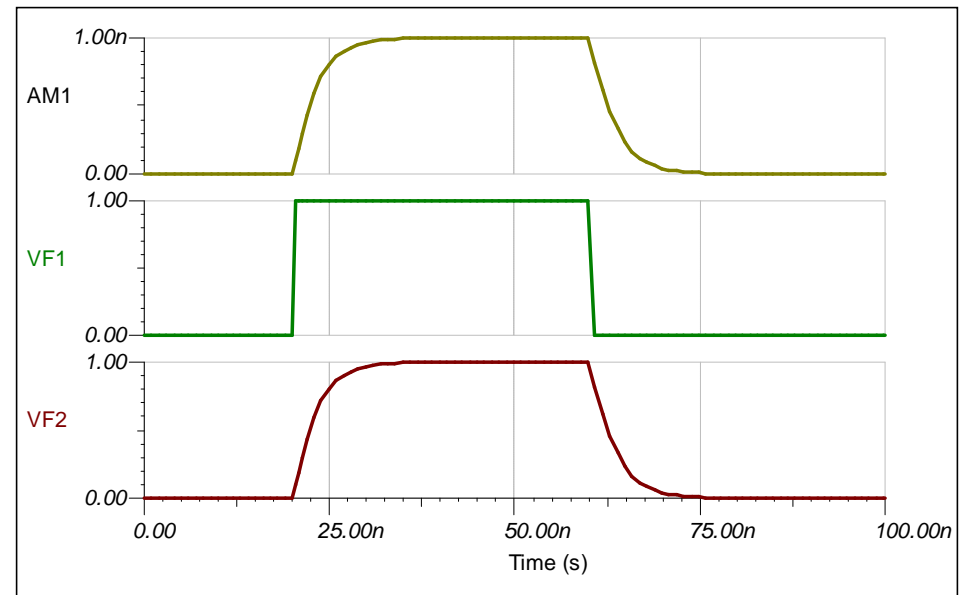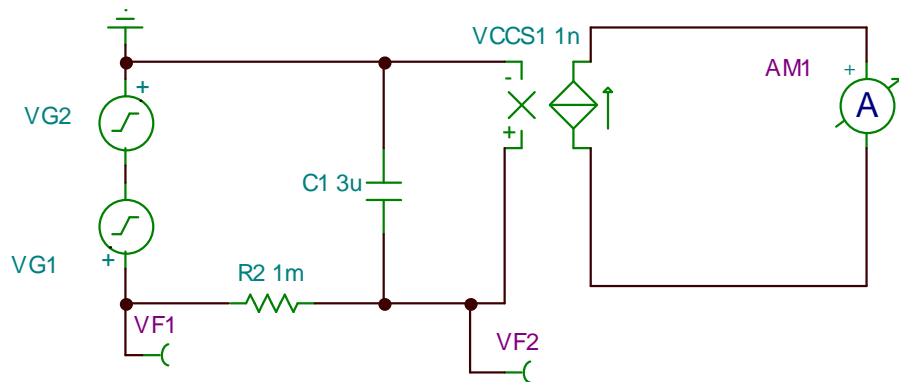**Rise/Fall time  $\approx R1 * C1 * 1.6 = 4.8ns$ ;**






# The basic amplifier



# Voltage Monitor Mode

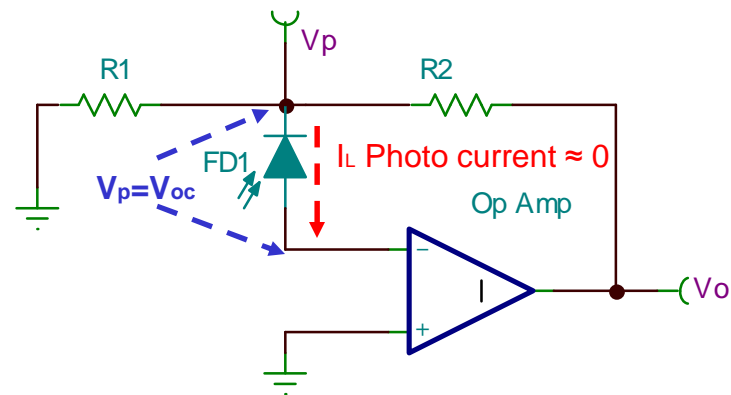

$$V_o = -(1 + R_2/R_1)V_p$$

In voltage monitor mode the diode is placed in series with an op amp input to avoid impedance loading but results in a nonlinear response and large dc offset. The nonlinearity results primarily from the logarithmic current-voltage characteristic of the diode junction. Photodiode operated in the voltage output mode produces a voltage described by:

$$V_{oc} := \frac{kT}{c} \ln \left( \frac{I_L - I'}{I_S} + 1 \right)$$

In the photovoltaic mode shown, the photodiode's own output voltage modulates the junction voltage to further increase nonlinearity. This circuit also produces a large dc offset due the flow of the op amp's input bias current  $I_b^-$  through the high resistance of the photodiode.



# Current Mode – Resistor Load

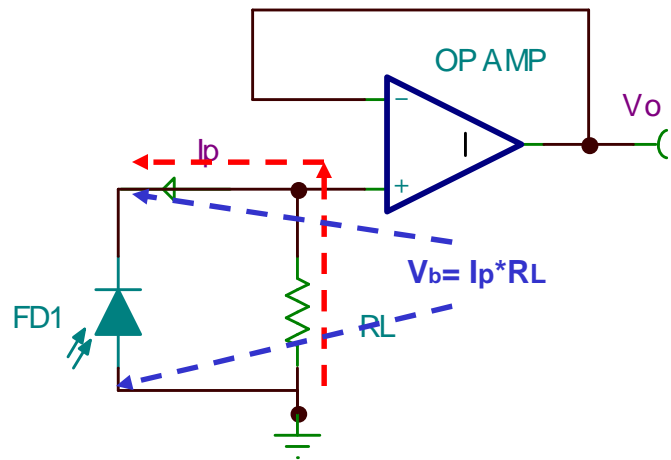


Figure (a)

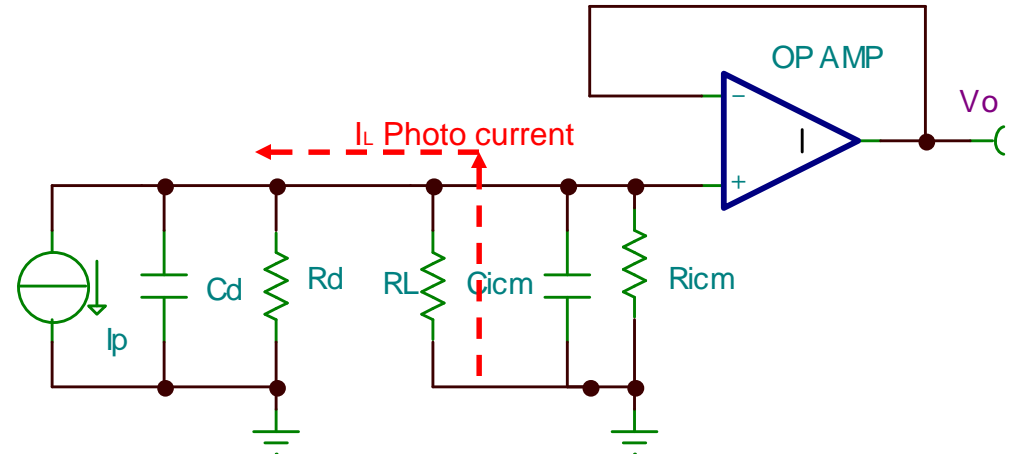


Figure (b)

- We can connect the photodiode as figure (a), so the photocurrent flow to  $R_L$  converting current to voltage. The op amp follower isolates  $R_L$  from any impedance loading error at the circuit output.
- However, this simple circuit also develops the full signal voltage  $V_o$  across the photodiode and its capacitance. The resulting signal current in this capacitance shunts the diode current at high frequency, producing a bandwidth limit.



## Current Mode

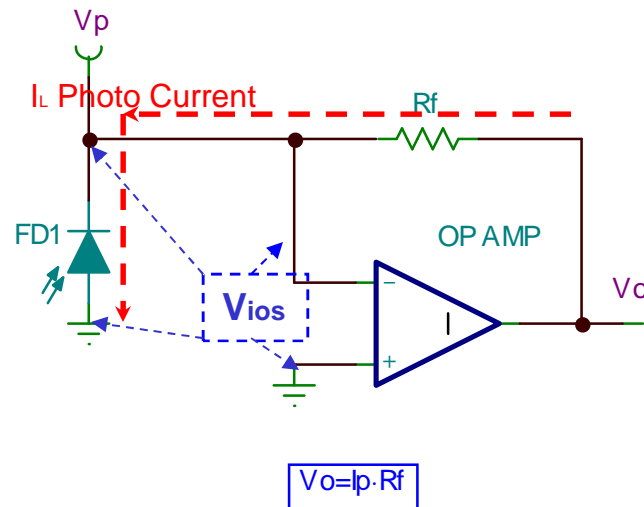



Figure (c)

Current Mode connection as figure (c). This circuit removed photodiode voltage and op-amp bias current  $I_{b-}$  from its capacitance and dark resistor. This alternative virtually eliminates  $V_p$  and the resulting nonlinearity, but only transfers  $I_{b-}$  to a smaller resistance.

Current monitoring requires that the monitor circuit present zero load impedance to the diode. Then the monitor absorbs the diode's current without producing a voltage across diode.



## Current Mode – Compensation resistor

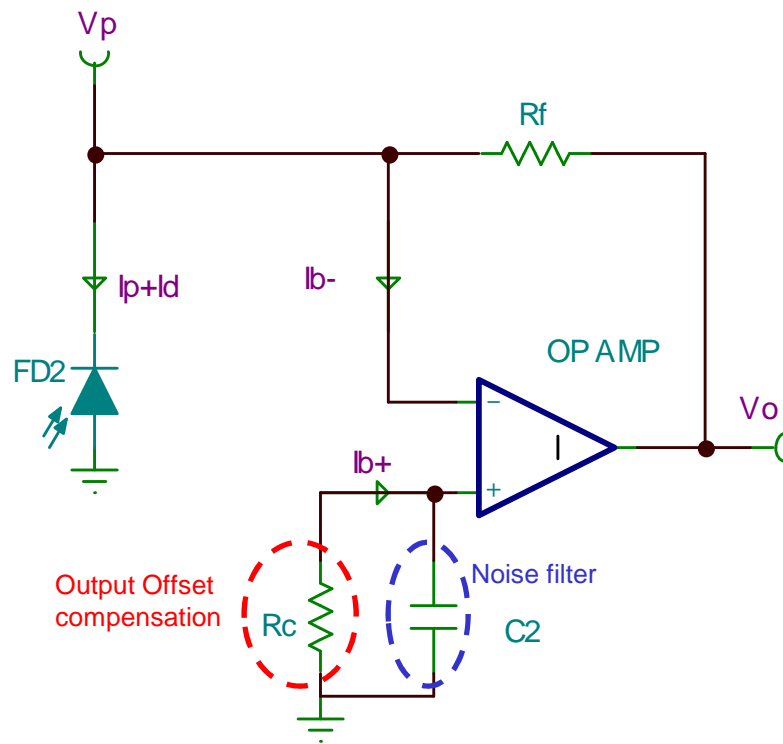

In real application, op-amp is not ideal and photodiode also have dark current, op amp need bias current at both inverting and non-inverting inputs. The bias current  $I_{b-}$  and dark current  $I_d$  will produce a Op amp output offset  $V_{oso}$ :

$$V_{oso} = R_f \cdot (I_d + I_{b-})$$

$I_d$  and  $I_{b-}$  multiplied by large resistor  $R_f$  will produce a large offset output. In order to reduce the offset, we can use a compensation resistor  $R_c$ , so the  $V_{oso}$  will be:

$$V_{oso} = R_f \cdot (I_d + I_{b-}) - R_c \cdot I_{b+}$$

Usually we set  $R_c = R_f$  to compensate the offset produced by  $I_{b-}$ . This reduced output offset a factor of 5 to 10 improvement over the initial offset and drift produced by the amplifier's input current.


Adding  $R_c$  also develops a voltage across the photodiode. The compensating voltage drop across  $R_c$ ,  $R_c \cdot I_{b+}$ , also drops across the photodiode and produce the diode's leakage current  $I_L(I_d)$ .

High sensitivity photodiodes require much larger junction areas than the typical op amp input FET and potentially larger leakage currents.

This requires evaluation of specific application conditions before adding  $R_c$ .



# Current Mode – Tee Network

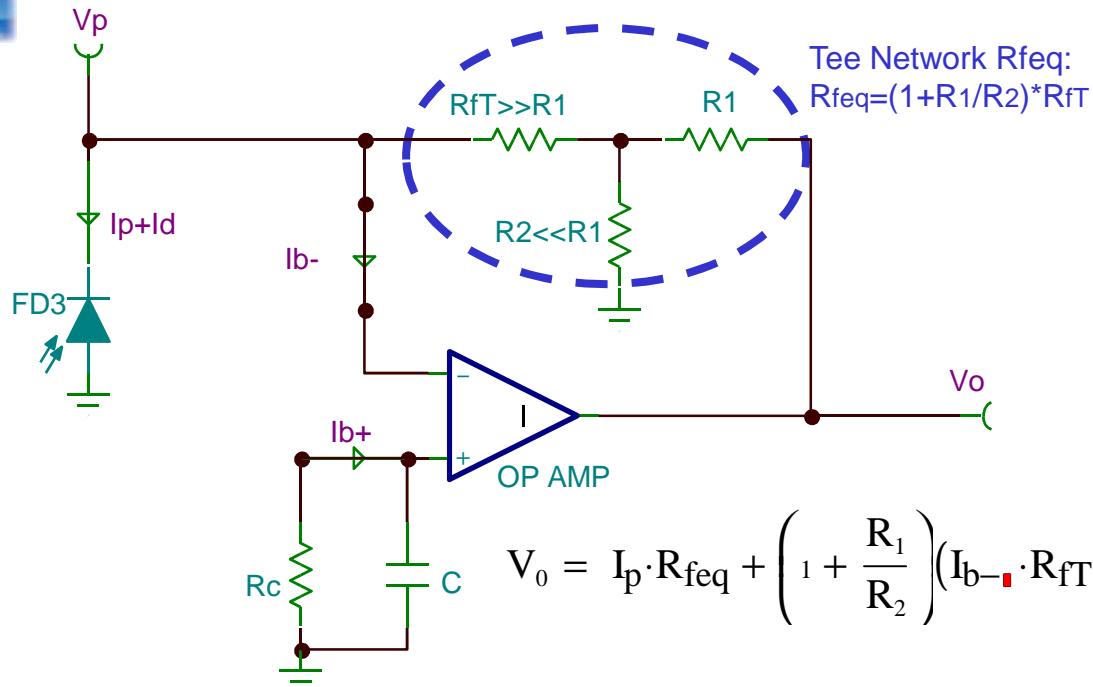

- Replacing  $R_f$  with a resistor tee **greatly reduce offset error** through reduced resistance levels.
- Reduced resistances **decrease** the  $R_c \cdot I_{b+}$  **voltage** impressed **upon the photodiode**, and reduced the resistance matching error of  $R_c$  to  $R_f$ .
- The tee also amplifiers the op amp's input offset voltage  $V_{os}$  and input noise voltage by factor  $1 + R_1/R_2$ .




# Bandwidth and Stability




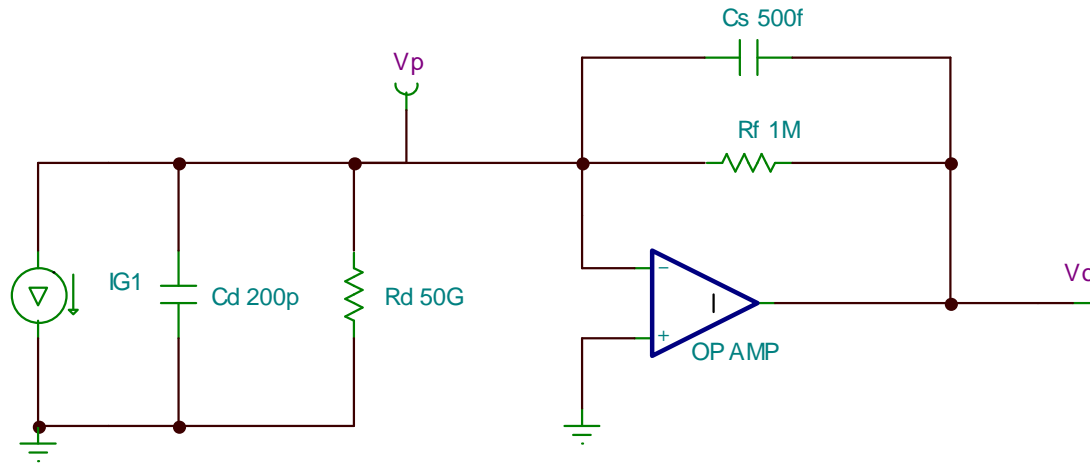
# Parasitic Capacitance limit the bandwidth




Higher feedback resistor value potentially make parasitic capacitance bypass dominate the photodiode amplifier's response and set the circuit bandwidth.

Good construction parasitic limit Cs around 0.5pF.

The parasitic capacitance and feedback resistance produce a gain pole at:


$$f_p = \frac{1}{2pR_f C_s} = 318kHz$$

**It is the same as simulation**

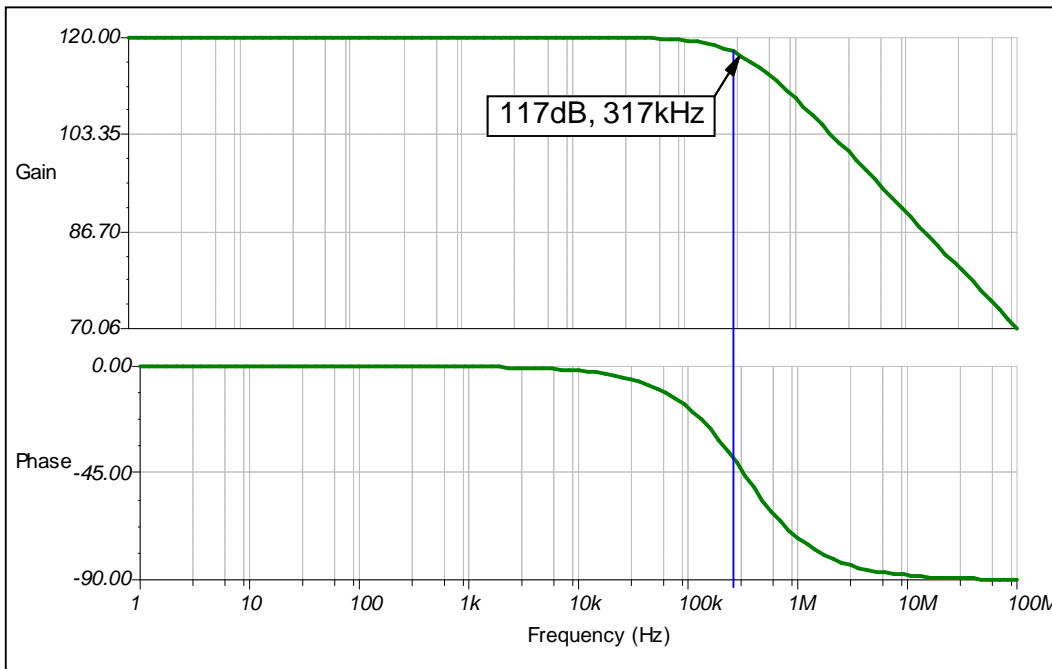



# Amplifier GBW limit bandwidth

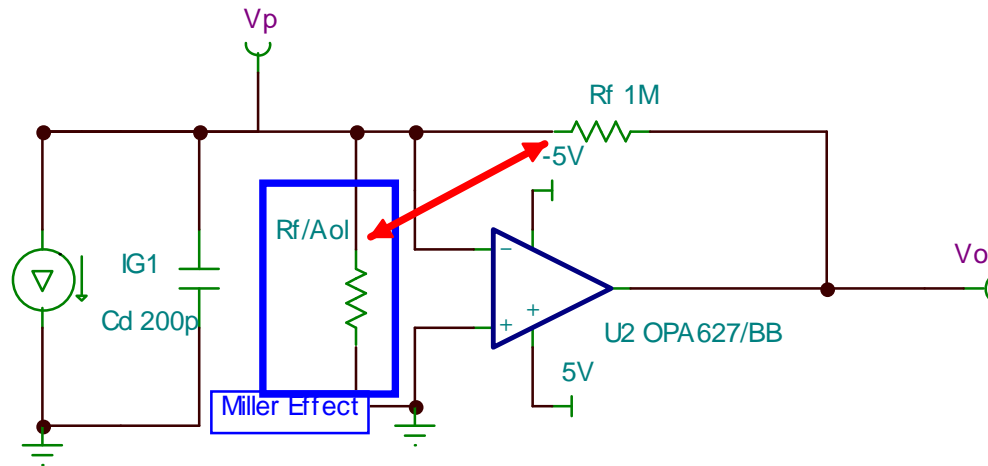

Because of miller effect, op amp's input resistor  $R_i' = R_f / A_{ol}$ , which will produce another pole to limit circuit's bandwidth. The pole frequency  $f_p$  is:

$$f_{pf} = \frac{A_{ol}}{2\pi R_f C_i}, \quad A_{ol} = \frac{f_c}{f}$$

$$f_{pf} = \frac{f_c}{2\pi R_f C_i f_{pf}}$$

$$f_{pf} = \sqrt{\frac{f_c}{2\pi R_f C_i}}$$

$f_c$  is unity gain bandwidth


$C_i = C_d + C_{id} + C_{icm}$

We select OPA627 to simulate:

OPA627,  $f_c = 16\text{MHz}$ ,  $C_{id} = 8\text{pF}$ ,  $C_{icm} = 7\text{pF}$


Calculation :  $f_{pf} = 109\text{KHz}$

Simulation :  $f_{pf} = 114\text{KHz}$

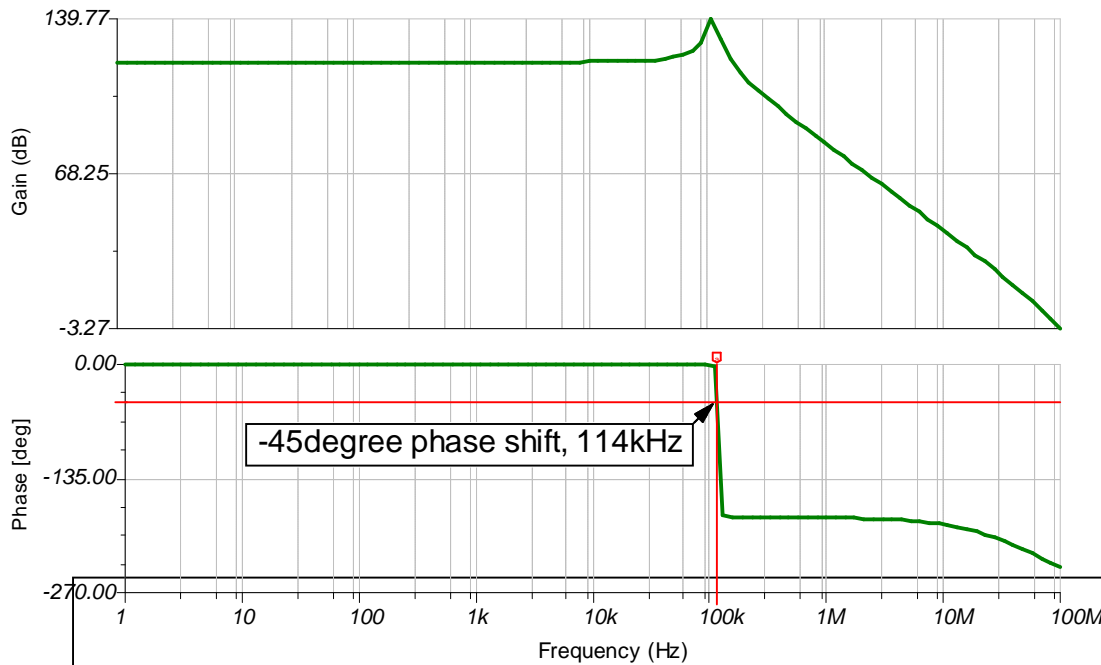





# Phase compensation limit bandwidth

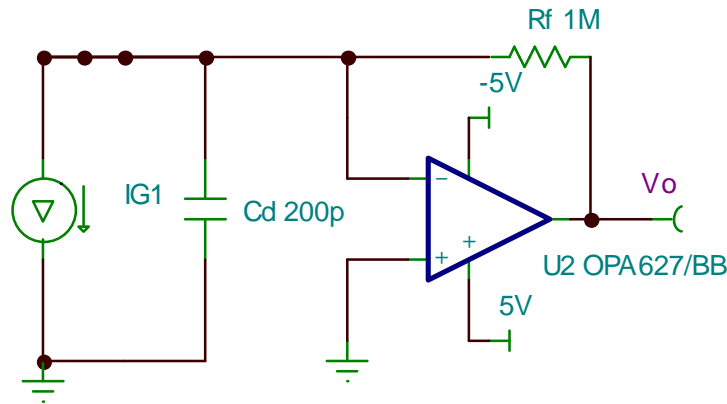


Rf and Cd will produce a zero at  $1/\beta$  curve, and it will cross with Aol curve at 20dB/dec, it make Acl closure in -40dB/dec, the circuit is unstable. As the simulation, the output is ringing.

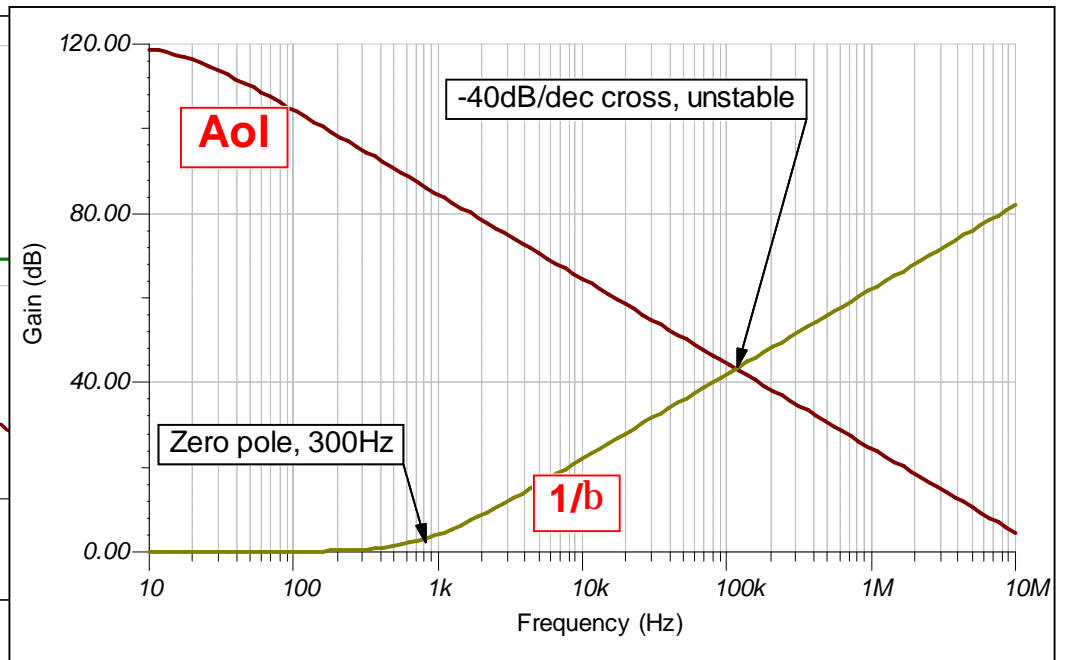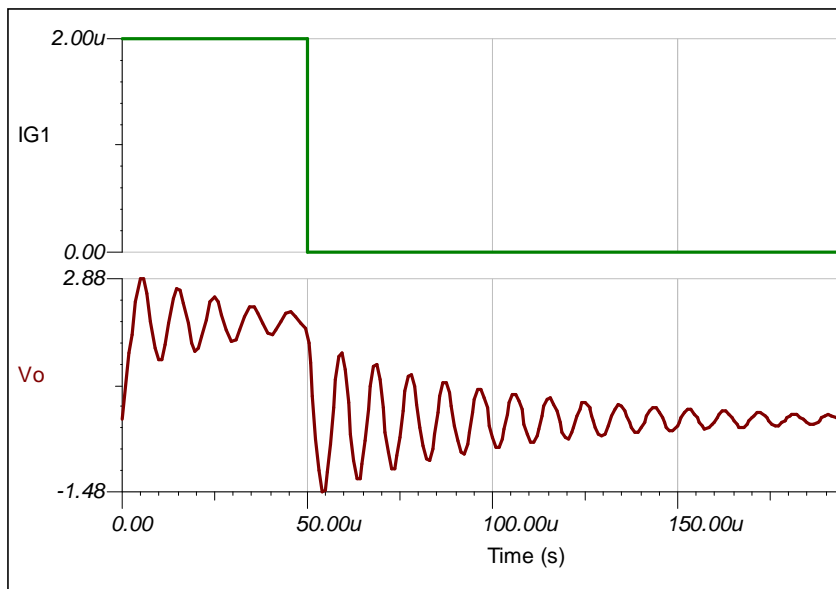In order to stabilize the circuit, we need add a capacitor parallel with Rf to produce a zero at Acl for phase compensation





# Phase compensation limit bandwidth

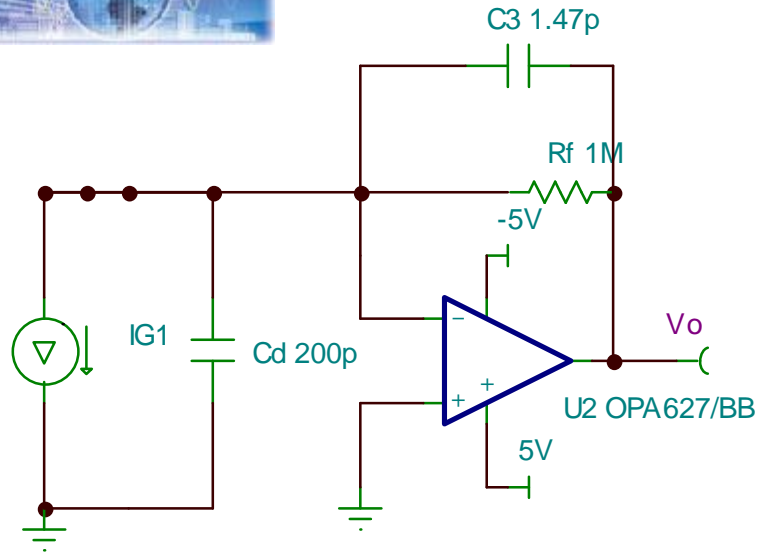


$$BW = 1.4 f_i \quad f_i = \sqrt{f_{zf} f_c}$$

$$f_{zf} = 1 / 2\pi R_f (C_i + C_f)$$

$$C_c = 1 / 2\pi R_f f_c$$

$$C_f = \sqrt{\frac{C_i}{2\pi R_f f_c}}$$
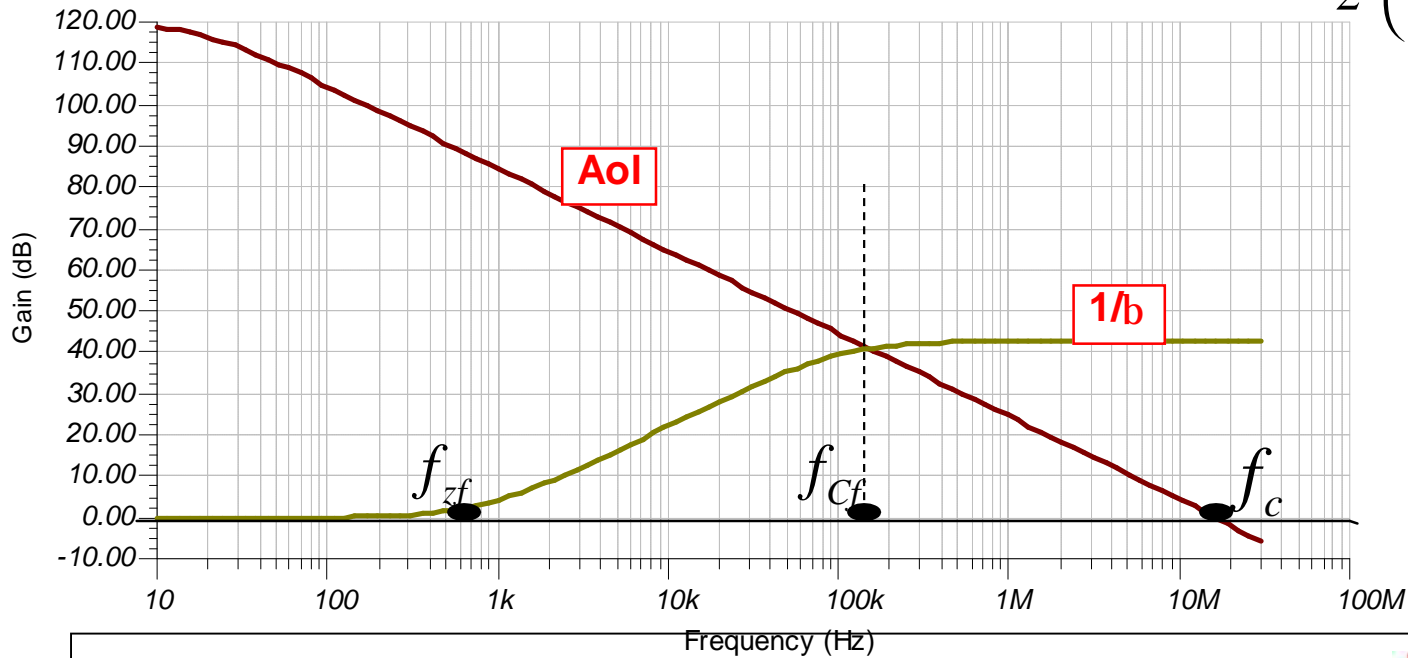
$$C_f = \frac{C_c}{2} \left( 1 + \sqrt{1 + \frac{4C_i}{C_c}} \right)$$






# Wideband photodiode Amplifier




# Biassing

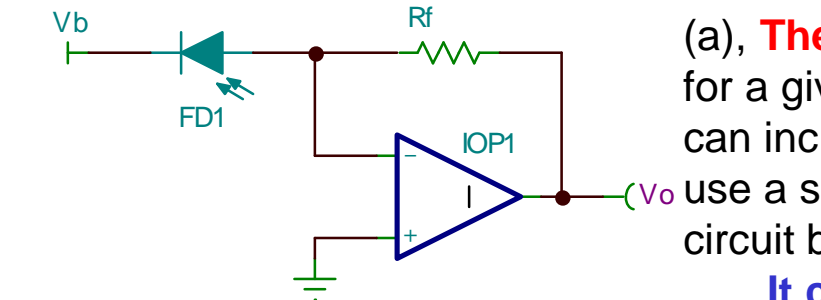

(a)

(a), **The bias voltage can decrease photo diode capacitor**, for a given amplifier, if we decrease photodiode capacitor, we can increase  $1/\beta$  curve zero frequency which make us may use a smaller compensation capacitance so that can increase circuit bandwidth. It will also reduce noise gain region.

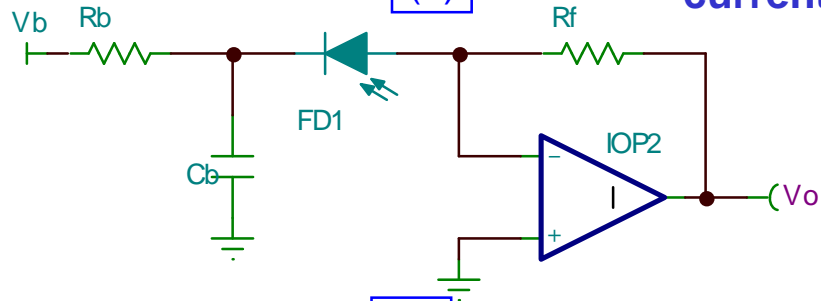
**It can still introduce bias noise and increase leak current**, which will make output a larger noise and offset.



(b)

(b) We can **use RC filter to limit bias voltage noise** pass to circuit output. Also, photodiode operating current can also pass  $R_b$  also, which produce AC modulation on  $V_b'$ , it will reintroduce some nonlinearity to output. We need set  $R_b \ll R_f$ ,  $C_b \gg C_d$ . The bias noise gain could be:

$$A_n = \frac{R_f C_D}{R_B C_B}$$

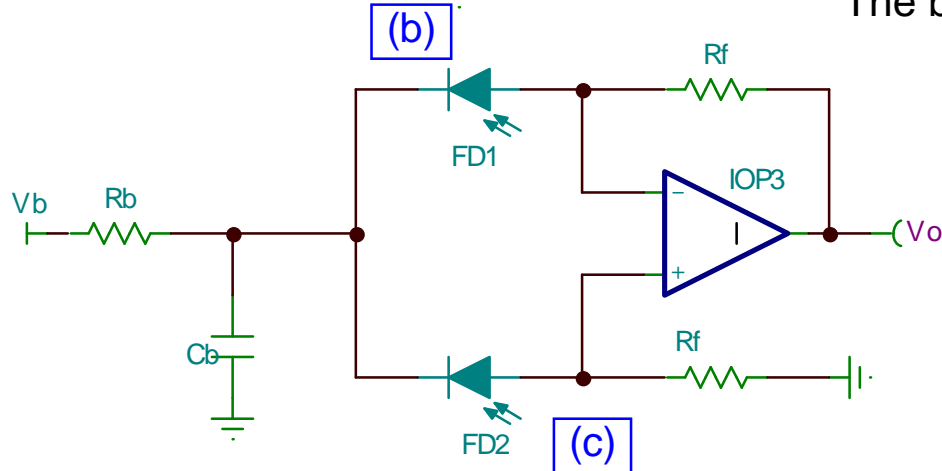


(c)

(c) We still can not remove leak offset on output in the (b) circuit. We can use (c) circuit to both remove leak offset and bias noise. We use same two photodiode to set up differential input. Let one operating and let another one in dark just provide cancellation leak current.



# Bootstrapping

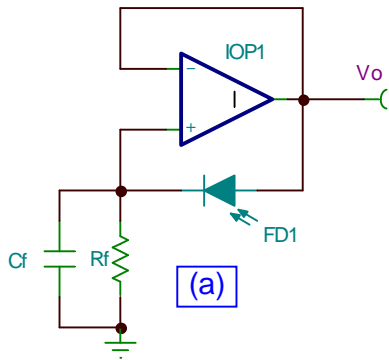

Bias circuit can decrease photodiode capacitor but it also more or less introduced noise, offset and nonlinearity to output. We can setup bootstrapping circuit as left (a), in bootstrapping mode, it removes signal voltage on photodiode, this void photodiode absorb diode's signal current at high frequencies.

$$BW = 1.4 f_i \quad f_i = \sqrt{f_{zf} f_c}$$


$$f_{zf} = \frac{1}{2pR_f(C_D + C_{id} + C_{icm} + C_f)}$$

$$C_c = 1 / 2pR_f f_c$$

$$C_f = \frac{C_c}{2} \sqrt{1 + \frac{4C_i}{C_c}} - C_{icm}$$


$$C_i = C_D + C_{id}$$

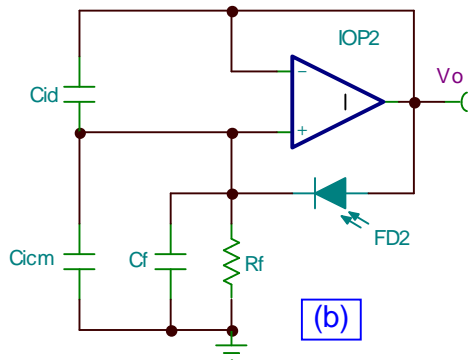Bootstrapping circuit actually use amplifier's differential input capacitance as part of compensation capacitance, so we can use a smaller value Cf. Obviously bootstrapping circuit improves bandwidth through a decrease in Cf that increase fzf in the bandwidth expression. It can only benefits the small capacitance case.



If we combine current monitor mode and bootstrapping mode, it has greater bandwidth improvement. The buffer amplifier need to be low input capacitance, low output noise, low output impedance and wideband.

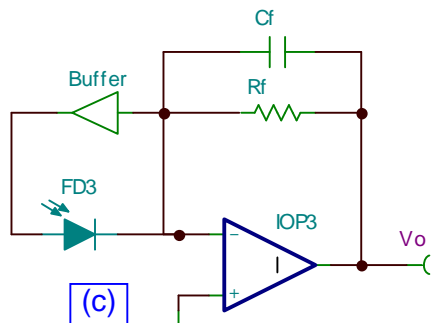This combination best serves larger photodiodes with high capacitances.





# Noise





# Photodiode noise

The lower limits of light detection for photodiodes are determined by the noise characteristics of the device. The photodiode noise is the sum of the thermal noise (or Johnson noise)  $i_j$  of a resistor which approximates the shunt resistance and the shot noise  $i_{sD}$  and  $i_{sL}$  resulting from the dark current and the photocurrent.

$$i_n = \sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2}$$

$$i_j = \sqrt{4 \cdot k \cdot T \cdot BW / R_{sh}}$$

$$i_{sD} = \sqrt{2 \cdot q \cdot I_D \cdot BW}$$


$$i_{sL} = \sqrt{2 \cdot q \cdot I_L \cdot BW}$$

K: Boltzmann's constant  
 T: Absolute temperature of the element  
 B: Noise bandwidth  
 q: Electron charge  
 I<sub>D</sub>: Dark current (Leak current)  
 I<sub>L</sub>: Photocurrent

If  $I_L \gg 0.026/R_{sh}$  or  $I_L \gg I_D$ , the shot noise becomes predominant. The lower limit of light detection for a photodiode is usually expressed as the intensity of incident light required to generate a current equal to the noise current. Essentially this is the noise equivalent power (NEP).

$$NEP = \frac{i_n}{S} [W / Hz^{1/2}]$$

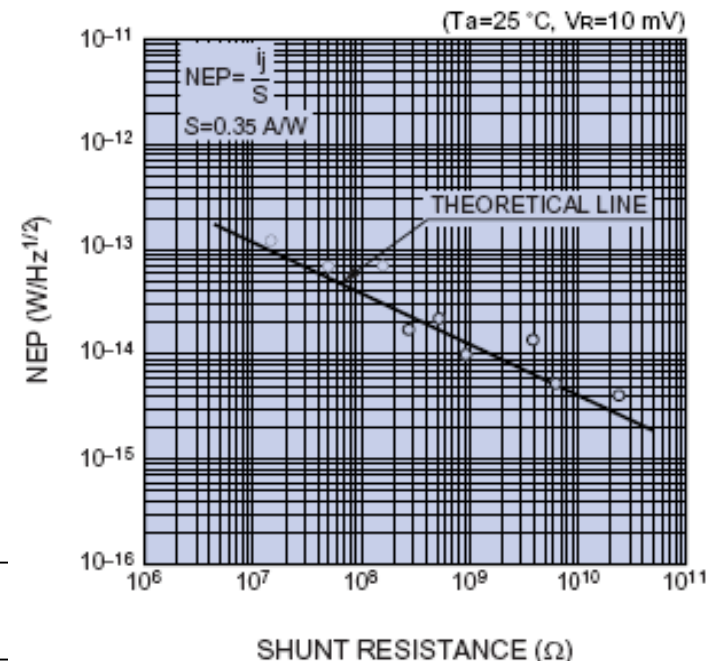In: noise current (A/ $\sqrt{Hz}$ )  
 S: Photo Sensitivity (A/W)





# Circuit Noise


Exclude photodiode noise, there are three kinds of circuit noise: Input voltage noise ( $V_{ni}$ ), Input current noise ( $I_{ni}$ ) and feedback resistor noise ( $V_{nR}$ ).

Different noise has different noise gain amplifying input noise to output.

$$e_{no} = \sqrt{(e_{noR})^2 + (e_{noi})^2 + (e_{noe})^2}$$

$$A_{en} = \frac{e_{no}}{e_{ni}} = \frac{1 + sR_f C_i}{1 + sR_f C_S}, \quad A_{in} = \frac{e_{ino}}{i_{ini}} = R_f, \quad A_{e_{nR}} = \frac{e_{nR}}{e_{nR}} = 1$$

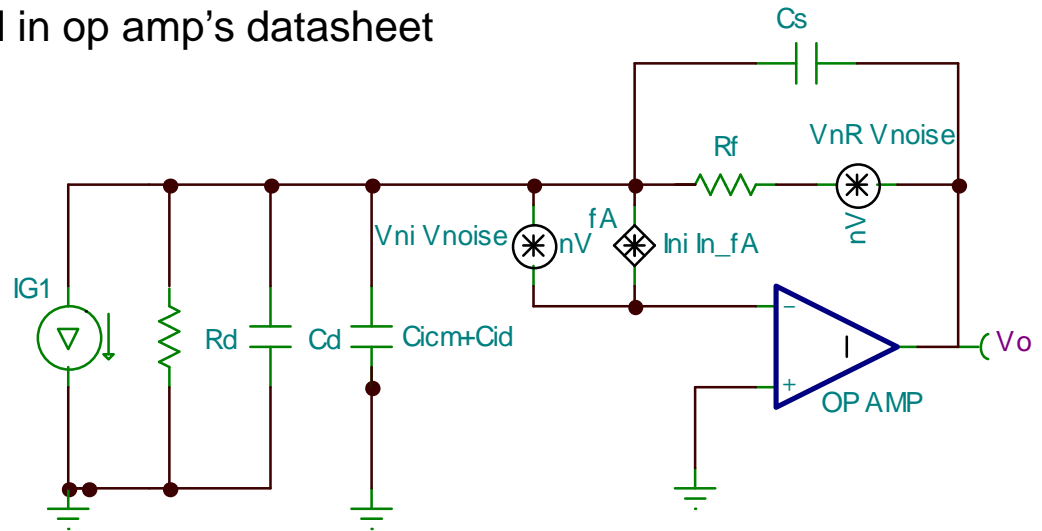$e_{noR} = \sqrt{4kTRf}$ ,  $e_{ni}$  and  $I_{ni}$  can find in op amp's datasheet






# Noise gain and noise bandwidth
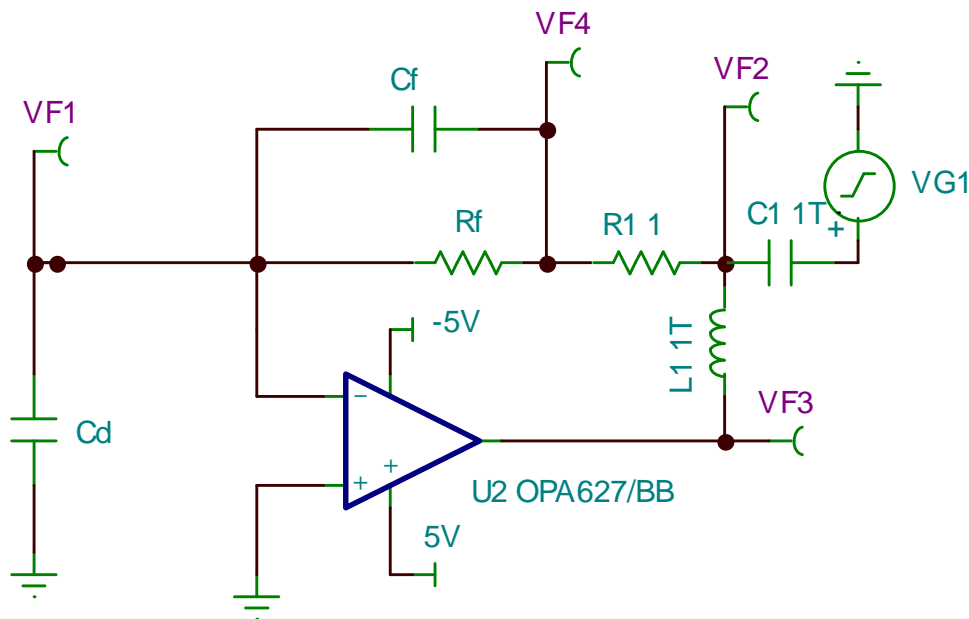
## We setup below simulation circuit:

In order to simulate I-V gain, we need add 1ohm resistor series with Rf and Cf. The voltage between 1ohm resistor present the current flow Rf and Cf. The voltage drop on Cf and Rf divide current to calculate amplifier's trans impedance. Amplifier's trans impedance is not exactly equals to I-V gain. But at low frequency, they are almost the same.




$$A_{ol} = -\frac{VF3}{VF1}$$

$$1/b = \frac{VF4}{VF1}$$

$$I-V_{gain} = \frac{VF4 - VF1}{VF2 - VF4}$$



# Noise gain and noise bandwidth

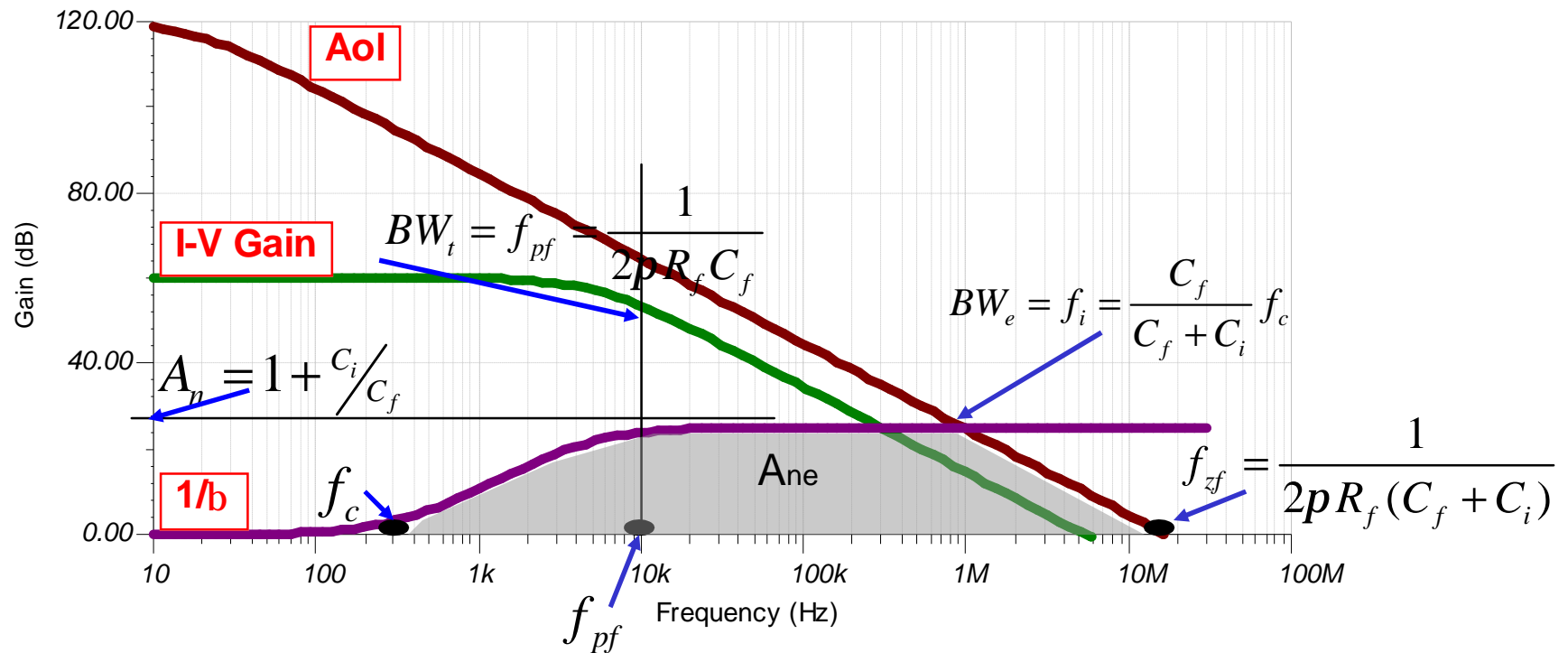




Photodiode parasitic capacitance and amplifier's input capacitance make circuit noise gain increase with frequency until leveled by compensation or stray capacitance and finally rolled off by the amplifier open-loop response.

From figure we can see the bandwidth of current noise, voltage noise are different. current noise and feedback resistor noise we should use  $BW_t$  in calculation while using  $f_{zf}$  in voltage noise calculation.



# Voltage Noise $e_{ni}$ , $e_{no}$ and $E_{no}$

INPUT VOLTAGE NOISE SPECTRAL DENSITY

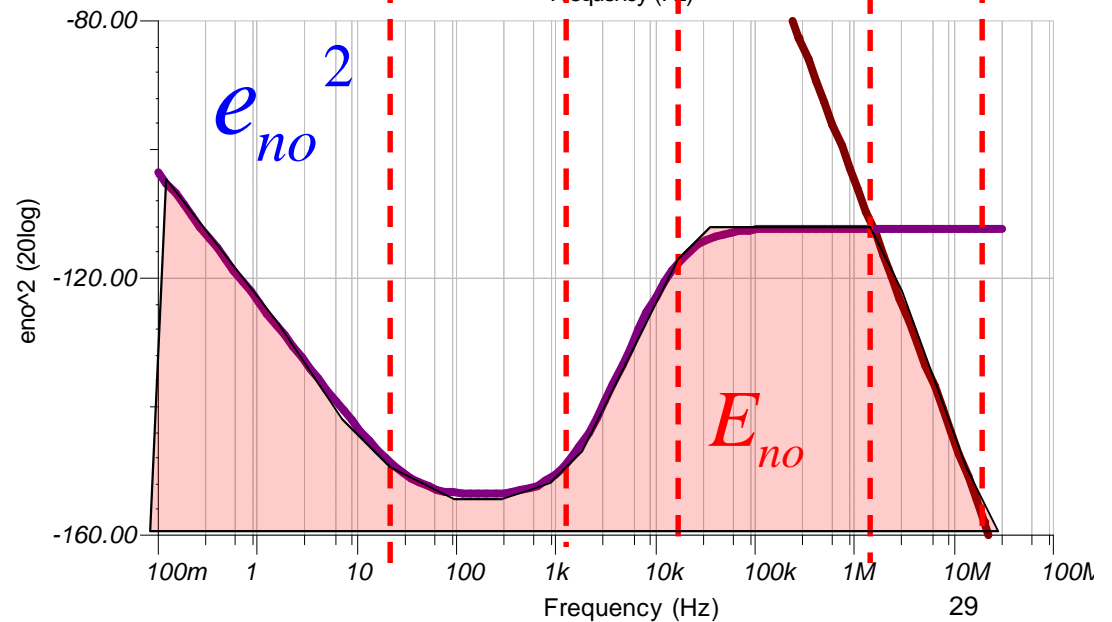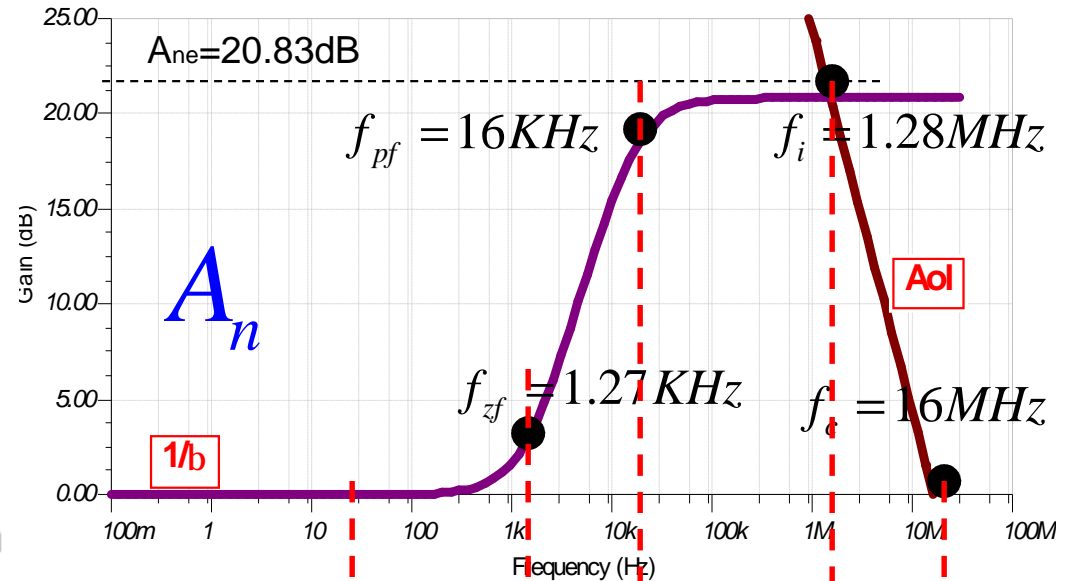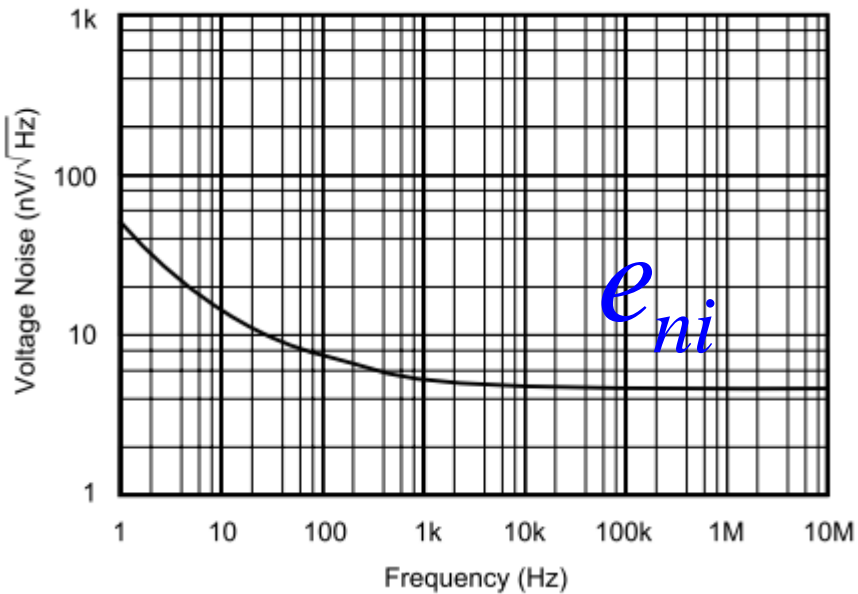


$$e_{no} = A_n e_{ni}$$

$$E_{no} = \int_0^{\infty} e_{no}^2 d_f = \int_0^{\infty} A_n^2 e_{ni}^2 d_f$$


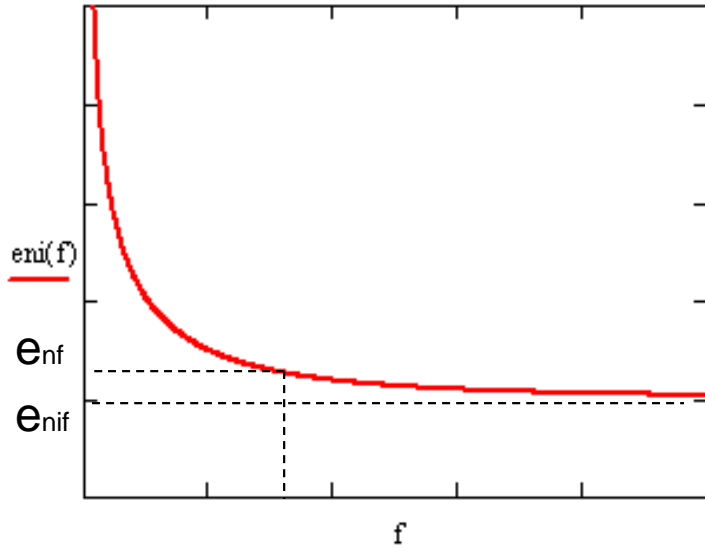
## Voltage Noise $e_{ni}$ , $e_{no}$ and $E_{no}$



Voltage noise expression is:

$$e_{ni} = e_{nif} \sqrt{1 + \frac{W_f}{s}}$$

$$W_f = 2p f_f$$

$f_r$  is corner frequency where noise density is  $\sqrt{2}$  times of flat value

The magnitude response is:  $e_{ni} = e_{nif} \sqrt[4]{1 + \left(\frac{f_f}{f}\right)^2}$

In the trans impedance amplifier circuit,  $C_i + C_f$  and  $R_f$  create a zero,  $C_f$  and  $R_f$  create a pole, at  $f_c \cdot \beta$  there is another pole. So the noise gain can be expressed as:

$$A_n = \frac{1 + \frac{s}{W_{zf}}}{\left(1 + \frac{s}{W_p}\right) \left(1 + \frac{s}{W_i}\right)}$$




# Voltage Noise $e_{ni}$ , $e_{no}$ and $E_{no}$

From  $A_n$  and  $e_{ni}$  expression we can express  $e_{no}$  as below:

$$e_{no} = A_n e_{ni} = \frac{\left(1 + \frac{s}{W_{zf}}\right) \sqrt{1 + \frac{W_f}{s}}}{\left(1 + \frac{s}{W_p}\right) \left(1 + \frac{s}{W_i}\right)} e_{nif}$$

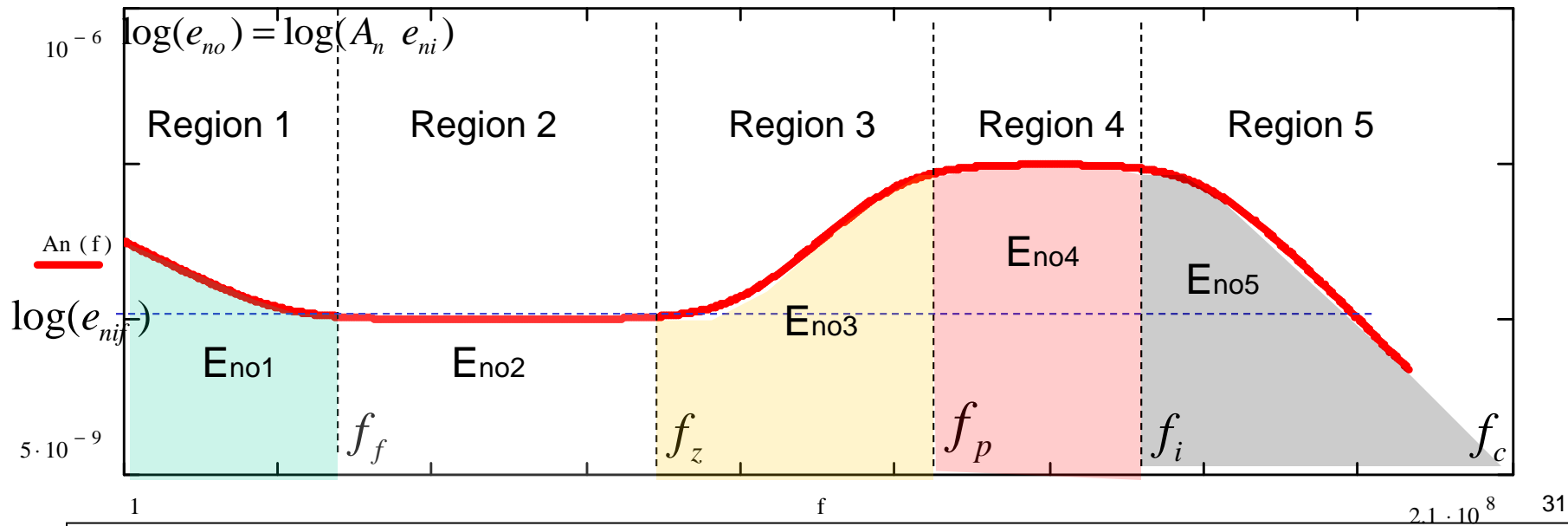Output noise density as below figure. Total output noise is integration of  $e_{no}$ . We separate the noise density into five regions for easy calculation.





## Voltage Noise $e_{ni}$ , $e_{no}$ and $E_{no}$

Region 1 noise: 
$$E_{noe1}^2 = \int_{f_L}^{f_f} \frac{e_{nif}^2 \cdot f_f}{f} d_f = e_{nif}^2 f_f \ln \frac{f_f}{f_L}$$

Region 2 noise: 
$$E_{noe2}^2 = \int_{f_f}^{f_z} e_{nif}^2 d_f = e_{nif}^2 (f_z - f_f)$$

Region 3 noise: 
$$E_{noe3}^2 = \int_{f_z}^{f_p} \frac{e_{nif}^2 \cdot f^2}{f_z^2} d_f = \left( \frac{e_{nif}}{f_z} \right)^2 \frac{f_p^3 - f_z^3}{3}$$

Region 4 noise: 
$$E_{noe4}^2 = \int_{f_p}^{f_i} \left( \frac{e_{nif}}{b} \right)^2 d_f = \left( e_{nif} \cdot \frac{C_i + C_f}{C_f} \right)^2 (f_i - f_p)$$


Region 5 noise: 
$$E_{noe5}^2 = \int_{f_i}^{\infty} \left( \frac{e_{nif} f_c}{f} \right)^2 d_f = \frac{(e_{nif} f_c)^2}{f_i}$$

**Total voltage noise:** 
$$E_{noe}^2 = E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2$$





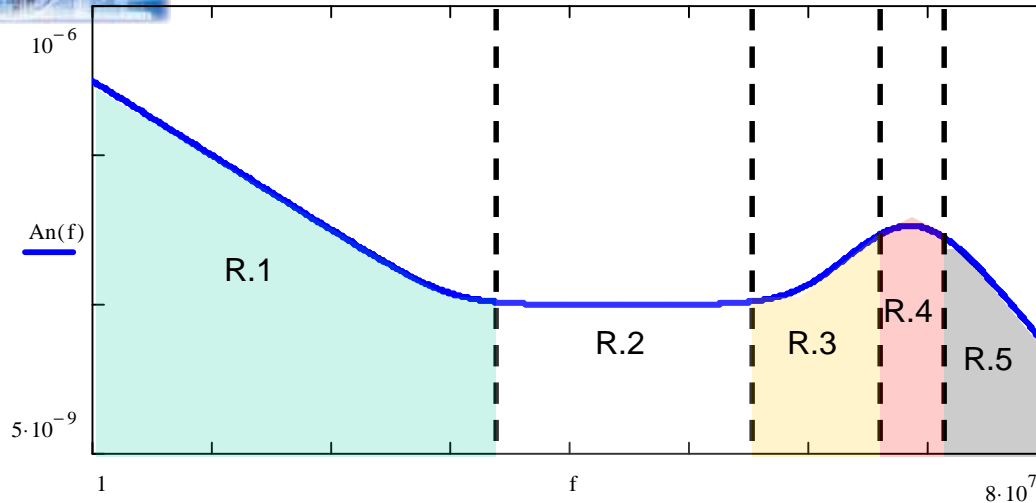
# Voltage Noise $e_{ni}$ , $e_{no}$ and $E_{no}$



$e_{no}$   
Log scale

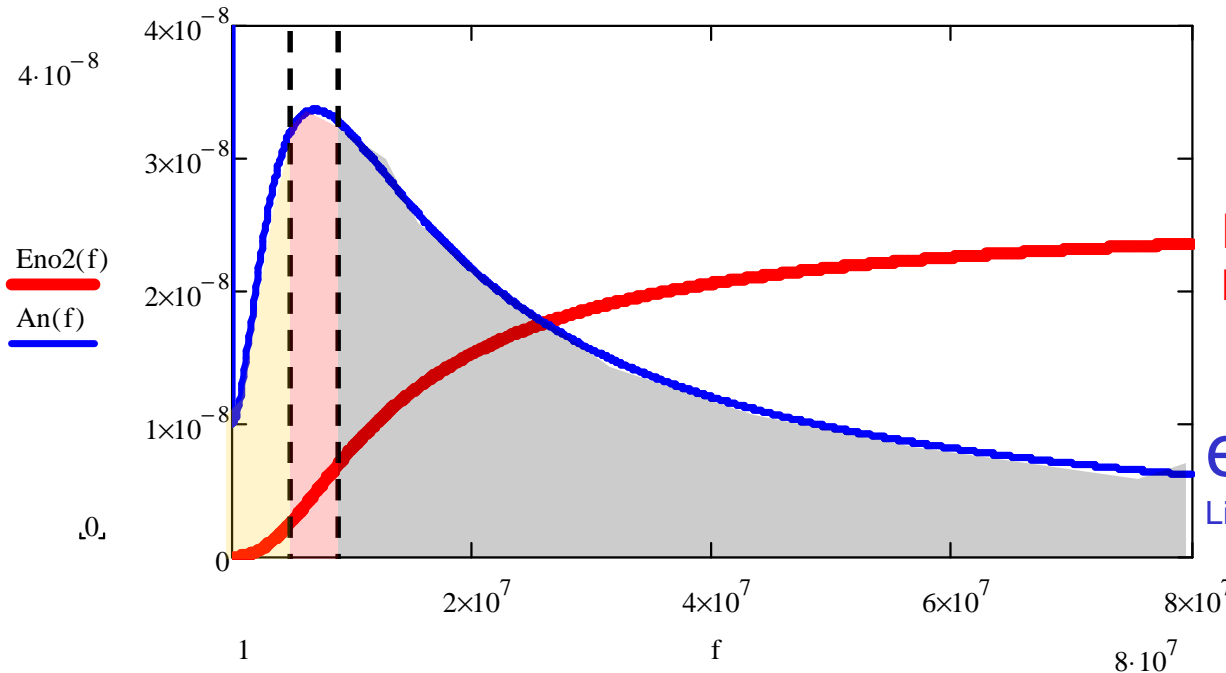Two left figures obviously present: although  $1/f$  noise density is very large in noise density, but noise gain and bandwidth make region (3,4,5) contribute to output noise ( $E_{no}$ ) most.




$E_{no}^2$   
Linear scale

$e_{no}$   
Linear scale

Noise gain effect region is controlled by  $C_i, C_f, R_f, f_c$ . Compensation design and op amp selection is critical for noise characters.




# Resistor Noise and Current Noise

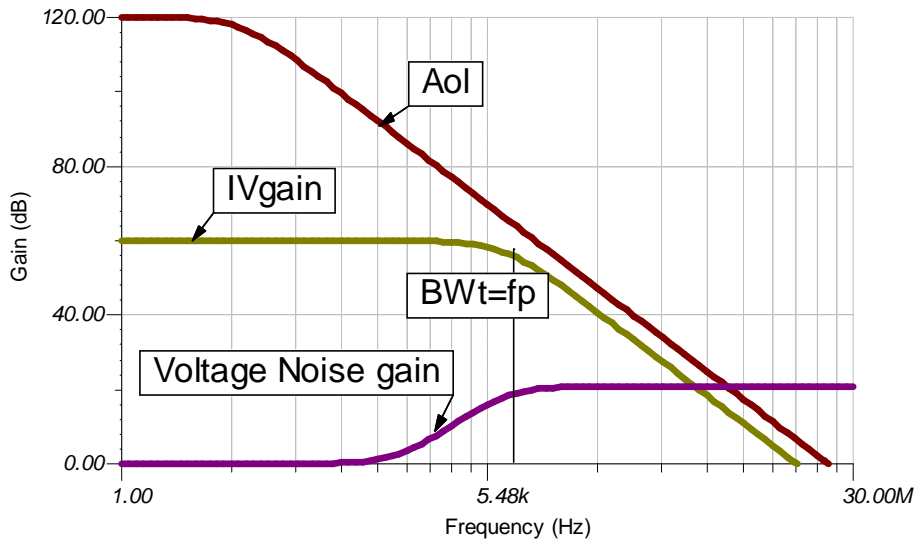

Current noise and resistor noise are pass trans impedance. IV frequency curve is LP filter.

$$BW_n = (f_H)(K_n) \quad \text{Effective Noise Bandwidth}$$


| Poles | $K_n$        |
|-------|--------------|
| 1     | $\pi/2=1.57$ |
| 2     | 1.22         |
| 3     | 1.16         |

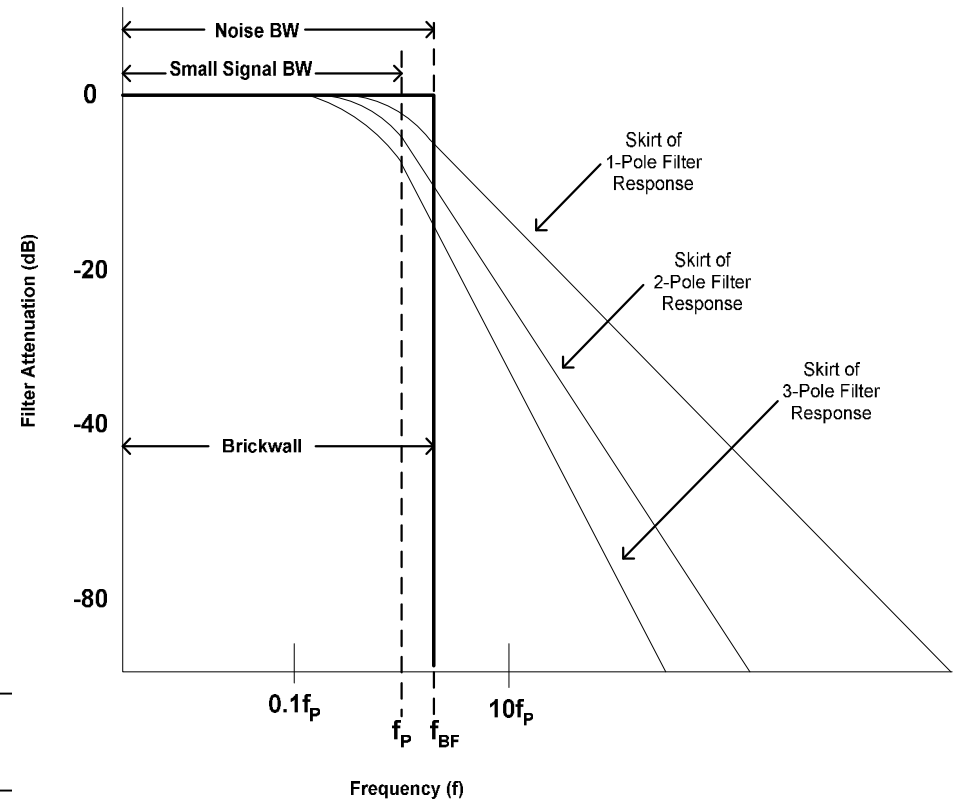

$$E_{noR} = \sqrt{4KTR_f BW_n} = \sqrt{2pKTR_f f_p}$$

$$E_{noI} = i_{ni} R_f \sqrt{\frac{p}{2} f_p}$$

$i_{ni}$  is current noise density

 




# Noise Hands calculation

We have a amplifier with 500Mhz GBW, 120dB open loop gain, noise specific as below:

|                                   |  |                       |     |  |     |  |                              |
|-----------------------------------|--|-----------------------|-----|--|-----|--|------------------------------|
| <b>NOISE</b>                      |  |                       |     |  |     |  |                              |
| Input Voltage Noise               |  |                       |     |  |     |  |                              |
| Noise Density: f = 10Hz           |  | 15                    | 40  |  | 20  |  | nV/ $\sqrt{\text{Hz}}$       |
| f = 100Hz                         |  | 8                     | 20  |  | 10  |  | nV/ $\sqrt{\text{Hz}}$       |
| f = 1kHz                          |  | 5.2                   | 8   |  | 5.6 |  | nV/ $\sqrt{\text{Hz}}$       |
| f = 10kHz                         |  | 4.5                   | 6   |  | 4.8 |  | nV/ $\sqrt{\text{Hz}}$       |
| Voltage Noise, BW = 0.1Hz to 10Hz |  | 0.6                   | 1.6 |  | 0.8 |  | $\mu\text{Vp-p}$             |
| Input Bias Current Noise          |  |                       |     |  |     |  |                              |
| Noise Density, f = 100Hz          |  | 1.6                   | 2.5 |  | 2.5 |  | fA/ $\sqrt{\text{Hz}}$       |
| Current Noise, BW = 0.1Hz to 10Hz |  | 30                    | 60  |  | 48  |  | fAp-p                        |
| <b>INPUT IMPEDANCE</b>            |  |                       |     |  |     |  |                              |
| Differential                      |  | $10^{13} \parallel 8$ |     |  | *   |  | $\Omega \parallel \text{pF}$ |
| Common-Mode                       |  | $10^{13} \parallel 7$ |     |  | *   |  | $\Omega \parallel \text{pF}$ |

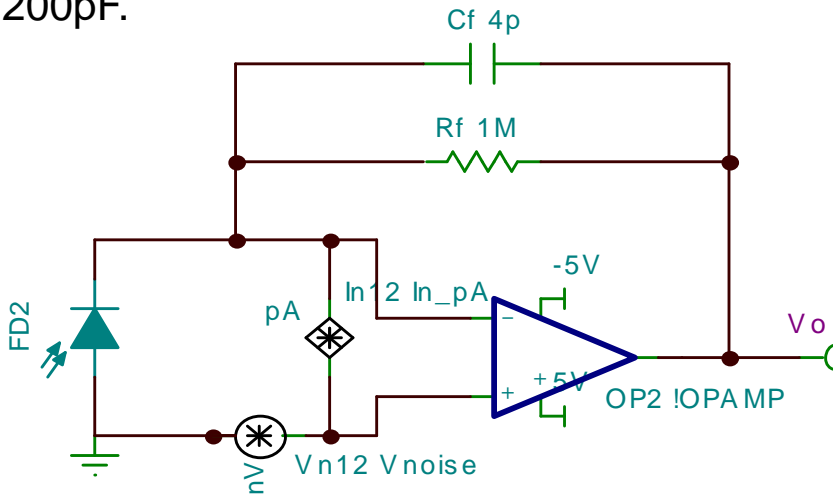The circuit total input capacitor is 200pF.





## Noise Hands calculation

$$C_i = 200\text{pF}, C_f = 4\text{pF}, f_f = 100\text{Hz}, R_f = 1\text{M}\Omega, b = \frac{C_f}{C_i + C_f} = \frac{4}{200 + 4} = 0.02, e_{nif} = 4.5 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

$$f_z = \frac{1}{2\pi R_f (C_i + C_f)} = 780\text{Hz}, f_p = \frac{1}{2\pi R_f C_f} = 40\text{kHz}, f_i = b f_c = 9.8\text{MHz}$$

$$E_{noe1} = \sqrt{e_{nif}^2 f_f \ln \frac{f_f}{f_L}} = 118.3\text{nV}$$

$$E_{noe2} = \sqrt{e_{nif}^2 (f_z - f_f)} = 117.4\text{nV}$$

$$E_{noe3} = \sqrt{\left(\frac{e_{nif}}{f_z}\right)^2 \frac{f_p^3 - f_z^3}{3}} = 26.43\text{mV}$$

$$E_{noe4} = \sqrt{\left(e_{nif} \cdot \frac{C_i + C_f}{C_f}\right)^2 (f_i - f_p)} = 717.1\text{mV}$$

$$E_{noe5} = \sqrt{\frac{(e_{nif} f_c)^2}{f_i}} = 718.6\text{mV}$$



# Noise Hands calculation

Output voltage noise, resistor noise and current noise are:

$$E_{noe} = \sqrt{E_{no1}^2 + E_{no2}^2 + E_{no3}^2 + E_{no4}^2 + E_{no5}^2} = 1.016mV$$


$$E_{noR} = \sqrt{2pKTR_f f_p} = 32.17mV$$

$$E_{noi} = i_{ni} R_f \sqrt{\frac{p}{2} f_p} = 0.4mV$$

Total output noise is:  $E_{no} = \sqrt{(E_{noR})^2 + (E_{noi})^2 + (E_{noe})^2} = 1.016mV$

We can see in this circuit, output noise is mainly contributed by voltage noise.

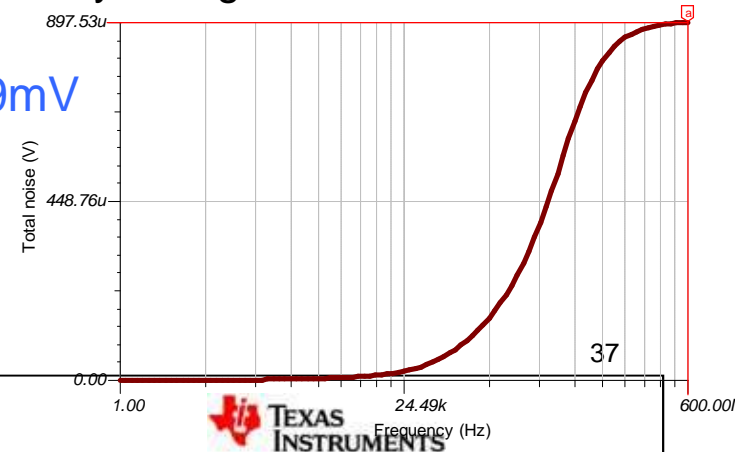Tina Simulation Result: Total output noise  $E_{no}=0.9mV$





# Calculation Accuracy

There are 0.1 mV error in hands calculation and TINA simulation. As Noise is mainly contributed by voltage noise, we compared TINA simulation output noise density and Our noise model density as below:

| Unit : nV/ $\sqrt{\text{Hz}}$ | 1Hz   | 260Hz  | 600KHz | 16MHz  | 70MHz | 140MHz | 200MHz |
|-------------------------------|-------|--------|--------|--------|-------|--------|--------|
| TINA                          | 137.2 | 128.88 | 227.5  | 121.71 | 31.89 | 15.82  | 10.86  |
| Calculation Model             | 45    | 4.91   | 228.6  | 119.9  | 31.83 | 16.03  | 11.24  |


At high frequency two curve values are very close to each other, At low frequency the noise density is different on resistor and current noise. Resistor noise density is 128nV/ $\sqrt{\text{Hz}}$ .

Integrate the calculation mode from 0.1Hz to  $\infty$ .


$$E_{oe}' = \sqrt{\int_{0.1\text{Hz}}^{\infty} \left| \frac{\left(1 + \frac{s}{w_{zf}}\right) \sqrt{1 + \frac{w_f}{s}}}{\left(1 + \frac{s}{w_p}\right) \left(1 + \frac{s}{w_i}\right)} e_{nif} \right|^2 df} = 0.8947\text{mV}$$

$$s = jw$$

TINA Simulated output noise density

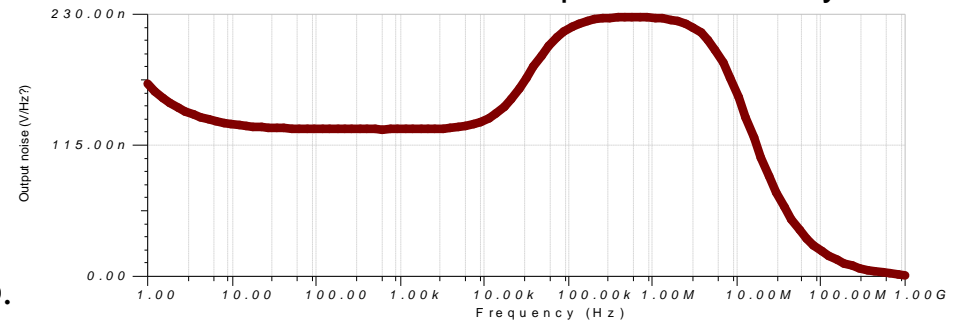

Calculation model noise density

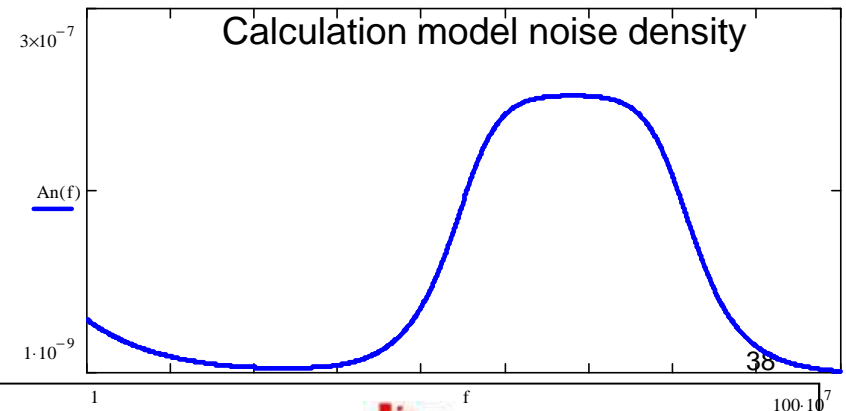



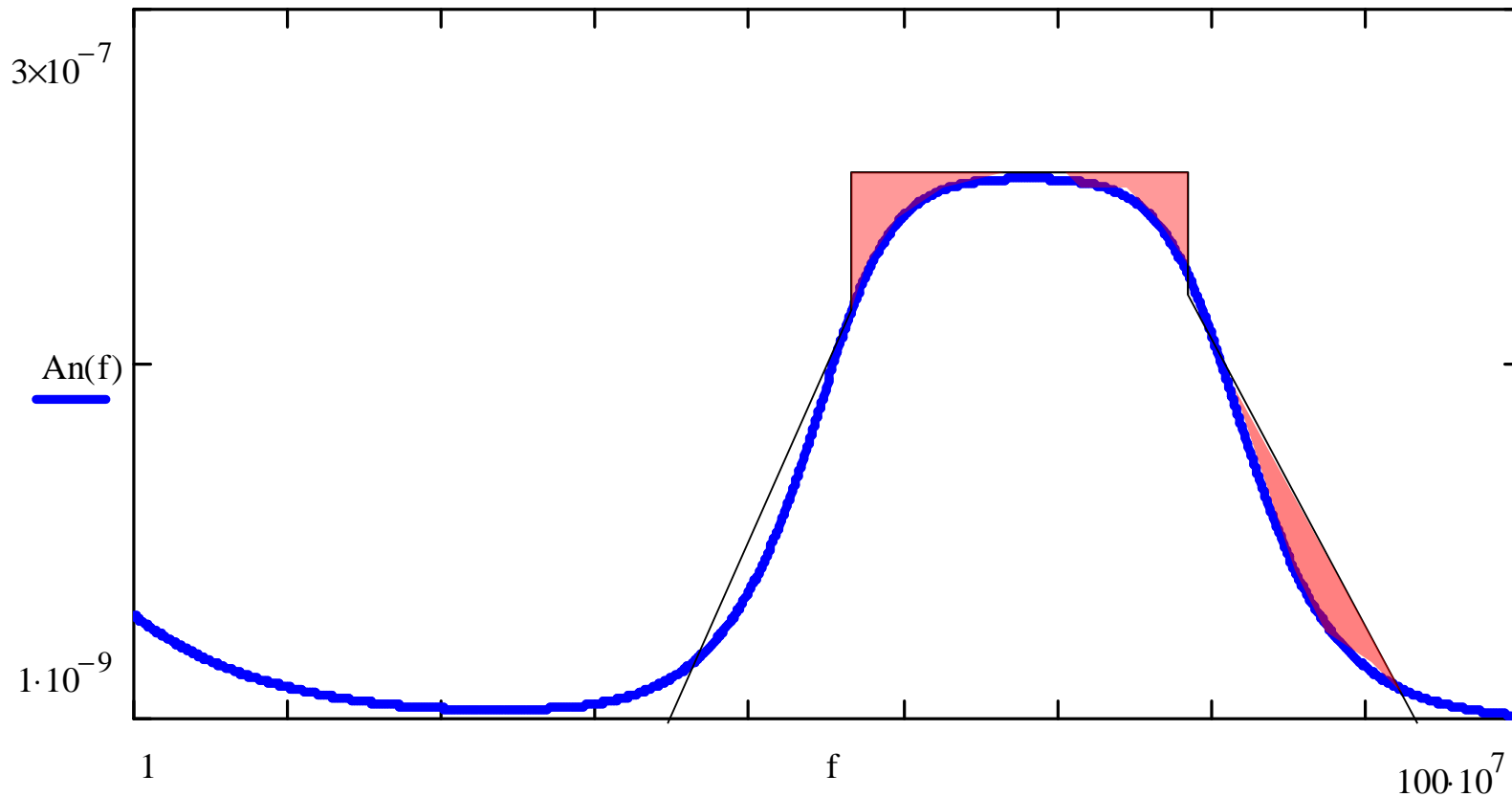
# Calculation Accuracy

Integration value is very close to TINA simulation value, which illustrate the calculation noise expression model is accurate. We simplified the curve especially corner frequency's 3dB attenuation.

In low noise gain and wide fp-fz circuit, the error will be more significant





# Calculation Accuracy

Five different region's hand calculation errors as below. Obviously, the error is mainly comes from Region4 and Rgeion5

$$E_{noe1} = \sqrt{e_{nif}^2 f_f \ln \frac{f_f}{f_L} - \int_{f_L}^{f_f} (A_n e_{ni})^2 d_f} = 65nV$$

$$E_{noe2} = \sqrt{e_{nif}^2 (f_z - f_f) - \int_{f_f}^{f_z} (A_n e_{ni})^2 d_f} = 78nV$$

$$E_{noe3} = \sqrt{\left(\frac{e_{nif}}{f_z}\right)^2 \frac{f_p^3 - f_z^3}{3} - \int_{f_z}^{f_p} (A_n e_{ni})^2 d_f} = 16mV$$

$$E_{noe4} = \sqrt{\left(e_{nif} \cdot \frac{C_i + C_f}{C_f}\right)^2 (f_i - f_p) - \int_{f_p}^{f_i} (A_n e_{ni})^2 d_f} = 0.335mV$$

$$E_{noe5} = \sqrt{\frac{(e_{nif} f_c)^2}{f_i} - \int_{f_i}^{\infty} (A_n e_{ni})^2 d_f} = 0.26mV$$






# Noise Reduction


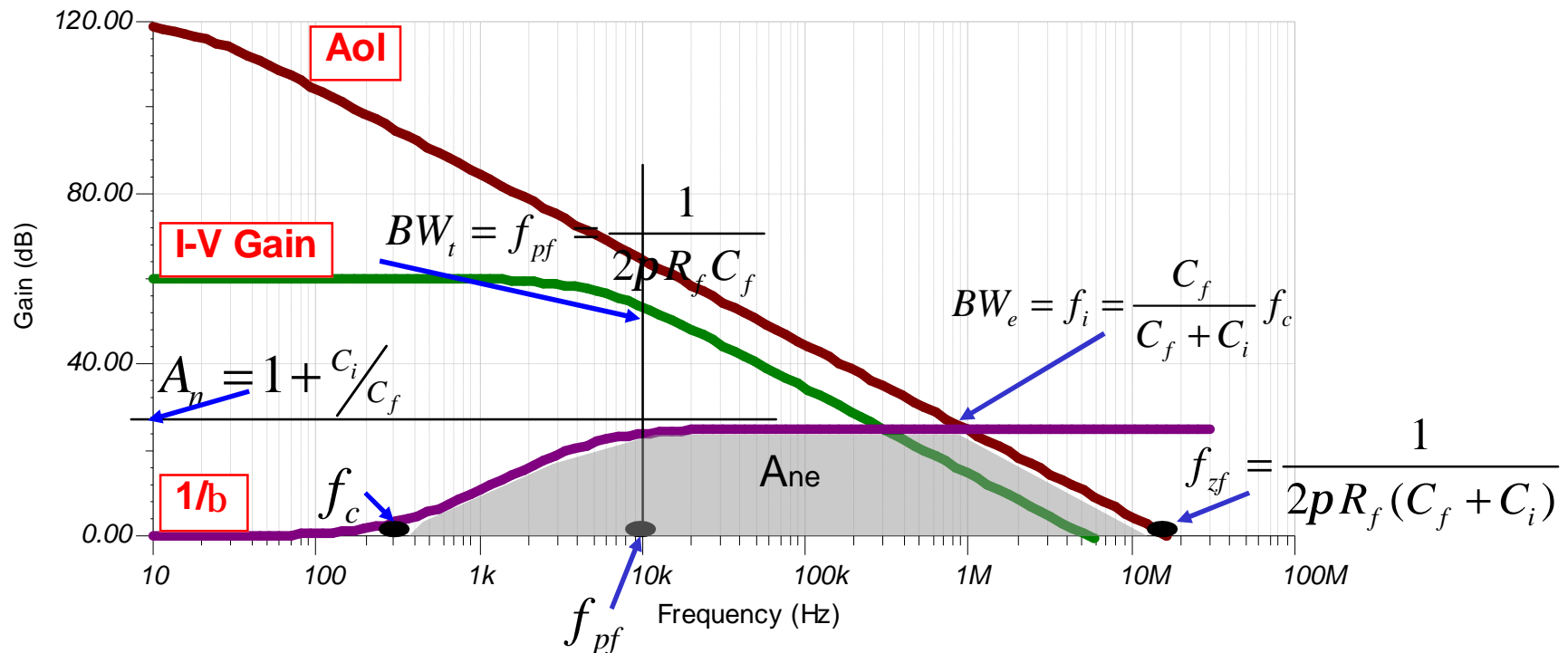
# Noise Reduction

As analyzed, trans impedance amplifier's noise mainly comes from Region 3,4,5 especially region 4 and 5. We have two guide line to reduce noise:

- Reduce noise gain
- Reduce noise bandwidth






## Noise Reduction

As analyzed, trans impedance amplifier's noise mainly comes from Region 3,4,5 especially region 4 and 5. We have two guide lines to reduce noise:

- I Reduce noise gain
- I Reduce noise bandwidth

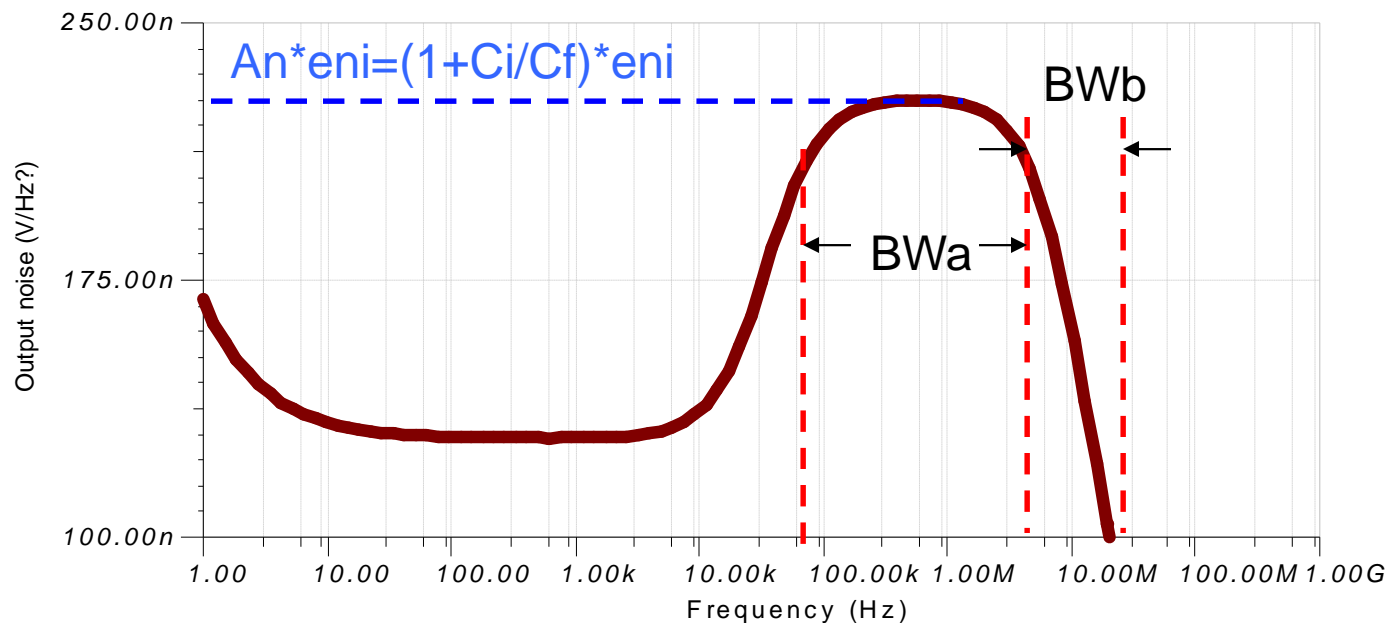In trans impedance amplifier, peak noise gain equals to  $1+C_i/C_f$ . We select a larger feedback capacitor can effective reduce noise.





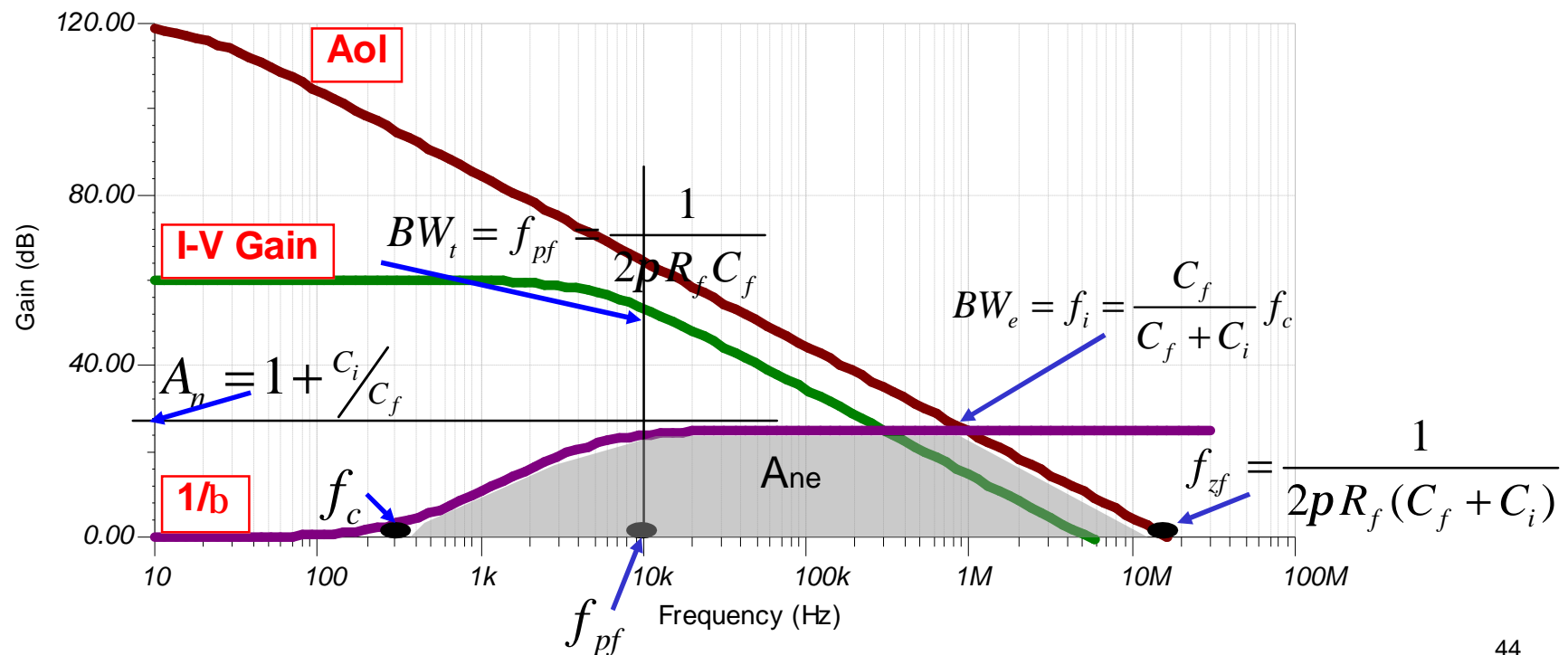
# Noise Reduction


Signal bandwidth  $BW_t = 1/(2\pi R_f C_f)$ , when we increase feedback capacitor signal bandwidth  $BW_t$  also decreased, noise bandwidth  $BW_e$  increase. We need synthetically consider whether the total noise is effective reduced or not.

However, as long as bandwidth requirements permit, use a suitable capacitor offers the simplest method to reduce noise.






# Noise Reduction

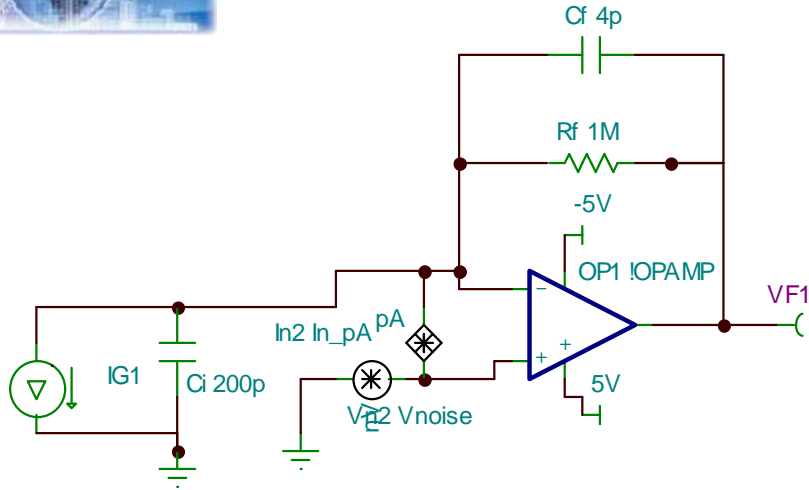


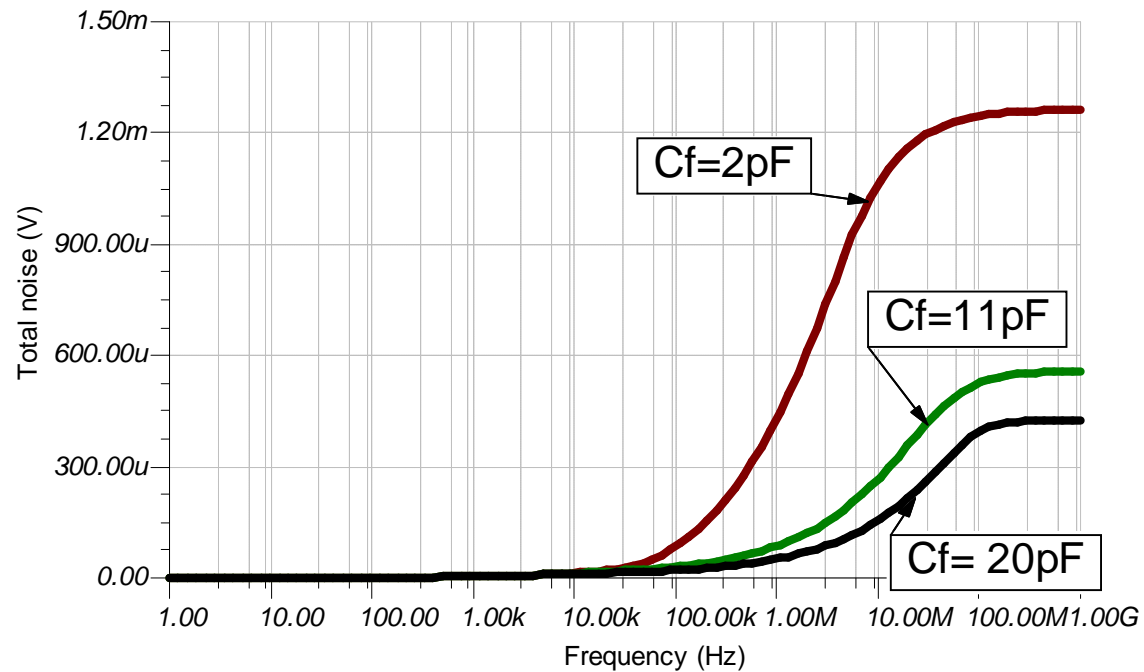Using the op amp we just analyzed, the simulation circuit as left. We select three feedback capacitor value 2pF, 11pF, 20pF. Output noise is obviously decrease with feedback capacitance value increase.







# Noise Reduction, Serial Resistor

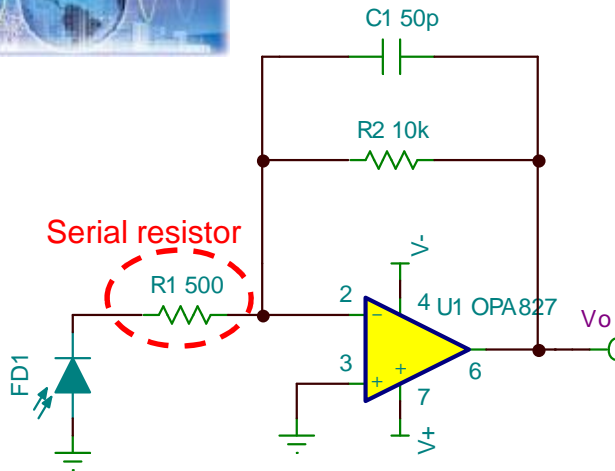

Use a resistor R1 serial with photodiode as figure (a), The noise gain is changed by the serial resistor R1. A noise gain curve pole will produced by the serial resistor and photodiode capacitor C3 at  $1/(2\pi \cdot R2 \cdot C3)$ , as figure (b). The total output noise is apparently reduced.

But when current flow R1 will also modulate non-inverting bias voltage across photodiode which will increase dark current and affect AC specifics like linearity.

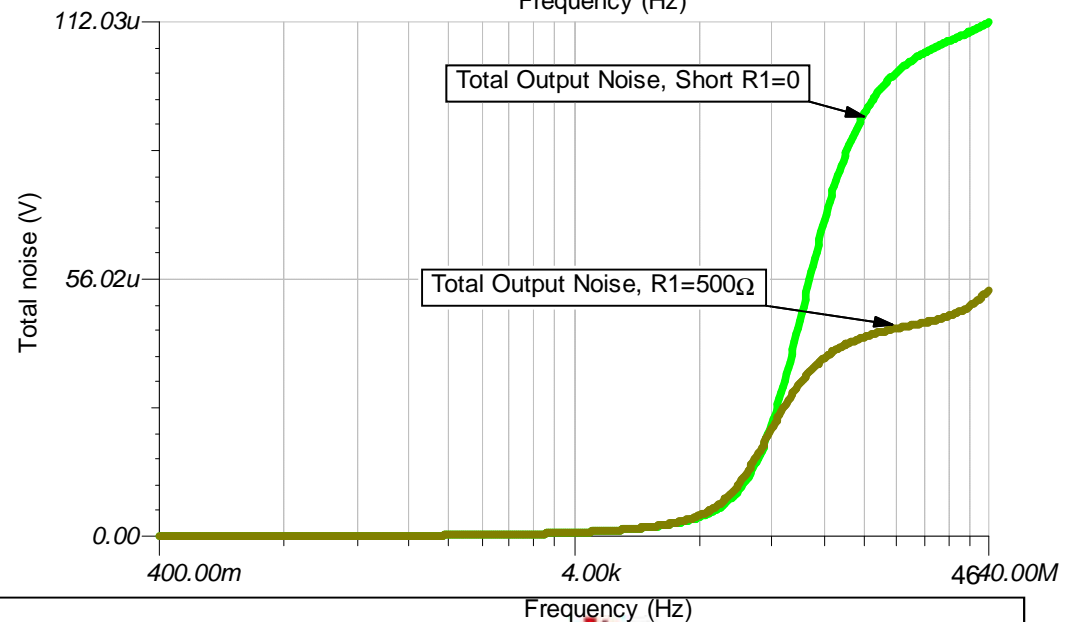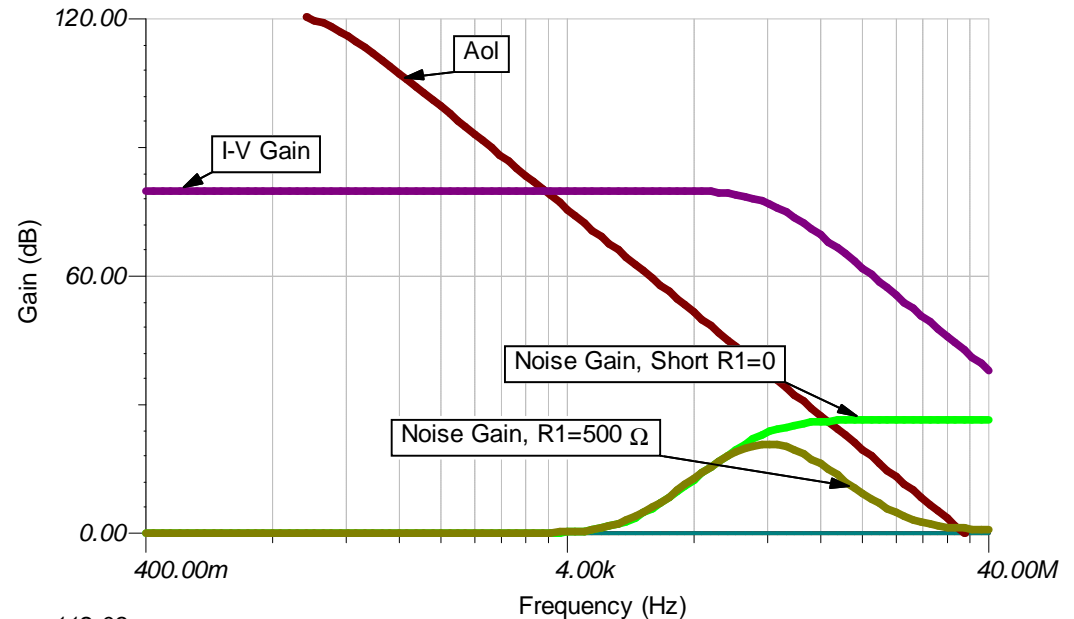So a the resistance need to be small. This requires evaluation of specific application conditions before adding Rc.





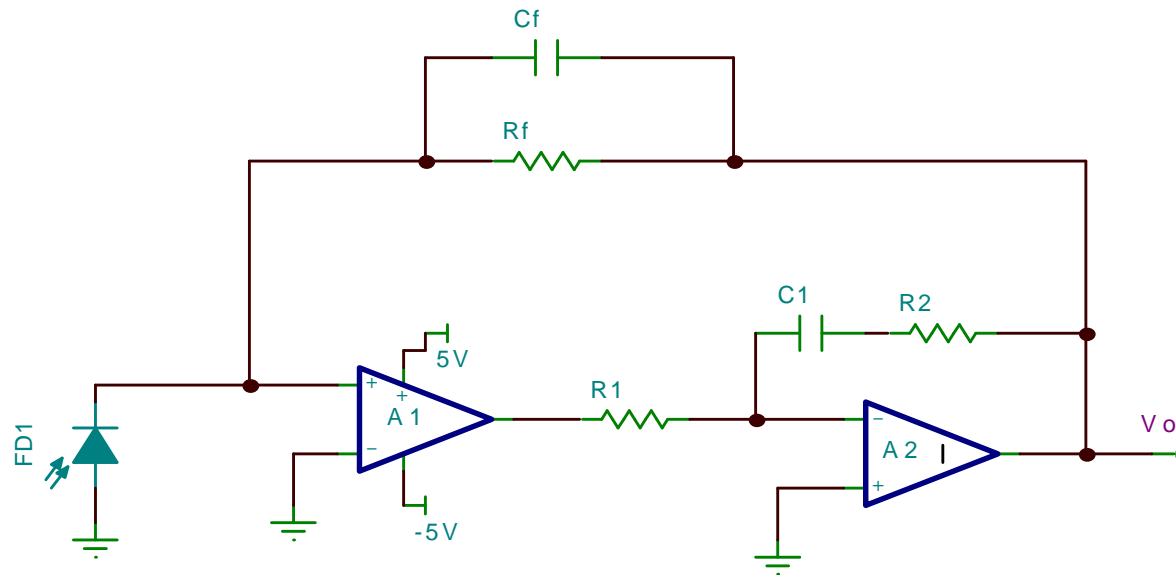
# Noise Reduction

Another way to reduce noise is to reduce noise bandwidth. Below circuit can reduce noise bandwidth while not change signal bandwidth. It uses two amplifiers to build up a composite op amp which has modified Aol curve. We can modify the Aol curve by adjusting R1, R2 and C2.



At low frequencies, C1 blocks A2's local feedback, and this amplifier contributes its full open loop gain to composite feedback. At intermediate frequencies, the integrator feedback formed by R1 and C1 reduces the A2 gain support in a transition to the attenuator mode. At high frequencies, C1 becomes short circuit, A2 circuit's gain stable at  $-R2/R1$ . Make  $R2 > R1$  to produce desired high-frequency attenuation.




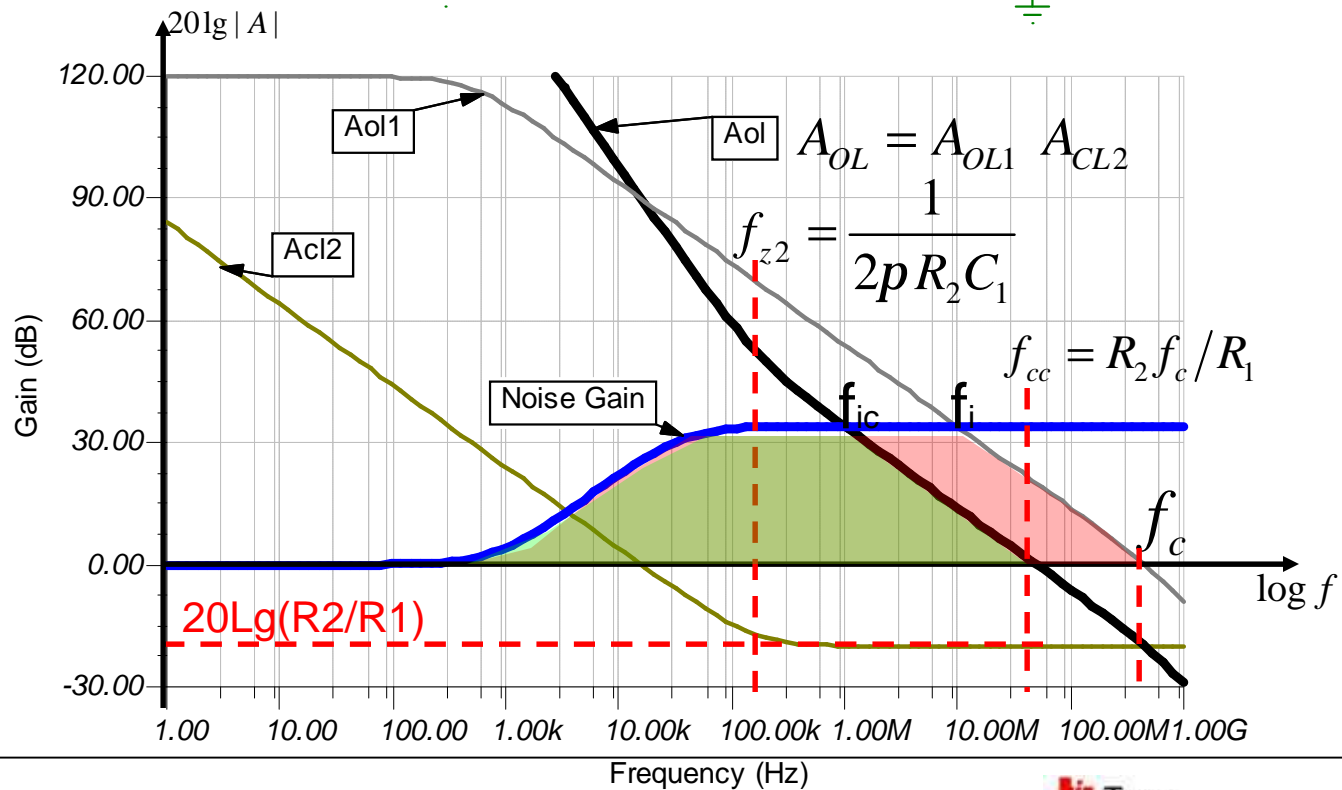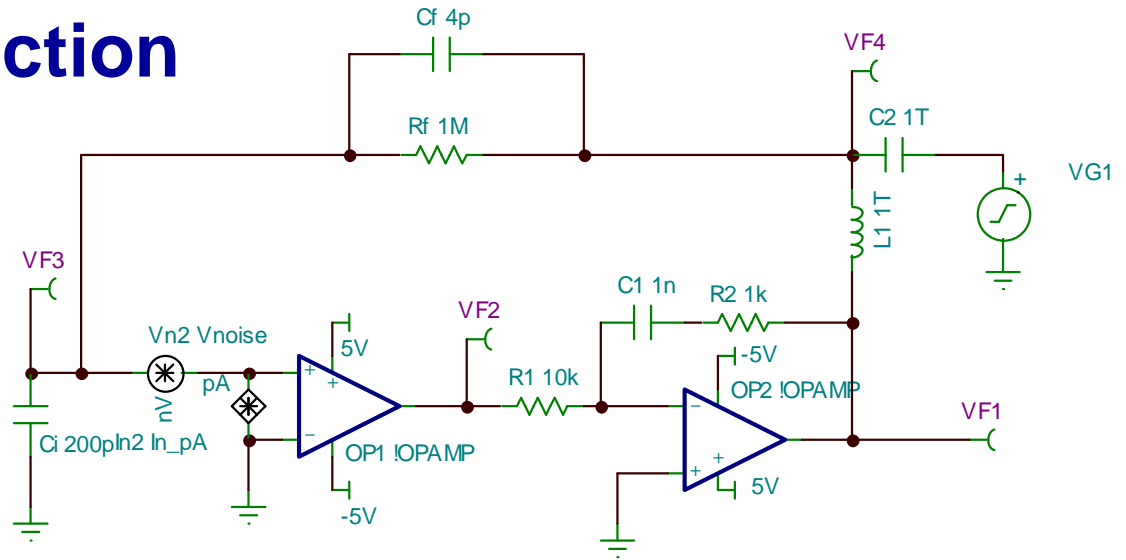
# Noise Reduction

Using the circuit on right for TINA simulation. the noise bandwidth has been changed smaller. We set R1, R2 and C1 to realize Aol modify.







# Noise Reduction

How to optimize R1, R2 and C1?

R2/R1 factor produces a compromise between noise and signal bandwidths through placement of  $f_{ic}$ . Decrease R2/R1 factor will move Aol curve left, expending the shaded area removed from the noise response. However, this move also brings a new signal bandwidth limit into significance. In compromise, setting  $f_{ic}=f_{pf}$  makes the two limits coincident for the maximum possible noise reduction with out a major reduction of signal bandwidth.

The optimized value is:

$$\frac{R_2}{R_1} = \frac{f_{pf}}{b f_{cf}} \quad C_1 = \frac{10R_f}{R_2}$$




We can also use a active filter following trans impedance opamp for noise filtering and composite noise Aol modify, but added op amp also added it's noise in to the circuit. Composite solution attenuated op2's noise by op1's Aol, but series filter op amp added it's noise in to signal chain directly.


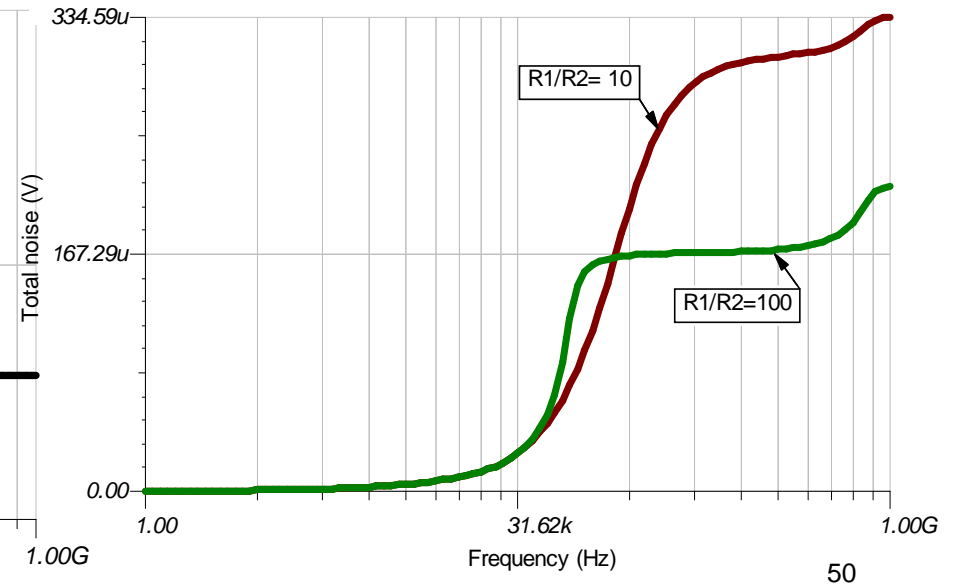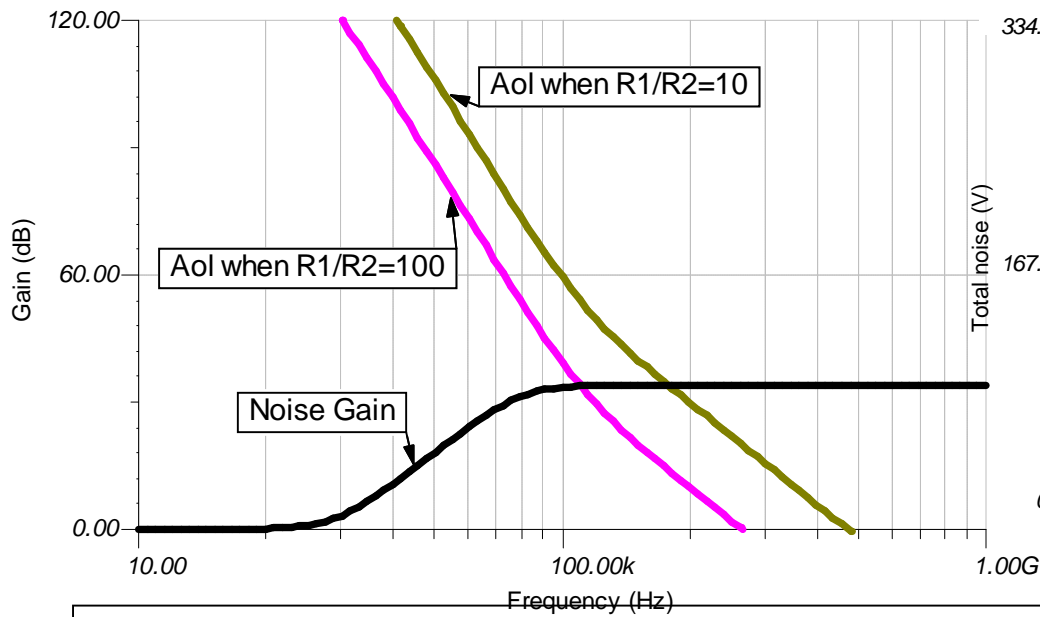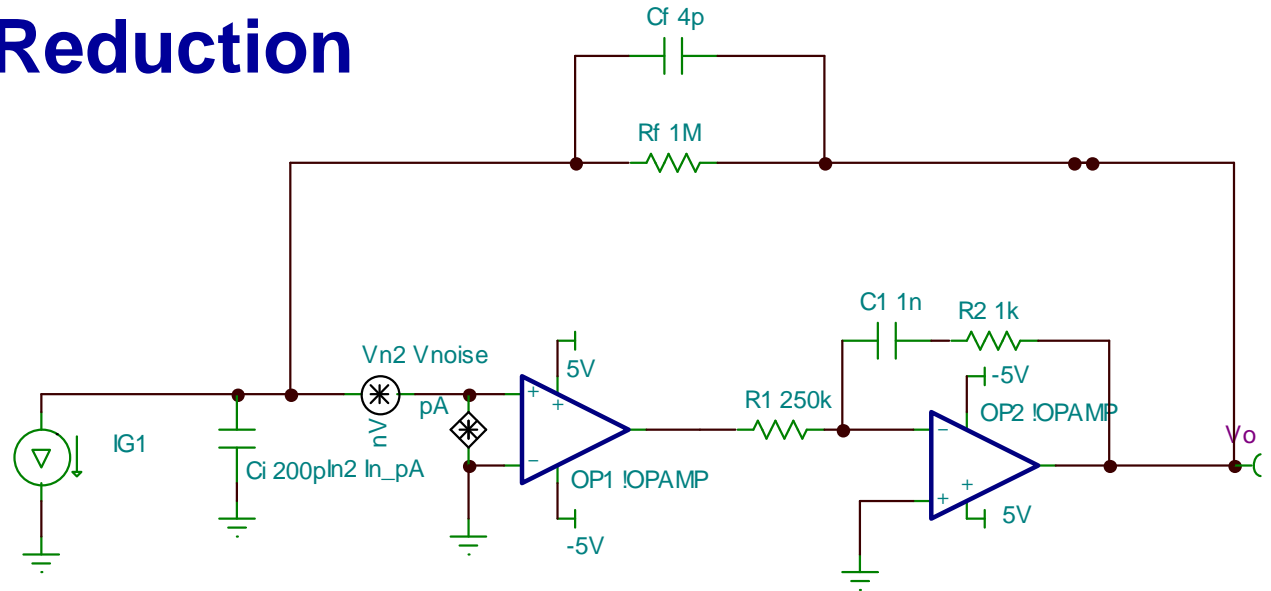
# Noise Reduction

Use right circuit for noise simulation.  
Stepping R1 as 10K and 100K, the total output noise obviously different.

Decrease R2/R1 factor will move Aol curve left, expending the shaded area removed from the noise response





# Transimpedance amplifier Noise Test, Calculation and Simulation




# Test Equipment

- Tektronix DPO 4034 Oscilloscope
- Hewlett Packard 3458A Digital Multimeter
- Agilent 35670A dynamic Signal Analyzer
- Agilent 4395A Spectrum Analyzer



# Tektronix DPO 4034 Oscilloscope

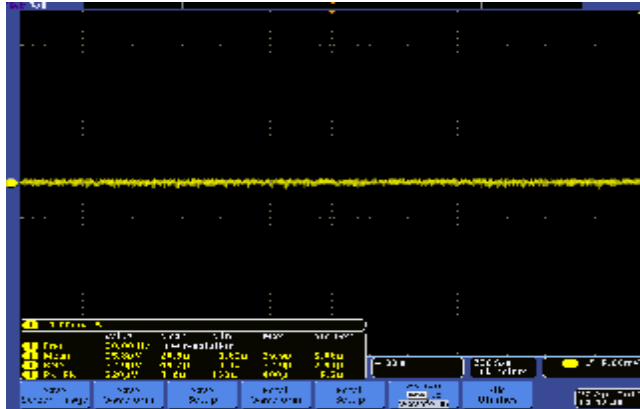

**STDEV:** 48uV  
**P-P:** 6.6\*STDEV=319uV  
**40s P-P:** 320uV

- 1) Set DC couple, 20MHz bandwidth limits;
- 2) Use BNC short Cap to short input channel at panel to measure background noise;
- 3) Use BNC wire to connect board and scope;



## Hewlett Packard 3458A Digital Multimeter

- 1) True RMS Meter;
- 2) SETACV RNDM mode;
- 3) 20~10MHz Bandwidth;
- 4) 0.1% accuracy;
- 5) Maximum Resolution 1uV





# Spectrum Analyzer


## Agilent 35670A dynamic Signal Analyzer

- 1, Frequency Range: 122uHz~102.4KHz;
- 2, Noise floor: 20nV/sqrt-Hz
- 3, 90dB Dynamic range
- 4, Input Impedance: 1MΩ



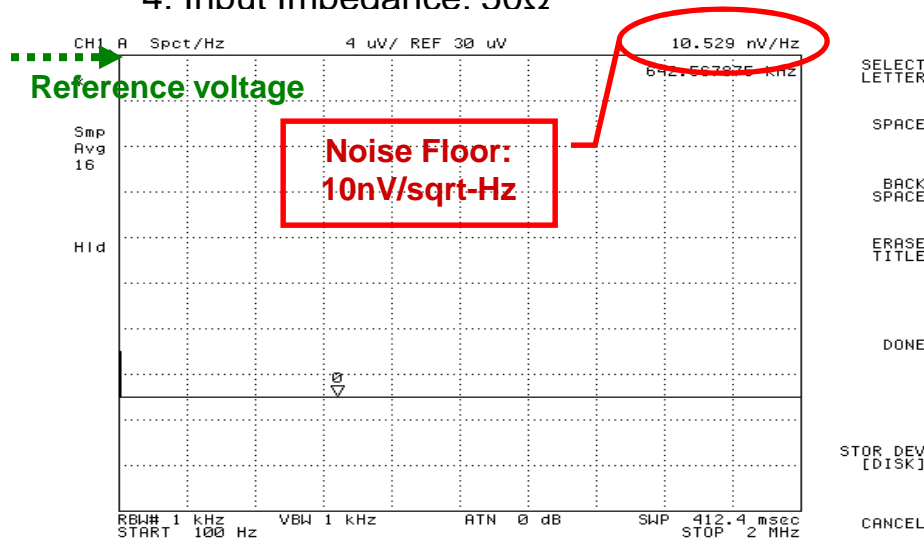
## Agilent 4395A spectrum analyzer

- 1, Frequency Range: 10Hz~500MHz;
- 2, Noise floor: 10nV/sqrt-Hz, but min reference voltage is about 2uV, so it can only present more than hundreds nano density
4. Input Impedance: 50Ω





# Test in Can

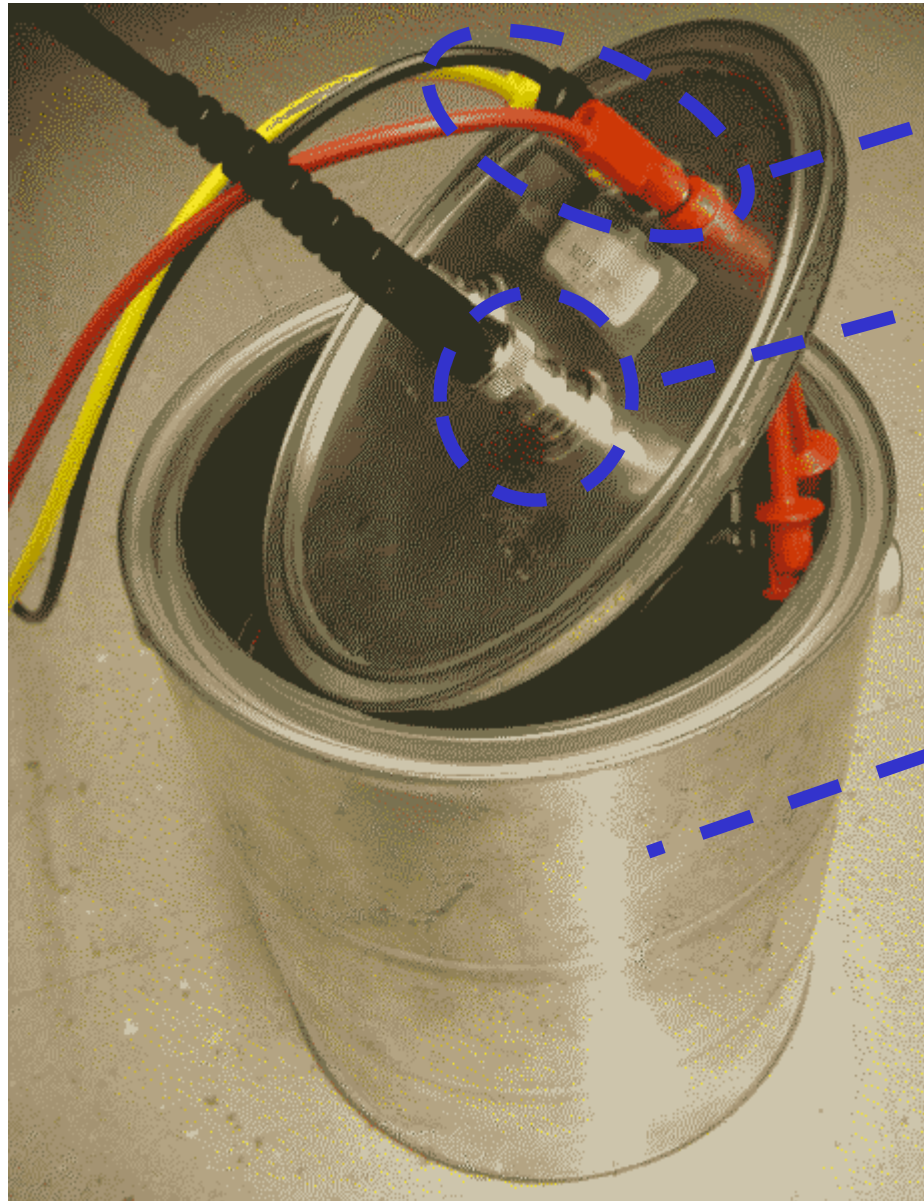

Power Supply  
Vcc, Vss, GND

Input & Output BNC  
connectors

Shield






# Post Amplifier




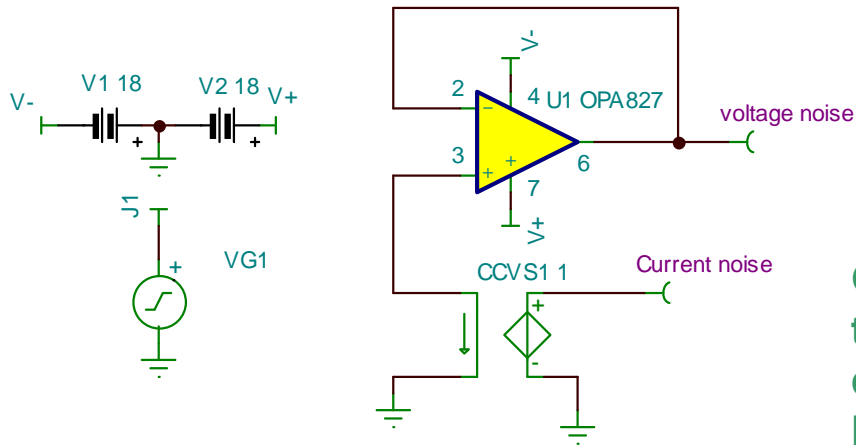
# OPA827

- Low Noise Voltage:  $4\text{nV}/\sqrt{\text{Hz}}$  at 1kHz
- Low Offset Voltage:  $150\mu\text{V}$  max
- JFET Input:  $I_B = 15\text{pA}$  typ
- Wide Bandwidth:  $22\text{MHz}$



In most transimpedance circuit, amplifier GBW determines noise bandwidth. If we need test the opa827 transimpedance amplifier circuit, we **must ensure** signal chain BW is not less than 22MHz.

The noise performance is the same as datasheet.



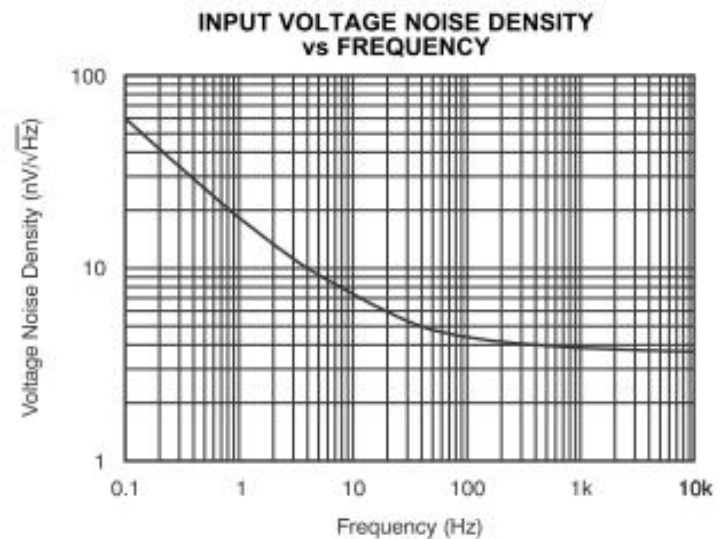




Figure 1.

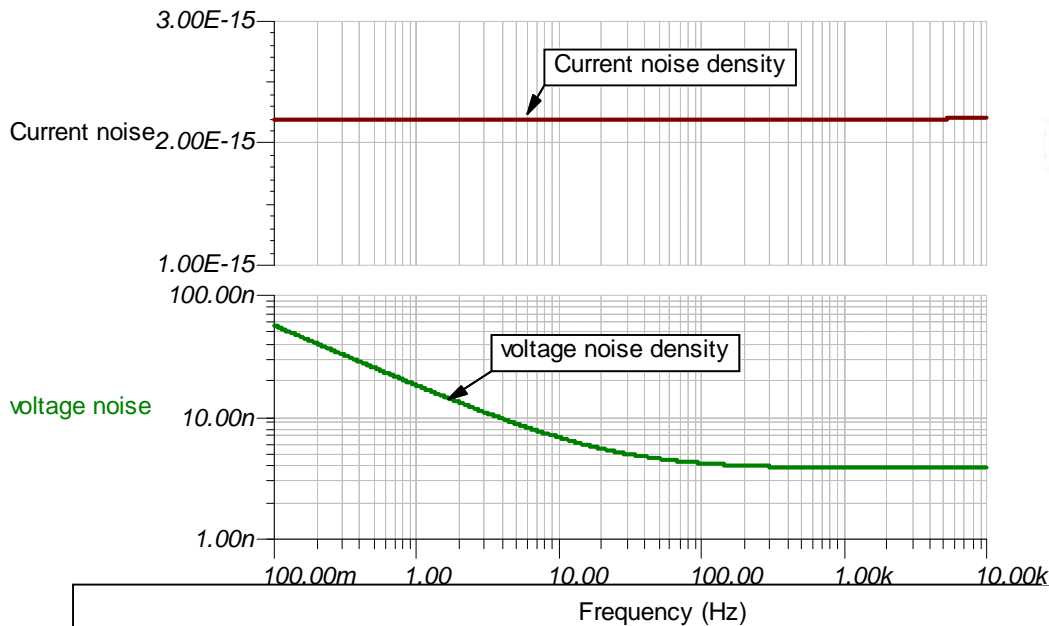

# Current Monitor mode

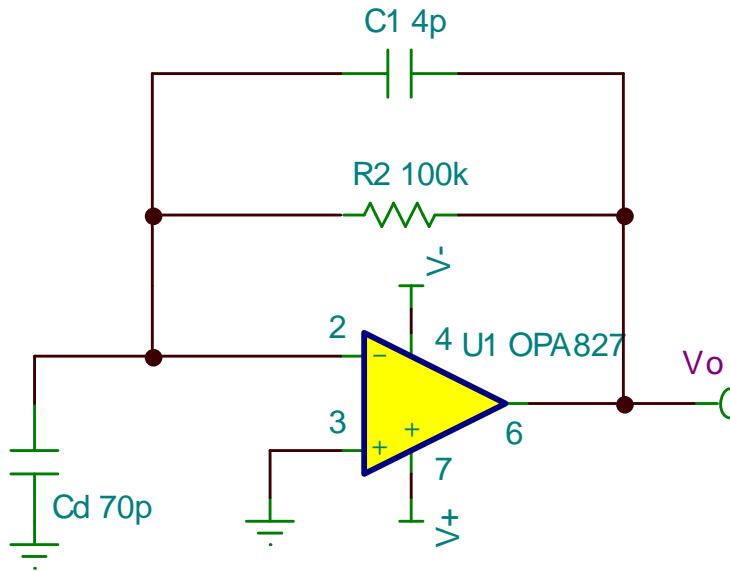

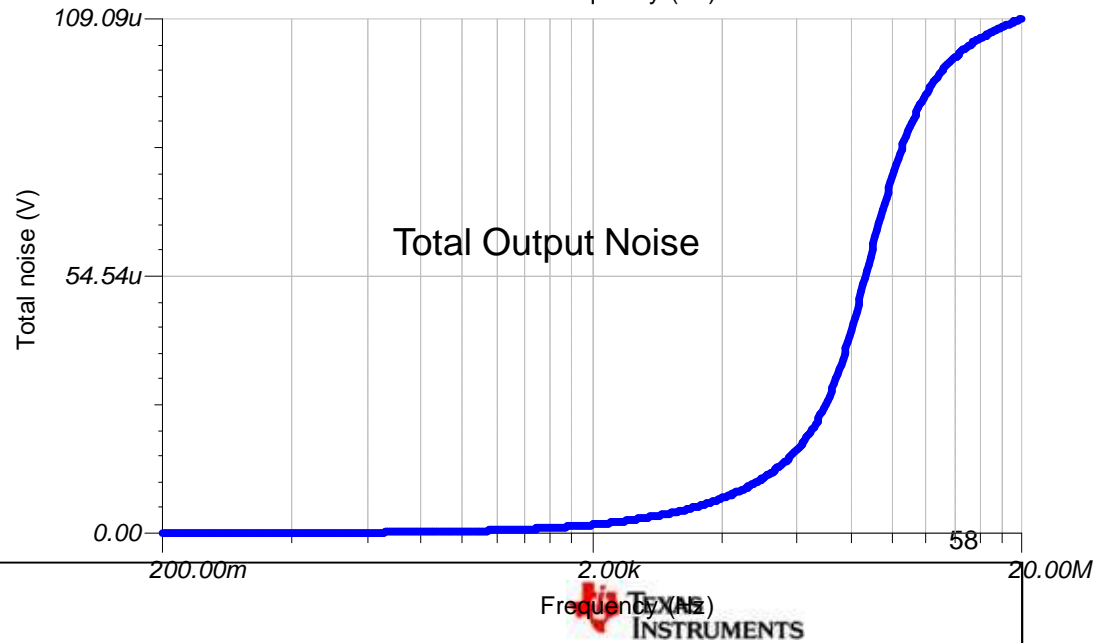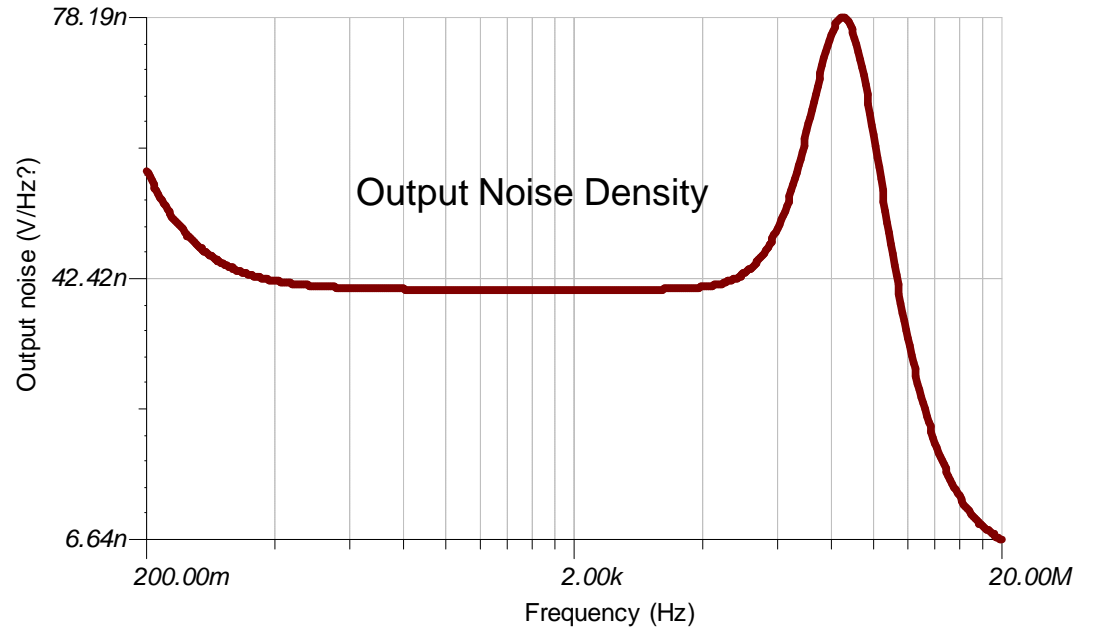Very small noise, will be flood in test equipments noise. We need post amplifier with high gain to zoom out noise so that we can check it in test equipments.








# Use OPA847 as post amplifier

*Wideband, Ultra-Low Noise, Voltage Feedback, Operational Amplifier*

- 350MHz Bandwidth (Gain of +20)
- 3900Mhz Gain Bandwidth Product
- 0.85nV/√Hz Input Voltage Noise
- 2.5pA/√Hz Input Current Noise
- ± 100uV Input Offset Voltage (Typical))


At the gain of 150, the bandwidth is 26Mhz

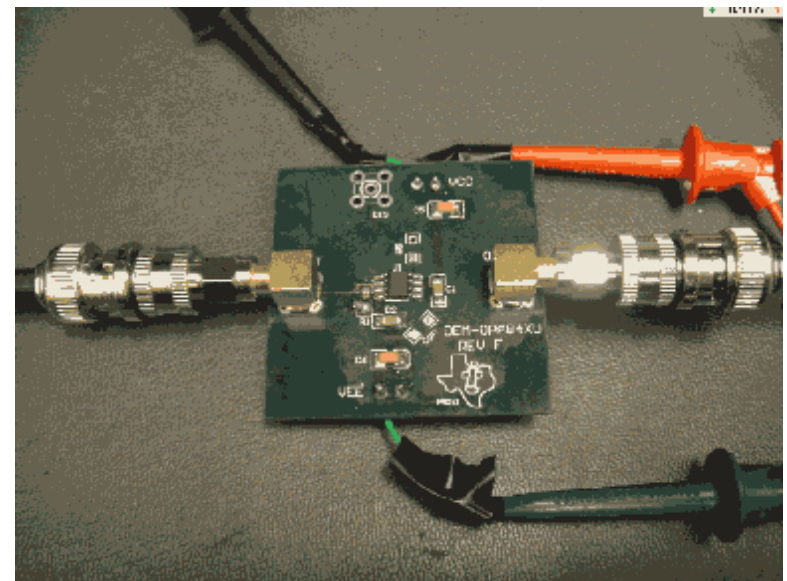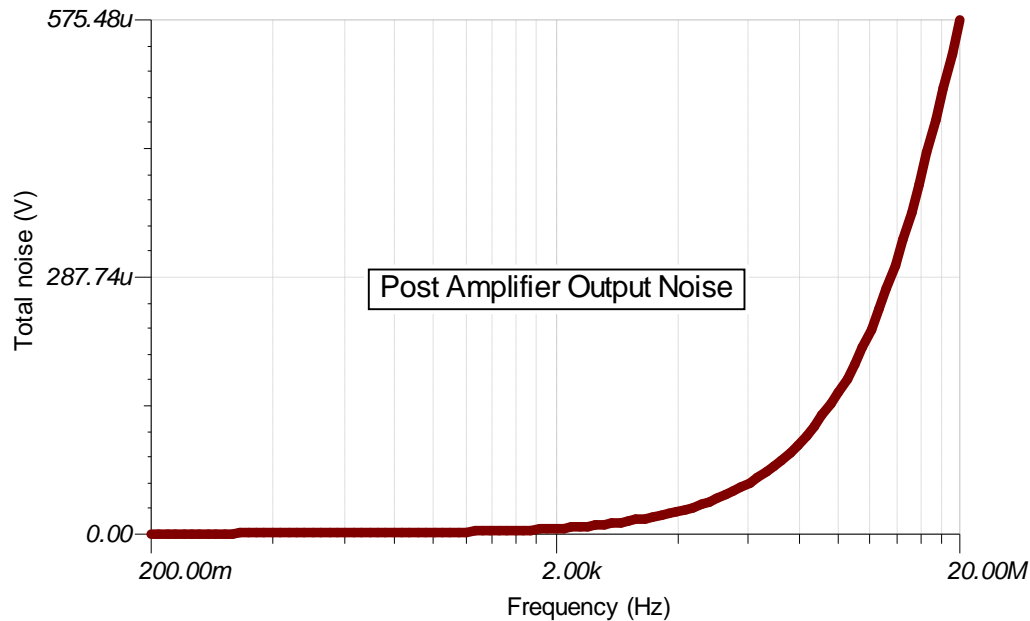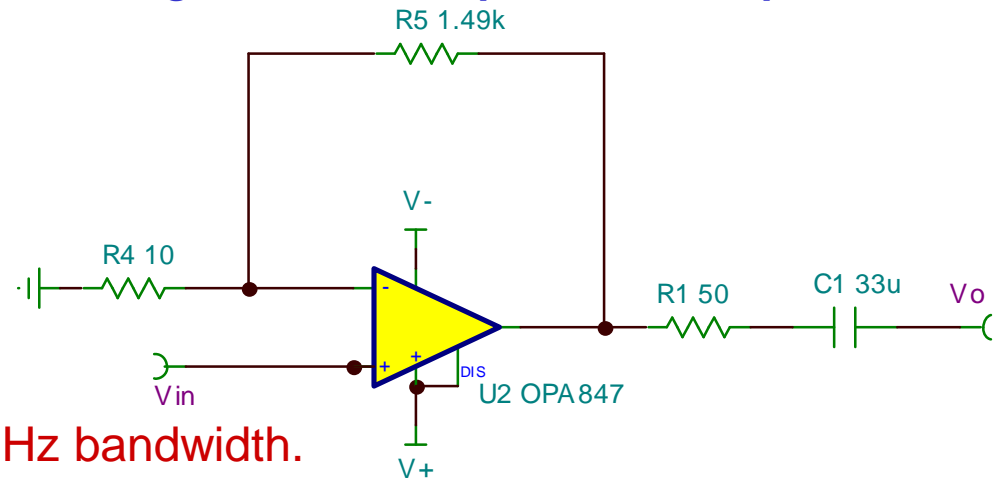575uVrms post amplifier noise in 20MHz bandwidth.





# Post amplifier noise in oscilloscope

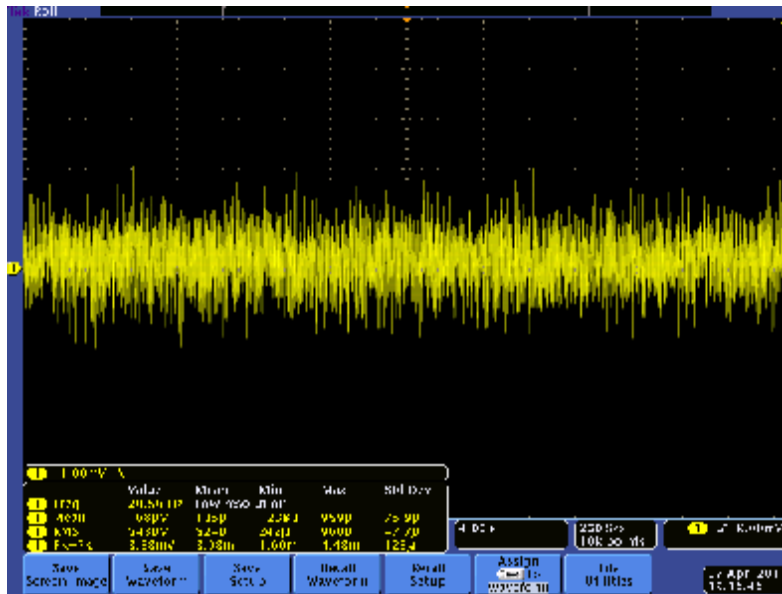

**STDEV:** 518uV

**P-P:** 6.6\*STDEV=3.4mV

**40s P-P:** 3.88mV

Tested Post Amplifier Noise is:

$$\sqrt{518^2 - 48^2} = 515.771 \text{ uV}$$

**Test Result is very close with simulation result 575uV. The difference may come from:**


- (1) 20MHz Oscilloscope's 20MHz bandwidth limit will also reduce some noise in 20Mhz;
- (2) Component value accuracy and variation;
- (3) Board parasitic parameter affect.






# Current Monitor Mode



# Current monitor

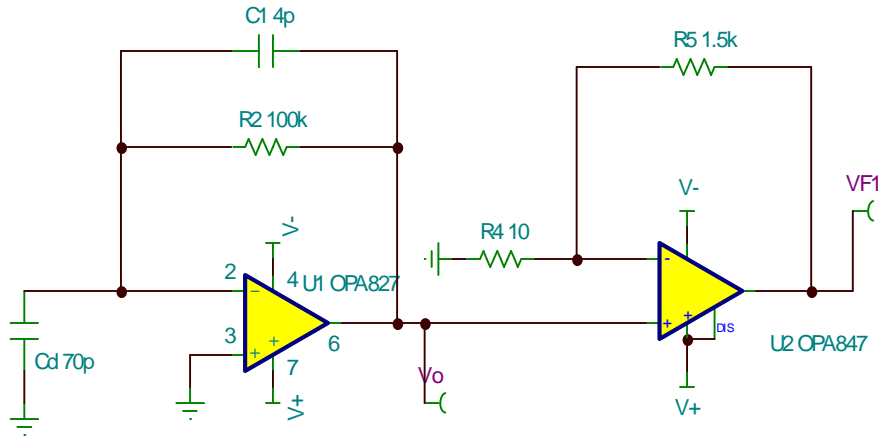

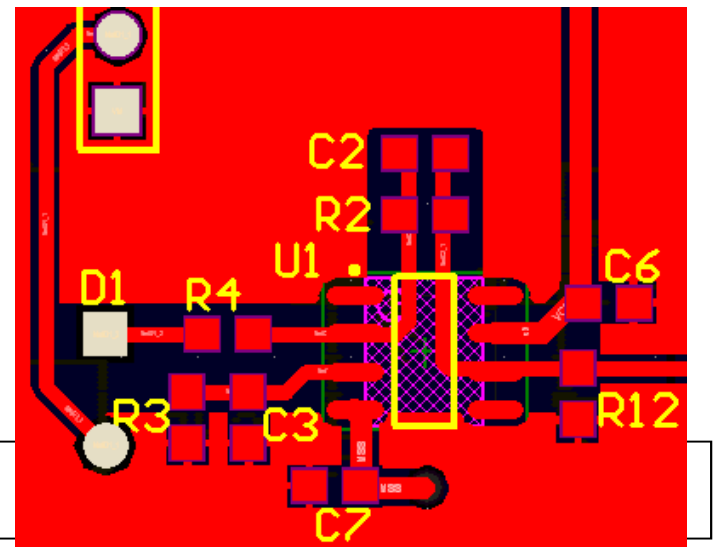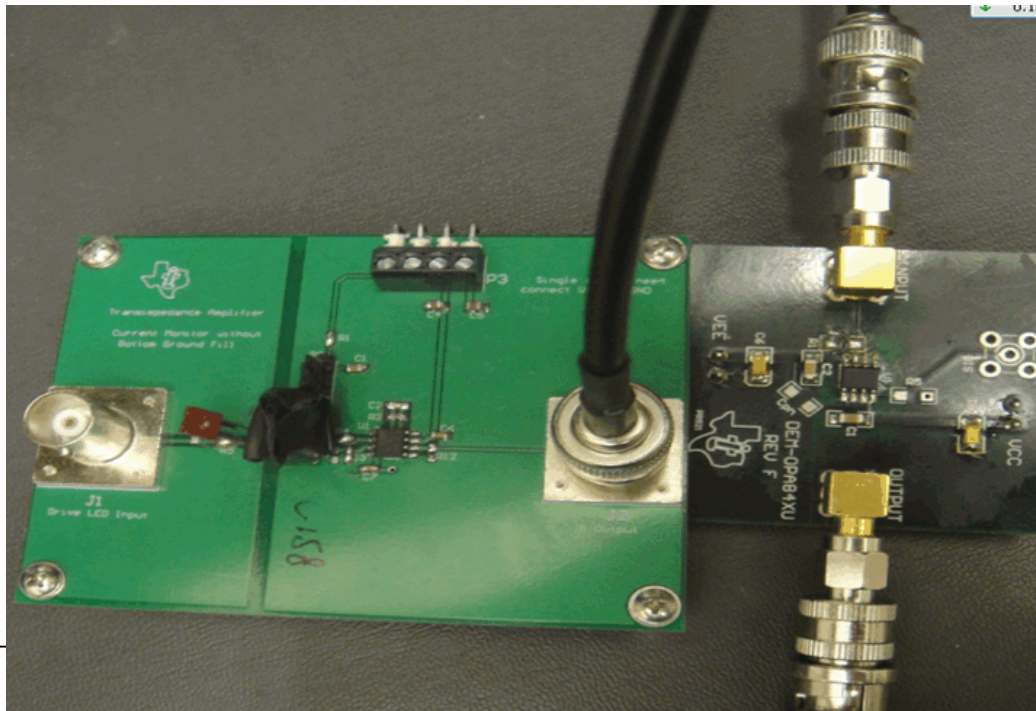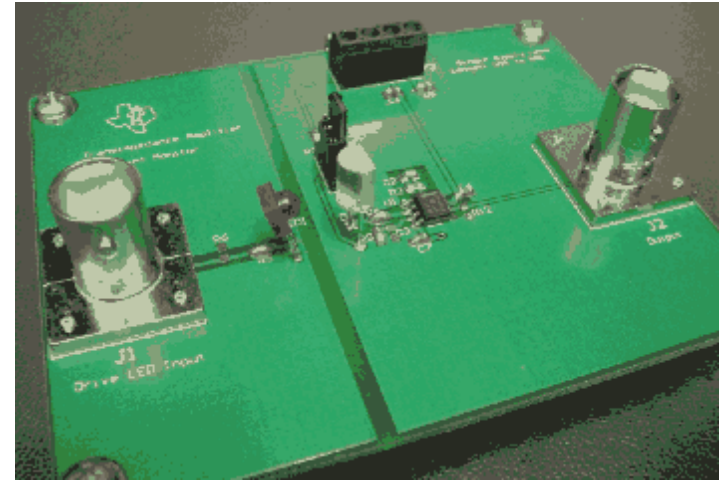
- 1, Use PDB-C158-ND photodiode, 70pF junction capacitance at  $V_r=0$  V;
- 2, 100dB C-V gain;
- 3, 4pF compensation capacitor;
- 4,  $\pm 5$ V power supply.







# Tested Total output Noise

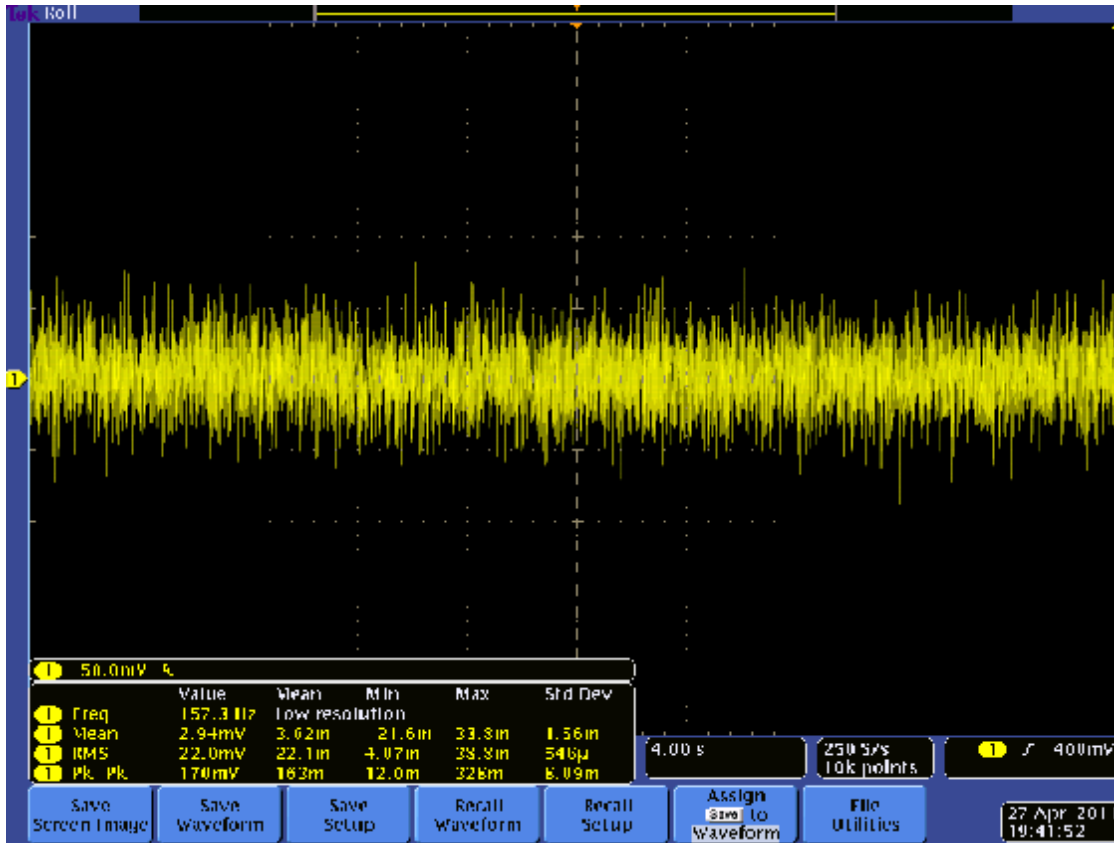

**Tested:**

**STDEV:** 21.7mV

**P-P:** 6.6\*STDEV=143mV

**40s P-P:** 170mV


**TA output noise:**

$$\frac{21.7}{150} = 0.145 \text{ mV} = 145\mu\text{V}$$

**Simulation:**

**Total output noise:** 16.24mV

**TA Output noise:** 110uV

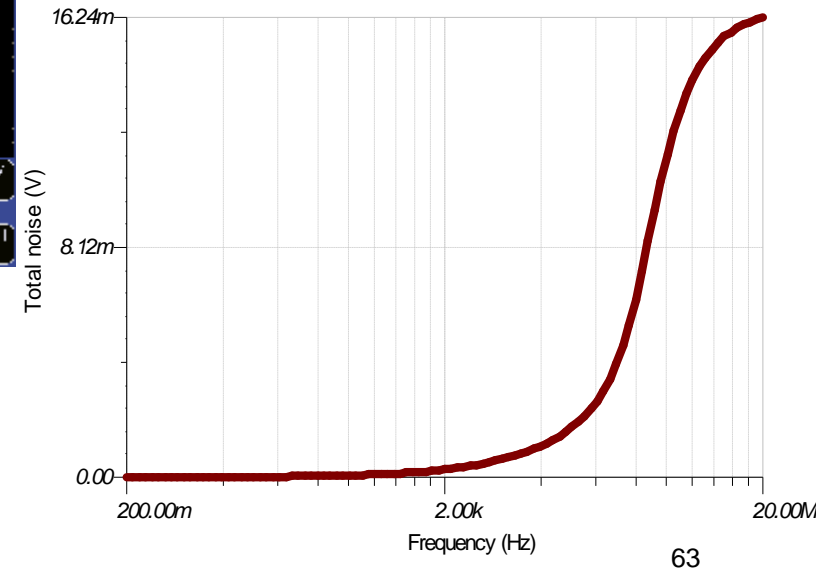



# Noise Hand calculation

Feedback resistor:  $\underline{\mathbf{R}} := 100 \cdot 10^3$

Compensation Cap:  $\mathbf{C1} := 4 \cdot 10^{-12}$  F

Photodiode Junction Cap:  $\mathbf{C2} := 70 \cdot 10^{-12}$  F

Amplifier Input Cap:  $\mathbf{Copa} := 18 \cdot 10^{-12}$  F

Total Cap:  $\mathbf{CT} := \mathbf{C1} + \mathbf{C2} + \mathbf{Copa} = 9.2 \times 10^{-11}$  F

Zero Frequency:  $\mathbf{fz} := \frac{1}{2\pi \cdot \mathbf{R} \cdot \mathbf{CT}} = 1.73 \times 10^4$  Hz

Pole Frequency:  $\mathbf{fp} := \frac{1}{2\pi \cdot \mathbf{R} \cdot \mathbf{C1}} = 3.979 \times 10^5$  Hz

Required bandwidth:  $\mathbf{BW_0} := 400 \times 10^3$  Hz

Voltage Noise density at 1Hz:  $\mathbf{en1} := 10.5 \cdot 10^{-9}$  V/sqrt(Hz)

Voltage wideband noise density:  $\mathbf{en} := 5.1 \cdot 10^{-9}$  V/sqrt(Hz)

Low frequency noise (1/f) Low frequency:  $\mathbf{fL} := 0.1$  Hz

Lower frequency noise (1/f) High frequency:  $\mathbf{fH} := 100$  Hz

Amplifier GBW:  $\mathbf{fc} := 11 \times 10^6$  Hz

1/!Â and Aol cross point frequency:  $\mathbf{fi} := \frac{\mathbf{C1}}{\mathbf{CT}} \cdot \mathbf{fc} = 4.783 \times 10^5$  Hz





## Noise Hand calculation

$$\text{Region 1 Noise: } \mathbf{Een1} := \sqrt{\mathbf{en1}^2 \ln\left(\frac{\mathbf{fH}}{\mathbf{fL}}\right)} = 2.76 \times 10^{-8} \text{ V}$$

$$\text{Region 2 Noise: } \mathbf{Een2} := \sqrt{\mathbf{en}^2 \cdot (\mathbf{fz} - \mathbf{fH})} = 6.688 \times 10^{-7} \text{ V}$$

$$\text{Region 3 Noise: } \mathbf{Een3} := \sqrt{\frac{\mathbf{en}^2 \cdot (\mathbf{fp}^3 - \mathbf{fz}^3)}{\mathbf{fz}^2 \cdot 3}} = 4.272 \times 10^{-5} \text{ V}$$

$$\text{Region 4 Noise: } \mathbf{Een4} := \sqrt{\left(\mathbf{en} \cdot \frac{\mathbf{CT}}{\mathbf{C1}}\right)^2 \cdot (\mathbf{fi} - \mathbf{fp})} = 3.325 \times 10^{-5} \text{ V}$$

$$\text{Region 5 Noise: } \mathbf{Een5} := \sqrt{(\mathbf{en} \cdot \mathbf{fc})^2 \cdot \left(\frac{1}{\mathbf{fi}} - \frac{1}{\mathbf{fc}}\right)} = 7.934 \times 10^{-5} \text{ V}$$

Voltage output noise:

$$\mathbf{Veo} := \sqrt{\mathbf{Een1}^2 + \mathbf{Een2}^2 + \mathbf{Een3}^2 + \mathbf{Een4}^2 + \mathbf{Een5}^2} = 9.605 \times 10^{-5} \text{ V}$$



# Noise Hand calculation

Photodiode current noise:  $\underline{\text{in1}} := 4.5 \cdot 10^{-15} \text{ fA/sqrt(Hz)}$

Amplifier input current noise is:  $\underline{\text{in2}} := 0.8 \cdot 10^{-15} \text{ fA/sqrt(Hz)}$

Current noise contribute in noise volatge at circuit output is:

$$\mathbf{V_i} := \sqrt{\mathbf{R^2 \cdot (in1^2 + in2^2)}} = 4.571 \times 10^{-10} \text{ V}$$

Resistor Thermal Noise is:

Bolzmann constant  $\underline{\mathbf{K}} := 1.38 \cdot 10^{-23} \text{ J/K}$

Temperature:  $\underline{\mathbf{T}} := 300 \text{ K}$

$$\mathbf{V_r} := \sqrt{4\mathbf{K \cdot T \cdot R \cdot fp}} = 2.567 \times 10^{-5}$$


Total Output Noise:

$$\mathbf{V_n} := \sqrt{\mathbf{V_{eo}^2 + V_r^2 + V_i^2}} = 9.942 \times 10^{-5}$$

| Simulation | Calculation | Test  |
|------------|-------------|-------|
| 110uV      | 99.4uV      | 145uV |



# Noise Density

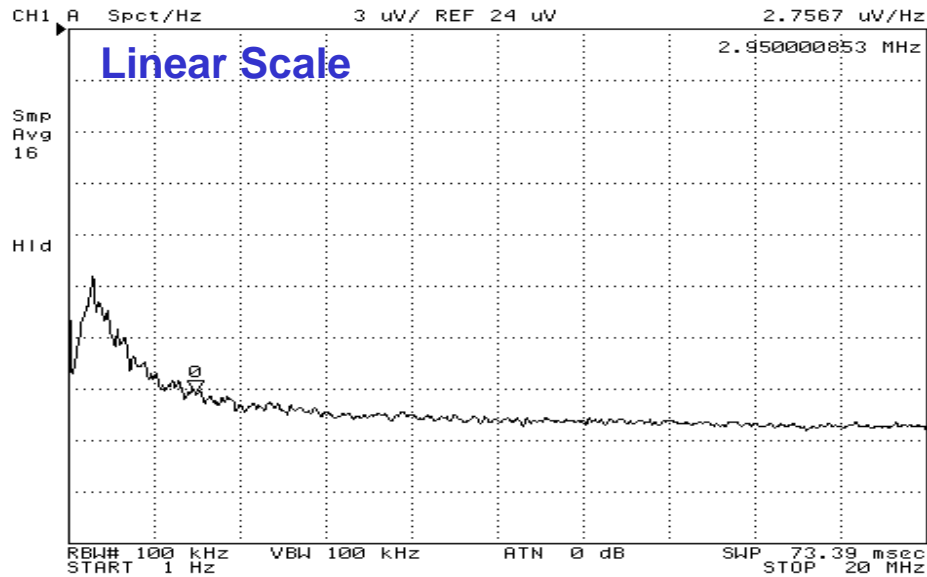

SELECT LETTER

SPACE

BACK SPACE

ERASE TITLE



DONE

STOR DEV [DISK]

CANCEL


1, Agilent 4395A spectrum Analyzer test **1Hz~20MHz** span, **3uV/div, REF=24uV**.

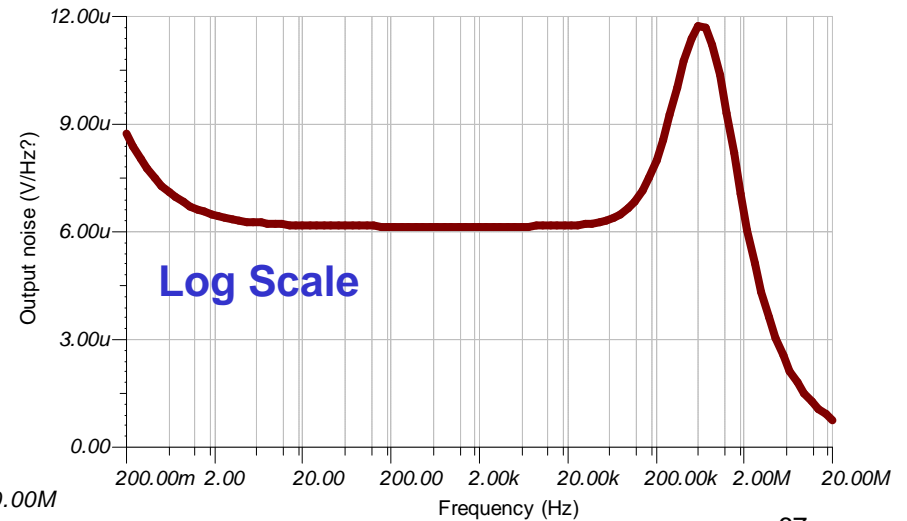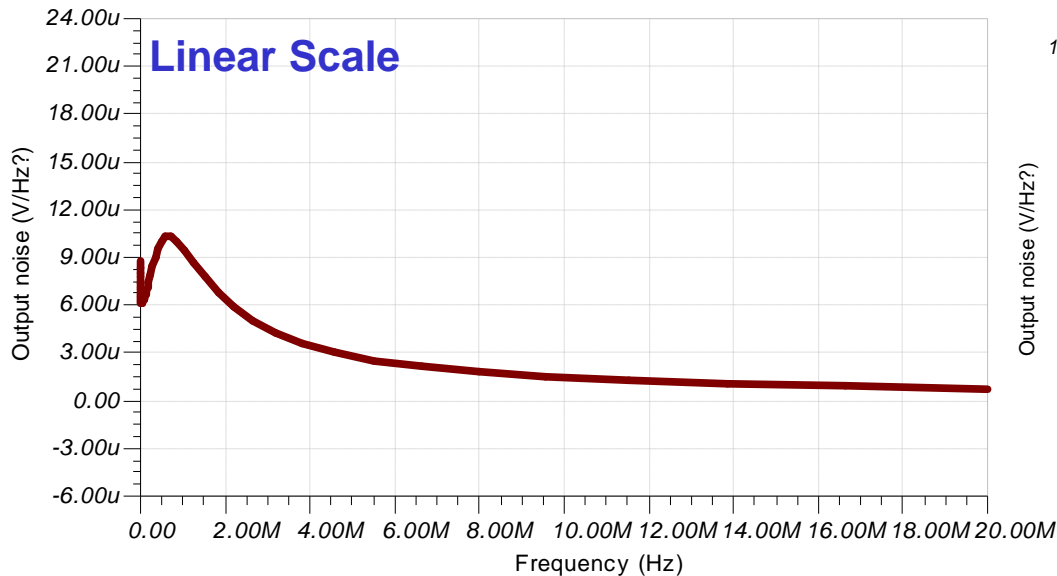2, The tested noise density curve shape is the same as simulation.






# Noise Density

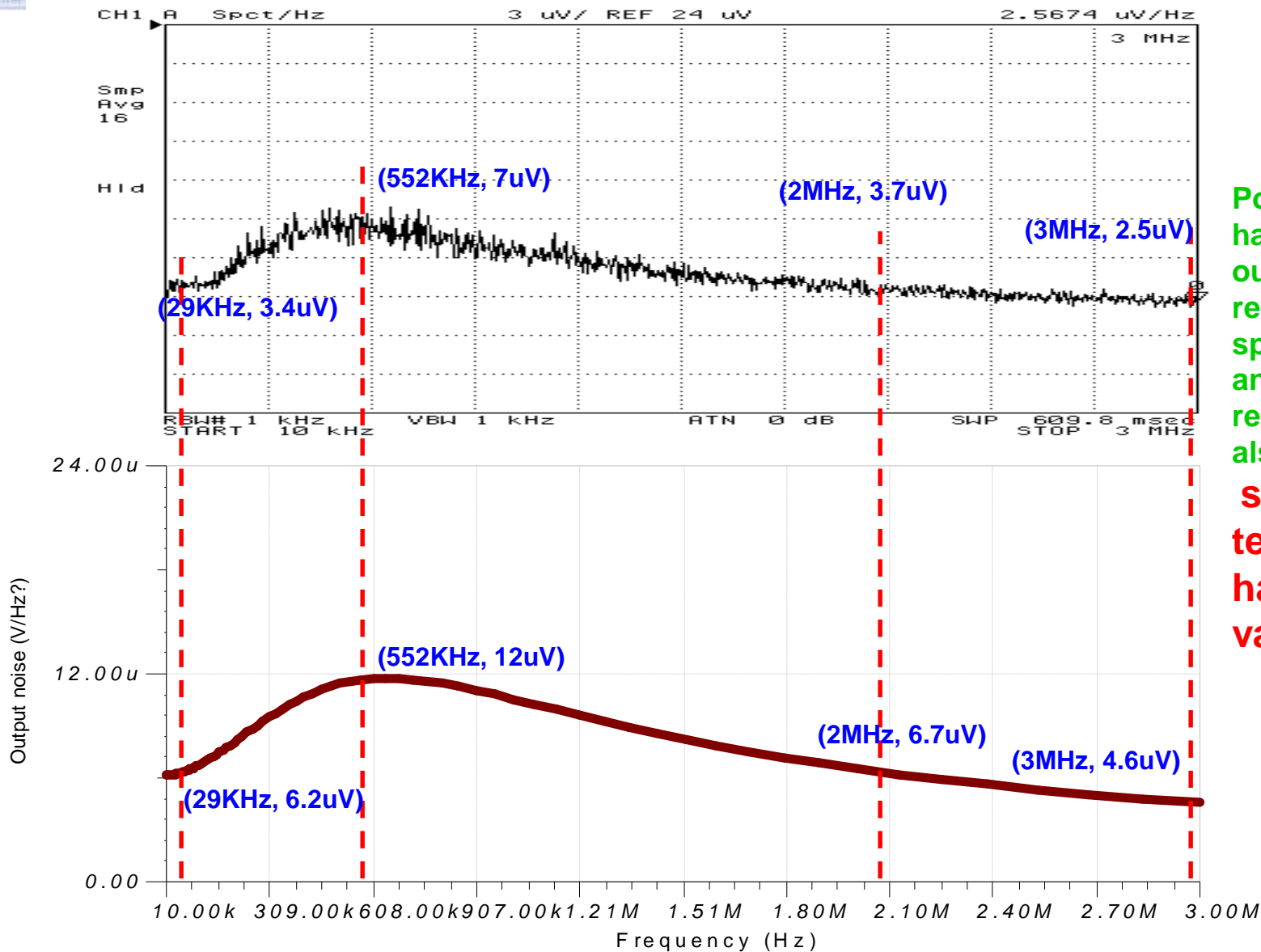

Post amplifier has 50ohm output resistance, spectrum analyzer's input resistance is also 50 ohm, so 4395A test value is half of real value.





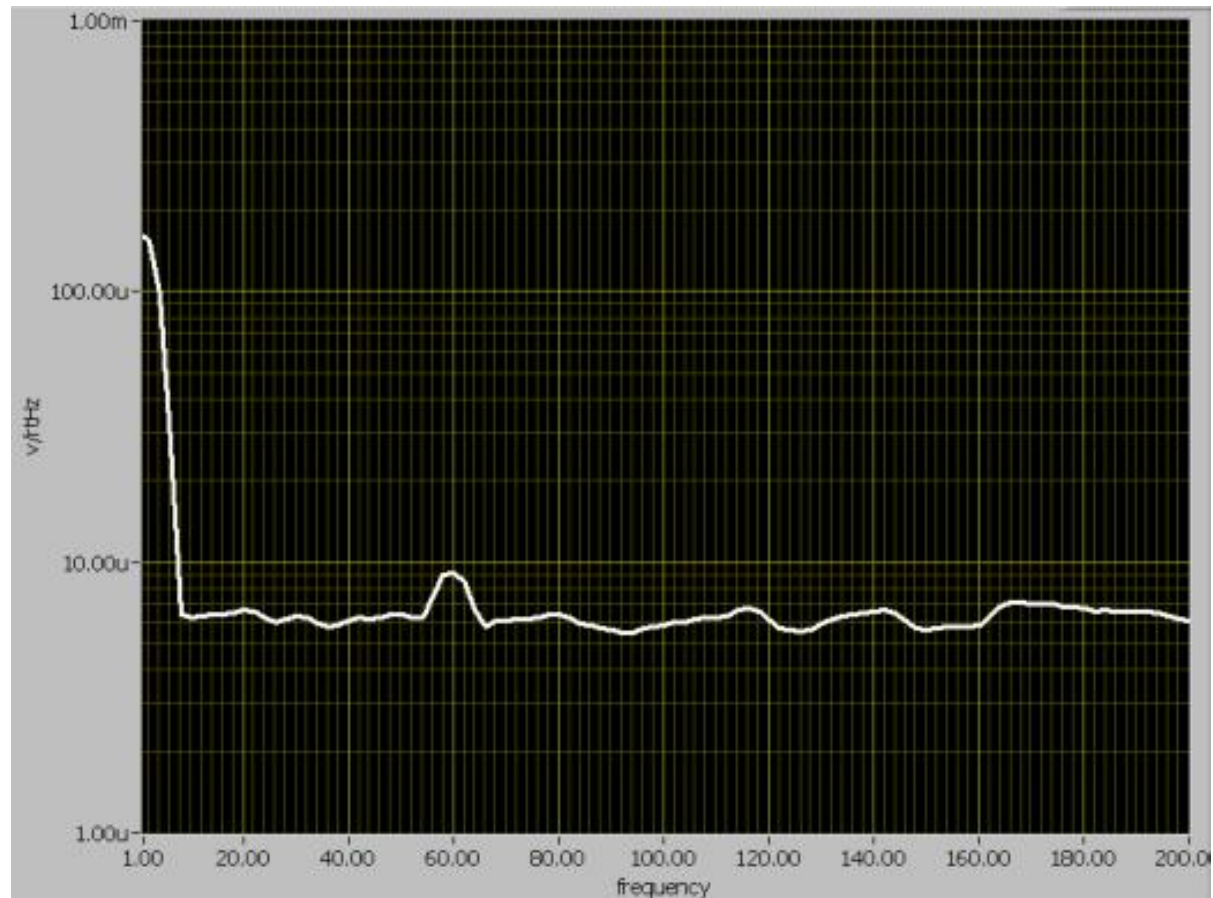
## Agilent 35670A, 1M $\Omega$ Input impedance



Agilent 35670A Dynamic signal analyzer's input impedance is 1Mohm, From 1Hz to 200Hz, Noise floor is about 6.3uV, almost the same as simulation value.




# Composite

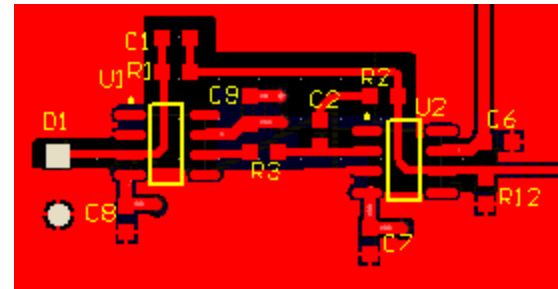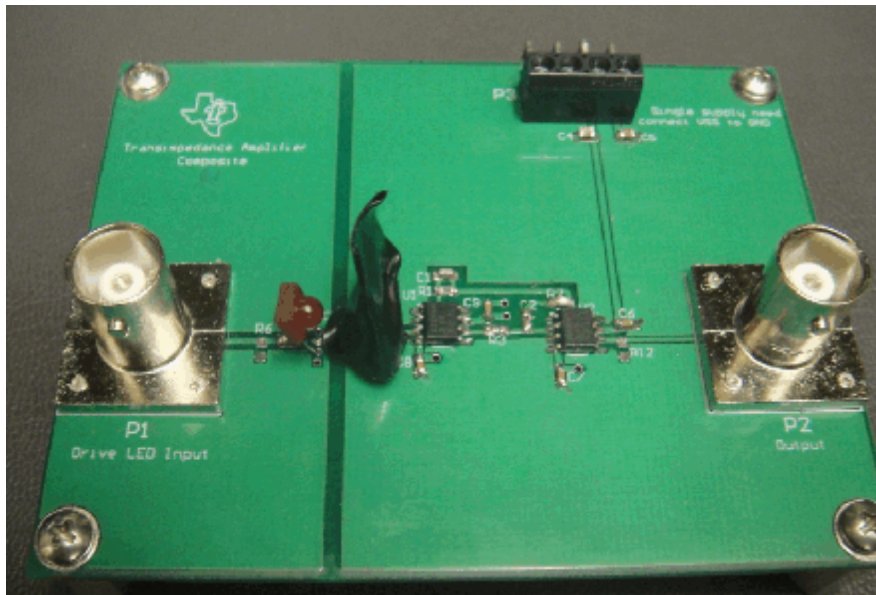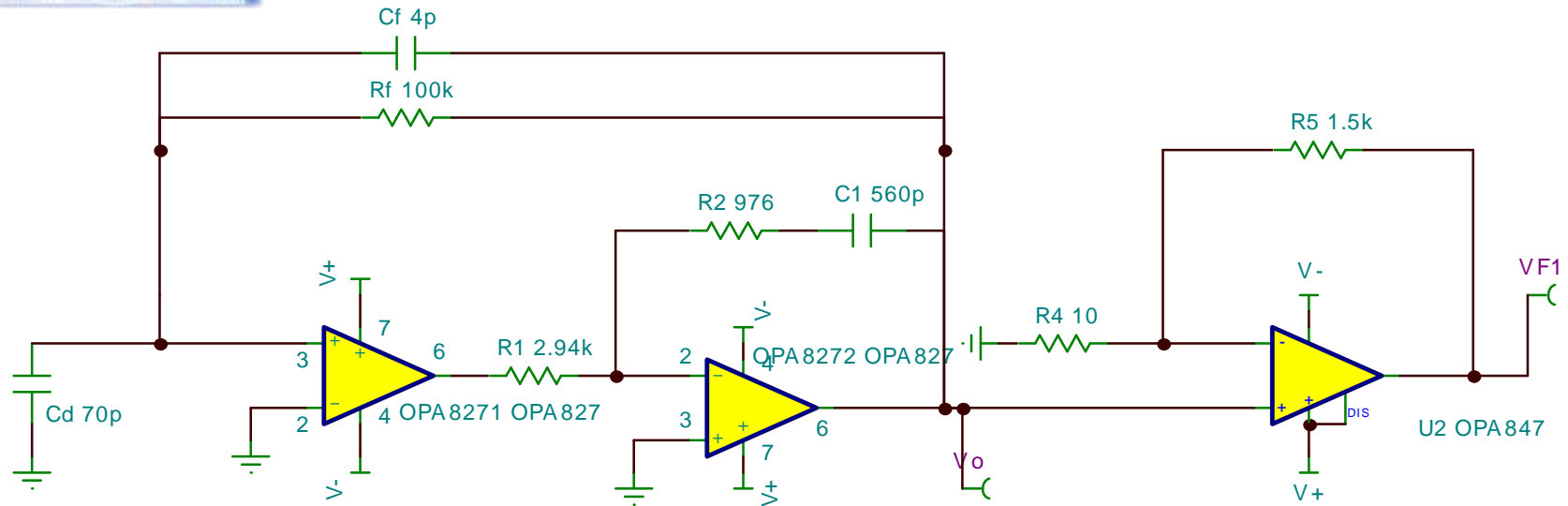




# Composite

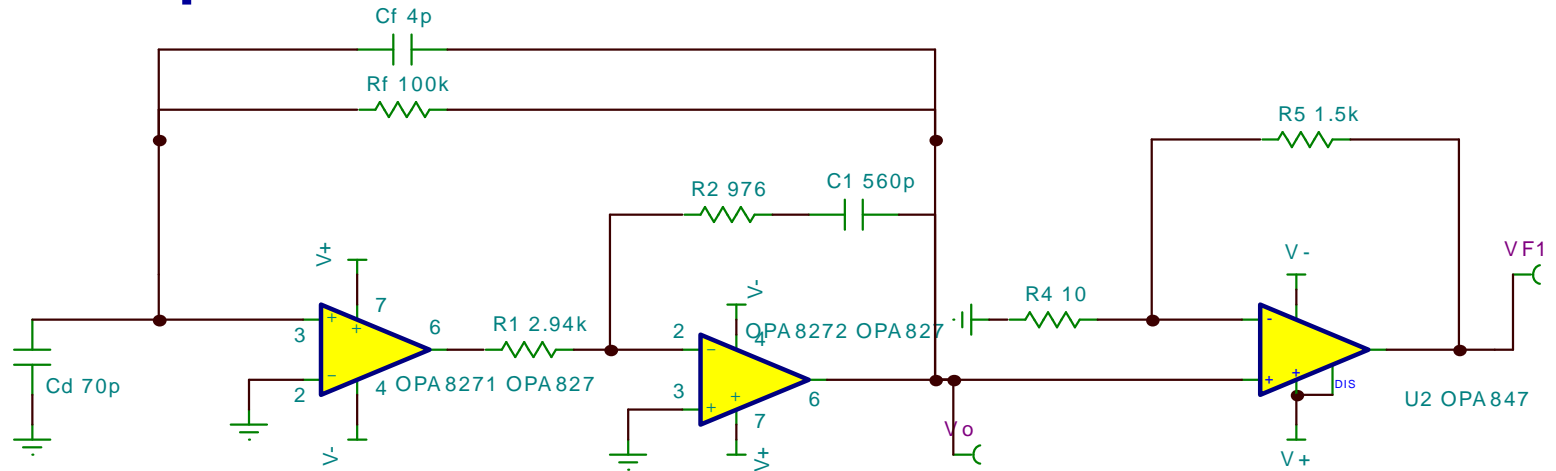


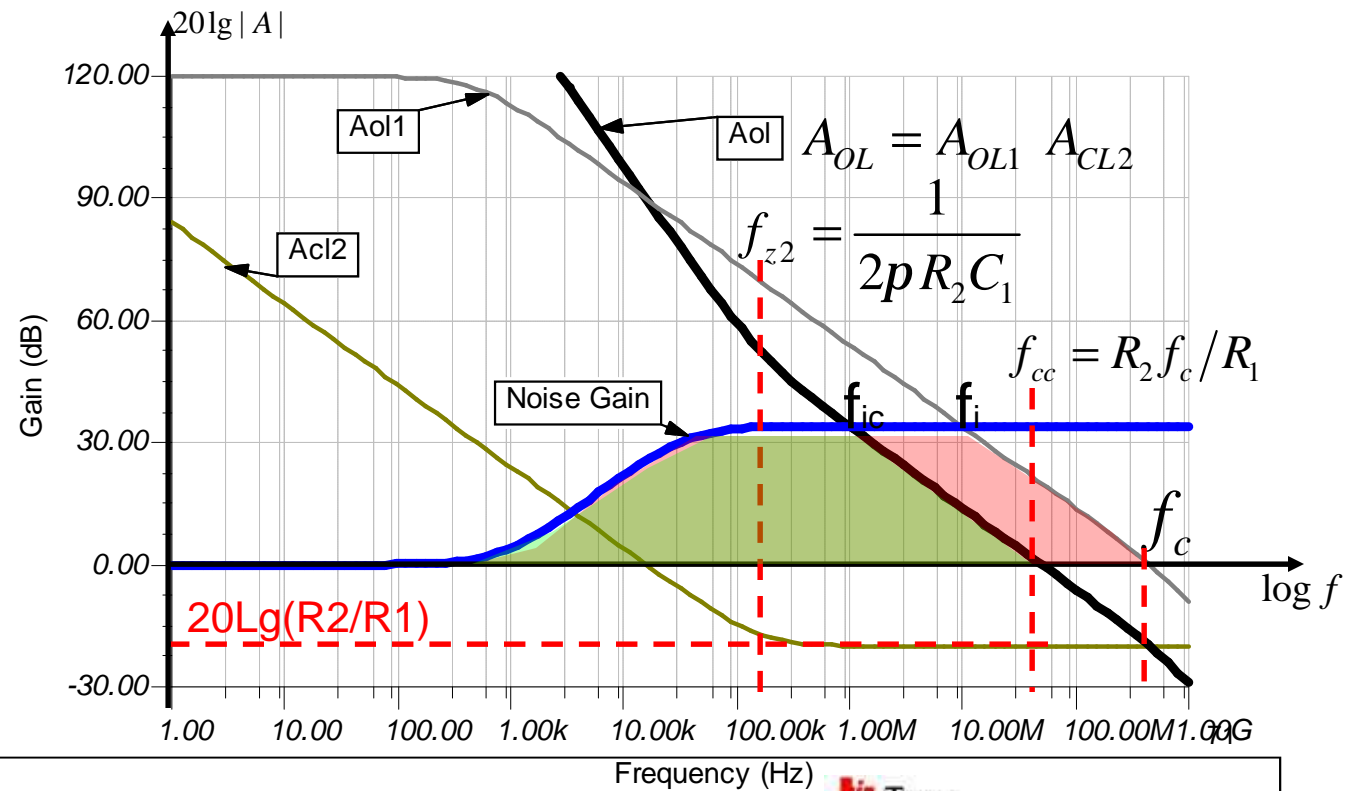
Using the circuit on right for TINA simulation. the noise bandwidth has been changed smaller. We set R1, R2 and C1 to realize Aol modify.







# Composite amplifier Noise

R1=2.9K, R3=2.9K, C2 short

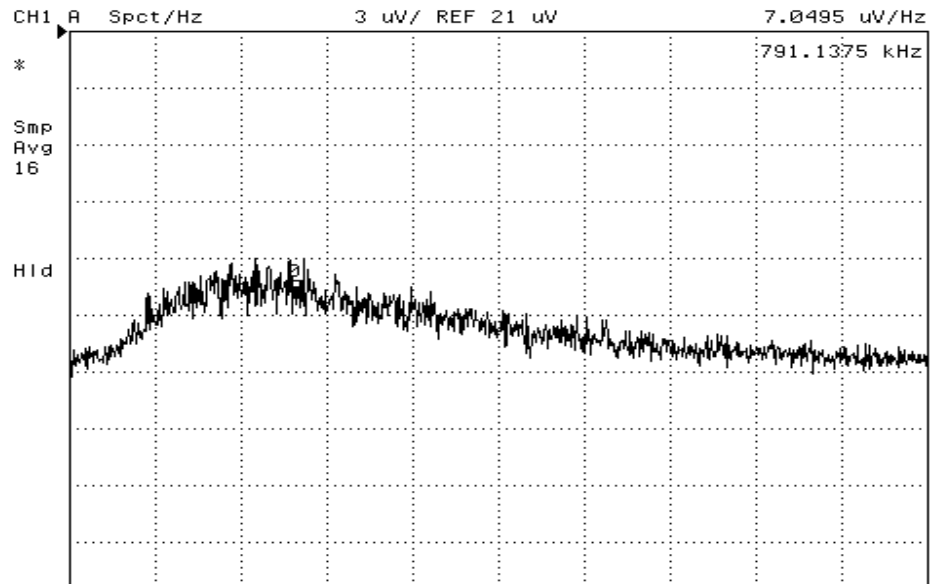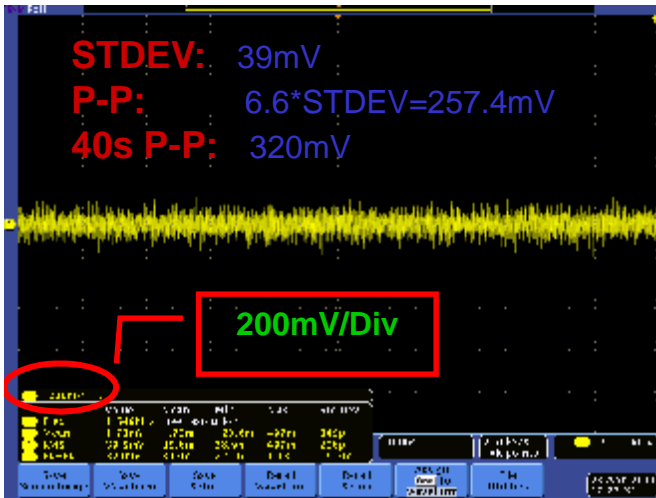

SELECT LETTER  
SPACE  
BACK SPACE  
ERASE TITLE  
DONE  
STOR DEV [DISK]

R1=2.9K, R2=K, C1=560pF


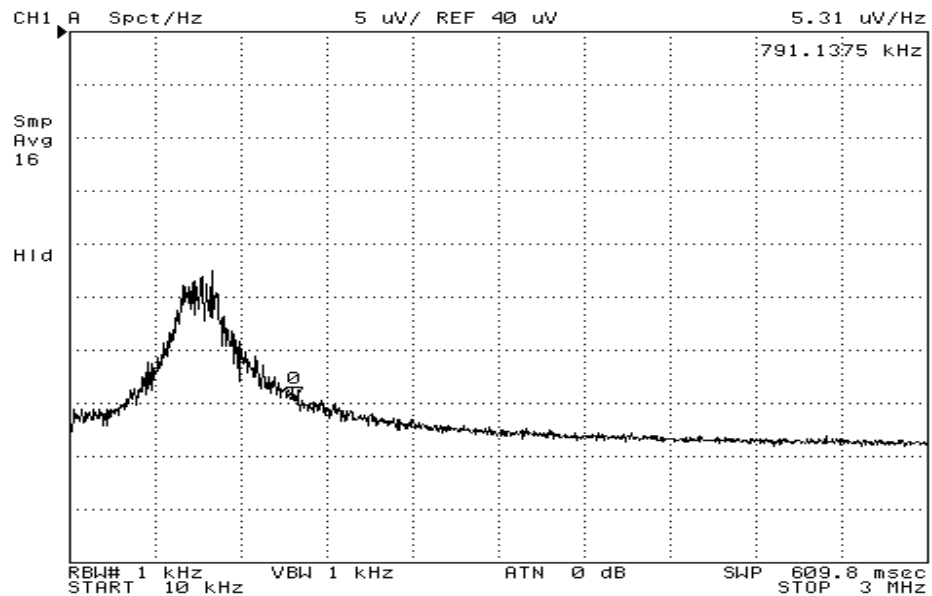
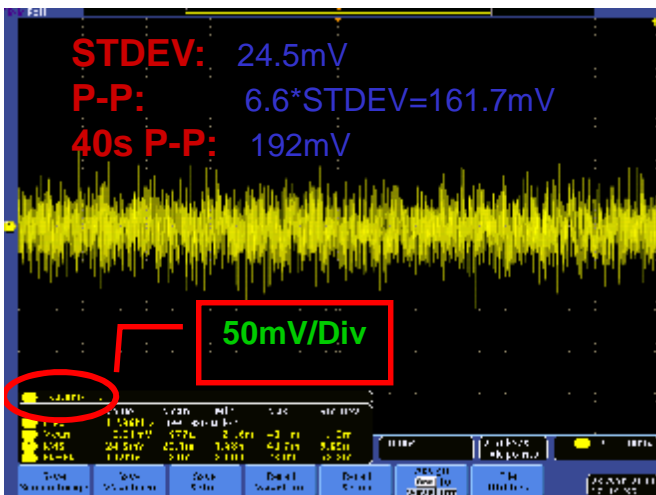


SELECT LETTER  
SPACE  
BACK SPACE  
ERASE TITLE  
DONE  
STOR DEV [DISK]  
CANCEL







# Differential

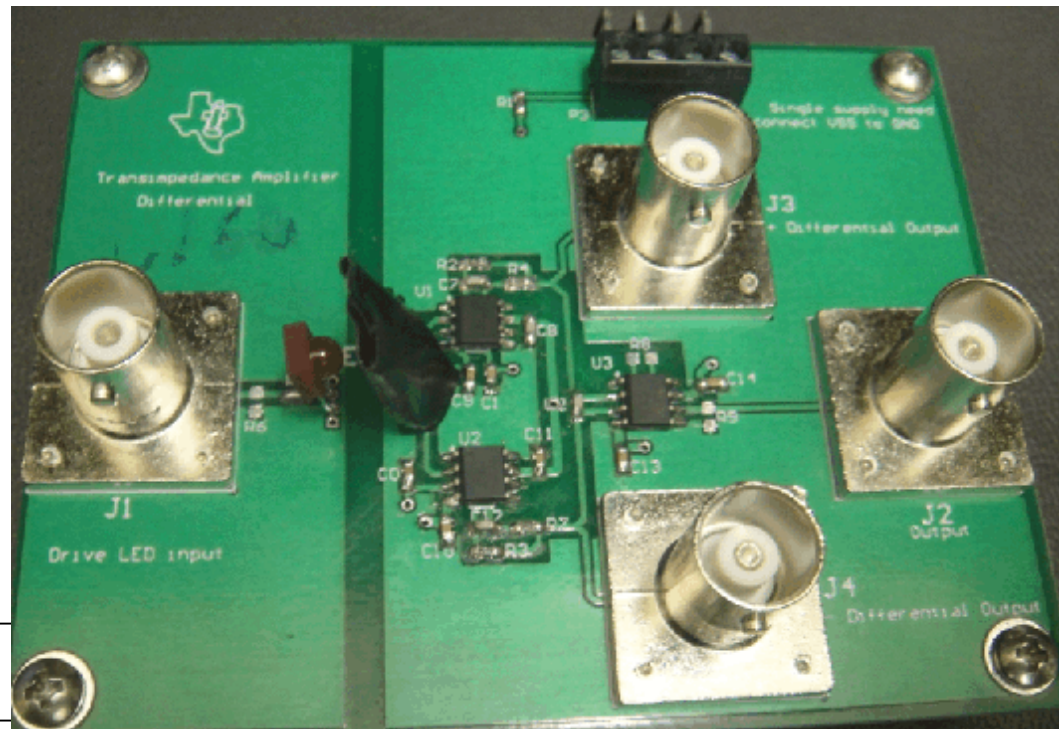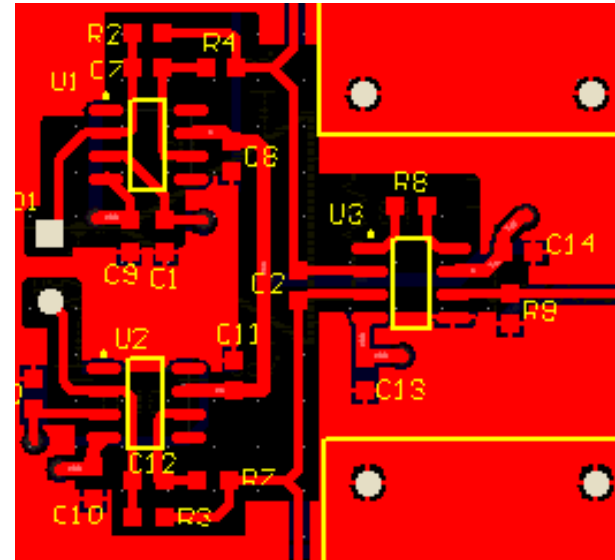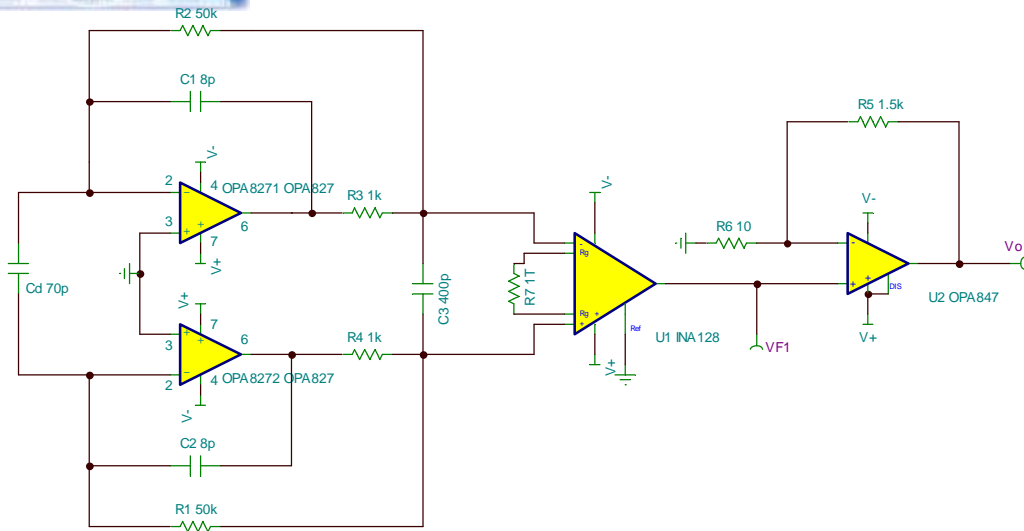





# How to Analyze?

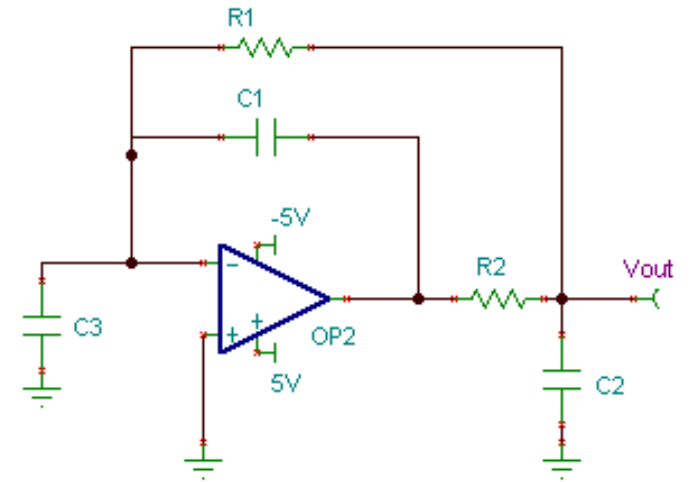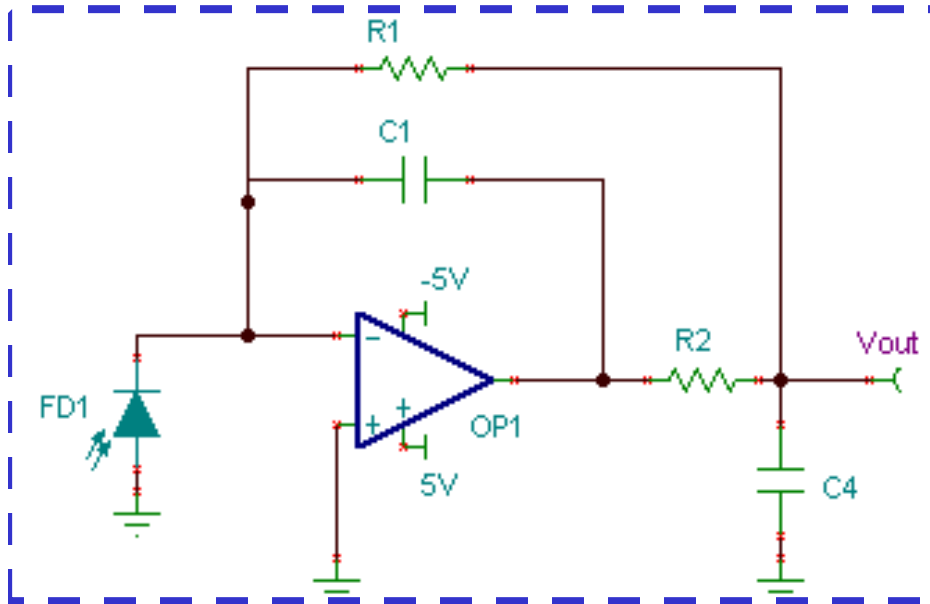

1, Dual feedback circuit usually used in High Cap load application.


2, Dual feedback is used to compensate close loop phase margin to make circuit stable.

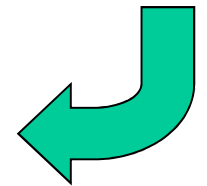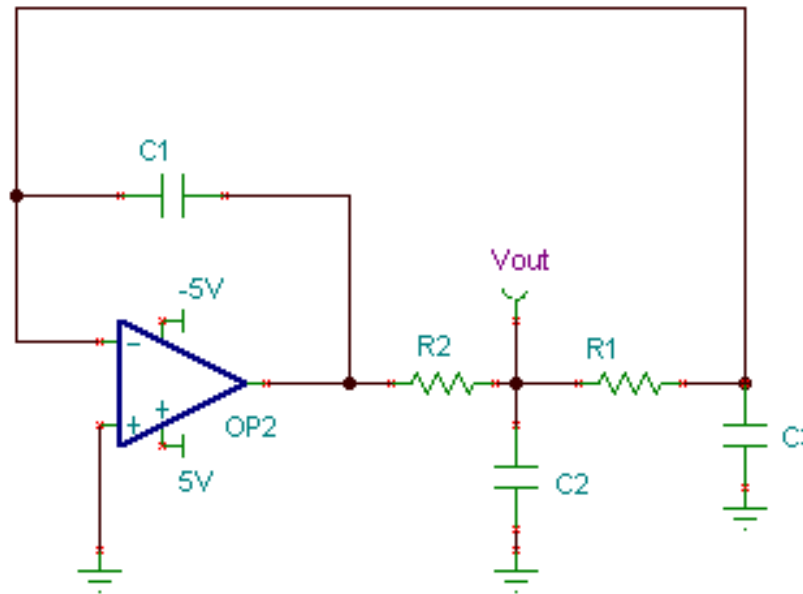3, But in photo current amplifier application, circuit has very large input capacitance. The circuit is different to normal use.






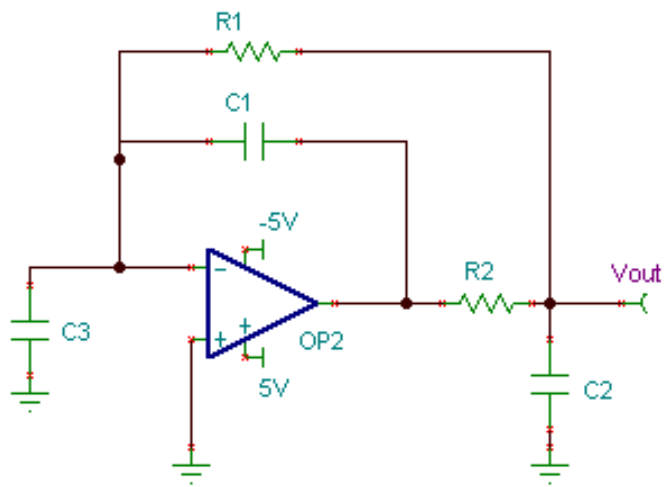
# Dual feedback circuit in PD application



$\beta_2$

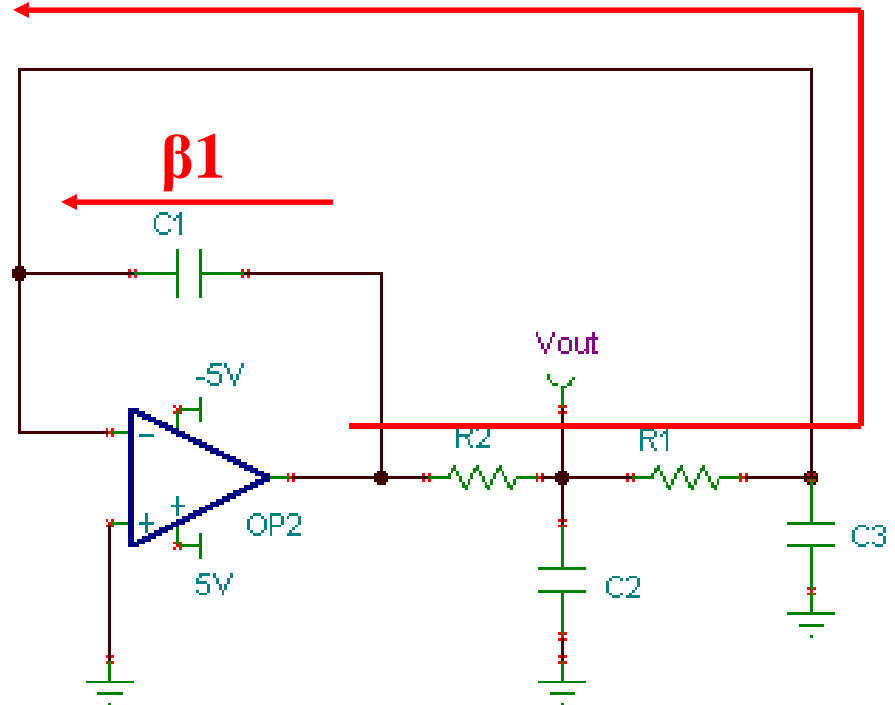

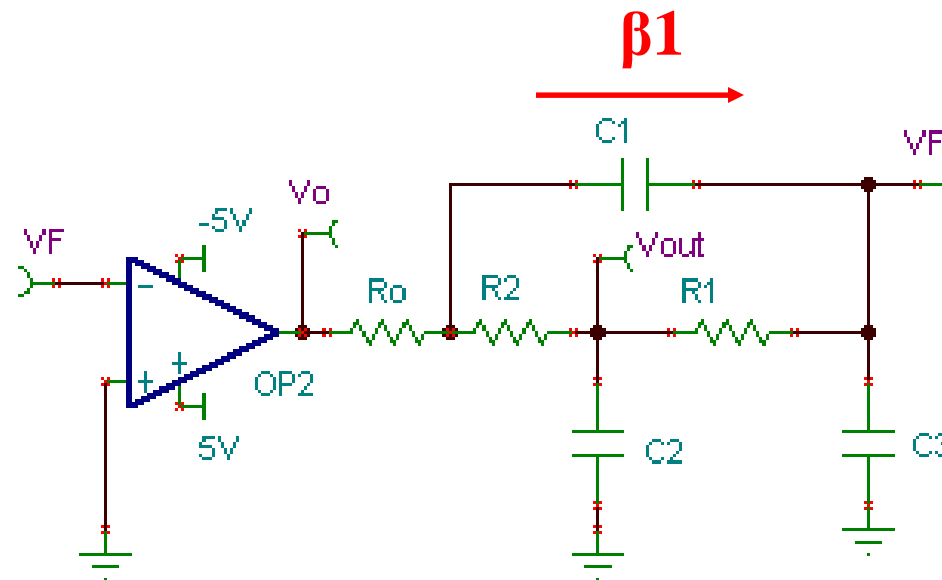

## In $1/\beta_1$ Curve:

1), At Low frequency,  $V_o/V_F=1$

2), At low frequency,  $V_F$  is mainly contributed by current from  $R_1$ . Signal pass  $R_0$ ,  $R_2$ ,  $R_1$   $C_3$  to ground, there is a zero created by  $R_0$ ,  $R_2$  and  $R_1$ :

$$f_z = 1/[2\pi \cdot (R_0 + R_1 + R_2) \cdot C_3] \approx 1/[2\pi \cdot R_1 \cdot C_3]$$


3), At higher frequency,  $C_1$ 's impedance decrease,  $V_F$  is contributed by currents from both  $C_1$  and  $R_1$ . When frequency is higher enough, most current comes from  $C_1$ , the  $V_o/V_F = (C_1 + C_3)/C_1$

Pole frequency is:

$$f_p = 1/[2\pi \cdot R_1 \cdot C_1]$$


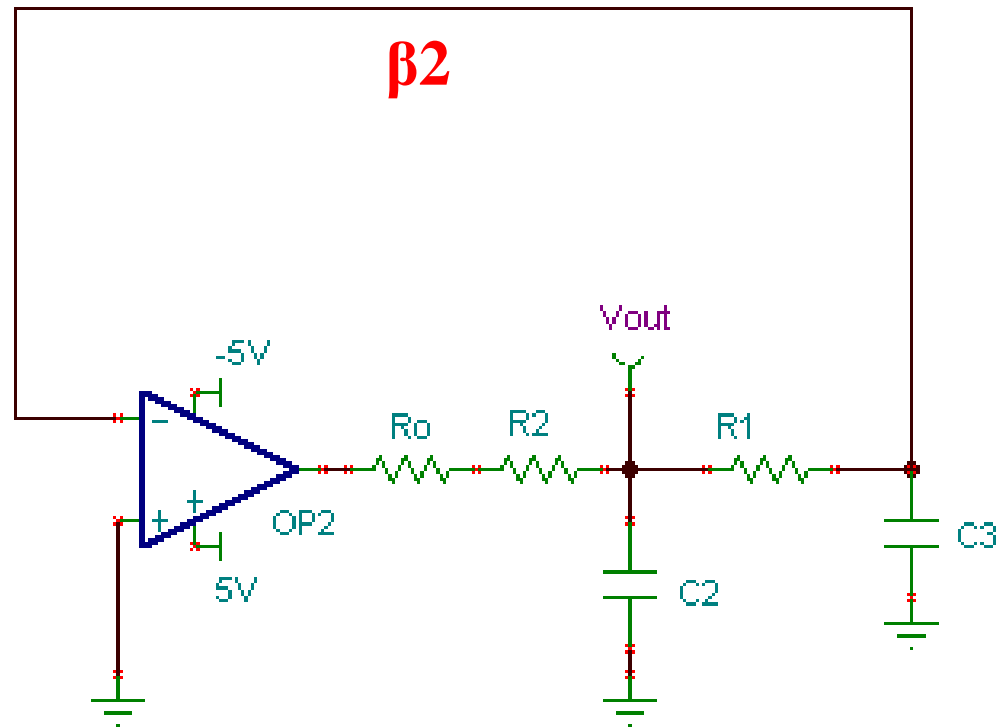
# Dual feedback circuit in PD application




In  $1/\beta_2$  Curve

- 1), Will Create First zero at  $1/[2*\pi*R1*C3]$
- 2), Will Create Second zero at  $1/[2*\pi*(R0+R2)*C2]$



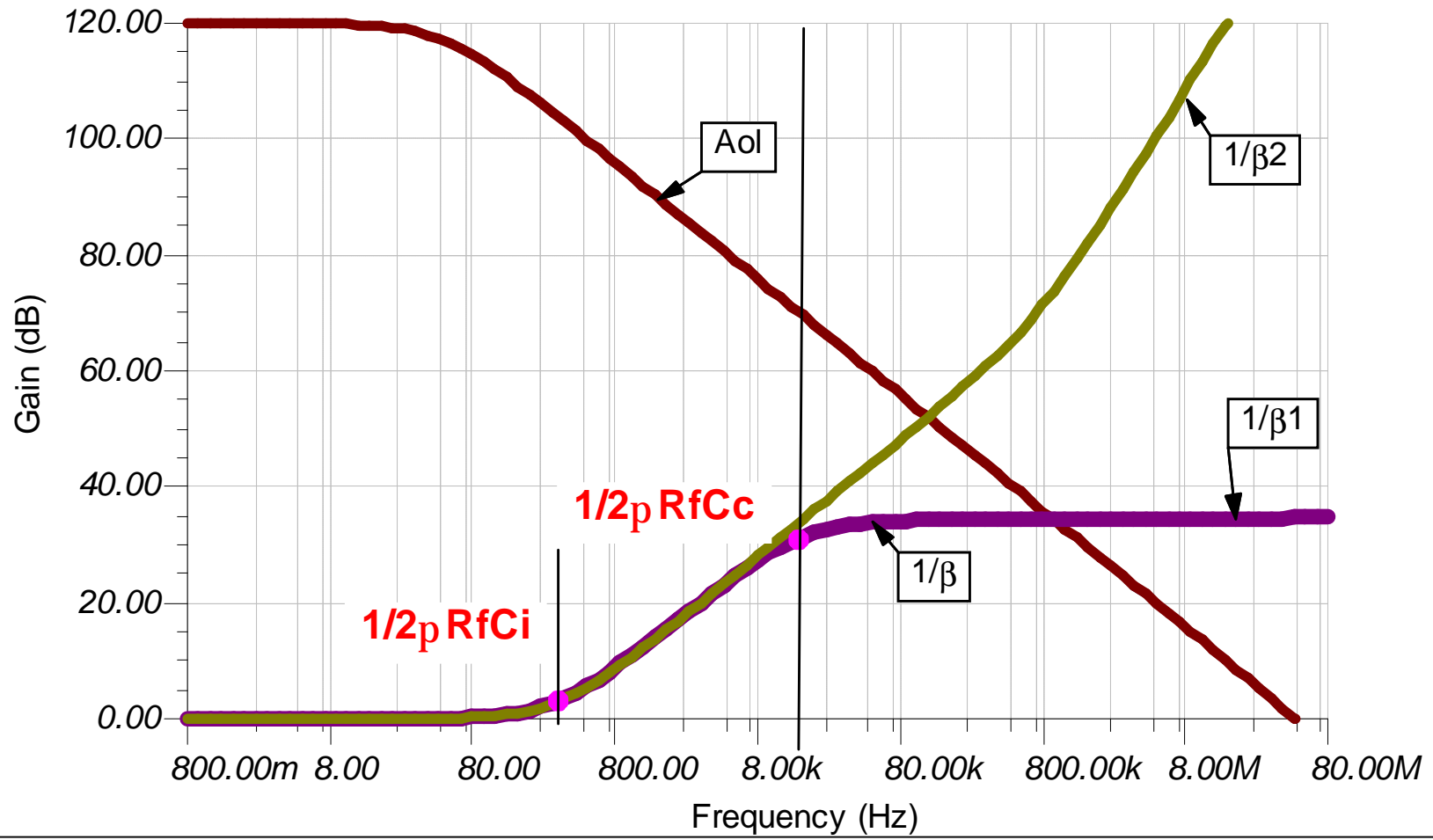
## Dual Feedback, Superposition : The largest $\beta$ (smallest $1/\beta$ ) will dominate!






## How about Signal Bandwidth?

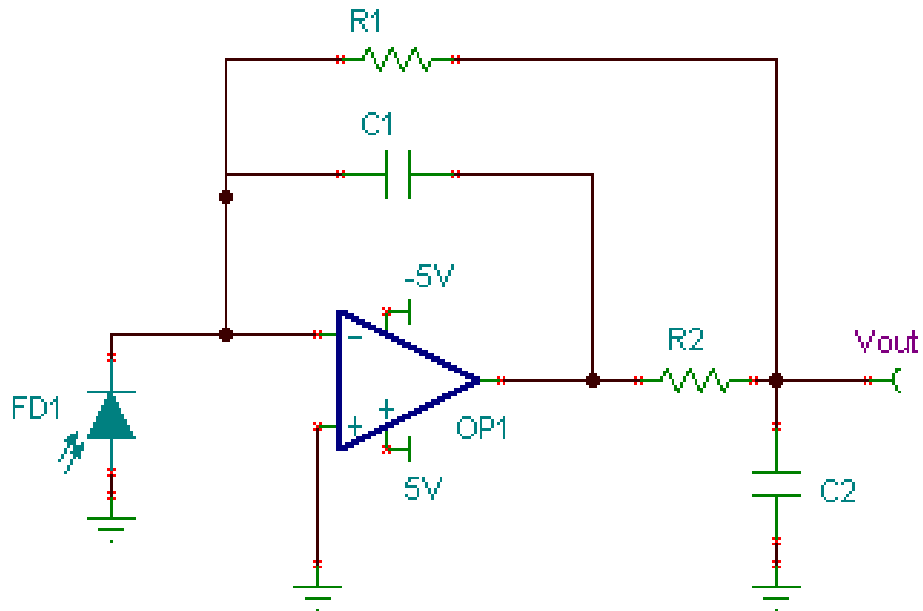

- (1) At low frequency, the photo current mainly pass through R1, R1 will dominate the gain.
- (2) When frequency goes high, C1 will split more current, so R1 and C1 will create a gain curve pole at:  
$$f_{p1} = 1 / (2 * \pi * R1 * C1)$$

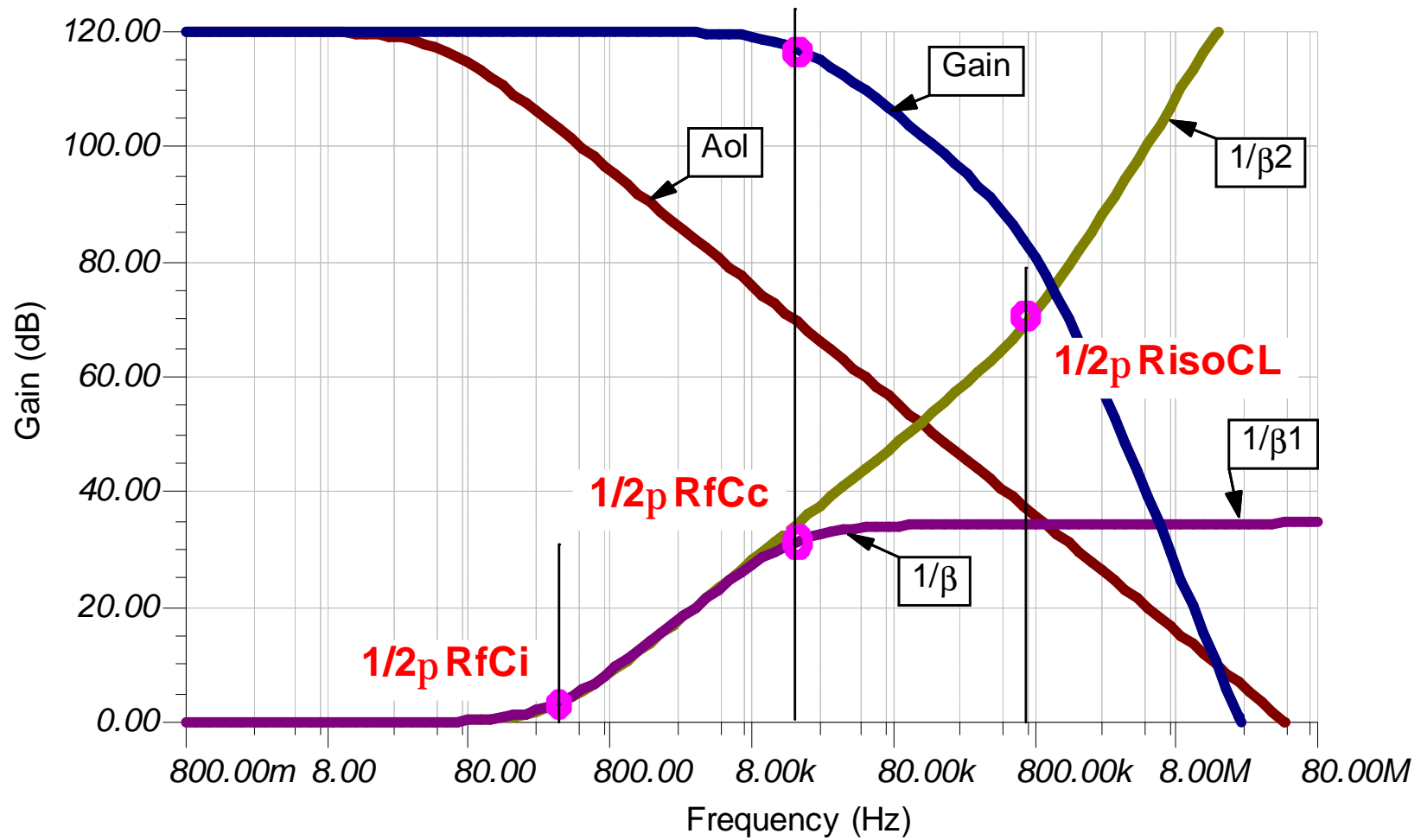
**The signal bandwidth is set by R1 and C1**







## How about Output Noise Gain?

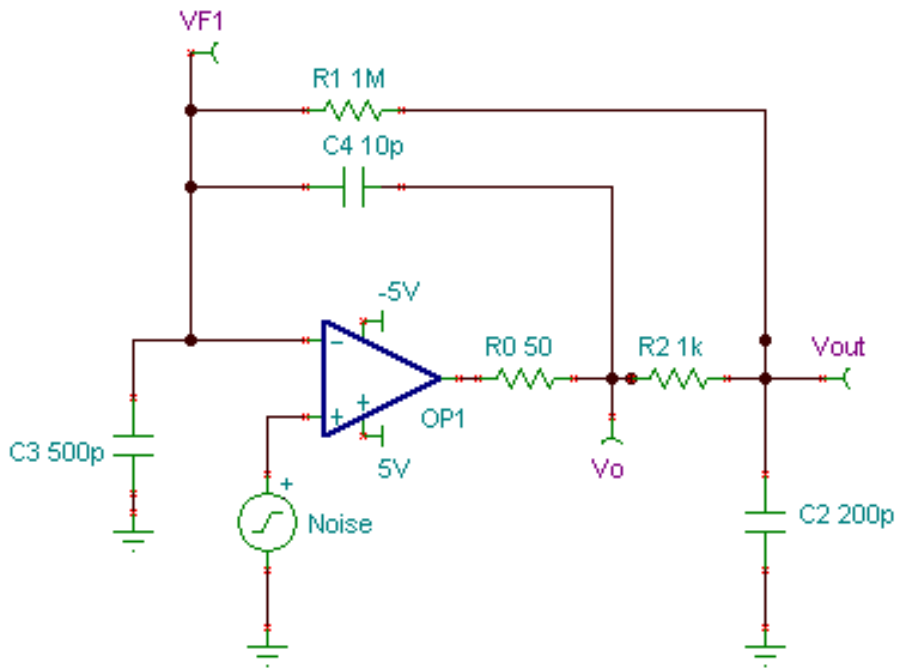


(1) At low frequency, C2 impedance is much larger than R2, the voltage difference between  $V_o$  and  $V_{out}$  is small, so the noise gain at  $v_{out}$  is restricted by  $1/\beta$  Curve.

(2) At high frequency, R2 and C2 is a filter which can reduce the noise at -20dB/dec.

(3) The output noise gain curve will **not** be restricted by Aol.




# Output Noise Gain

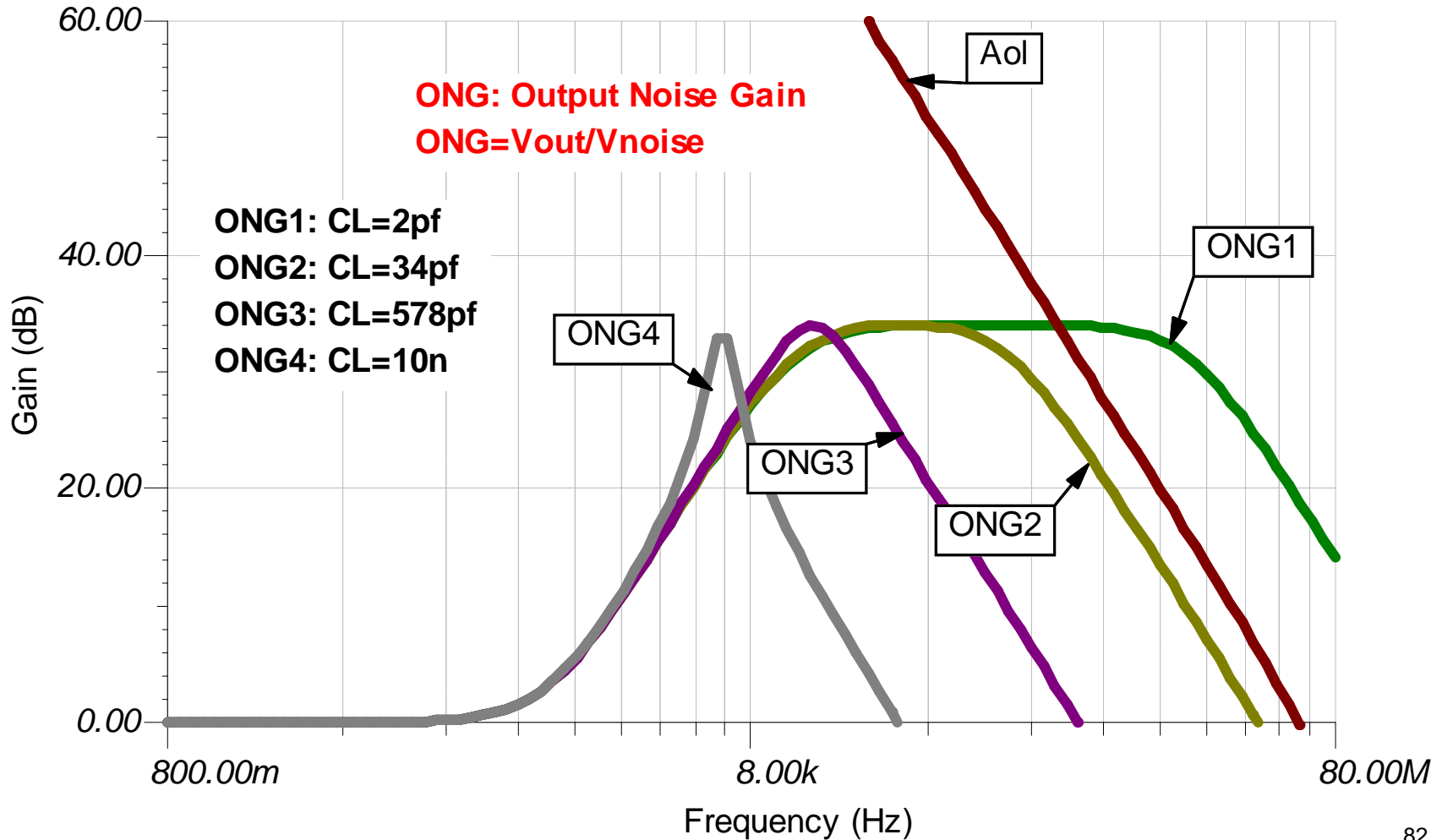




# CL vs Gain , $1/\beta$ and ONG

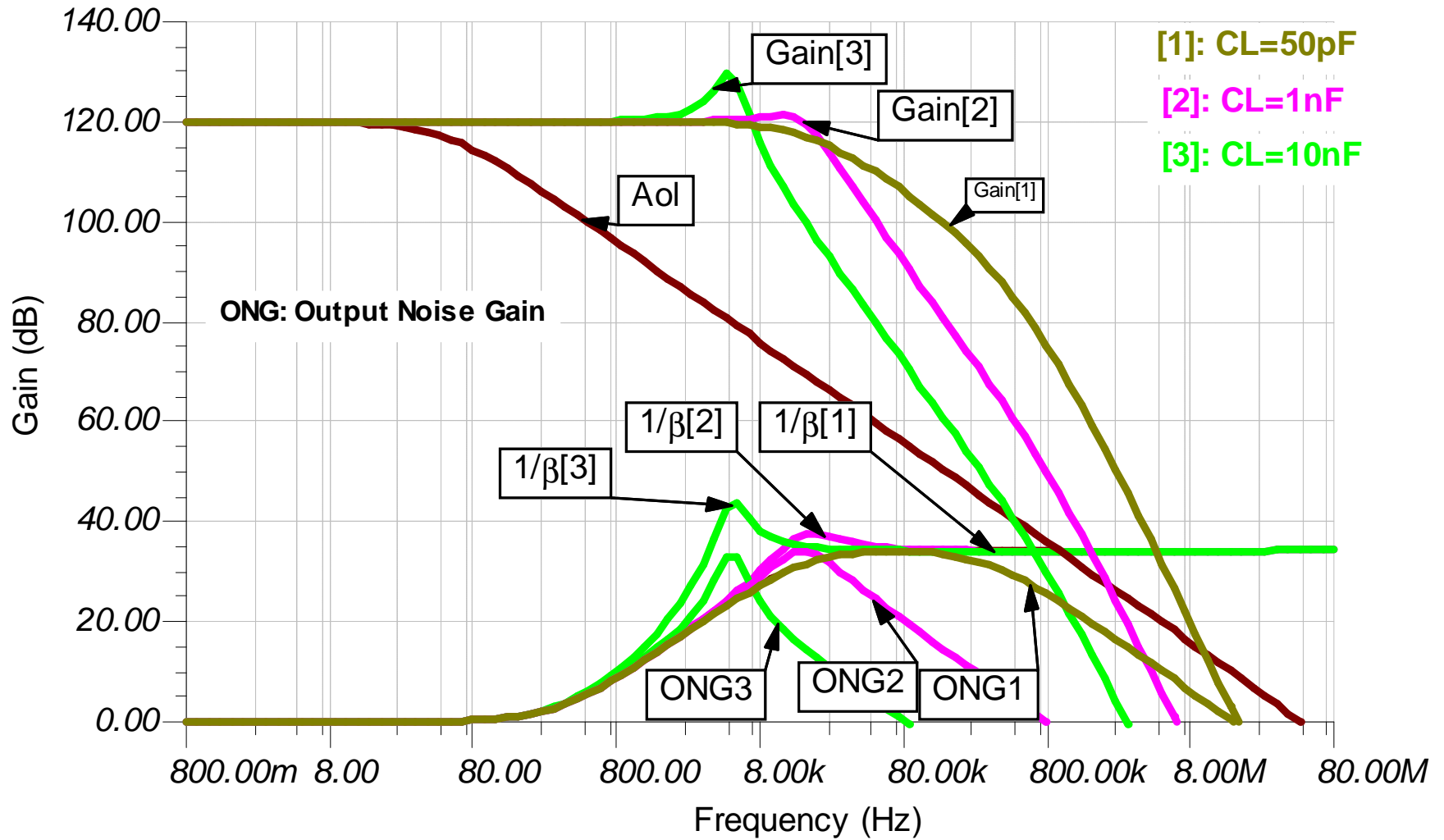



# How to optimize Riso and CL?

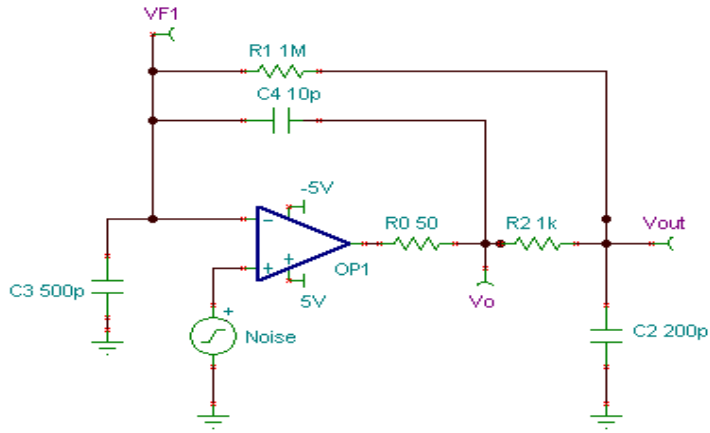


We need Riso and CL as filter in differential circuit to strict noise bandwidth.

.From simulation we can see, filter 's bandwidth can affect signal bandwidth.


In order not to decrease signal bandwidth. we can select:

$$R_{iso} * C_L = R_f * C_c$$

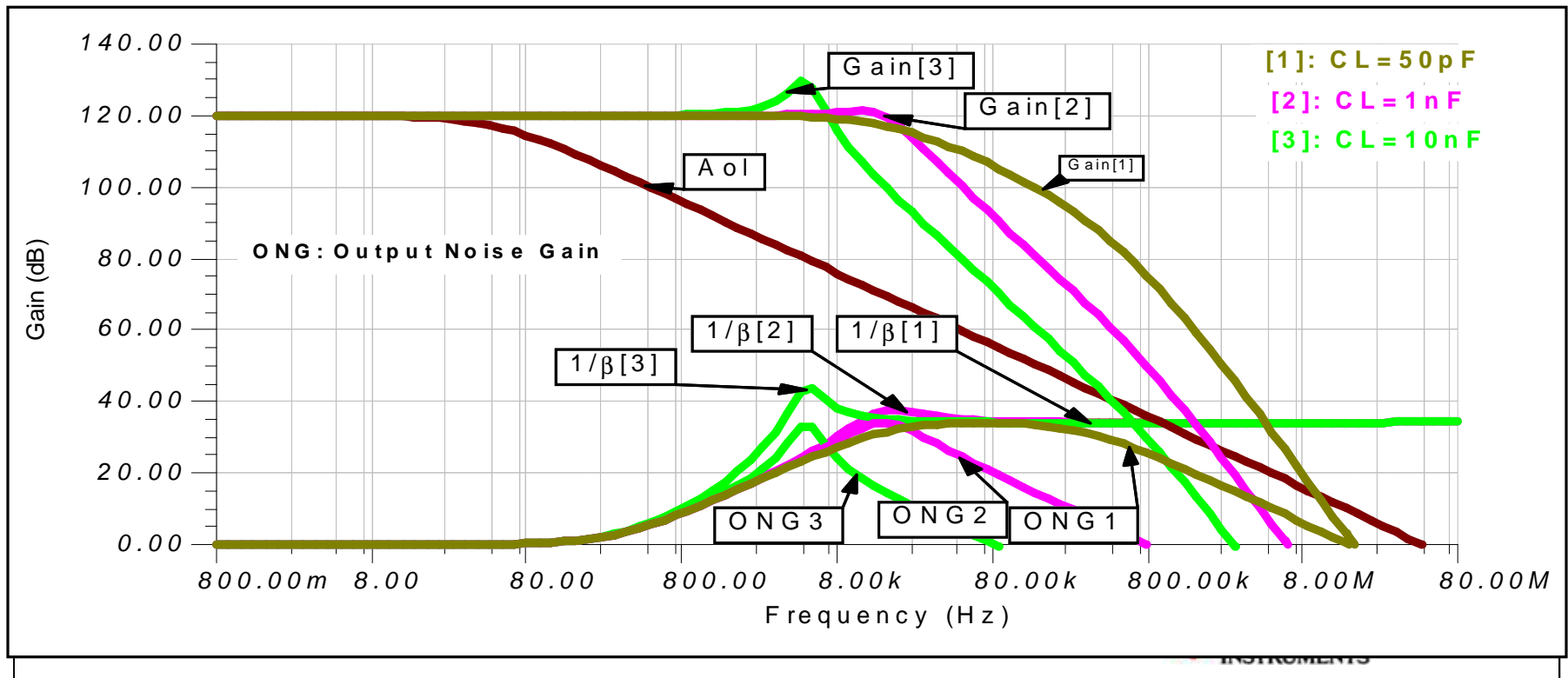




# Different?

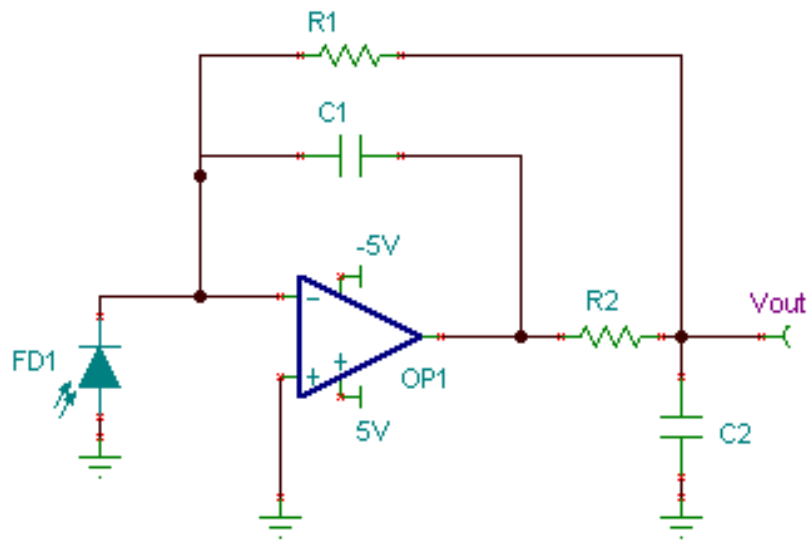

Dual Feedback

VS

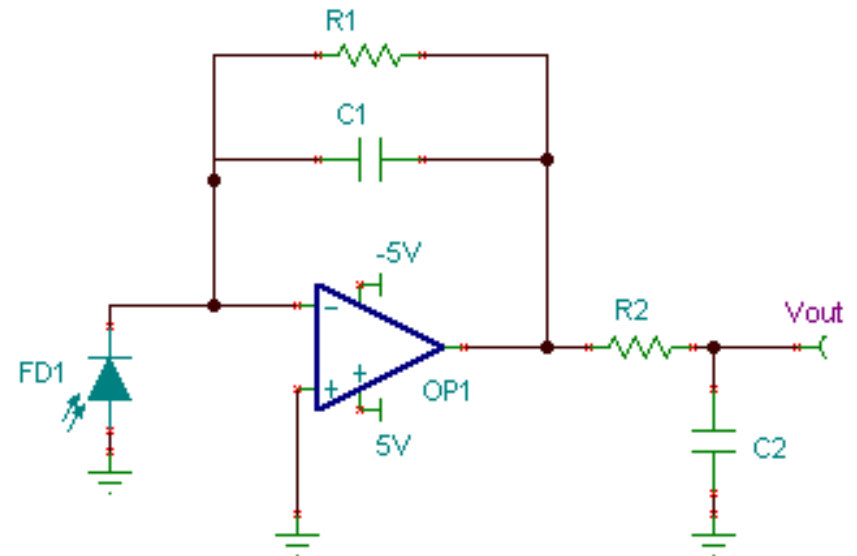


Normal


If  $R2 \ll R1$ , these two circuits are almost the same.



## Signal Gain

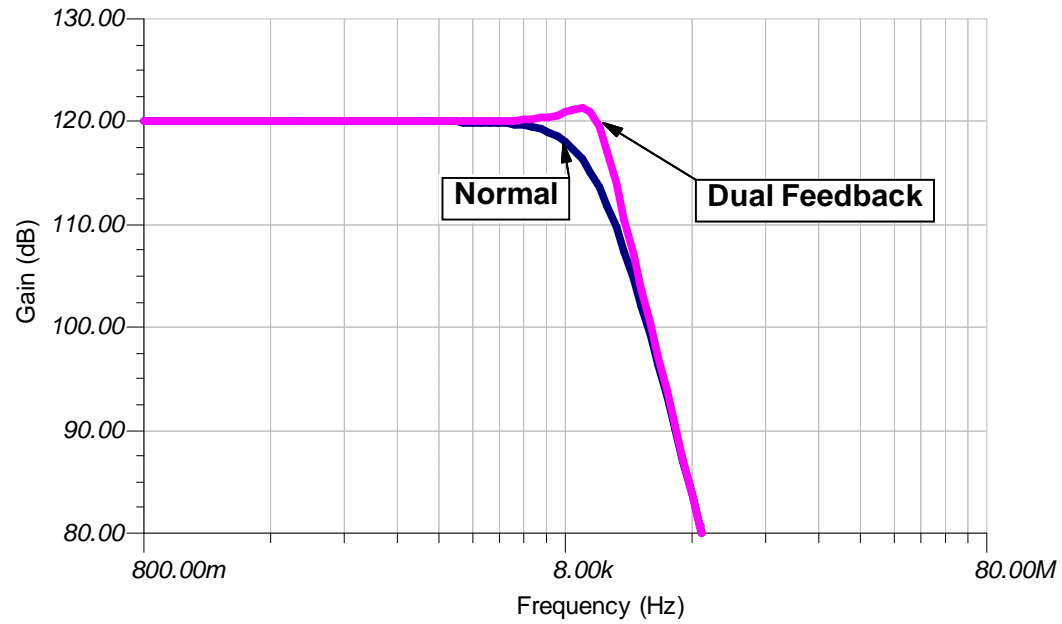


## Output Noise Gain

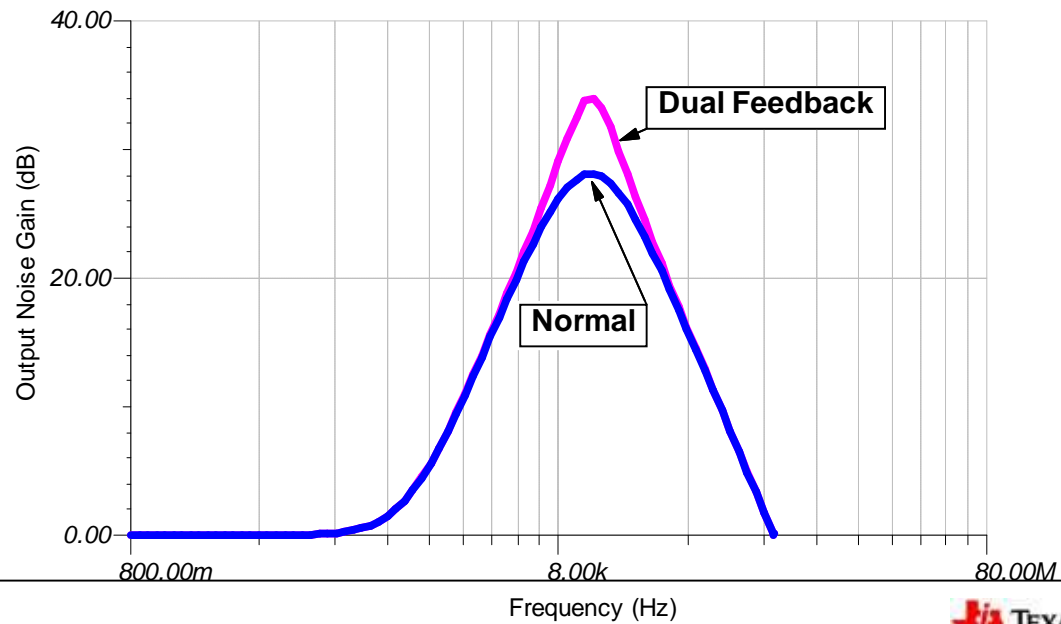




# Total Output Noise

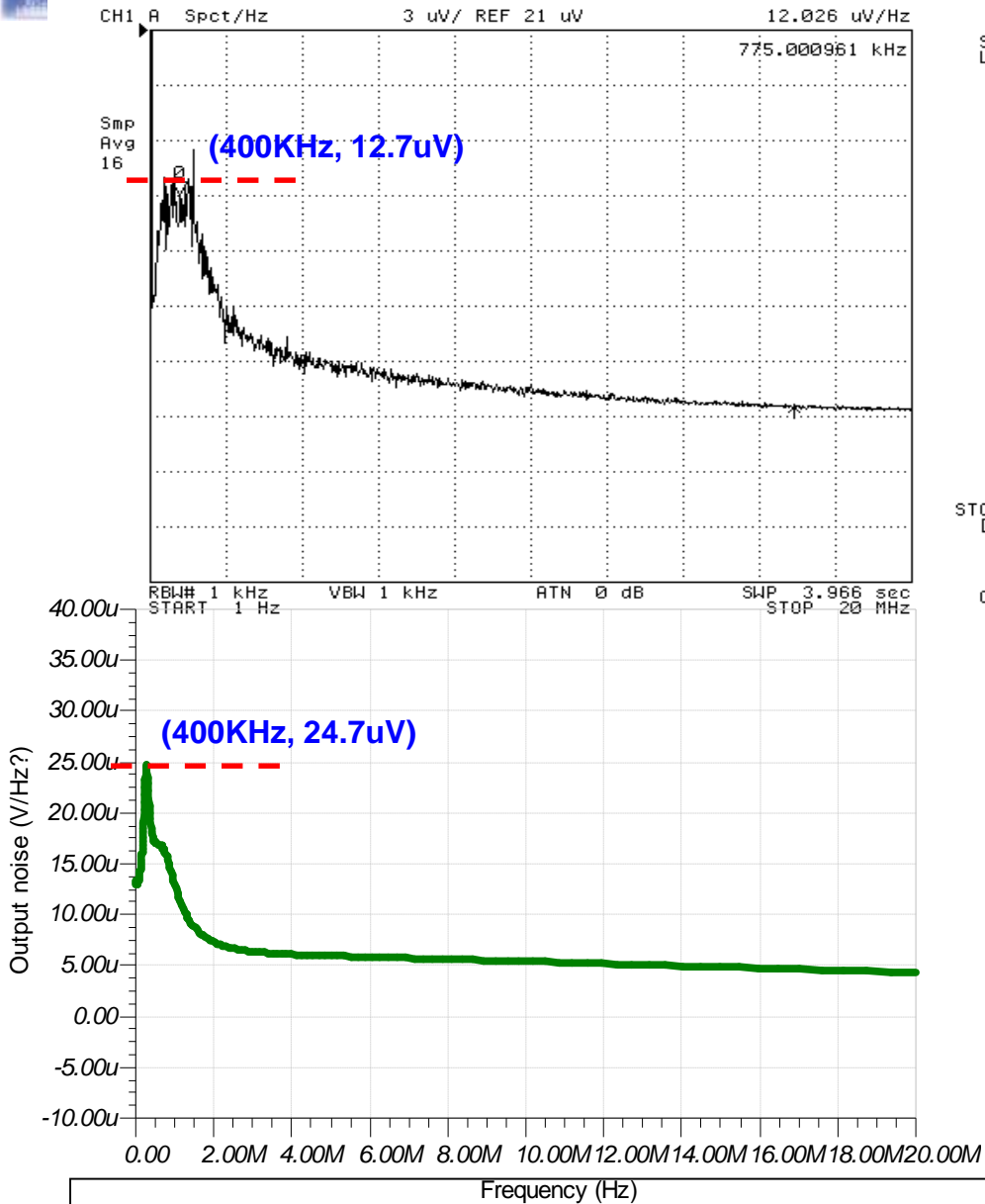

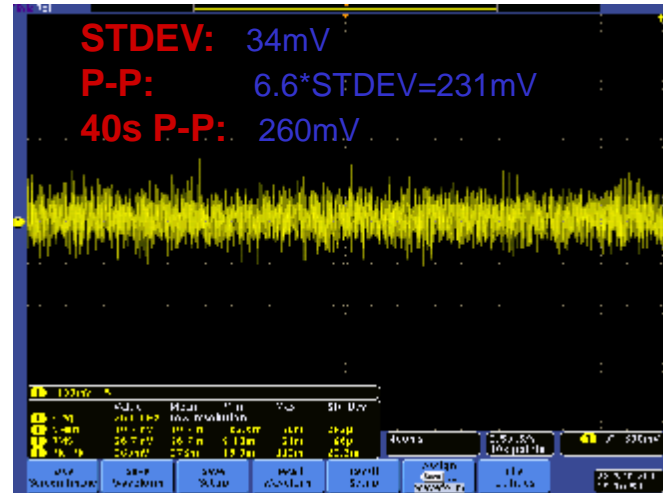SELECT LETTER  
SPACE  
BACK SPACE  
ERASE TITLE  
DONE  
STOR DEV [DISK]  
CANCEL



## Noise calculation:


In tina simulation, from 1Hz~20MHz  
INA128 output noise is: 207uV;

Each differential transimpedance  
amplifier output noise is:

$$\frac{\sqrt{\left(\frac{34000}{150}\right)^2 - 207^2}}{\sqrt{2}} = 65.302 \text{ uV}$$




# Noise simulation

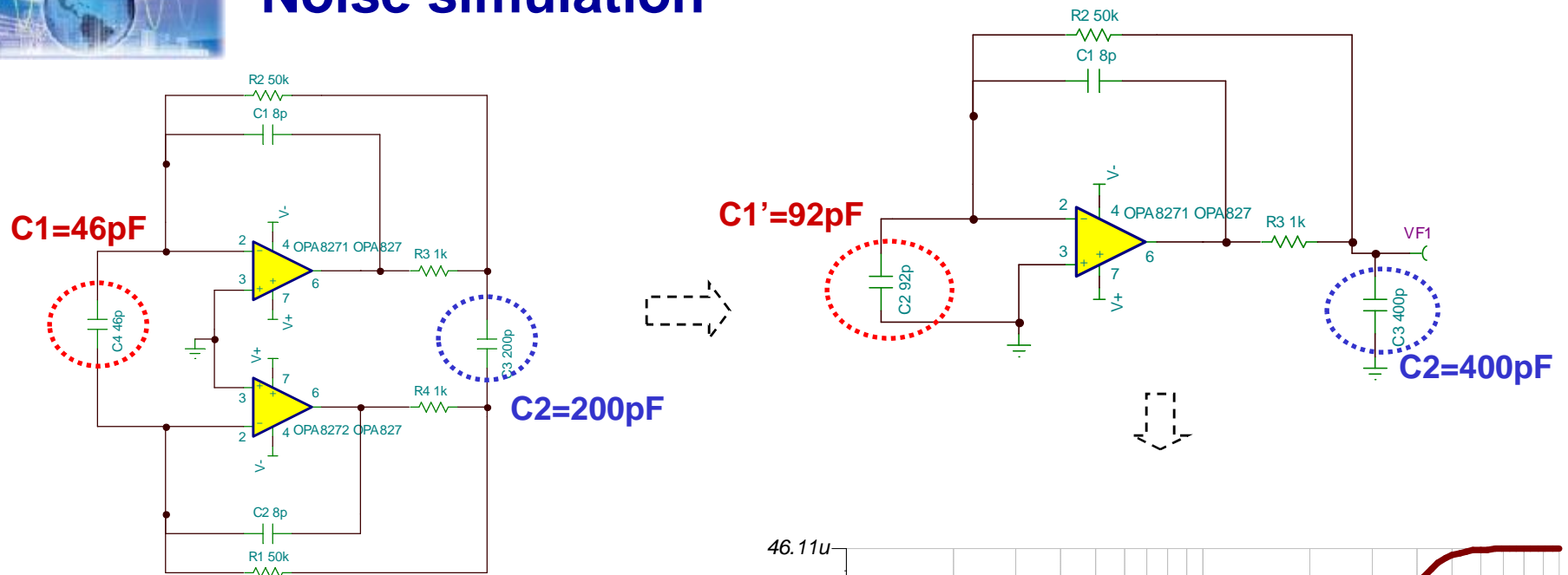

Simulation value: 46uV  
 Calculation value: 65uV

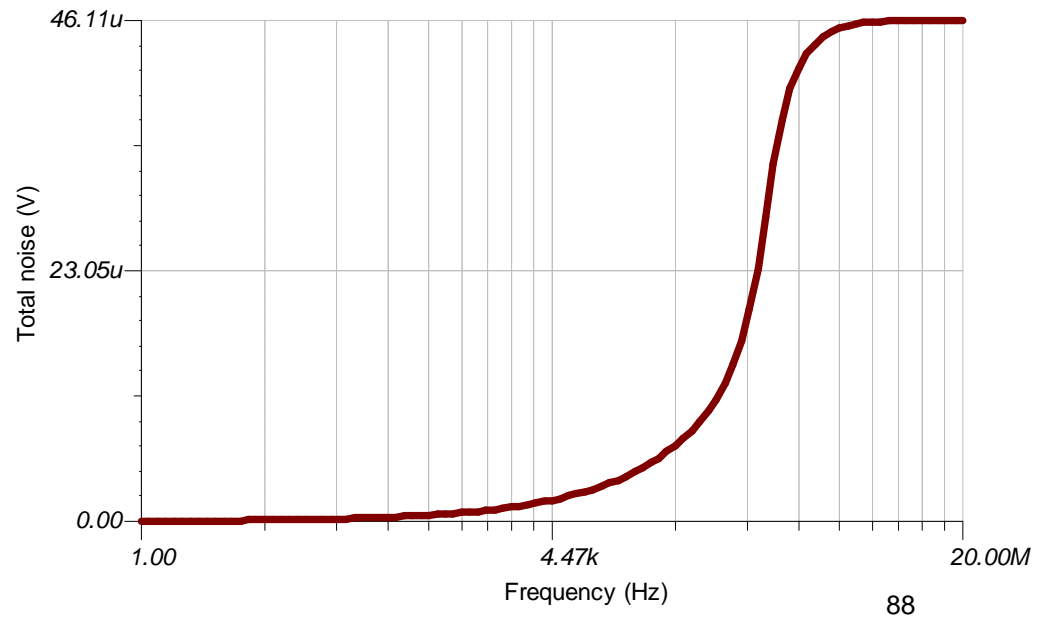The difference comes from photo diode junction capacitance value, in simulation we use 46uF, but photo diode junction capacitance will vary with temperature, frequency, bias voltage....







# References

- Jerald Graeme <Photodiode Amplifiers>
- Art Kay < Op-Amp Noise Calculation and Measurement >
- HAMAMATSU <Photodiode Technical Information>
- Tim Green <Operational amp stability>
- ...