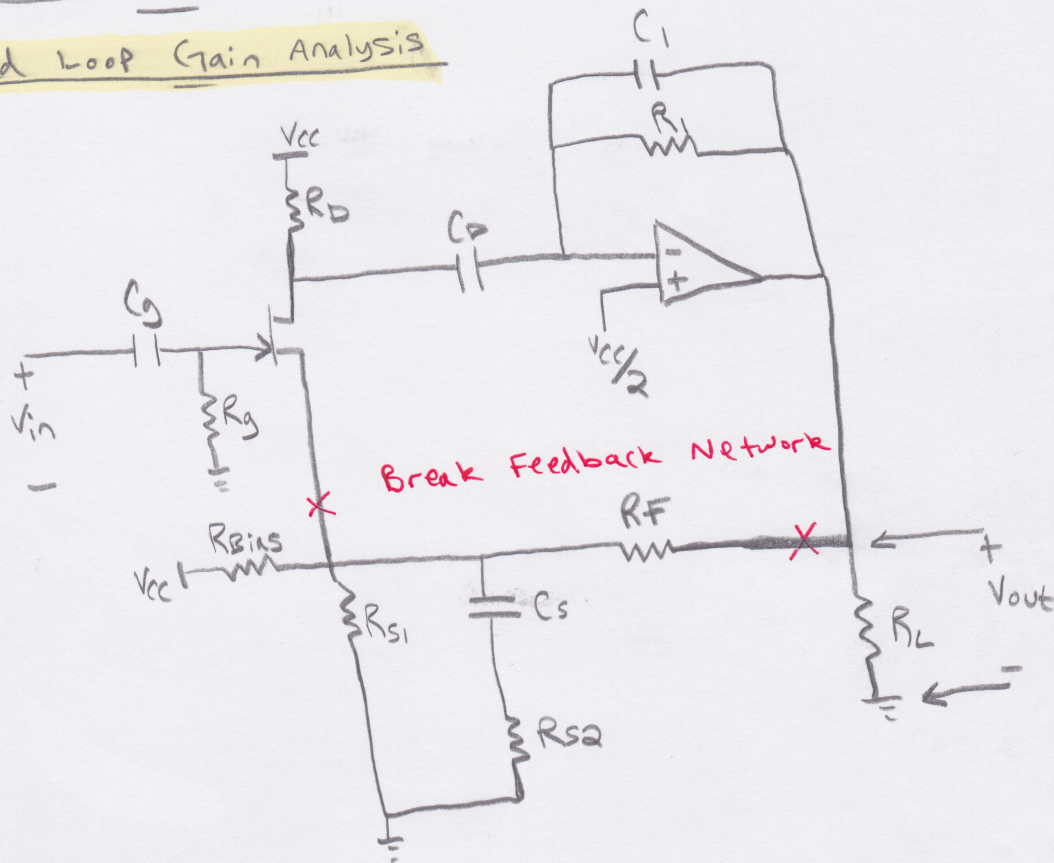


# JFE Pre-AMP Circuit

①

## Closed Loop Gain Analysis




Kill all DC sources and make gnd, For AC Analysis

From Gray and Meyer 5th Edition Page 557
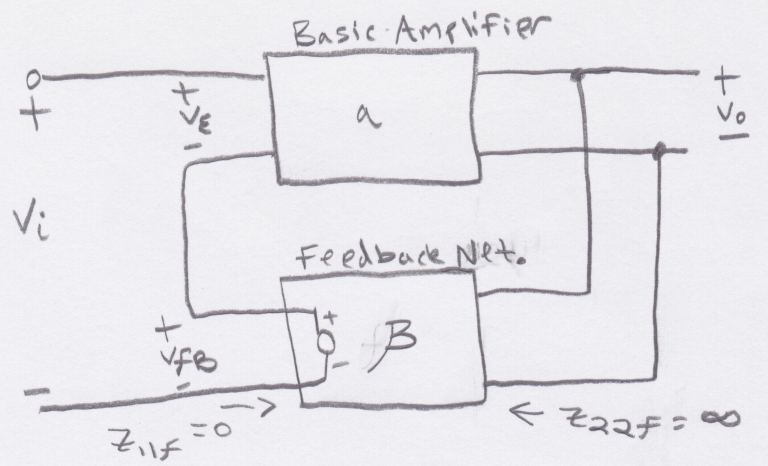
### Series - Shunt Feedback

Suppose it is required to design a feedback amplifier that stabilizes a voltage transfer function. That is, a given input voltage should produce a well defined proportional output voltage. This will require sampling the output voltage and feeding back a proportional voltage for comparison with the incoming voltage.







Series - shunt feedback

The  $\beta$  feedback Network shunts the output of the basic amplifier to sample  $V_o$ . The feedback voltage  $V_{FB}$  is connected in series with the input to allow comparison with  $V_i$ . The signal  $V_E$  is the difference between  $V_i$  and  $V_{FB}$  and is fed to the basic Amplifier.



Two-Port for  $\beta$

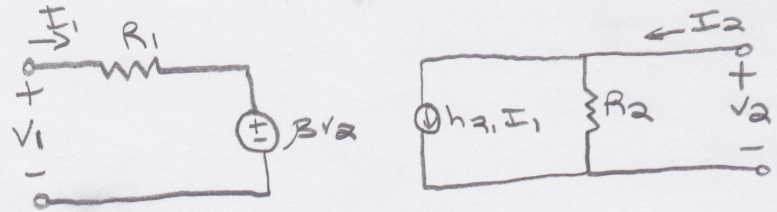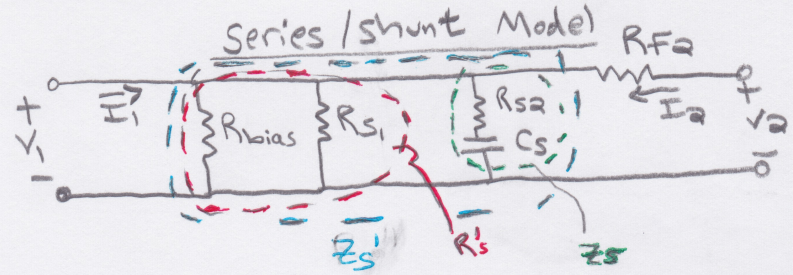

Eb's From Model

- $V_1 = I_1 R_1 + \beta V_2$
- $I_2 = \frac{V_2}{R_2} + h_{21} I_1$
- $R_1 = \frac{V_1}{I_1} \Big|_{V_2=0} = Z_S' \parallel R_F$
- $R_2 = \frac{V_2}{I_2} \Big|_{I_1=0} = R_F + Z_S'$
- $\beta = \frac{V_1}{V_2} \Big|_{I_1=0} = \frac{Z_S'}{Z_S' + R_F}$
- $\frac{1}{\beta} = 1 + \frac{R_F}{Z_S'}$

Example

- IF
- $R_{bias} = 2.5k\Omega$
  - $R_1 = 100\Omega$
  - $R_{s2} = 10\Omega$
  - $C_2 = 1mF$
  - $R_F = 10k$



$$R_s' = R_{bias} // R_{s1} = \frac{2.5k\Omega \cdot 100}{2.5k\Omega + 100} = 96\Omega$$

$$Z_s' = [R_{bias} // R_{s1}] // [R_{s2} + \frac{1}{sC_2}] = \frac{96\Omega \cdot [10\Omega + \frac{1}{s1m}]}{96\Omega + 10\Omega + \frac{1}{s1m}}$$

$$Z_s' = \frac{960 + \frac{9600}{s}}{106 + \frac{1000}{s}} = \frac{960[s + 100]}{106[s + 9.434]}$$

$$\therefore \beta = \frac{\left[ \frac{960[s + 100]}{106[s + 9.434]} \right]}{\frac{960[s + 100]}{106[s + 9.434]} + 10k}$$

$$\frac{1}{\beta} = \frac{\frac{960[s + 100]}{106[s + 9.434]} + 10k}{\frac{960[s + 100]}{106[s + 9.434]}}$$

$$\frac{1}{\beta} = \frac{10k + 1}{\frac{960[s + 100]}{106[s + 9.434]}}$$

$$\frac{1}{\beta} = 1 + \frac{106[s + 9.434] \cdot 10k}{960[s + 100]}$$


$$\frac{1}{\beta} = 105.168 \frac{V}{V} \quad \text{or} \quad 40.4376 \text{ dB} \quad @ \quad s \approx 0 \text{ Hz}$$

$$\frac{1}{\beta} = 1104.55 \frac{V}{V} \quad \text{or} \quad 60.86 \text{ dB} \quad @ \quad s \approx 1 \text{ kHz}$$



# A-circuit (Gain circuit)

5

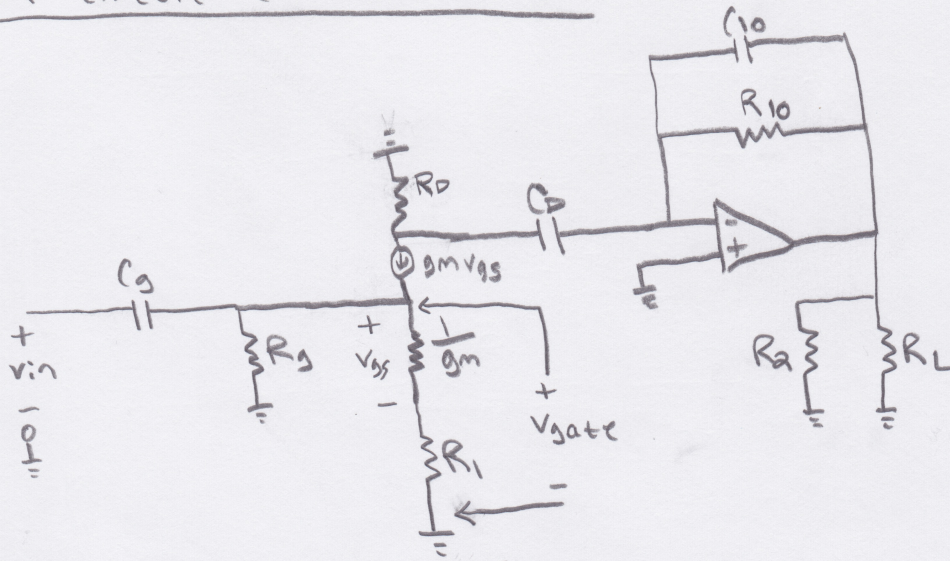

$$\frac{V_{gate}}{\frac{1}{g_m} + R_i} = g_m V_{gs}$$

$$V_{gate} = \frac{V_{in} \cdot [R_i + \frac{1}{g_m}] // R_g}{[R_i + \frac{1}{g_m}] // R_g + \frac{1}{sC_g}}$$

$$g_m V_{gs} = \left[ \frac{V_{in} \cdot [R_i + \frac{1}{g_m}] // R_g}{[R_i + \frac{1}{g_m}] // R_g + \frac{1}{sC_g}} \right]$$

if  $R_g \gg [R_i + \frac{1}{g_m}]$


$$g_m V_{gs} = \frac{V_{in}}{[R_i + \frac{1}{g_m}] + \frac{1}{sC_g}}$$



# Equations without $R_g$

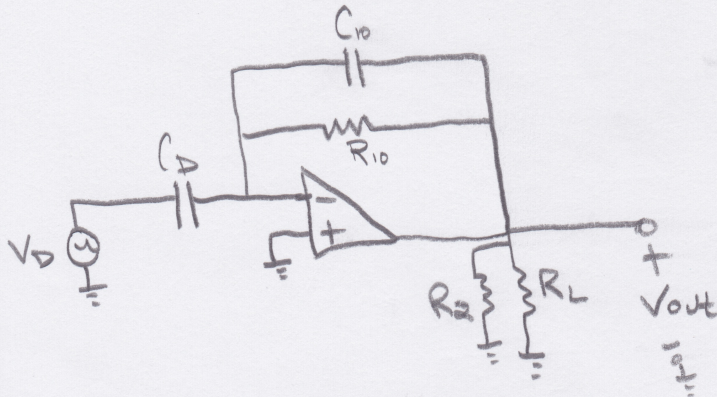(6)

$$V_D = -g_m V_{GS} \cdot R_D // Z_{CD} = \frac{-v_{in} R_D // Z_{CD}}{\left[ R_1 + \frac{1}{g_m} \right] + \frac{1}{sC_g}}$$




$$V_{out} = -V_D \frac{[Z_{CD} // R_{D0}]}{Z_{CD}} = - \left[ \frac{-v_{in} \cdot R_D // Z_{CD}}{\left[ R_1 + \frac{1}{g_m} \right] + \frac{1}{sC_g}} \right] \cdot \frac{[Z_{CD} // R_{D0}]}{Z_{CD}}$$

$$A_{ol} = \frac{V_{out}}{v_{in}} = \frac{R_D // Z_{CD}}{\left[ R_1 + \frac{1}{g_m} \right] + \frac{1}{sC_g}} \cdot \frac{[Z_{CD} // R_{D0}]}{Z_{CD}}$$



Equations With Rg
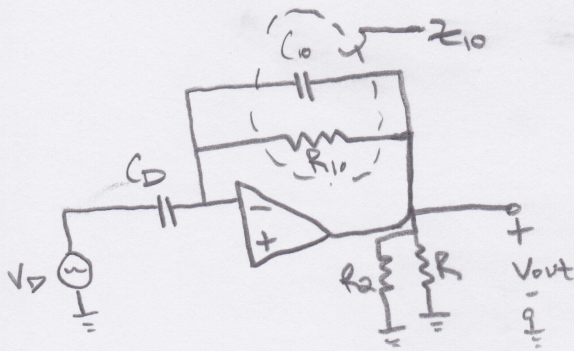
$$V_D = -g_m V_{gs} \cdot R_D // Z_{CD} = - \frac{v_{in} \cdot [R_i + \frac{1}{g_m}] // R_g}{[R_i + \frac{1}{g_m}] // R_g + \frac{1}{sC_g}} \cdot R_D // Z_o \quad (7)$$



$$V_{out} = -V_D \cdot \frac{[Z_{C10} // R_{10}]}{Z_{CD}}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{[R_i + \frac{1}{g_m}] // R_g}{[R_i + \frac{1}{g_m}] // R_g + \frac{1}{sC_g}} \cdot \frac{R_D // Z_{CD}}{Z_D} \cdot \frac{Z_o}{Z_{CD}}}{[R_i + \frac{1}{g_m}]}$$

$R_{i,prime}$

$$A_{ol} = \frac{V_{out}}{V_{in}} = \frac{R_{in} \cdot Z_D}{(R_{in} + Z_{Cg}) R_{i,prime}} \cdot \frac{Z_o}{Z_{CD}}$$

$$A_{cl} = \frac{A_{ol}}{1 + A_{ol} \beta} \quad \text{Plug into Matlab}$$