

INA148 & INA149 Transfer function math

General derivation of inverting T network

Inverting T network amp

$$\frac{0 - V_{in}}{R_{in}} + \frac{0 - V_x}{R_f} = 0 \quad \text{Equ 1}$$

$$V_x = \frac{-(R_f \cdot V_{in})}{R_{in}} \quad \text{Solve Equ 1 for } V_x$$


$$\frac{V_x - 0}{R_f} + \frac{V_x}{R_x} + \frac{V_x - V_{out}}{R_f} = 0 \quad \text{Equ 2}$$

$$-\frac{V_{out}}{R_f} - \left(\frac{2 \cdot V_{in}}{R_{in}} + \frac{R_f \cdot V_{in}}{R_{in} \cdot R_x} \right) = 0 \quad \text{Substitute Equ 1 into Equ 2}$$

$$G_{invT} = \frac{V_{out}}{V_{in}} = \frac{-R_f}{R_{in}} \cdot \left(2 + \frac{R_f}{R_x} \right) \quad \text{Solve for } V_{out}/V_{in} \text{ and simplify}$$

$$V_{out} = G_{invT} \cdot V_{in} = \frac{-R_f}{R_{in}} \cdot \left(2 + \frac{R_f}{R_x} \right) V_{in} \quad \text{General Relationship}$$
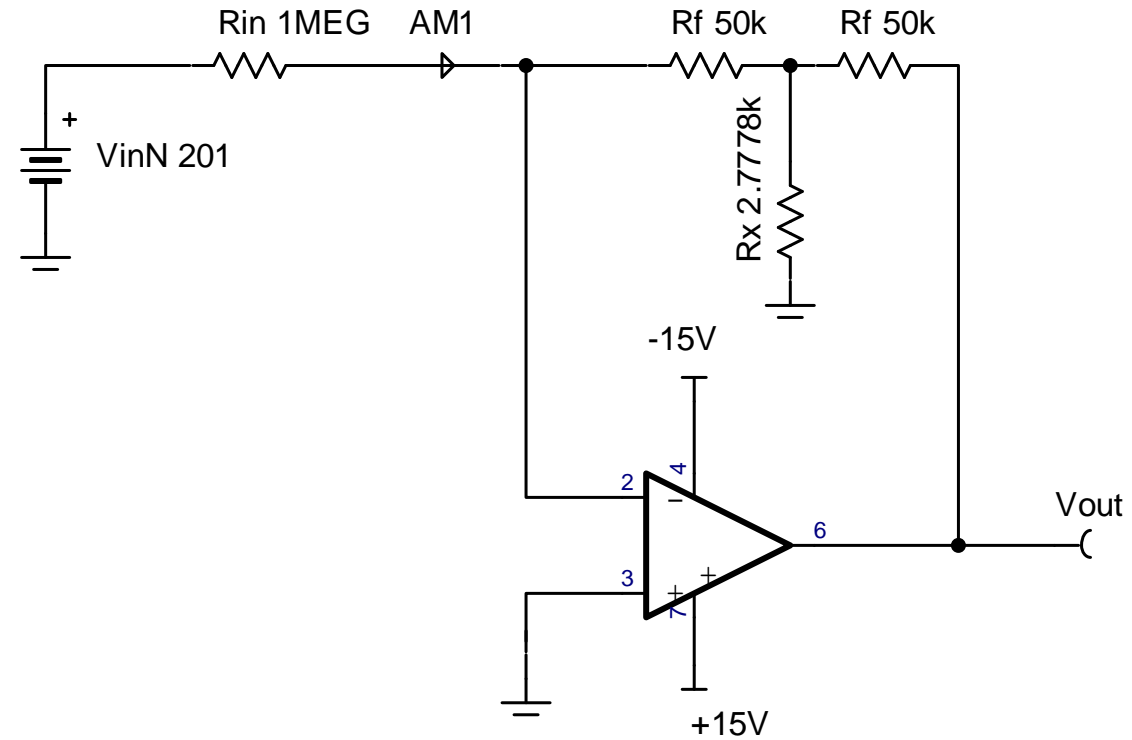
$$V_{out} = \frac{-50 \text{ k}\Omega}{1 \text{ M}\Omega} \left(\left(2 + \frac{50 \text{ k}\Omega}{2.7778 \text{ k}\Omega} \right) \right) = -V_{in} \quad \text{Equ 3: INA148 example}$$



General derivation of non-inverting t-network

$$\frac{V_{in} - 0}{R_{in}} + \frac{V_{in} - V_x}{R_f} = 0 \quad \text{Equ 4}$$

$$V_x = \frac{(R_{in} + R_f) \cdot V_{in}}{R_{in}} \quad \text{Solve Equ 4 for } V_x$$


$$\frac{V_x - V_{in}}{R_f} + \frac{V_x}{R_x} + \frac{V_x - V_{out}}{R_f} = 0 \quad \text{Equ 5}$$

$$-\frac{V_{out}}{R_f} + \frac{V_{in}}{R_f} + \frac{2 \cdot V_{in}}{R_{in}} + \frac{V_{in}}{R_x} + \frac{R_f \cdot V_{in}}{R_{in} \cdot R_x} = 0 \quad \text{Substitute 4 into 5}$$


$$G_{nonI} = \left(1 + \frac{R_f}{R_x}\right) + \frac{R_f}{R_{in}} \left(2 + \frac{R_f}{R_x}\right) \quad \text{Solve for gain and simplify}$$

$$G_{nonI} := \left(1 + \frac{50 \text{ k}\Omega}{2.7778 \text{ k}\Omega}\right) + \frac{50 \text{ k}\Omega}{1 \text{ M}\Omega} \left(2 + \frac{50 \text{ k}\Omega}{2.7778 \text{ k}\Omega}\right) = 20$$
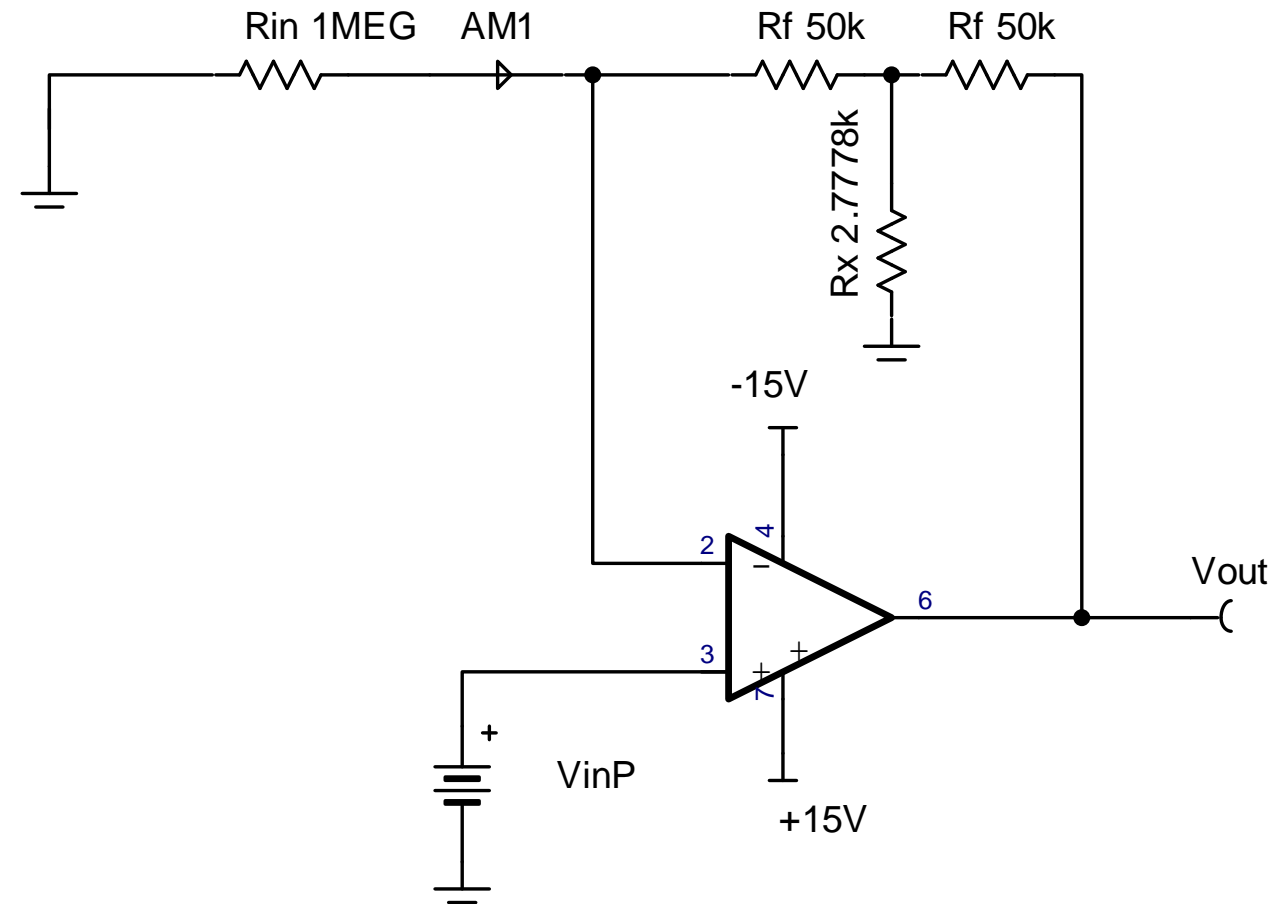
$$V_{out} = 20 V_{in} \quad \text{For INA148 example}$$



INA148 Gain – use superposition

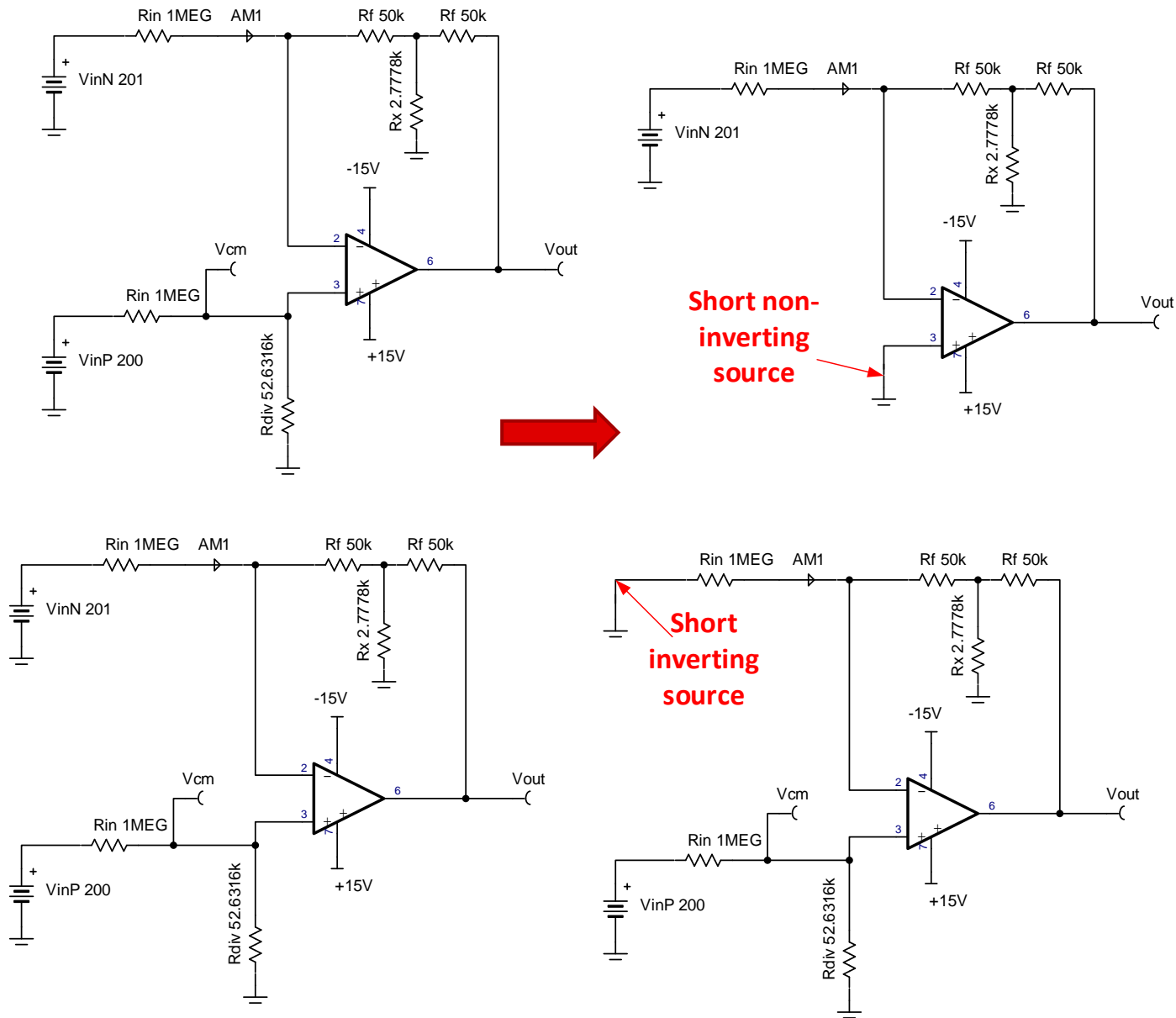

$$V_{outN} = -V_{inN}$$

Equ 3: Noninverting with voltage divider for INA148 example

$$V_{outP} = G_{nonI} \cdot \left(V_{inP} \cdot \frac{R_{div}}{R_{div} + R_{in}} \right) = 20 \quad \text{with voltage divider}$$

$$V_{outP} = G_{nonI} \cdot \left(\frac{R_{div}}{R_{div} + R_{in}} \right) \cdot V_{inP} = 20 \cdot \left(\frac{1}{20} \right) \cdot V_{inP} = V_{inP}$$

$$V_{outP} = V_{inP} \quad \text{Equ 6: Noninverting with voltage divider}$$

$$V_{outN} + V_{outP} = V_{inP} - V_{inN} \quad \text{Final result: add equation 3 and 6 from superposition}$$

$$\frac{V_{outN} + V_{outP}}{V_{inP} - V_{inN}} = 1 \quad \text{Differential gain} = 1$$

INA149 derivation

$$\frac{V_{cm} - V_{inN}}{R_{in}} + \frac{V_{cm}}{R_x} + \frac{V_{cm} - V_{out}}{R_f} = 0$$

Equ 1: node at Vx

$$R_{div} = \frac{R_f \cdot R_x}{R_f + R_x}$$

Equ 2: let $R_{div} = R_f \parallel R_x$

$$V_{cm} = \frac{R_{div}}{R_{div} + R_{in}} \cdot V_{inP}$$


Equ 3: Voltage divider

$$V_{cm} = \frac{R_f \cdot R_x \cdot V_{inP}}{(R_{in} + R_f) \cdot R_x + R_f \cdot R_{in}}$$


Equ 4: substitute 2 into 3

$$V_{out} = \frac{R_f}{R_{in}} \cdot (V_{inP} - V_{inN})$$


Equ 5: substitute 4 into 1

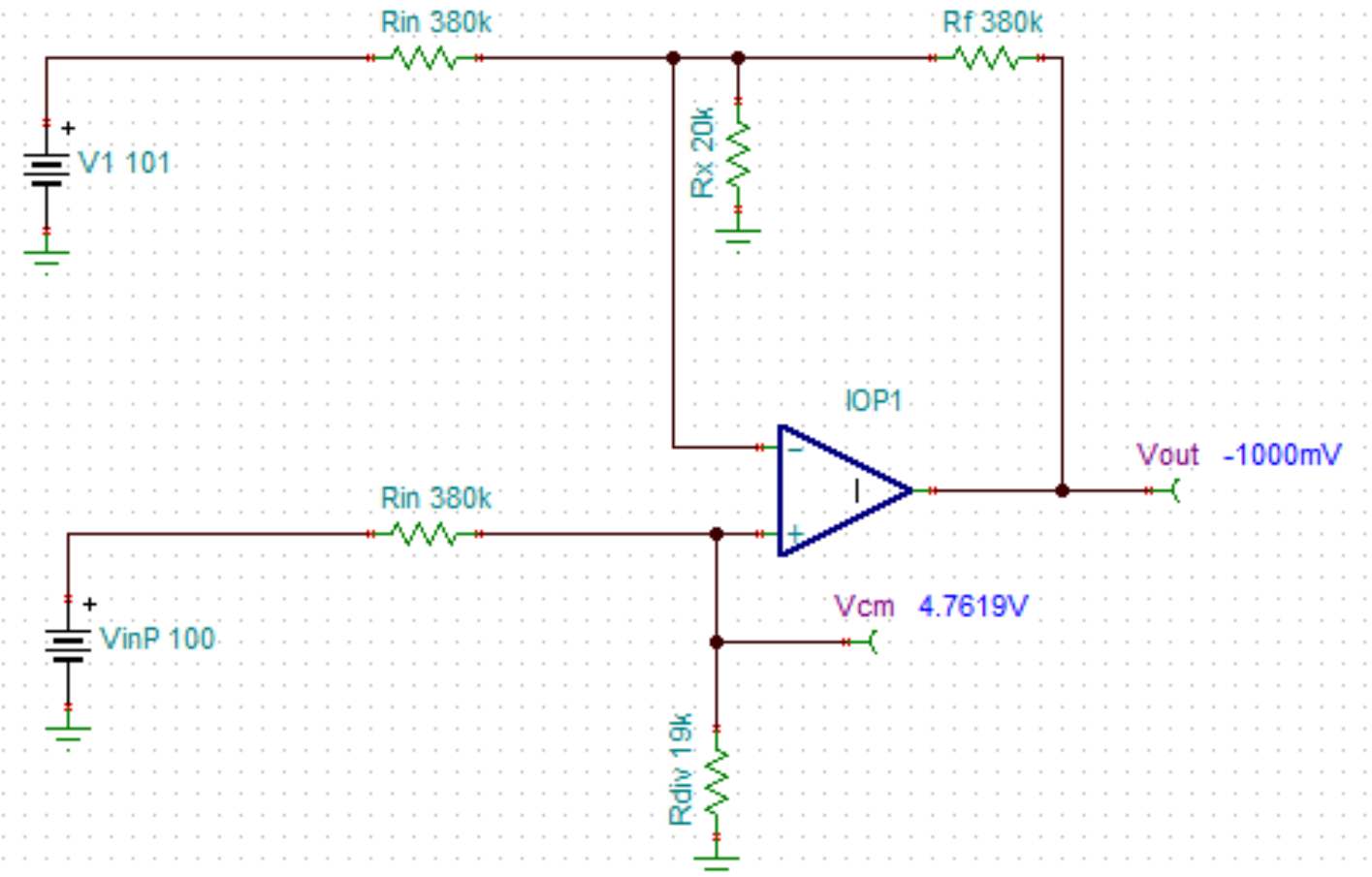

Common mode applied to the amplifiers

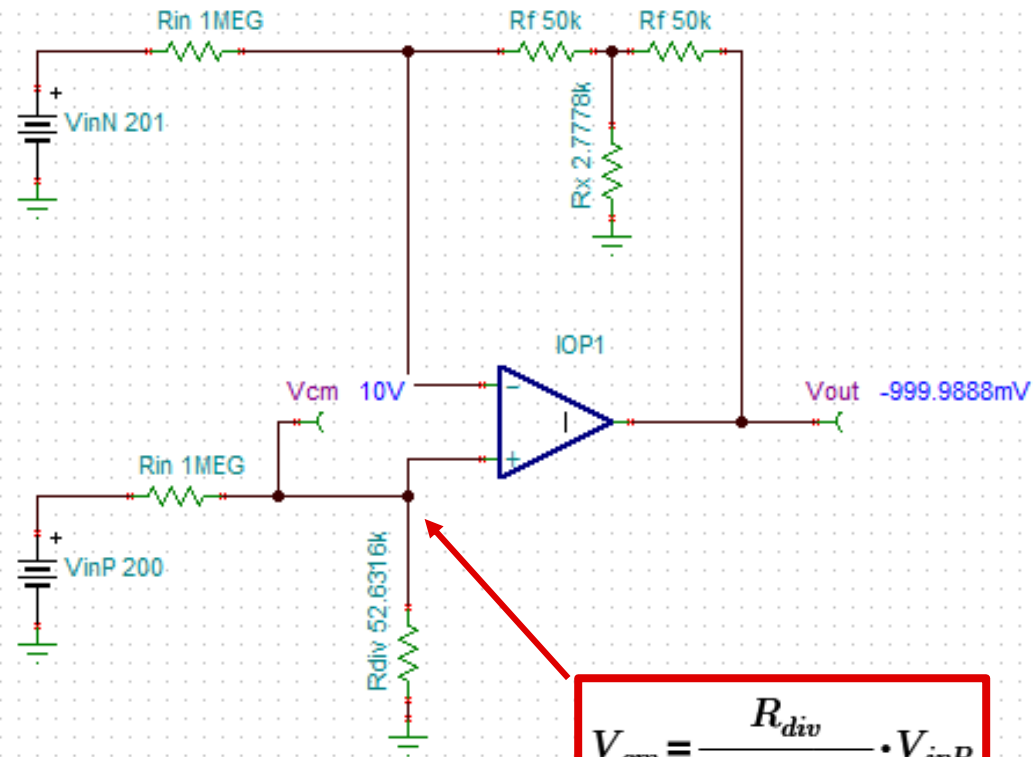
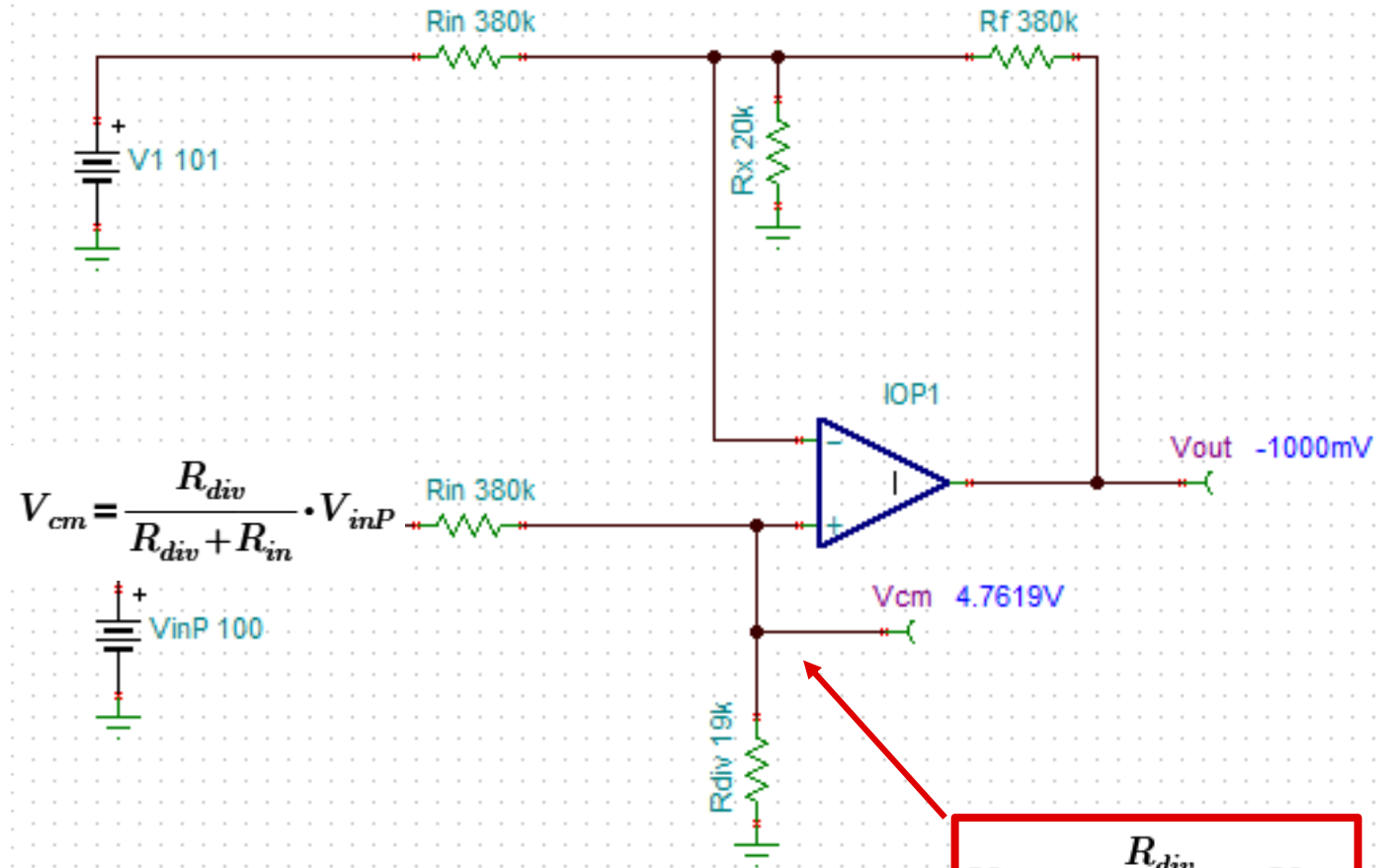
$$V_{cm} = \frac{R_{div}}{R_{div} + R_{in}} \cdot V_{inP}$$



$$V_{cm} = \frac{R_{div}}{R_{div} + R_{in}} \cdot V_{inP}$$

$$V_{cm} = \frac{R_{div}}{R_{div} + R_{in}} \cdot V_{inP}$$