

TL072



Application review

Art Kay

12-22-2024



Simple version of IC5B circuit

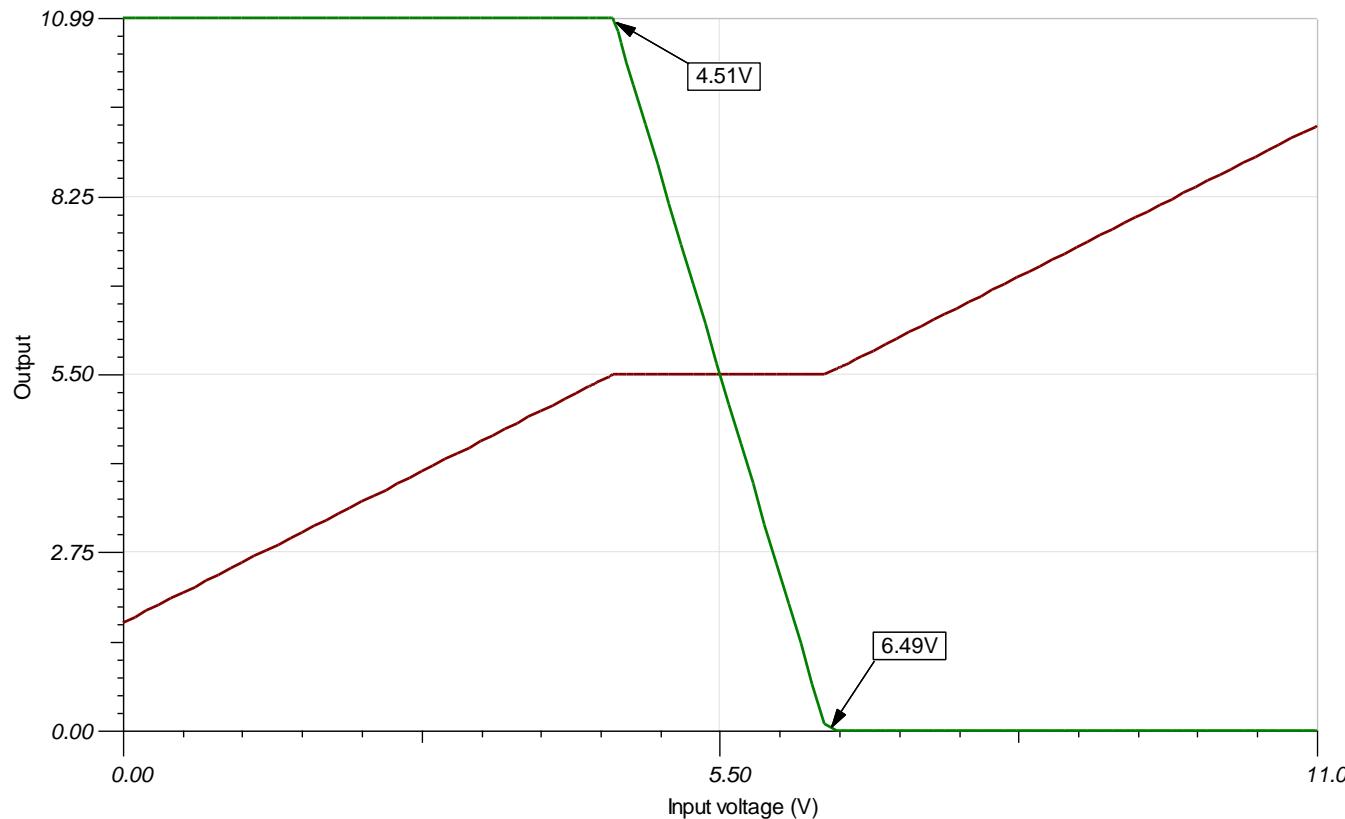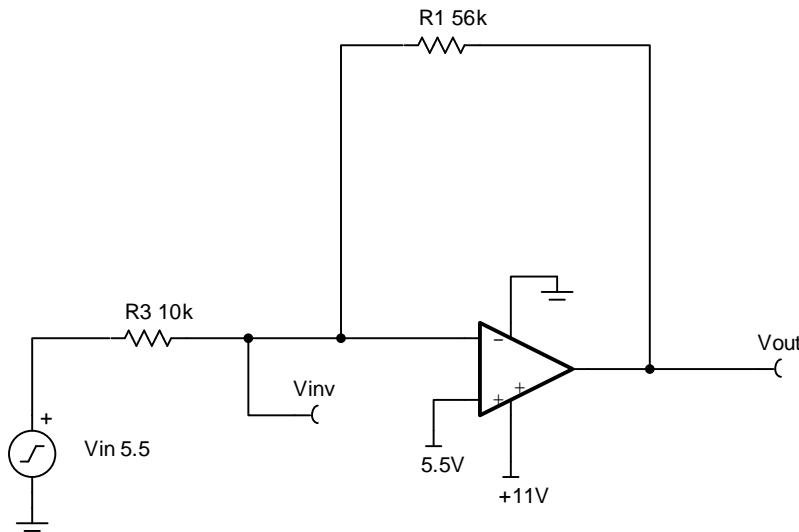

Here is the circuit without the diodes. Note that the output is only linear for input signals from the range of 4.51V to 6.49V. This is predicted with both simulation and calculation

$$R_f := 56$$

$$R_g := 10$$

$$G_{inv} := \frac{-R_f}{R_g} = -5.6$$

$$G_{non} := \frac{R_f}{R_g} + 1 = 6.6$$

$$V_{out} = G_{inv} \cdot V_{in} + (5.5) \cdot G_{non}$$

$$V_{out} = -5.6 V_{in} + 36.3$$


$$\text{solve for } V_{out} = 0V$$

$$0V = -5.6 V_{in} + 36.3 \xrightarrow{\text{solve}, V_{in}} 6.482142$$

$$\text{solve for } V_{out} = 11V$$

$$11V = -5.6 V_{in} + 36.3 \xrightarrow{\text{solve}, V_{in}} 4.5178571$$

Simple version of IC5B circuit (V_{inv})

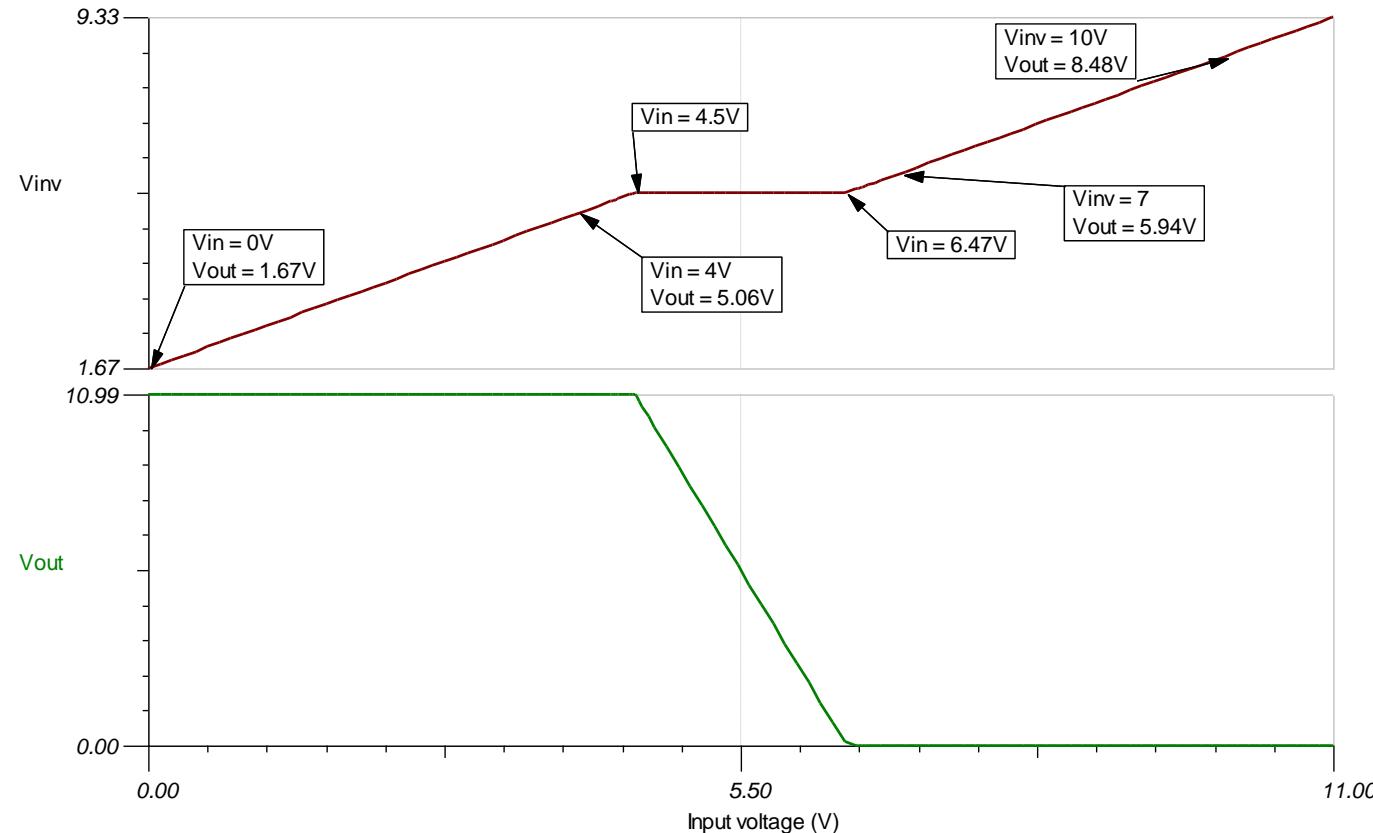

Below 4.5V and above 6.47V the circuit is open loop. To understand V_{inv} in this case you can just erase the op amp and think of this as a series circuit with two power supplies: V_{out} and V_{in} . The equations in these two regions are given to the right.

for inputs below 4.5V

$$V_{inv} = (V_{out} - V_{in}) \cdot \frac{R_3}{R_1 + R_3} + V_{in}$$

for $V_{in} = 0V$

$$V_{inv0} := (11 - 0) \cdot \left(\frac{10}{56 + 10} \right) + 0 = 1.667$$

for $V_{in} = 4V$

$$V_{inv4} := (11 - 4) \cdot \left(\frac{10}{56 + 10} \right) + 4 = 5.061$$

for inputs above 6.47V

$$V_{inv} = (V_{in}) \cdot \frac{R_1}{R_1 + R_3}$$


for $V_{in} = 7V$

$$V_{inv7} := (7) \cdot \left(\frac{56}{56 + 10} \right) = 5.939$$


for $V_{in} = 10V$

$$V_{inv10} := (10) \cdot \left(\frac{56}{56 + 10} \right) = 8.485$$



Circuit IC5B (Vout and Vinv only)

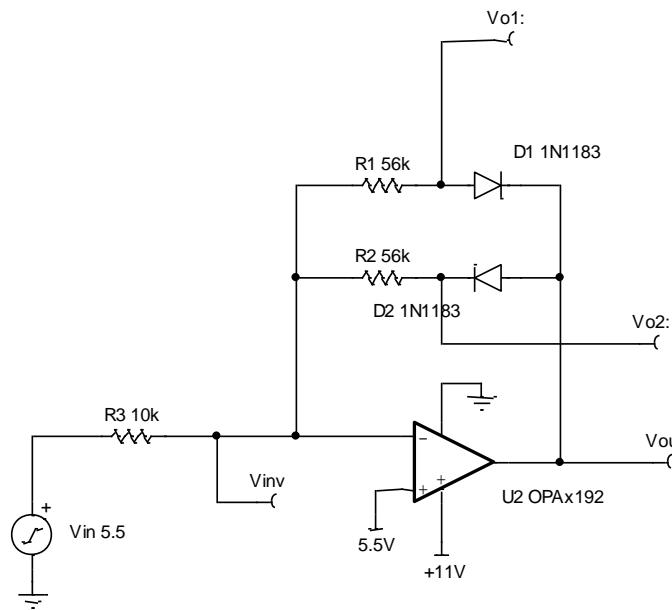



Add the diodes back in and look at the output pin. Notice from the output pin perspective, the two circuits are basically the same. If you look closely at the circuit with diodes you will see a small non-linearity when the output signal passes through 5.5V. The non-linearity occurs when switching from one diode to the other diode. In this circuit either one of the two diodes are always on, but they are never on at the same time.

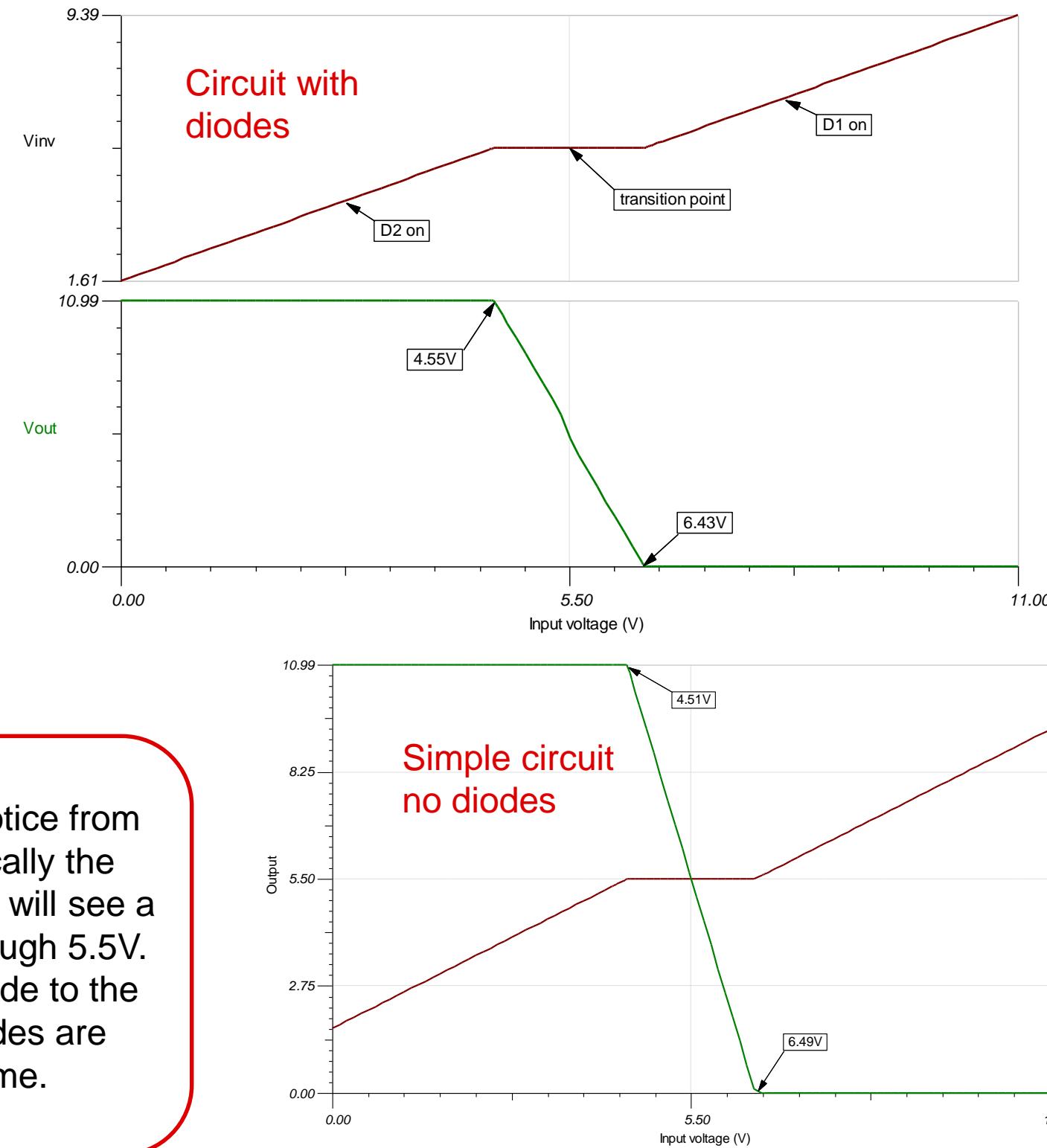


Circuit IC5B

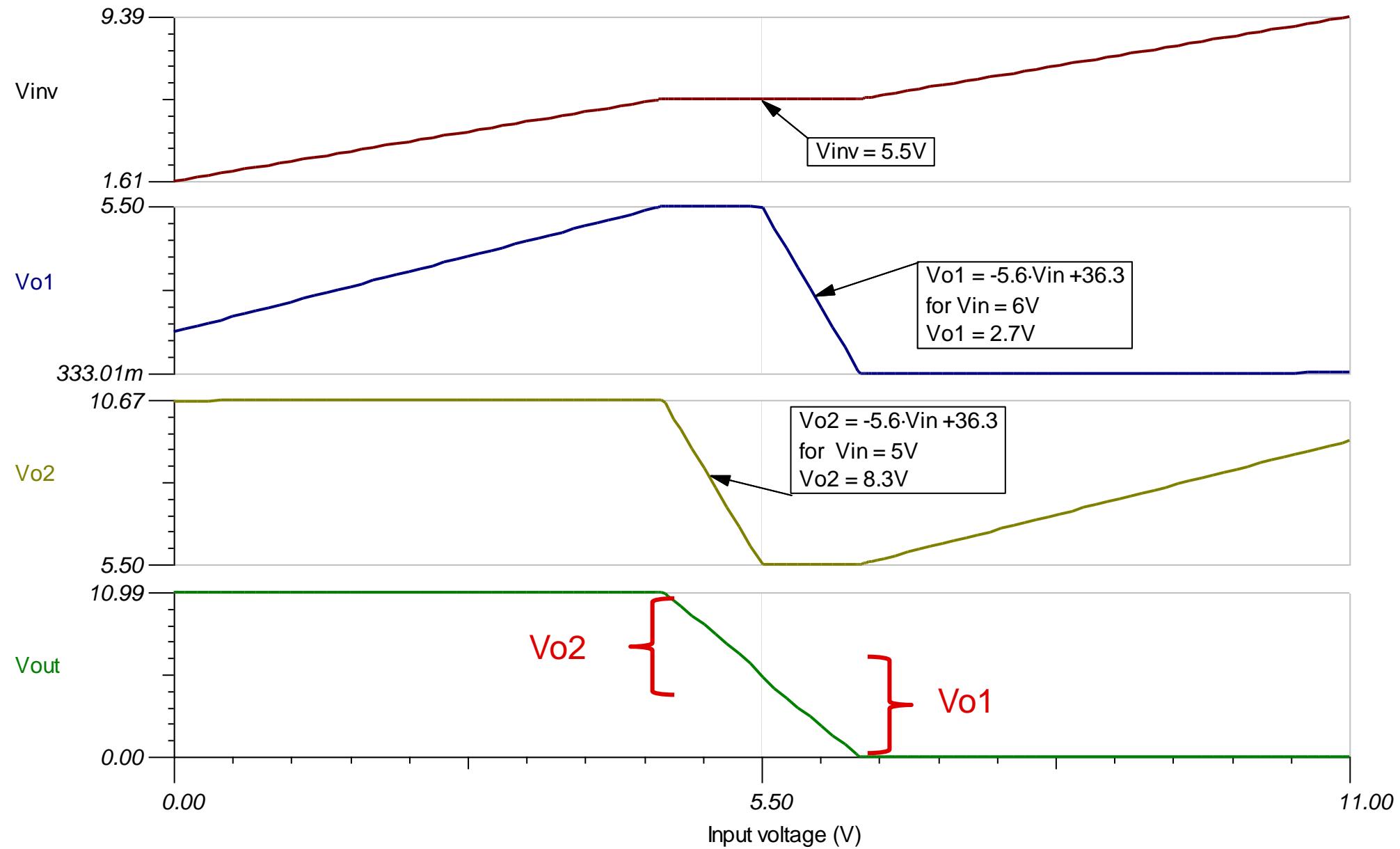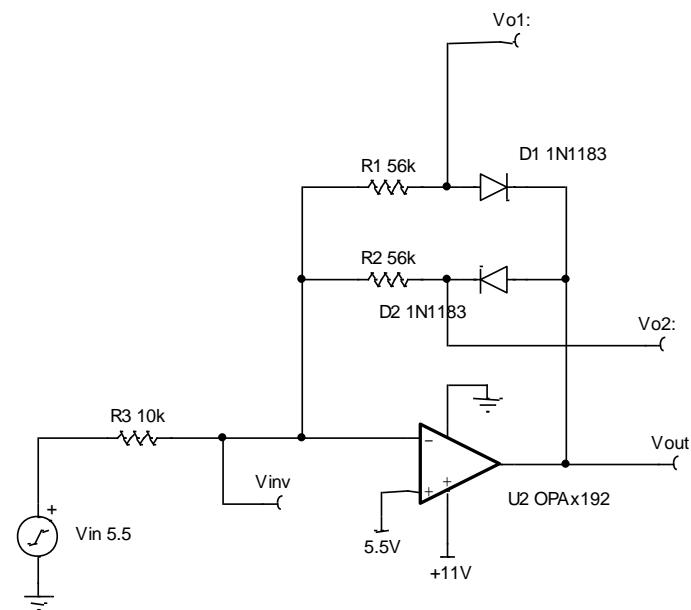



IC6A circuit

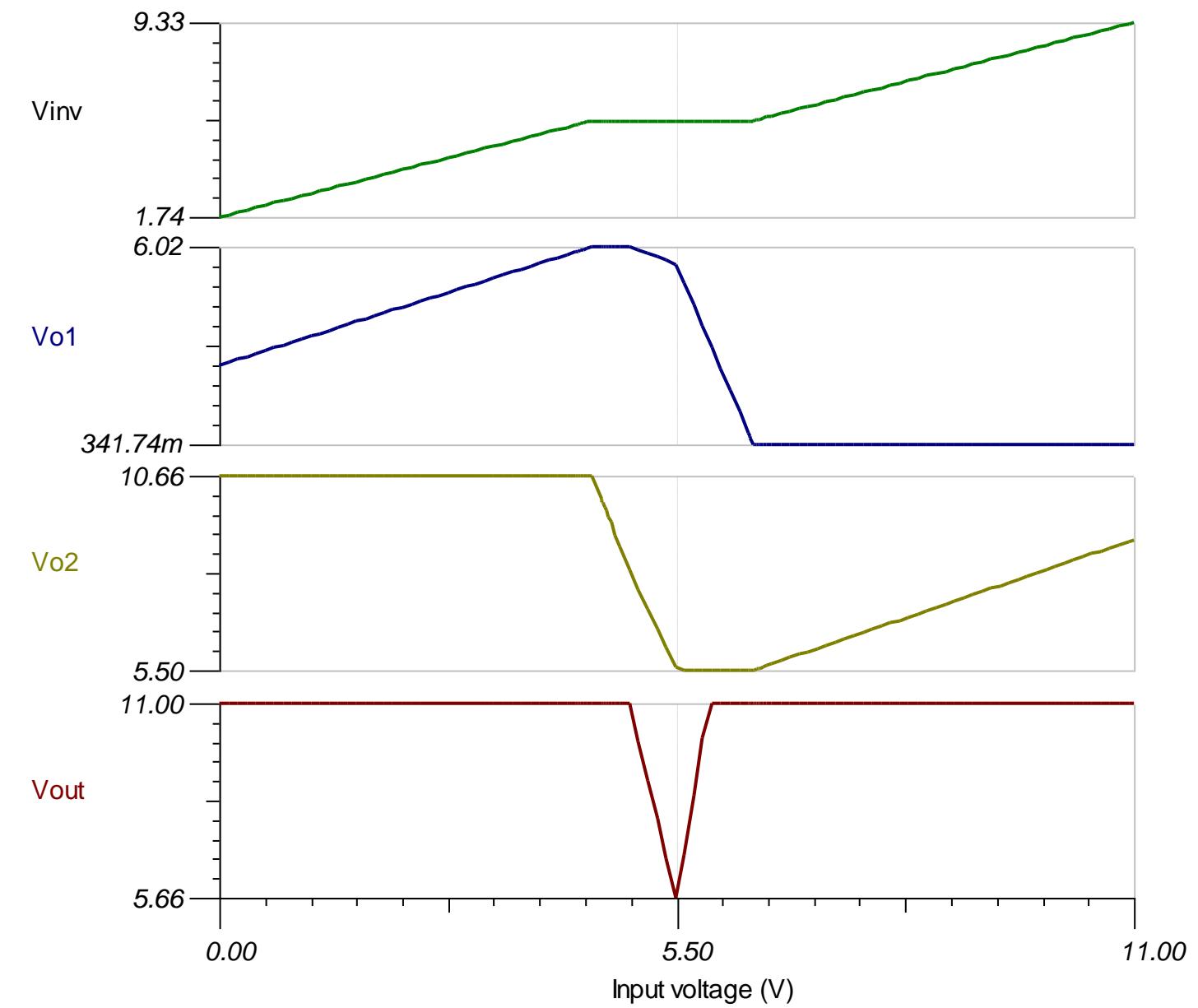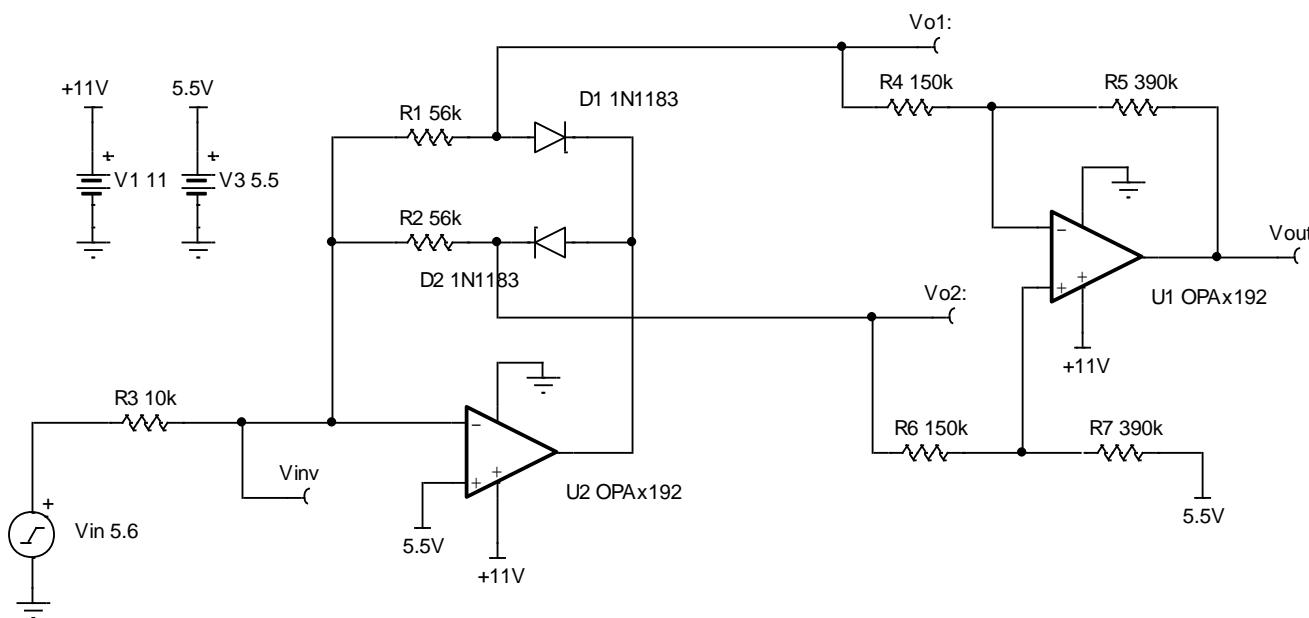


Add buffer

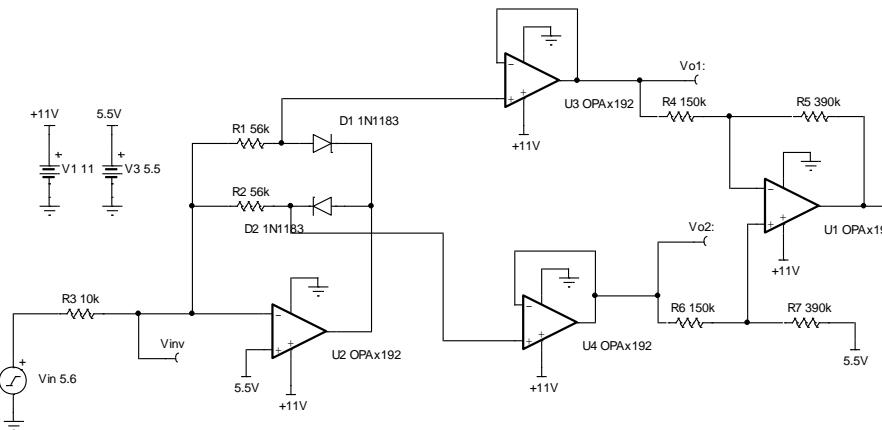


No buffer

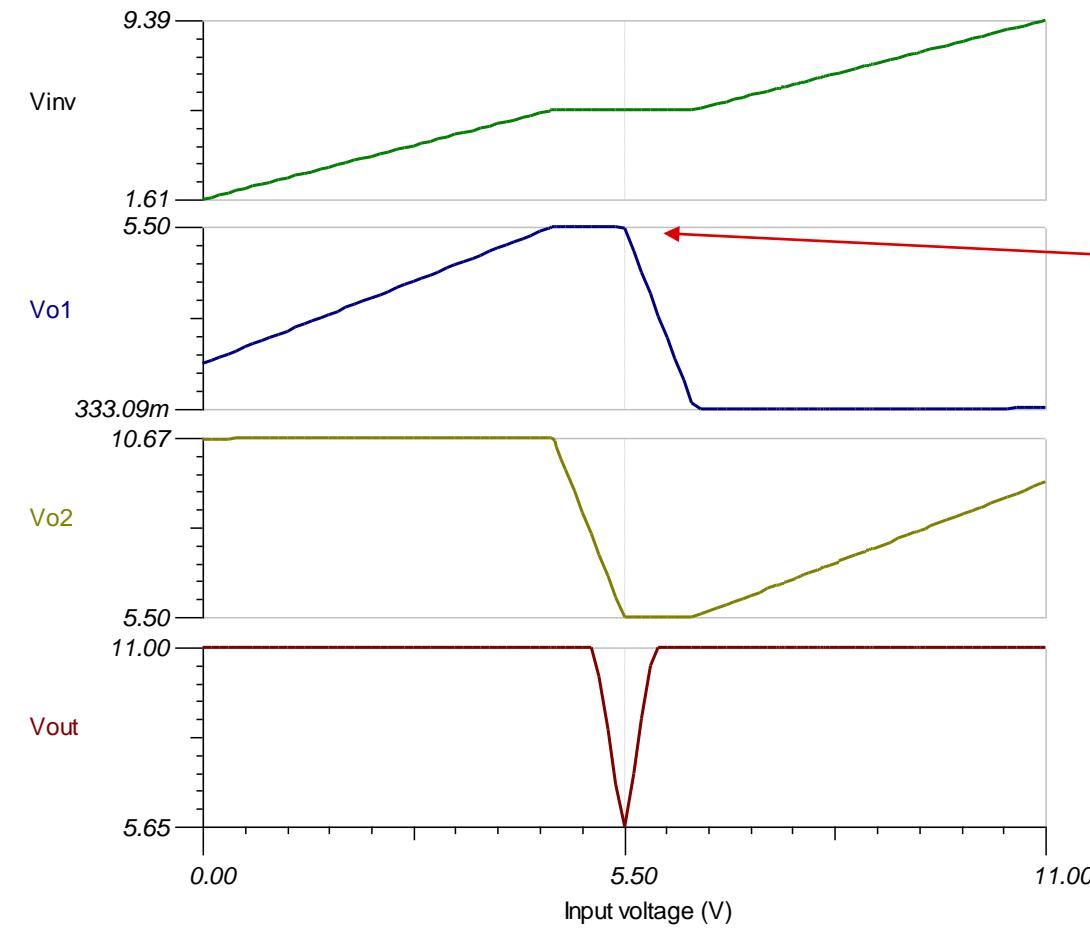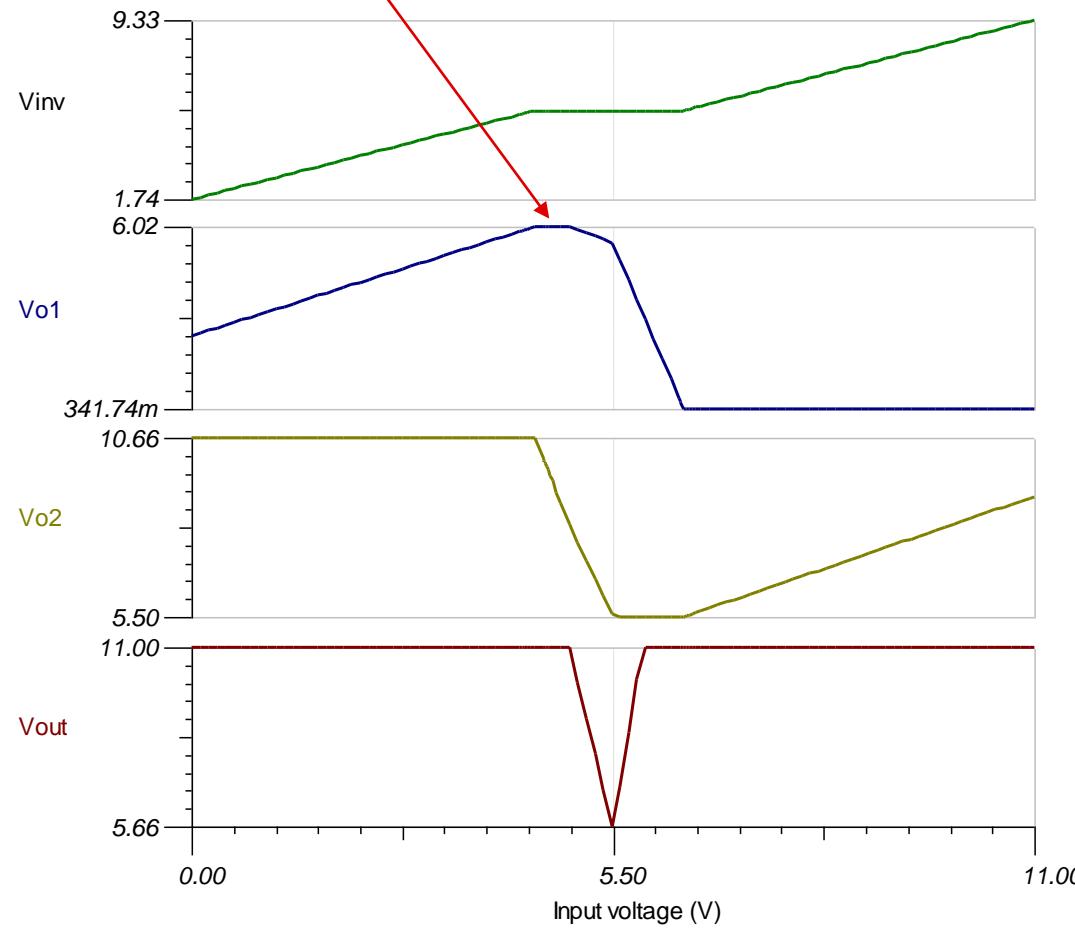

Zoom in on linear range

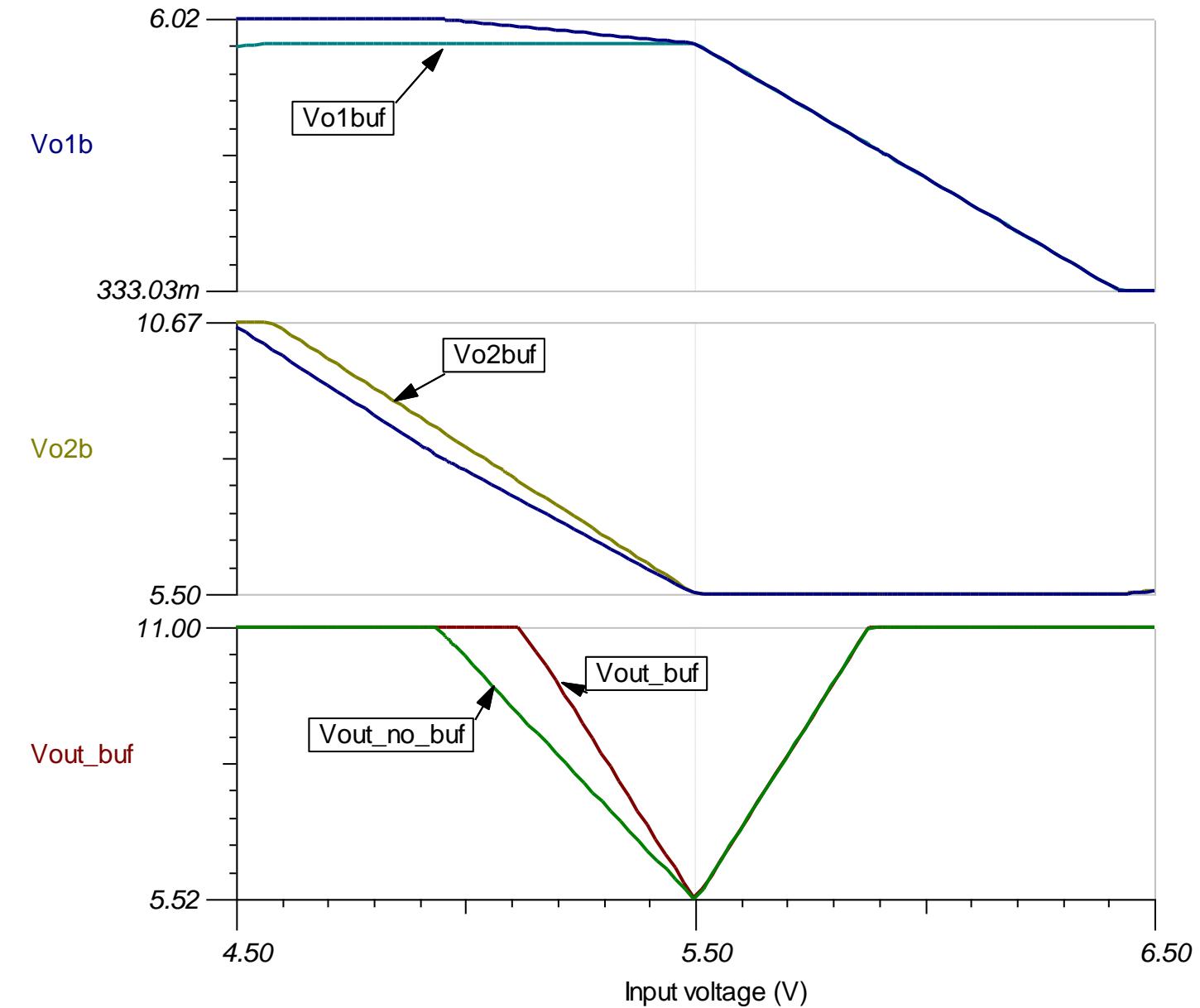

Slope when not loaded.

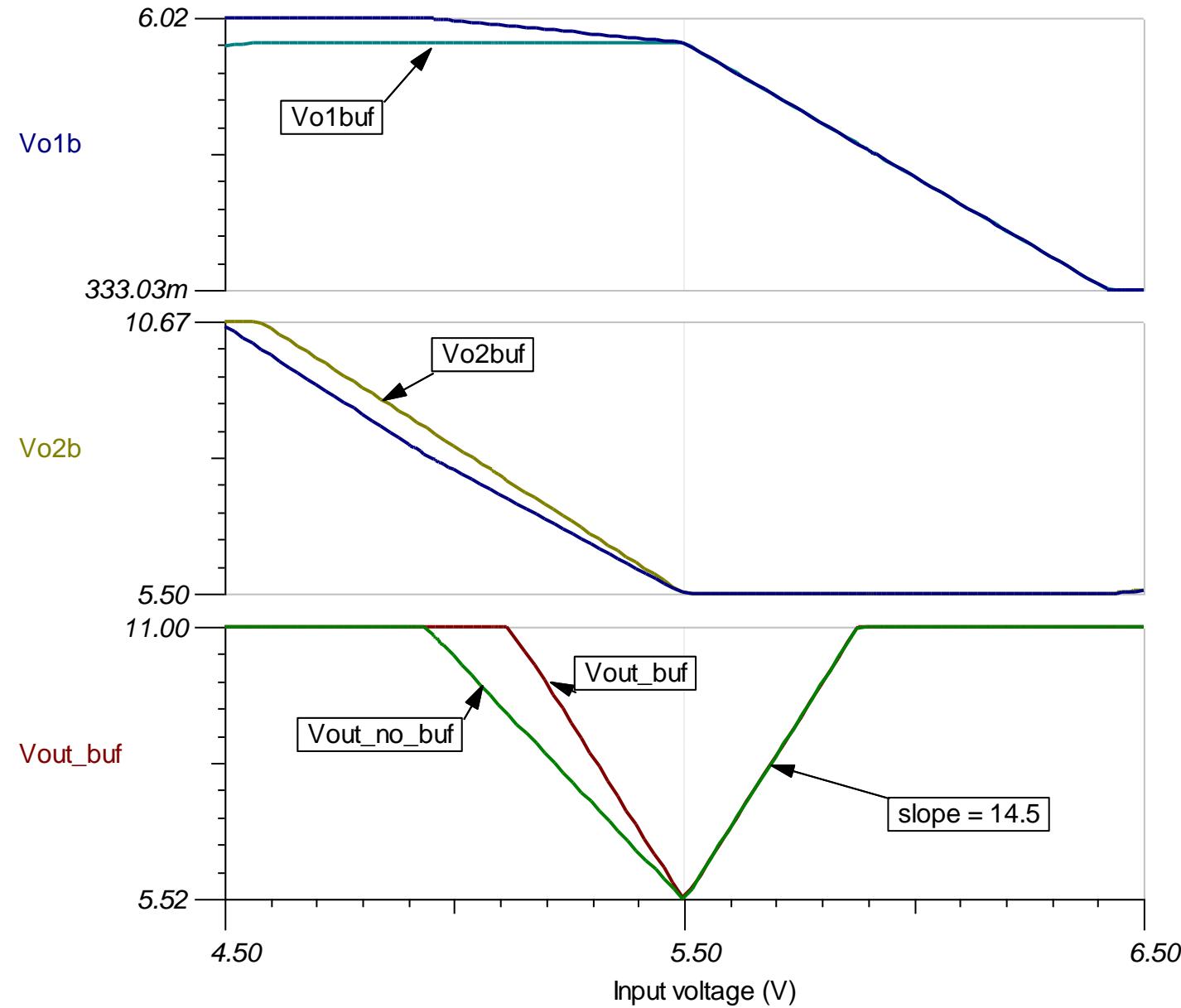

$$\frac{56}{10} \cdot \frac{389}{150} = 14.523$$