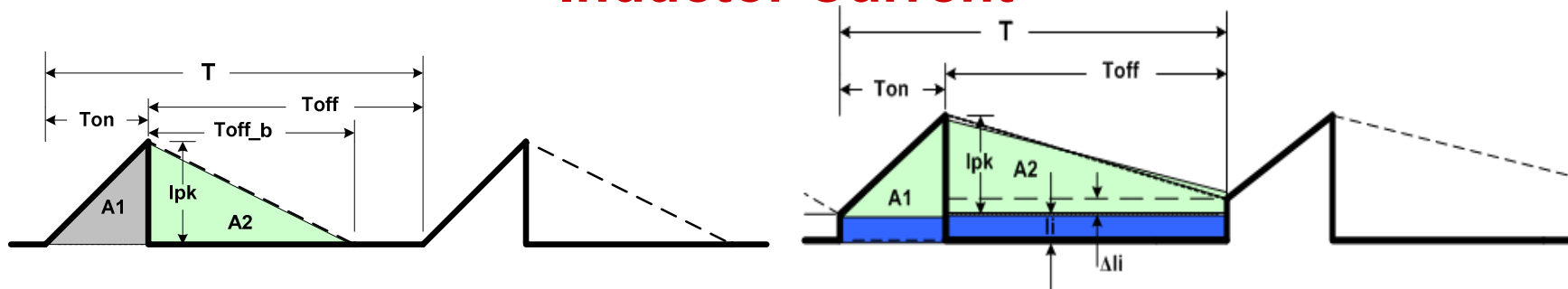


Conversion factor relating PFC Sampled Switch Current & Average Inductor Current

Shamim Choudhury
C2000 Systems & Applications
Texas Instruments Inc.

Bridgeless PFC Sampled Switch Current & Average Inductor Current



PFC Switch and Inductor Current under DCM

$$L \cdot \Delta I_{L_ON} \approx L \cdot \Delta I_{L_OFF}$$

$$\Rightarrow V_{in} T_{ON} = -(V_{in} - V_o) T_{off_b}$$

$$D_a \cdot V_{in} = D_b (V_o - V_{in}), \quad D_a = \frac{T_{ON}}{T}, \quad D_b = \frac{T_{off_b}}{T}$$

Average inductor current under DCM,

$$I_{L_dcm} = (T_{on} + T_{off_b}) \cdot \left(\frac{I_{pk}}{2}\right) \cdot \frac{1}{T} = (D_a + D_b) \frac{I_{pk}}{2}$$

For bridgeless PFC, switch current is always sensed at the center of the on-time T_{on} .

$$\text{So, } I_{sw} = \frac{I_{pk}}{2} + I_i \quad \text{under CCM, and } I_{sw} = \frac{I_{pk}}{2} \quad \text{under DCM } [I_i = 0]$$

Therefore, the switch current I_{sw} in terms of average inductor current I_L in both CCM and DCM modes

$$I_L = (D_a + D_b) I_{sw} \Rightarrow I_{sw} = \frac{I_L \cdot (V_o - V_{in})}{D_a \cdot V_o}$$

PFC Switch and Inductor Current under CCM

Average inductor current under CCM,

$$\begin{aligned} I_{L_ccm} &\approx (T_{on} + T_{off}) \cdot \left(\frac{I_{pk}}{2} + I_i\right) \cdot \frac{1}{T} \\ &= (D_a + D_b) \left(\frac{I_{pk}}{2} + I_i\right) \end{aligned}$$