

# **3 phase PFC and APF application with TI C2000 MCU**

**Igor AN**

**C2000 System Application Engineer**










# Content

- **Introduction**
- **PFC Application**
  - Software Design
  - Close-Loop Controller
- **APF Application**
  - Software Design
  - Close-Loop Controller
- **\*Unbalanced grid voltage treatment**
- **TI EVM Implementation**

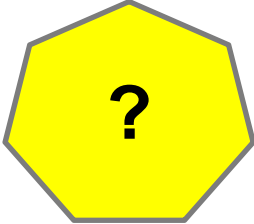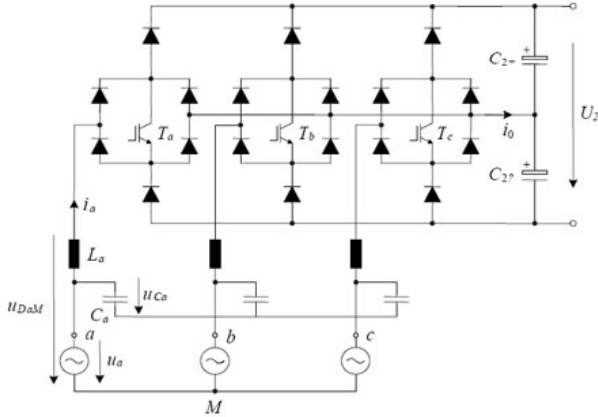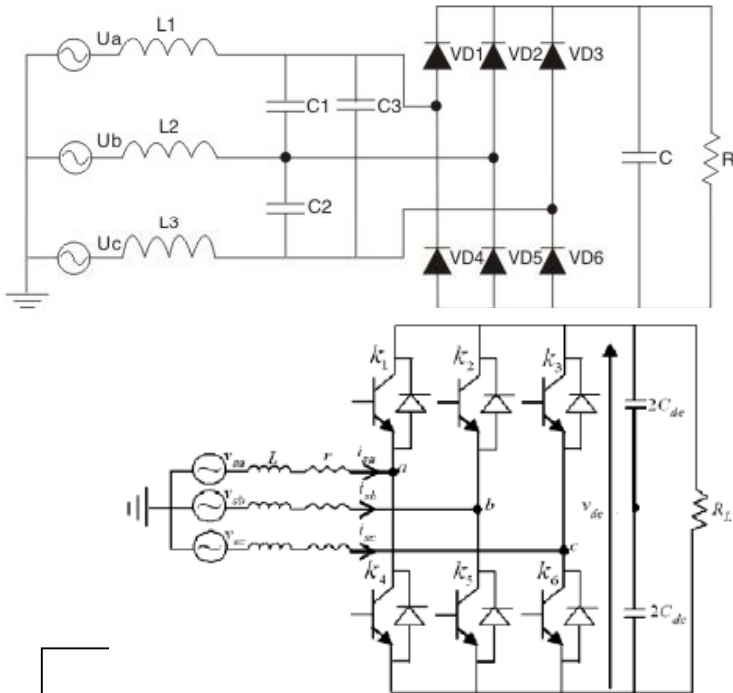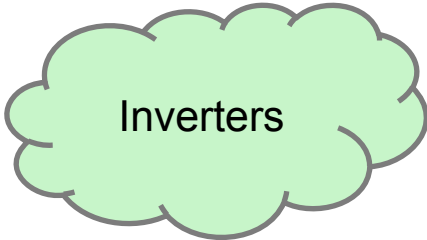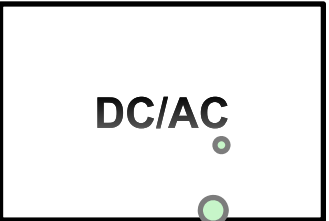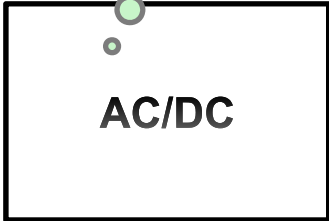
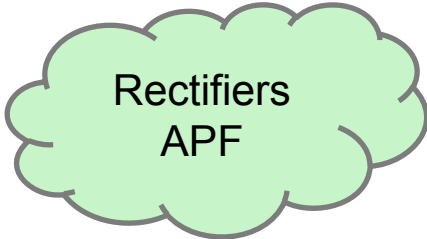
# Introduction

- 3 phase Power electronics rectifier device
  - Objectives
    - AC to Dc , get constant Dc Voltage
    - Harmonic regulation/compensation
    - Active power/reactive power regulation/compensation


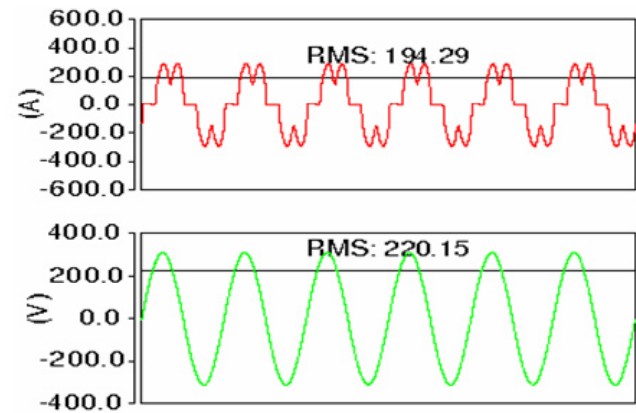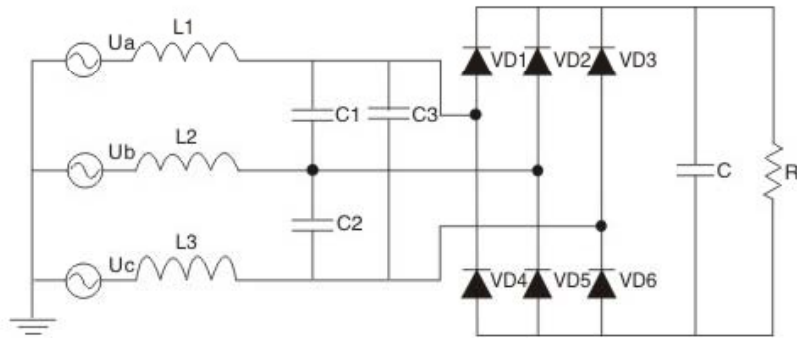
# Introduction

- Three Phase PFC Topology - 6 Pulse + SCR + LC





It is a non-controllable rectifier, the input current contains many harmonic waves. (ie, 5,7,11,13....)

So the PF and the THDi performance is bad.
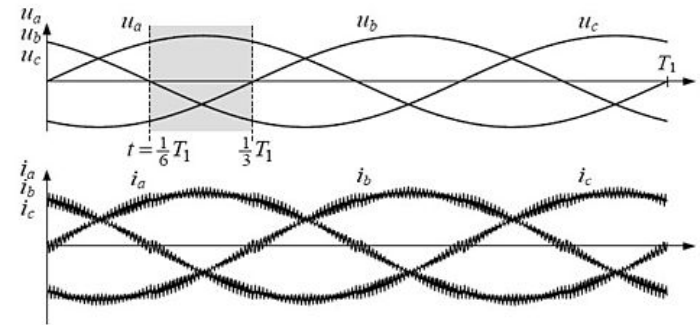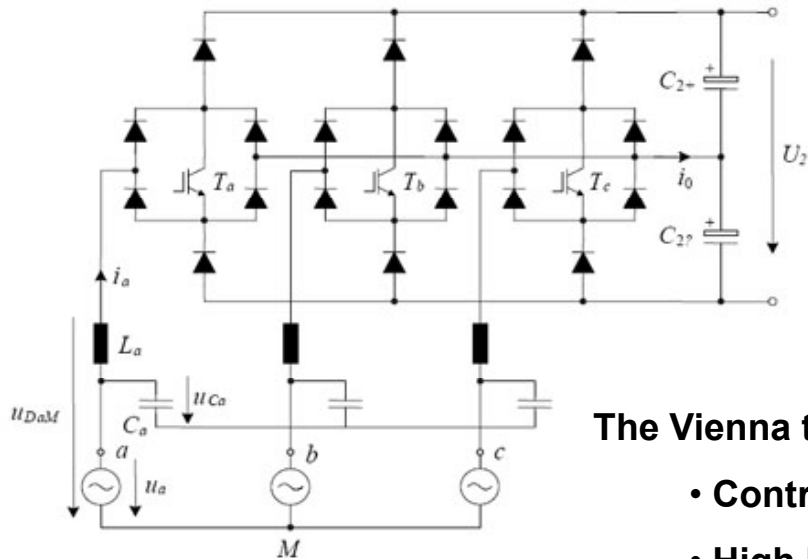
# Introduction

- **Three Phase PFC Topology - Vienna topology**





The Vienna topology is a controllable active power rectifier.

- Controllable output voltage and BUS balance
- High PF and low THDi
- High efficiency
- The controller is complicated
- Worse EMI than passive AC-DC
- irreversible current


# Introduction

- **Three Phase PFC Topology - 3 phase 2-level PWM rectifier**

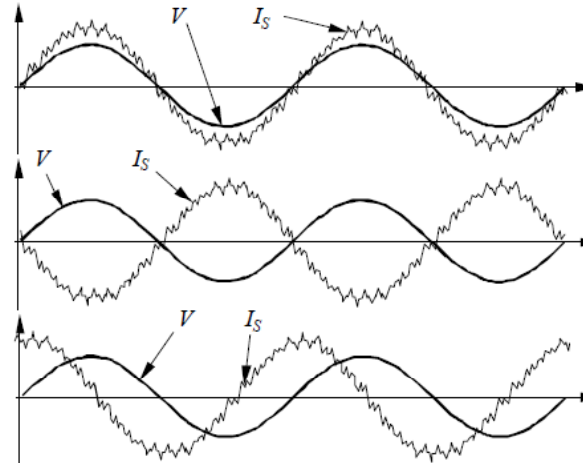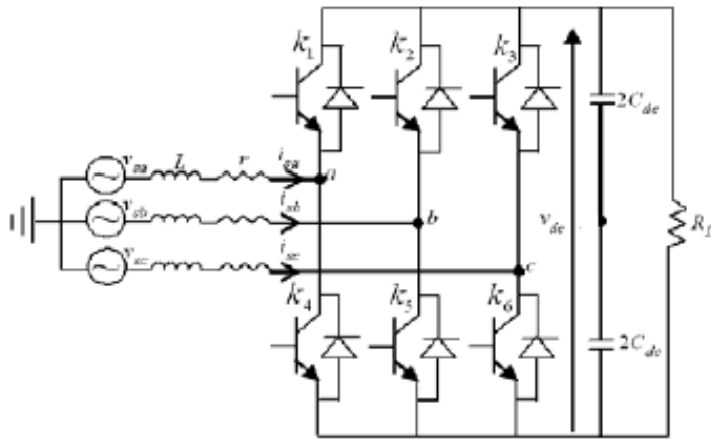

The 3-phase PWM rectifier topology is a controllable active power rectifier.

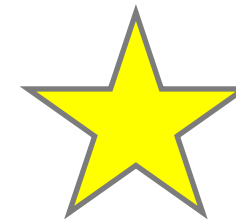- Controllable output voltage.
- High PF and low THDi, controllable PF
- Can share the same board with 3 phase inverter
- High efficiency
- The controller is complicated
- Worse EMI than passive AC-DC
- Reversible bi-direction current



# Harmonic related Standards

- IEEE-std-519-1992 Total THDI < 5%
- IEC\_61000-3-2-2009
- GB-T\_14549-1993


# Content

- Introduction
- **PFC Application**
  - Modeling
  - Control Loop Structure
- **APF Application**
  - Modeling
  - Control Loop Structure
- **\*Unbalanced grid voltage treatment**
- **TI EVM Implementation**


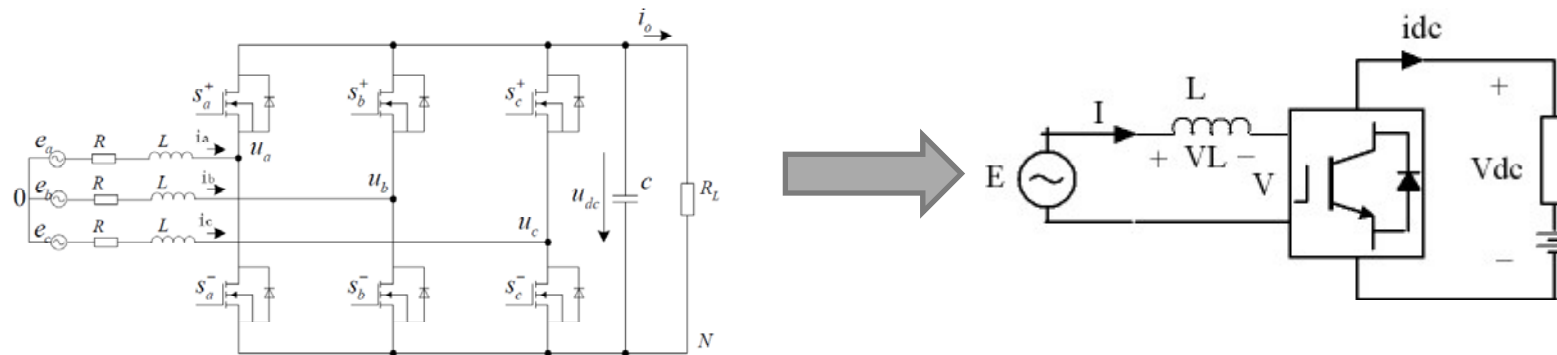
# PFC Application

- 3-Phase 2-level PWM Rectifier principle




The PWM Rectifier can be equivalent to the figure above, then we can get the the equation:

$$E = V_L + V$$

$$i_{ac} V_{ac} = i_{dc} V_{dc}$$
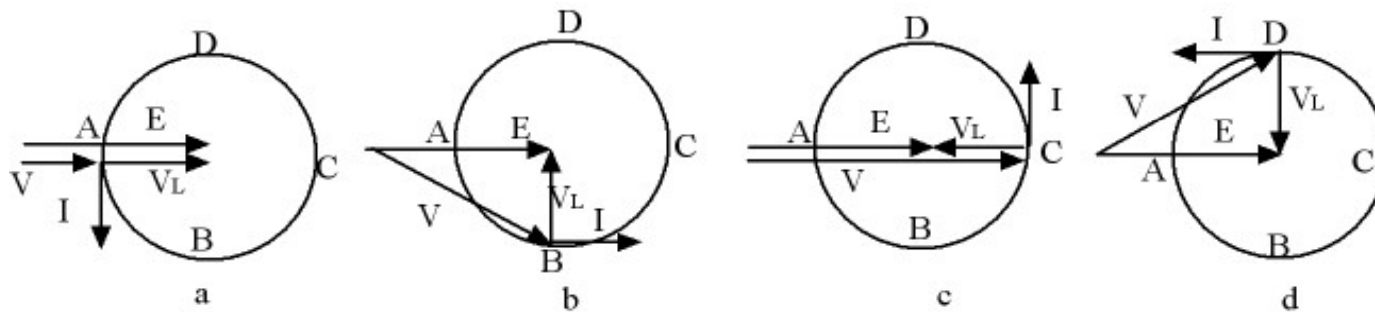
# PFC Application

- **Three Phase PWM Rectifier principle**




When the  $V$  trace from the A to B in the above figure, the converter can work in rectifier mode, when the  $V$  at the B, then the we can get the highest power factor.

**Control Objective:**

-Constant Bus Voltage

-Sinusoidal current wave, PF= 1


# Modeling

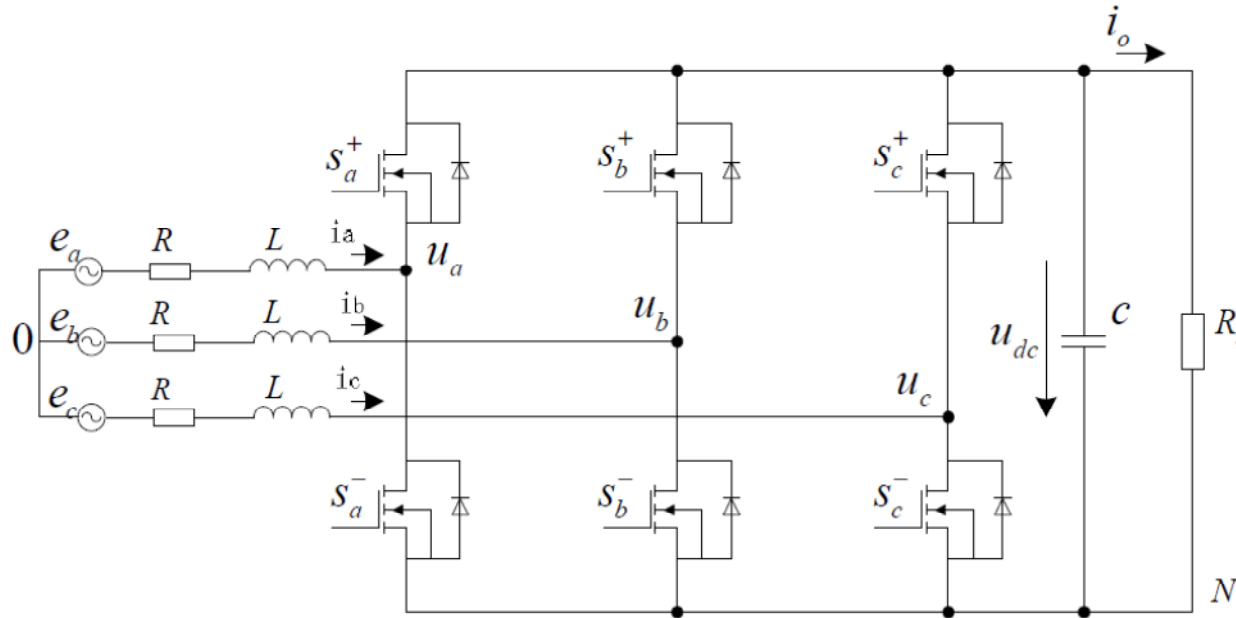

- $e_a, e_b, e_c$  → source voltages;
- $i_a, i_b, i_c$  → line currents;
- $u_a, u_b, u_c$  → rectifier input voltages;
- $u_{dc}$  → bus voltage;
- $R$  → resistance of the line reactor;
- $L$  → inductance of the line reactor;
- $C$  → smoothing capacitor;
- $i_o$  → load current;
- $R_L$  → resistance;
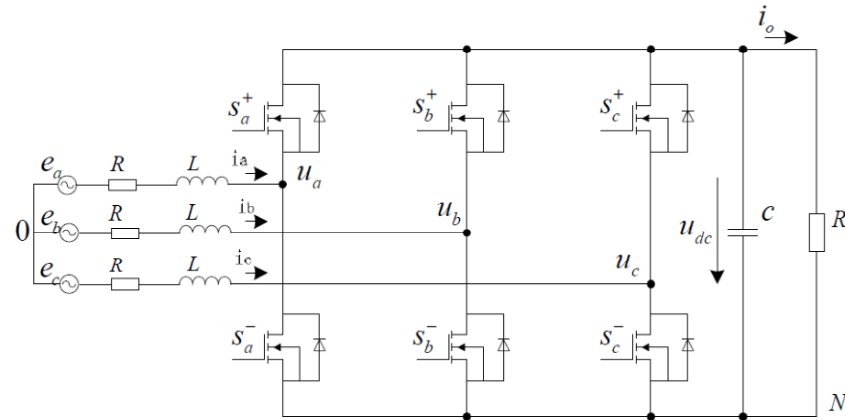
# Modeling

$$\left\{ \begin{array}{l} L \frac{di_a}{dt} + Ri_a = e_a - (u_a + u_{N0}) \\ L \frac{di_b}{dt} + Ri_b = e_b - (u_b + u_{N0}) \\ L \frac{di_c}{dt} + Ri_c = e_c - (u_c + u_{N0}) \\ C \frac{du_{dc}}{dt} = i_a * s_a + i_b * s_b + i_c * s_c - i_0 \end{array} \right.$$



$$s_k = \begin{cases} 1, & \text{up switch closed, down switch opened} \\ 0, & \text{up switch opened, down switch closed} \end{cases}$$

$$\begin{cases} u_k = u_{dc} * s_k, (k = a, b, c) \\ u_{N0} = -\frac{u_{dc}}{3} (s_a + s_b + s_c) \end{cases}$$

$$\left\{ \begin{array}{l} L \frac{di_a}{dt} = e_a - \frac{u_{dc}}{3} (2d_a - d_b - d_c) \\ L \frac{di_b}{dt} = e_b - \frac{u_{dc}}{3} (2d_b - d_a - d_c) \\ L \frac{di_c}{dt} = e_c - \frac{u_{dc}}{3} (2d_c - d_a - d_b) \\ C \frac{du_{dc}}{dt} = (i_a d_a + i_b d_b + i_c d_c) - \frac{u_{dc}}{R} \end{array} \right.$$



# Frequency domain model

$$\begin{cases} L \frac{di_a}{dt} = e_a - \frac{u_{dc}}{3} (2d_a - d_b - d_c) \\ L \frac{di_b}{dt} = e_b - \frac{u_{dc}}{3} (2d_b - d_a - d_c) \\ L \frac{di_c}{dt} = e_c - \frac{u_{dc}}{3} (2d_c - d_a - d_b) \\ C \frac{du_{dc}}{dt} = (i_a d_a + i_b d_b + i_c d_c) - \frac{u_{dc}}{R} \end{cases}$$







$$\begin{cases} LsI_a(s) = E_a(s) - \frac{u_{dc}}{3} (2d_a(s) - d_b(s) - d_c(s)) \\ LsI_b(s) = E_b(s) - \frac{u_{dc}}{3} (2d_b(s) - d_a(s) - d_c(s)) \\ LsI_c(s) = E_c(s) - \frac{u_{dc}}{3} (2d_c(s) - d_a(s) - d_b(s)) \\ CU_{dc}(s) = (I_a(s)d_a(s) + I_b(s)d_b(s) + I_c(s)d_c(s)) - \frac{U_{dc}(s)}{R} \end{cases}$$
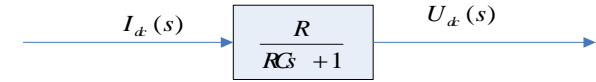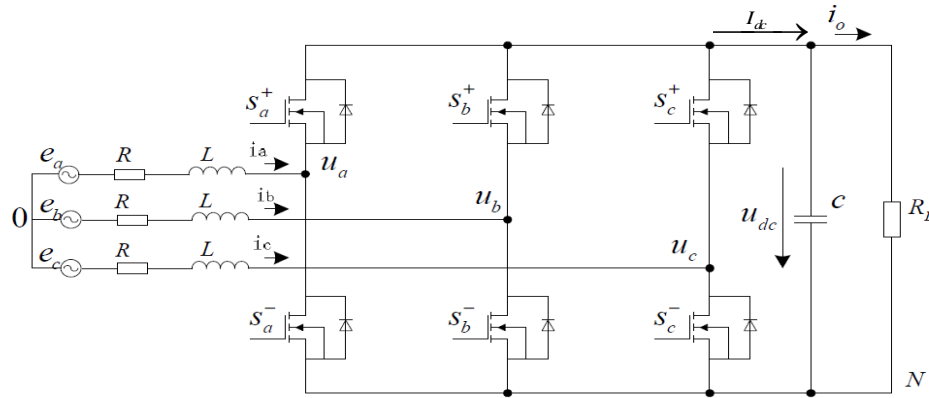
# abc ordinate model & Direct Current Control



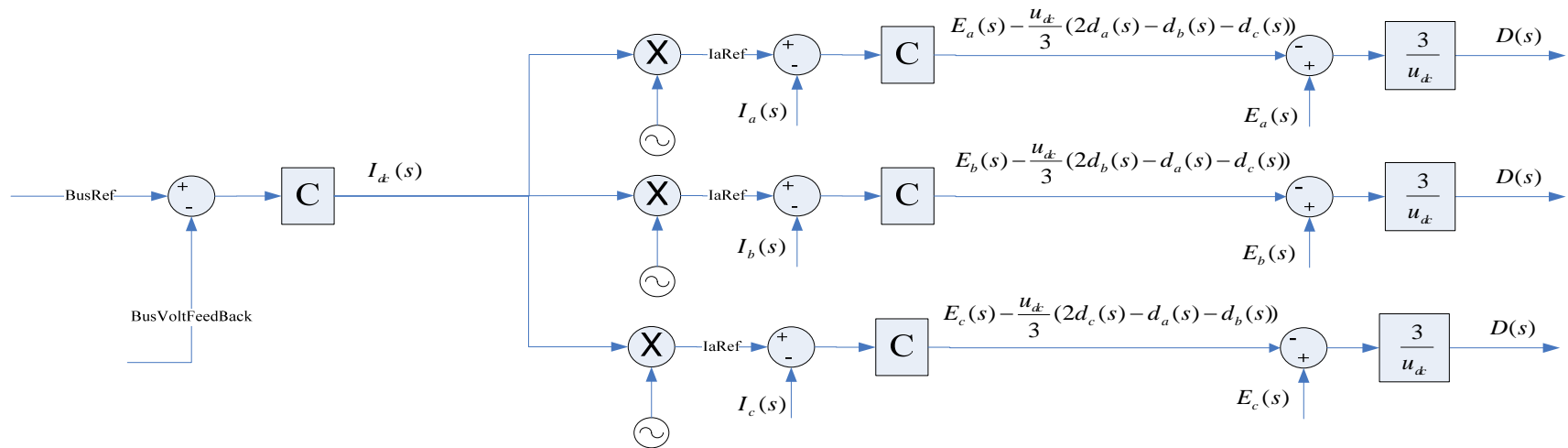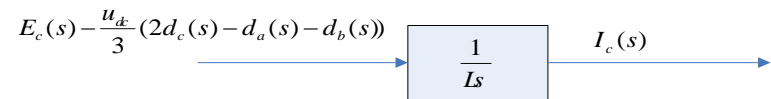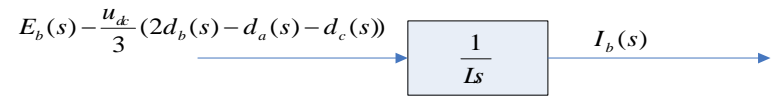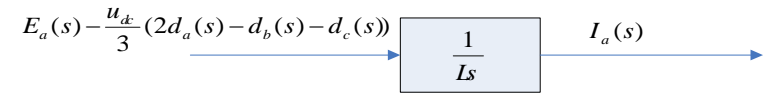
$$I_{\hat{x}}(s) = (I_a(s)d_a(s) + I_b(s)d_b(s) + I_c(s)d_c(s))$$



# abc ordinate model & Direct Current Control


- In steady state, and with the balanced input voltage  $U_a + U_b + U_c = 0$ ,  $I_a + I_b + I_c = 0$ ,
- so the hypotheses could be made:

$$d_a(s) + d_b(s) + d_c(s) = 0$$

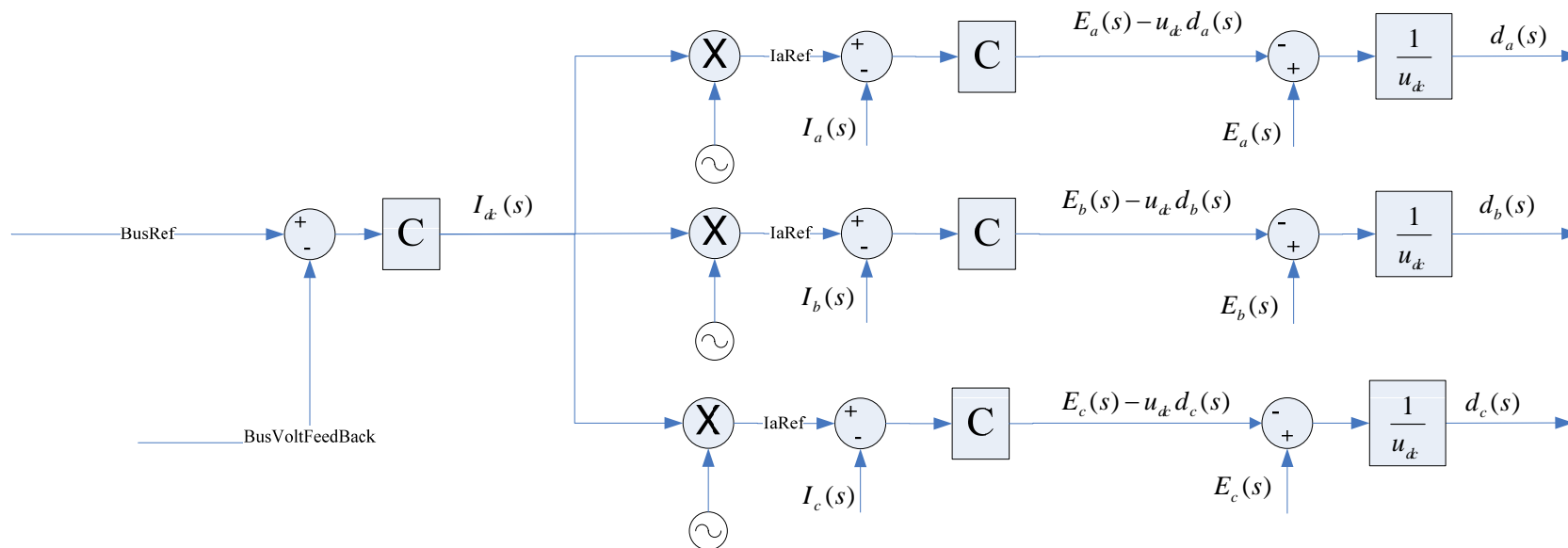
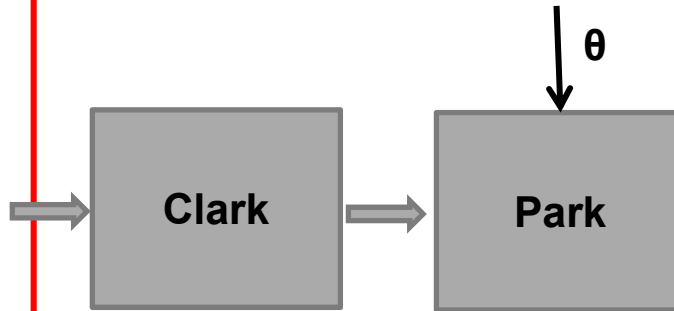
# dq ordinate modeling

$$\left\{ \begin{aligned} L \frac{di_a}{dt} &= e_a - \frac{u_{dc}}{3} (2d_a - d_b - d_c) \\ L \frac{di_b}{dt} &= e_b - \frac{u_{dc}}{3} (2d_b - d_a - d_c) \\ L \frac{di_c}{dt} &= e_c - \frac{u_{dc}}{3} (2d_c - d_a - d_b) \\ C \frac{du_{dc}}{dt} &= (i_a d_a + i_b d_b + i_c d_c) - \frac{u_{dc}}{R} \end{aligned} \right.$$



$$V_a(t) + V_b(t) + V_c(t) = 0$$

$$I_a(t) + I_b(t) + I_c(t) = 0$$


$$\left\{ \begin{aligned} L \frac{di_d}{dt} &= e_d - u_{dc} d_d + L \omega i_q \\ L \frac{di_q}{dt} &= e_q - u_{dc} d_q - L \omega i_d \\ C \frac{du_{dc}}{dt} &= \frac{3}{2} (i_d d_d + i_q d_q) - \frac{u_{dc}}{R} \end{aligned} \right.$$



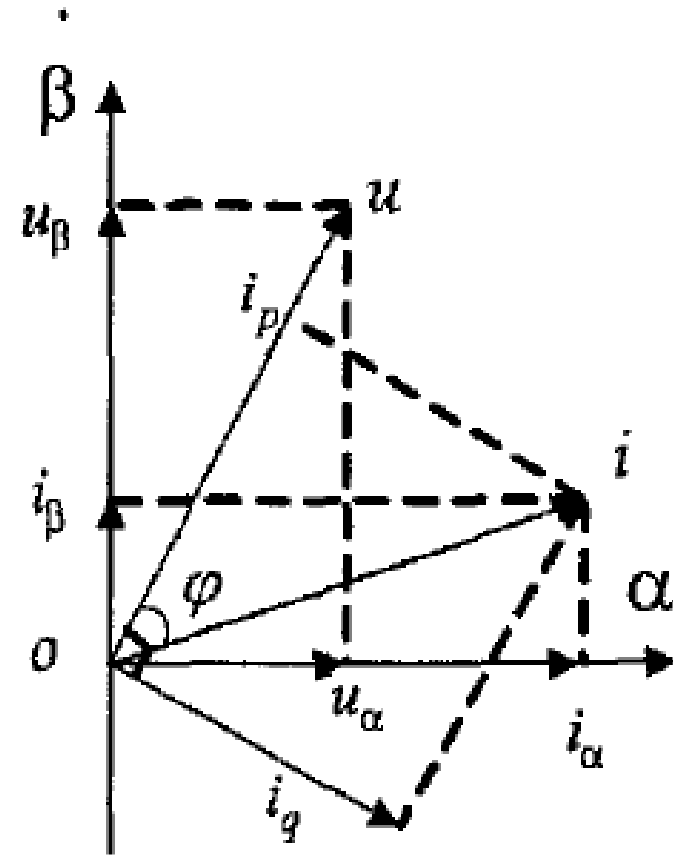
# Clark and Park Transfer

$$\begin{cases} V_a(t) = V_m \cos(\omega t + \alpha) \\ V_b(t) = V_m \cos(\omega t - 120^\circ + \alpha) \\ V_c(t) = V_m \cos(\omega t + 120^\circ + \alpha) \end{cases}$$

$$\begin{cases} I_a(t) = I_m \cos(\omega t + \alpha) \\ I_b(t) = I_m \cos(\omega t - 120^\circ + \alpha) \\ I_c(t) = I_m \cos(\omega t + 120^\circ + \alpha) \end{cases}$$




# dq ordinate modeling

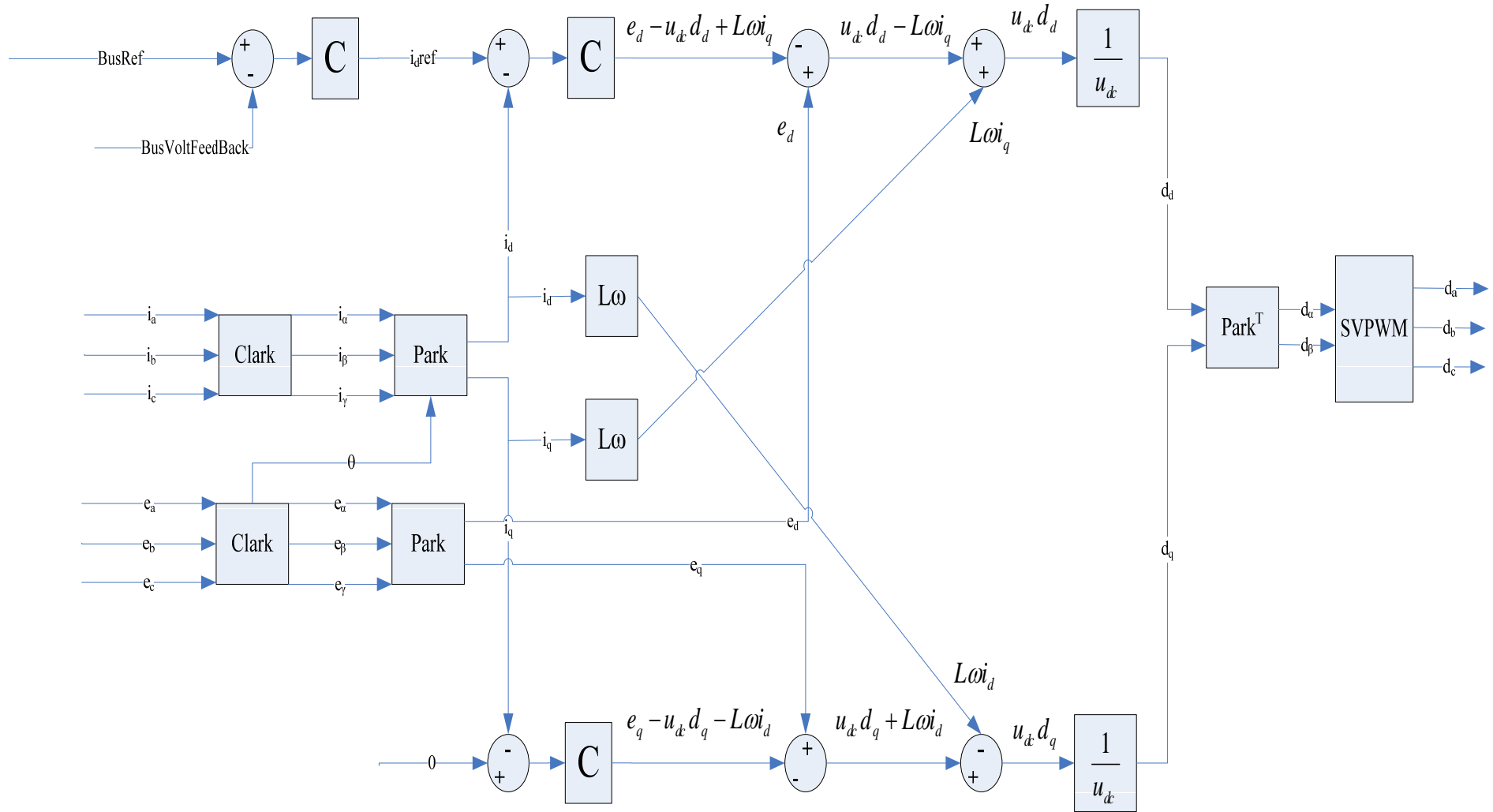


# Content

- Introduction
- PFC Application
  - Modeling
  - Control Loop Structure
- APF Application
  - Modeling
  - Control Loop Structure
- \*Unbalanced grid voltage treatment
- TI EVM Implementation

# What's APF

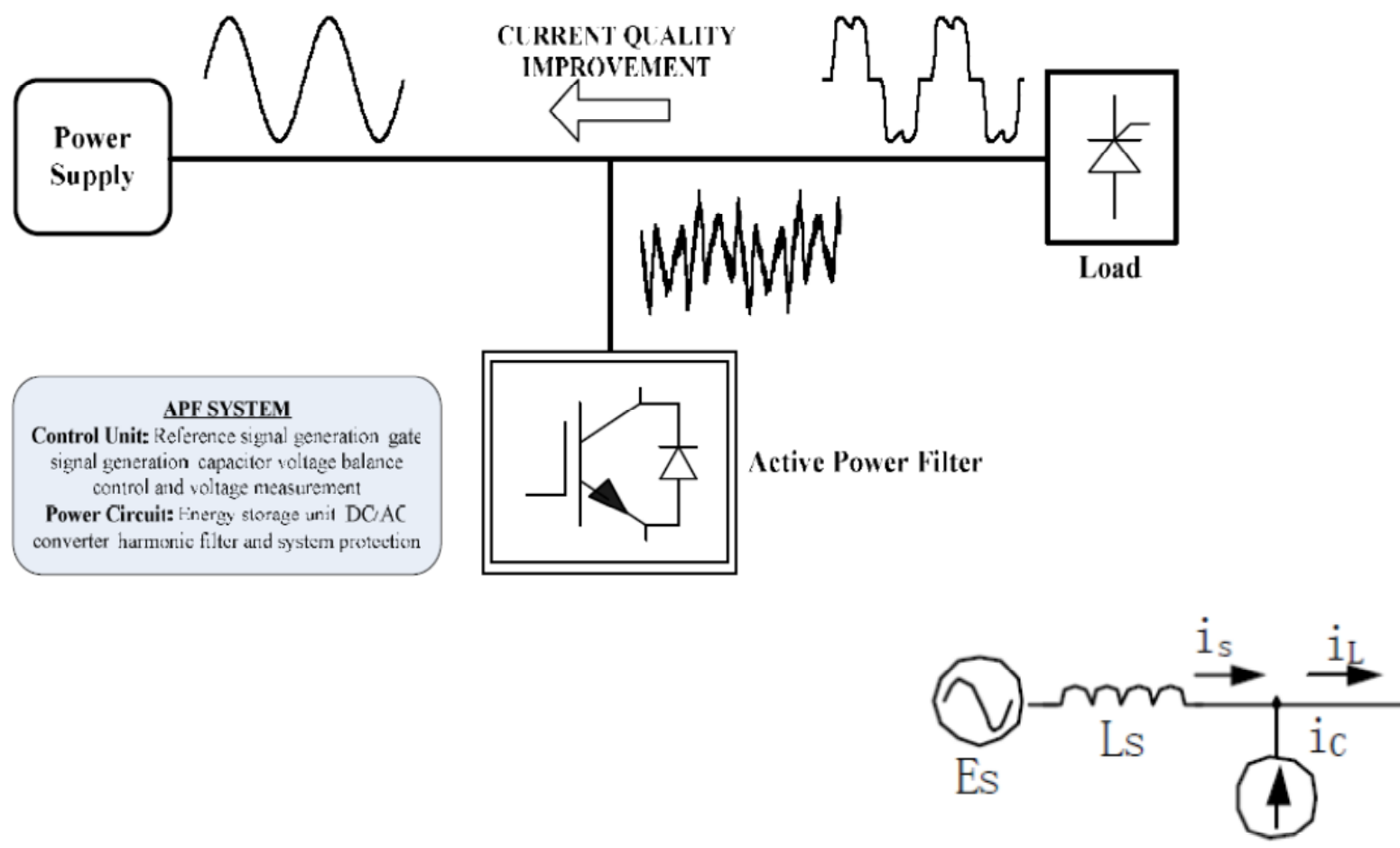

# APF


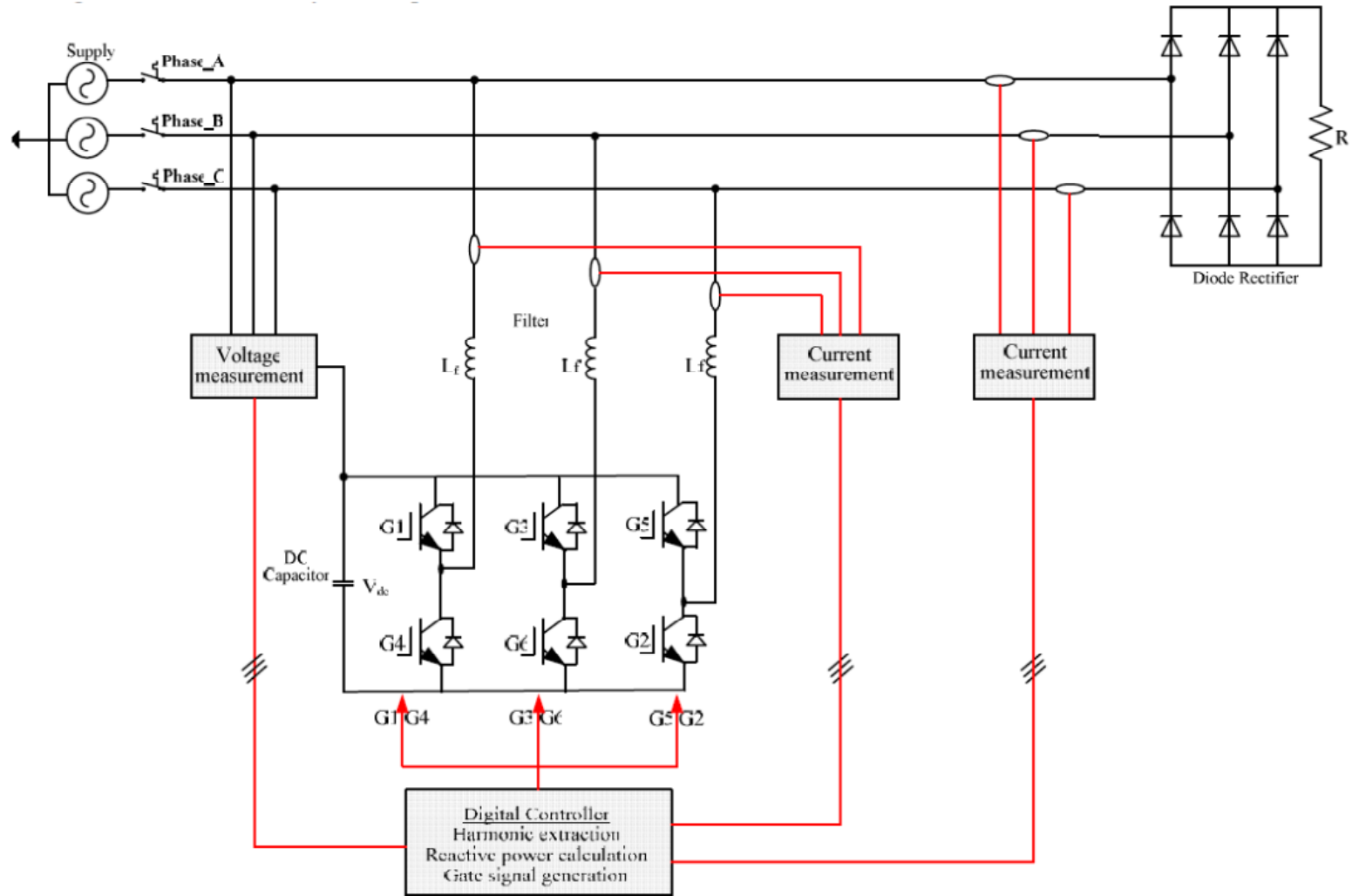


# Key Techniques

- Harmonic detection technique
  - Detection algorithm
  - Response time (The best product 10ms response time)
- Decrease the volume of APF
  - Only consider harmonic compensation  
Volume  $\approx$  25% of load power
  - Reactive power considered  
Volume  $\approx$  100% of load power
- Duplicated functionality of APF
  - Solar inverter + APF
- Paralleled APF
  - Different APF in charge of different range of Harmonic compensation

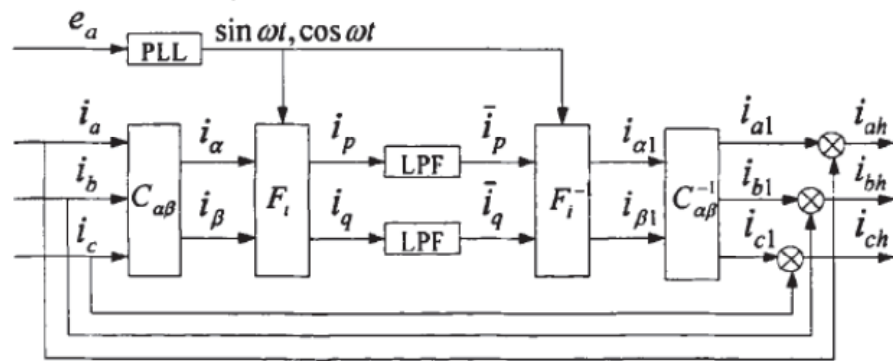
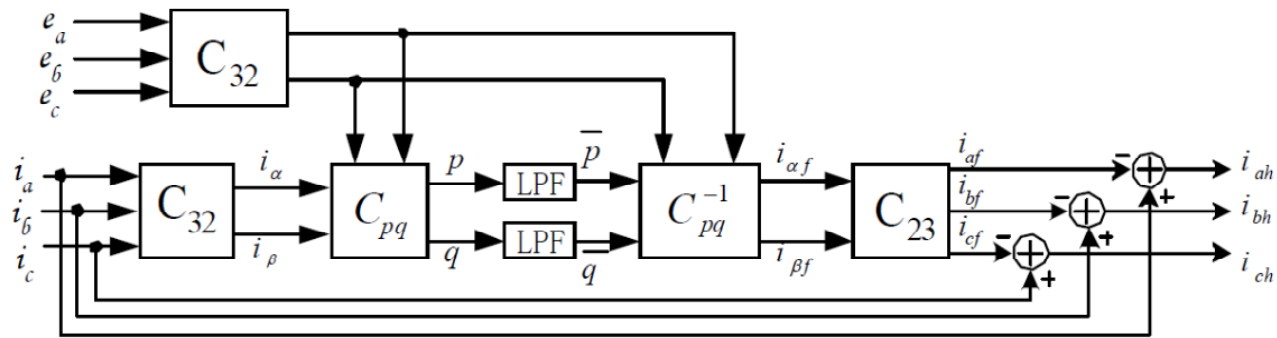
# Harmonic detection

- Instantaneous reactive power theory\*
- FFT





# Control loop Schema

- Control Loop of APF

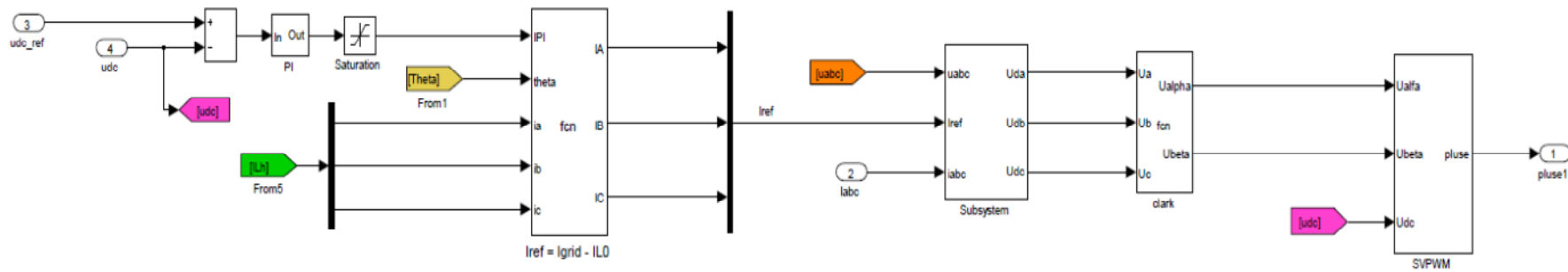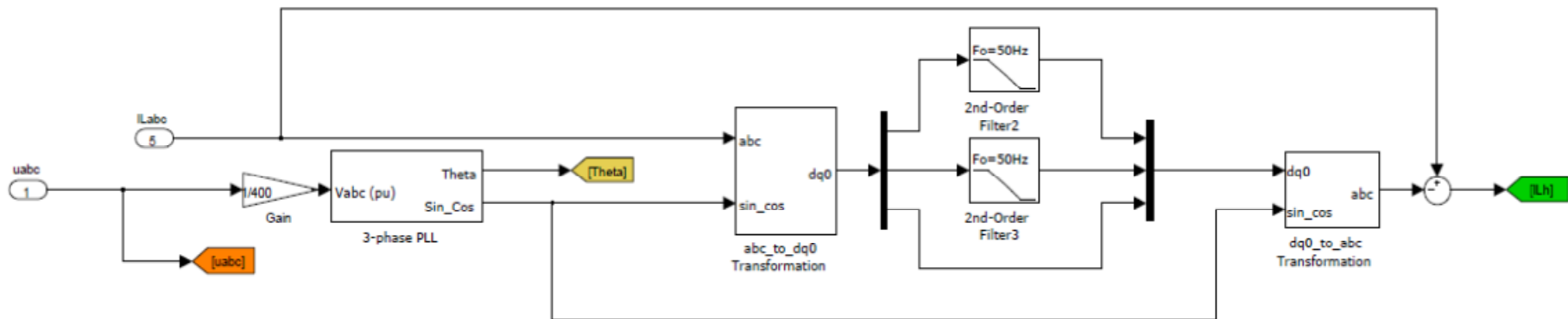



# Simulation Result

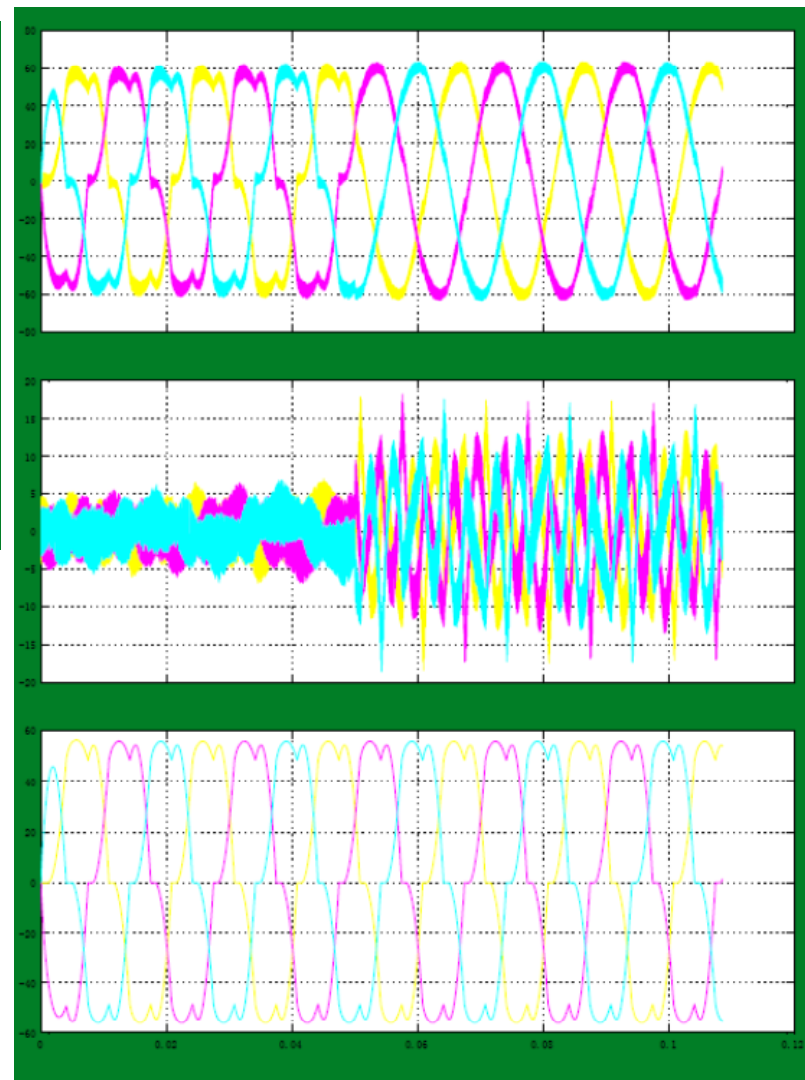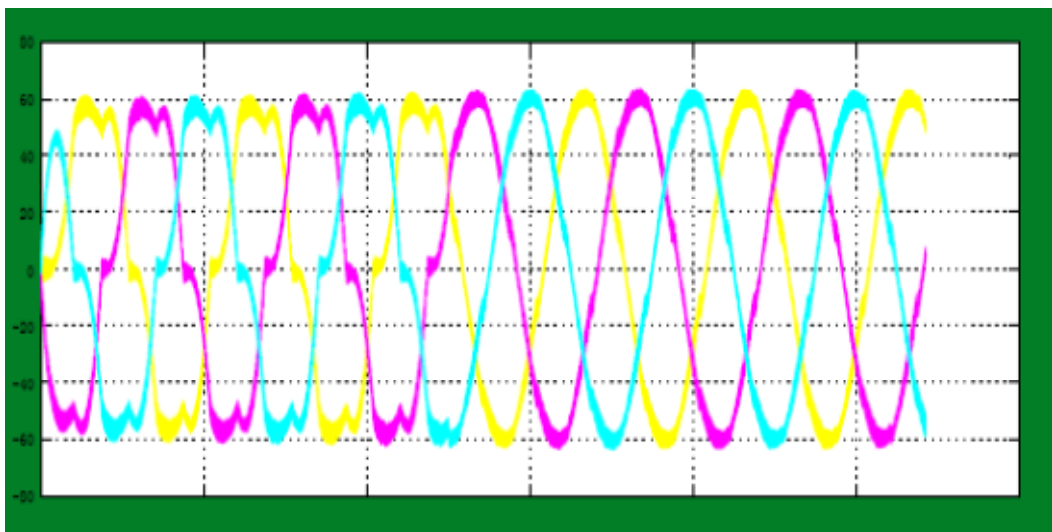

# Content

- Introduction
- PFC Application
  - Modeling
  - Control Loop Structure
- APF Application
  - Modeling
  - Control Loop Structure
- **\*Unbalanced grid voltage treatment**
- TI EVM Implementation

# Unbalanced grid voltage

All the above control loop are build based on hypotheses : balanced three voltage!

But the reality is not so accurate.

**\* Positive and Negative sequence decomposition and control**

# Respect to Dr C.L.FORTESCUE


- Dr C.L.FORTESCUE's research in 1918, any unbalanced three vectors could be decomposed into a balanced positive sequence, a balanced negative sequence and a zero sequence.

- Positive Sequence PARK:

$$Park^p = \begin{bmatrix} \cos \omega t & \sin \omega t \\ -\sin \omega t & \cos \omega t \end{bmatrix}$$

- Negative Sequence PARK:
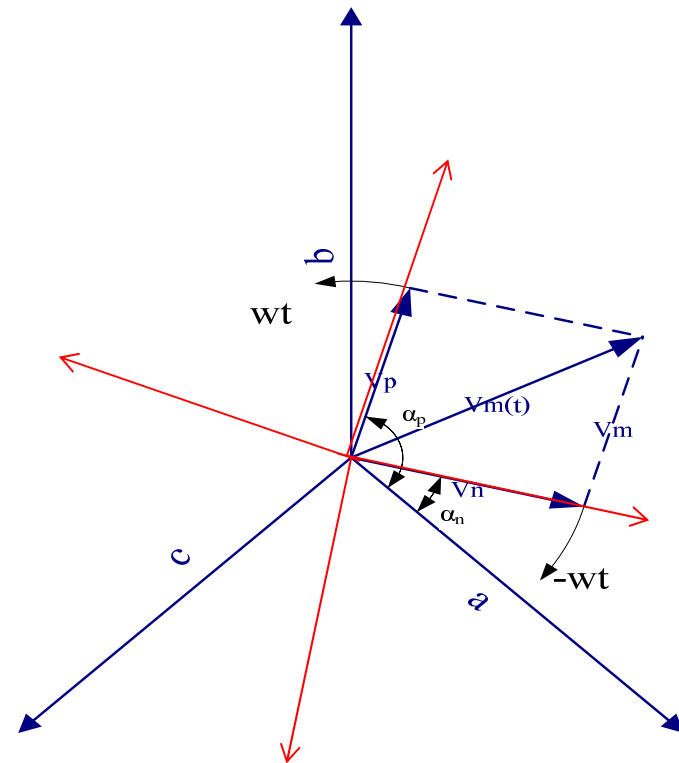
$$Park^n = \begin{bmatrix} \cos \omega t & -\sin \omega t \\ \sin \omega t & \cos \omega t \end{bmatrix}$$



# Positive & Negative sequence decomposition

$$\left\{ \begin{array}{l} V_{di}^p(t) = V_p \cos(\alpha_p) + V_n \cos(2\omega t + \alpha_n) \\ V_{qi}^p(t) = V_p \sin(\alpha_p) - V_n \sin(2\omega t + \alpha_n) \\ V_{di}^n(t) = V_p \cos(2\omega t + \alpha_p) + V_n \cos(\alpha_n) \\ V_{qi}^n(t) = V_p \sin(2\omega t + \alpha_p) - V_n \sin(\alpha_n) \end{array} \right. \begin{bmatrix} V_{di}^p(t) \\ V_{qi}^p(t) \\ V_{di}^n(t) \\ V_{qi}^n(t) \end{bmatrix} * [NotchFilter] = \left\{ \begin{array}{l} V_d^p(t) = V_p \cos(\alpha_p) \\ V_q^p(t) = V_p \sin(\alpha_p) \\ V_d^n(t) = V_n \cos(\alpha_n) \\ V_q^n(t) = -V_n \sin(\alpha_n) \end{array} \right.$$

$$\left\{ \begin{array}{l} I_{di}^p(t) = I_p \cos(\alpha'_p) + I_n \cos(2\omega t + \alpha'_n) \\ I_{qi}^p(t) = I_p \sin(\alpha'_p) - I_n \sin(2\omega t + \alpha'_n) \\ I_{di}^n(t) = I_p \cos(2\omega t + \alpha'_p) + I_n \cos(\alpha'_n) \\ I_{qi}^n(t) = I_p \sin(2\omega t + \alpha'_p) - I_n \sin(\alpha'_n) \end{array} \right. \begin{bmatrix} I_{di}^p(t) \\ I_{qi}^p(t) \\ I_{di}^n(t) \\ I_{qi}^n(t) \end{bmatrix} * [NotchFilter] = \left\{ \begin{array}{l} I_d^p(t) = I_p \cos(\alpha'_p) \\ I_q^p(t) = I_p \sin(\alpha'_p) \\ I_d^n(t) = I_n \cos(\alpha'_n) \\ I_q^n(t) = -I_n \sin(\alpha'_n) \end{array} \right.$$

# Content


- **Introduction**
- **PFC Application**
  - Modeling
  - Control Loop Structure
- **APF Application**
  - Modeling
  - Control Loop Structure
- **\*Unbalanced grid voltage treatment**
- **TI EVM Implementation**

# Specifications

- **3-phase PFC EVM basic specification**
  - **3 phase 4 wire(or 3wire) input**
  - **1200W @ 380VAC/50Hz**
  - **Output Voltage: 700VDC**
  - **Efficiency: >95%**
  - **THDi<5% @ Full load**
  - **Current unbalance ratio: <3%**
  - **Power Factor > 0.99 @ >50% Load**
  - **Piccolo B**
  - **GUI support**

# 3-phase PFC EVM


- 3-phase PFC EVM Picture

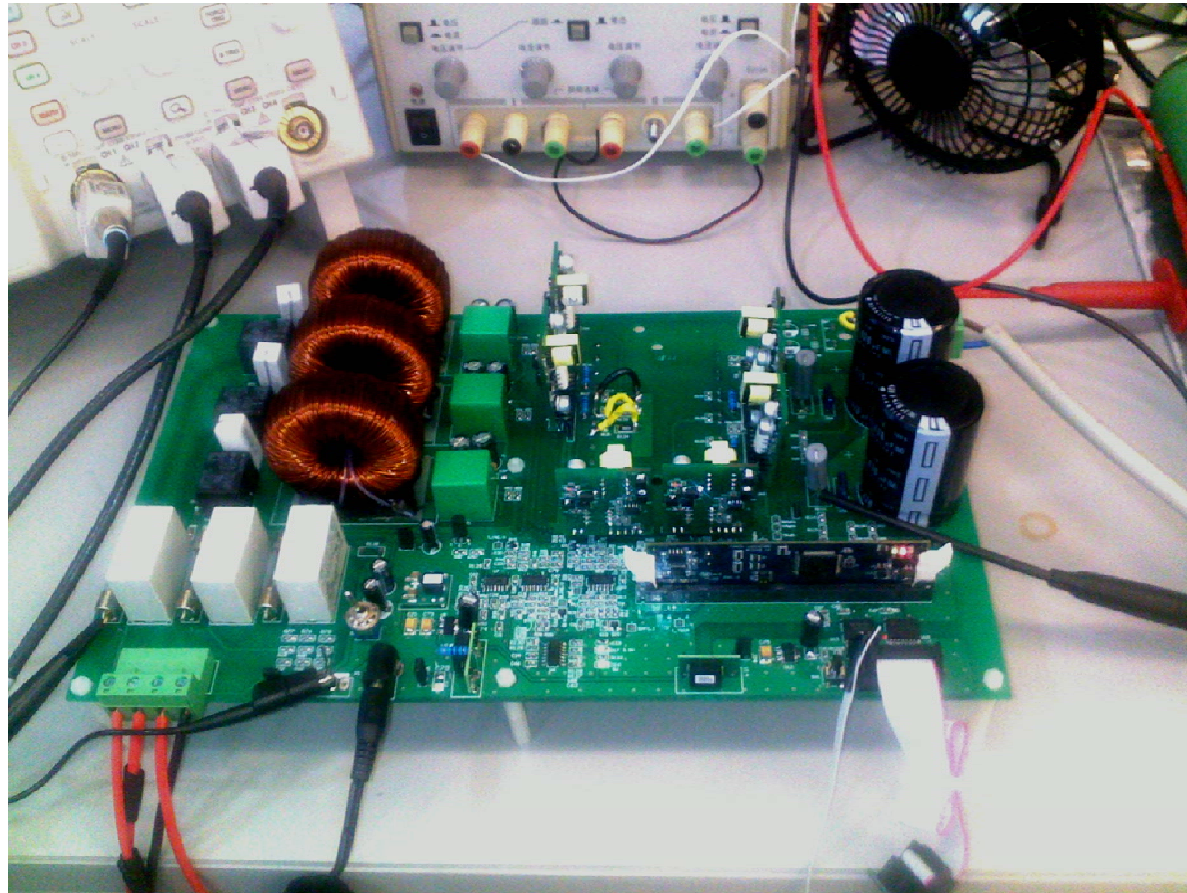



# Hardware Description

- **Main circuit topology**

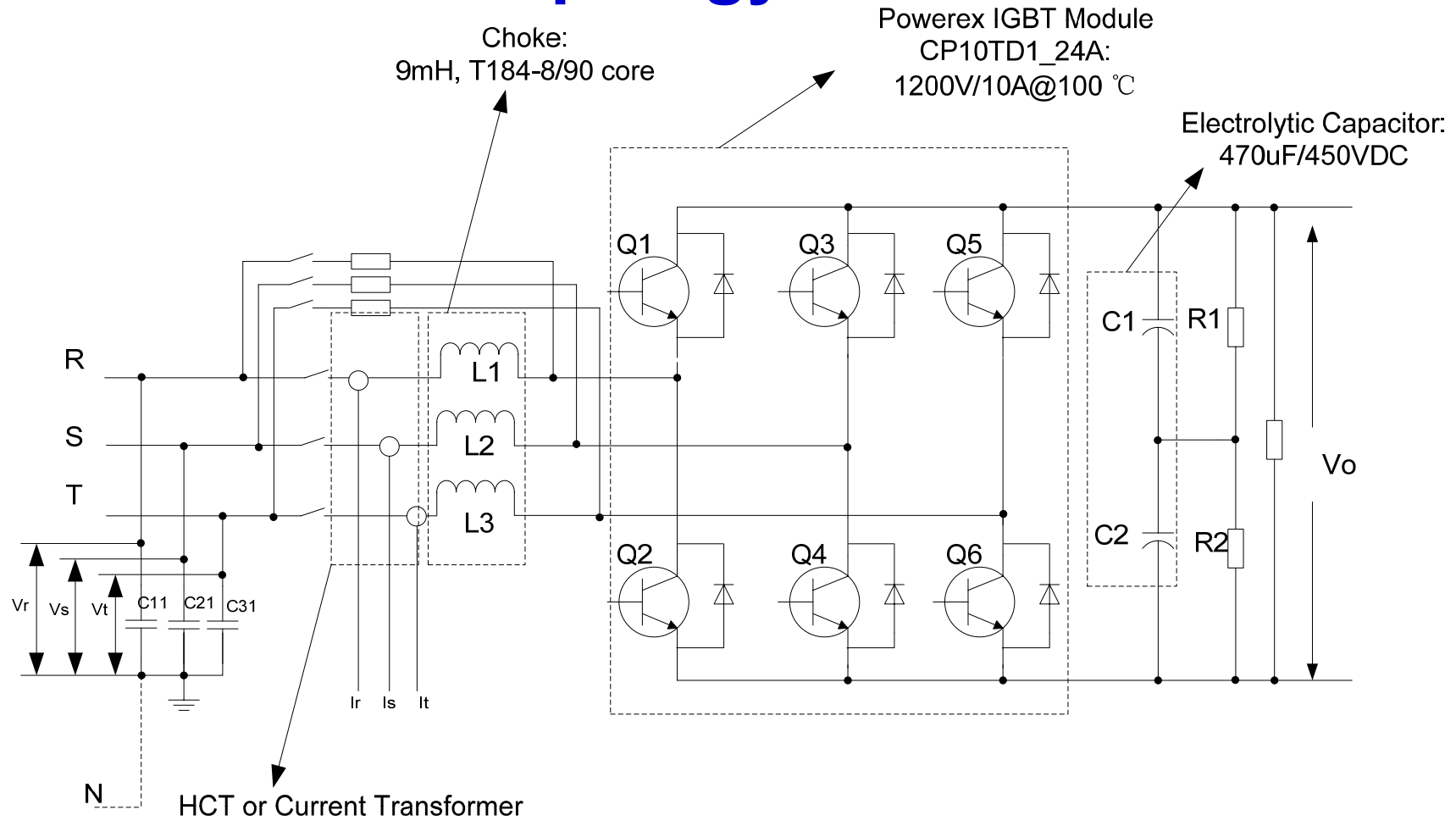

# Hardware Description

- **Main circuit considerations**

1. **Switch Frequency ---- 20kHz.**

For motor control application, the  $F_s$  can be reduced to 10kHz, and the choke size will be bigger and the inductance is higher.

2. **IGBT**

1200V IGBT must be used in this topology, because the maximum voltage between the  $V_{ce}$  is over 700V in theory. Actually, the 30% margin need to be considered.

3. **Electrolytic Capacitor**

The output DC voltage is larger than 600VDC in 380VAC system, then we must use 2 electrolytic capacitors in series.

4. **Current sensing ---- HCT need to be used for current controller. 2 HCTs at least.**

5. **Line voltage sensing --- Line- Neutral voltage(or Line to Line) need to be sensed**

# Hardware Description

- **Auxiliary Power**

The project did not design a three phase input auxiliary power for the system, all the power is from the external +15V adapter.

- The +5V is generated by the PTH08080 with the +15V input
- The +3.3V is generated by the TLV1117-33, with the +5V input
- The -15V used by the HCT, is generated by the DCH010515S with +5V input.



# Hardware Description

- **Soft start circuit**

When the line voltage connect to the board, the bus capacitor will be charged by the soft start circuit, and the voltage will rise to about 300V. The soft start must be finished before the converter start to work. In order to charge the bus in a limited current, there is a 1k/5w resistor in each phase. Besides, 3 relays are used to connect the line input to softstart circuit.


# Hardware Description

- MCU interface

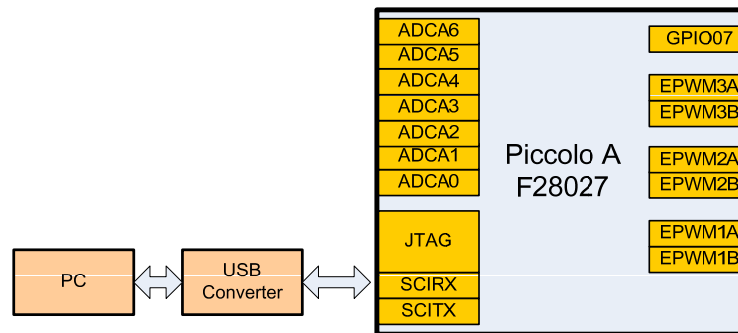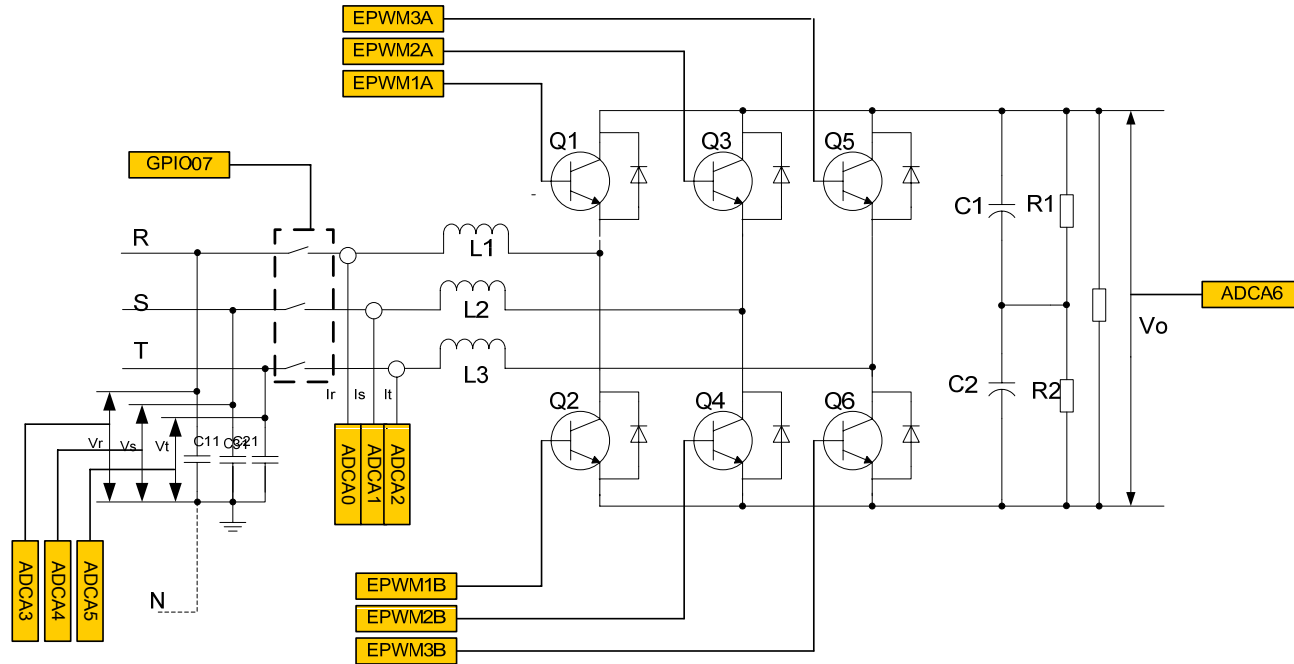


# Software Description

- **Software Flow**

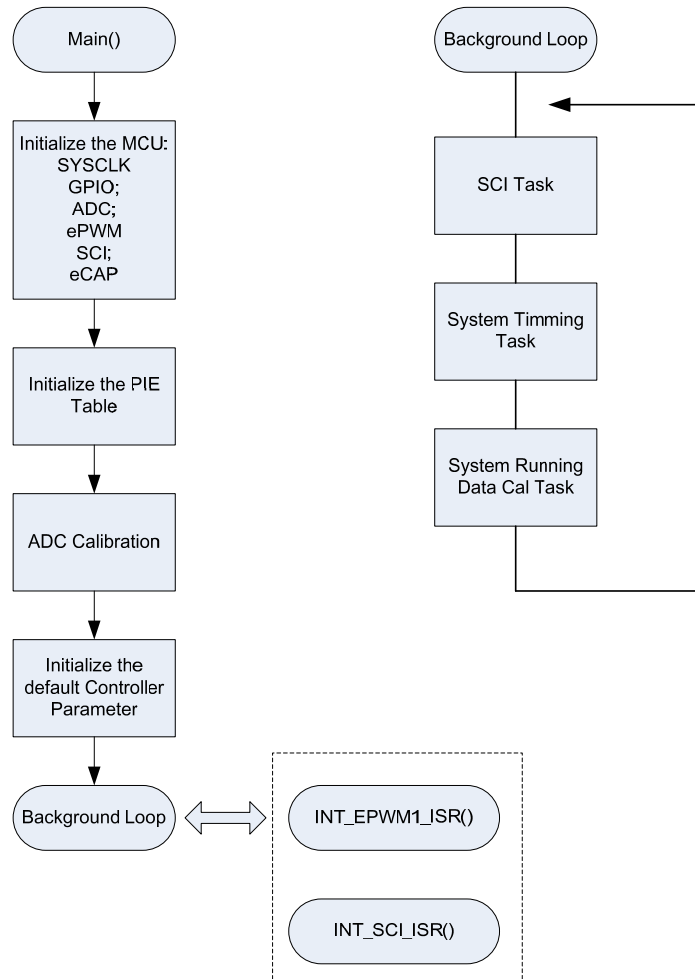


# Software Description

## •System Timing – Status machine

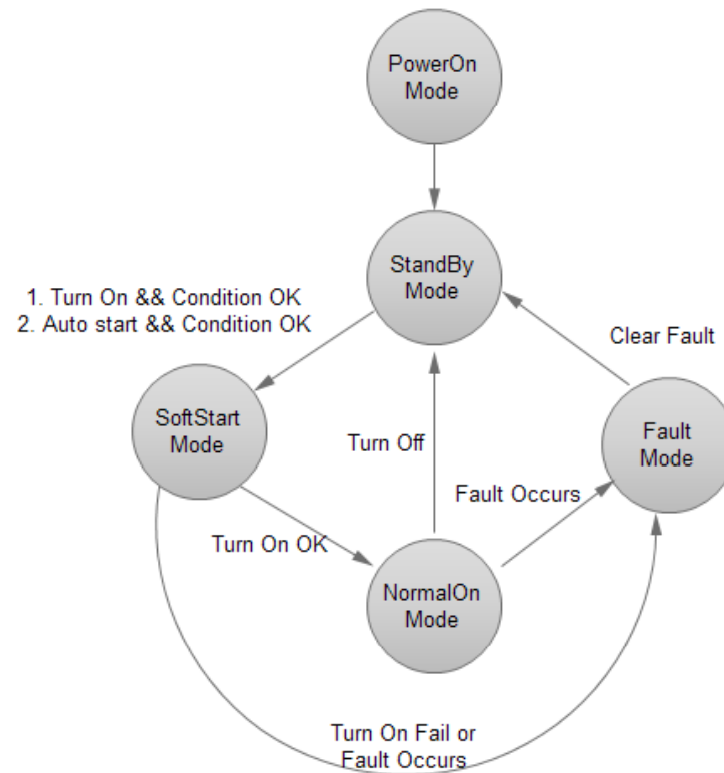

# Software Description


- **Software Flow**

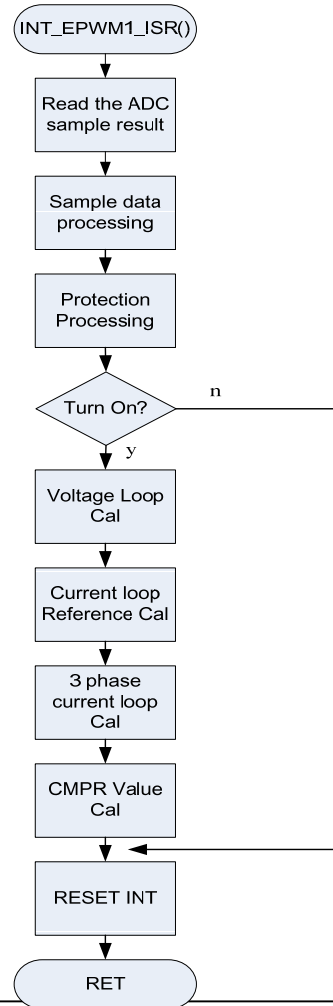




# Software Description

- ADC & ePWM

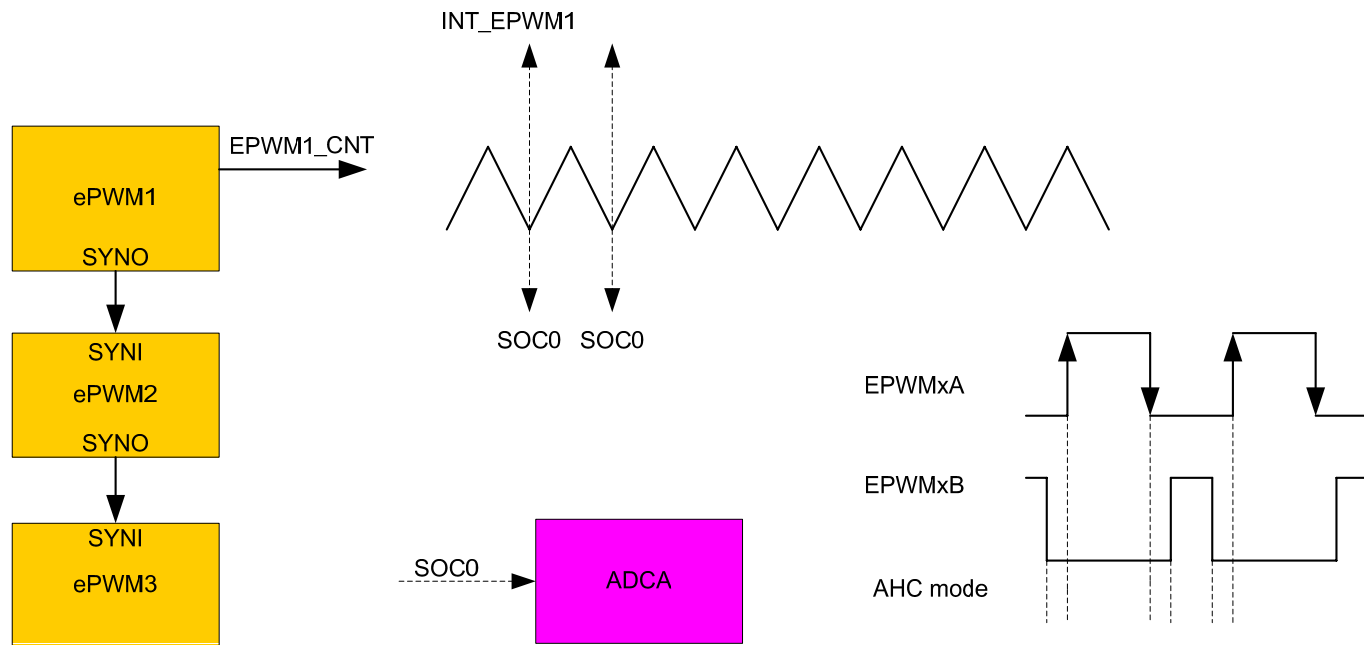
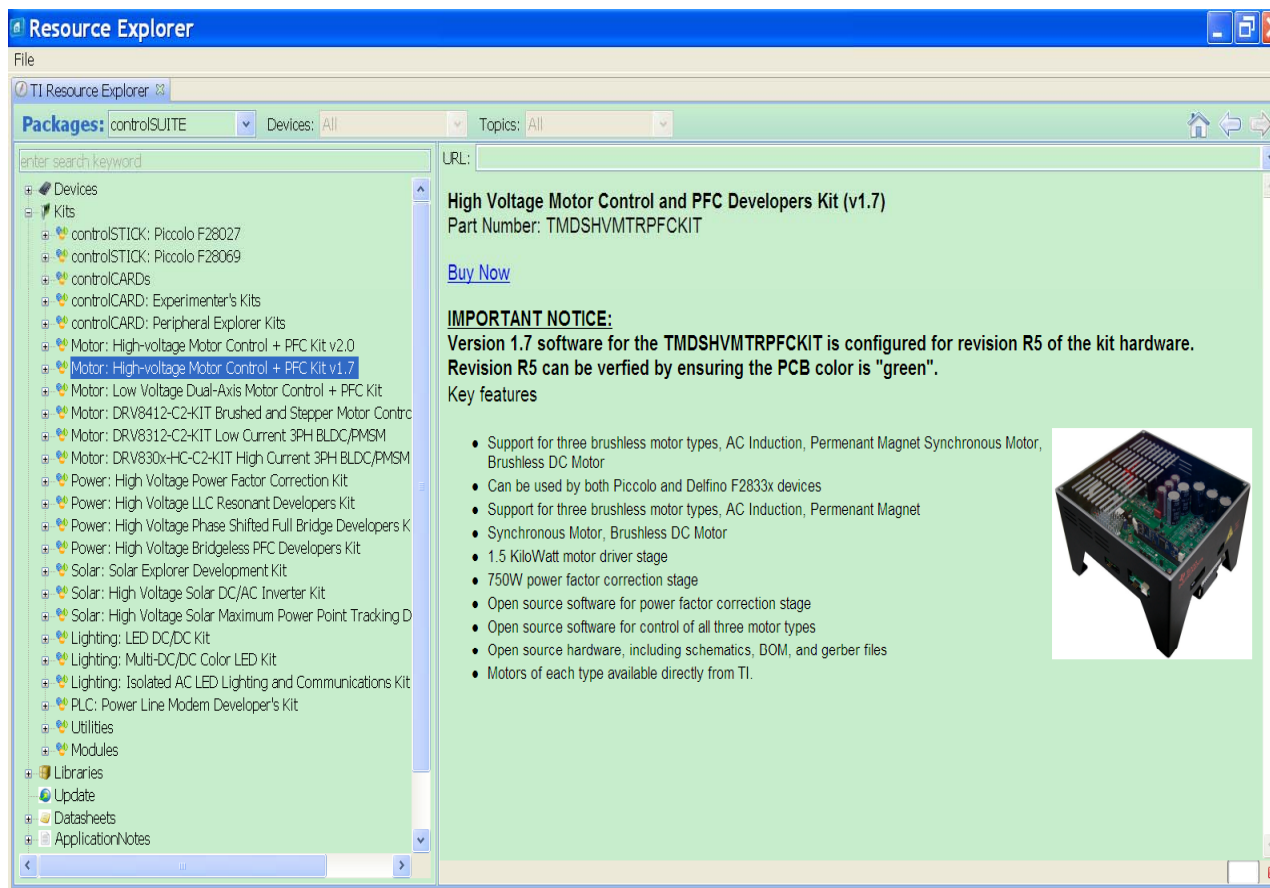
# Control SUITE

- <http://www.ti.com/mcu/docs/mcuproductcontentnp.tsp?sectionId=95&familyId=916&tabId=2656>



The screenshot shows the TI Resource Explorer interface. The left sidebar contains a tree view of categories: Devices, Kits, Power, Solar, Lighting, PLC, Utilities, Modules, Libraries, Update, Datasheets, and Application Notes. The 'Kits' category is expanded, and 'Motor: High-voltage Motor Control + PFC Kit v1.7' is selected. The main content area displays the product title, part number (TMDSHVMTRPFCKIT), a 'Buy Now' link, and an 'IMPORTANT NOTICE' regarding revision R5. Below the notice is a list of key features and a photograph of the physical development kit.


**High Voltage Motor Control and PFC Developers Kit (v1.7)**  
Part Number: TMDSHVMTRPFCKIT

[Buy Now](#)

**IMPORTANT NOTICE:**  
Version 1.7 software for the TMDSHVMTRPFCKIT is configured for revision R5 of the kit hardware. Revision R5 can be verified by ensuring the PCB color is "green".


**Key features**

- Support for three brushless motor types, AC Induction, Permanent Magnet Synchronous Motor, Brushless DC Motor
- Can be used by both Piccolo and Delfino F2833x devices
- Support for three brushless motor types, AC Induction, Permanent Magnet Synchronous Motor, Brushless DC Motor
- 1.5 KiloWatt motor driver stage
- 750W power factor correction stage
- Open source software for power factor correction stage
- Open source software for control of all three motor types
- Open source hardware, including schematics, DOM, and gerber files
- Motors of each type available directly from TI.




# Simulation

- The simulation diagram

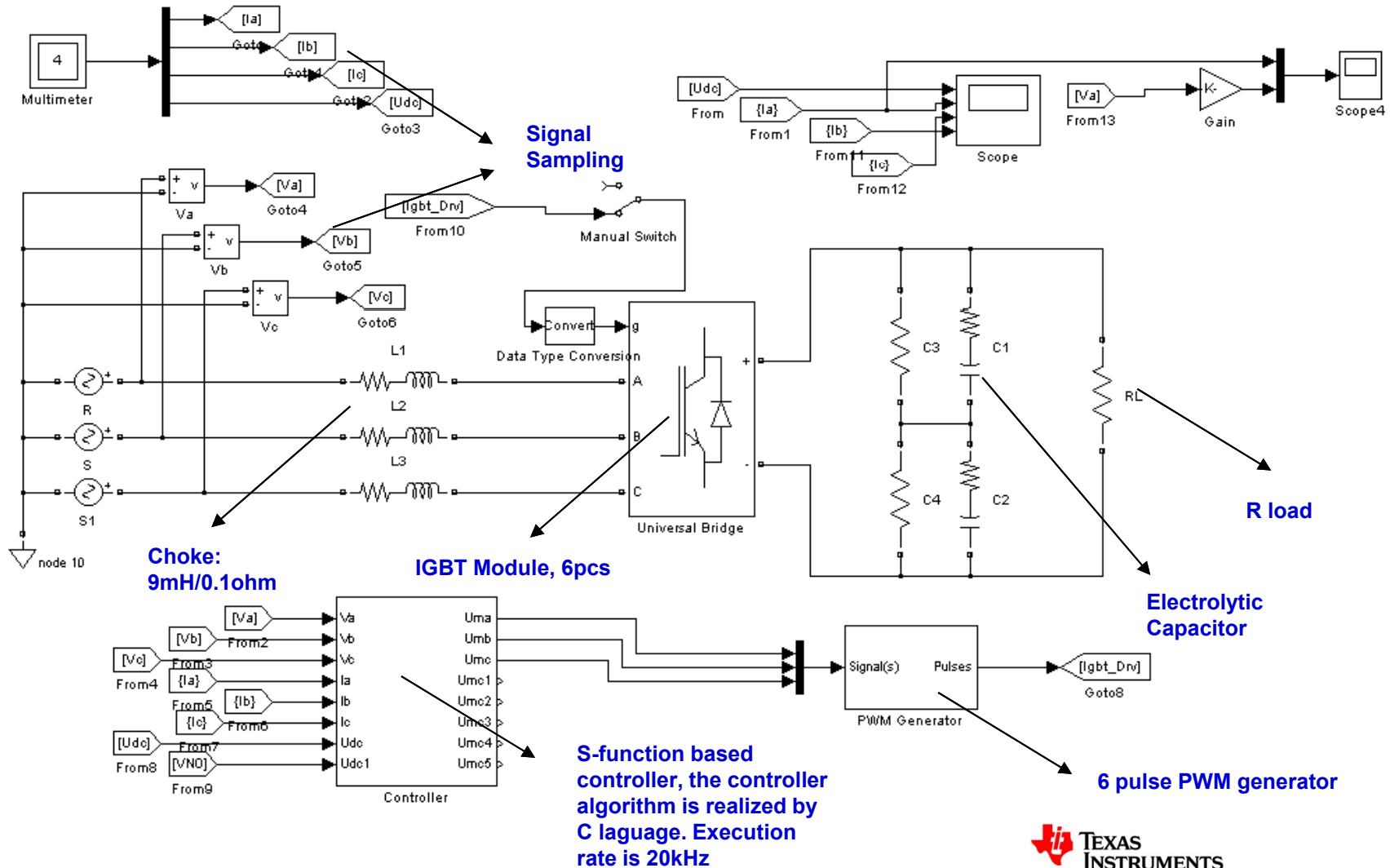

# Simulation Result

- The simulation result

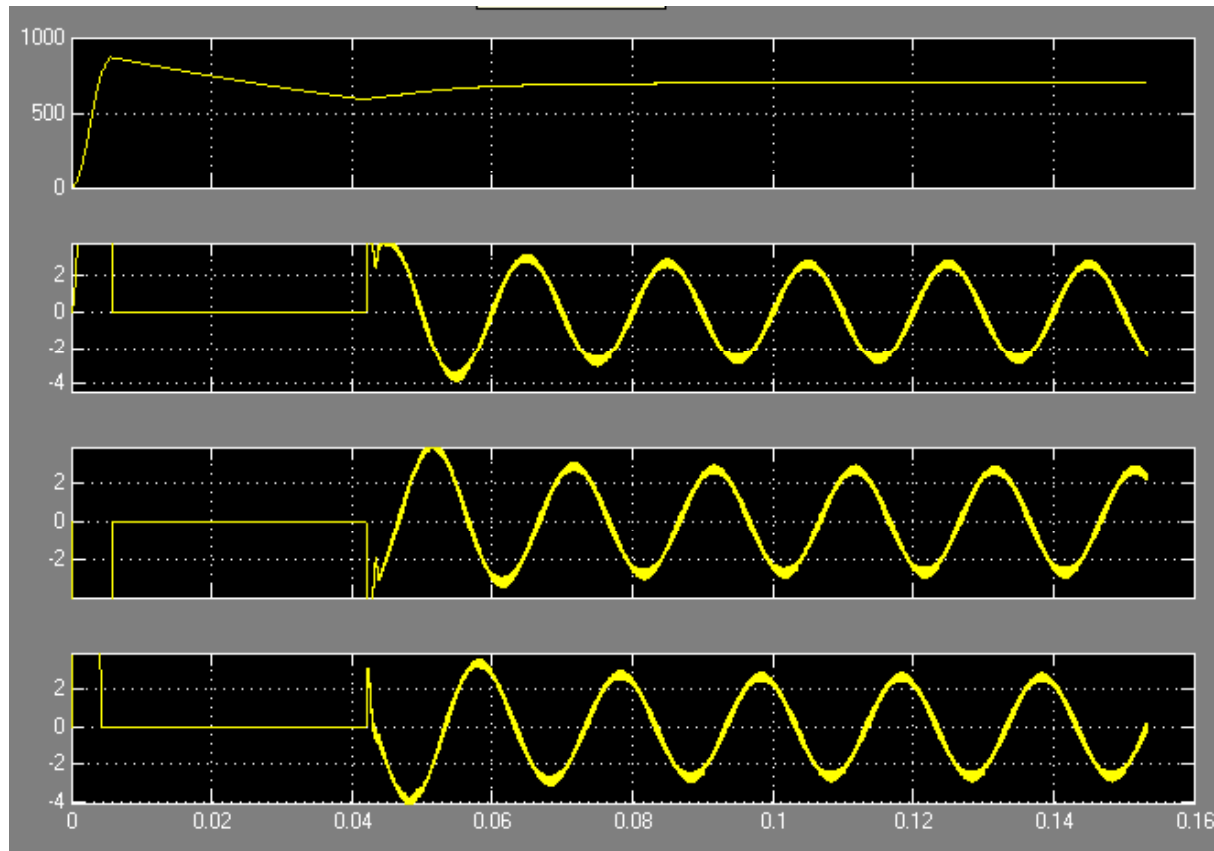


CH1: V<sub>dc</sub>  
CH2: R phase current  
CH3: S phase current  
CH4: T phase current

Conditions:

1. Directly input the line voltage to the converter from 0~0.04s;
2. At 0.04s, step to 700V<sub>dc</sub> reference;
3. Full load.

# Close loop Controller Design

- The simulation result --- Stable state

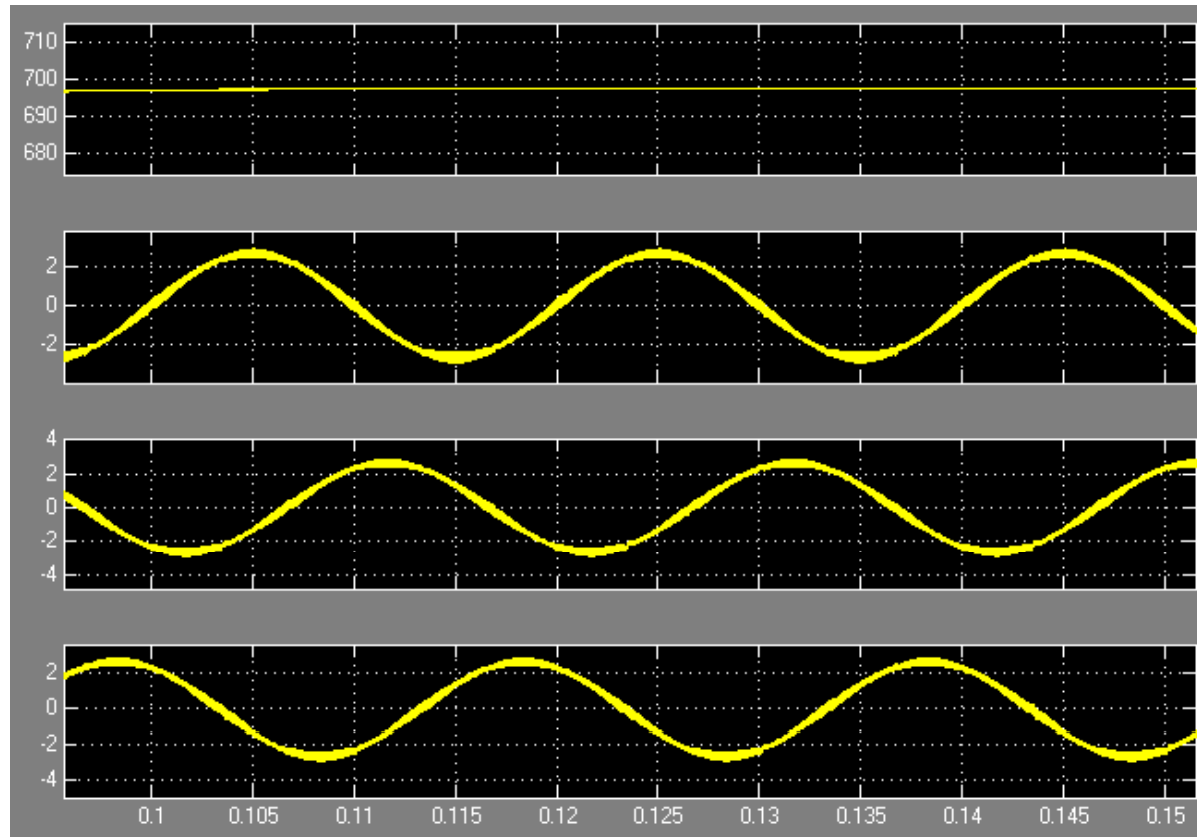


CH1: V<sub>dc</sub>  
CH2: R phase current  
CH3: S phase current  
CH4: T phase current

Conditions:

Full load at stable state.

# Close loop Controller Design

- The simulation result --- Stable state

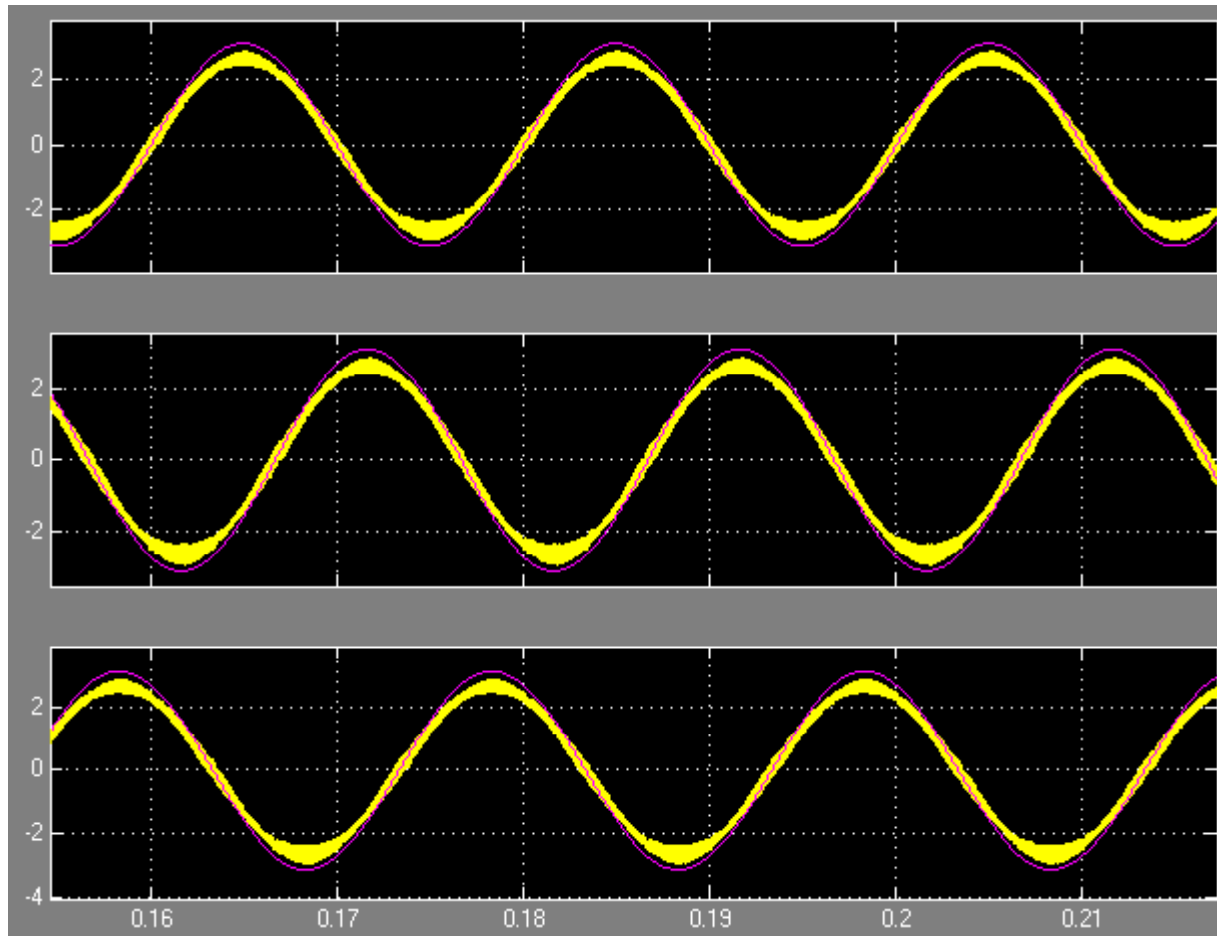


Yellow : phase current

Red: Line Voltage( 1/100)

# Close Loop Controller Design


- **The simulation result --- Stable state**

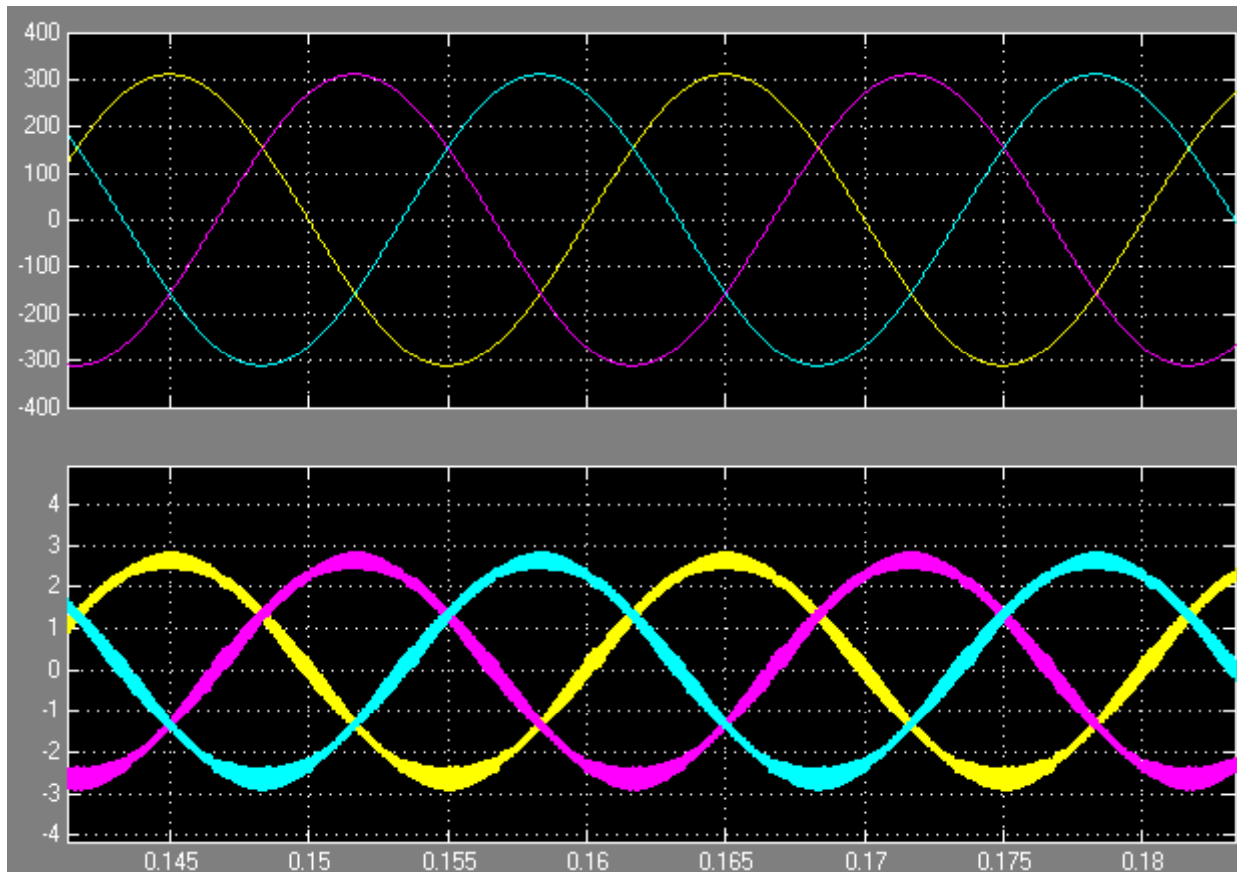

CH2 : phase current


CH1: Line Voltage( 1/100)

# EVM Performance

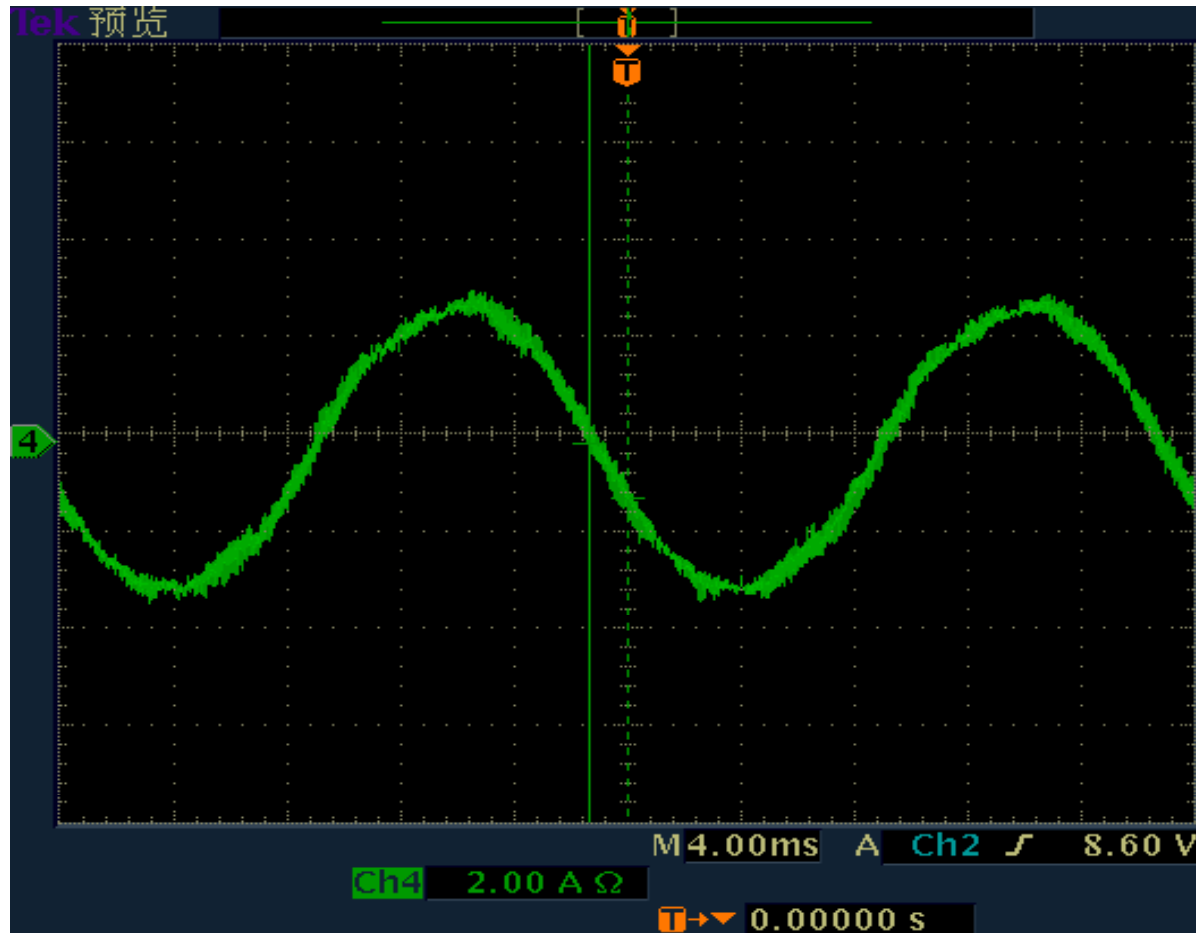



# EVM Performance

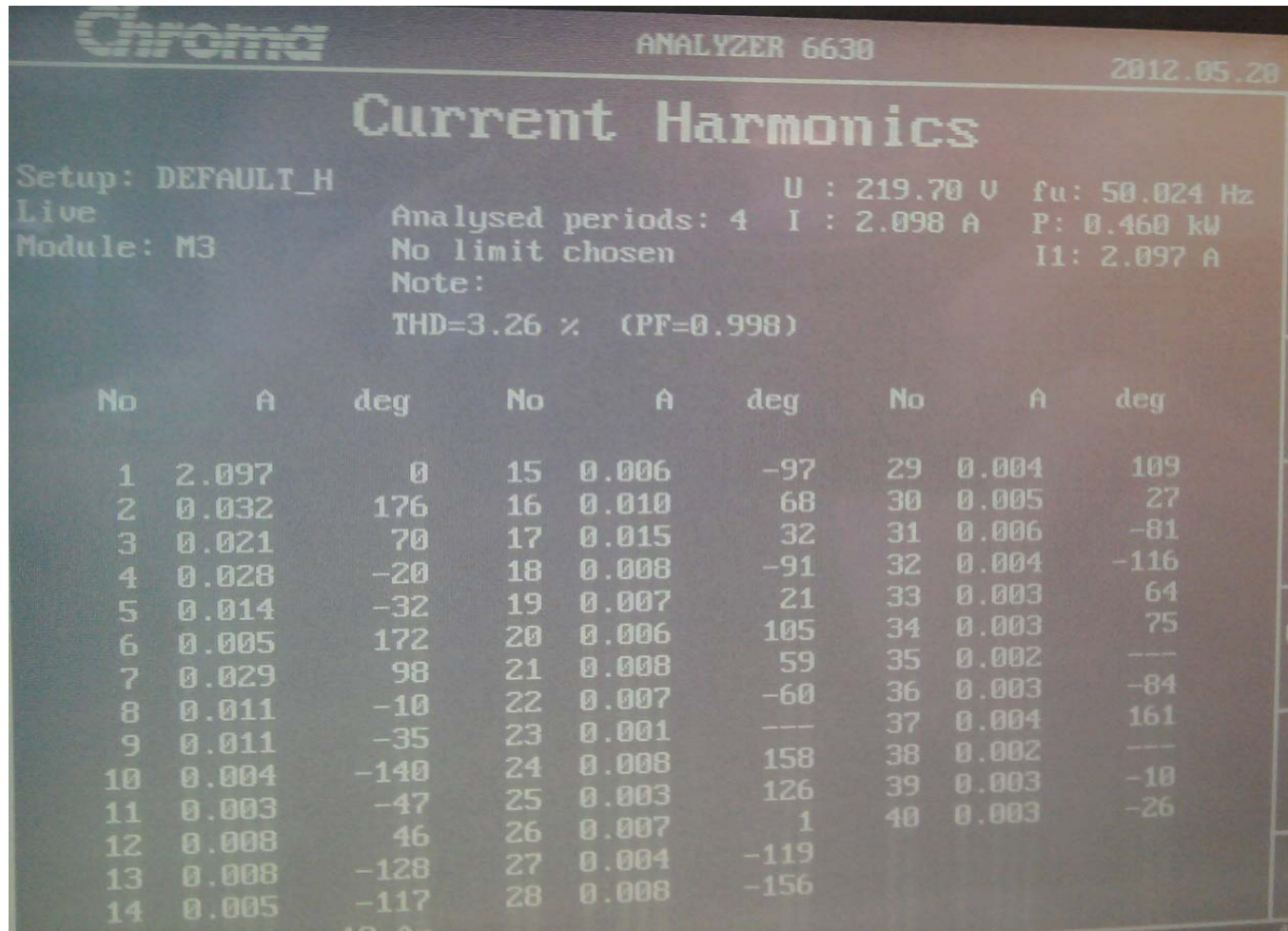

**Q&A**

**Thanks!**