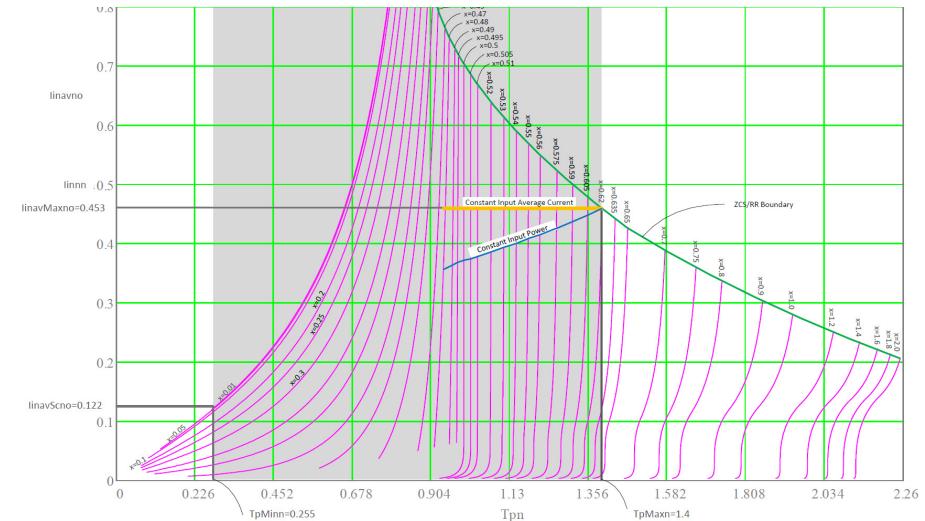


**LLC Design for UCC29950**

Dr. J M Leisten

Power Stage


**Figure 18. LLC Steady-State Normalized Operating Characteristic for Fixed Output Voltage  $I_m = 5$** 

Clearly, there are a range of constant power curves running between these two gain curves that could be used to deliver the required input voltage regulation range. For a particular input power, the curve that is highest up the Y-axis delivers the highest characteristic impedance ( $Z_n$ ) and hence the lowest total RMS current. To avoid excess switching power loss (and possibly damage to the primary MOSFETs) avoid having the peak power regulation curve cross the ZCS /RR Boundary curve. This forces us to place the peak power regulation curve no higher than the position of the blue curve indicated in Figure 18.

- Because our application is with fixed input (380V) and fixed output(5V) for 400W- all GaN, we need to optimize in a very different way. Our controller is  $\frac{1}{2}$  of Delfino(CPU2) so we essentially need to figure out n, Lm, k and Cr. Can we get the mathworks file used for this design guide?