



# Buck Converter Modeling, Control, and Compensator Design




# OUTLINE

- **Three terminal PWM switch modeling**
- **Open loop transfer function**
- **Voltage Mode Control and Peak Current Mode Control**
  - **Closed loop transfer functions**
  - **Closed loop gain**
  - **Compensator Design**
  - **Pspice and Mathcad Simulation**
  - **Experimental verification**



# Voltage Mode Switching Regulator

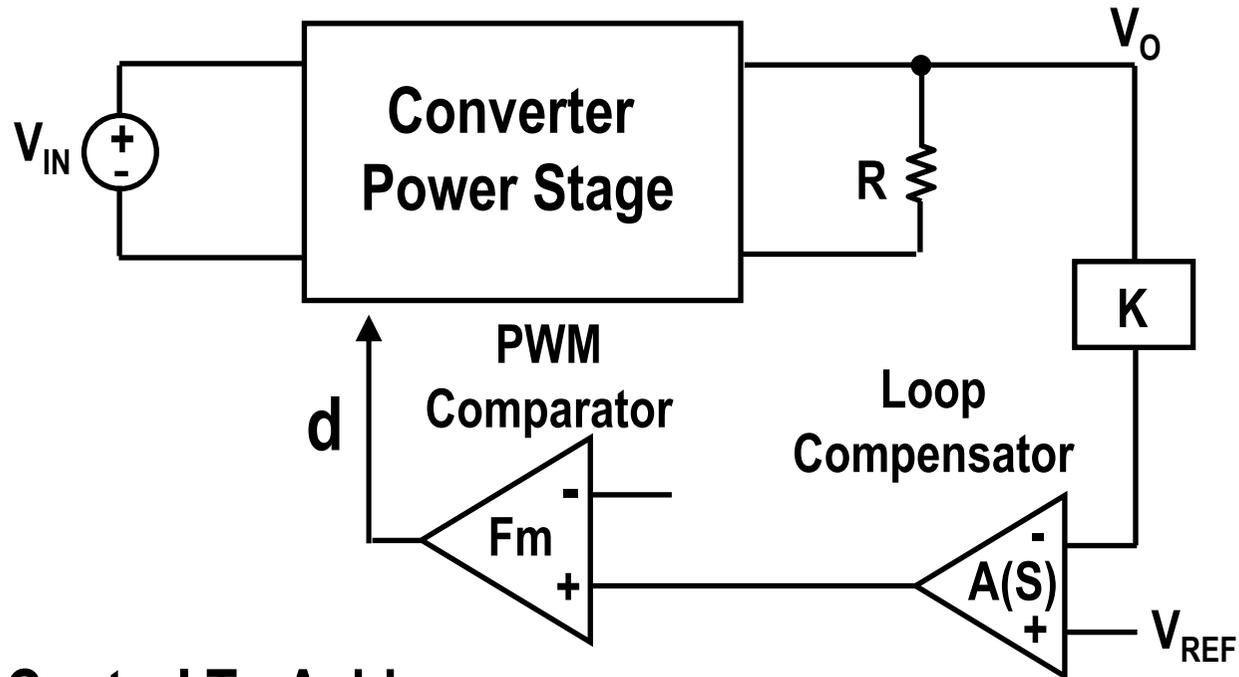

## Feedback Control To Achieve


- **Accuracy:** Steady-State Error
- **Speed:** Transient Response
- **Stability** Gain and Phase Margin



# Average **Small Signal** PWM Switch Modeling



# Average Model

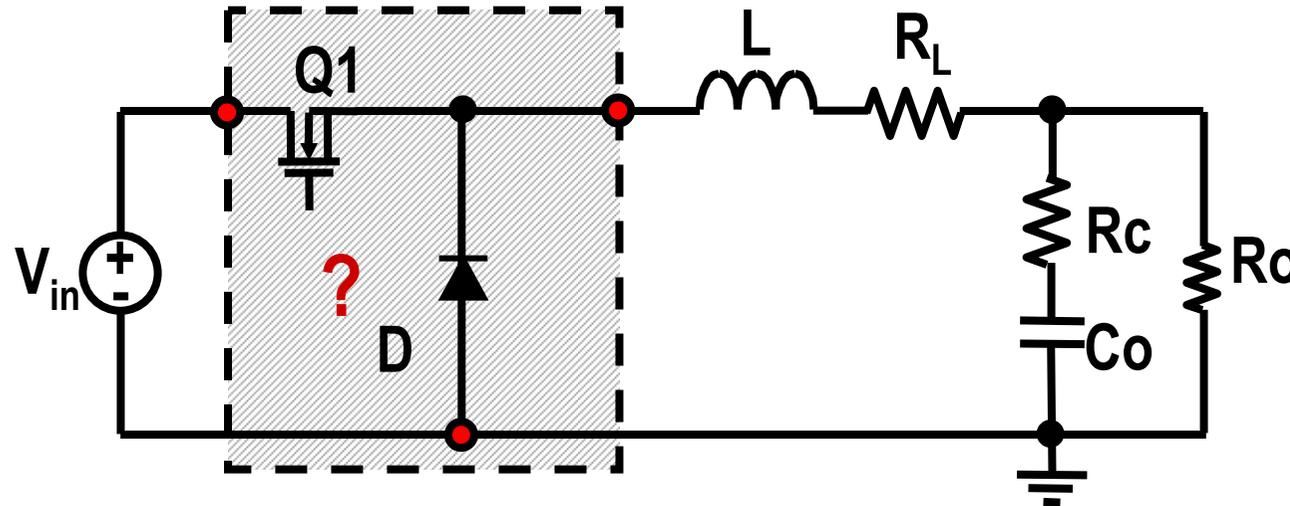

## Nonlinear Characteristics for Switching Elements Q1 and Q2


### Modeling Method:

1. Space Average Model-----Middlebrook (CIT)
2. Three Terminal Switch --- Vorperian (VPEC)
3. DC Transformer Based




# PWM Switch in Basic DC-DC Converters


## Buck

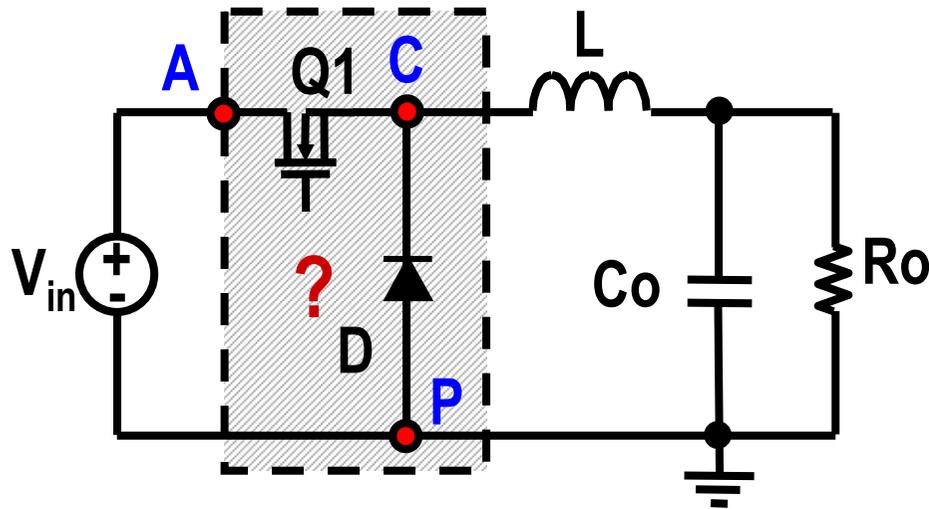

## Boost

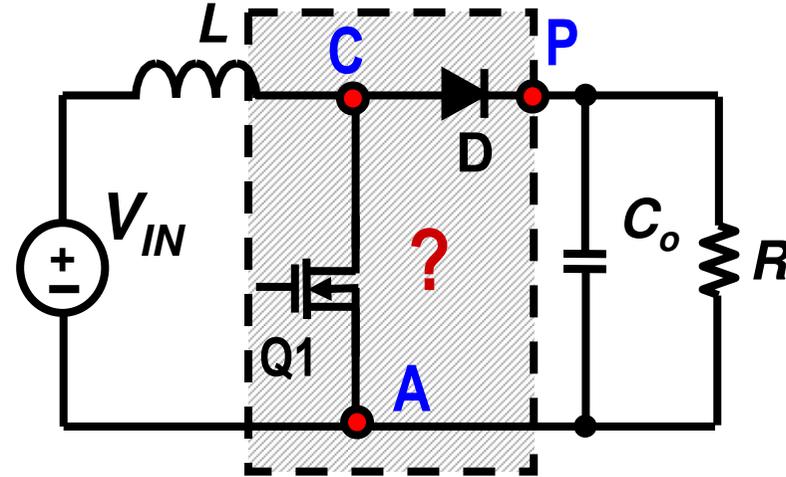


## Buck-Boost

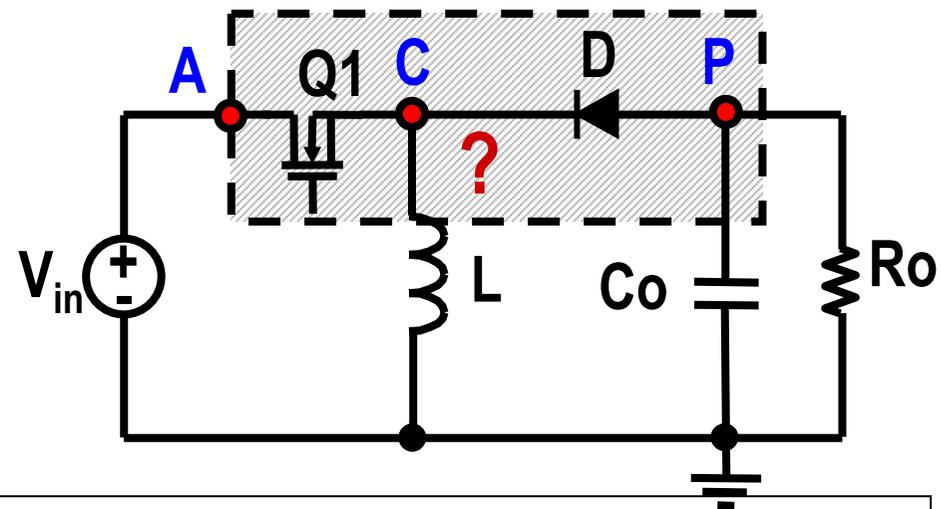


- A: Active Switch Node
- C: Common Node
- P: Passive switch (Diode)




# Non-Linear PWM Switch

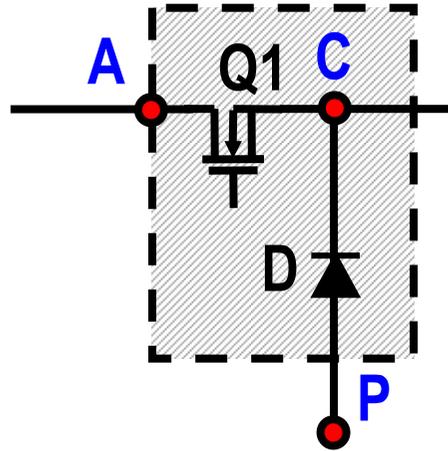

DC Model

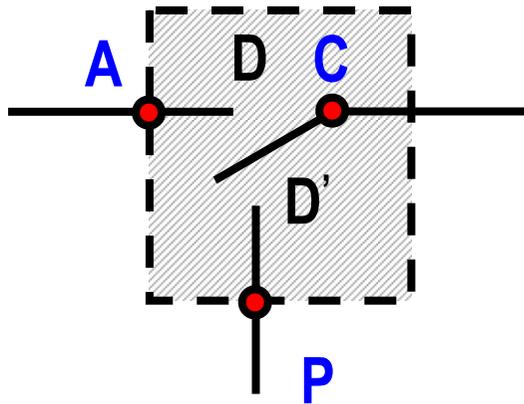



AC Model

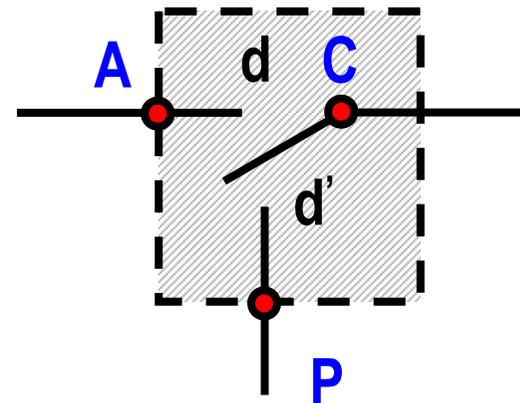

Where  $D' = 1 - D$


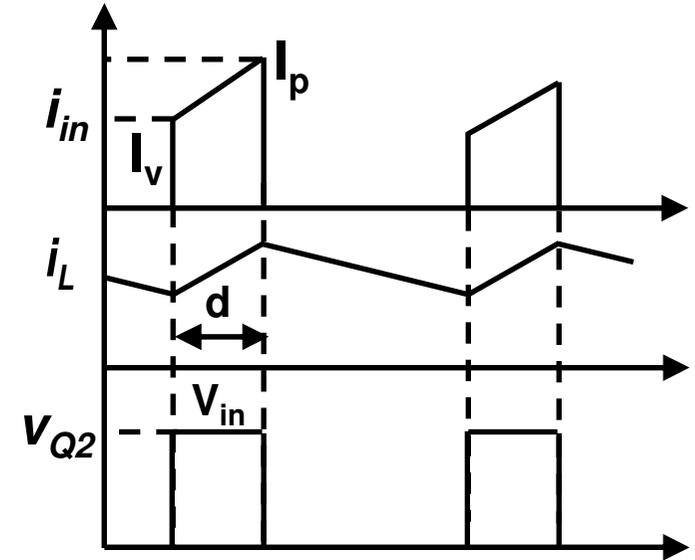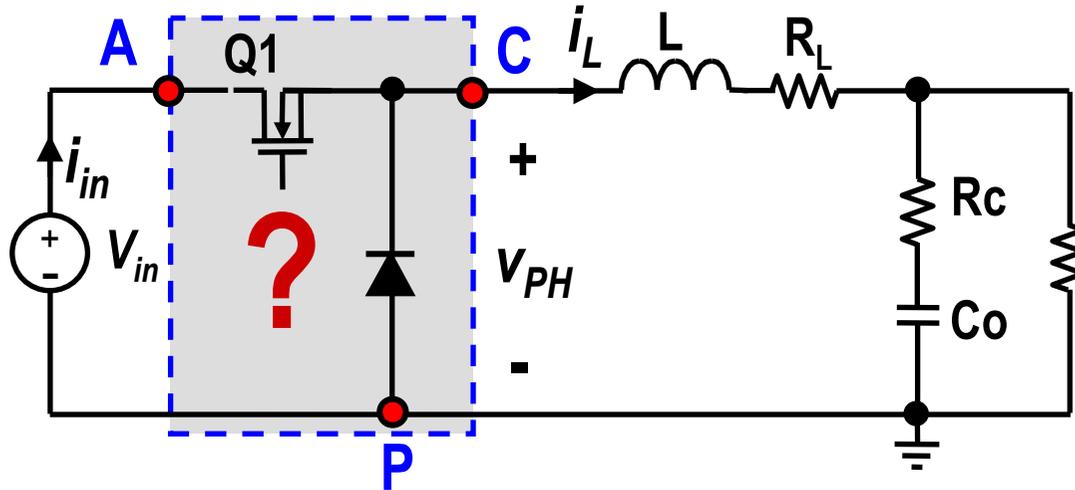
## Average Model for Buck Regulator (Cont.)




$$\bar{i}_{in} = \frac{I_p + I_v}{2} \cdot d = d \bar{i}_L$$

**Transformer Characteristics**


$$\bar{i}_{in} = \bar{i}_L d$$

$$\bar{V}_{PH} = \bar{V}_{in} d$$

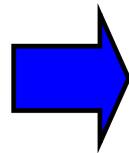

**Model valid only at CCM**

**DC Average Model**

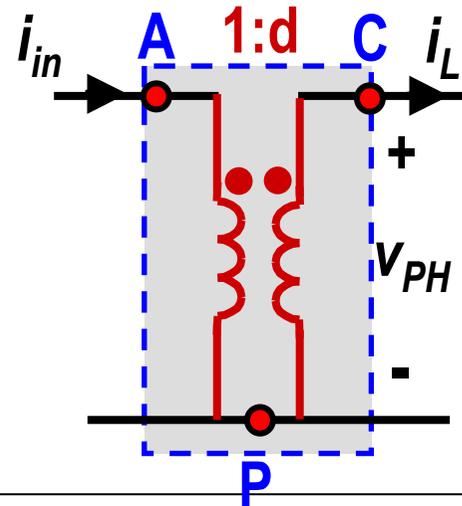



## What is Small Signal Model?

- Adding a small signal near the operating point


$$v_{in} = V_{in} + \hat{v}_{in}$$

$$i_{in} = I_{in} + \hat{i}_{in}$$

$$d = D + \hat{d}$$

$$i_L = I_L + \hat{i}_L$$

$$v_{PH} = V_{PH} + \hat{v}_{PH}$$

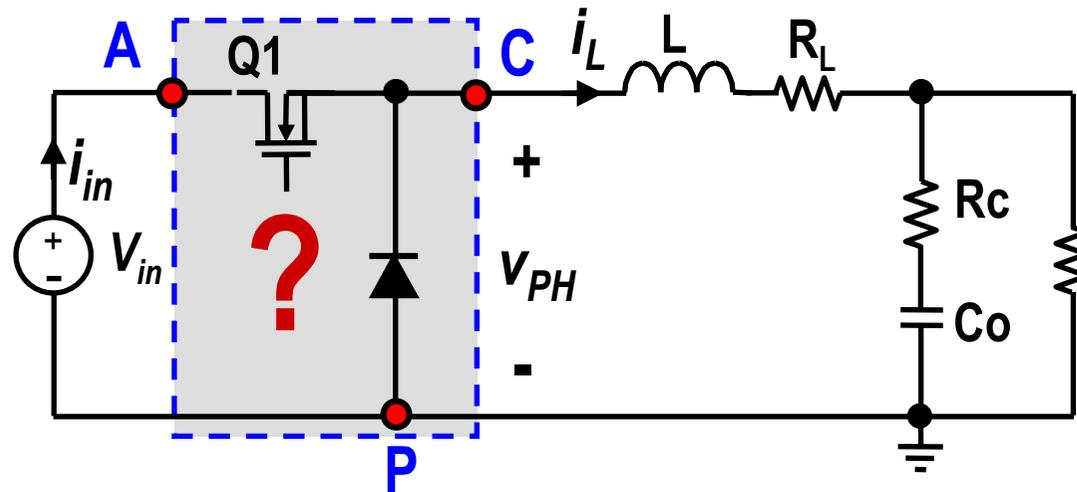



# Small Signal Average Model of three Terminal PWM Switch

$$i_{in} = i_L d$$

$$V_{PH} = v_{in} d$$

## Linearization


$$v_{in} = V_{in} + \hat{v}_{in}$$

$$i_{in} = I_{in} + \hat{i}_{in}$$

$$d = D + \hat{d}$$


$$i_L = I_L + \hat{i}_L$$

$$V_{PH} = V_{PH} + \hat{v}_{PH}$$

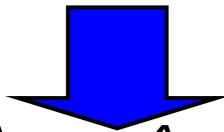


$$\hat{i}_{in} = I_L \hat{d} + D \hat{i}_L$$
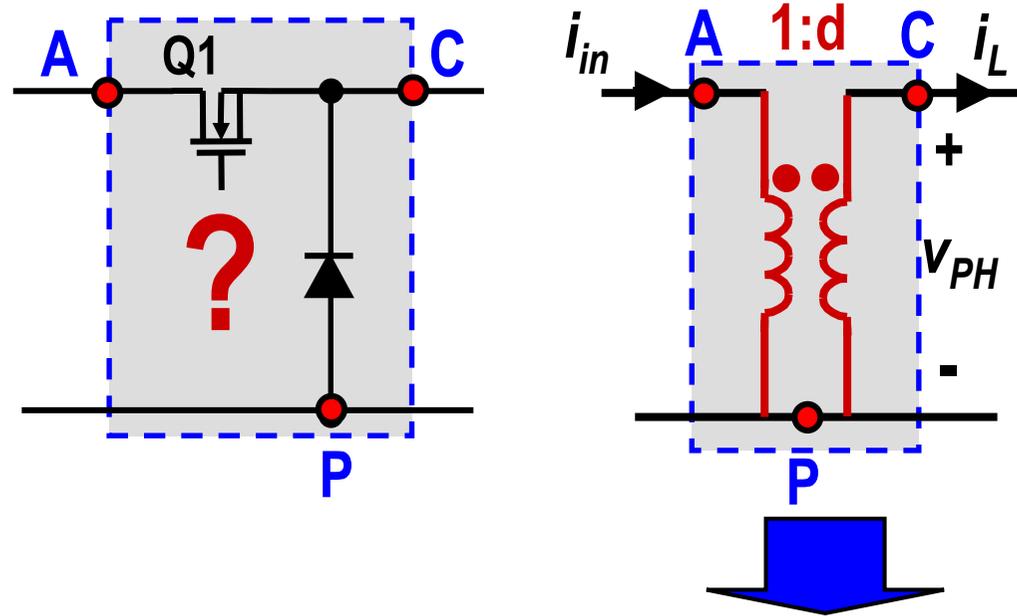
$$\hat{v}_{PH} = V_{in} \hat{d} + D \hat{v}_{in}$$






## Small Signal Average Model

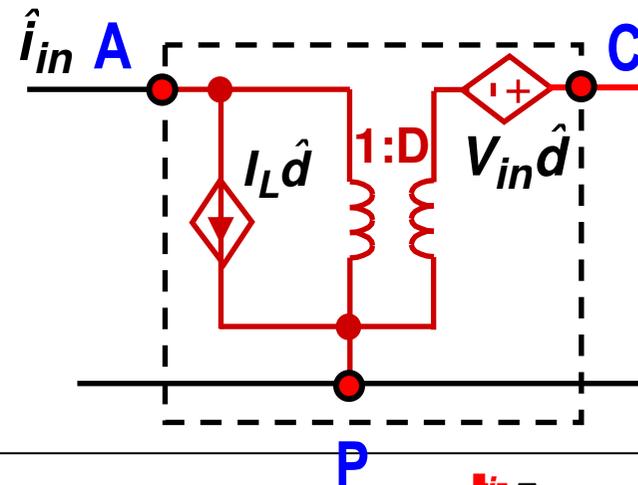


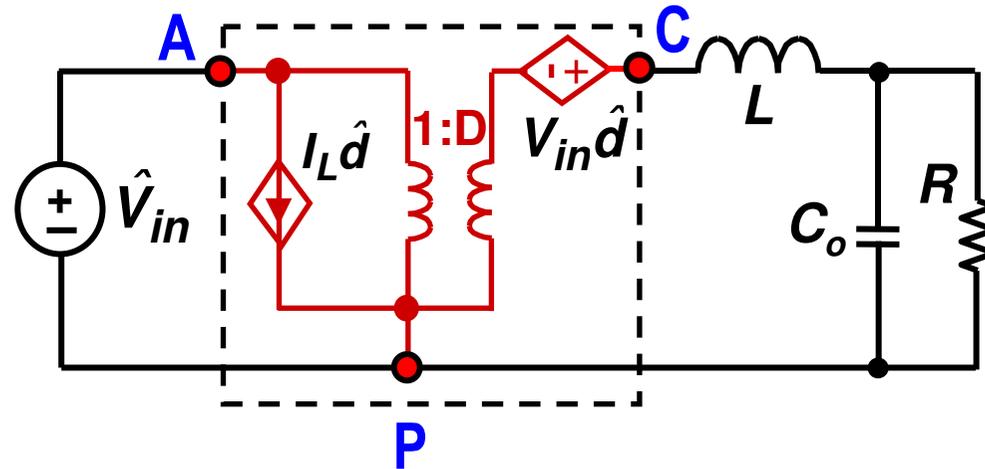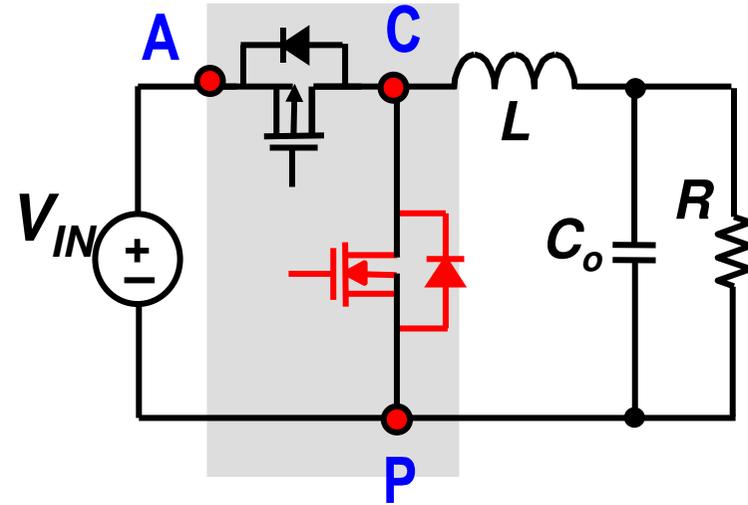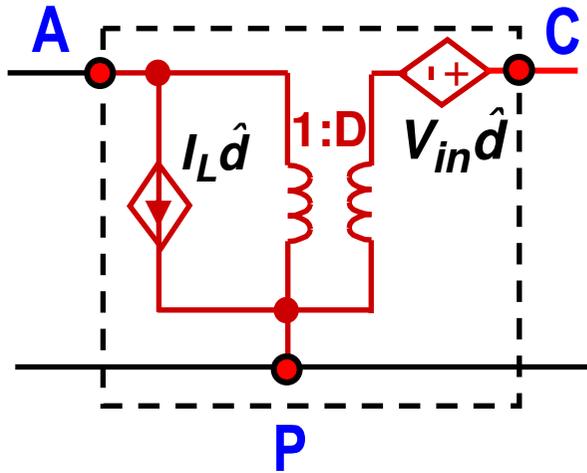
# Small Signal Average Model Buck Converter







# Open Loop Line to Output Transfer Function (Buck)

$$G_V = \left. \frac{\hat{V}_o}{\hat{V}_{in}} \right|_{\hat{d}=0} = D \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$

$$G_V = \left. \frac{V_o}{V_{in}} \right|_{s=0} = D$$

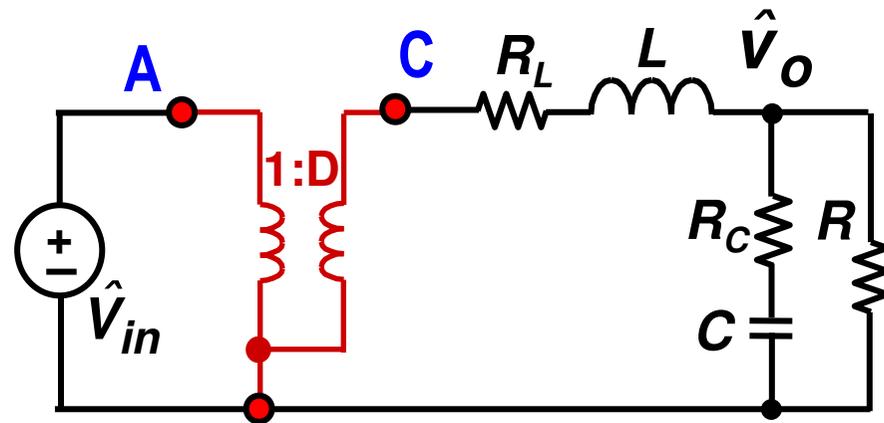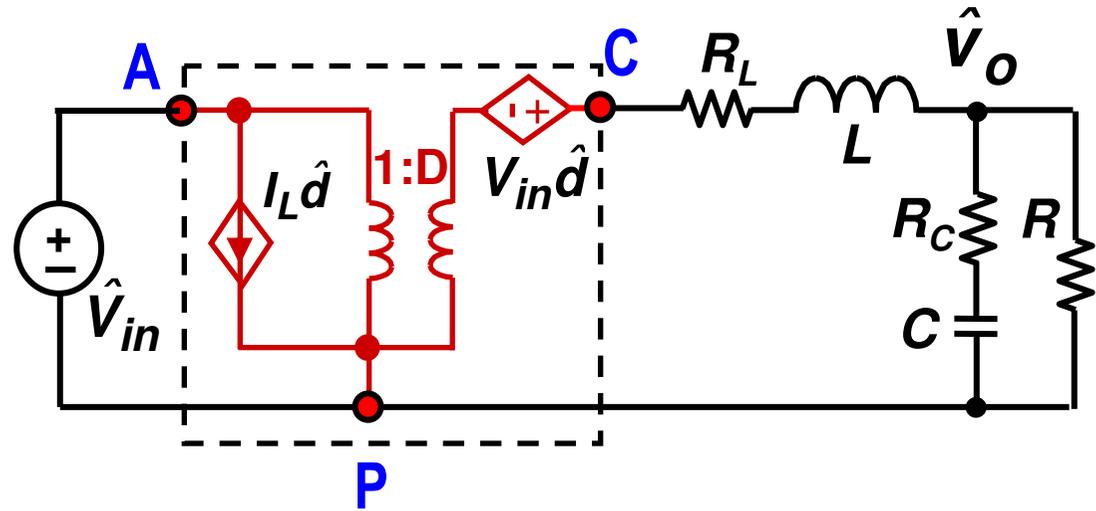


$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_C C}, \quad \omega_{zL} = \frac{R_L}{L}, \quad Q \approx \frac{R}{\sqrt{\frac{L}{C}}}$$



## Open Loop Line to Output Transfer Function (buck)

$$G_V = \frac{\hat{V}_o}{\hat{V}_{in}} \Big|_{\hat{d}=0} = D \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$


$$G_V = \frac{V_o}{V_{in}} \Big|_{s=0} = D$$

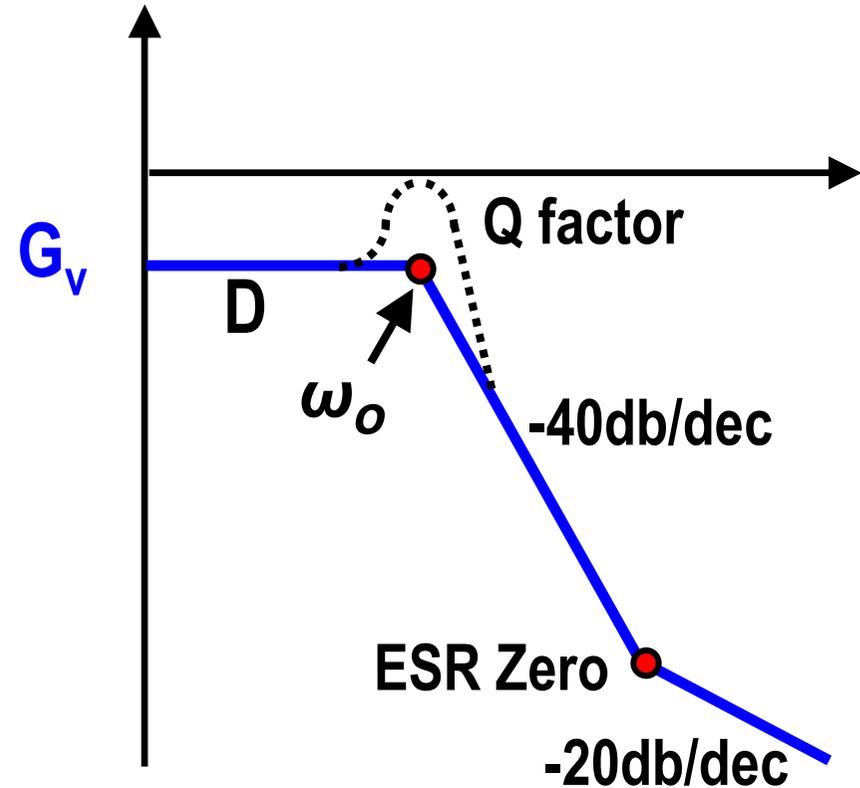

$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad \omega_{zL} = \frac{R_L}{L}, \quad Q \approx \frac{R}{\sqrt{L/C}}$$



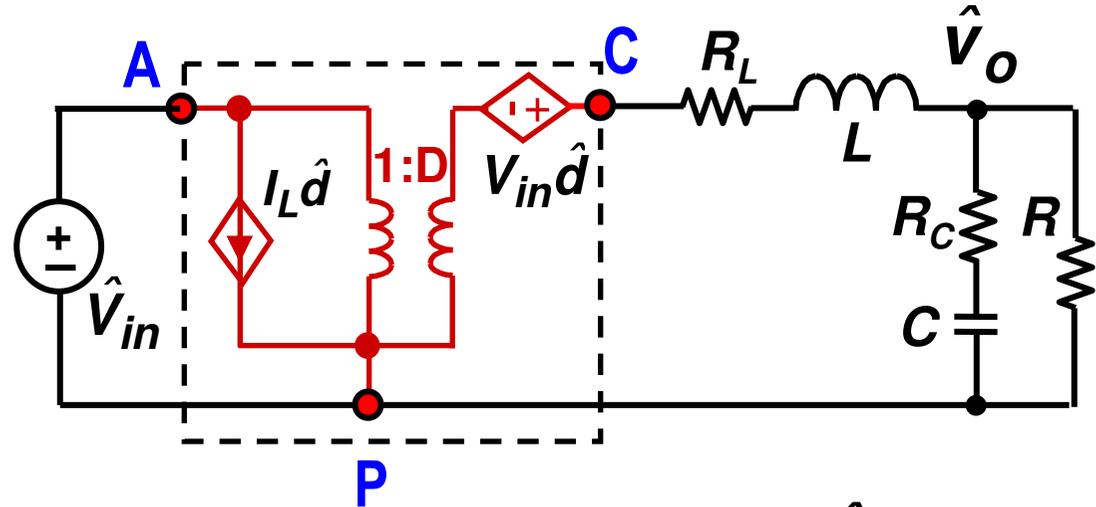
# Open Loop Control to Output Transfer Function (Buck)



$$G_d = \left. \frac{\hat{V}_o}{\hat{d}} \right|_{\hat{v}_{in}=0} = V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$

$$G_d(DC) = \frac{V_o}{D} = V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \Bigg|_{s=0}$$

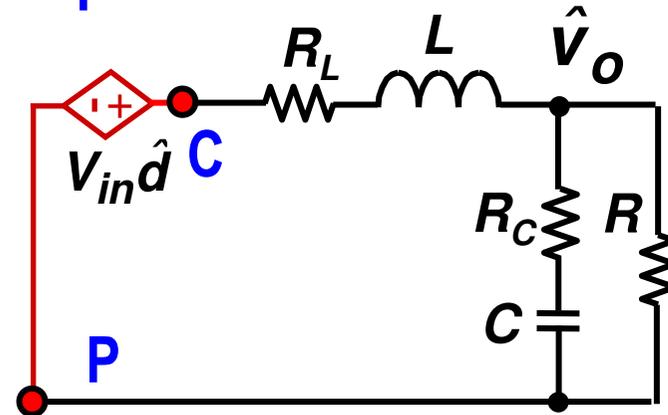


$$= V_{IN} \quad \omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad \omega_{zL} = \frac{R_L}{L}, \quad Q \approx \frac{R}{\sqrt{\frac{L}{C}}}$$



## Control to Output Transfer Function (buck)

$$G_d = \frac{\hat{v}_o}{\hat{d}} \Big|_{\hat{v}_{in}=0} = V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$

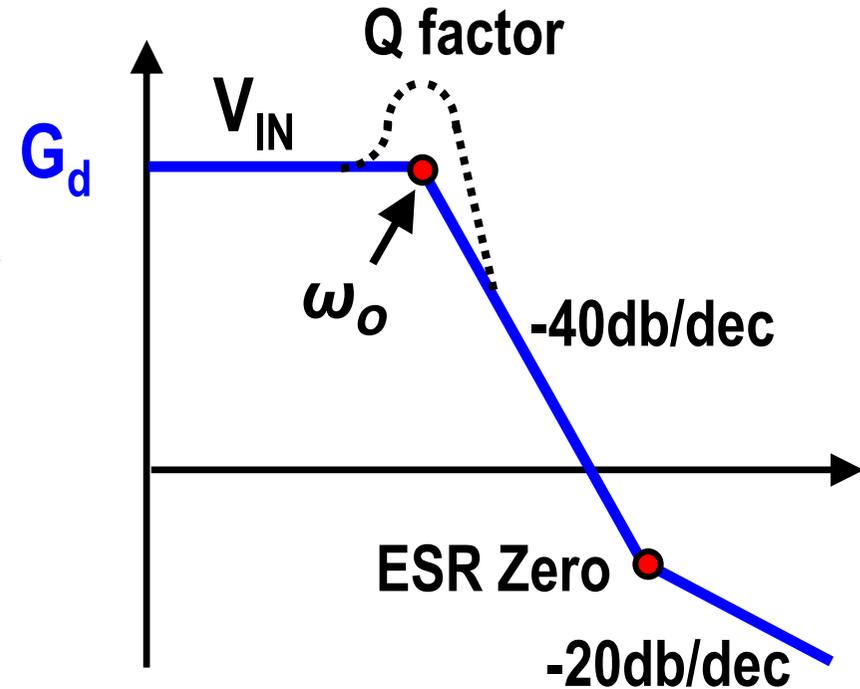


$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad \omega_{zL} = \frac{R_L}{L}, \quad Q \approx \frac{R}{\sqrt{L/C}}$$



# Open Loop Output Impedance


$$Z_p = \frac{\hat{V}_o}{\hat{i}_o} \Big|_{\hat{d} = \hat{v}_{in} = 0}$$

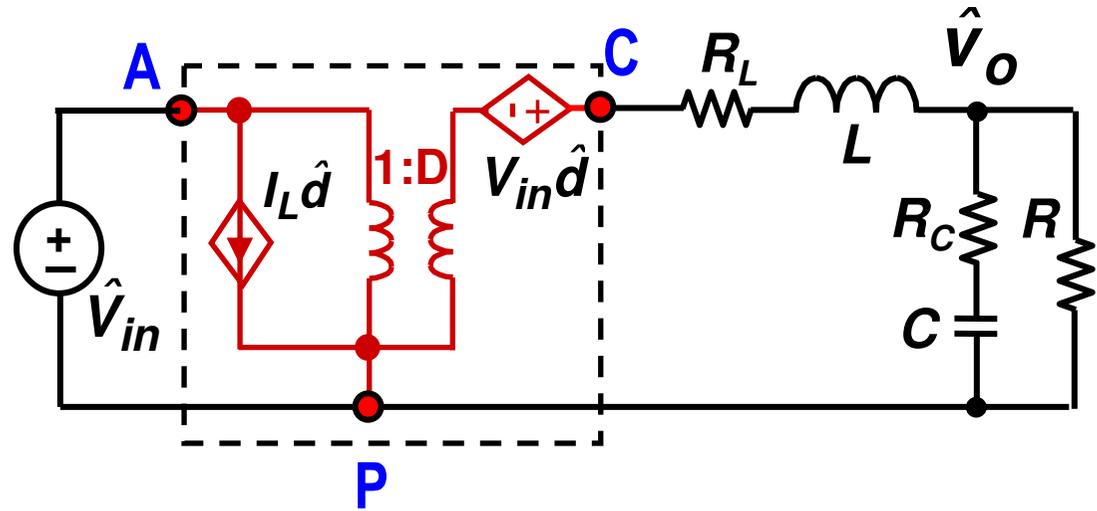

$$Z_p = \frac{\hat{V}_o}{\hat{i}_o} = R_L // R \cdot \frac{(1 + \frac{s}{\omega_z}) \cdot (1 + \frac{s}{\omega_{zL}})}{1 + \frac{s}{Q\omega_0} + \frac{s^2}{\omega_0^2}}$$

$$Z_p(s = 0) = R_L // R$$

$$Z_p(s = \infty) = R_C // R$$

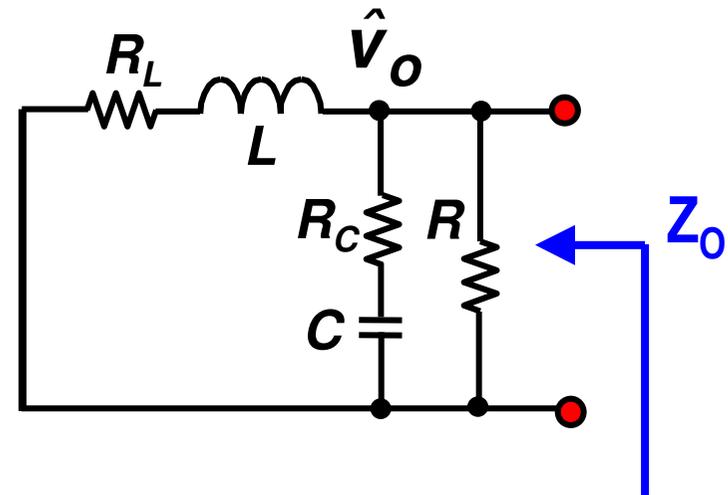





# Open Loop Output Impedance

$$Z_p = \frac{\hat{V}_o}{\hat{i}_o} = R_L // R \cdot \frac{(1 + \frac{s}{\omega_z}) \cdot (1 + \frac{s}{\omega_{zL}})}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$

$$Z_p(s=0) = R_L // R$$

$$Z_p(s=\infty) = R_c // R$$

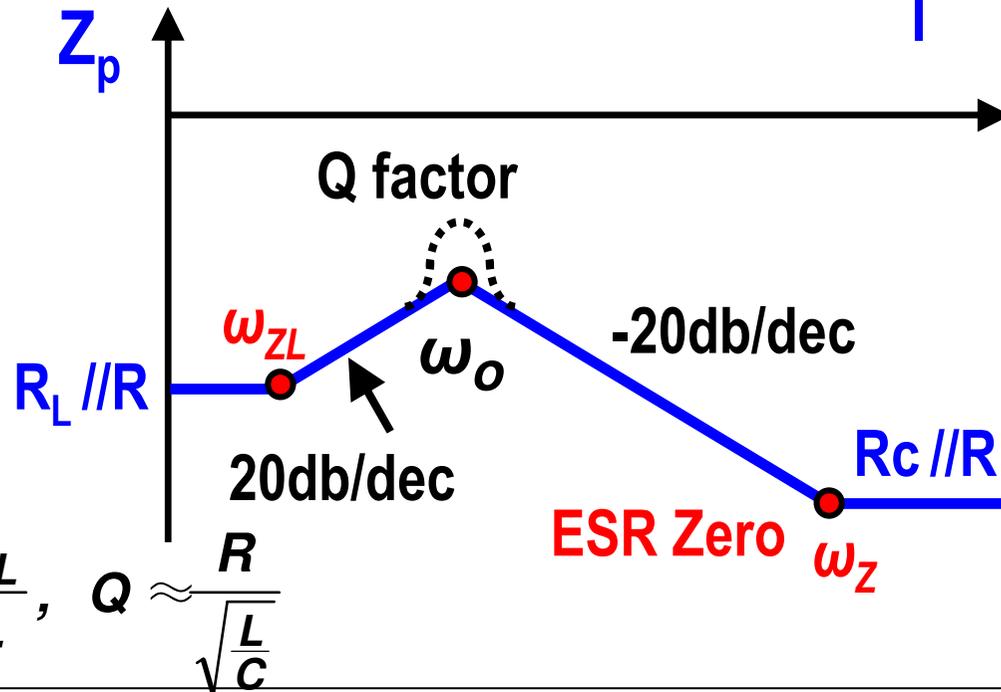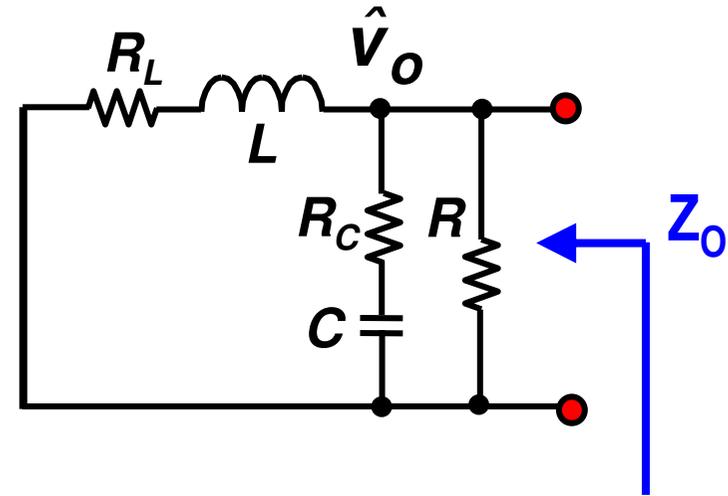


$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad \omega_{zL} = \frac{R_L}{L}, \quad Q \approx \frac{R}{\sqrt{\frac{L}{C}}}$$




# Single Close Loop Controlled Switching Regulator


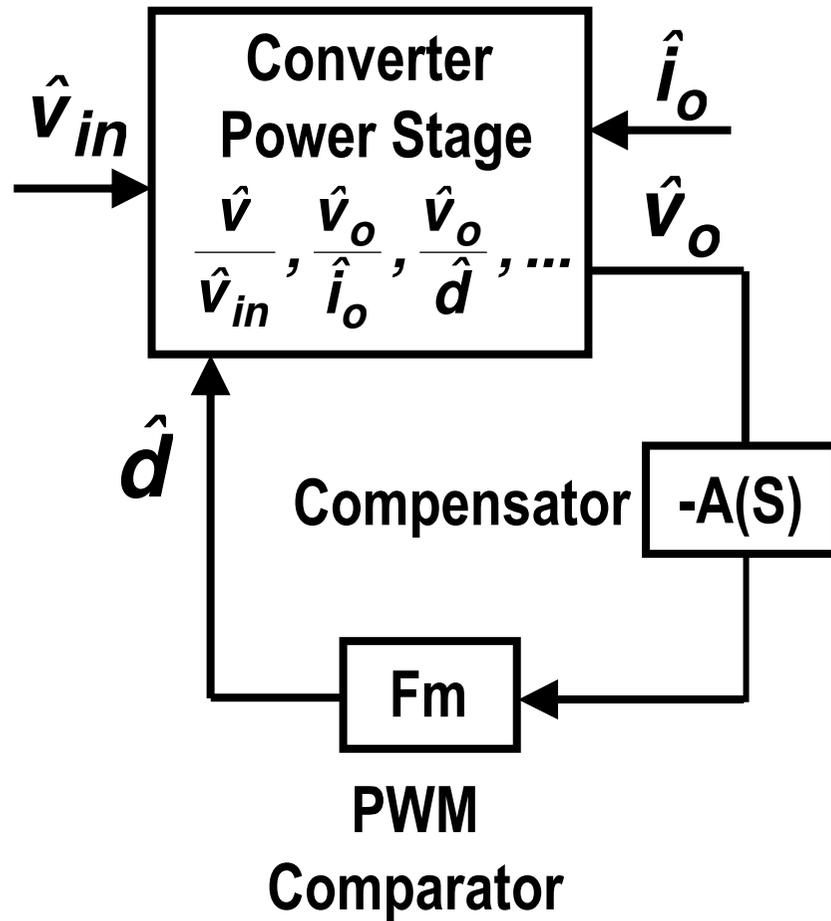
# Small Signal Close Loop Controlled Switching Regulator



## Small Signal Block Diagram

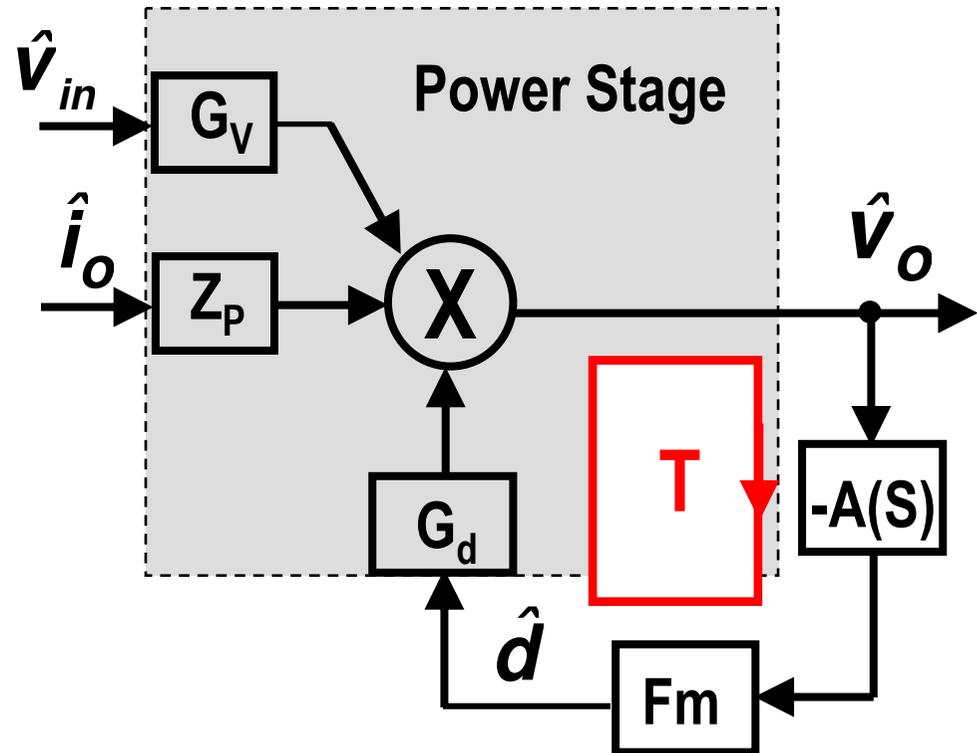




# Open-loop Transfer Function

**Open Loop Voltage Gain**  
*(Open loop audio Susceptibility)*

$$G_V = \frac{\hat{v}_o}{\hat{v}_{in}} @ \hat{i}_o = 0 \text{ and } \hat{d} = 0$$

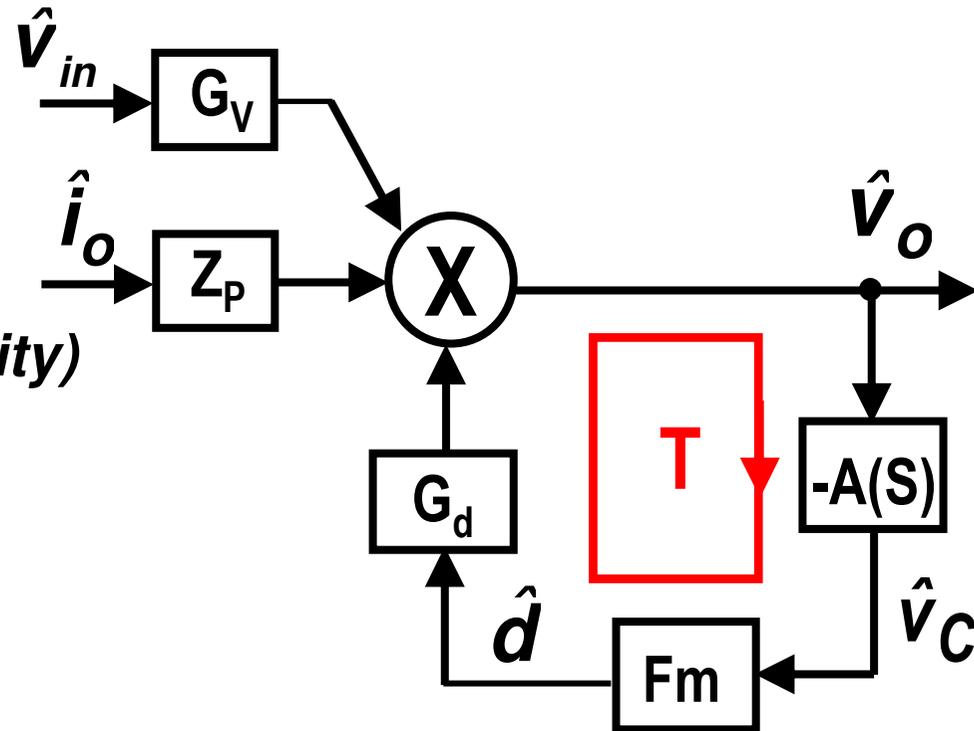**Open Loop Output Impedance**

$$Z_p = \frac{\hat{v}_o}{\hat{i}_o} @ \hat{d} = 0 \text{ and } \hat{v} = 0$$





## Open-loop Transfer Function (Cont.)

### Control to Output Transfer Function


$$G_d = \frac{\hat{v}_o}{\hat{d}} @ \hat{v}_{in} = \hat{i}_o = 0$$

### Loop Compensator Gain

$$A(s) = \frac{\hat{v}_c}{\hat{v}_o}$$


### PWM Comparator Gain

$$F_m = \frac{\hat{d}}{\hat{v}_c}$$

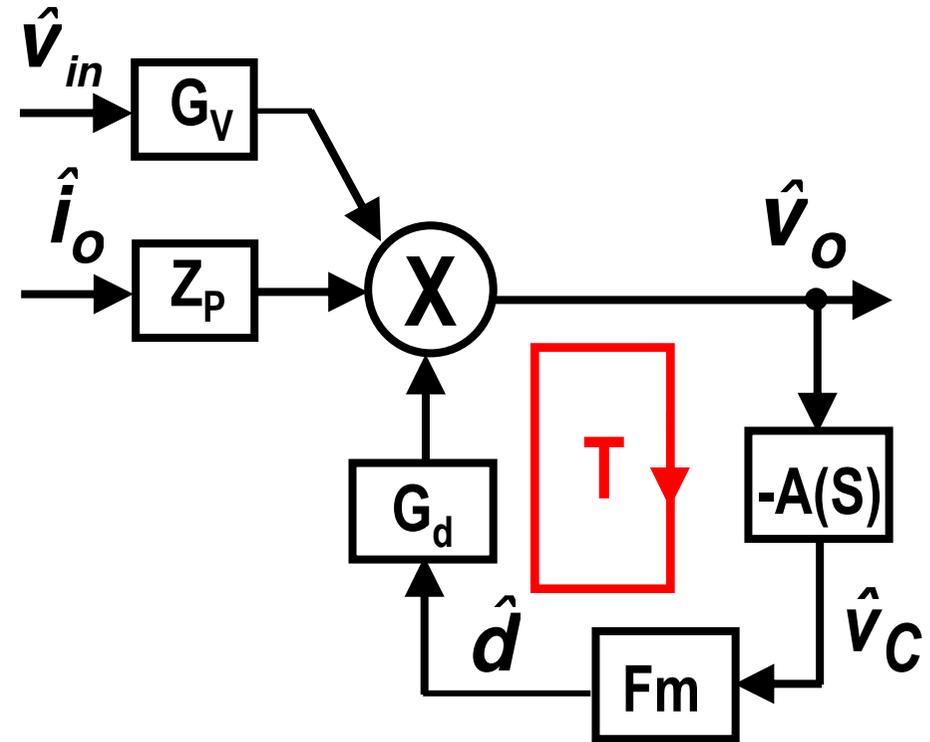


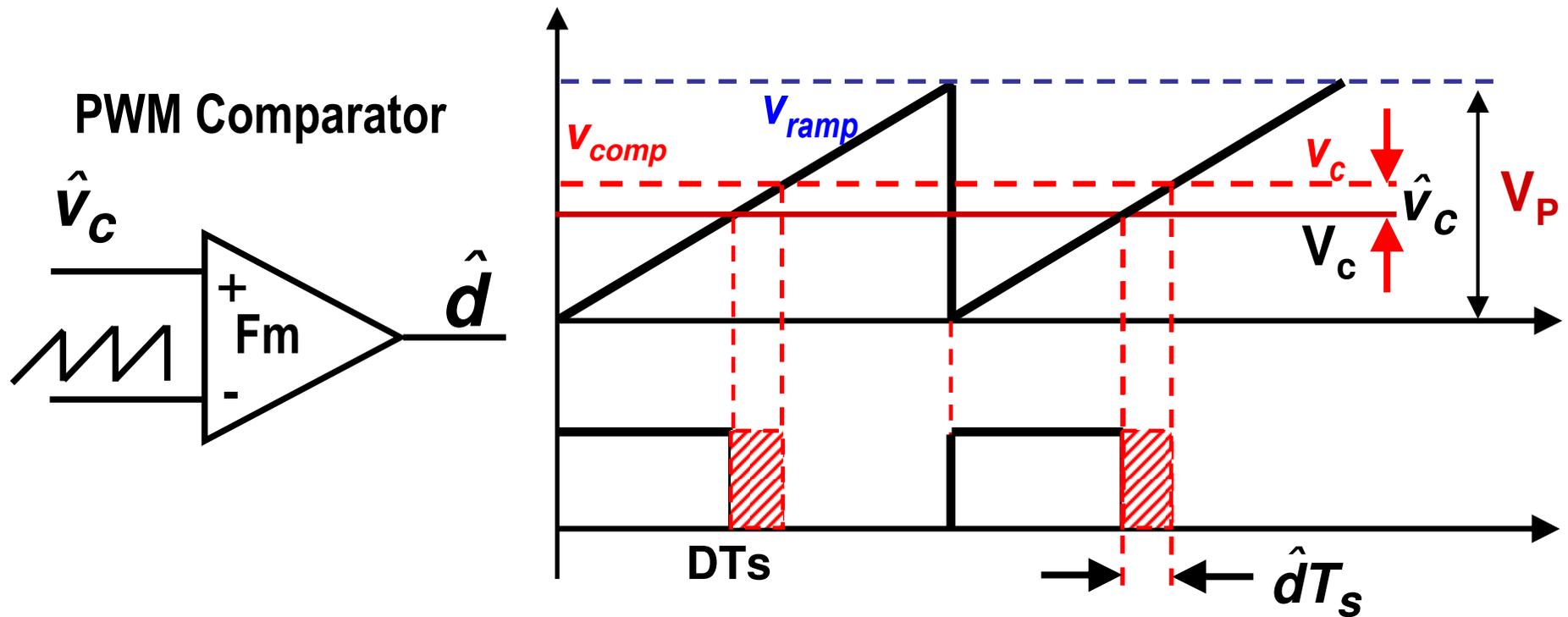
## Small Signal PWM Comparator Gain $F_m$



$$F_m = \frac{dd}{dv_c} = \frac{\hat{d}}{\hat{v}_c} = \frac{1}{V_P}$$




## Closed Loop Audio-Susceptibility (Line Trans. Response)

**Audio Susceptibility**  $\left. \frac{\hat{v}_o}{\hat{v}_{in}} \right|_{\hat{i}_o = 0}$

$$\hat{v}_o = G_v \hat{v}_{in} + G_d \hat{d}$$

$$\hat{d} = -F_m A \hat{v}_o$$
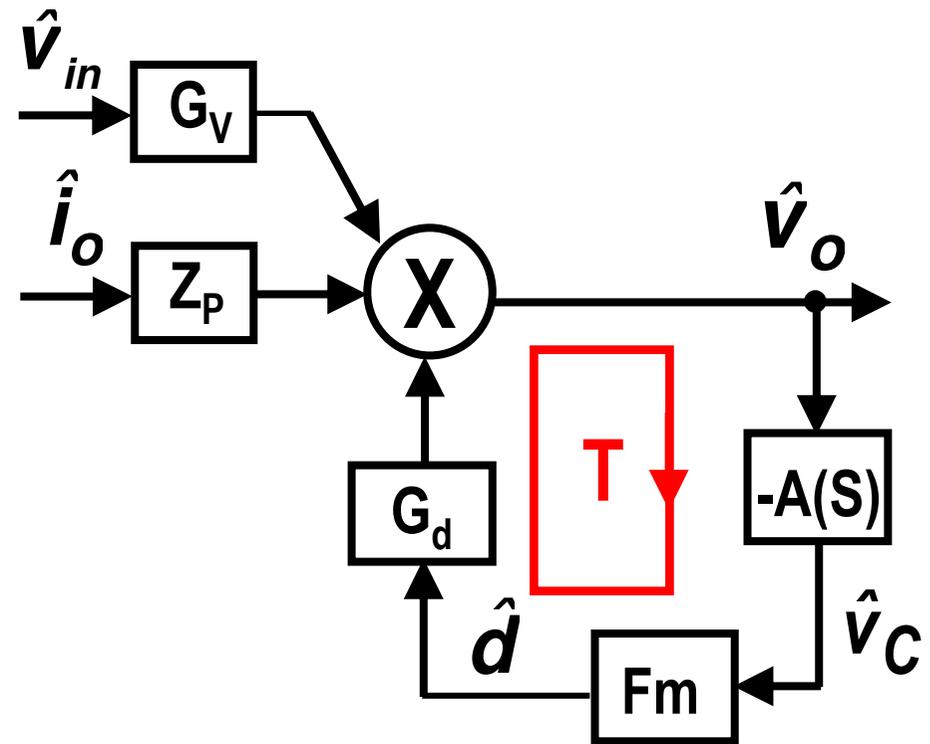
$$\frac{\hat{v}_o}{\hat{v}_{in}} = \frac{G_v}{1 + G_d F_m A} = \frac{G_v}{1 + T}$$



**Audio-Susceptibility Physical meaning: Line transient response**

Loop Gain:  $T = F_m G_d A$

- High loop gain T will improve the line transient response




## Closed Loop Output Impedance (Load Transient Response)

Closed Loop Output Impedance

$$\left. \frac{\hat{v}_o}{\hat{i}_o} \right|_{\hat{v}_{in} = 0}$$

$$\hat{v}_o = Z_p \hat{i}_o - G_d F_m A \hat{v}_o$$
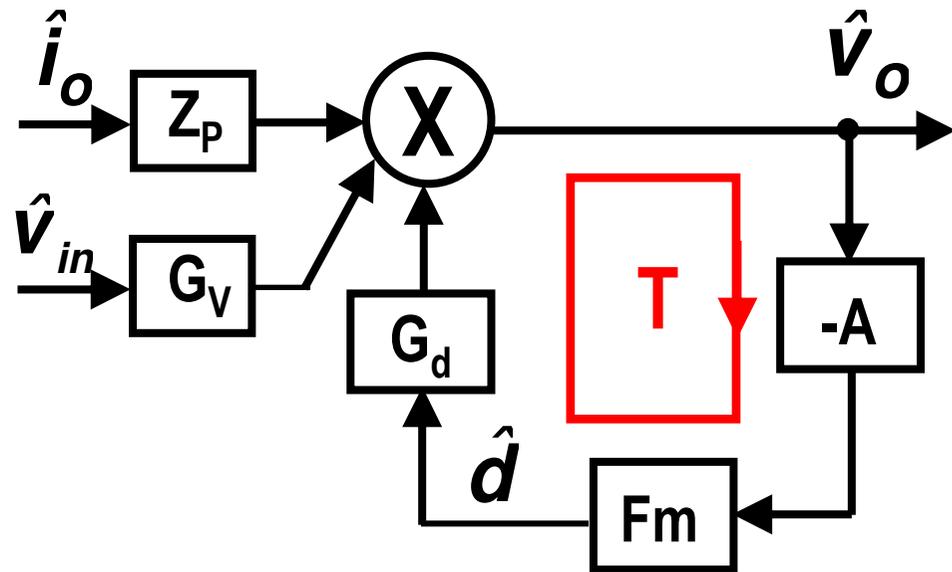
$$\frac{\hat{v}_o}{\hat{i}_o} = \frac{Z_p}{1 + G_d F_m A} = \frac{Z_p}{1 + T}$$



**Output Impedance Physical meaning: Load step transient response**

- The smaller the output impedance, the faster the transient response
- Higher loop gain is desired



# Loop Gain Analysis



## Loop Gain Provides:

- **System performance analysis: Transient response**
- **Stability analysis:**
  - **Absolute stability**
  - **Degree of stability**
- **Design insight**
- **Measurement verification**


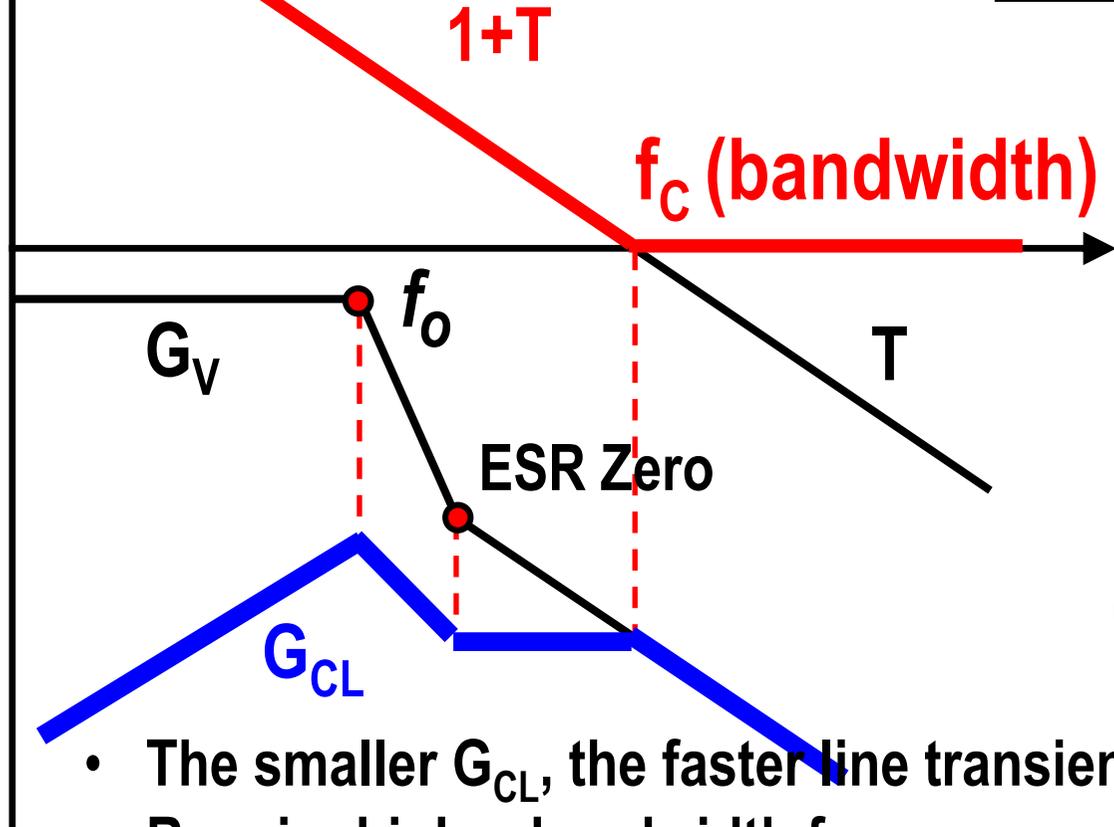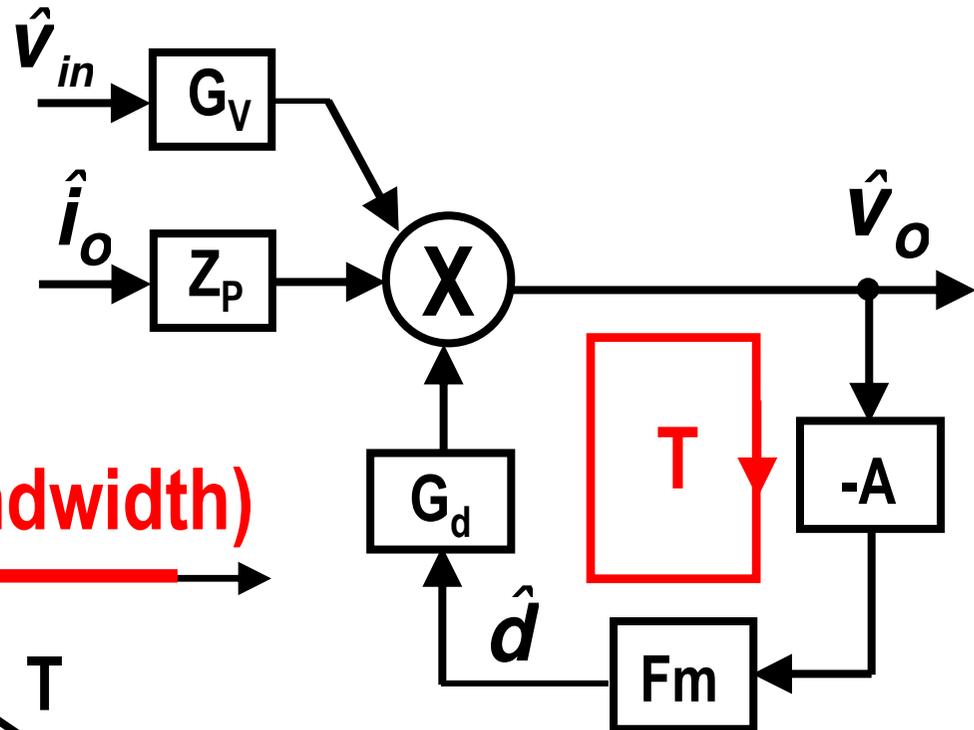
# Function of Loop Gain T: Closed-Loop Audio Susceptibility

$$G_V = \frac{\hat{V}_o}{\hat{V}_{in}} = D \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$





$$G_{CL} = \frac{\hat{V}_o}{\hat{V}_{in}} = \frac{G_V}{1+T}$$

- The smaller  $G_{CL}$ , the faster line transient response
- Require higher bandwidth  $f_c$


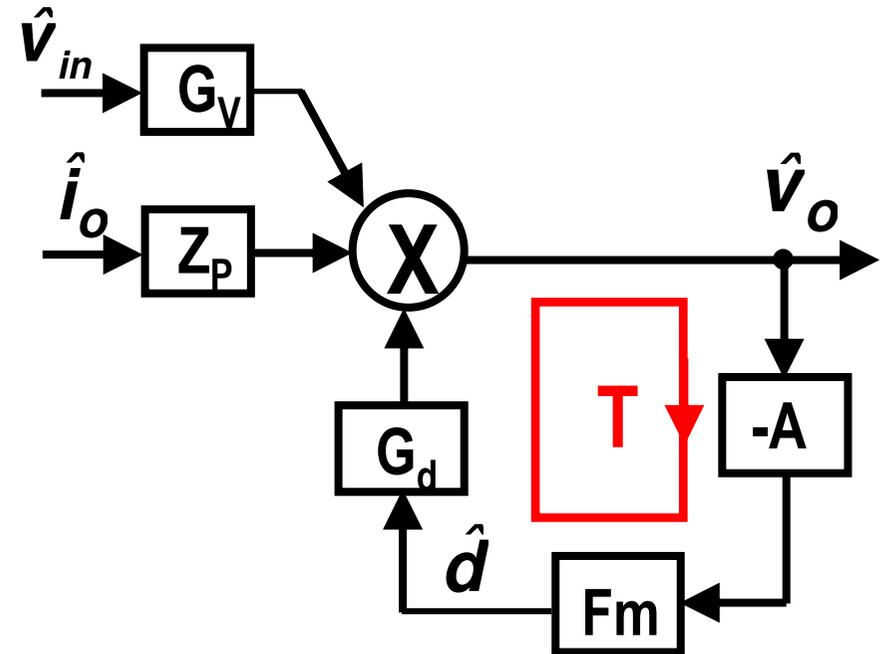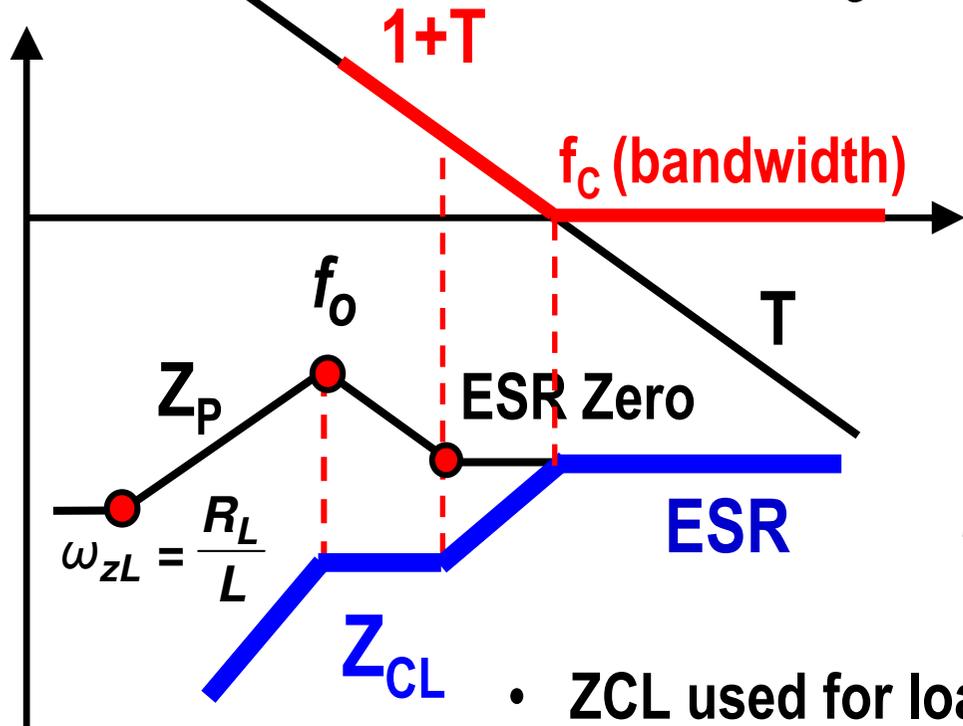
# Function of Loop Gain T: Closed-Loop Output Impedance

$$Z_p = \frac{\hat{v}_o}{\hat{i}_o} = R_L // R \cdot \frac{(1 + \frac{s}{\omega_z}) \cdot (1 + \frac{s}{\omega_{zL}})}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}}$$





$$Z_{CL} = \frac{\hat{v}_o}{\hat{i}_o} = \frac{Z_p}{1+T}$$

- ZCL used for load transient analysis
- The smaller  $Z_{CL}$ , the faster load transient response
- The minimum high frequency  $Z_o$  is ESR



## Closed-Loop Output Impedance

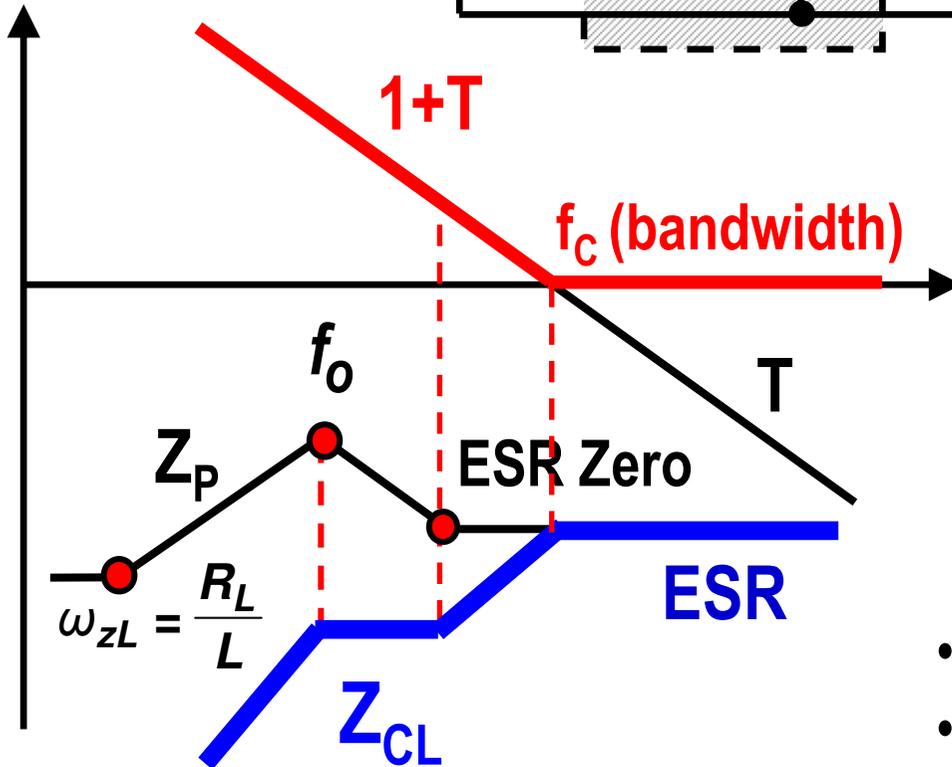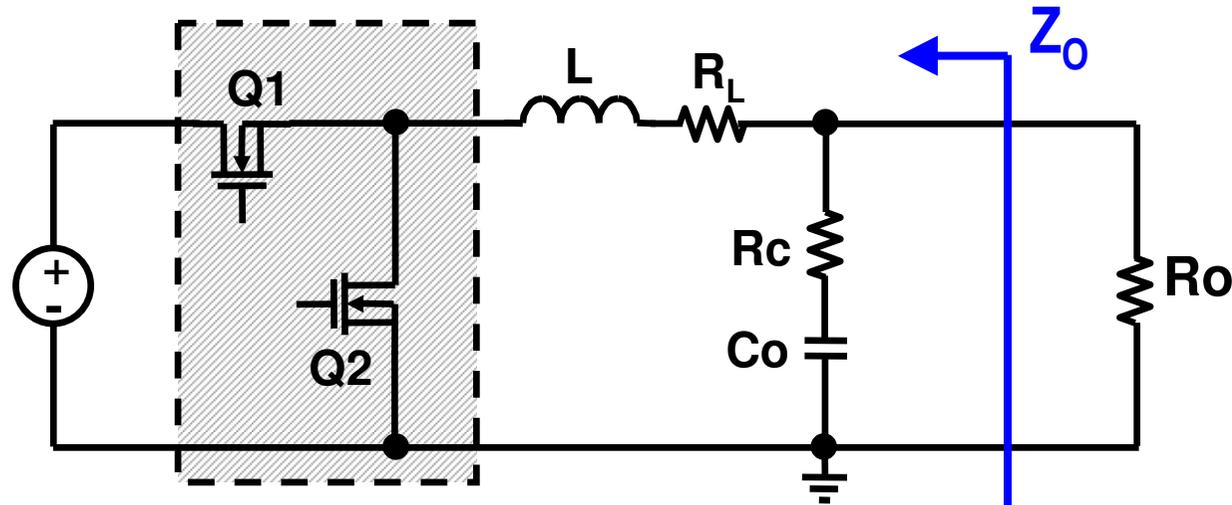

$$Z_{CL} = \frac{\hat{v}_o}{\hat{i}_o} = \frac{Z_p}{1+T}$$


When  $f \uparrow$

- C shorts and L open
- Minimum  $Z_o$ : ESR
- Smaller ESR, better load transient
- Higher T, better load transient


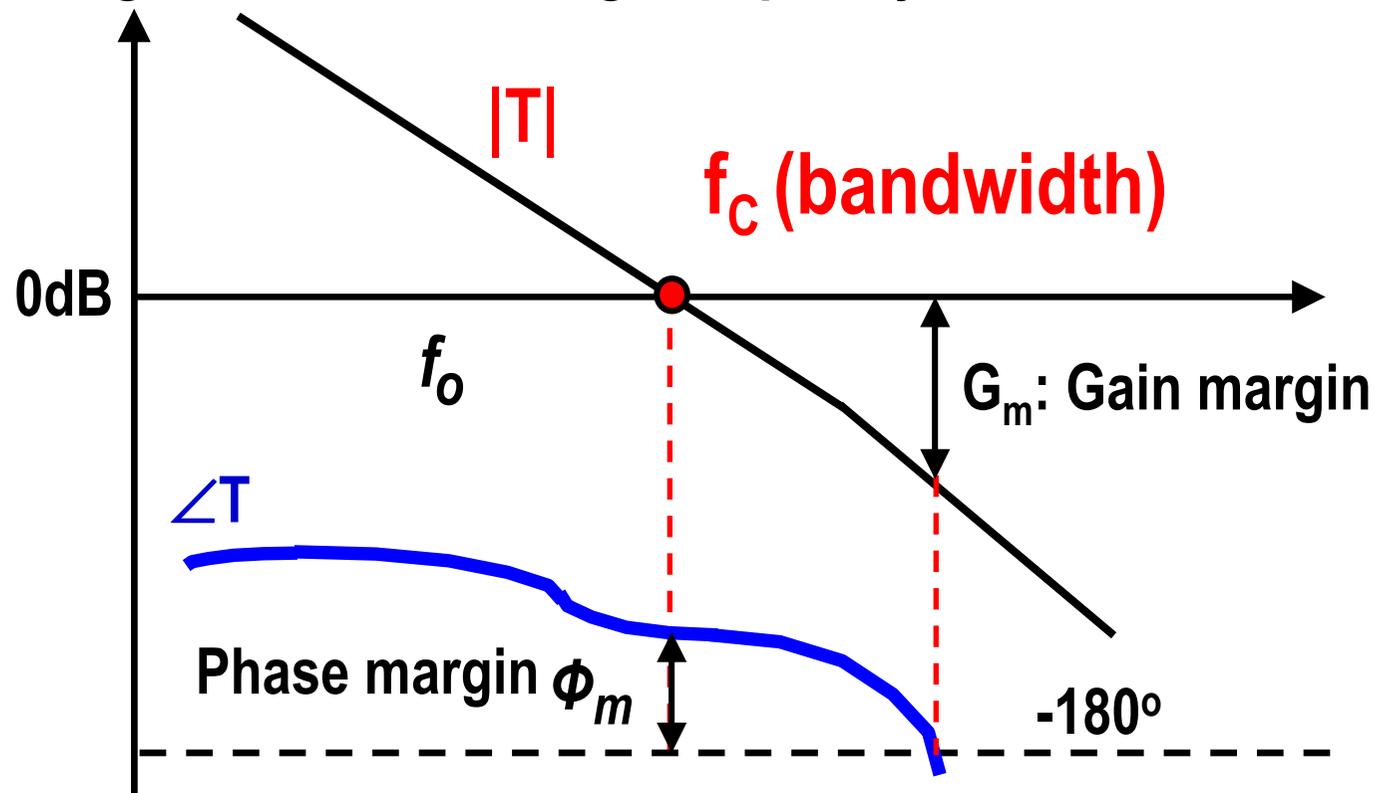
# Ideal Loop Gain Characteristics


- High DC gain (Low frequency) for small DC error
- Wide bandwidth for fast transient response
- -20dB/dec slope near cross-over frequency for higher phase margin
- High attenuation at high frequency for noise reduction




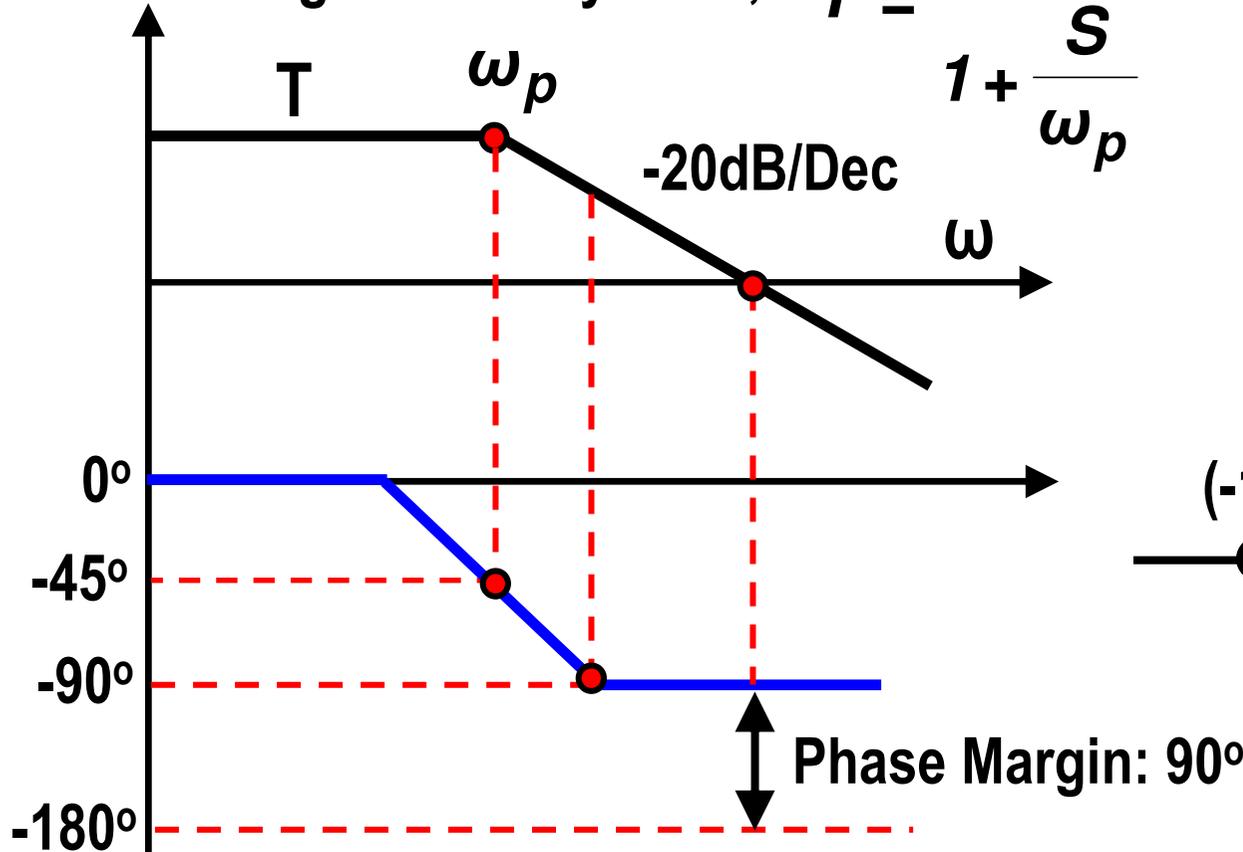
# Examples of Loop Gain T

• Single Order System ;  $T = \frac{G_m}{1 + \frac{S}{\omega_p}}$




- Always stable
- 90° phase margin

$S=j\omega$

Definition

$Magnitude = 20 \log|T|$

$Phase = Angle(T)$

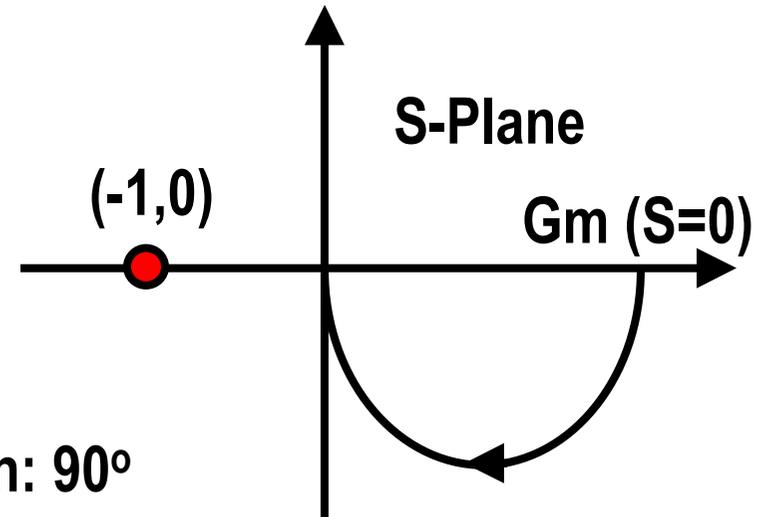

$T=1/(1 + j) @ S=j\omega_p$


Magnitude =  $-20 \log\sqrt{2}$

Phase = -45 degree



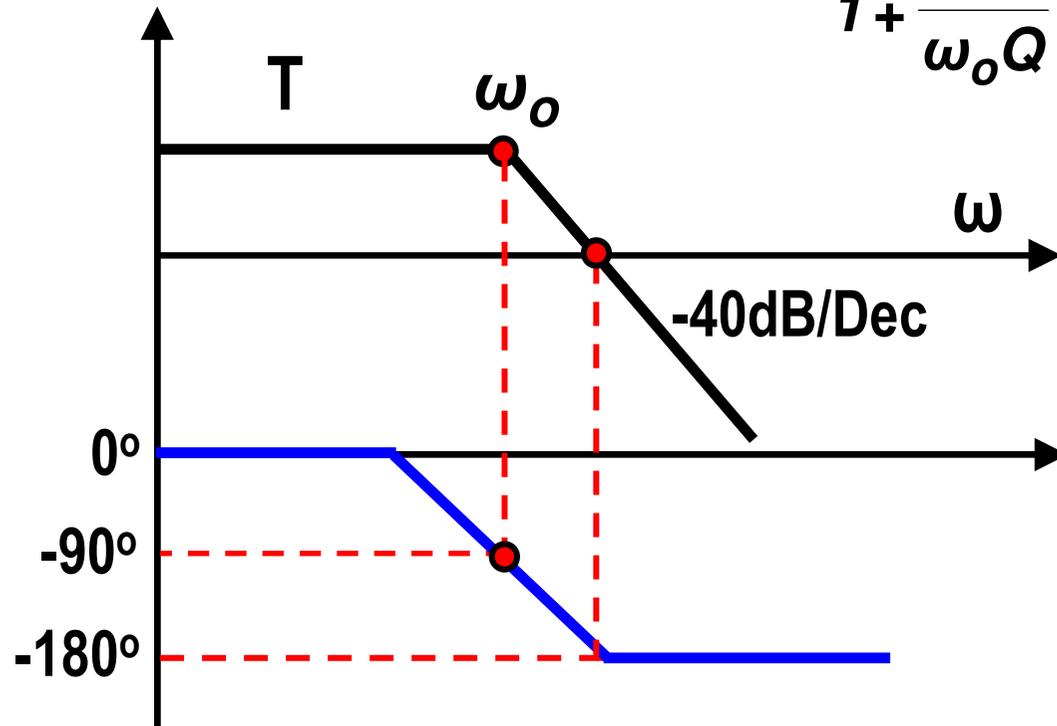
## Examples of Loop Gain T

- 2nd Order System ;  $T = \frac{G_m}{1 + \frac{S}{\omega_o Q} + \frac{S^2}{\omega_o^2}}$



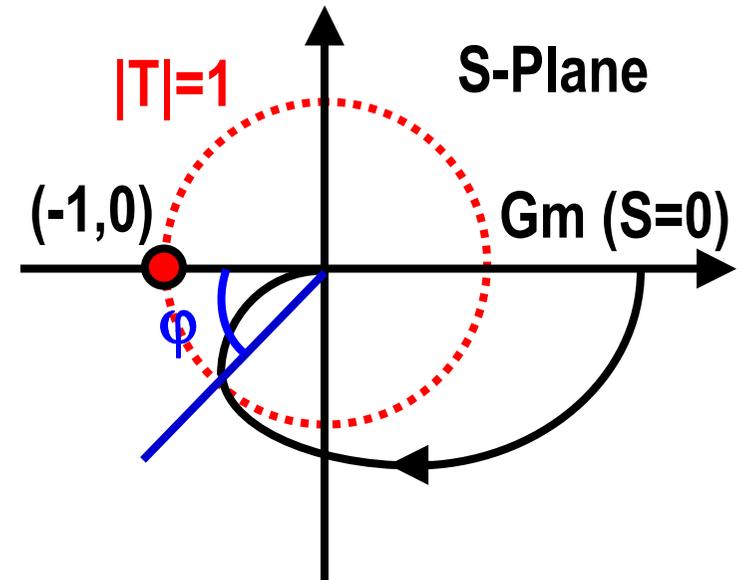- Stable
- $\phi$  phase margin: may be very small
- Gain margin: infinite (theoretical)



$$S = j\omega_o$$

$$T = \frac{QG_m}{j}$$



## Basic Pole and Zero Characteristics


### One Pole

- 45 degree at the Pole (frequency  $f_p$ )
- Total of 90° phase delay after  $>10 f_p$
- -20 db/dec
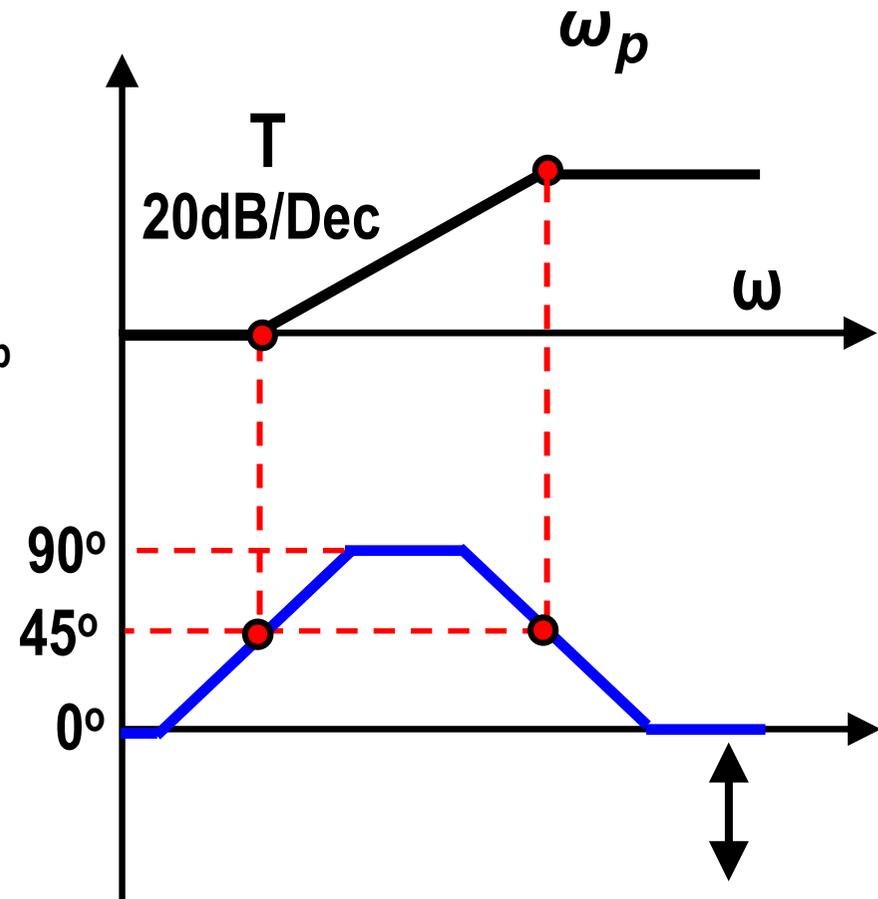
### One Zero


- 45° phase lead at the zero
- Total of 90° phase lead after  $>10 f_z$
- +20db/dec

$$G(S) = \frac{1 + \frac{S}{10^3}}{1 + \frac{S}{10^5}}$$





## DC Loop Gain

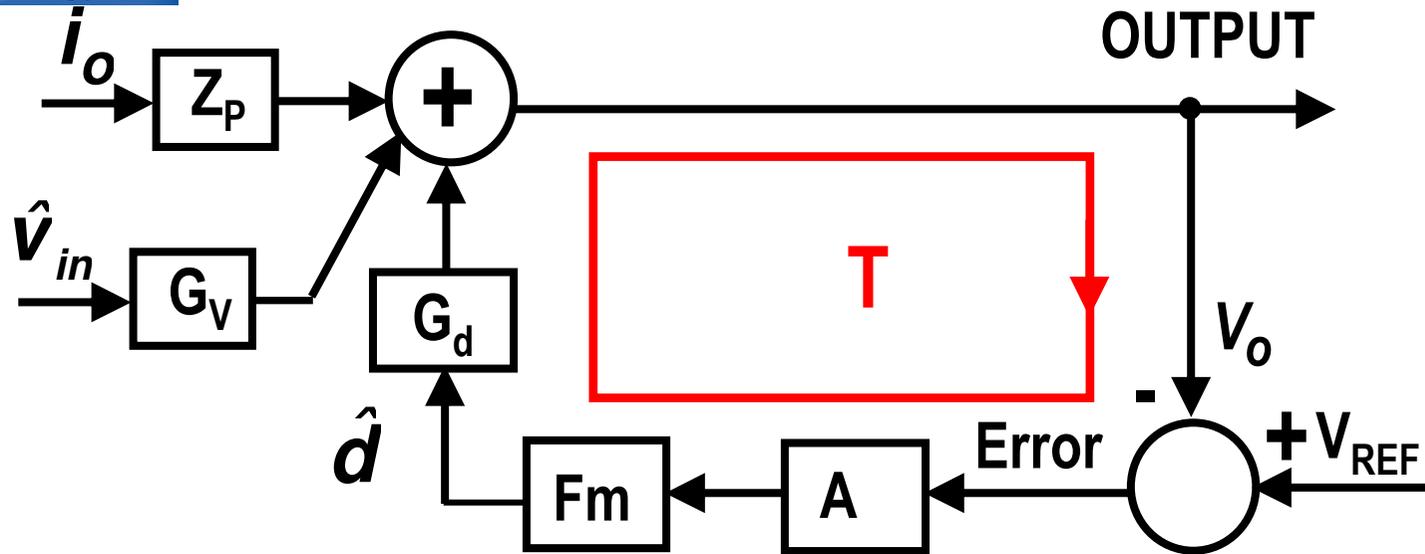

$$\hat{v}_{in} = \hat{i}_o = 0$$

$$DC \text{ Error} = V_{REF} - V_o = \frac{V_o}{AF_m G_d} \Big|_{s=0} = \frac{V_o}{T(\text{DC loop gain})}$$

- The higher DC loop gain, the smaller the DC steady-state error
- 40dB DC loop gain, 1% error



# Compensator Design Considerations




## Objectives of Loop Gain Design

### Objective:

- To shape the loop gain  $T$  for achieving
  - High DC gain at low frequency
  - >40 degree phase margin
  - > 10 dB gain margin
  - High bandwidth for fast transient response


$$T = G_d \cdot A(S) \cdot F_m$$

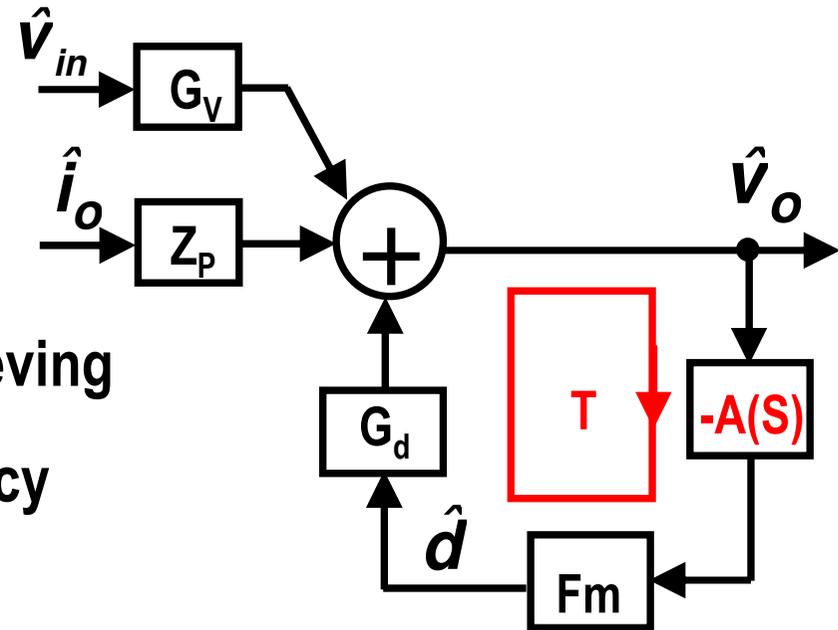


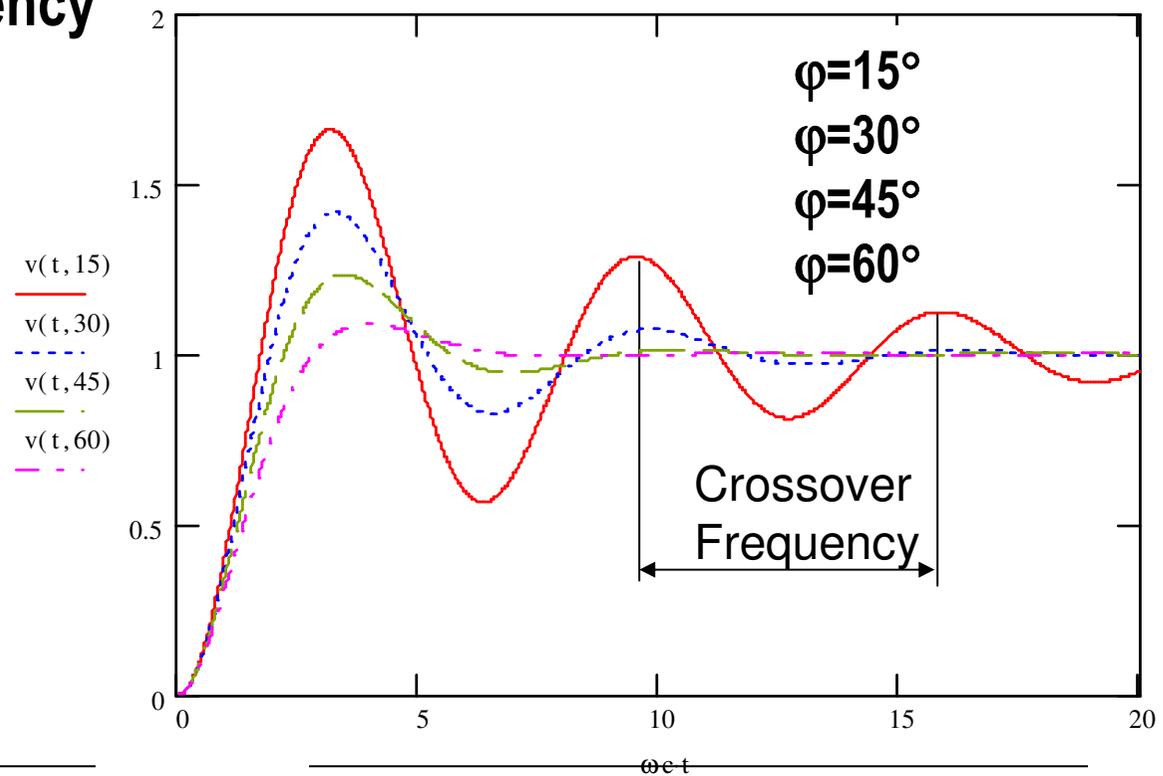
# Load Transient Step Response vs Phase Margin

- The amount of ringing determines the phase margin
  - 45° phase margin is sufficient
- The crossover frequency is equal to the ringing frequency
  - Crossover frequency should be 1/5 or 1/10 of the converter switching frequency





# Compensator Design Considerations (Voltage mode)


## Compensator: Constant Gain

$$T = G_d A F_m, \quad A(s) = K_c;$$

$$T = F_m V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \cdot K_c$$

$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad Q \approx \frac{R}{\sqrt{\frac{L}{C}}}$$

## Buck Converter

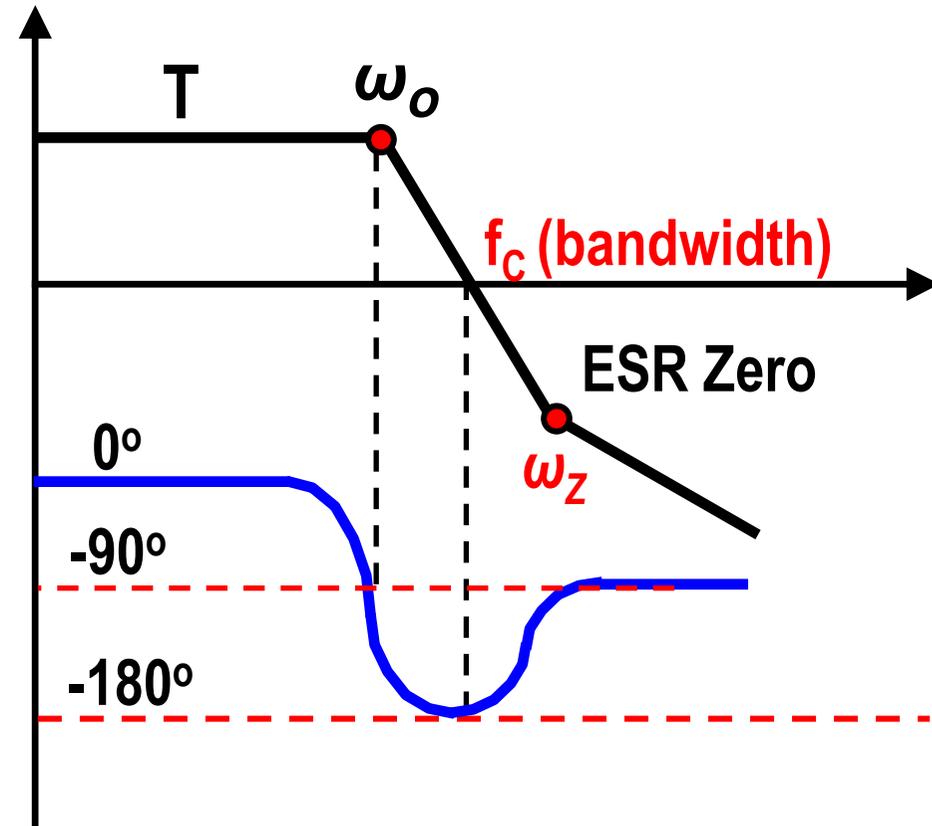

- Low DC gain, need an integrator
- Almost  $0^\circ$  phase margin if  $\omega_z > 3 \omega_o$
- Stable if ESR zero  $\omega_z < 3 \omega_o$




## Compensator Design Considerations (cont.)

### Compensator: Integrator

$$T = G_d A F_m, \quad A(s) = \frac{K_c}{s};$$

$$T = F_m V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \cdot \frac{K_c}{s}$$
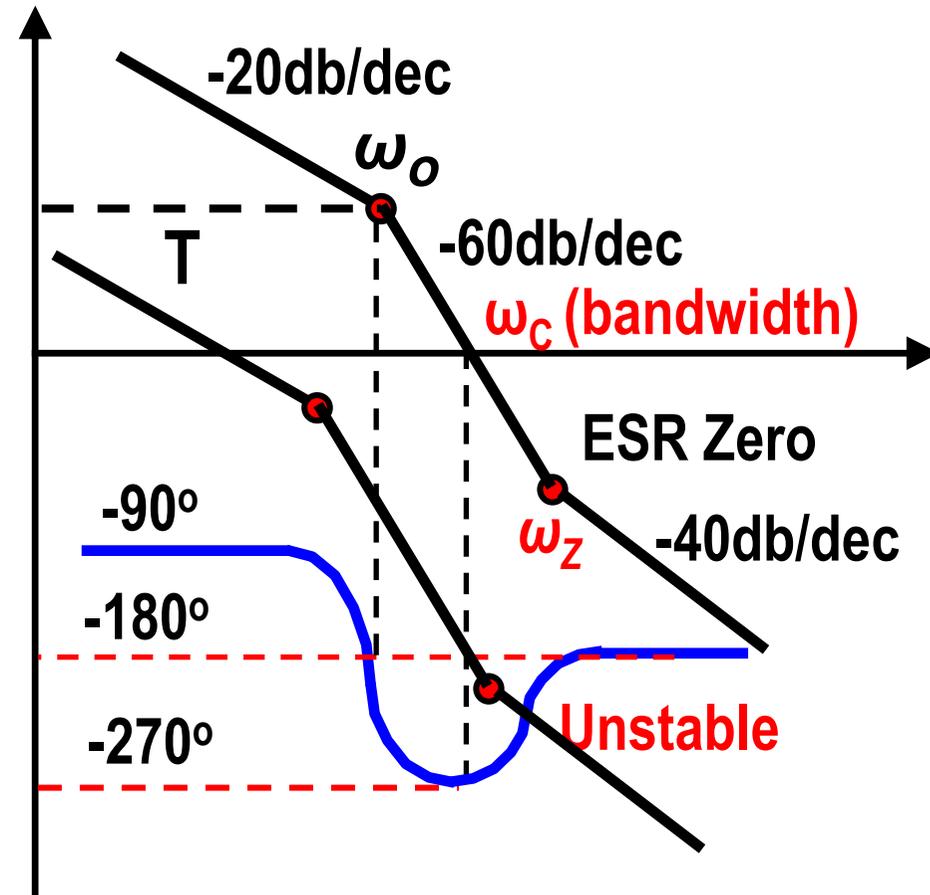
$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad Q \approx \frac{R}{\sqrt{\frac{L}{C}}}$$



- Integrator: 90° delay; Double pole: 180° delay
- low bandwidth or unstable
- Need to introduce two zeros before cross-over frequency  $\omega_c$




# Type III Compensator Characteristics

$$T_{OPEN} = G_d F_m$$

$$T_{CLOSE} = G_d F_m A(s)$$

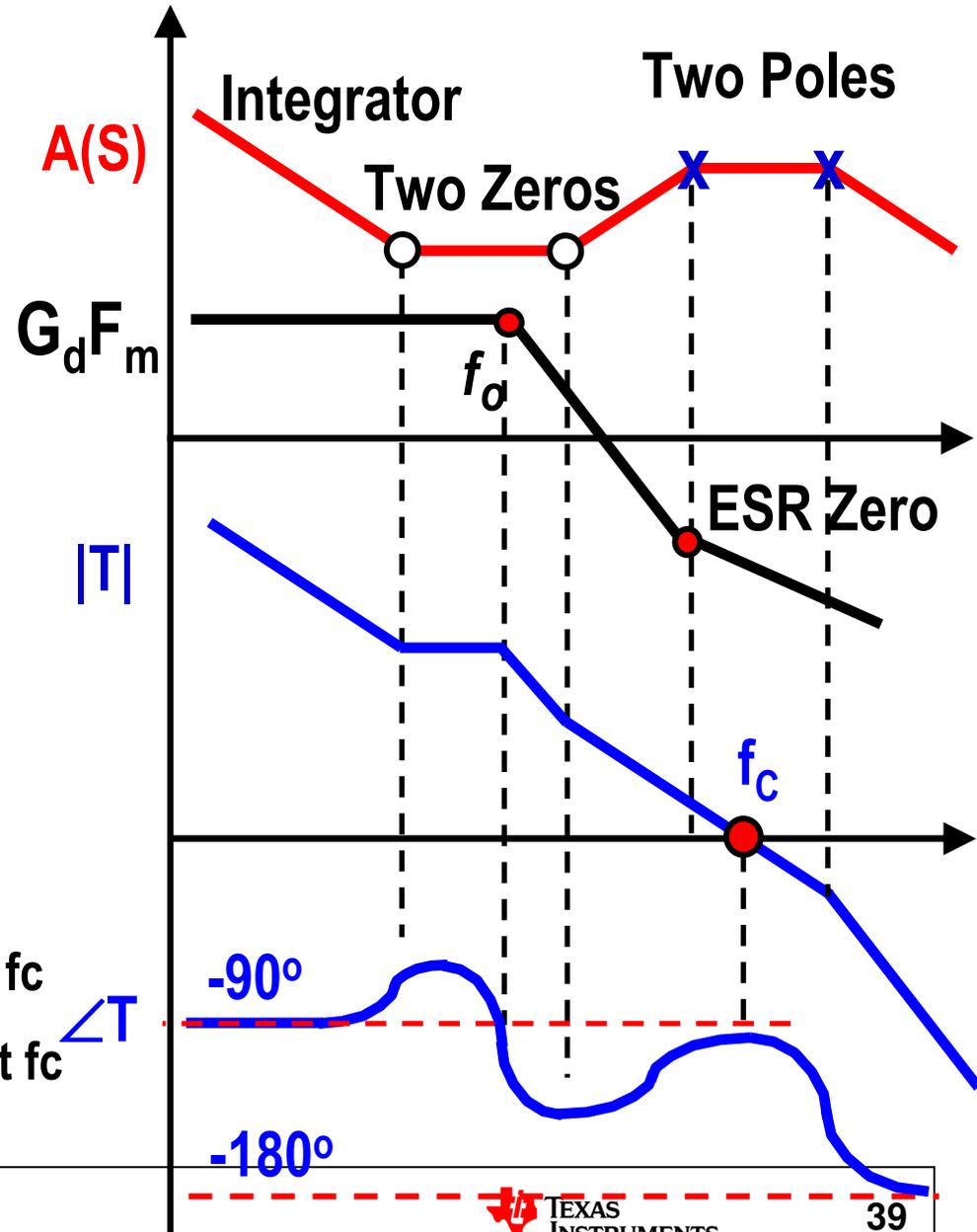- Design based on OPEN LOOP GAIN
- An integrator for high DC gain
- Place two zeros around  $f_o$  for compensating phase delay due to the integrator and double poles
- Two high frequency poles
  - to cancel ESR zero
  - to attenuate high frequency noise
  - to ensure the gain decreasing after  $f_c$
  - to ensure the phase lag minimum at  $f_c$






# Type III Loop compensator Circuit

$$A(S) = \frac{\hat{V}_c}{\hat{V}_o} = -\frac{Z_F}{Z_I},$$

$$Z_F = \frac{1}{SC_3} \parallel \left( R_2 + \frac{1}{SC_1} \right);$$
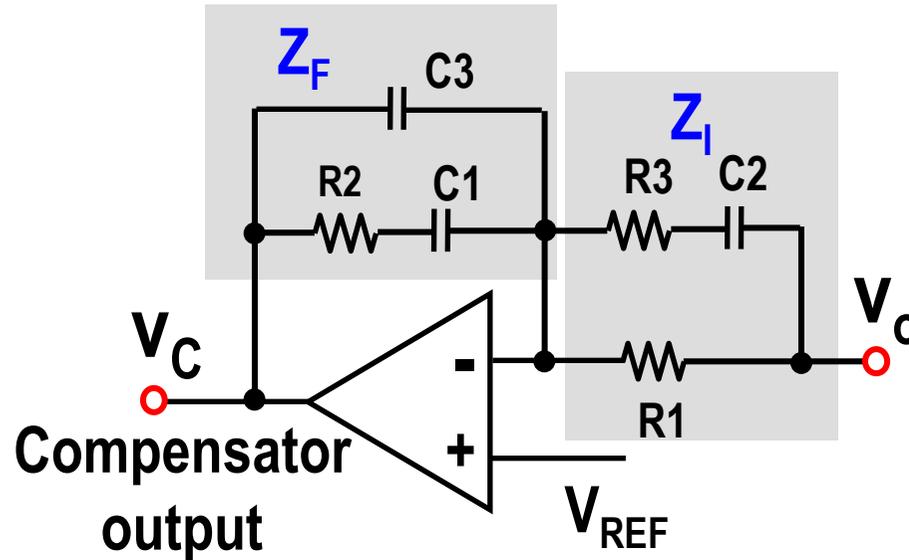
$$Z_I = R_1 \parallel \left( R_3 + \frac{1}{SC_2} \right)$$



$$A(S) = -\frac{K_I}{S} \frac{\left(1 + \frac{S}{\omega_{z1}}\right) \cdot \left(1 + \frac{S}{\omega_{z2}}\right)}{\left(1 + \frac{S}{\omega_{p1}}\right) \cdot \left(1 + \frac{S}{\omega_{p2}}\right)}$$

$$K_I = \frac{1}{R_1(C_1 + C_3)},$$

$$\omega_{z1} = \frac{1}{R_2 C_1}, \quad \omega_{z2} = \frac{1}{C_2(R_1 + R_3)}$$

$$\omega_{p1} = \frac{1}{R_3 C_2}, \quad \omega_{p2} = \frac{1}{R_2 \frac{C_1 C_3}{C_1 + C_3}}$$

- **Zeros:**
  1. R2, C1;
  2. R1+R3, C2
- **Poles:**
  1. DC
  2. R2, C3 if C1 >> C3
  3. R3, C2



# Loop Gain Design (voltage mode)

$$T = G_d A F_m$$


$$T = F_m V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \frac{K_c (1 + \frac{s}{\omega_{z1}}) \cdot (1 + \frac{s}{\omega_{z2}})}{s \cdot (1 + \frac{s}{\omega_{p1}}) \cdot (1 + \frac{s}{\omega_{p2}})}$$

$G_d(s)$

$A(s)$ : Compensator

$$\omega_o \approx \frac{1}{\sqrt{LC}}, \quad \omega_z = \frac{1}{R_c C}, \quad Q \approx \frac{R}{\sqrt{\frac{L}{C}}}$$

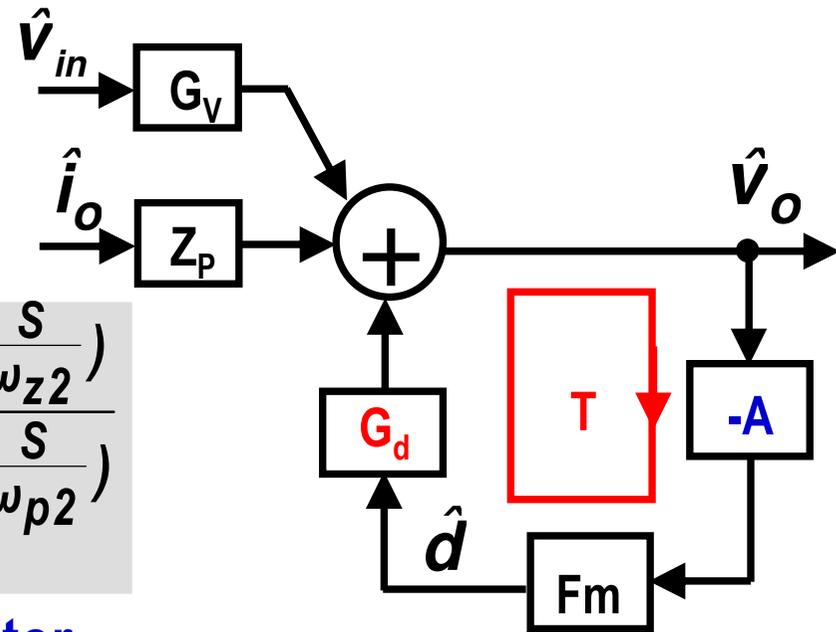- Type III compensator: two zeros ( $\omega_{z1}, \omega_{z2}$ ) and three poles ( $0, \omega_{p1}, \omega_{p2}$ )
- Loop gain is proportional to the input voltage.  
Need input voltage feed-forward function





## Objective of Compensator Design


$$T = G_d A F_m$$

$$T = F_m V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \frac{K_c (1 + \frac{s}{\omega_{z1}}) \cdot (1 + \frac{s}{\omega_{z2}})}{s \cdot (1 + \frac{s}{\omega_{p1}}) \cdot (1 + \frac{s}{\omega_{p2}})}$$

- Objective is to design a compensator,  $K_c$ ,  $\omega_{z1}$ ,  $\omega_{z2}$ ,  $\omega_{p1}$ ,  $\omega_{p2}$ , to **SHAPE** the loop gain  $T$  for stability and optimum performance for given power stage parameters,  $\omega_z$ ,  $\omega_o$ ,  $Q$ ,  $V_{IN}$ , and PWM gain  $F_m$ .



# Loop Gain Design Procedure (Case 1)

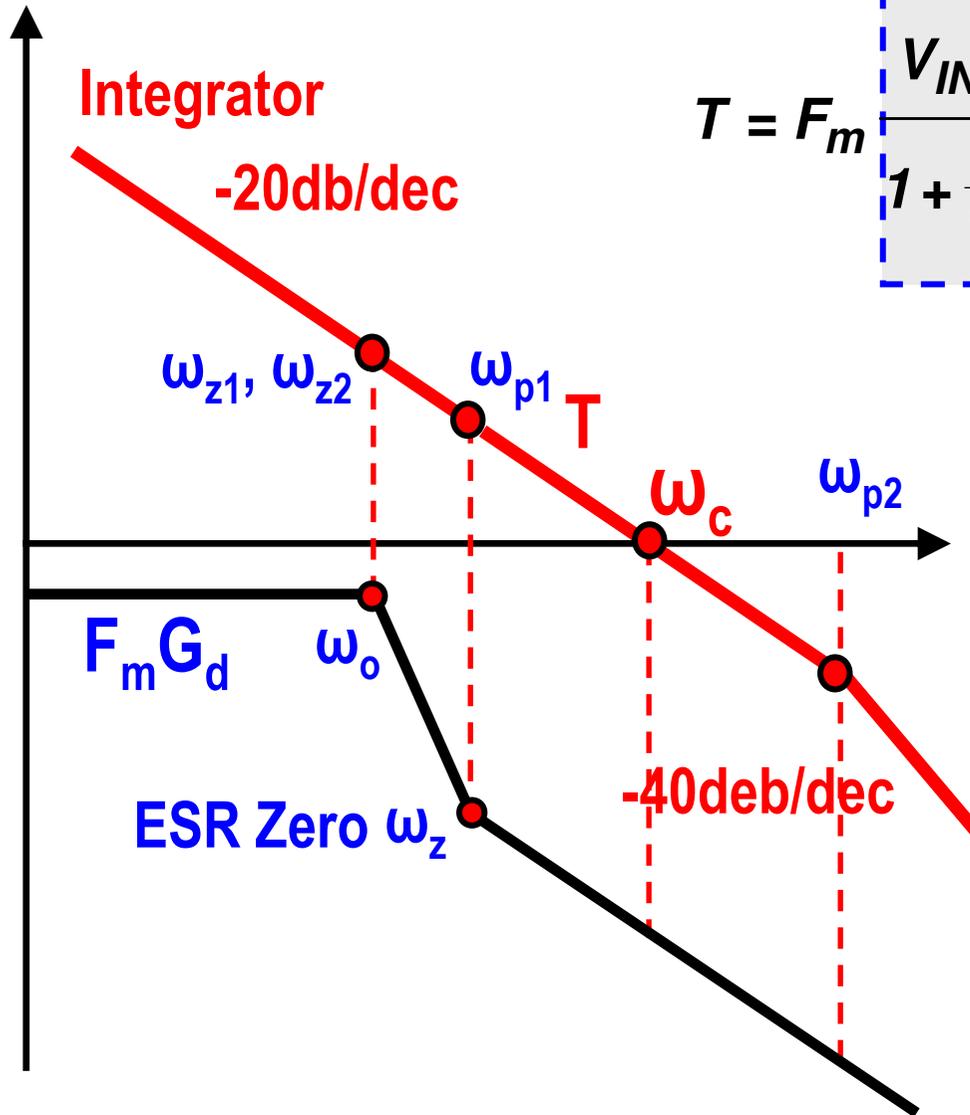

$$T = F_m \frac{V_{IN} \left(1 + \frac{S}{\omega_z}\right)}{1 + \frac{S}{Q\omega_o} + \frac{S^2}{\omega_o^2}} \frac{K_c \left(1 + \frac{S}{\omega_{z1}}\right) \cdot \left(1 + \frac{S}{\omega_{z2}}\right)}{S \cdot \left(1 + \frac{S}{\omega_{p1}}\right) \cdot \left(1 + \frac{S}{\omega_{p2}}\right)}$$


$G_d(S)$ 
 $A(S)$

- Bandwidth  $f_c = (1/5 - 1/10) f_s$
- $\omega_{z1}, \omega_{z2}$  near  $\omega_o$
- $\omega_{p1}$  cancel ESR zero  $\omega_z$
- $\omega_{p2} = 10 \omega_c$
- Determine  $K_c$
- Select compensator R's and C's


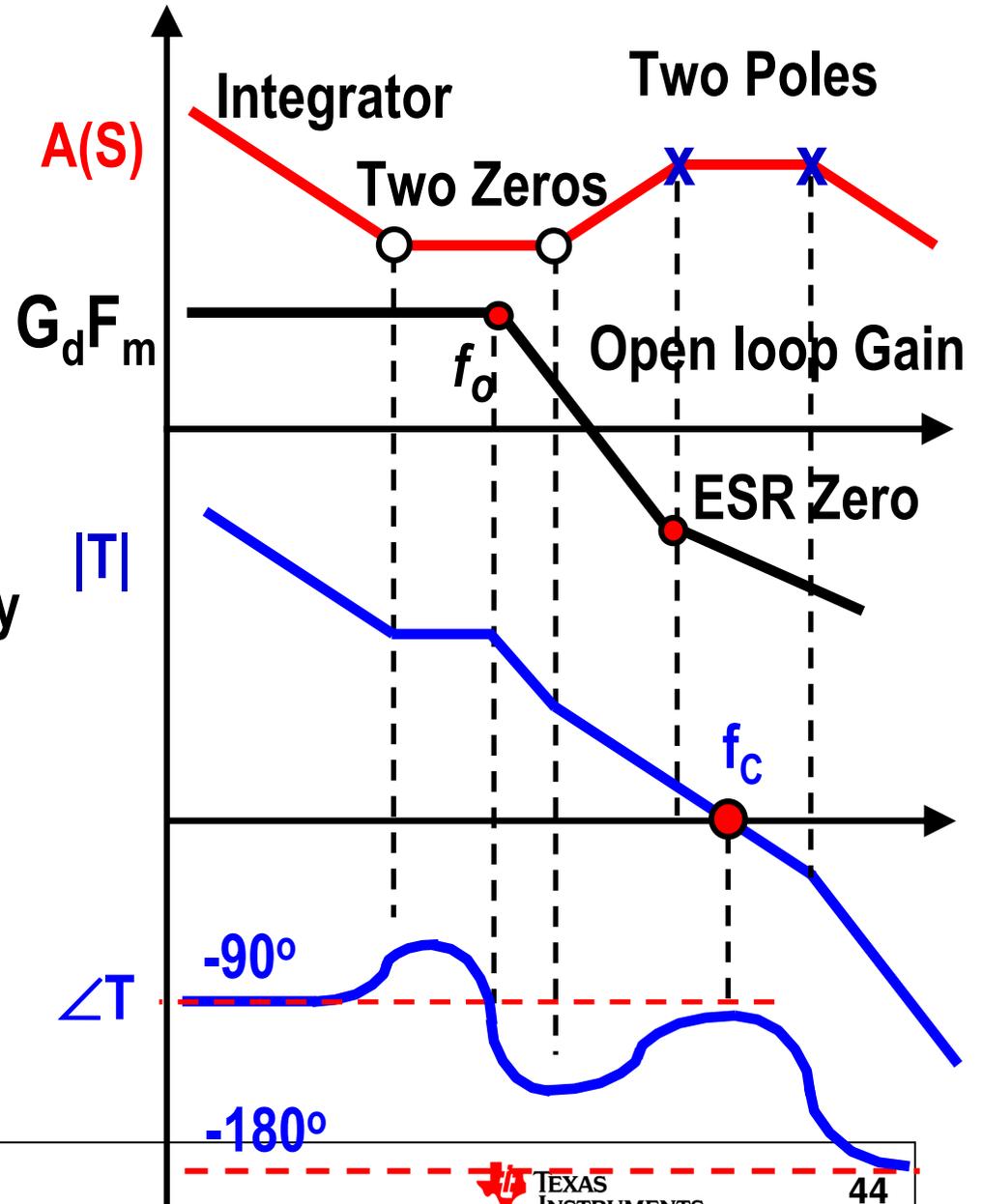
## Type III Compensator Design (Case II)

- An integrator for high DC gain
- Place two zeros around  $f_o$
- Two high frequency poles to cancel ESR zero and increase gain attenuation at high frequency






# Type II Compensator
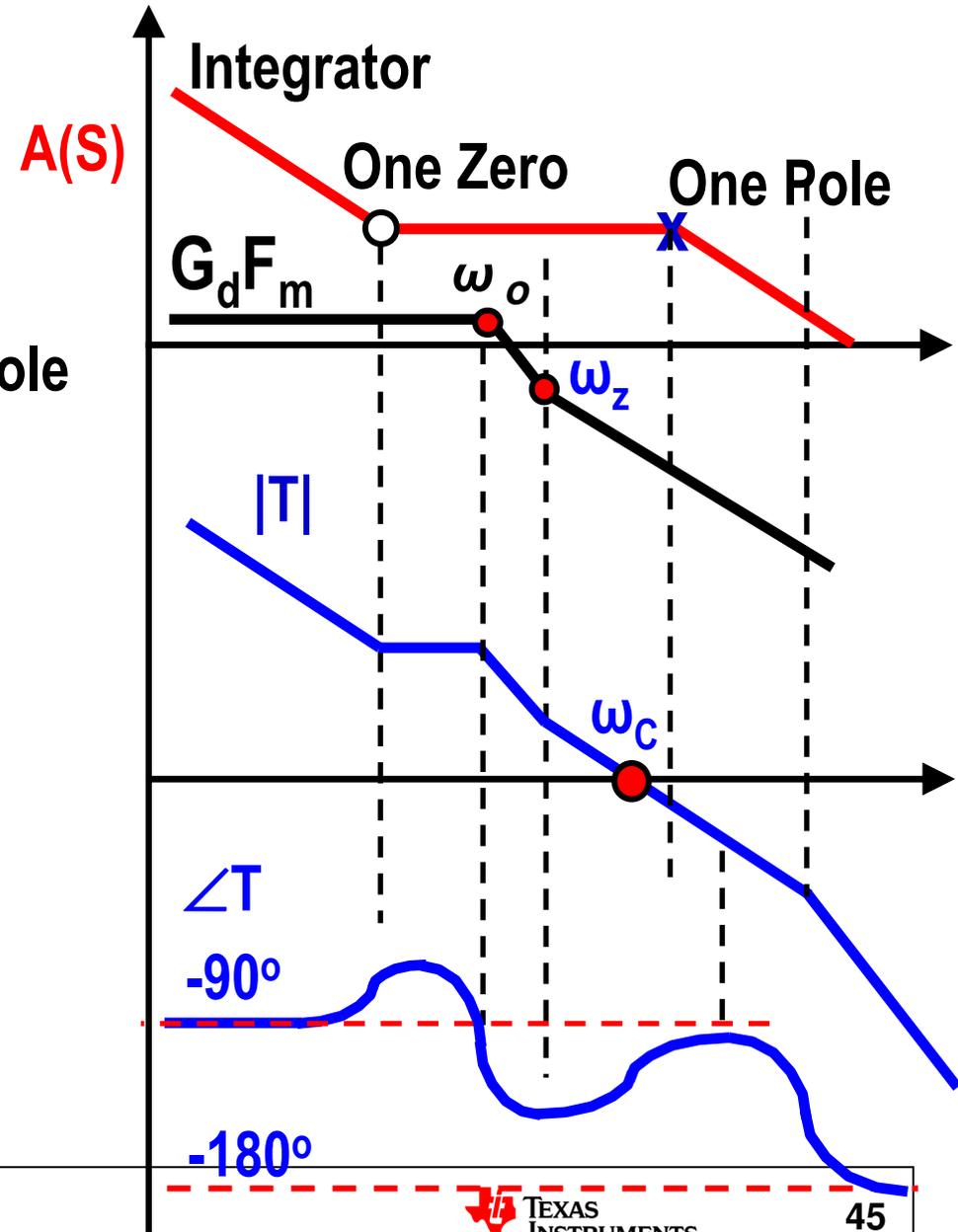
## Type II Compensator

- One zero and two poles
- if ESR zero is close to double pole  $\omega_z < 3 \omega_o$


$$A(S) = \frac{K_I}{S} \cdot \frac{1 + \frac{S}{\omega_{z1}}}{1 + \frac{S}{\omega_{p1}}}$$




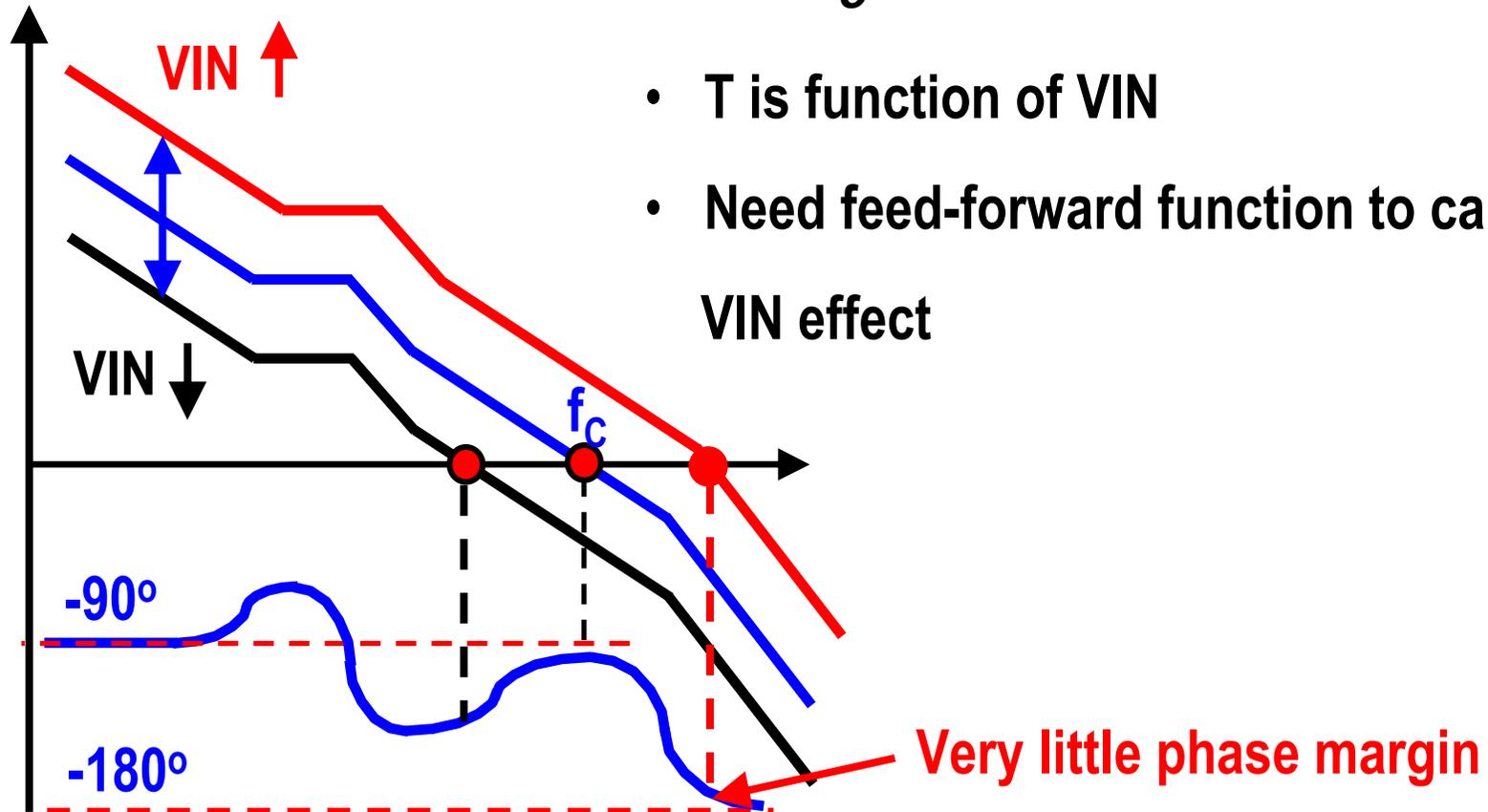
# Loop Gain T function of Input Voltage

$$T = F_m \frac{V_{IN} \left(1 + \frac{s}{\omega_z}\right) K_c \left(1 + \frac{s}{\omega_{z1}}\right) \cdot \left(1 + \frac{s}{\omega_{z2}}\right)}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2} S \cdot \left(1 + \frac{s}{\omega_{p1}}\right) \cdot \left(1 + \frac{s}{\omega_{p2}}\right)}$$



- T is function of VIN
- Need feed-forward function to cancel



# Comparator Gain with Feed-Forward Function

**Feed-Forward:**

**PWM ramp is function of the input voltage**



$$\frac{d}{V_{comp}} = \frac{1}{V_P}$$



$$F_m = \frac{dd}{dv_{comp}} = \frac{\hat{d}}{\hat{v}_{comp}} = \frac{1}{V_P}$$

$$V_P = K V_{IN} \quad F_m = \frac{1}{K V_{IN}}$$

**PWM Comparator**

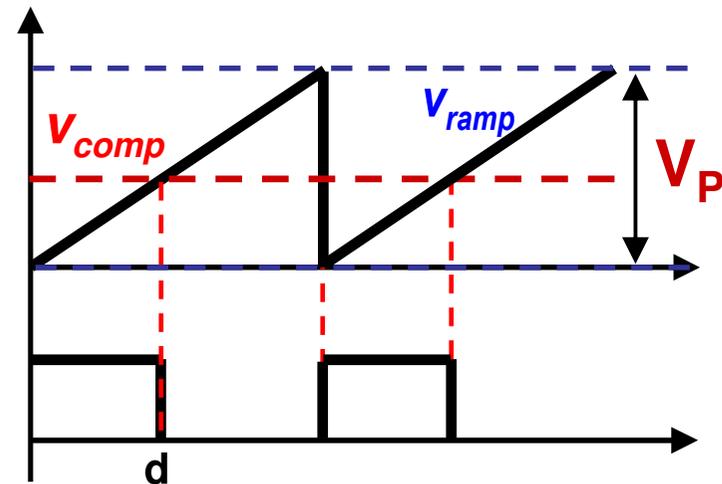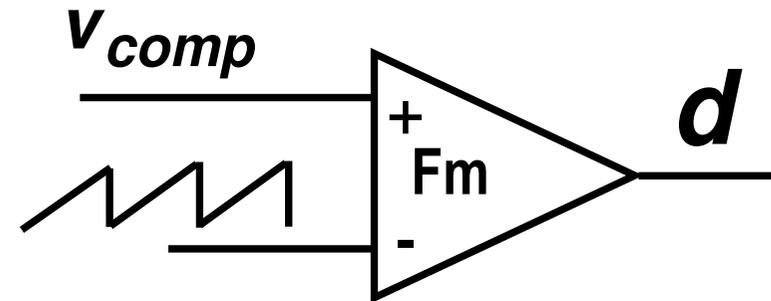



## Loop Gain with Feed-Forward Function

$$T = G_d A F_m$$

$$T = F_m \cdot V_{IN} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \frac{K_c (1 + \frac{s}{\omega_{z1}}) \cdot (1 + \frac{s}{\omega_{z2}})}{s \cdot (1 + \frac{s}{\omega_{p1}}) \cdot (1 + \frac{s}{\omega_{p2}})}$$


$$F_m = \frac{1}{KV_{IN}}$$

$$T = \frac{1}{KV_{IN}} \cancel{V_{IN}} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}} \frac{K_c (1 + \frac{s}{\omega_{z1}}) \cdot (1 + \frac{s}{\omega_{z2}})}{s \cdot (1 + \frac{s}{\omega_{p1}}) \cdot (1 + \frac{s}{\omega_{p2}})}$$

- Loop Gain is **INDEPENDENT** of input voltage.
- Fast line step transient response, Only depends on conversion speed of  $V_{ramp} = f(V_{IN})$



# How to Measure the Loop Gain

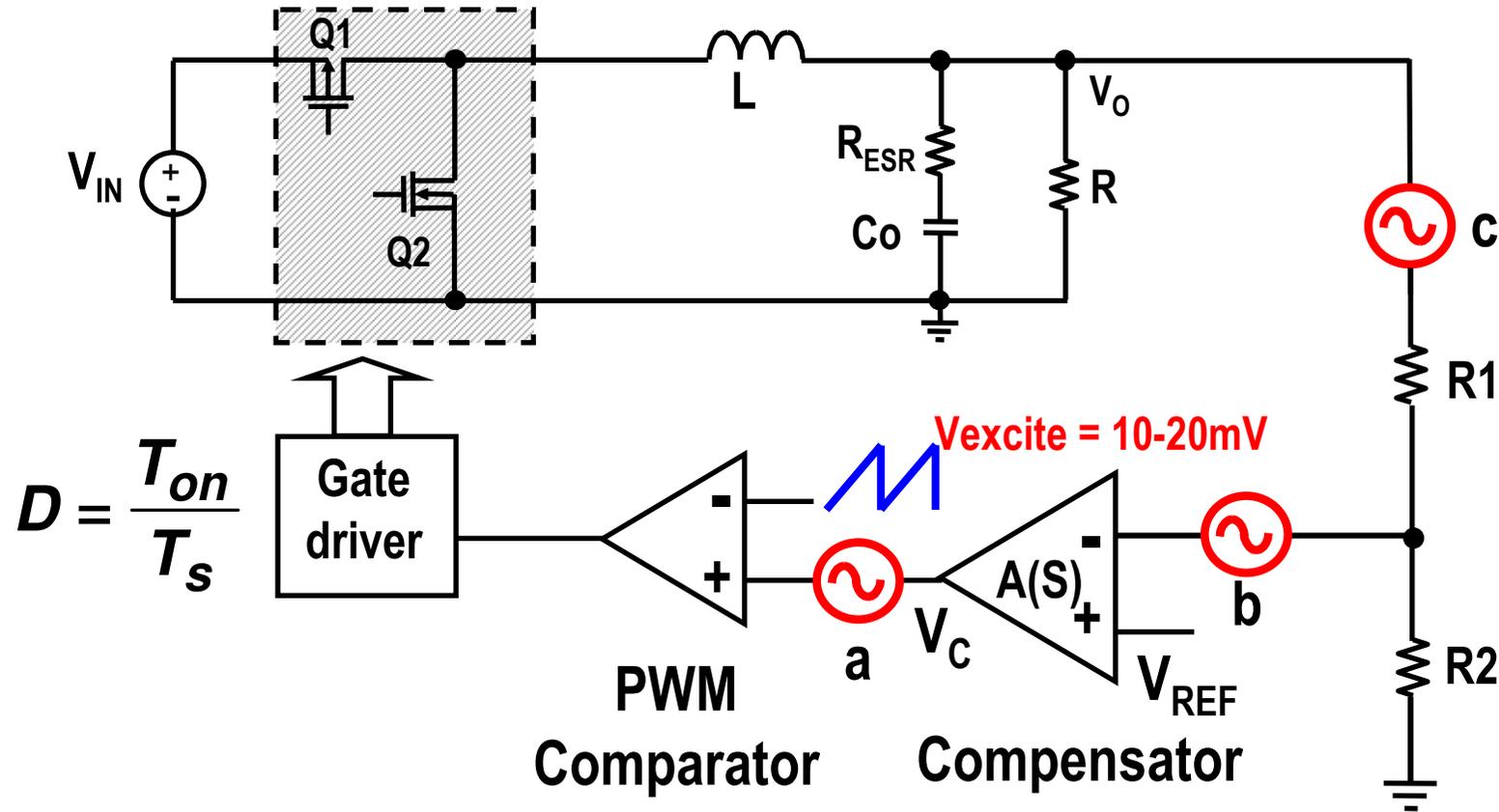

- Network Analyzer
- AP200
- a and b: 20-50mV perturbation; c: depends on output voltage



# Modeling, Simulation and Test Example

## TPS40200

- Voltage mode PWM controller
- Input Voltage range: 4.5V to 50V
- Input Voltage Feed Forward function


PWM ramp voltage =  $V_{IN}/10$

- Programmable switching frequency
- Vout: 0.7V to 90% of  $V_{IN}$

$V_{IN}=20V$ ,  $V_{OUT}= 5V$ ,  $f_s = 300kHz$ ,  $L=47\mu H$ ,  $C_o=22\mu F/10m\Omega$



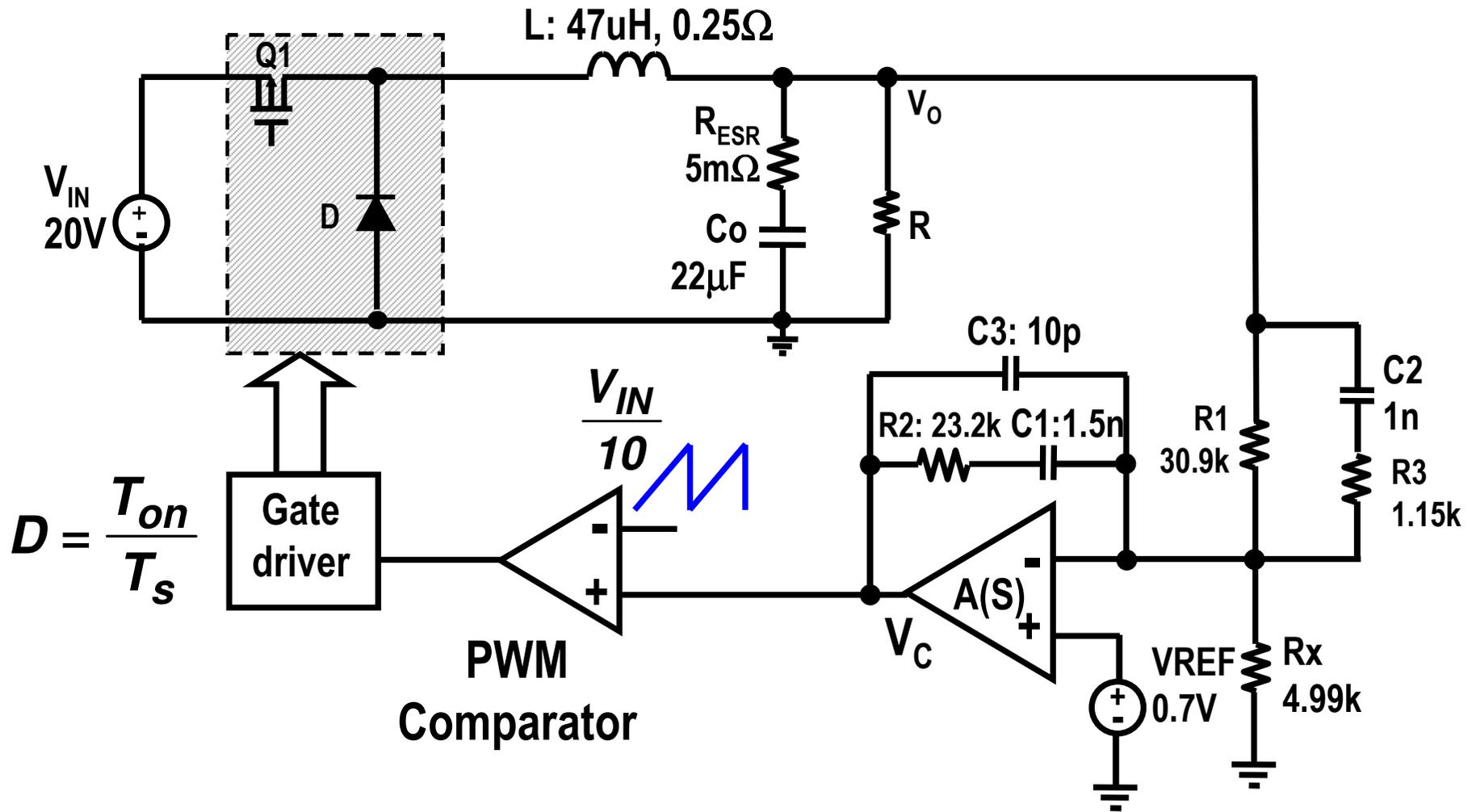
# Buck Converter with Voltage Mode and Type III Compensator





# Pspice Simulation Schematic

## PWM small signal average model

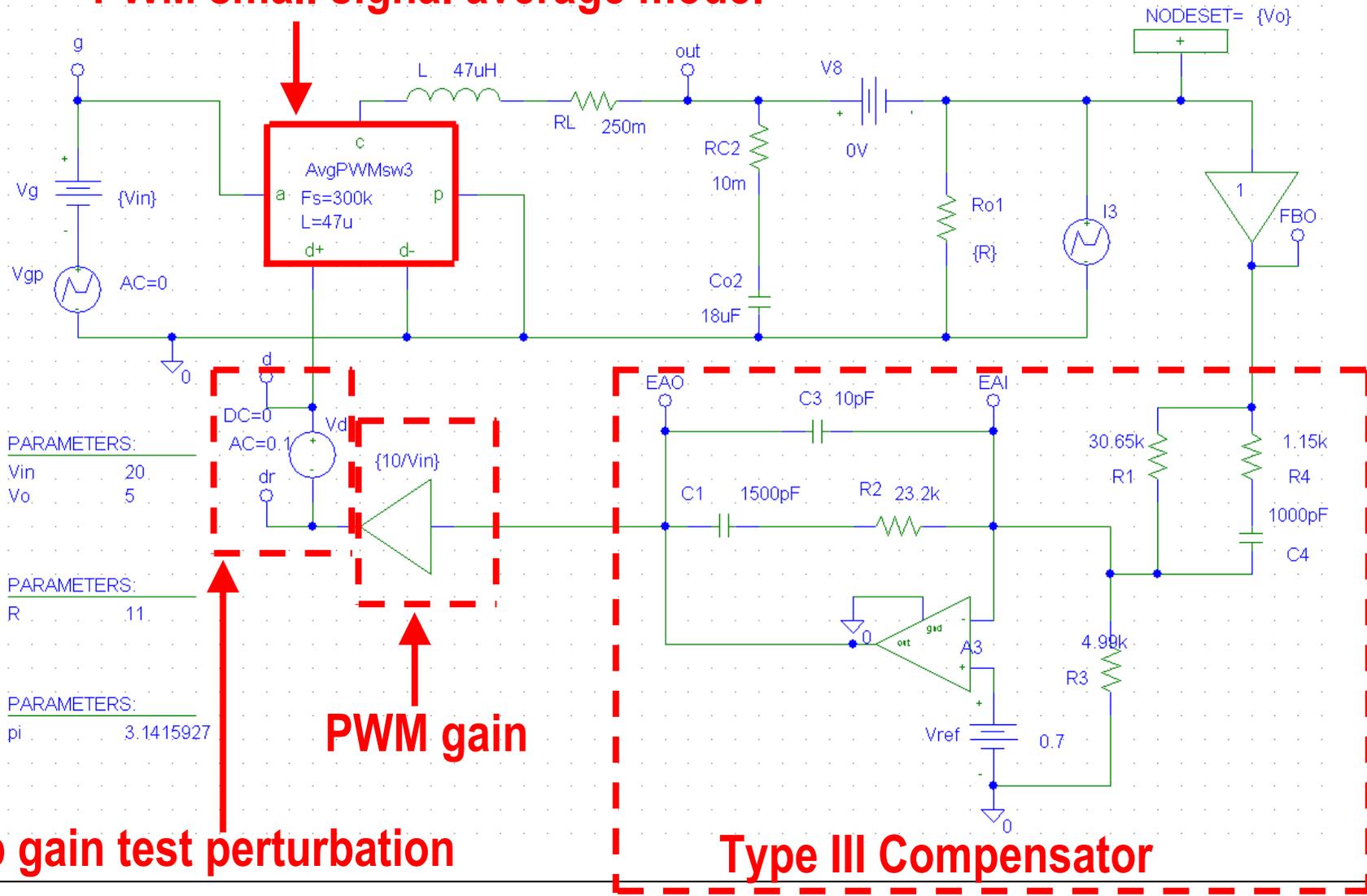

Loop gain test perturbation


PWM gain

Type III Compensator




# Simulation and Test Results

## PSPICE Simulation Results

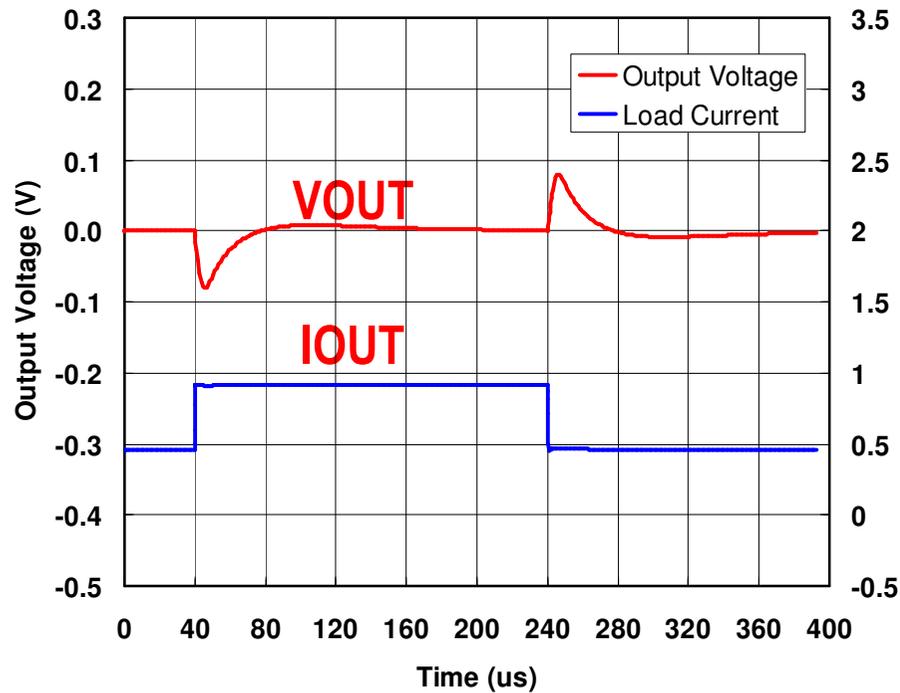

## Test Results

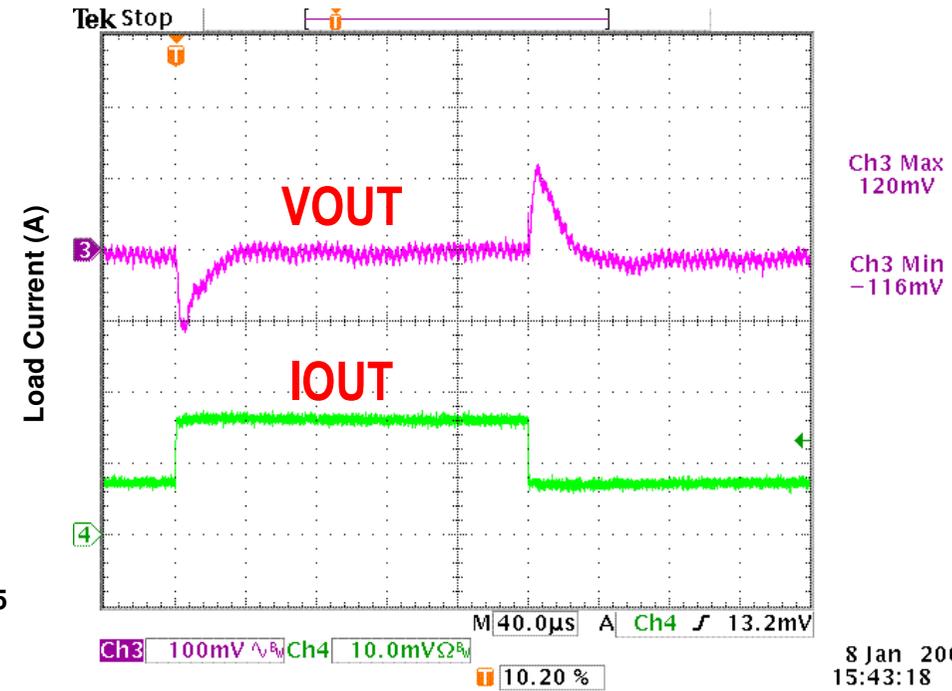


Load Step Transient: 0.4A to 0.8A




# Simulation and Test Results

## PSPICE Simulation Results

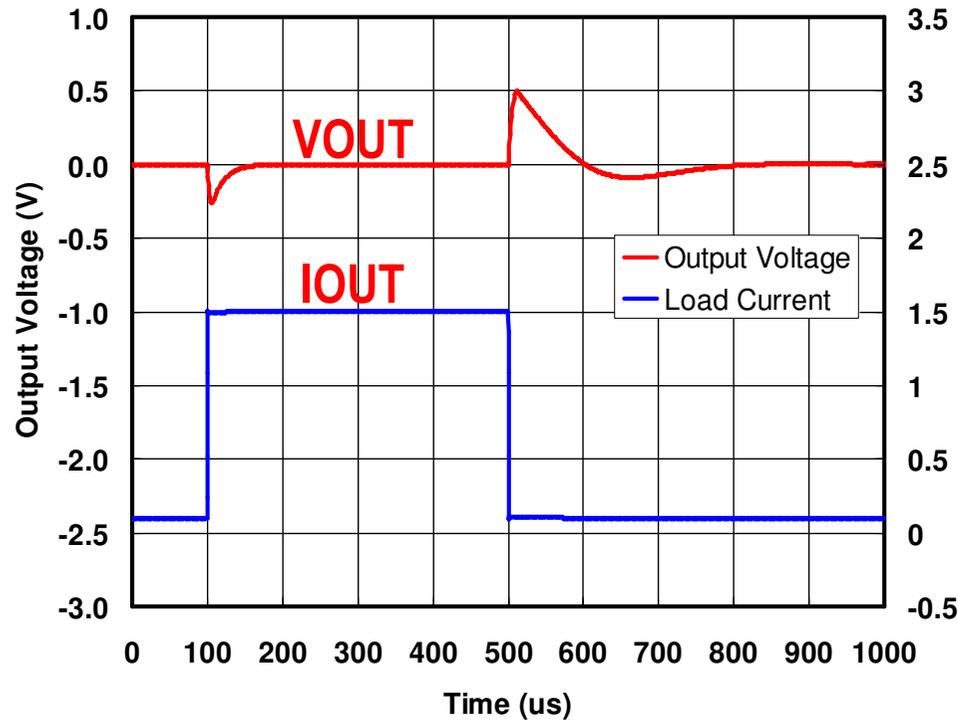

## Test Results

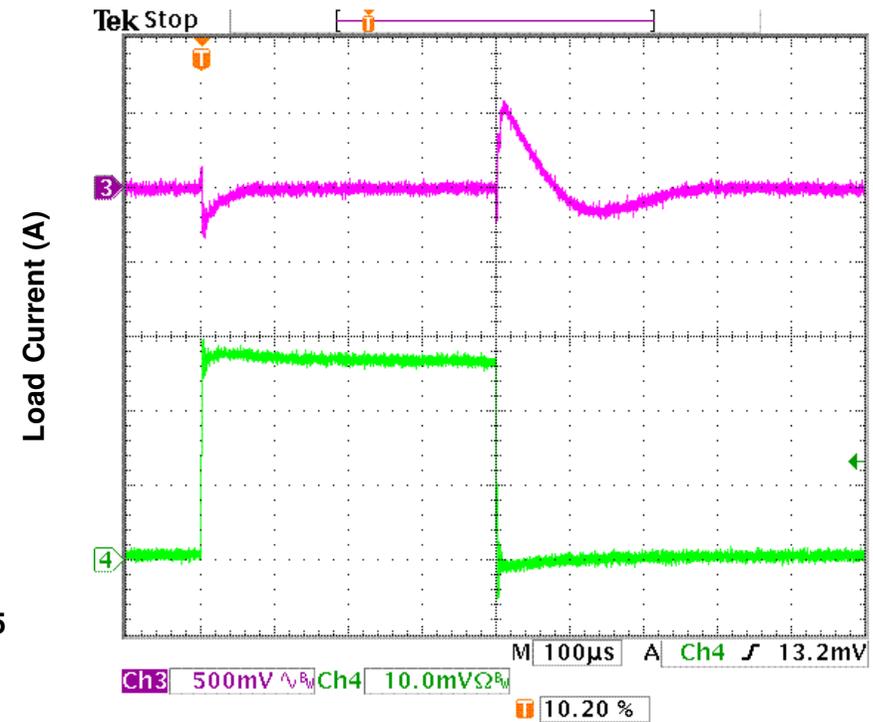


**Load Step Transient: 0.1A to 1.5A**




# Loop Bandwidth Simulation: Mathcad and Pspice

## Mathcad

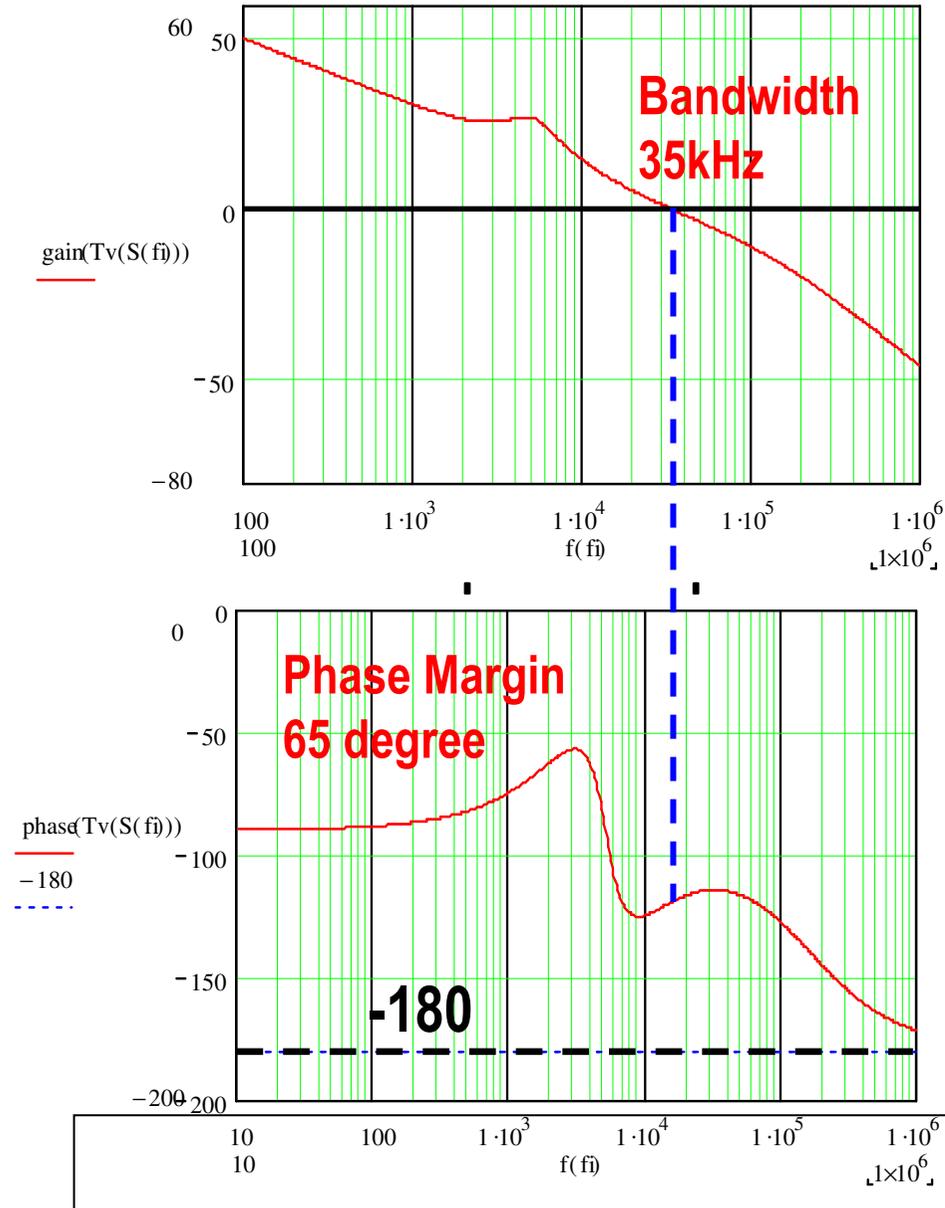

## Pspice

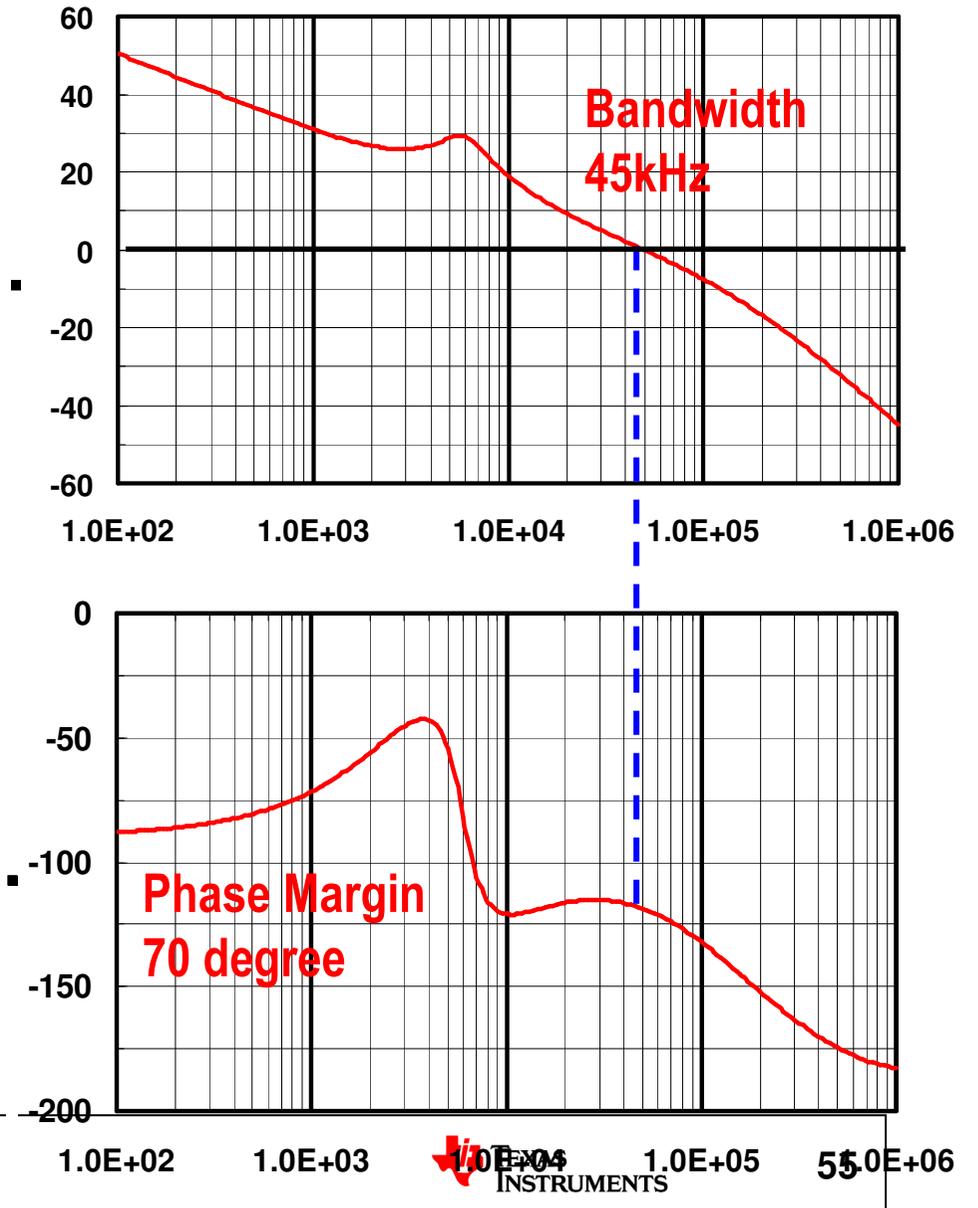



**Thanks!**

**Current Mode Loop Compensator Design will be next time**