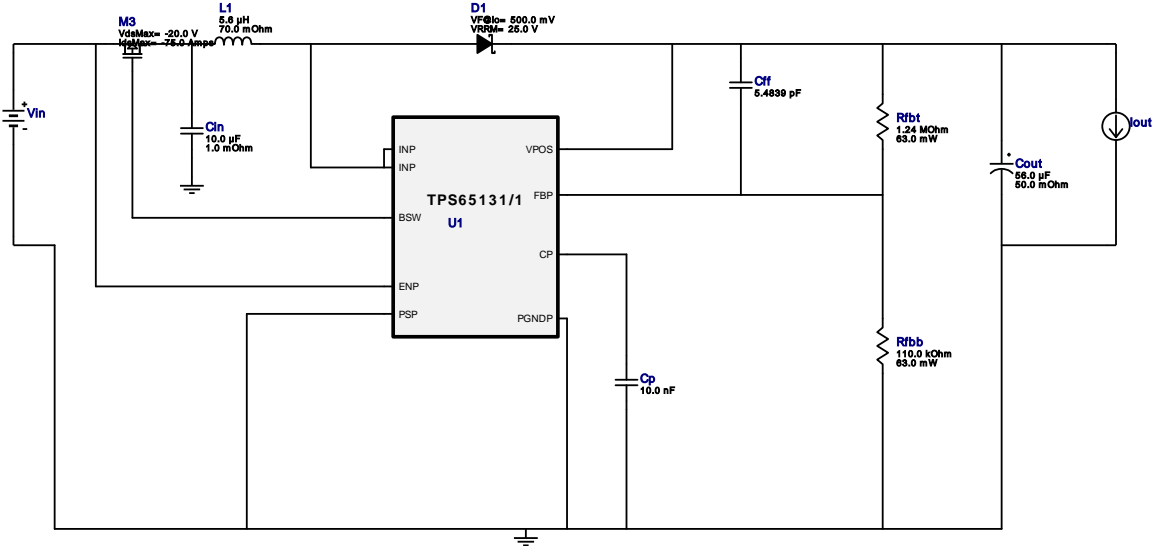



# WEBENCH® Design Report







Design : 176 TPS65131RGER  
 TPS65131RGER 5V-5V to 15.00V @ 0.2A















## Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cff	CUSTOM	CUSTOM Series= ?	Cap= 5.4839 pF VDC= 0.0 V IRMS= 0.0 A	1	NA	CUSTOM 0 mm <sup>2</sup>
Cin	TDK	C2012X7R1A106M125AC Series= X7R	Cap= 10.0 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.10	0805 7 mm <sup>2</sup>
Cout	Panasonic	EEHZC1E560P Series= ZC	Cap= 56.0 uF ESR= 50.0 mOhm VDC= 25.0 V IRMS= 900.0 mA	1	\$0.29	SM_RADIAL_6.3AMM 80 mm <sup>2</sup>
Cp	Samsung Electro-Mechanics	CL10C103JA8NNNC Series= C0G/NP0	Cap= 10.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.04	0603 5 mm <sup>2</sup>
D1	Vishay-Semiconductor	BYS10-25-E3/TR	Vf@Io= 500.0 mV VRRM= 25.0 V	1	\$0.11	SMA 37 mm <sup>2</sup>
L1	NIC Components	NPI54C5R6MTRF	L= 5.6 µH 70.0 mOhm	1	\$0.09	IND_NPI54C 61 mm <sup>2</sup>
M3	Texas Instruments	CSD25402Q3A	VdsMax= -20.0 V IdsMax= -75.0 Amps	1	\$0.22	DNH0008A 18 mm <sup>2</sup>
Rfbb	Vishay-Dale	CRCW0402110KFKED Series= CRCW..e3	Res= 110.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>
Rfbt	Vishay-Dale	CRCW04021M24FKED Series= CRCW..e3	Res= 1.24 MOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm <sup>2</sup>

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
U1	Texas Instruments	TPS65131RGER	Switcher	1	\$1.07	 RGE0024B 25 mm <sup>2</sup>

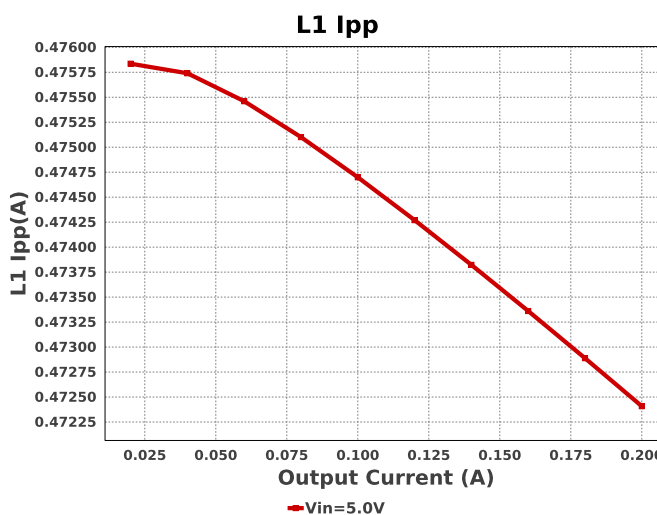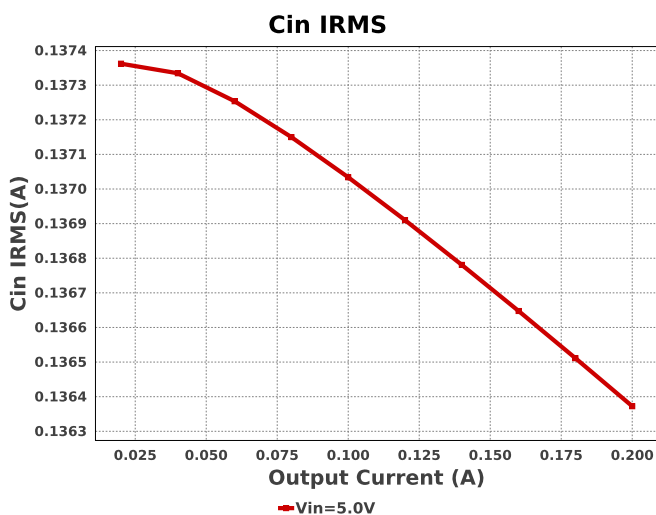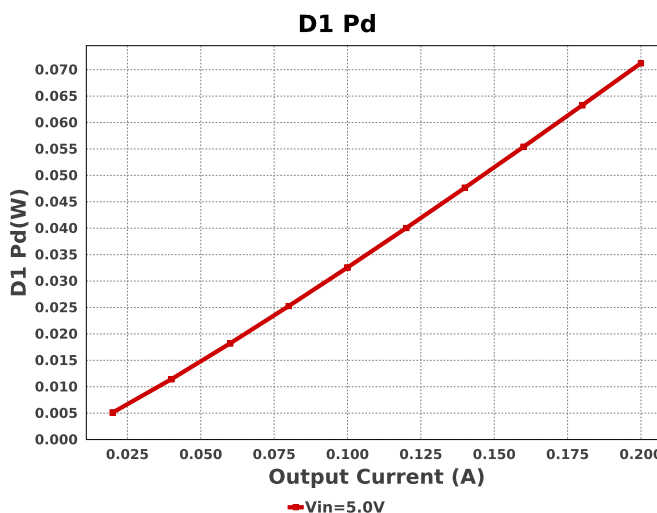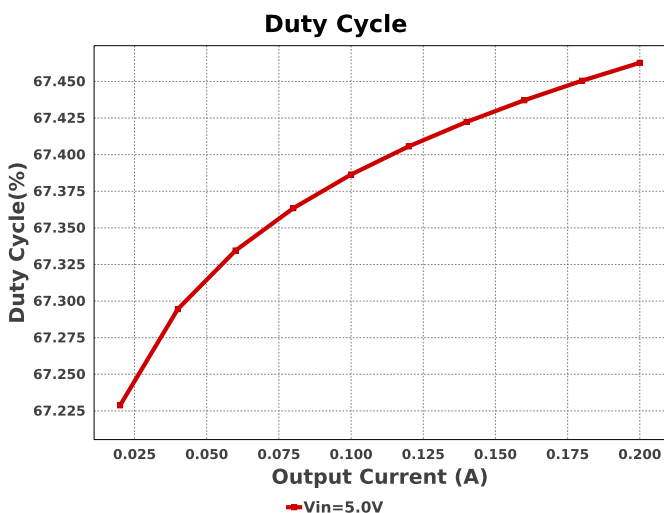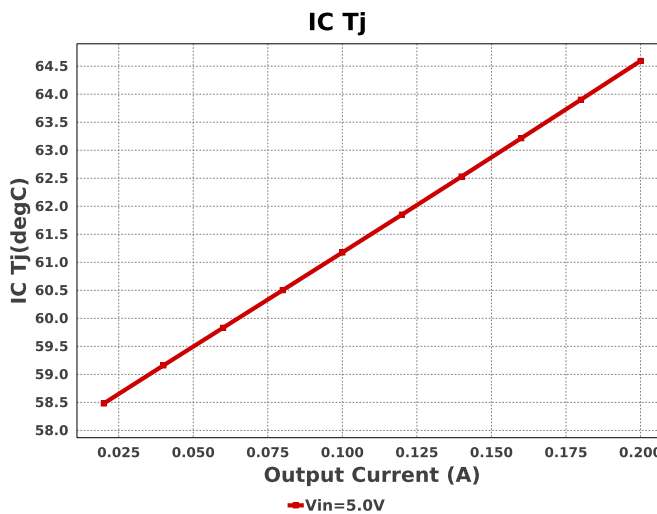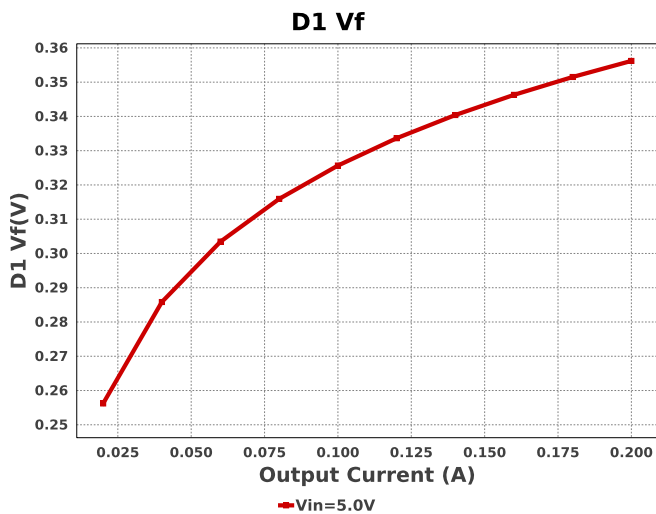

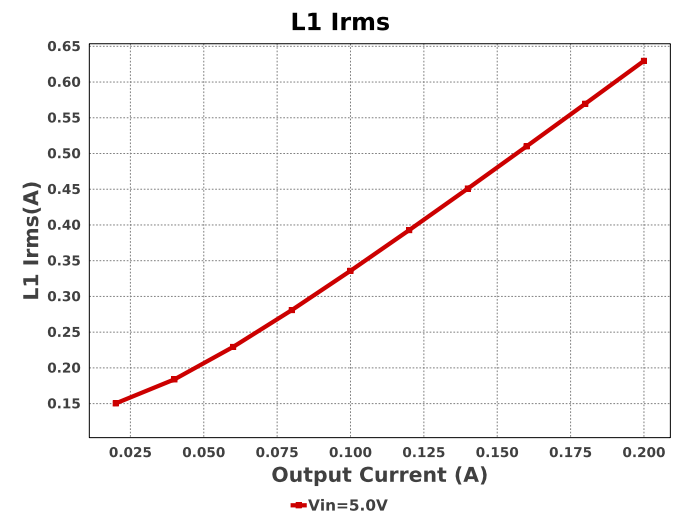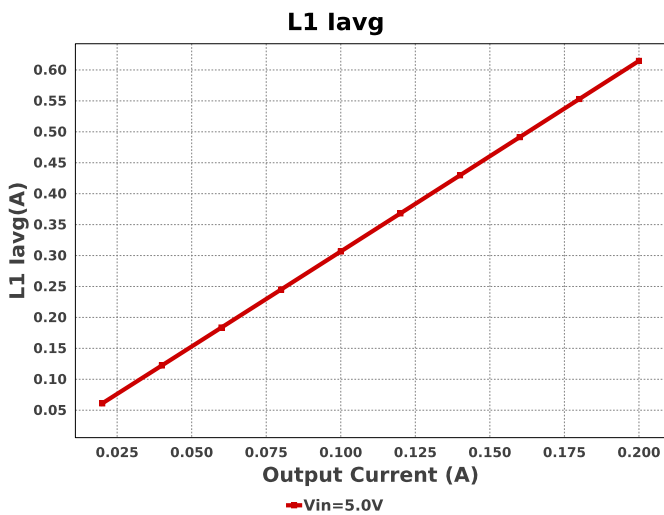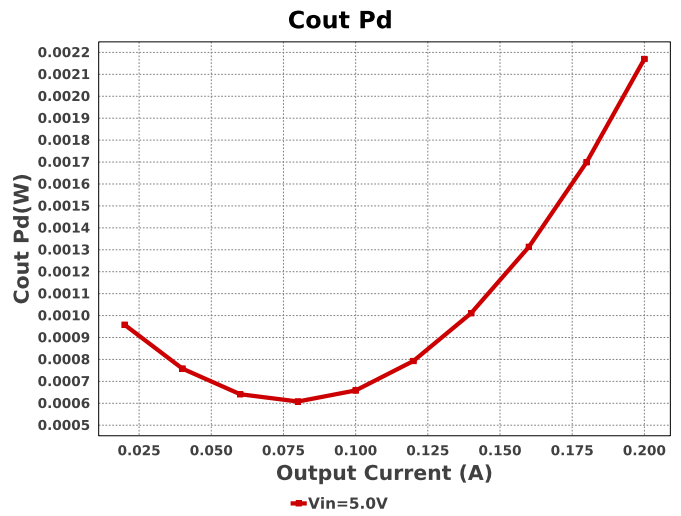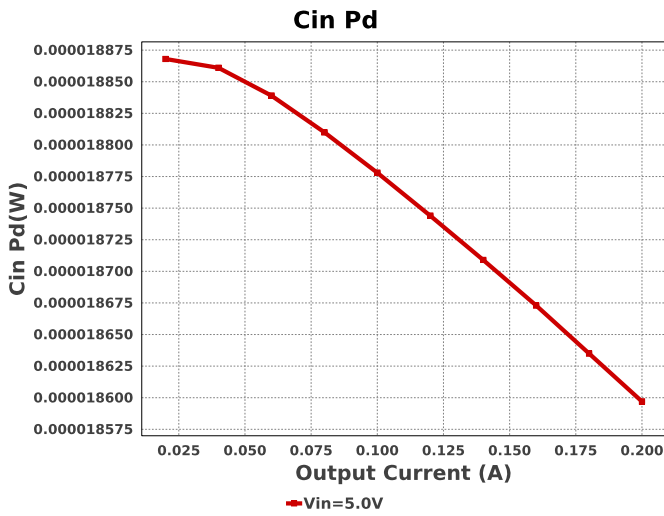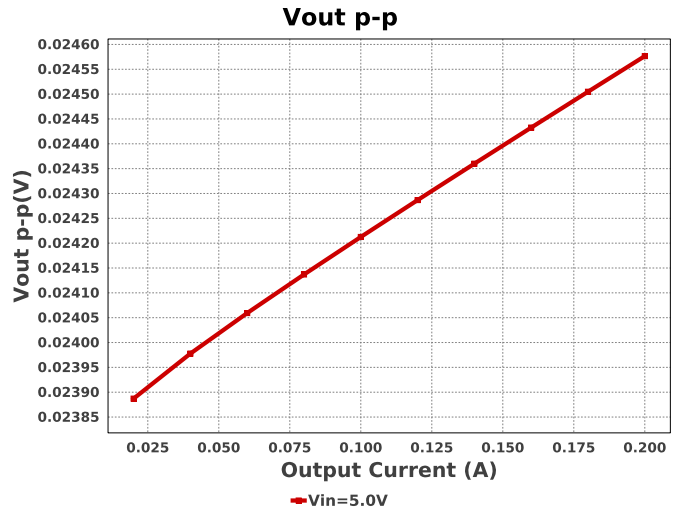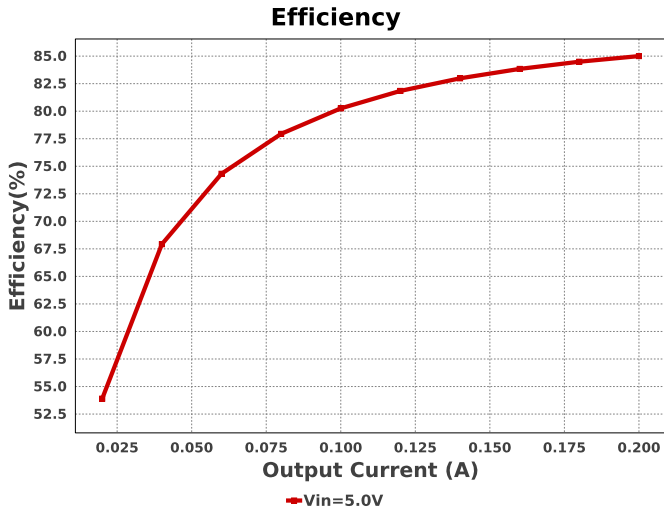

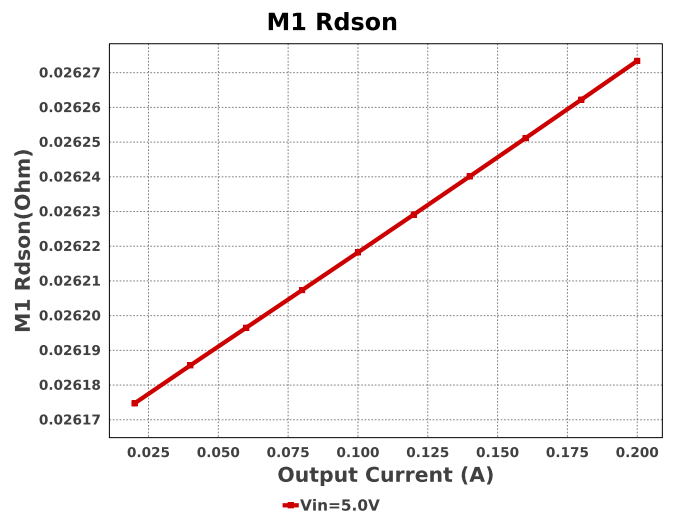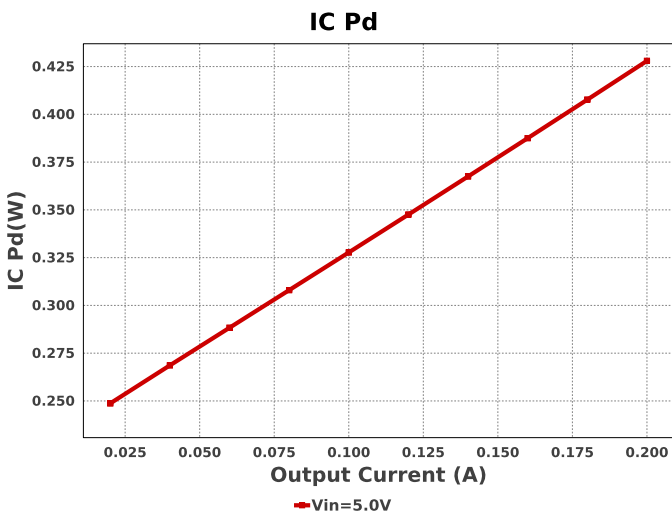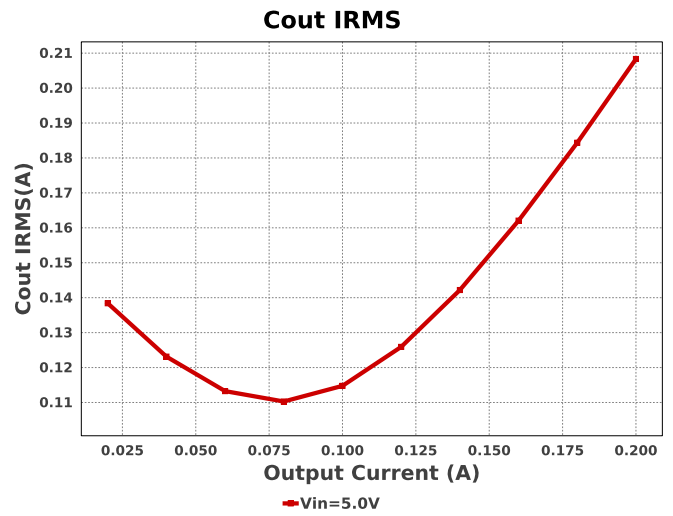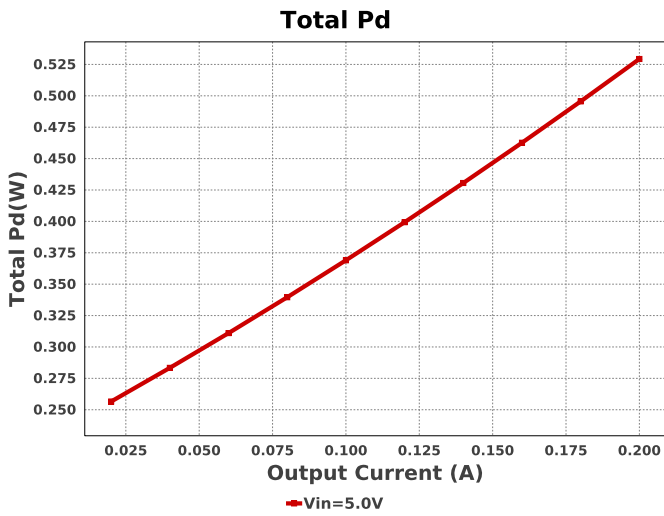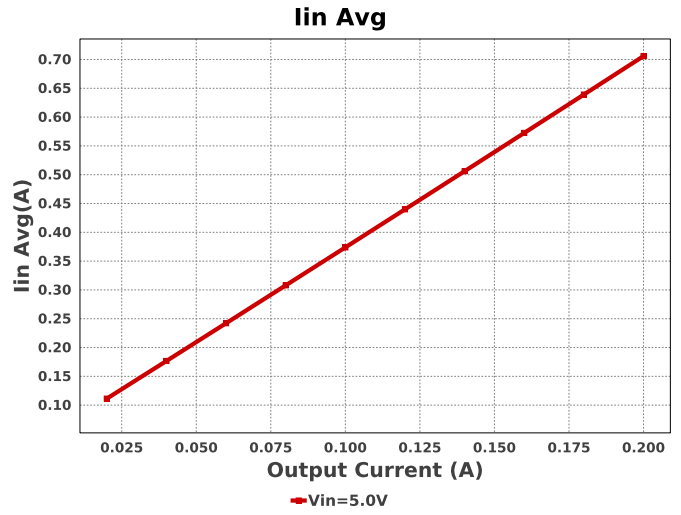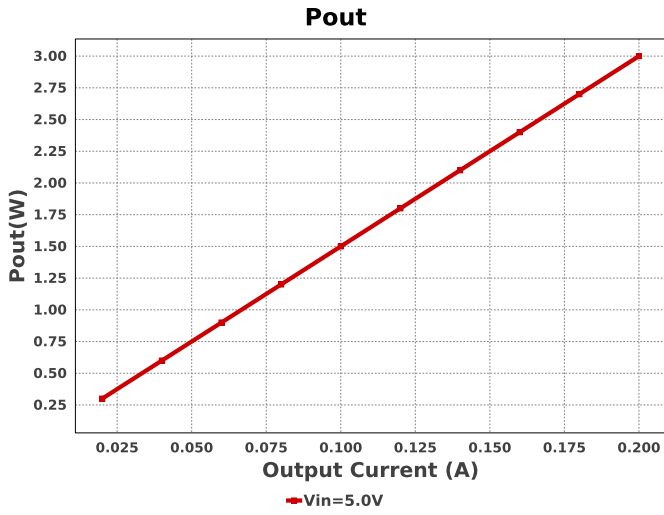

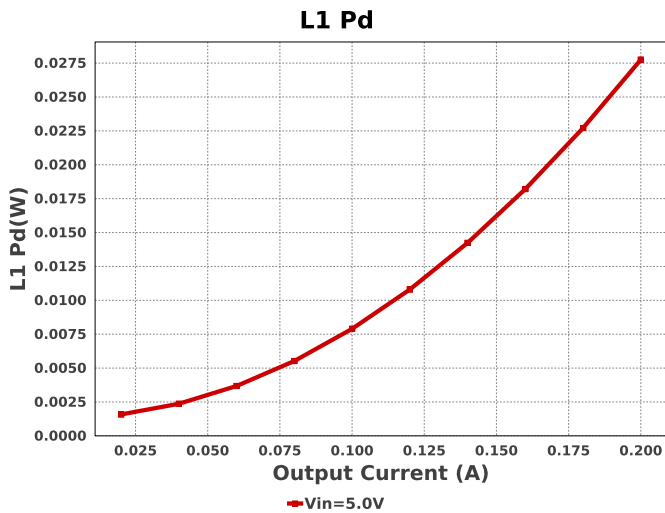

## Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	136.372 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	18.597 $\mu$ W	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	208.328 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	2.17 mW	Capacitor	Output capacitor power dissipation
5.	D1 Pd	71.239 mW	Diode	Output Diode Power Dissipation
6.	IC Pd	427.98 mW	IC	IC power dissipation
7.	IC Tj	64.594 degC	IC	IC junction temperature
8.	ICThetaJA	34.1 degC/W	IC	IC junction-to-ambient thermal resistance
9.	Iin Avg	705.87 mA	IC	Average input current
10.	L1 Iavg	614.68 mA	Inductor	Inductor average current
11.	L1 Ipp	472.408 mA	Inductor	Inductor 1 peak to peak current
12.	L1 Irms	629.626 mA	Inductor	Inductor ripple current
13.	L Pd	27.75 mW	Inductor	Power Dissipation in the Inductor
14.	M1 Rdson	26.273 mOhm	Mosfet	
15.	Cin Pd	18.597 $\mu$ W	Power	Input capacitor power dissipation
16.	Cout Pd	2.17 mW	Power	Output capacitor power dissipation
17.	D1 Pd	71.239 mW	Power	Output Diode Power Dissipation
18.	IC Pd	427.98 mW	Power	IC power dissipation
19.	L Pd	27.75 mW	Power	Power Dissipation in the Inductor
20.	Total Pd	529.332 mW	Power	Total Power Dissipation
21.	BOM Count	10	System	Total Design BOM count
			Information	
22.	Duty Cycle	67.463 %	System	Duty cycle
			Information	
23.	Efficiency	85.002 %	System	Steady state efficiency
			Information	
24.	FootPrint	244.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
			Information	
25.	Frequency	1.26 MHz	System	Switching frequency
			Information	
26.	Iout	200.0 mA	System	Iout operating point
			Information	
27.	Mode	PWM CCM	System	PWM/PFM Mode
			Information	
28.	Pout	3.0 W	System	Total output power
			Information	
29.	Total BOM	NA	System	Total BOM Cost
			Information	
30.	Vin	5.0 V	System	Vin operating point
			Information	
31.	Vout Actual	14.887 V	System	Vout Actual calculated based on selected voltage divider resistors
			Information	
32.	Vout Tolerance	3.871 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider
			Information	resistors if applicable
33.	Vout p-p	24.577 mV	System	Peak-to-peak output ripple voltage
			Information	
34.	D1 Vf	356.197 mV		

## Design Inputs

Name	Value	Description
Iout	200.0 m	Maximum Output Current

---

Name	Value	Description
VinMax	5.0	Maximum input voltage
VinMin	5.0	Minimum input voltage
Vout	15.0	Output Voltage
base_pn	TPS65131/1	Base Product Number
source	DC	Input Source Type
Ta	50.0	Ambient temperature

## WEBENCH® Assembly

### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of  $C_{in}$  and  $C_{out}$ , and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

### Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 5.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to  $V_{in}$  and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from  $V_{out}$  and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between  $V_{in}$  and GND, a load is connected between  $V_{out}$  and GND and a current meter is connected in series between  $V_{out}$  and the load. The load must be able to handle at least rated output power + 50% ( 7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



### Design Assistance

1. Master key : B813C5D1755B3B11[v1]
2. **TPS65131/1** Product Folder : <http://www.ti.com/product/TPS65131> : contains the data sheet and other resources.

**Important Notice and Disclaimer**

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.