

AN-2239 LM5018 Isolated Evaluation Board

1 Introduction

An isolated bias supply is implemented in this evaluation board with LM5018 Constant-On-Time regulator. LM5018 regulator integrates both the high and low side power switches essential for creating isolated buck converter.

Board Specifications:

- Input Range: 20V to 100V
- Primary Output Voltage: 10V
- Secondary (Isolated) Output Voltage: 9.5V
- Maximum Load Current (Primary + Secondary): 250mA
- Maximum Power Output: 2.5W
- Nominal Switching Frequency: 750kHz
- Efficiency (FIN = 36V, IOUT2 = 250mA): 77 percent
- Board size: 2 inch × 2 inch

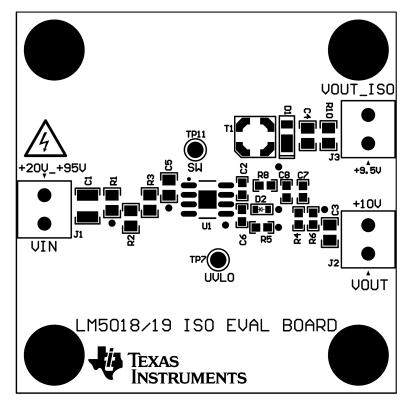


Figure 1. LM5018 Evaluation Board (Top View)

All trademarks are the property of their respective owners.

1

2

The UVLO resistors are selected using the following two equations:

 $V_{\rm IN(HYS)} = I_{\rm HYS} R_1$

and

$$V_{IN (UVLO,rising)} = 1.225V \times \left(\frac{R_1}{R_2} + 1\right)$$

On this evaluation board R1 = $127k\Omega$ and R2 = $8.25k\Omega$, resulting in UVLO rising threshold at VIN = 20.5V and a hysteresis of 2.54V.

3 Board Connection and Start-Up

The input connections are made using TP1 (VIN) and TP2 (GND) terminals. The primary output appears at TP3 (VOUT1) and TP4 (GND). The secondary (isolated) output is available across TP5 (VOUT2) and TP6 (IGND). The input voltage should be gradually increased above UVLO set point of 20.5V. Both the outputs (VOUT1 and VOUT2) should be close to 10V at this point. This board is designed to function with input voltage range of 20V to 100V. The minimum VIN threshold can be changed by changing the UVLO resistors R1, R2. VIN should not exceed 100V.

The magnetics in this design is optimized for solution size, and therefore limits the output power. The total load at the output should not exceed 250mA, otherwise the coupled inductor will saturate/overheat, which can destroy both the coupled inductor and the regulator IC U1. If a sustained over-current situation is to be tolerated, a coupled inductor with higher saturation and rms ratings should be used.

4 Complete Evaluation Board Schematic

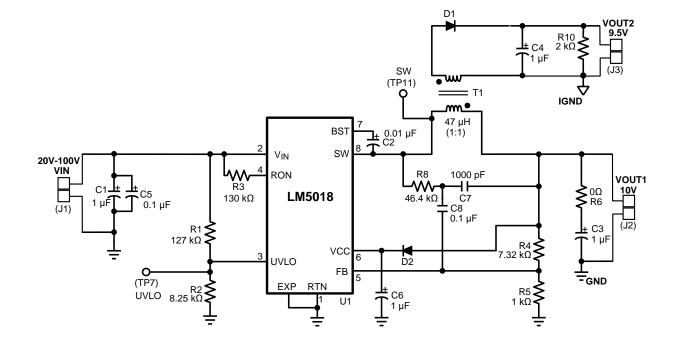


Figure 2. Complete Evaluation Board Schematic

(1)

(2)

www.ti.com

5 Bill of Materials


Item	Description	Mfg., Part Number	Package	Value
U1	Sync Switching Regulator	Texas Instruments, LM5018	SO PowerPAD-8	100V, 300mA
T1	Coupled Inductor, 1500 VDC	Coilcraft, LPD5030V-473ME	5mm × 5mm	47uH, 0.47A
	Alternate Part	Wurth, 750312750	h, 750312750 8.26mm × 6.60mm	
D1	Schottky Diode	Diodes Inc., DFLS1100-7	Pwr–DI123	100V, 1A
D2	Schottky Diode	Diodes Inc., SDM10U45-7	SOD-523	40V, 100mA
C1	Ceramic Capacitor	MuRata, GRM32CR72A105KA35L	1210	1uF, 100V, X7R
C2	Ceramic Capacitor	TDK, C1608X7R1C103K	0603	0.01uF, 16V, X7R
C3, C4	Ceramic Capacitor	TDK, C2012X7R1E105K	0805	1uF, 25V, X7R
C5	Ceramic Capacitor	Kemet, C0805C104K1RACTU	0805	0.1uF, 100V, X7R
C6	Ceramic Capacitor	TDK, C1608X7R1C105K	0603	1uF, 16V, X7R
C7	Ceramic Capacitor	Murata, GRM188R71E102KA01D	0603	1000pF,25V, X7R
C8	Ceramic Capacitor	AVX, 0603YC104KAT2A	0603	0.1uF, 16V, X7R
R1	Resistor	Vishay/Dale, CRCW0805127KFKEA	0805	127kΩ, 1%
R2	Resistor	Vishay/Dale, CRCW08058K25FKEA	0805	8.25kΩ, 1%
R3	Resistor	Vishay/Dale, CRCW0805130KFKEA	0805	130kΩ, 1%
R4	Resistor	Panasonic, ERJ-3EKF7321V	0603	7.32kΩ, 1%
R5	Resistor	Panasonic, ERJ-3EKF1001V	0603	1.0kΩ,1%
R6	Resistor	Yageo, RC0603JR-070RL	RC0603JR-070RL 0603	
R8	Resistor	Panasonic, ERJ-3EKF4642V 0603 46.4		46.4kΩ, 1%
R10	Resistor	Panasonic, ERJ-6GEYJ202V	0805	2kΩ, 5%



Performance Curves

www.ti.com

6 **Performance Curves**

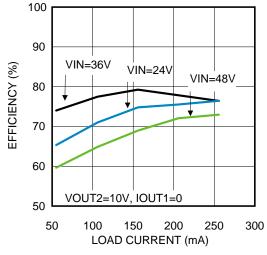

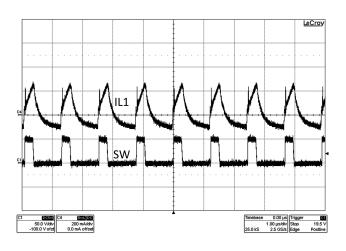


Figure 3. Efficiency at 750 kHz, VOUT1 = 10V

Figure 4. Steady State Waveform (VIN = 48V, IOUT1 = 0mA, IOUT2 = 100mA)

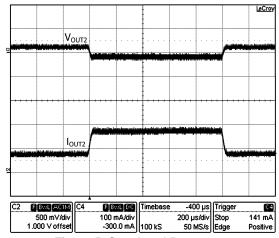


Figure 5. Step Load Response (VIN = 48V, IOUT1 = 0, Step Load on IOUT2 = 80mA to 180mA)



www.ti.com

PC Board Layout

7 PC Board Layout

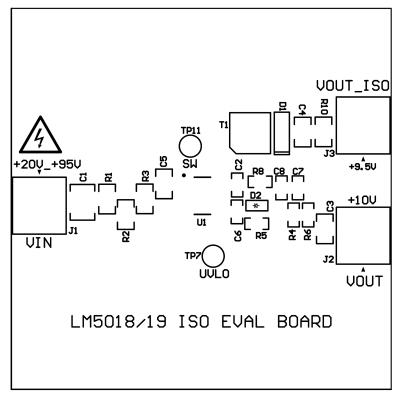


Figure 6. Board Silkscreen

5



www.ti.com

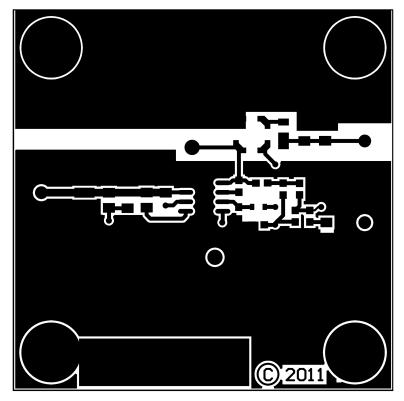


Figure 7. Board Top Layer

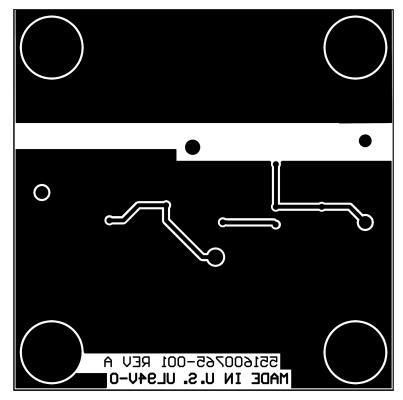


Figure 8. Board Bottom Layer

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have *not* been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products		Applications		
Audio	www.ti.com/audio	Automotive and Transportation	www.ti.com/automotive	
Amplifiers	amplifier.ti.com	Communications and Telecom	www.ti.com/communications	
Data Converters	dataconverter.ti.com	Computers and Peripherals	www.ti.com/computers	
DLP® Products	www.dlp.com	Consumer Electronics	www.ti.com/consumer-apps	
DSP	dsp.ti.com	Energy and Lighting	www.ti.com/energy	
Clocks and Timers	www.ti.com/clocks	Industrial	www.ti.com/industrial	
Interface	interface.ti.com	Medical	www.ti.com/medical	
Logic	logic.ti.com	Security	www.ti.com/security	
Power Mgmt	power.ti.com	Space, Avionics and Defense	www.ti.com/space-avionics-defense	
Microcontrollers	microcontroller.ti.com	Video and Imaging	www.ti.com/video	
RFID	www.ti-rfid.com			
OMAP Applications Processors	www.ti.com/omap	TI E2E Community	e2e.ti.com	
Wireless Connectivity	www.ti.com/wirelessconnectivity			

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2013, Texas Instruments Incorporated