



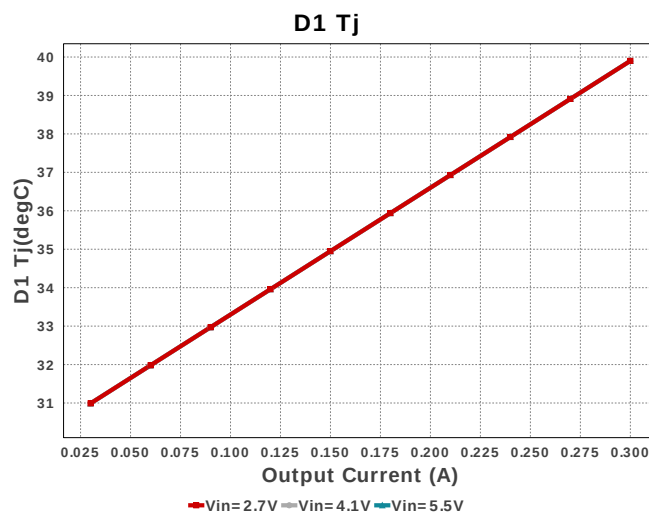
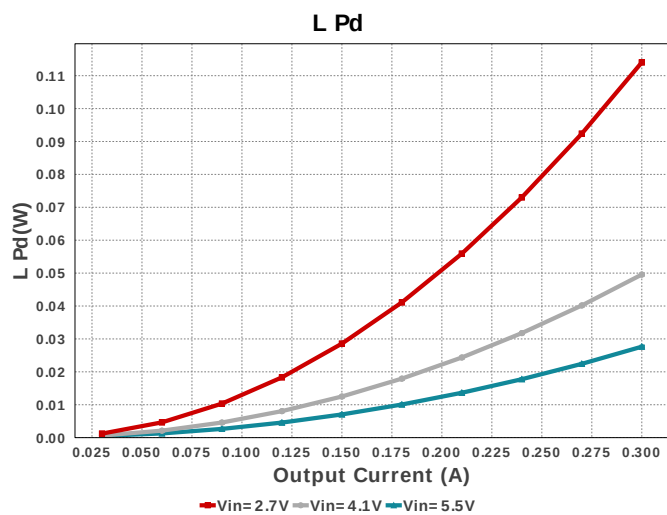
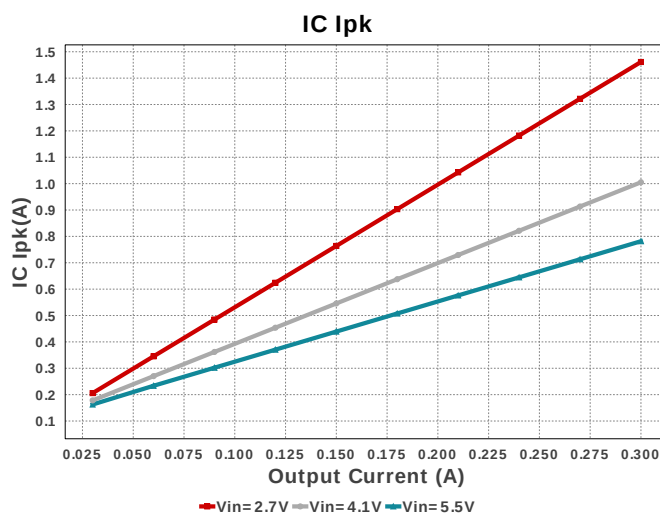
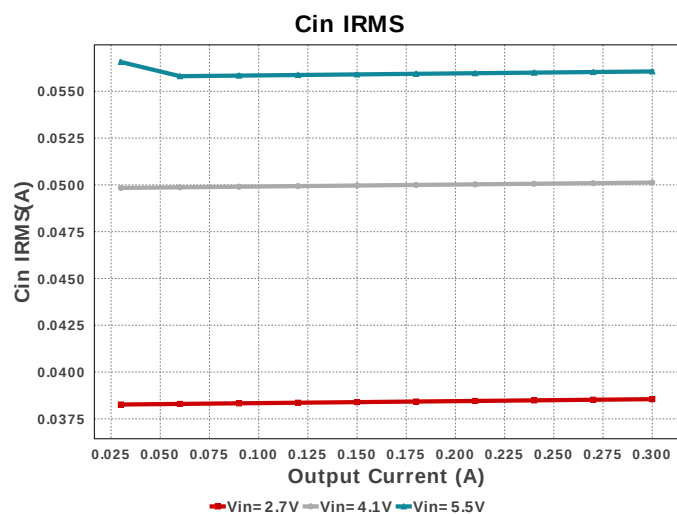
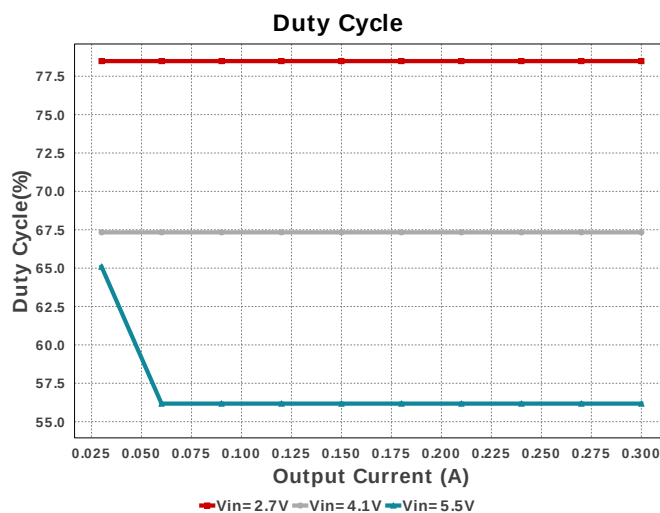
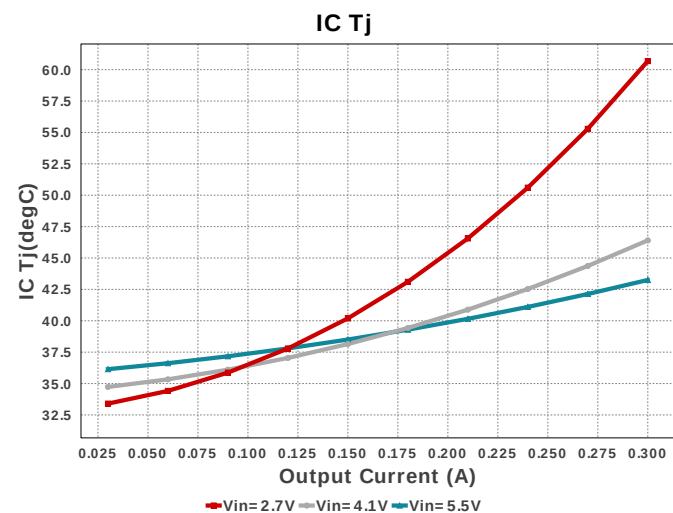
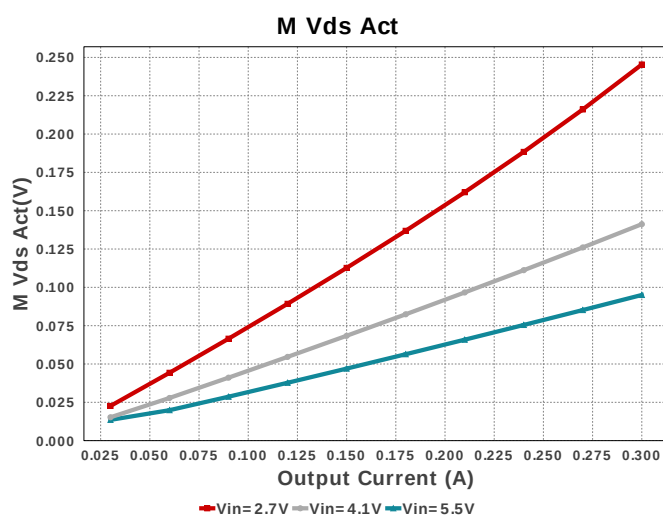
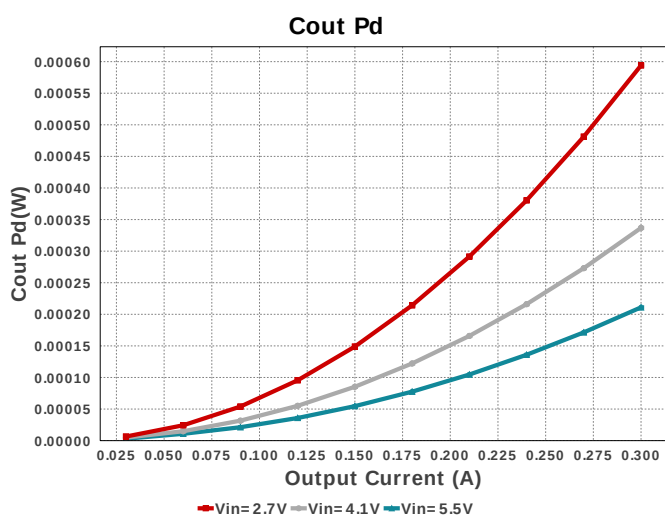
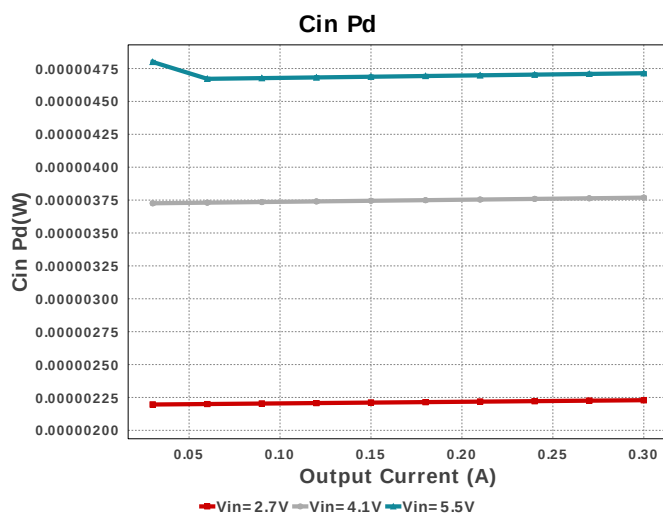
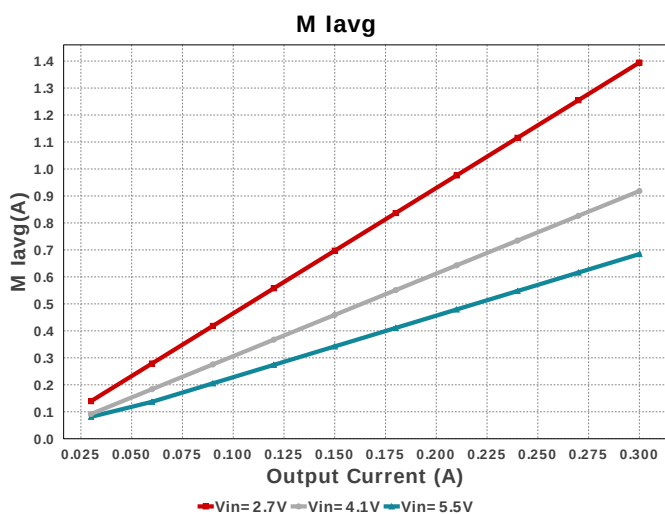
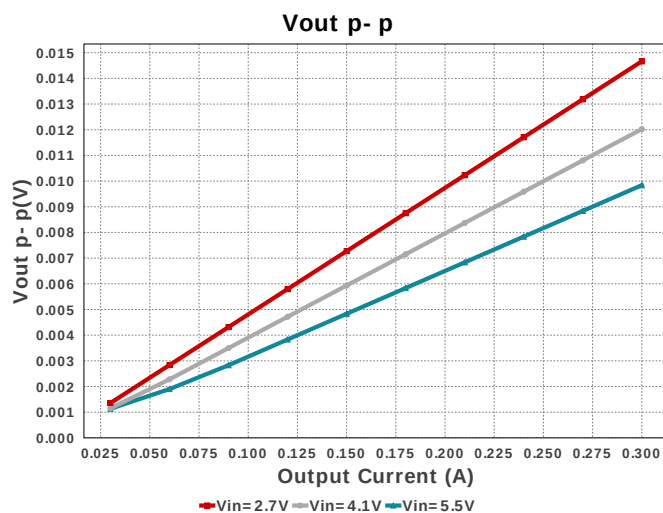
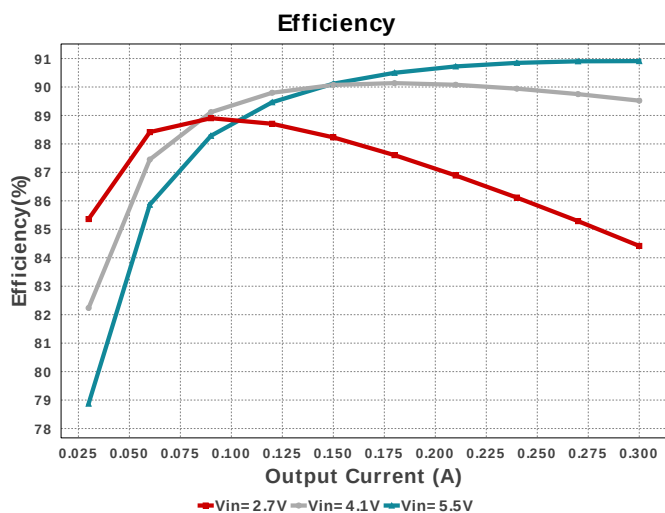
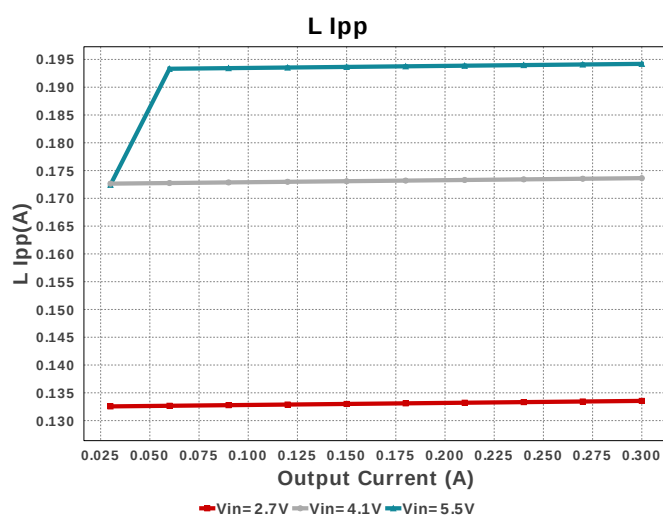
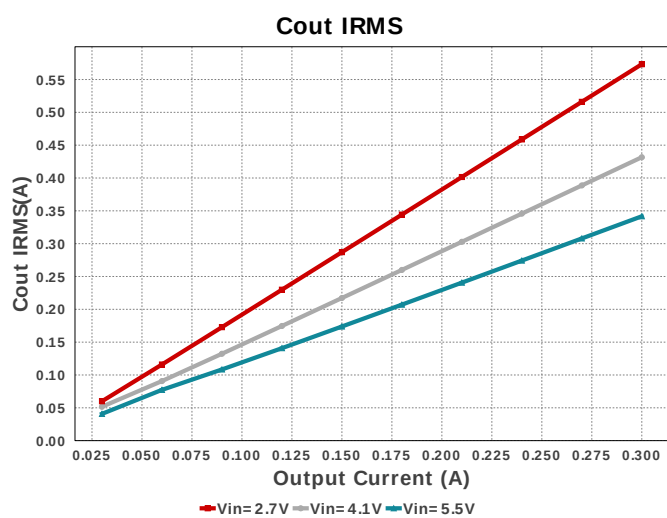


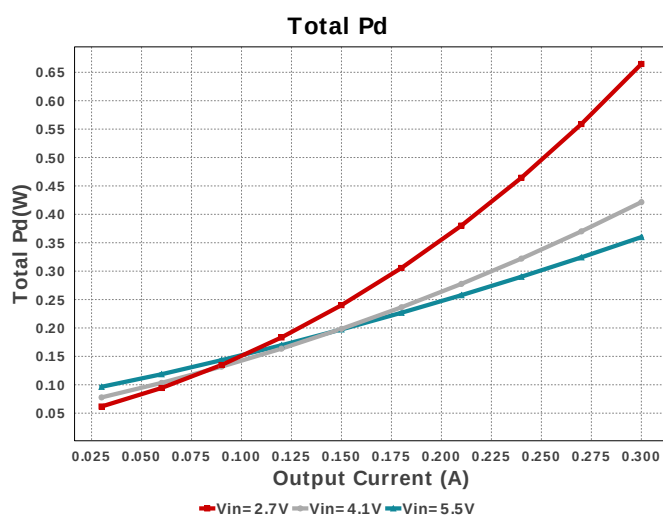


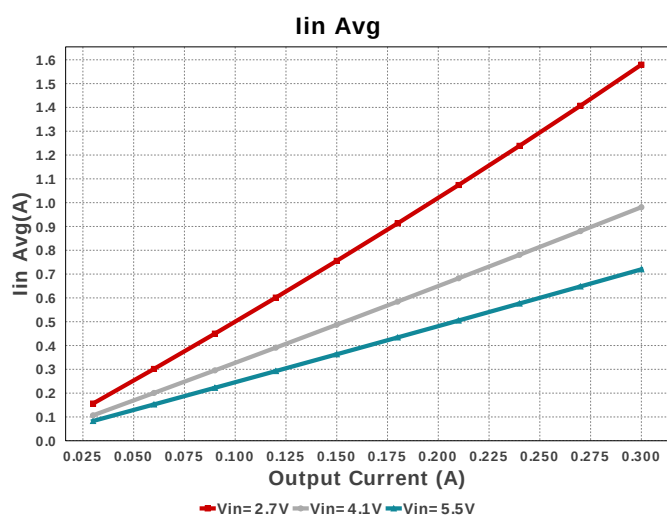Device = LMR62421XSD/NOPB
Topology = Boost
Created = 2021-07-20 06:58:26.282
BOM Cost = \$0.96
BOM Count = 11
Total Pd = 0.66W



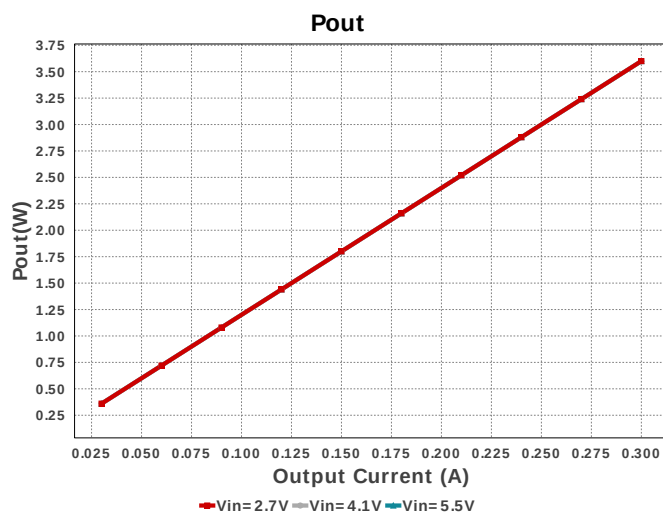

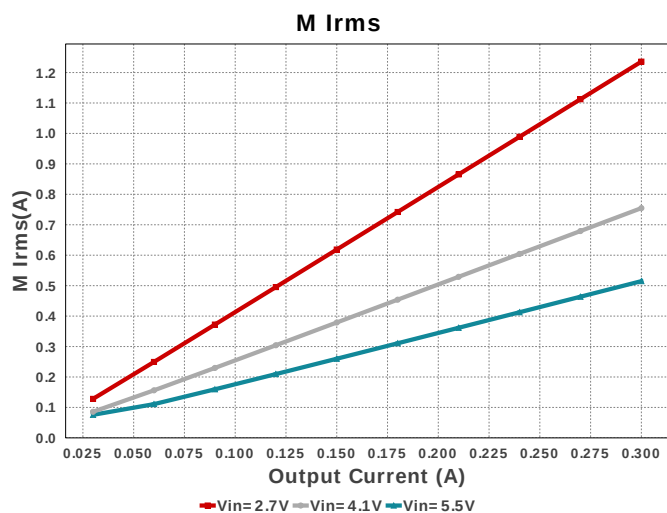

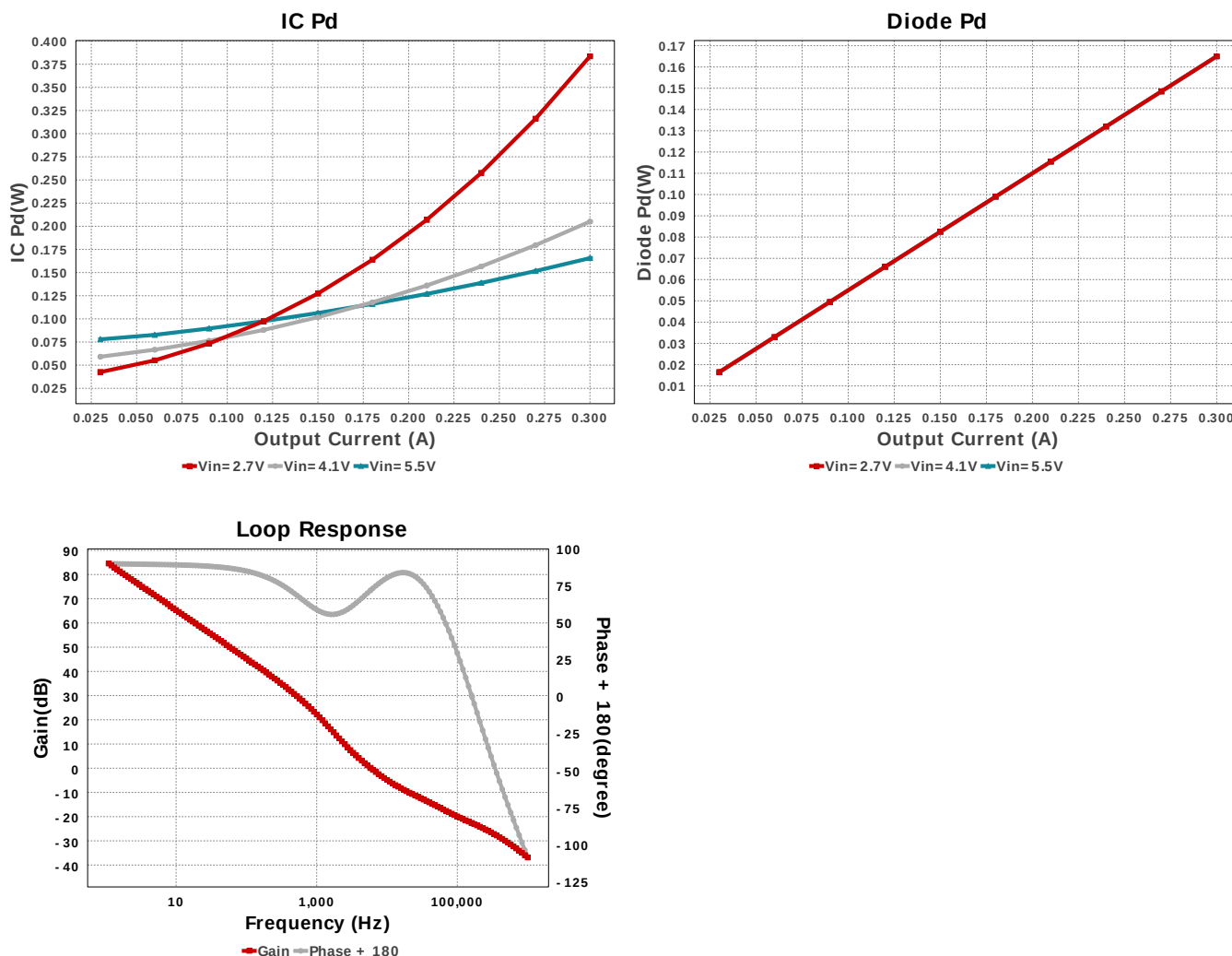

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	38.551 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	2.229 μ W	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	573.283 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	594.04 μ W	Capacitor	Output capacitor power dissipation
5.	D1 Tj	39.9 degC	Diode	D1 junction temperature
6.	Diode Pd	165.0 mW	Diode	Diode power dissipation
7.	IC Ipk	1.461 A	IC	Peak switch current in IC
8.	IC Pd	383.52 mW	IC	IC power dissipation
9.	IC Tj	60.682 degC	IC	IC junction temperature
10.	IC Tolerance	25.0 mV	IC	IC Feedback Tolerance
11.	ICThetaJA	80.0 degC/W	IC	IC junction-to-ambient thermal resistance
12.	Iin Avg	1.58 A	IC	Average input current
13.	L Ipp	133.54 mA	Inductor	Peak-to-peak inductor ripple current
14.	L Pd	114.03 mW	Inductor	Inductor power dissipation
15.	M Iavg	1.394 A	Mosfet	MOSFET Average current
16.	M Irms	1.236 A	Mosfet	MOSFET RMS ripple current
17.	M Vds Act	245.371 mV	Mosfet	Voltage drop across the MosFET
18.	Cin Pd	2.229 μ W	Power	Input capacitor power dissipation
19.	Cout Pd	594.04 μ W	Power	Output capacitor power dissipation
20.	Diode Pd	165.0 mW	Power	Diode power dissipation
21.	IC Pd	383.52 mW	Power	IC power dissipation
22.	L Pd	114.03 mW	Power	Inductor power dissipation
23.	Total Pd	664.646 mW	Power	Total Power Dissipation
24.	BOM Count	11	System	Total Design BOM count
25.	Cross Freq	3.474 kHz	System	Bode plot crossover frequency
26.	Duty Cycle	78.486 %	System	Duty cycle
27.	Efficiency	84.415 %	System	Steady state efficiency

#	Name	Value	Category	Description
28.	FootPrint	136.0 mm ²	System Information	Total Foot Print Area of BOM components
29.	Frequency	1.6 MHz	System Information	Switching frequency
30.	Gain Marg	-16.818 dB	System Information	Bode Plot Gain Margin
31.	Iout	300.0 mA	System Information	Iout operating point
32.	Low Freq Gain	80.281 dB	System Information	Gain at 1Hz
33.	Mode	CCM	System Information	Conduction Mode
34.	Phase Marg	55.604 deg	System Information	Bode Plot Phase Margin
35.	Pout	3.6 W	System Information	Total output power
36.	Total BOM	\$0.96	System Information	Total BOM Cost
37.	Vin	2.7 V	System Information	Vin operating point
38.	Vout	12.0 V	System Information	Operational Output Voltage
39.	Vout Actual	12.123 V	System Information	Vout Actual calculated based on selected voltage divider resistors
40.	Vout Tolerance	3.839 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
41.	Vout p-p	14.986 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	300.0 m	Maximum Output Current
VinMax	5.5	Maximum input voltage
VinMin	2.7	Minimum input voltage
Vout	12.0	Output Voltage
base_pn	LMR62421X	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 2.7V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

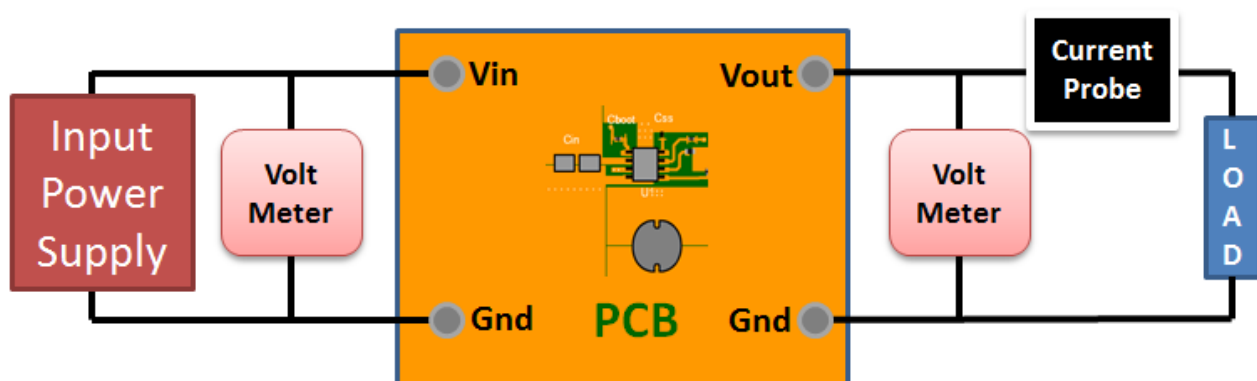

Design Assistance

1. Master key : 63A9C3F7EEDF6BCC[v1]
2. **LMR62421X** Product Folder : <http://www.ti.com/product/LMR62421> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.