
VinMin = 2.7V VinMax = 12.0V Vout = 5.5V Iout = 1.0A Device = TPS63070RNMR Topology = Buck\_Boost Created = 2022-03-17 11:14:47.675 BOM Cost = \$3.22 BOM Count = 11 Total Pd = 1.64W

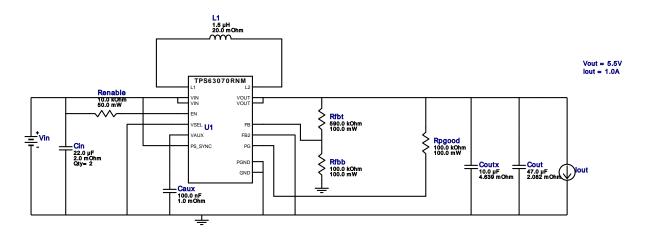
# WEBENCH® Design Report


Design: 75 TPS63070RNMR TPS63070RNMR 2.7V-12V to 3.00V @ 1A





#### **Electrical BOM**

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Caux	MuRata	GRM155R71C104KA88D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm <sup>2</sup>
Cin	MuRata	GRM32ER61E226KE15L Series= X5R	Cap= 22.0 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.67 A	2	\$0.65	1210 15 mm <sup>2</sup>
Cout	TDK	C3216X5R1E476M160AC Series= X5R	Cap= 47.0 uF ESR= 2.082 mOhm VDC= 25.0 V IRMS= 5.0279 A	1	\$0.39	1206 11 mm <sup>2</sup>
Coutx	TDK	C1608X5R1E106M080AC Series= X5R	Cap= 10.0 uF ESR= 4.639 mOhm VDC= 25.0 V IRMS= 2.4141 A	1	\$0.20	■1 0603 5 mm²
L1	Bourns	SDR0805-1R5ML	L= 1.5 μH 20.0 mOhm	1	\$0.27	SDR0805 96 mm <sup>2</sup>
Renable	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm <sup>2</sup>
Rfbb	Vishay-Dale	CRCW0603100KFKEA Series= CRCWe3	Res= 100.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	■1 0603 5 mm²
Rfbt	Yageo	RC0603FR-07590KL Series= ?	Res= 590.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
Rpgood	Vishay-Dale	CRCW0603100KFKEA Series= CRCWe3	Res= 100.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	0603 5 mm <sup>2</sup>
U1	Texas Instruments	TPS63070RNMR	Switcher	1	\$1.01	RNM0015A 14 mm <sup>2</sup>

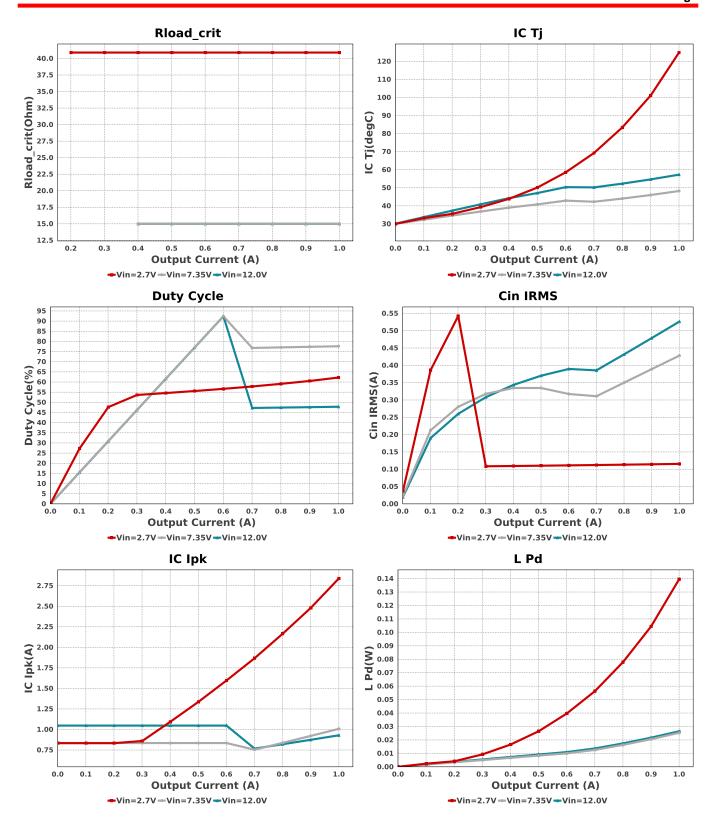

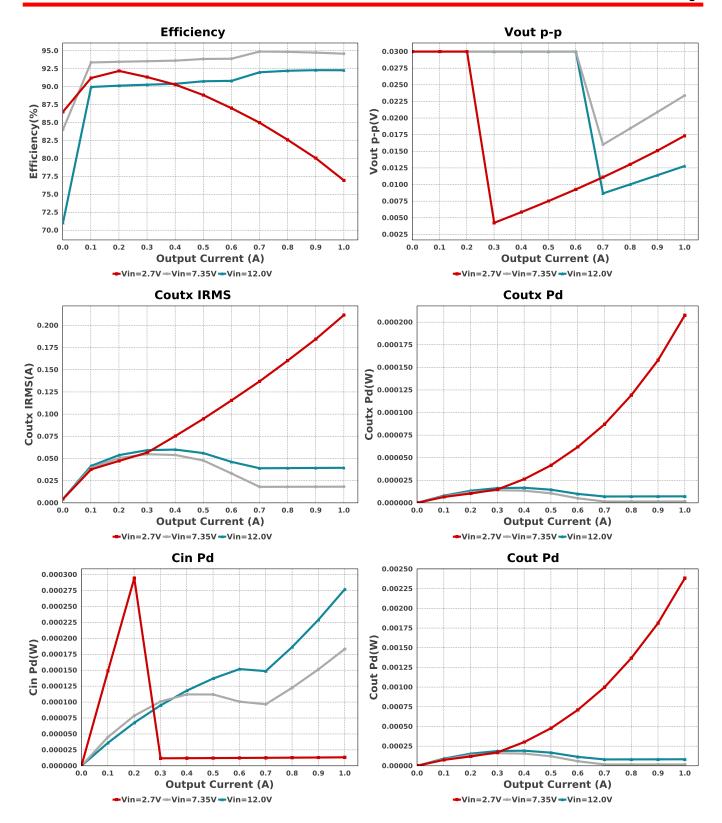

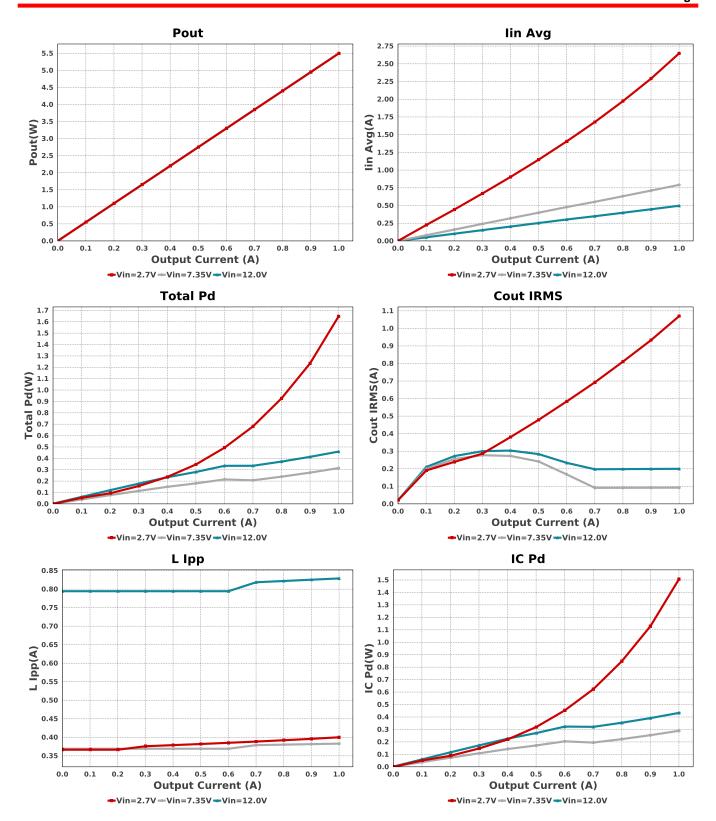

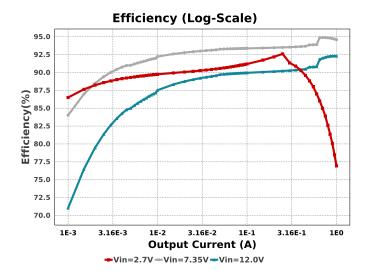

### **Operating Values**

#	Name	Value	Category	Description
1.	Cin IRMS	115.482 mA	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	13.336 μW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	1.069 A	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	0.0 W	Capacitor	Output capacitor power dissipation
5.	Coutx IRMS	211.425 mA	Capacitor	Output capacitor_x RMS ripple current
6.	Coutx Pd	0.0 W	Capacitor	Output capacitor_x power loss
7.	IC lpk	2.837 A	IC '	Peak switch current in IC
8.	IC Pd	1.504 W	IC	IC power dissipation
9.	IC Ti	124.751 degC	IC	IC junction temperature
10.	ICThetaJA	63.0 degC/W	iC	IC junction-to-ambient thermal resistance
11.	lin Avg	2.646 A	IC	Average input current
12.	L lpp	400.04 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	139.34 mW	Inductor	Inductor power dissipation
-		13.336 µW	Power	Input capacitor power dissipation
15.	Cout Pd	0.0 W	Power	Output capacitor power dissipation
16.	Coutx Pd	0.0 W		
			Power	Output capacitor_x power loss
17.		1.504 W	Power	IC power dissipation
	L Pd	139.34 mW	Power	Inductor power dissipation
19.	Total Pd	1.643 W	Power	Total Power Dissipation
20.	BOM Count	11	System	Total Design BOM count
			Information	
21.	Duty Cycle	62.196 %	System	Duty cycle
			Information	
22.	Efficiency	76.994 %	System	Steady state efficiency
			Information	
23.	FootPrint	174.0 mm <sup>2</sup>	System	Total Foot Print Area of BOM components
			Information	
24.	Frequency	2.5 MHz	System	Switching frequency
			Information	
25.	lout	1.0 A	System	lout operating point
			Information	
26.	Mode	BOOST PWM CCM	System	PWM/PFM Mode
			Information	
27.	Pout	5.5 W	System	Total output power
	1 001	0.0 11	Information	Total output porror
28.	Rload_crit	40.9 Ohm	System	Minimum Rload required during Start up
20.	Moad_cm	40.9 OIIII	Information	William Rioda required during Start up
29.	Total BOM	\$3.22	System	Total BOM Cost
29.	TOTAL BOW	φ3.22	•	Total Bolvi Cost
20	\ /:	0.7.1/	Information	Via an austina a sint
30.	Vin	2.7 V	System	Vin operating point
0.1		5.50.1/	Information	
31.	Vout Actual	5.52 V	System	Vout Actual calculated based on selected voltage divider resistors
			Information	
32.	Vout Tolerance	1.727 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divide
			Information	resistors if applicable
33.	Vout p-p	13.815 mV	System	Peak-to-peak output ripple voltage

## **Design Inputs**

Name	Value	Description	
lout	1.0	Maximum Output Current	

Name	Value	Description	
VinMax	12.0	Maximum input voltage	
VinMin	2.7	Minimum input voltage	
Vout	5.5	Output Voltage	
base_pn	TPS63070	Base Product Number	
source	DC	Input Source Type	
Ta	30.0	Ambient temperature	

## WEBENCH® Assembly

#### Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of Cin and Cout, and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

#### Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab town to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

#### Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 2.7V and set the input supply's current limit to zero. With the input supply off connect up the input supply to Vin and GND. Connect a digital volt meter and a load if needed to set the minimum lout of the design from Vout and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.
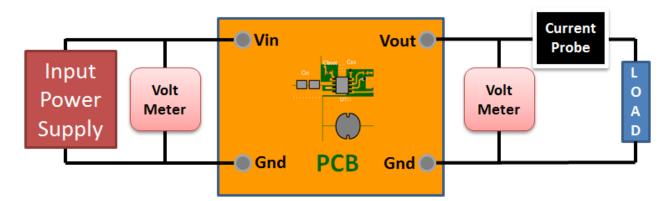
#### Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between Vin and GND, a load is connected between Vout and GND and a current meter is connected in series between Vout and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



#### **Design Assistance**

- 1. Master key: 41E8874367B5AA92[v1]
- 2. TPS63070 Product Folder: http://www.ti.com/product/TPS63070: contains the data sheet and other resources.

#### Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.