## **Experiment 3:**

Vbat / P+:0V no battery connected

Vin / PCHG+: 0V -> 21V (regular state).

We expect the LM9061 to open the output.

Figure 1:

CH1: PCHG+

CH2: P+


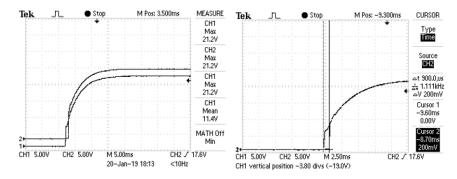


Figure 2:

CH1: PCHG+


CH2: Gate of Q14

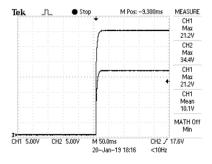

## Figure 3:

CH1: PCHG+

CH2: DELAY pin of LM9061

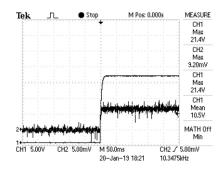

## **Experiment 2:**

Vbat / P+:0V no battery connected


Vin / PCHG+: 0V -> 30V (OVP mode).

We expect the LM9061 **not** to open the output.

Figure 1:

CH1: PCHG+

CH2: P+

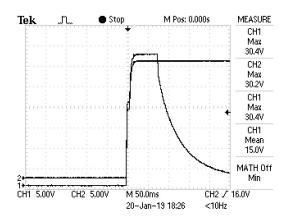


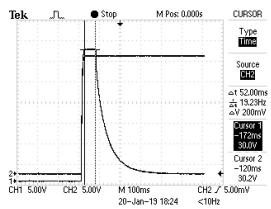


Figure 2:

CH1: PCHG+

CH2: Gate of Q14

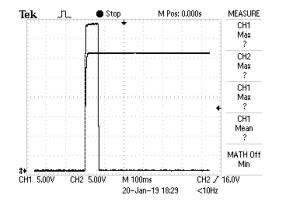

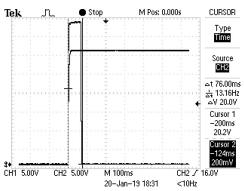


Figure 3:

CH1: PCHG+

CH2: DELAY pin of LM9061

