

Input to Output Isolation for the TPS61170

Jeff Falin

ABSTRACT

Many boost converters have an external rectifier diode. The input voltage of the TPS61170 main boost converter is connected to the output voltage when the device is disabled. Due to the direct pass from the input to the output, the input supply is not isolated from the output voltage when the IC is disabled. This application report describes how to use a **PMOS** transistor to disconnect the boost converter's input voltage from the output voltage (known as load disconnect or input to output isolation) when the device is disabled.

Figure 1 shows the schematic for a TPS61170EVM (SLVU222) that has been modified to include a PMOS transistor $Q_{(LD)}$, and a resistor $R_{(LD)}$ which form the load disconnect circuit. Capacitor $C_{(LD)}$ is the minimum capacitor necessary for control loop stability, and C_5 represents additional load capacitance.

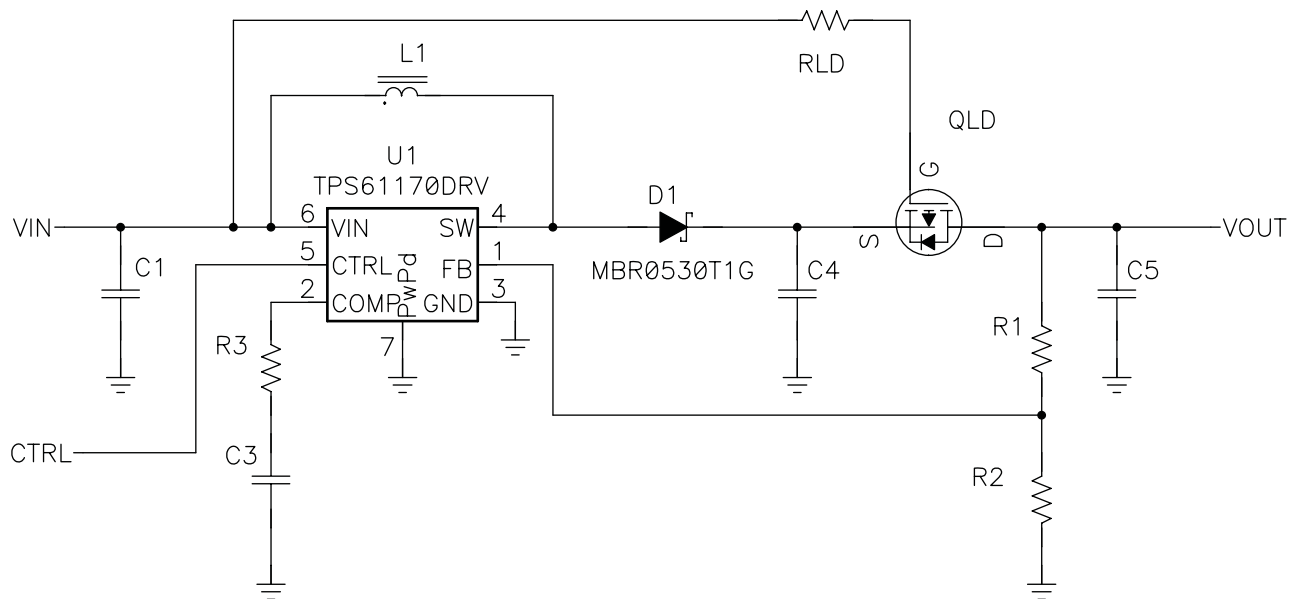


Figure 1. TPS61170 with Input to Output Isolation

The boost converter's diode is connected to the source of $Q_{(LD)}$, but the feedback network and output capacitor are connected after $Q_{(LD)}$. This allows a regulated output voltage even with the use of the transistor $Q_{(LD)}$. Select $Q_{(LD)}$ to have the following characteristics:

1. a V_{SD} breakdown voltage higher than V_{OUT}
2. a V_{GS} breakdown voltage higher than $V_{OUT} - V_{INmin}$
3. a low drain to source resistance ($R_{DS(on)}$) such that the voltage drop created by the maximum output current (I_{Omax}) times $R_{DS(on)}$ does not take the output voltage below the required minimum regulated voltage for the application.

Capacitor C4 provides a defined bias operation point for $Q_{(LD)}$ and can should be in the 0.1 μ F to 1 μ F range. $R_{(LD)}$ of approximately 100 Ω is recommended to prevent the input voltage from capacitively coupling to the boost converter output. Using Figure 1 with $V_{IN} = 5V$ and V_{OUT} set to 24 V by R1 and R2, and $R_{LOAD} = 240 \Omega$ ($I_{OUT} = 100$ mA), Figure 2 shows the circuit starting up while Figure 3 shows the circuit at shutdown. In both figures, CH1 shown in yellow and set to 5 V/div, shows output voltage before $Q_{(LD)}$, CH2 shown in pink and set to 5 V/div, shows the output voltage after $Q_{(LD)}$, and CH3 shown in blue, shows CTRL.

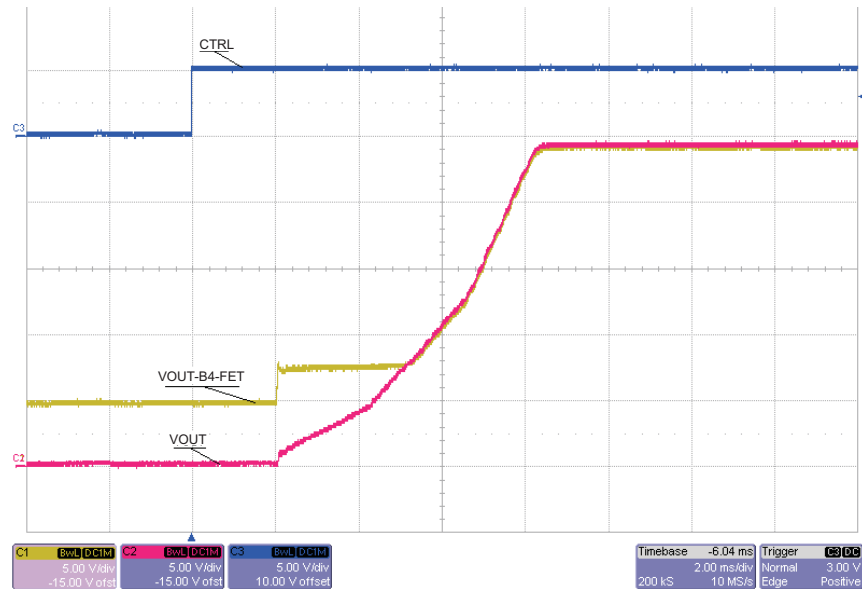


Figure 2. TPS61170 with Input to Output Isolation at Startup

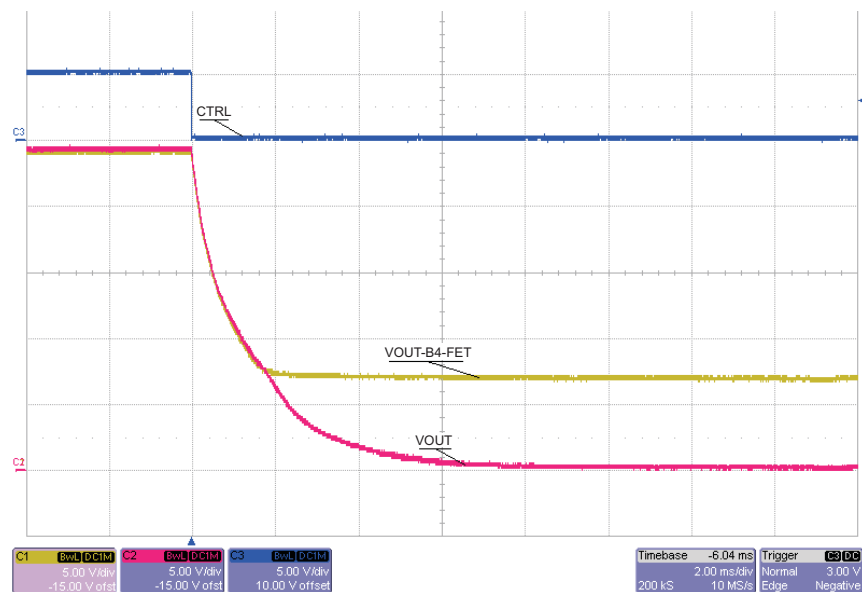


Figure 3. TPS61170 with Input to Output Isolation at Shutdown

Note that the load regulation at large loads is degraded by the $I_{OUT} \times R_{DS(on)}$ drop across the FET, i.e.,

$$V_{OUT} = V_{REF} \times (1 + R1/R2) - I_{OUT} \times R_{DS(on)}$$

Note also that efficiency will be degraded slightly due to the $I_{OUT}^2 \times R_{DS(on)}$ additional power loss across the FET, i.e. $\eta = ((V_{REF} \times (1 + R1/R2) - I_{OUT} \times R_{DS(on)}) \times I_{OUT}) / (V_{IN} \times I_{IN})$. In this example, the Si2343 -30-V PFET with $R_{DS(on)} = 45 \text{ m}\Omega$ at $V_{GS} = 10\text{V}$ was used. So, with $V_{IN} = 12\text{V}$, the change in load regulation and efficiency is negligible. At lower input voltages, higher currents, or when using FETs with higher $R_{DS(on)}$, the degradation in load regulation and efficiency is more apparent.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video
Wireless	www.ti.com/wireless-apps

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated