
VinMin = 26.0V VinMax = 30.0V Vout = 6.5V Iout = 1.0A Device = LM26003QMHX/NOPB Topology = Buck Created = 2022-07-23 05:08:39.775 BOM Cost = \$3.00 BOM Count = 17 Total Pd = 0.68W

WEBENCH® Design Report

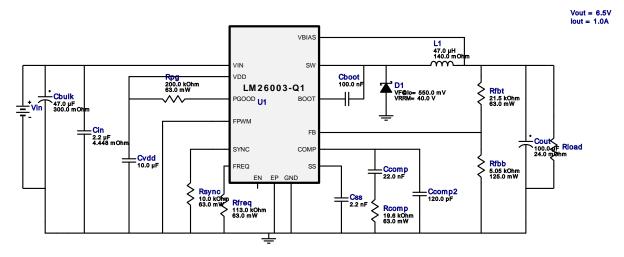Design: 5 LM26003QMHX/NOPB LM26003QMHX/NOPB 26V-30V to 6.50V @ 1A



1. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.

Design Alerts


Component Selection Information

The LM26003-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application.


Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cboot	AVX	08053C104JAZ2A Series= X7R	Cap= 100.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.06	0805 7 mm ²
Cbulk	Panasonic	EEE-FC1H470P Series= FC	Cap= 47.0 uF ESR= 300.0 mOhm VDC= 50.0 V IRMS= 500.0 mA	1	\$0.22	SM_RADIAL_G 172 mm ²
Ccomp	TDK	CGA4J2C0G1H223J125AA Series= C0G/NP0	Cap= 22.0 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.08	0805 7 mm ²
Ccomp2	Samsung Electro- Mechanics	CL21C121JBANNNC Series= C0G/NP0	Cap= 120.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
Cin	MuRata	GRM31CR61H225KA88L Series= X5R	Cap= 2.2 uF ESR= 4.448 mOhm VDC= 50.0 V IRMS= 2.2252 A	1	\$0.10	1206_190 11 mm ²
Cout	Panasonic	16SVPC100M Series= SVPC	Cap= 100.0 uF ESR= 24.0 mOhm VDC= 16.0 V IRMS= 2.49 A	1	\$0.30	SM_RADIAL_6.3AMM 80 mm²


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Css	Samsung Electro- Mechanics	CL21C222JBFNNNE Series= C0G/NP0	Cap= 2.2 nF VDC= 50.0 V IRMS= 0.0 A	1	\$0.03	0805 7 mm ²
Cvdd	Samsung Electro- Mechanics	CL10A106MQ8NNNC Series= X5R	Cap= 10.0 uF VDC= 6.3 V IRMS= 0.0 A	1	\$0.02	0603 5 mm ²
D1	Fairchild Semiconductor	SS14FL	VF@Io= 550.0 mV VRRM= 40.0 V	1	\$0.04	SOD-123F 12 mm ²
L1	NIC Components	NPI31W470MTRF	L= 47.0 μH 140.0 mOhm	1	\$0.24	
						IND_NPI31W 172 mm ²
Rcomp	Vishay-Dale	CRCW040219K6FKED Series= CRCWe3	Res= 19.6 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rfbb	Yageo	RT0805BRD075K05L Series= ?	Res= 5.05 kOhm Power= 125.0 mW Tolerance= 0.1%	1	\$0.06	0805 7 mm ²
Rfbt	Vishay-Dale	CRCW040221K5FKED Series= CRCWe3	Res= 21.5 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rfreq	Vishay-Dale	CRCW0402113KFKED Series= CRCWe3	Res= 113.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rpg	Vishay-Dale	CRCW0402200KFKED Series= CRCWe3	Res= 200.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rsync	Vishay-Dale	CRCW040210K0FKED Series= CRCWe3	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
U1	Texas Instruments	LM26003QMHX/NOPB	Switcher	1	\$1.78	•

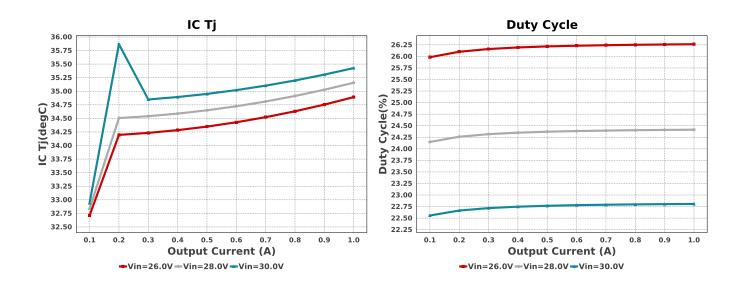

MXA20A 71 mm²

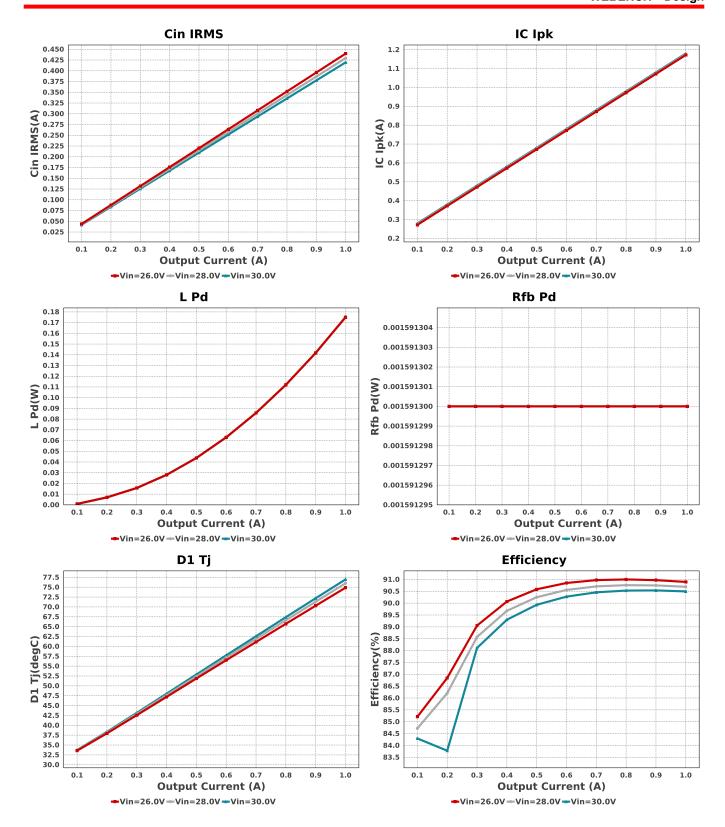

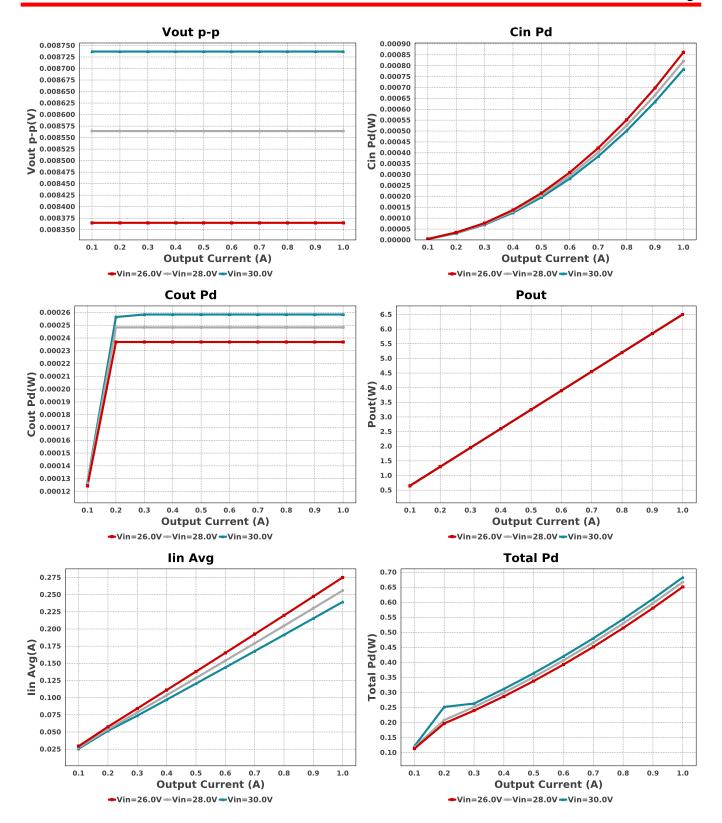

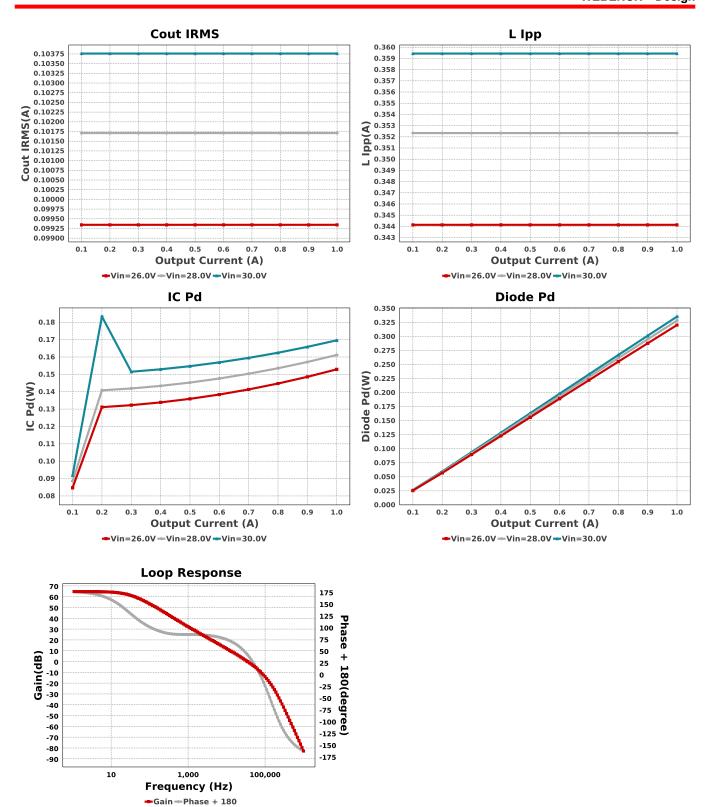

Operating Values

		9			
	#	Name	Value	Category	Description
-	1.	Cin IRMS	419.587 mA	Capacitor	Input capacitor RMS ripple current
	2.	Cin Pd	783.09 μW	Capacitor	Input capacitor power dissipation
	3.	Cout IRMS	103.76 mA	Capacitor	Output capacitor RMS ripple current
	4.	Cout Pd	258.39 μW	Capacitor	Output capacitor power dissipation
	5.	D1 Tj	76.968 degC	Diode	D1 junction temperature
	6.	Diode Pd	335.49 mW	Diode	Diode power dissipation
	7.	IC lpk	1.18 A	IC	Peak switch current in IC
	8.	IC Pd	169.6 mW	IC	IC power dissipation
	9.	IC Tj	35.427 degC	IC	IC junction temperature
	10.	ICThetaJA	32.0 degC/W	IC	IC junction-to-ambient thermal resistance
	11.	lin Avg	239.42 mA	IC	Average input current

#	Name	Value	Category	Description
12.	L Ipp	359.44 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	175.0 mW	Inductor	Inductor power dissipation
14.	Cin Pd	783.09 µW	Power	Input capacitor power dissipation
15.	Cout Pd	258.39 µW	Power	Output capacitor power dissipation
16.	Diode Pd	335.49 mW	Power	Diode power dissipation
17.	IC Pd	169.6 mW	Power	IC power dissipation
18.	L Pd	175.0 mW	Power	Inductor power dissipation
19.	Rfb Pd	1.591 mW	Power	Rfb Power Dissipation
20.	Total Pd	682.706 mW	Power	Total Power Dissipation
21.	Rfb Pd	1.591 mW	Resistor	Rfb Power Dissipation
22.	BOM Count	17	System	Total Design BOM count
			Information	3
23.	Cross Freq	35.265 kHz	System	Bode plot crossover frequency
			Information	,
24.	Duty Cycle	22.807 %	System	Duty cycle
	., ., .		Information	.,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,
25.	Efficiency	90.495 %	System	Steady state efficiency
	,		Information	,,
26.	FootPrint	572.0 mm ²	System	Total Foot Print Area of BOM components
		072.0 111111	Information	
27.	Frequency	324.583 kHz	System	Switching frequency
	- 1 7		Information	3 1,111,
28.	Gain Marg	-9.404 dB	System	Bode Plot Gain Margin
	J		Information	•
29.	lout	1.0 A	System	lout operating point
			Information	
30.	Low Freq Gain	64.701 dB	System	Gain at 1Hz
	·		Information	
31.	Mode	SleepMode	System	Conduction Mode
			Information	
32.	Phase Marg	43.171 deg	System	Bode Plot Phase Margin
			Information	
33.	Pout	6.5 W	System	Total output power
			Information	
34.	Total BOM	\$3.0	System	Total BOM Cost
			Information	
35.	Vin	30.0 V	System	Vin operating point
			Information	
36.	Vout	6.5 V	System	Operational Output Voltage
			Information	
37.	Vout Actual	6.498 V	System	Vout Actual calculated based on selected voltage divider resistors
			Information	
38.	Vout Tolerance	2.443 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider
			Information	resistors if applicable
39.	Vout p-p	8.737 mV	System	Peak-to-peak output ripple voltage
			Information	

Design Inputs

Name	Value	Description
lout	1.0	Maximum Output Current
VinMax	30.0	Maximum input voltage
VinMin	26.0	Minimum input voltage
VinTyp	28.0	Typical input voltage
Vout	6.5	Output Voltage
base_pn	LM26003-Q1	Base Product Number
source	DC	Input Source Type
Та	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of Cin and Cout, and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab town to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 26.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to Vin and GND. Connect a digital volt meter and a load if needed to set the minimum lout of the design from Vout and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between Vin and GND, a load is connected between Vout and GND and a current meter is connected in series between Vout and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

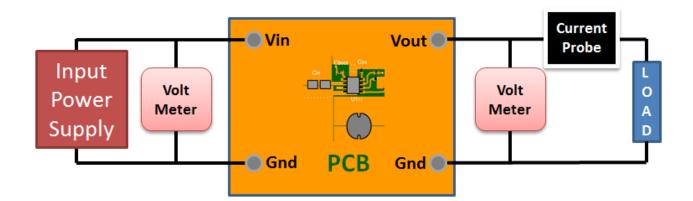

WEBENCH® Electrical Simulation Report


Design Id = 5

 $sim_id = 1$

Simulation Type = Bode Plot

Simulation Parameters

#	Name	Parameter Name	Description	Values	
1.	Cinj	С	Injection Isolation Capacitance	100 F	
2.	Linj	L	Injection Isolation Inductance	100 H	
3.	Vinj	AC	AC Voltage Source Amplitude	1 V	
4.	Rload	R	Load Resistance	6.5 Ohm	

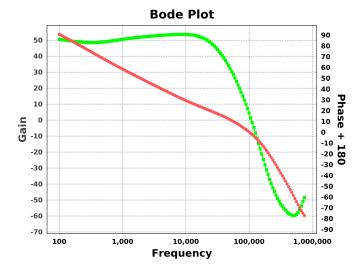

Design Assistance

- 1. The LM26003-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application
- 2. Master key: 82F3BB5AD0B953A69044792478707C05[v1]
- 3. LM26003-Q1 Product Folder: http://www.ti.com/product/LM26003%2DQ1: contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.