



**ON Semiconductor®**

# The Dark Side of Flyback Converters

Presented by Christophe Basso

Senior Scientist  
IEEE Senior Member



---

# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?
- More Power than Needed
- The Frequency Response
- Compensating With the TL431




# What is the Subject?

- ❑ There has been numerous seminars on Flyback converters
- ❑ Seminars are usually highly theoretical – link to the market?
- ❑ Industrial requirements usually not covered
- ❑ This 3-hour seminar will shed lights on less covered topics:
  - ❖ Why the converter delivers more power than expected? Solutions?
  - ❖ Books talk about compensation with op amps, I have a TL431!
  - ❖ The origin of the Right-Half Plane Zero, how do I deal with it?
  - ❖ Quasi-resonant converters presence increases, how do they work?
- In a 3-hour course, we are just scratching the surface...!


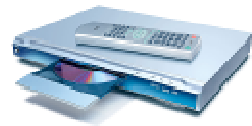
# The Flyback, a Popular Structure

- ❑ The flyback converter is widely used in consumer products
- ✓ Ease of design, low-cost, well-known structure
- Poor EMI signature, bulky transformer, practical up to 150 W



*DVD player*  
→  
*Set-top box*

flyback  $\approx$  10 – 35 W



→  
*Charger*

flyback  $\approx$  3 – 5 W




→  
*Notebook*  
*Netbook*

flyback  $\approx$  40 – 180 W



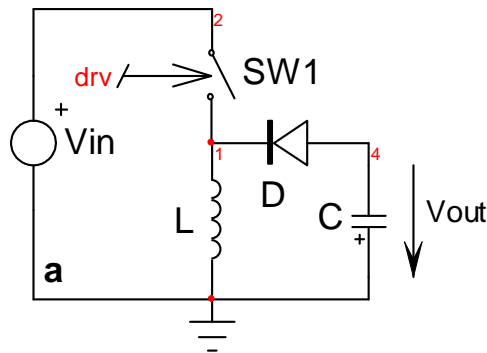
# An Isolated Buck-Boost


- The flyback converter is derived from the buck-boost cell



buck-boost  
ground referenced

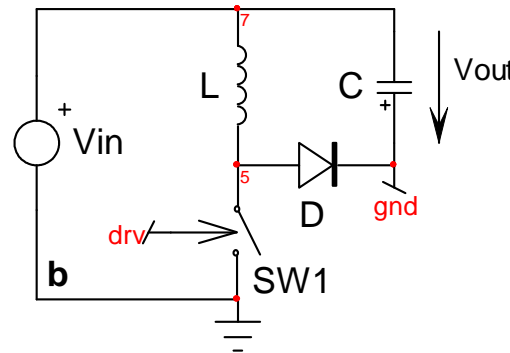


buck-boost  
input referenced

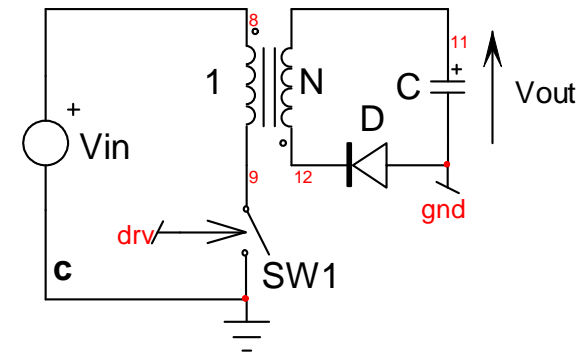

flyback  
isolated ground referenced

- The addition of a transformer brings:

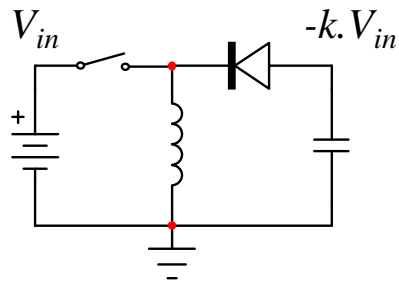

+





- Up or down scale  $V_{in}$
- Isolation
- Polarity change
- More than 1 output


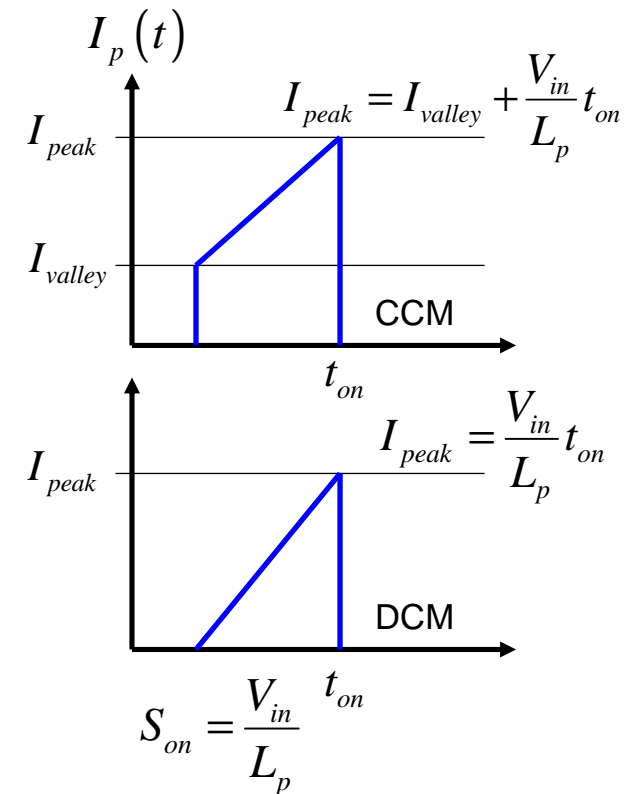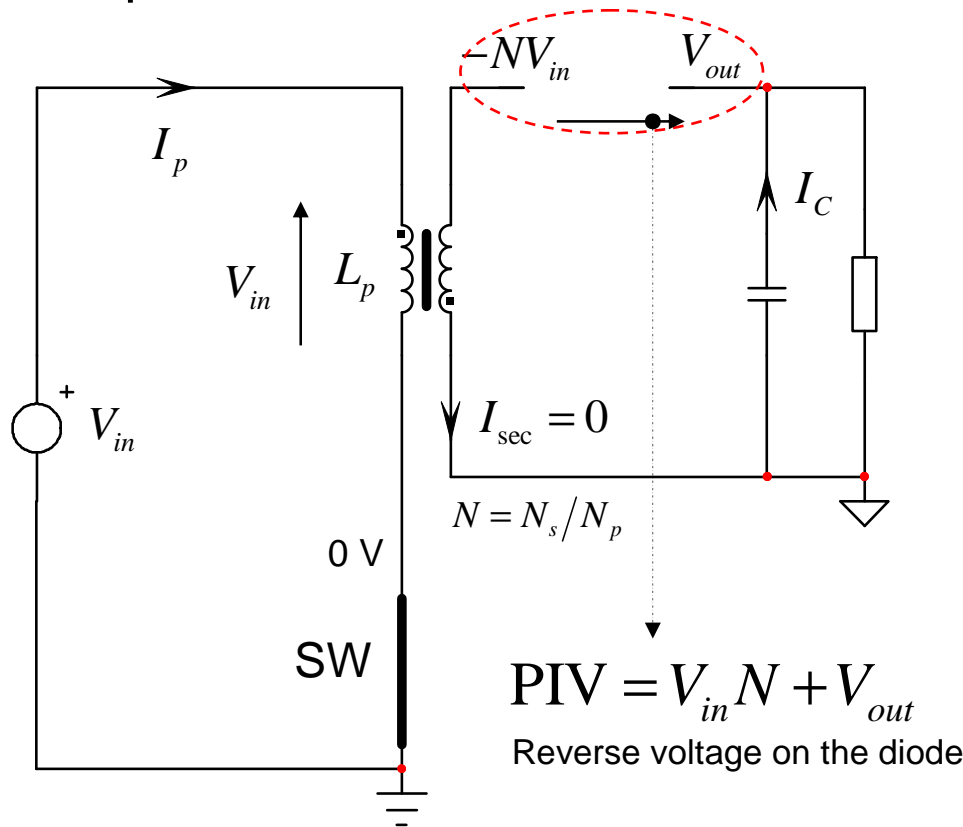
# The Turn-on Event

- The power switch turns on: current ramps up in  $L_p$ ,  $D$  is blocked




- The current increases in the inductor in relationship to  $V_{in}$  and  $L_p$
- The output capacitor supplies the load on its own

Simplified, no leakage


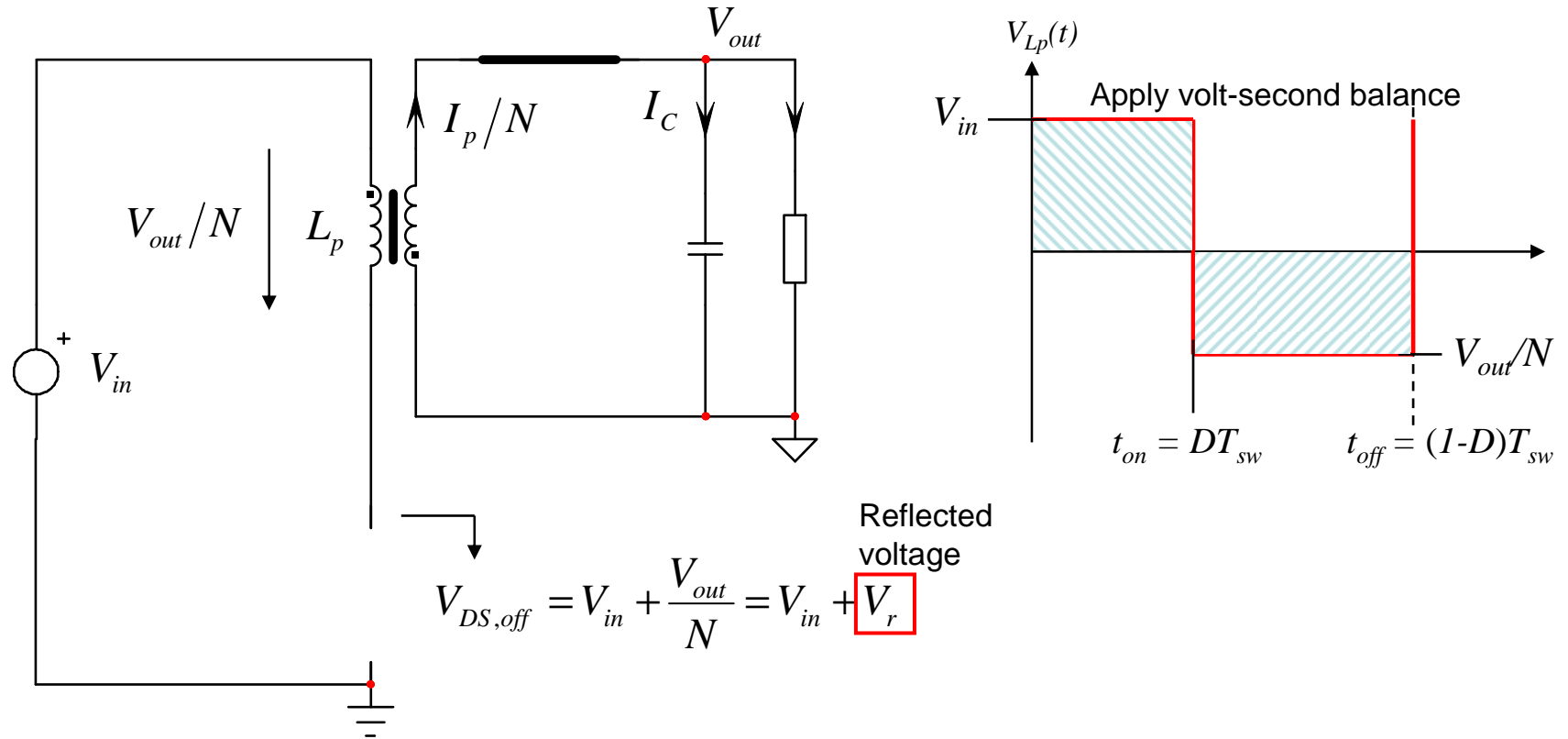
# Applying Volt-Second Balance, CCM

- The power switch turns off:  $D$  conducts,  $V_{out}$  "flies" back





$$\frac{V_{out}}{V_{in}} = \frac{Nt_{on}}{t_{off}} = \frac{NDT_{sw}}{(1-D)T_{sw}} = \frac{ND}{1-D}$$

dc transfer function in CCM
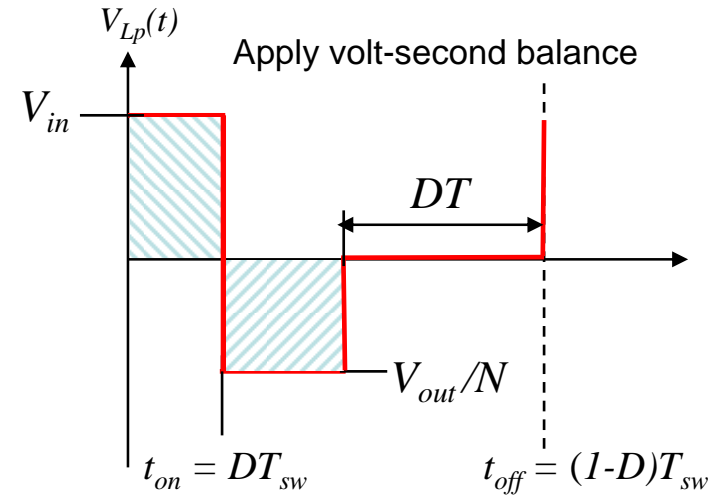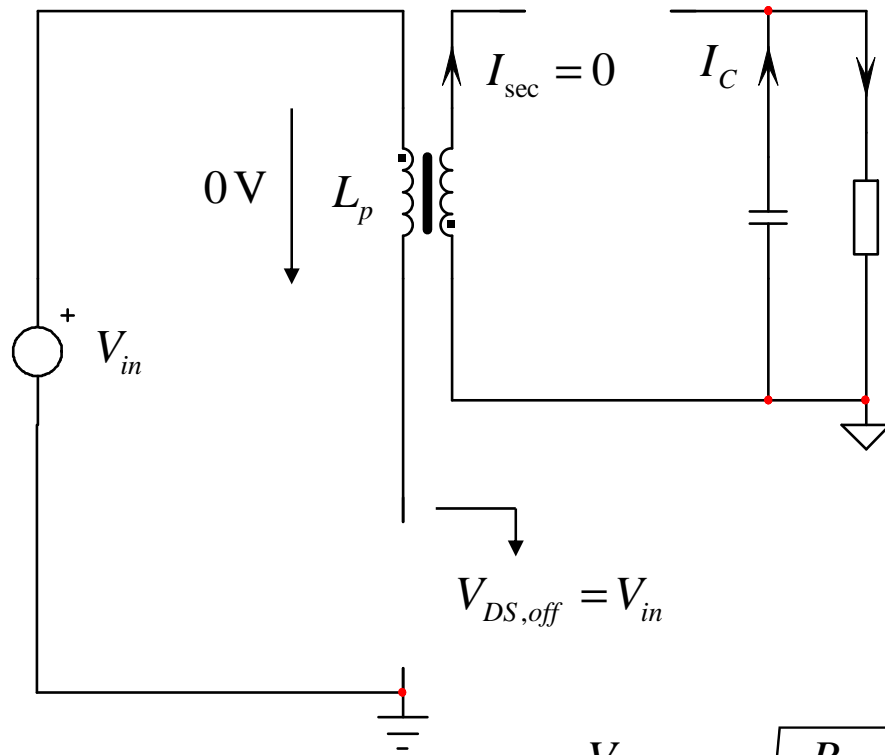
# Applying Volt-Second Balance, DCM

- In DCM, when  $L_p$  is fully depleted  $D$  opens:  $V_{out}$  reflection is lost



$$\frac{V_{out}}{V_{in}} = D \sqrt{\frac{R_{load}}{2L_p F_{sw}}}$$

dc transfer function in DCM


$N$  no longer plays a role  
 $R_{load}$ ,  $L_p$  and  $F_{sw}$  do







# Flyback, Typical Waveforms, CCM

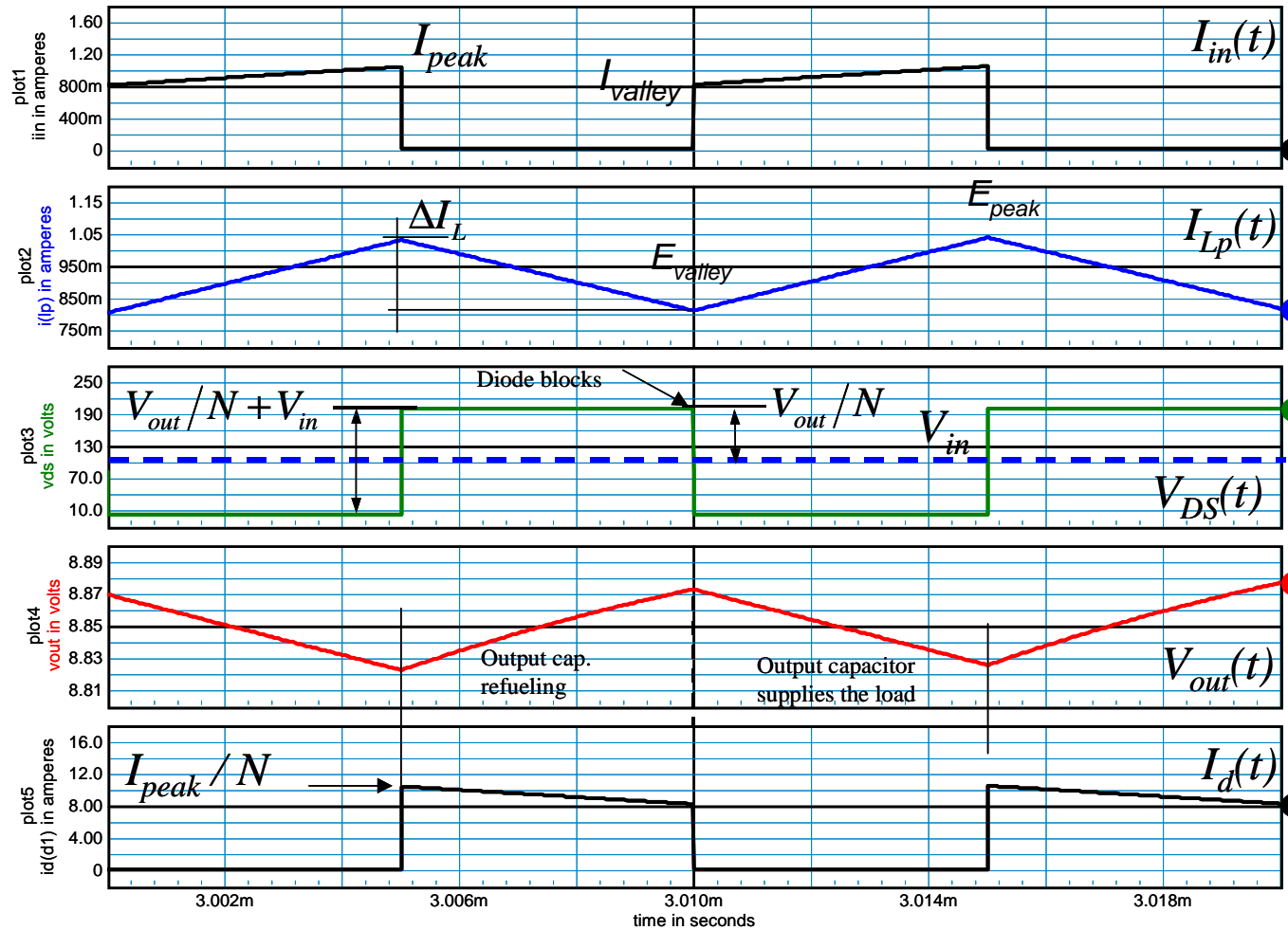

Input current

Inductor current

Drain voltage


Output voltage

Diode current

CCM flyback – no parasitics



# Flyback, Typical Waveforms, DCM

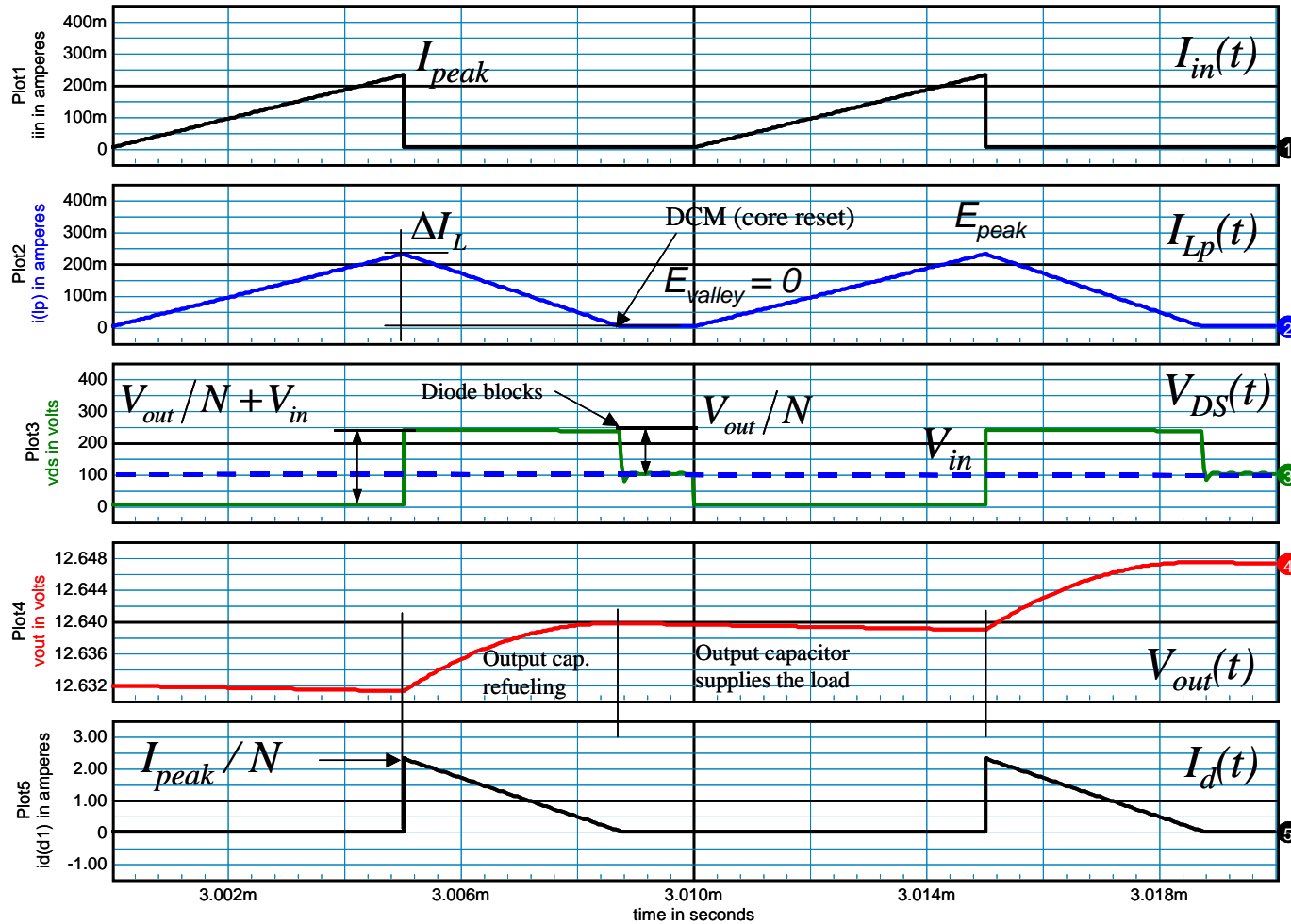

Input current

Inductor current

Drain voltage

Output voltage

Diode current

DCM flyback – no parasitics



# Energy Transfer in CCM and DCM

- The primary inductance,  $L_p$ , stores and releases energy

$$E_{L_p, valley} = \frac{1}{2} L_p I_{valley}^2 \quad \text{Initially stored energy}$$

$$E_{L_p, peak} = \frac{1}{2} L_p I_{peak}^2 \quad \text{Stored energy at } t_{on}$$

$$E_{L_p, trans} = \frac{1}{2} L_p I_{peak}^2 - \frac{1}{2} L_p I_{valley}^2 = \frac{1}{2} L_p (I_{peak}^2 - I_{valley}^2) \quad \text{Transmitted energy at } T_{sw}$$

- Power (W) is energy (J) averaged over time (s):

$$P_{out} = \frac{1}{2} (I_{peak}^2 - I_{valley}^2) L_p F_{sw} \eta \quad \text{CCM}$$

Eta, the efficiency

$$P_{out} = \frac{1}{2} I_{peak}^2 L_p F_{sw} \eta \quad \text{DCM, } I_{valley} = 0$$



---


# Course Agenda

- The Flyback Converter
- The Parasitic Elements**
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?
- More Power than Needed
- The Frequency Response
- Compensating With the TL431



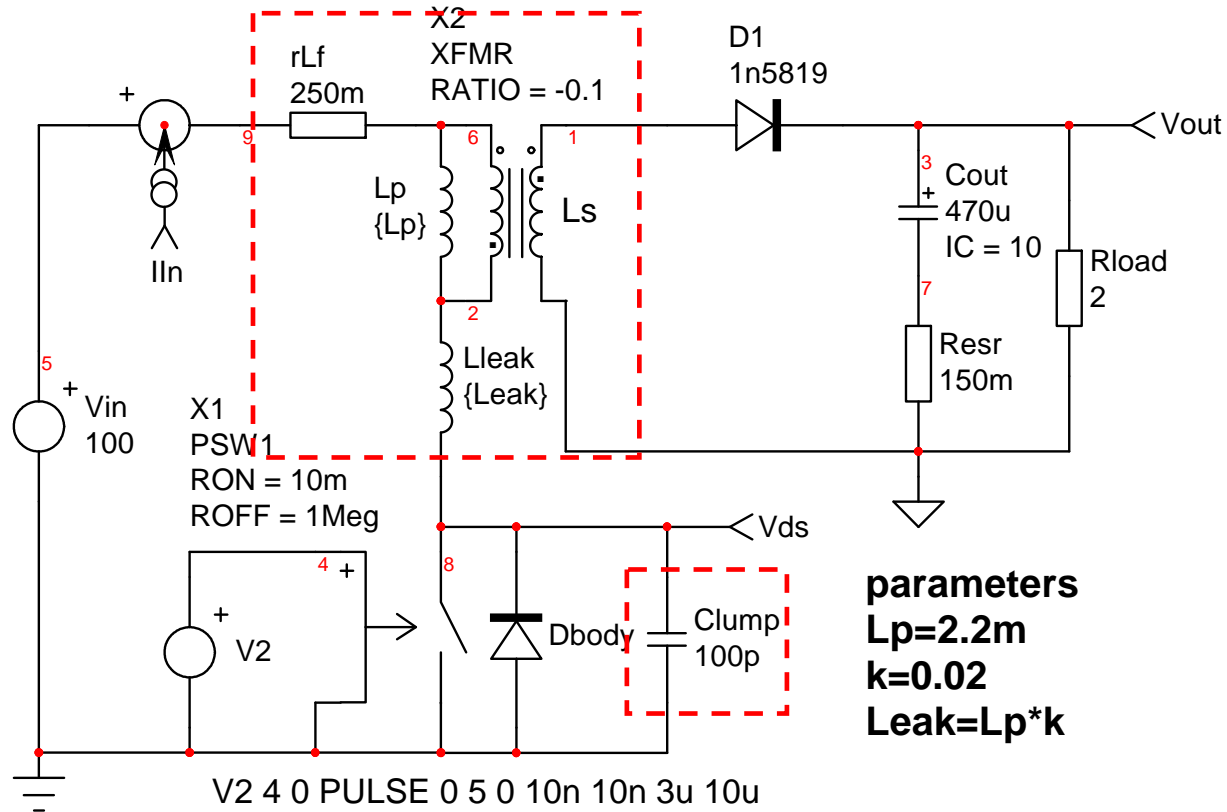
# Considering Parasitic Elements

- The transformer and the MOSFET include parasitics



With parasitics

# Considering Parasitic Elements, CCM

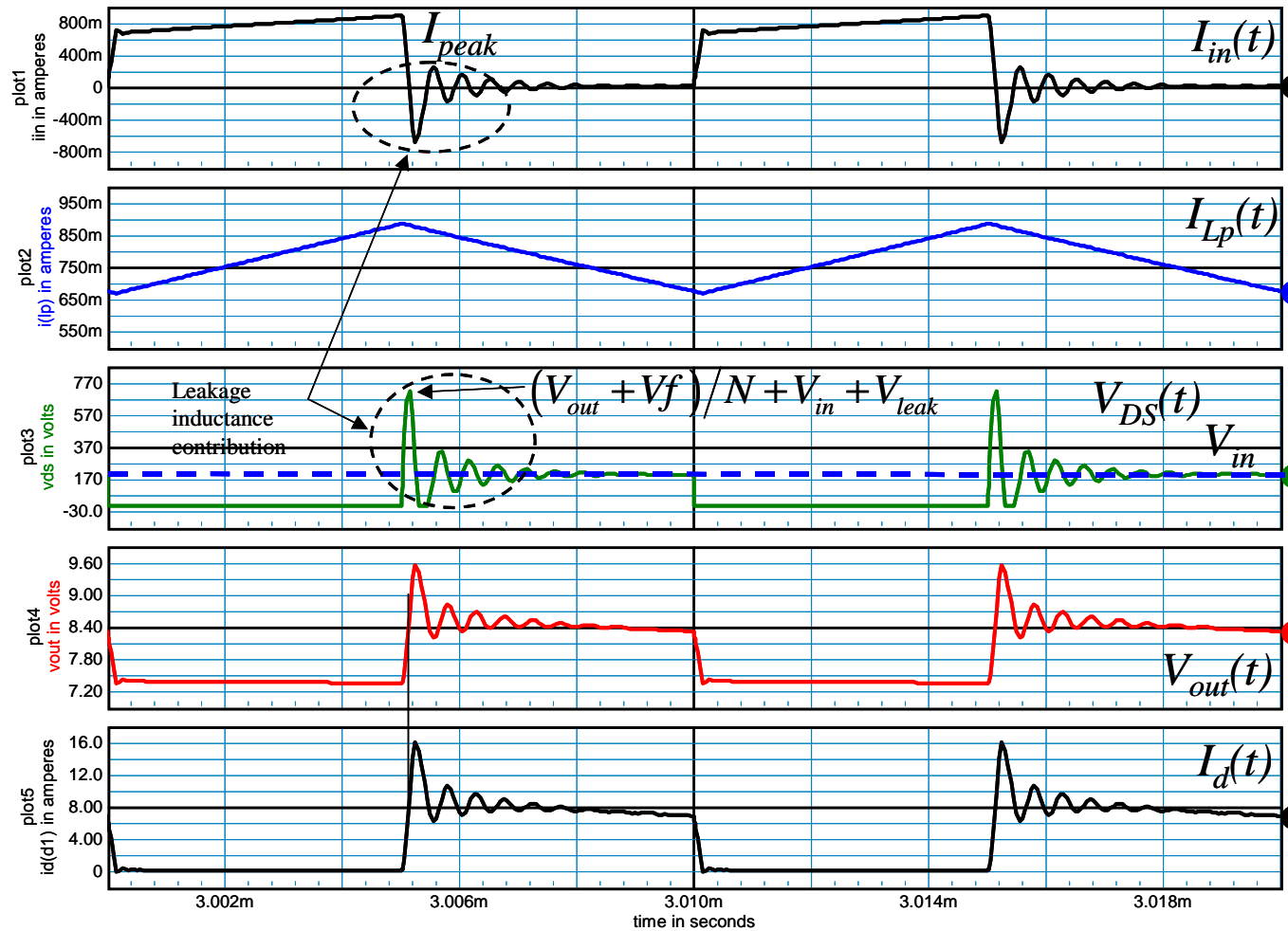

Input current

Inductor current

Drain voltage


Output voltage

Diode current

CCM mode – with parasitics



# Considering Parasitic Elements, DCM

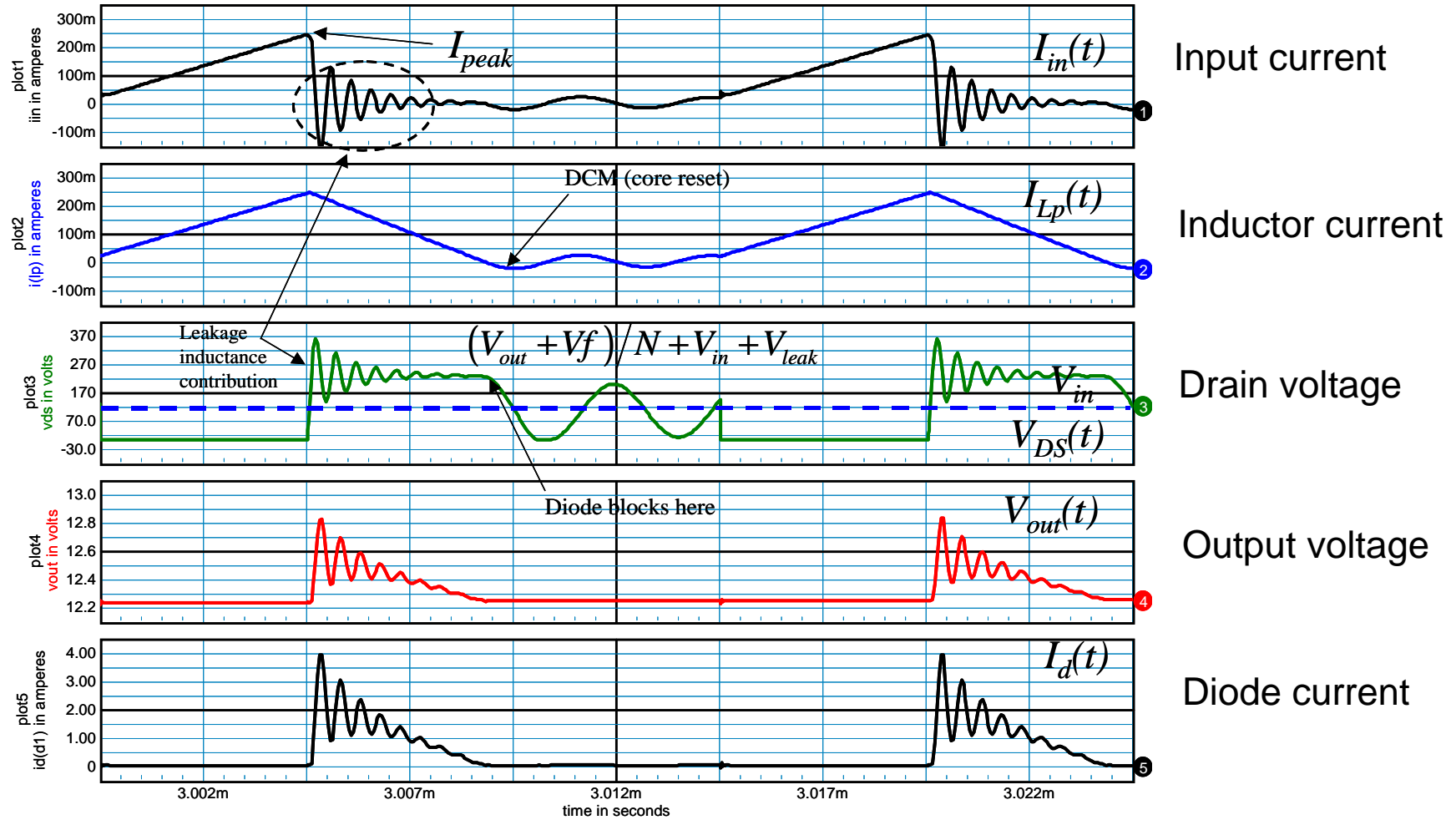


DCM mode – with parasitics






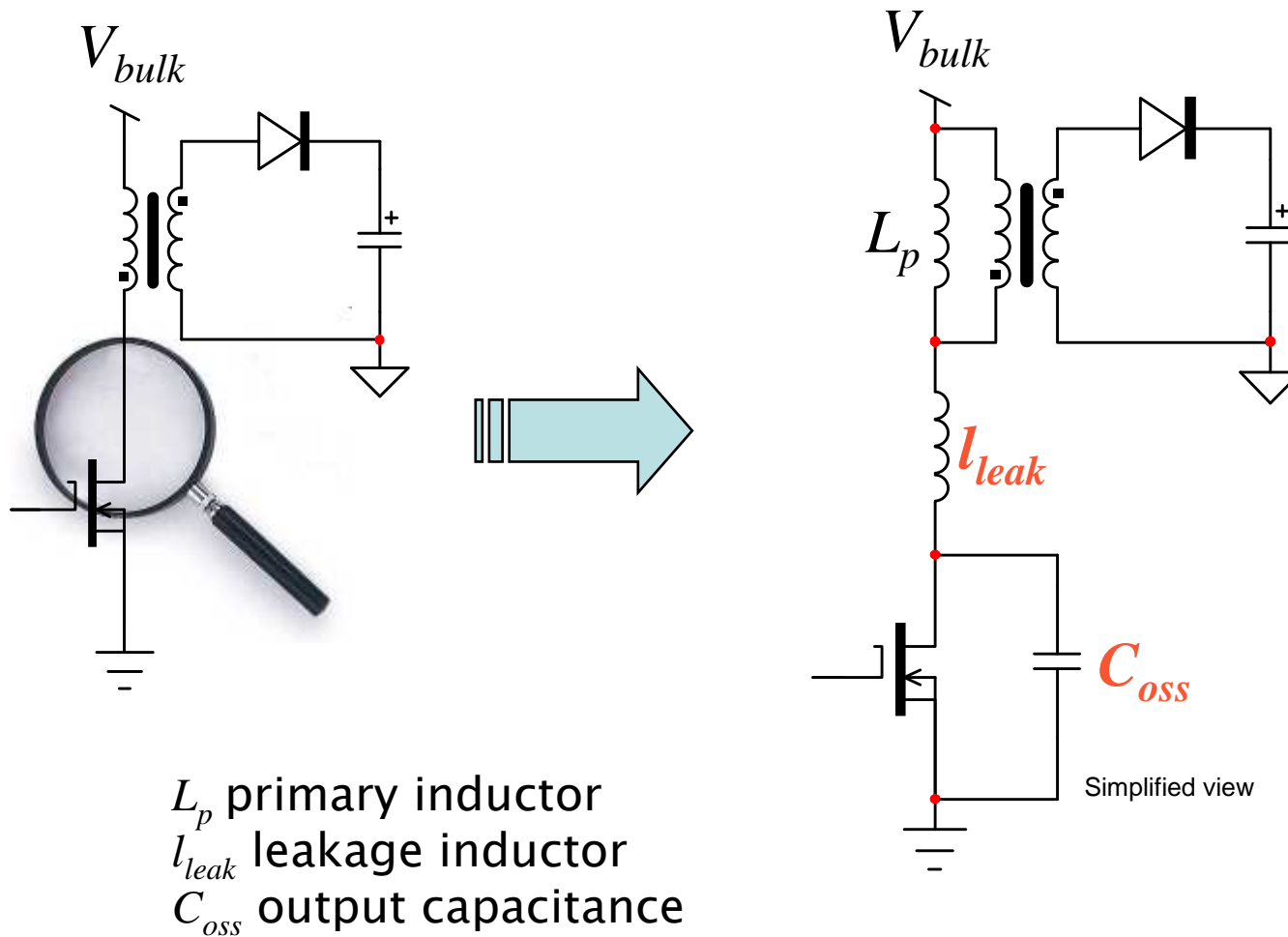
# Who Are the Stray Elements?

- The study of the drain node reveals a *LC* network


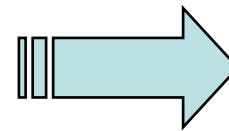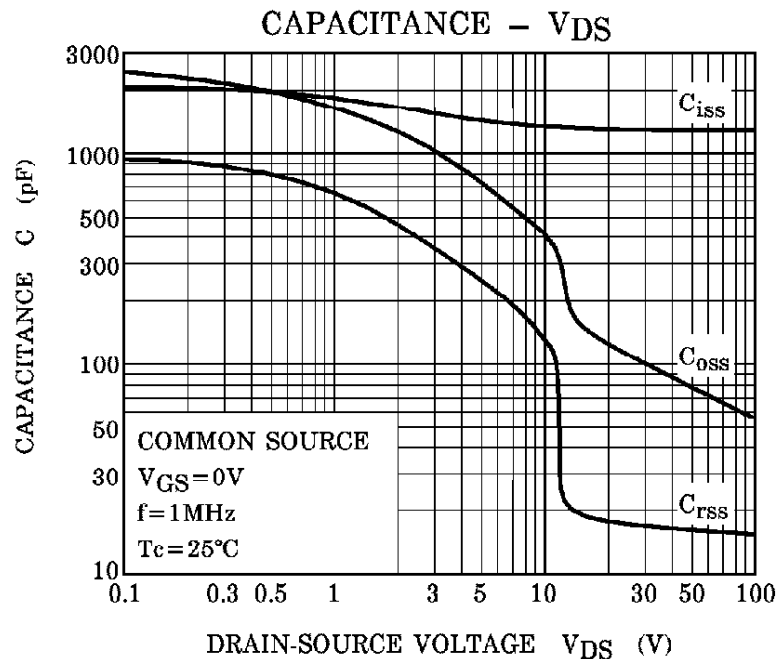
# The MOSFET $C_{OSS}$ is a Non-Linear Device

- ❑ The capacitor value changes with its bias voltage



$$C_{OSS}(V_{DS}) = \frac{C_{D0}}{\sqrt{\left(1 + \frac{V_{DS}}{V_0}\right)}}$$


$C_{D0}$  is the cap. for  $V_{DS} = V_0$

- ❑ Since bias affects the capacitor value:

~~$$W = \frac{1}{2} C_{OSS} V_{DS}^2$$~~
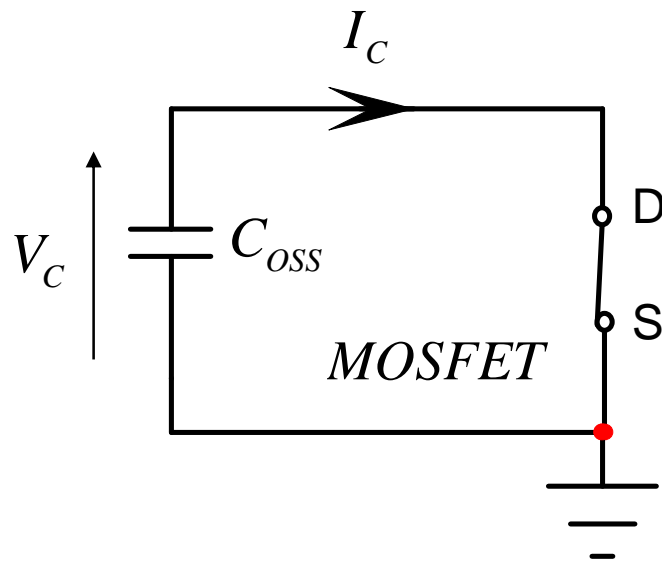
# As the Voltage Decreases, $C_{OSS}$ Value Changes

- ❑ The brutal discharge generates switching losses



$$I_C(t) = C \frac{dV_C(t)}{dt} \quad W = \int_0^t I_C(t) V_C(t) \cdot dt$$

$$W = \int_0^t C \frac{dV_{DS}(t)}{dt} V_{DS}(t) \cdot dt = \int_0^{V_{DS}} C(V_{DS}) V_{DS} \cdot dV_{DS}$$

$$C_{OSS}(V_{DS}) \approx \frac{C_{D0} \sqrt{V_0}}{\sqrt{V_{DS}}}$$

$$W = \frac{2}{3} V_{DS}^{3/2} C_{D0} \sqrt{V_0}$$

↑  
At turn-off

- ❑ The lost energy is smaller than with the non-linear variation!

# Using the Raw $C_{OSS}$ is an ... Overkill

- Re-compute the capacitor from the MOSFET data-sheet

Input Capacitance	$C_{iss}$	$V_{DS}=10V, V_{GS}=0V, f=1MHz$ $V_{D0}$	—	1300	—	pF
Reverse Transfer Capacitance	$C_{rss}$		—	130	—	
Output Capacitance	$C_{oss}$		—	400	—	

$C_{D0}$

- The classical equation gives:

$$W = \frac{1}{2} C_{OSS} V_{DS}^2 = 0.5 \times 400 p \times 100^2 = 2 \mu J \quad \text{or } 200 \text{ mW @ } 100 \text{ kHz}$$

- The updated equation gives:

$$W = \frac{2}{3} V_{DS}^{3/2} C_{D0} \sqrt{V_0} = \frac{2}{3} \times 100^{3/2} \times 400 p \times \sqrt{10} = 843 \text{ nJ}$$


or 84 mW @ 100 kHz = 58% reduction

Overkill


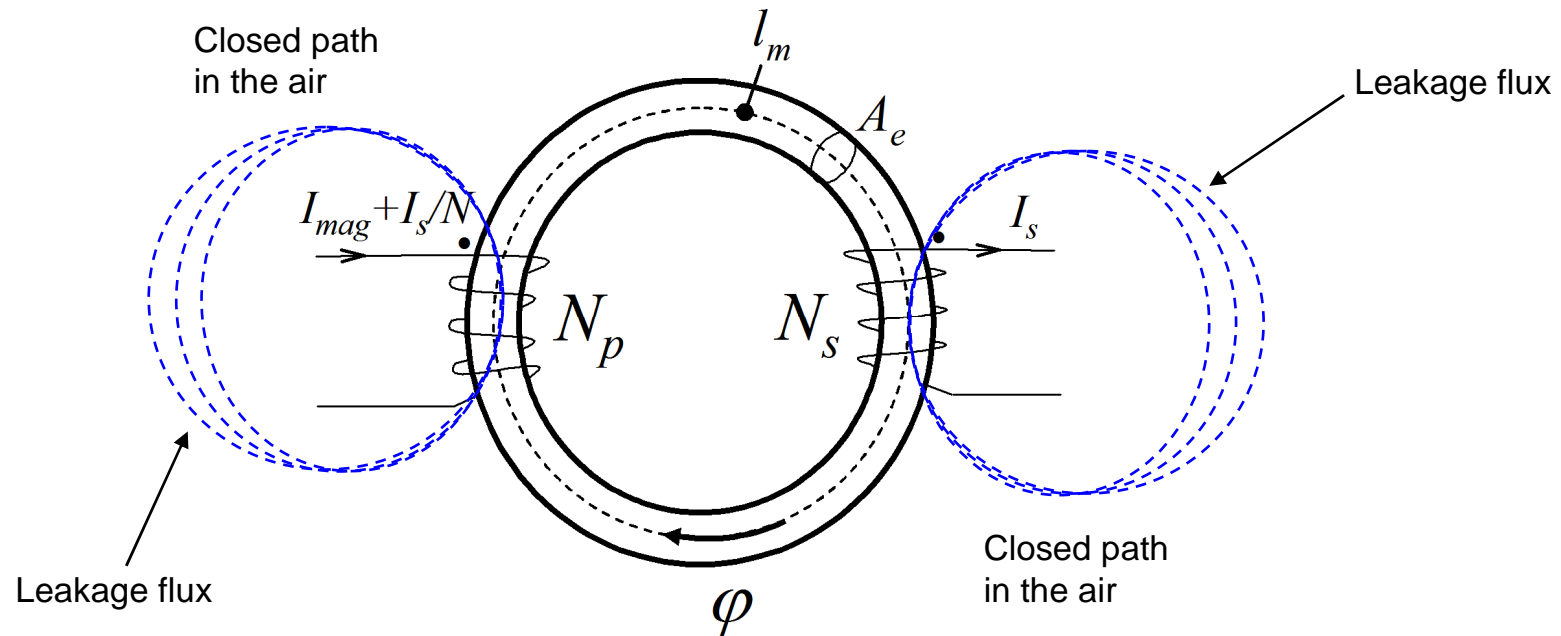
# The Leakage Inductance


- ❑ The coupling in a transformer is not perfect



- ❑ Some induction lines couple in the air: leakage flux
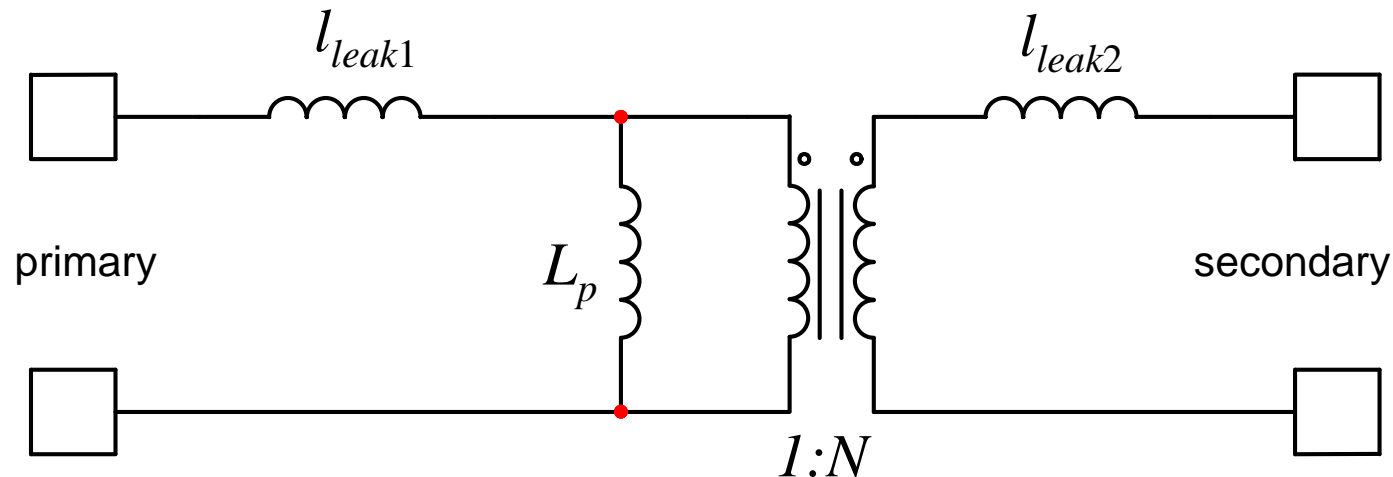
# An Equivalent Transformer Model


- For a two-winding transformer, the model is simple:
  - ✓ Two leakage inductors
  - ✓ One magnetizing inductor



- This is commonly known as the "PI" model

# The Transformer Scales the Primary Current


- In a perfect transformer, we have:

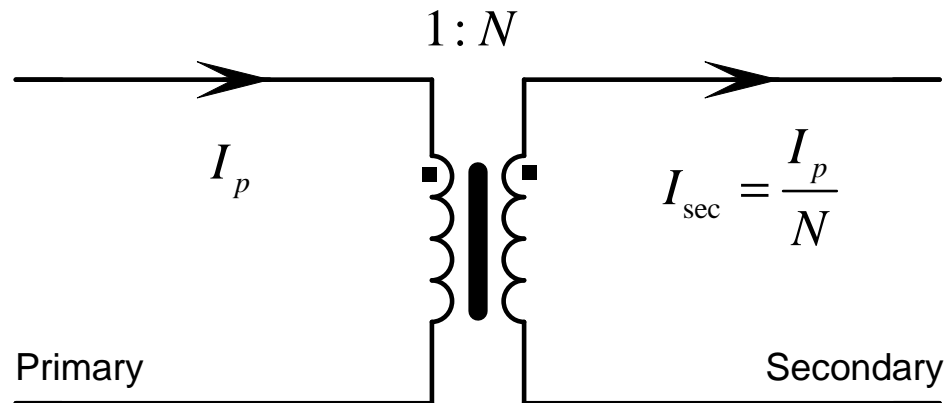

- The turns ratio is usually normalized to the primary


$$N_p : N_s \xrightarrow{\text{Divide by } N_p} \frac{N_p}{N_p} : \frac{N_s}{N_p} \longrightarrow 1 : N$$
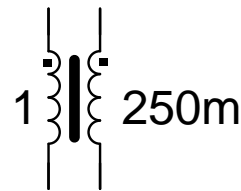
$$\left. \begin{array}{l} N_p = 100 \\ N_s = 25 \end{array} \right\} 1 : 0.25$$


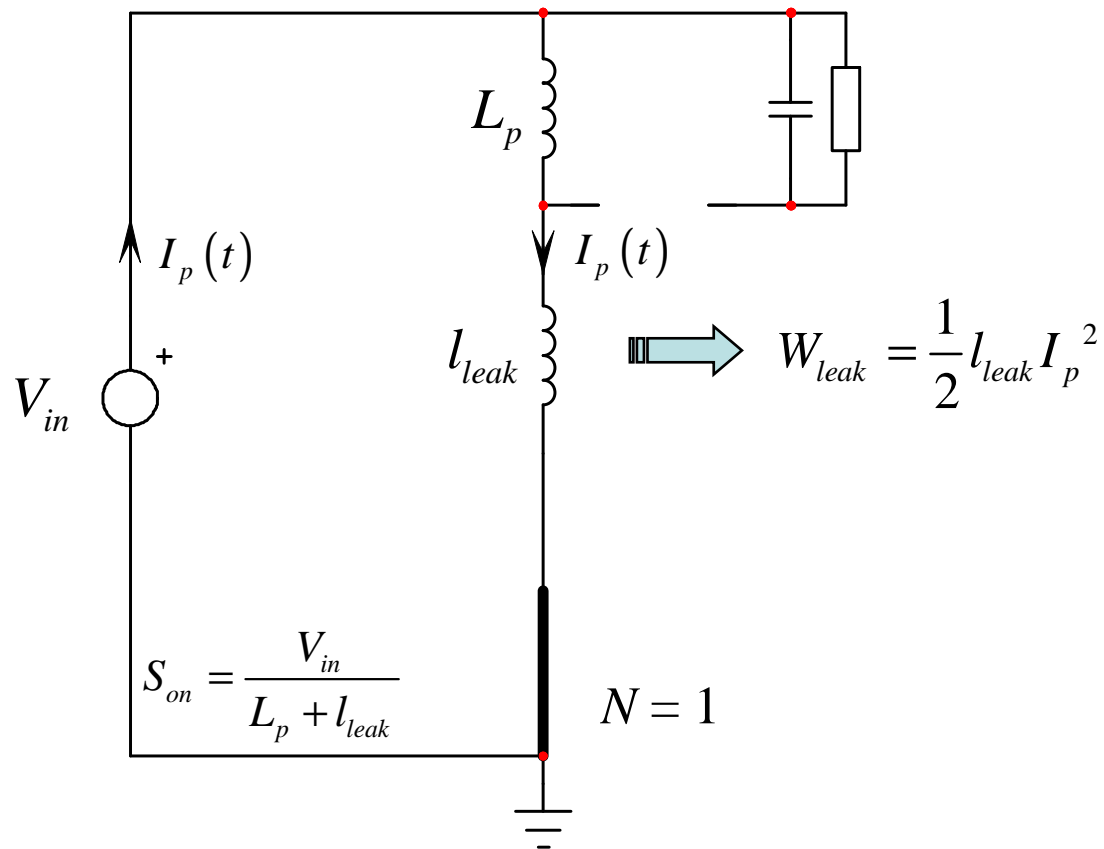
# The Leakage Term also Stores Energy

- At turn-on, the primary current flows in both  $l_{leak}$  and  $L_p$




- During the on-time, both  $L_p$  and  $l_{leak}$  store energy


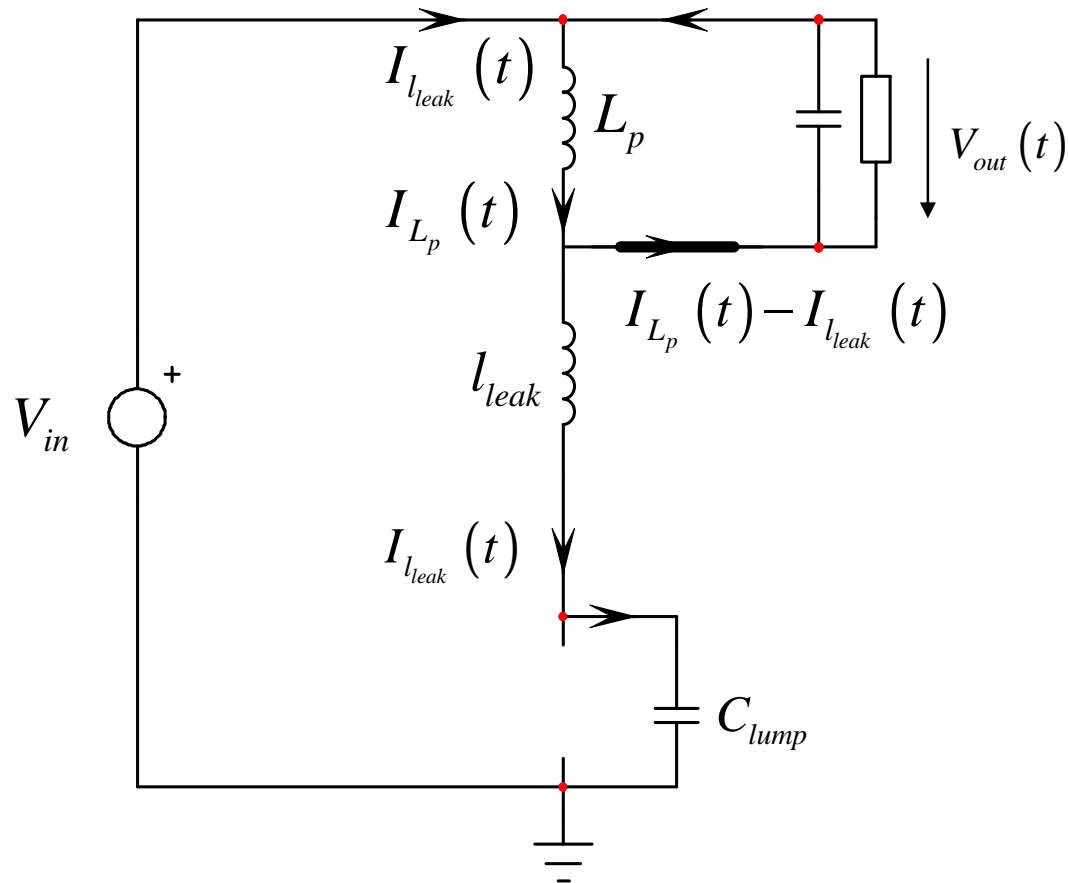
# Where does the Current Flow?



- At turn-off, the energy stored in  $L_p$  is dumped in the output cap.



- The leakage inductor current fills up the drain lump capacitor
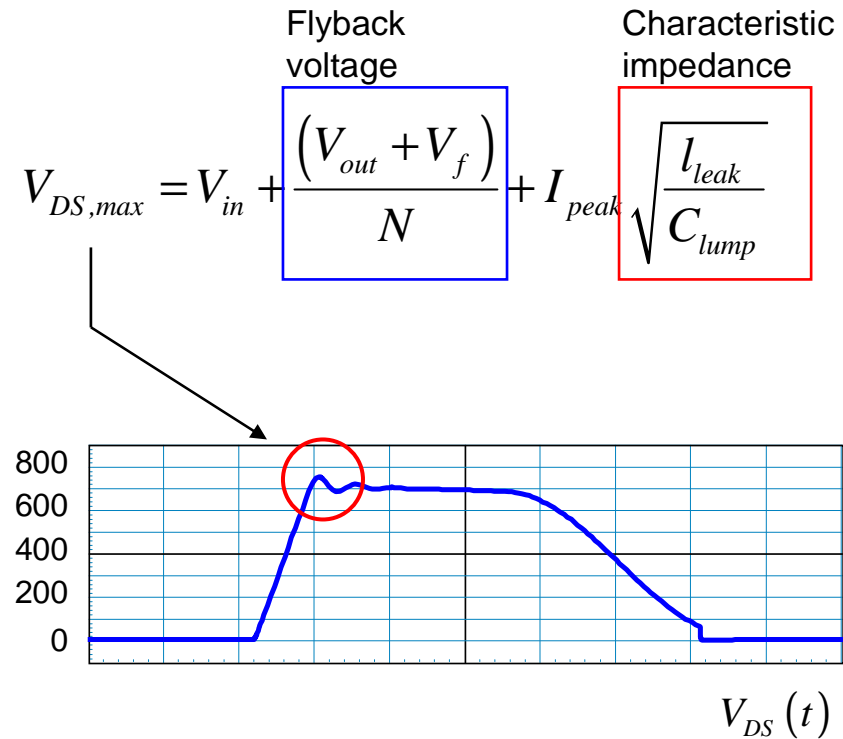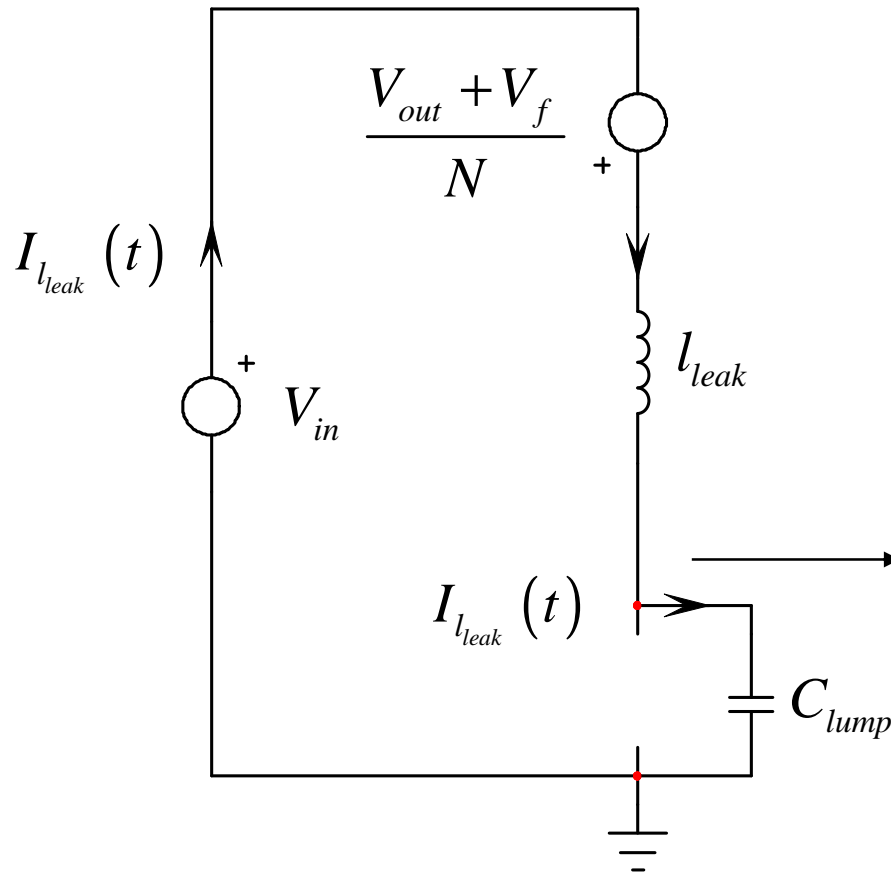
# Watch out for the Maximum Excursion!


- ❑ As the diode conducts,  $V_{out}$  reflects over  $L_p$



- ❑ The voltage on the drain increases dangerously!
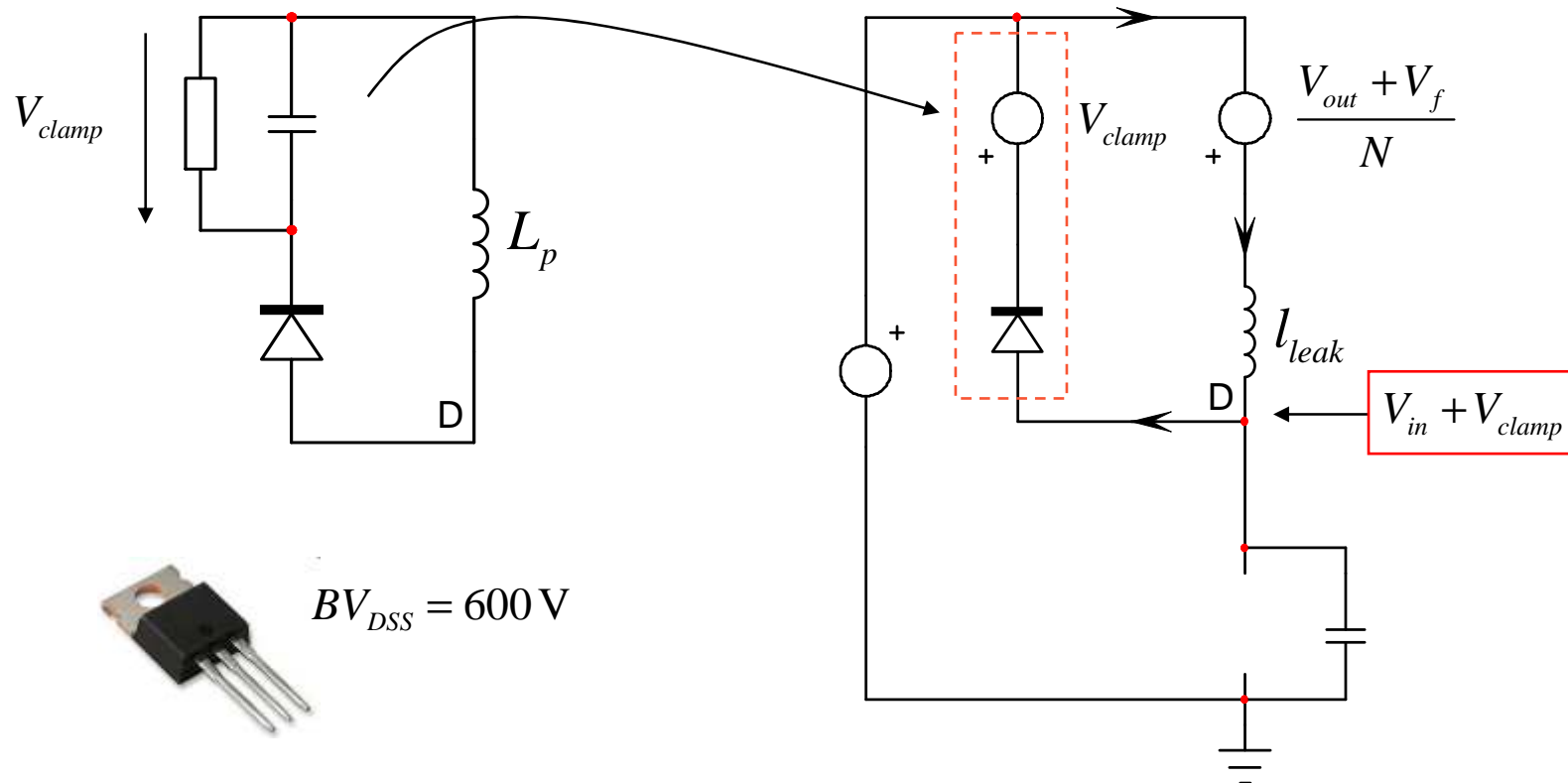
# We Need to Clamp that Voltage


- ❑ MOSFETs have a voltage limit they can fly up to:  $BV_{DSS}$
- ❑ A clamping circuit has been installed to respect a margin


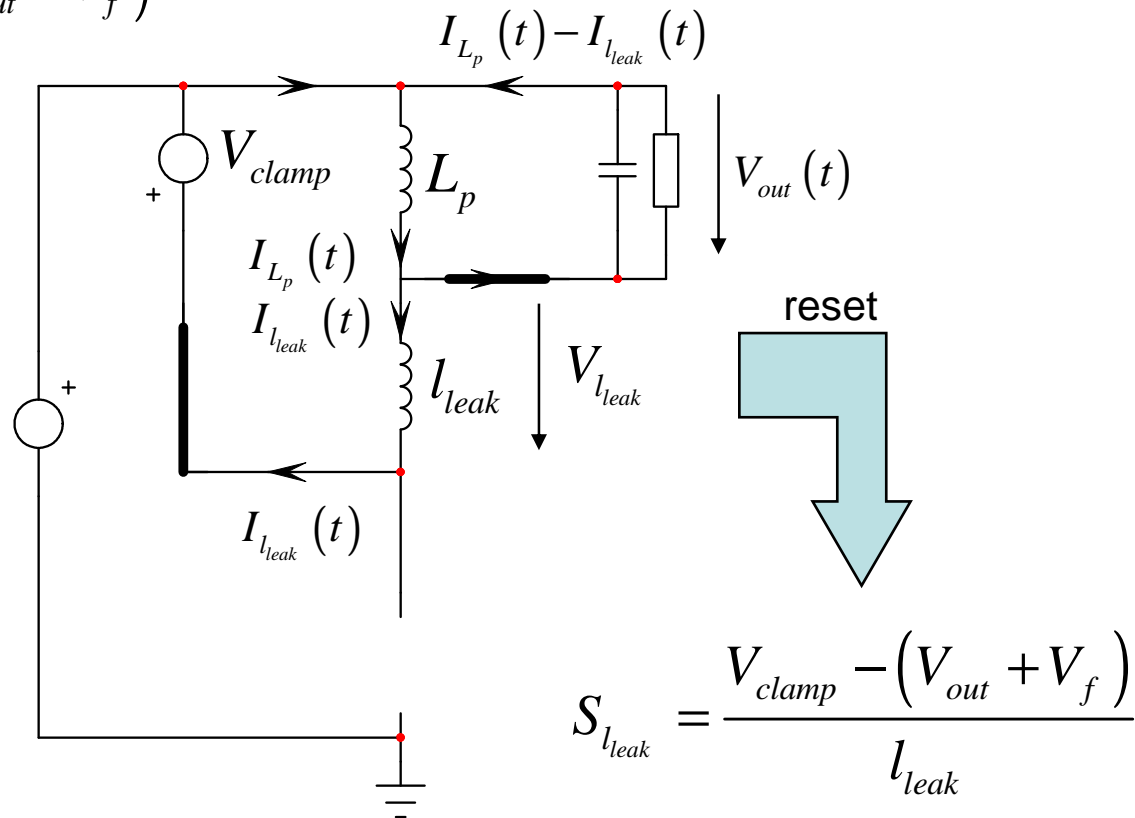
# Resetting the Leakage Inductance

- Because of the clamp action, a voltage appears across  $l_{leak}$


$$V_{l_{leak}} = V_{clamp} - (V_{out} + V_f)$$



- This voltage forces a reset of the leakage inductance

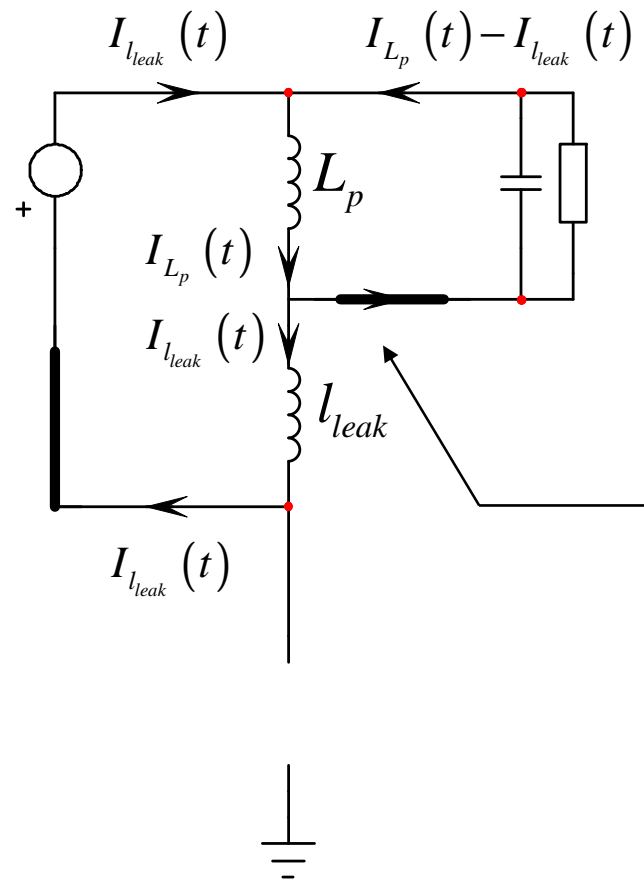
# Do we Need a Quick Reset?

- When current flows in  $I_{leak}$ , it is diverted from the secondary



At the switch opening:

$$I_{L_p}(t) = I_{leak}(t)$$

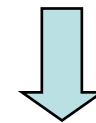


$$I_{sec}(t) = 0$$

- The leakage current delays the occurrence of the sec. current


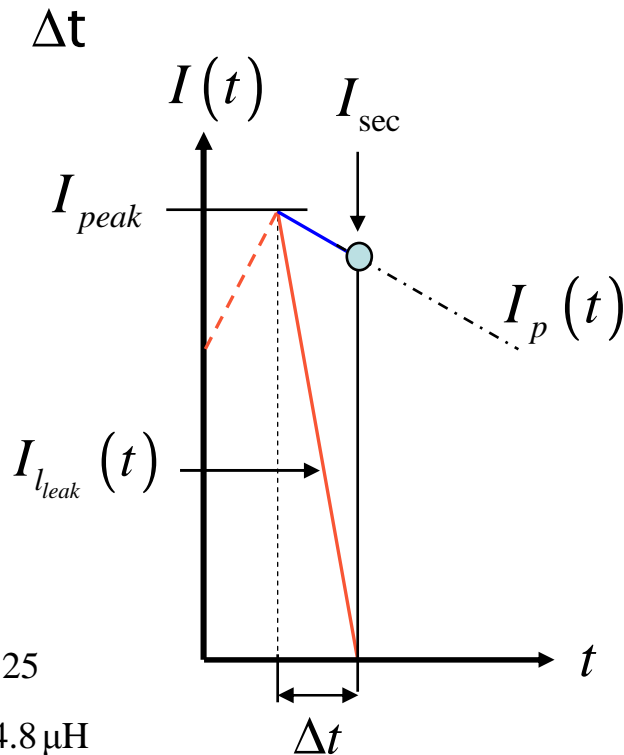
# A Reduced Secondary-Side Current

□ We can calculate the leakage inductor reset time  $\Delta t$



$$N = 0.25$$

$$l_{leak} = 4.8 \mu\text{H}$$

$$V_{clamp} = 150 \text{ V}$$

$$V_{out} = 19 \text{ V}$$

$$I_{peak} = 3 \text{ A}$$



$$\Delta t = \frac{0.25 \times (4.8 \mu \times 3)}{0.25 \times 150 - (19 + 1)} = 205 \text{ ns}$$


$$S_{l_{leak}} = \frac{V_{clamp} - (V_{out} + V_f)}{l_{leak}}$$

$$\Delta t = \frac{I_{peak}}{S_{l_{leak}}} = \frac{l_{leak} I_{peak}}{V_{clamp} - (V_{out} + V_f)}$$

$$\xrightarrow{N \neq 1} \Delta t = \frac{I_{peak}}{S_{l_{leak}}} = \frac{N l_{leak} I_{peak}}{N V_{clamp} - (V_{out} + V_f)}$$

$$I_{sec} = \frac{I_{peak}}{N} - S_{sec} \Delta t = \frac{I_{peak}}{N} \left( 1 - \frac{l_{leak}}{L_p} \frac{1}{\frac{N V_{clamp}}{V_{out} + V_f} - 1} \right)$$


# Typical Example Simulation Results

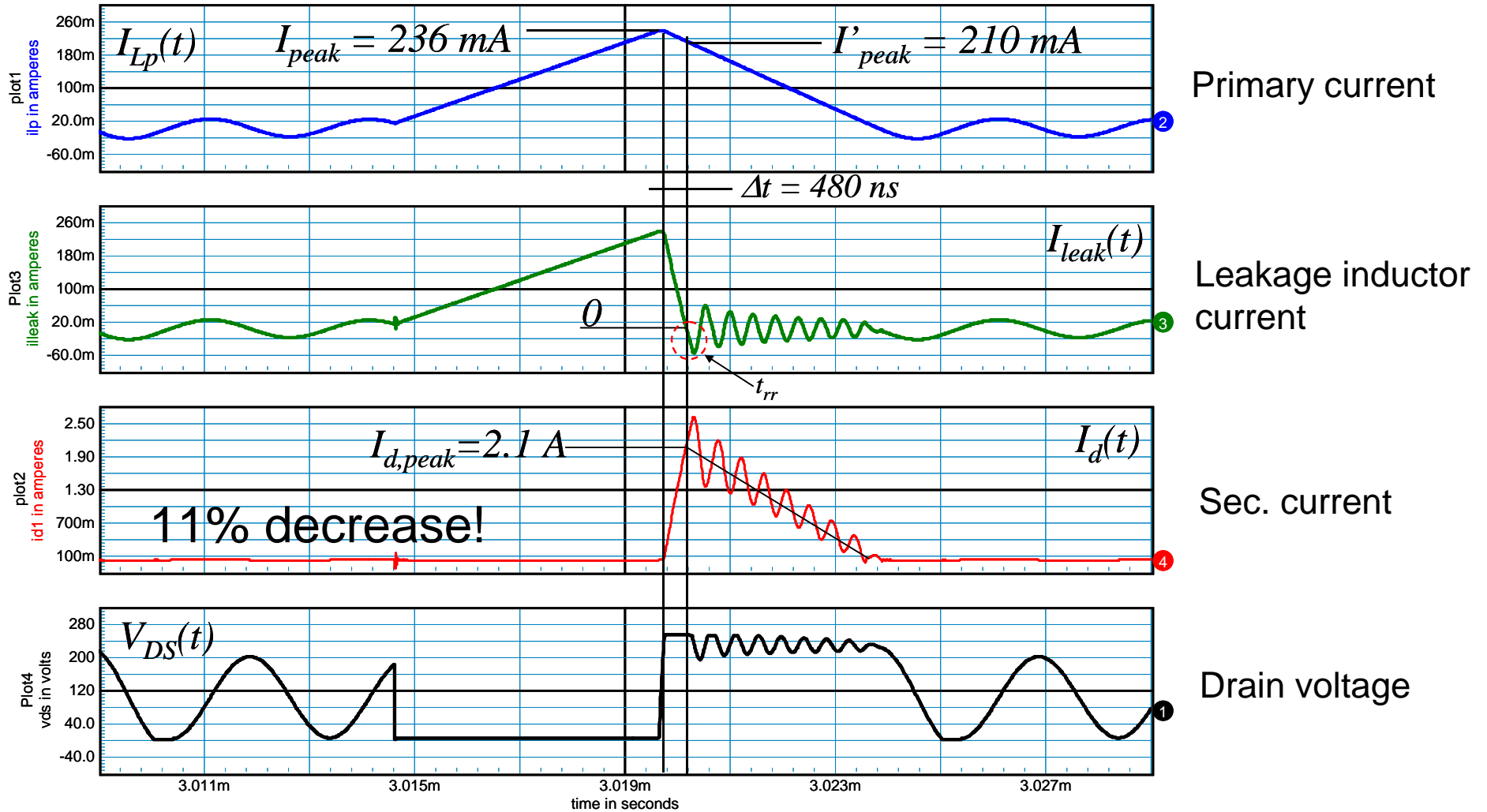



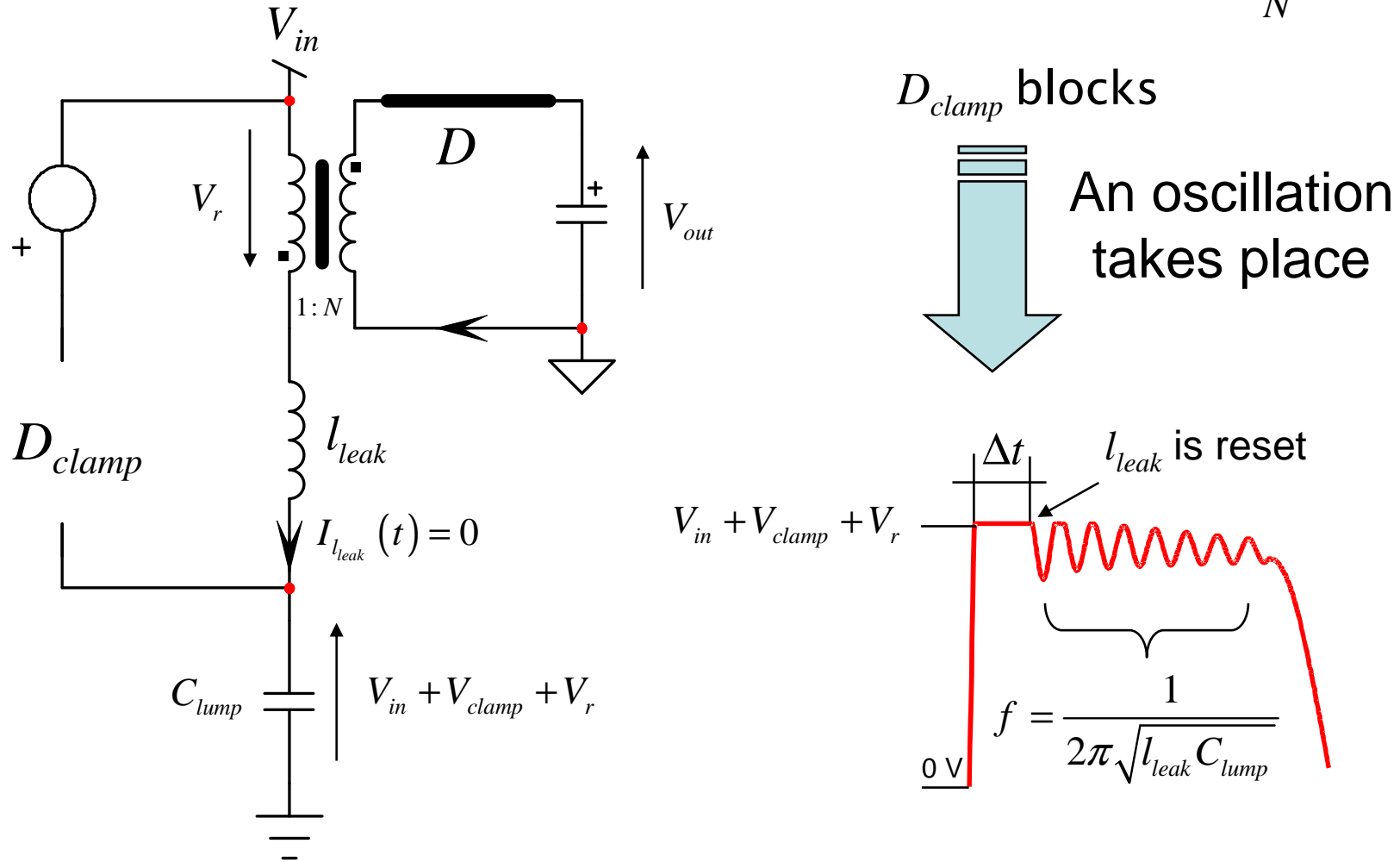
# A Ringing Appears as the Diode Blocks

- As the clamp diode blocks, the drain returns to  $\frac{V_{out} + V_f}{N}$


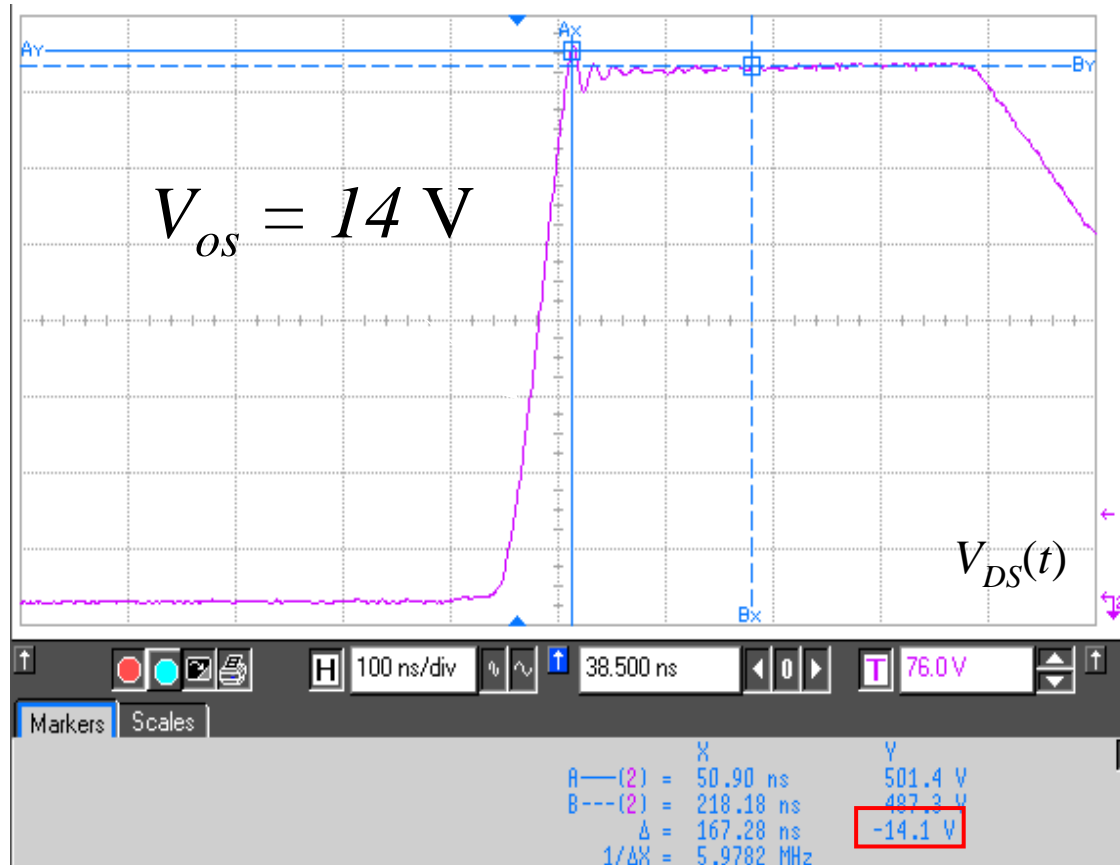
# The Clamp Circuit Overshoots


- The clamp diode forward transit time delays the clamping action




- This spike can be lethal to the power MOSFET – include margin!
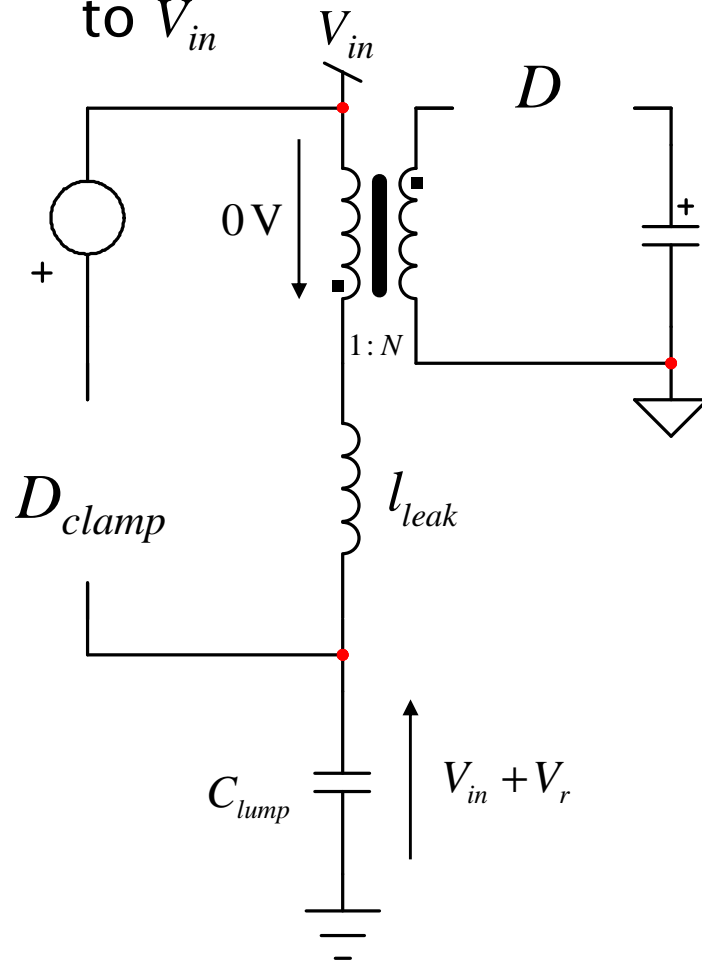
# The Primary Inductor also Rings in DCM


□ When  $L_p$  is reset, the capacitor voltage returns to  $V_{in}$



$D$  blocks

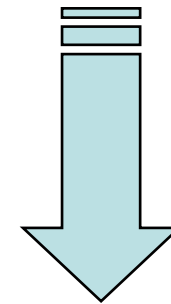

An oscillation takes place

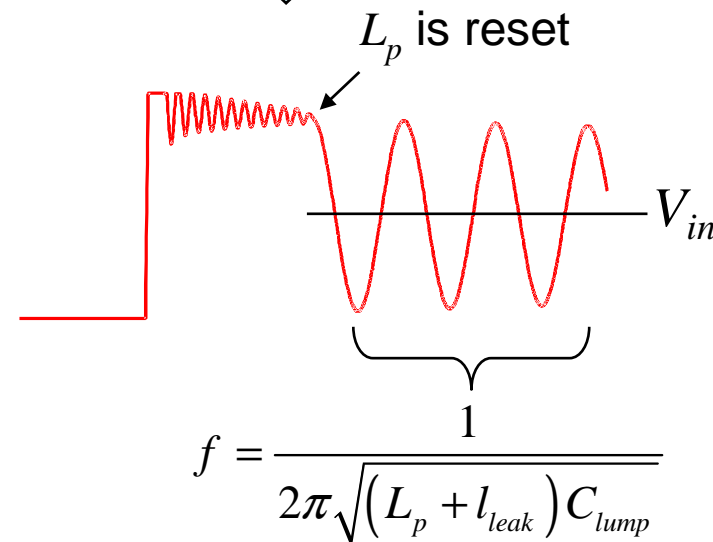

---


# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?**
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?
- More Power than Needed
- The Frequency Response
- Compensating With the TL431



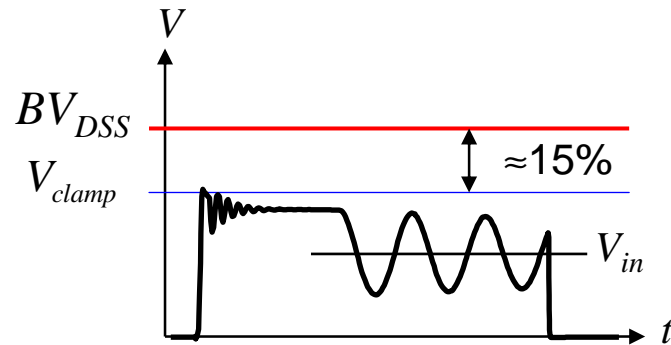
# How these Parasitics Affect your Design?

- ❑ The leakage inductor induces a large spike at turn-off
- ❑ This voltage excursion must be kept under control



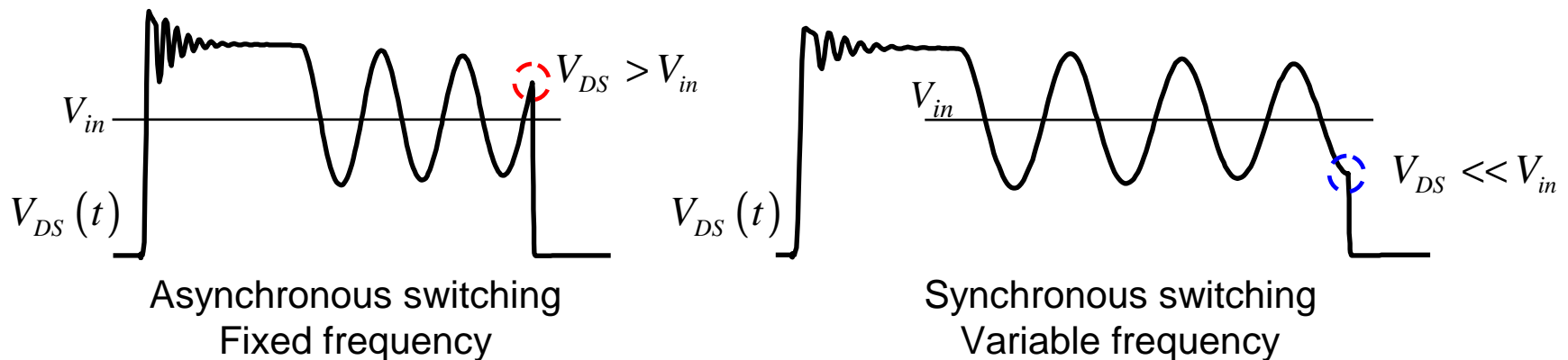- ❑ The lump capacitor on the drain brings switching losses
- ❑ Is there a way to switch on again when discharged?



# Protecting the Power MOSFET


- ❑ A vertical MOSFET features a buried parasitic NPN transistor
  - ❑ The collector-base junction of this transistor forms the body-diode
  - ❑ This « diode » can accept to avalanche in certain conditions
  - ❑ Do NOT use this diode as a Transient Voltage Suppressor!
- ✓ Adopt a safety coefficient  $k_D$  when choosing the maximum  $V_{DS}(t)$
- ✓ 15% derating is usually selected

$$k_D = 0.85$$

$$BV_{DSS} \times k_D = 600 \times 0.85 = 510 \text{ V}$$

$$V_{clamp} = BV_{DSS} \times k_D - V_{os} - V_{in} = \boxed{115 \text{ V}}$$


Take  $V_{os}$  around 15 – 20 V

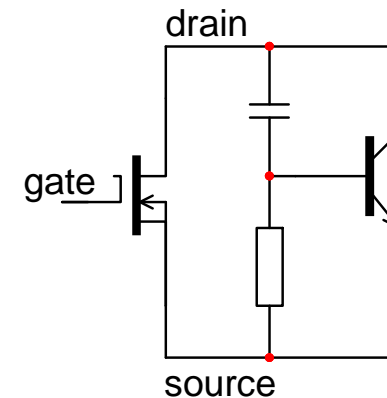

RCD clamp  
design entry
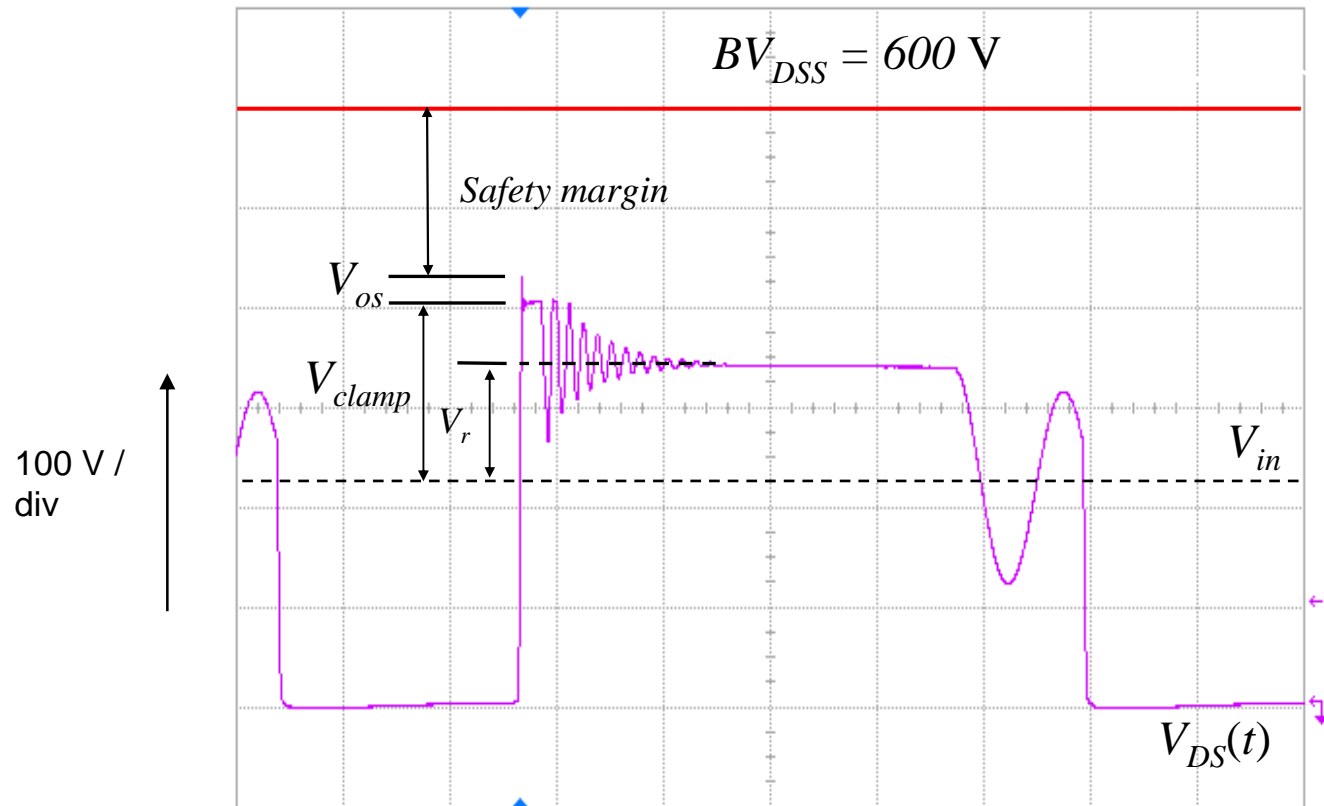
# Inclusion of a Safety Margin

- ❑ The voltage on the drain swings up to  $V_{clamp}$



$V_{out} = \text{nominal}$

$I_{out} = \text{max}$

$V_{in} = \text{max}$




Test at start-up  
and in short-circuit

- ❑ Capture this waveform in worst-case conditions
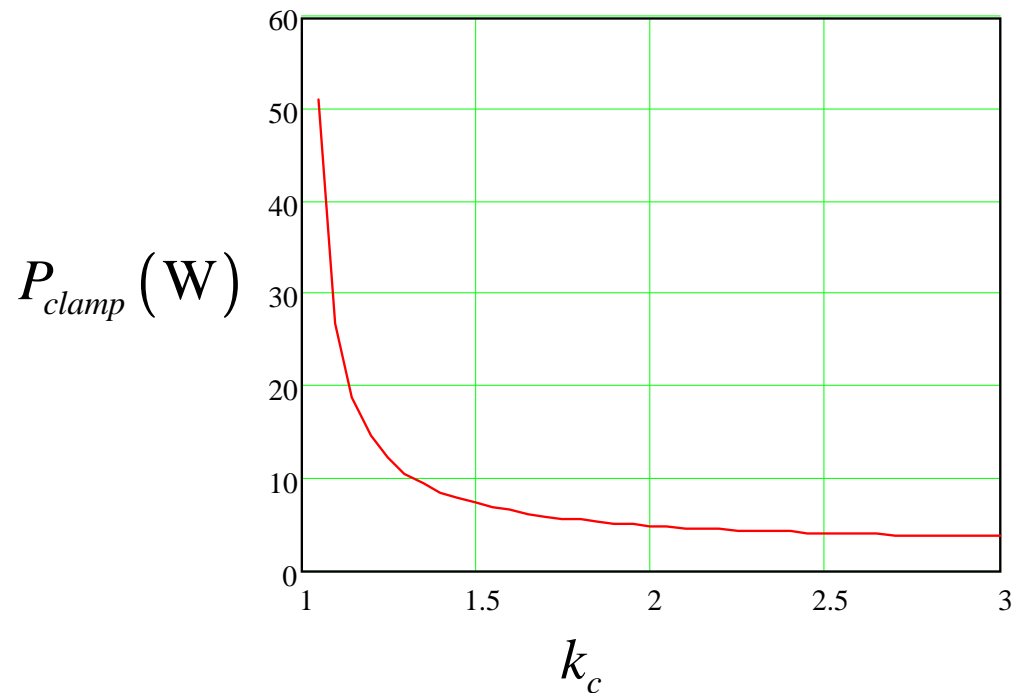
# Do not Reflect too Much Voltage

- ❑ The reflected voltage affects the power dissipation in the clamp

$$P_{V_{clamp},avg} = \frac{1}{2} F_{sw} L_{leak} I_{peak}^2 \frac{k_c}{(k_c - 1)} \quad k_c = \frac{V_{clamp}}{V_r}$$



- ❑ If  $V_{clamp}$  is too close to  $V_r$ , dissipation occurs  $\rightarrow k_c = 1.3$  to 2




# Compute the Transformer Turns Ratio

- The turns ratio affects the reflected voltage...

$$V_{clamp} k_c \geq \frac{(V_{out} + V_f)}{N} \quad \Rightarrow \quad N \geq \frac{k_c (V_{out} + V_f)}{V_{clamp}}$$

- But also the Peak Inverse Voltage of the secondary diode


$$PIV = V_{in} N + V_{out}$$

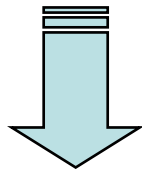

Choose a 100% derating factor

If  $PIV = 100 \text{ V}$

Then  $BV = 200 \text{ V}$

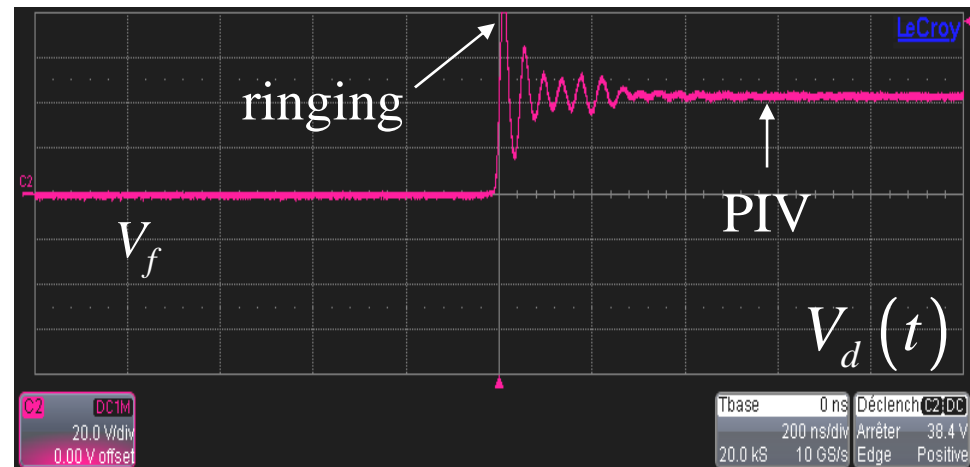


- Always check the margins are not violated in any operating modes

# Select the Clamp Passive Elements

- The clamp resistor depends on the maximum peak current


$$R_{clp} = \frac{2V_{clamp} \left[ V_{clamp} - \frac{(V_{out} + V_f)}{N} \right]}{F_{sw} I_{leak} I_{peak}^2}$$
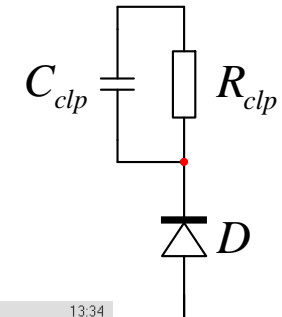
$$C_{clp} = \frac{V_{clamp}}{R_{clp} F_{sw} \Delta V}$$



$$I_{peak,max} = \underbrace{\frac{V_{sense,max}}{R_{sense}} + \frac{V_{in,max}}{L_p} t_{prop}}_{\text{Worst-case value}}$$


Worst-case value

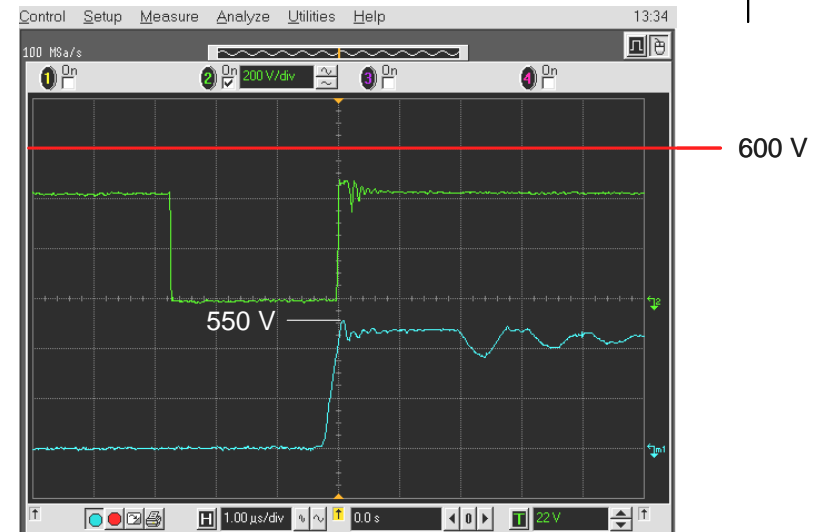

- Watch for the peak current overshoot in fault!
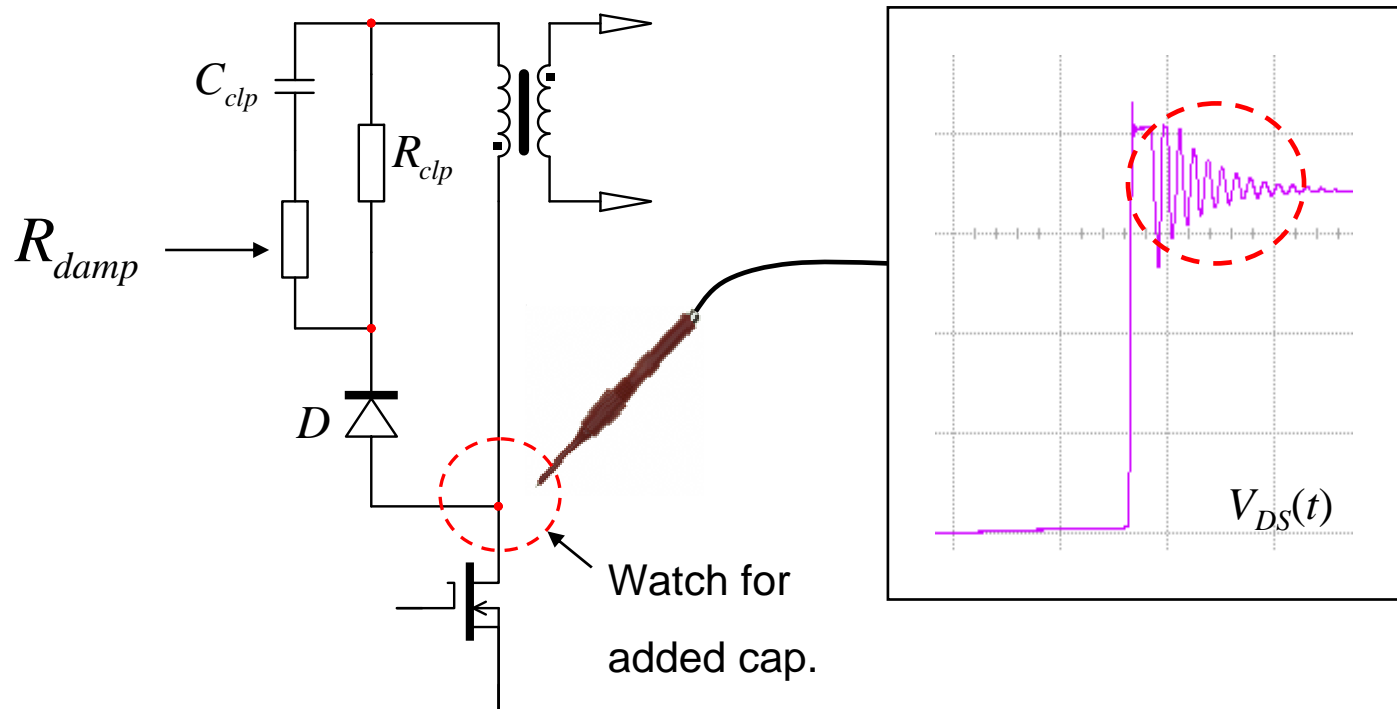
# The Leakage Inductor Rings


- ❑ This ringing can be of high frequency and is radiated-EMI rich



- ❑ It can also forward-bias the MOSFET body diode
- ❑ Damp it!
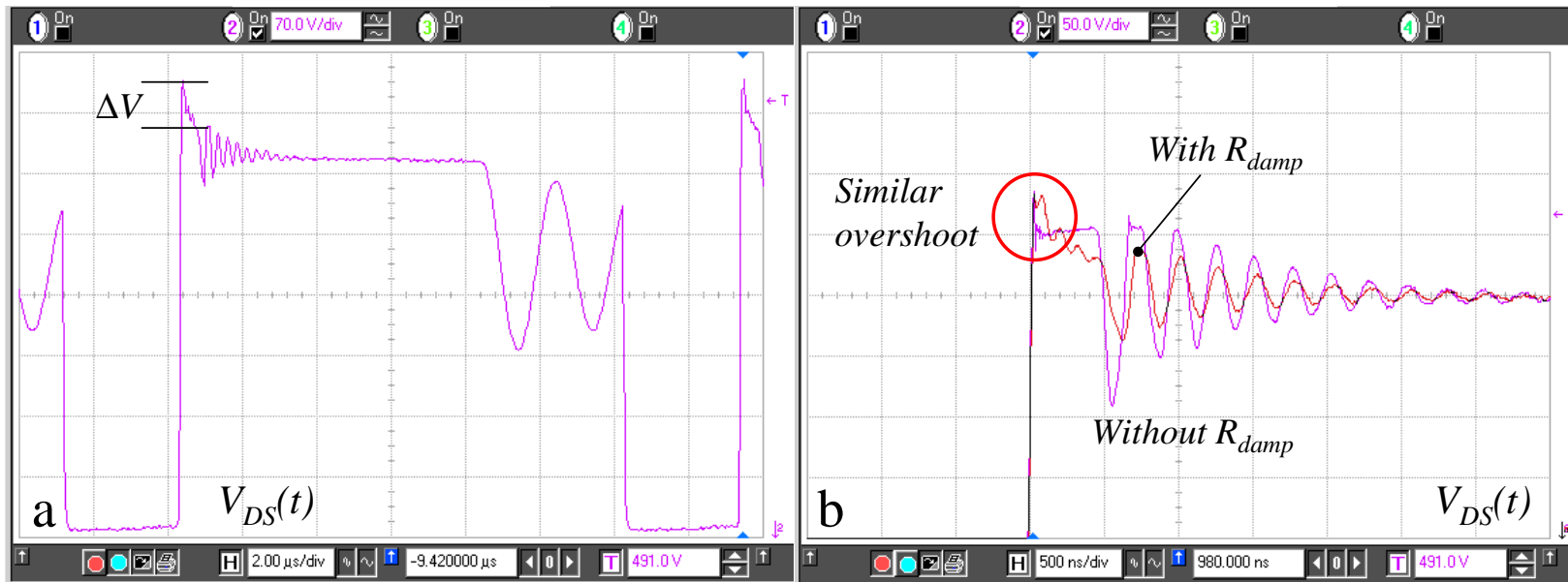
# Fighting Parasitic Ringing – part I

- The installed resistor reduces the ringing on the drain




$$Q = \frac{\omega_0 l_{leak}}{R_{damp}} = 1$$

$$Z_{l_{leak}} @ f_0 = R_{damp}$$
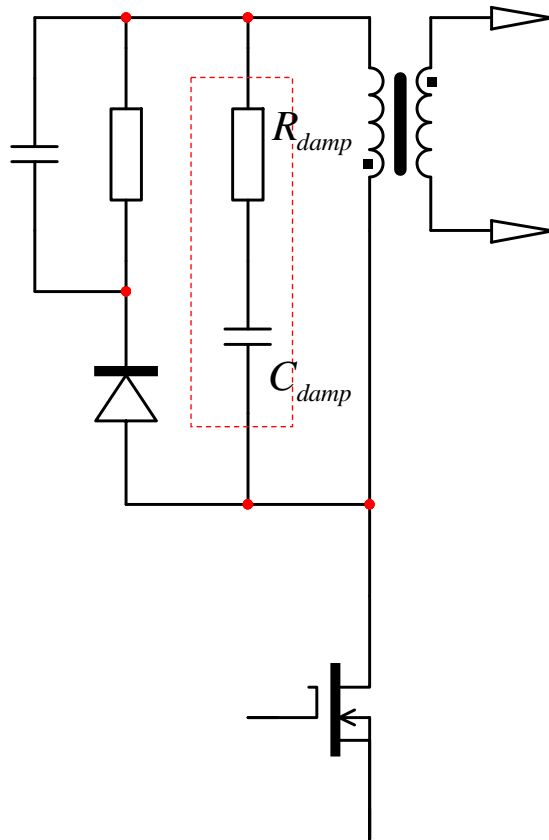
# Fighting Parasitic Ringing – part II

- If the series resistor is not enough, install a damper




1. Measure the ringing:  $f_0$
2. Evaluate leakage impedance at  $f_0$

$$Z_{l_{leak}} = 2\pi l_{leak} f_0$$

3. Make  $R_{damp} = Z_{l_{leak}}$
4. Try  $C_{damp} = \frac{1}{2\pi f_0 R}$
5. Tweak for power dissipation


Ray Ridley – Snubber design procedure

# Effects Brought by the Clamping Action

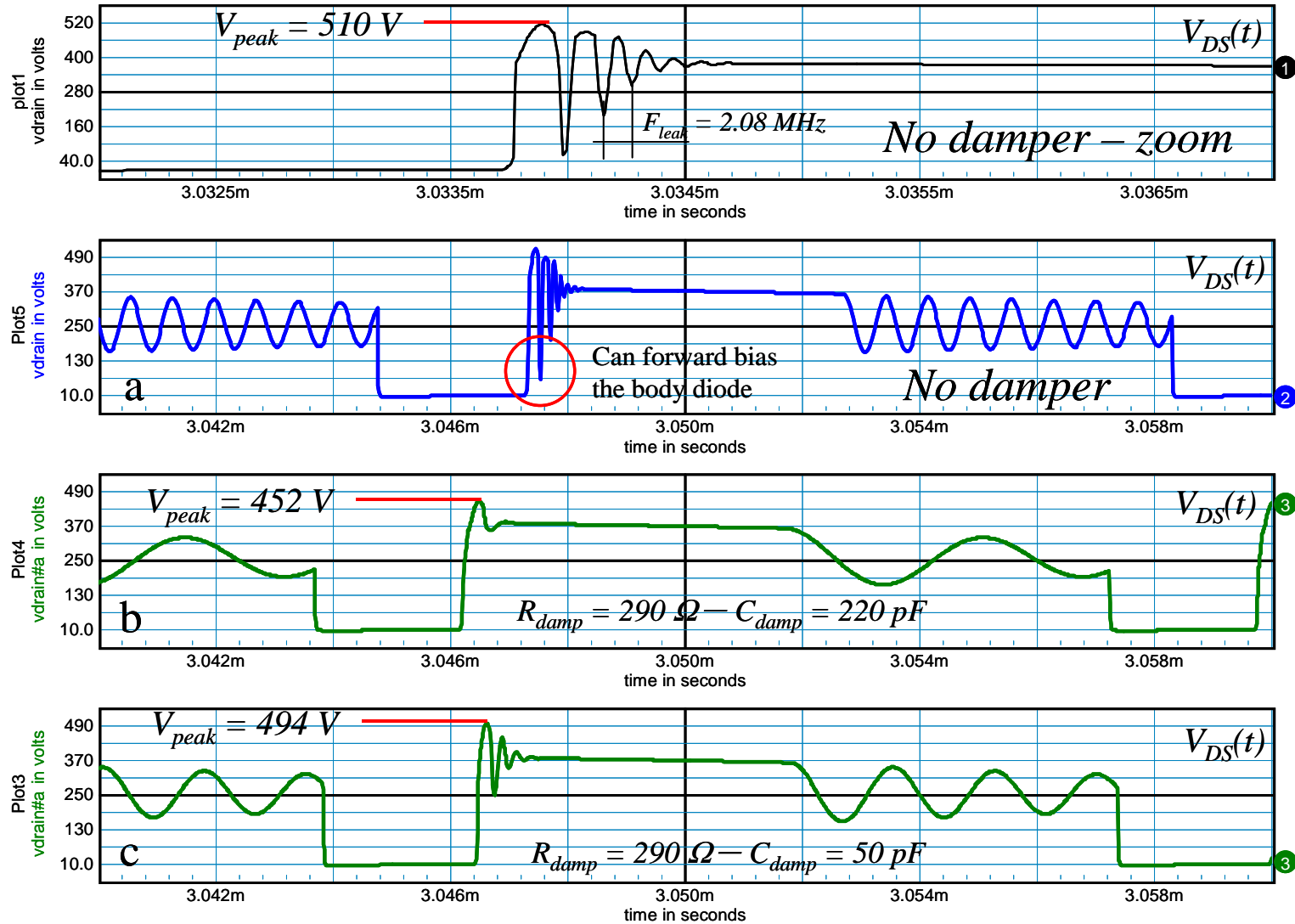
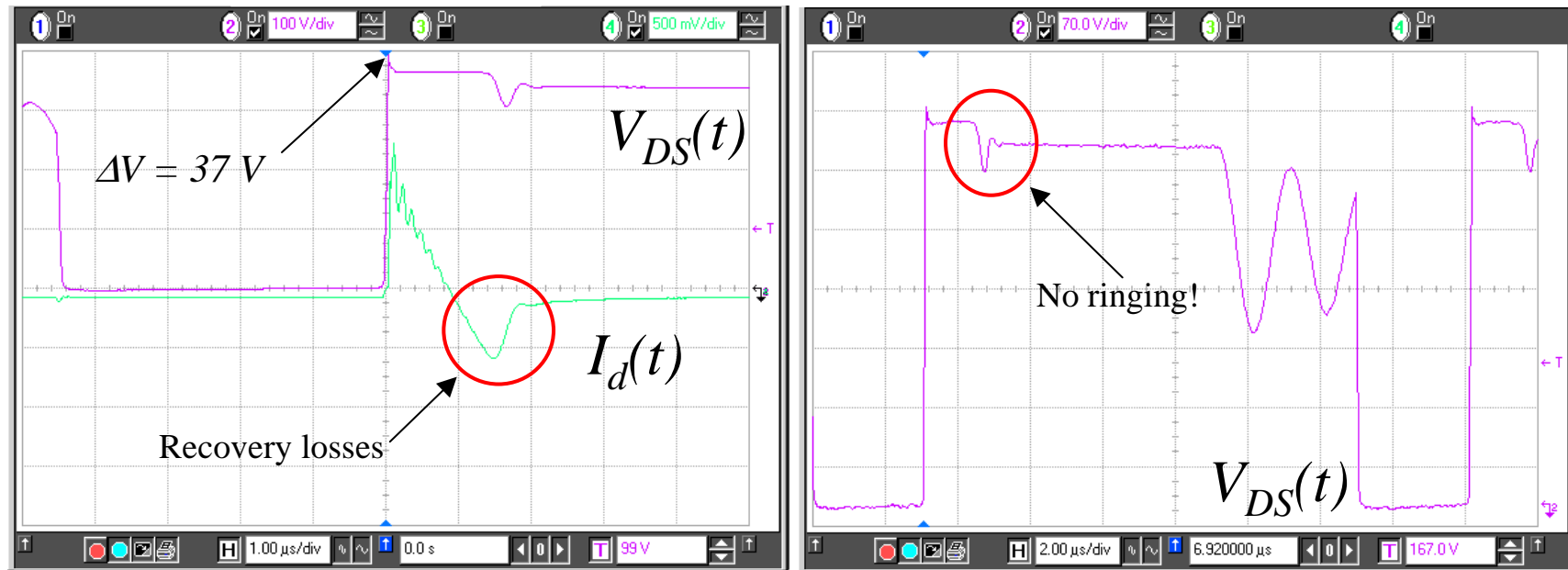
# What Diode to Select for the Clamp?


- ❑ A fast diode is a must: MUR160 is good fit



- ❑ Can a simple 1N4007 be used in a *RCD* clamping network?
- ❑ The answer is yes for low power applications (below 20 W)
- ❑ The long recovery time naturally damps the leakage inductor
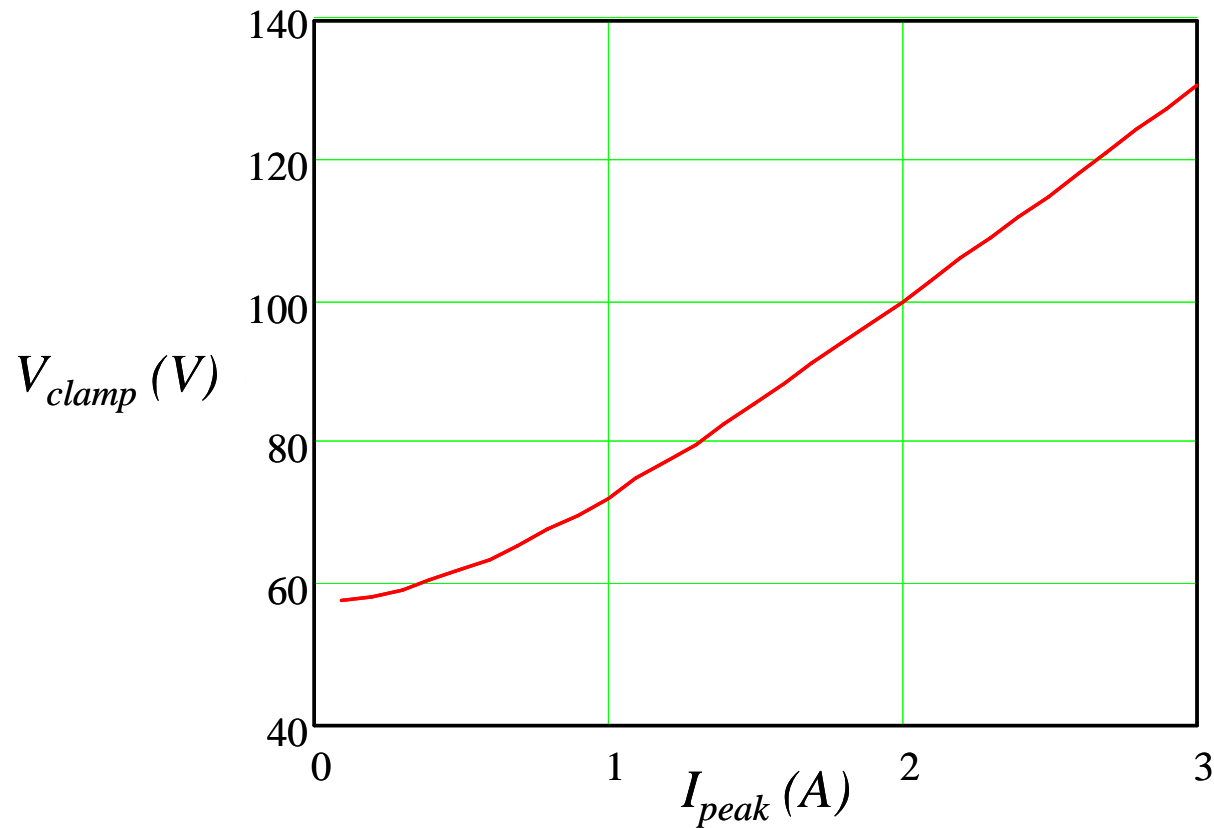
# Be Sure the Clamp Level does not Runaway


- ❑ Watch-out for clamp voltage variations, at start-up or in short-circuit
- ❑ The main problem comes from the propagation delay!






# Check the Clamp Voltage Variations


No design margin!

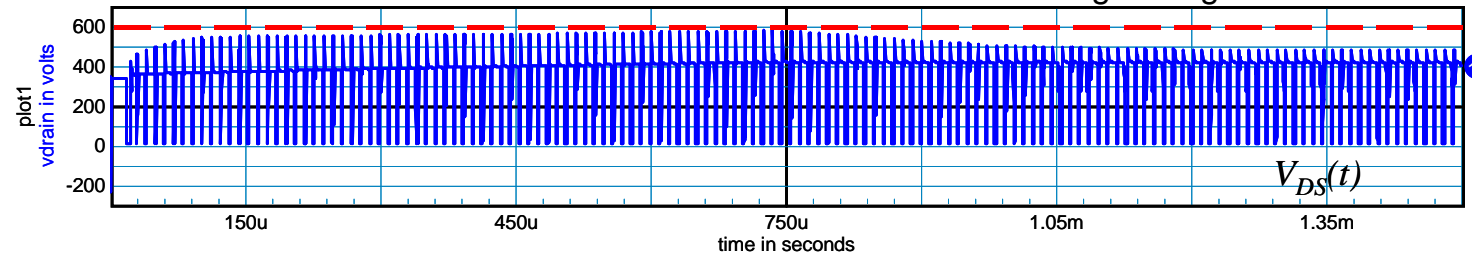


Drain voltage

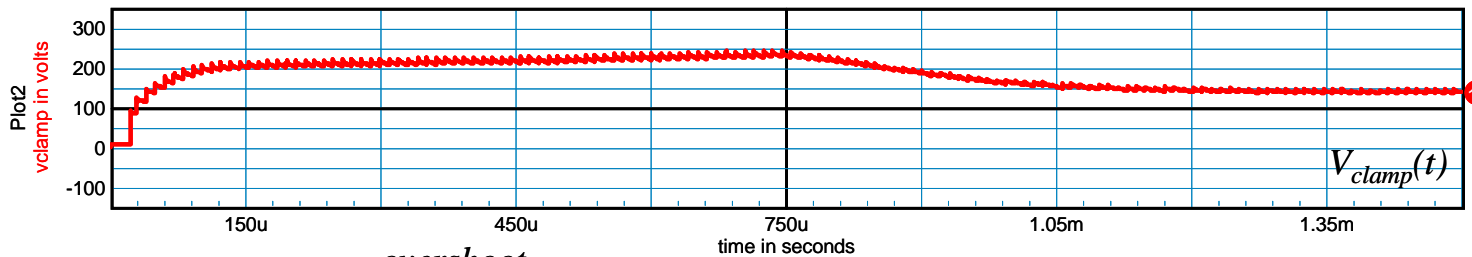

Clamp voltage

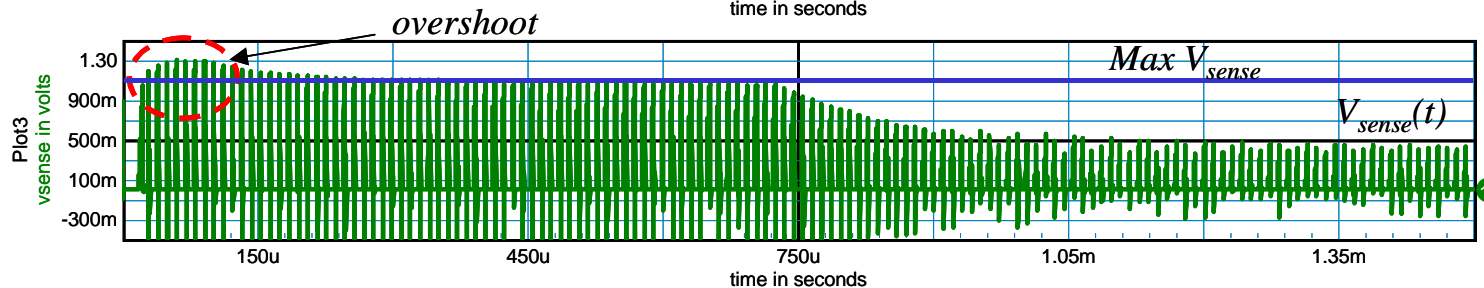

Sense voltage

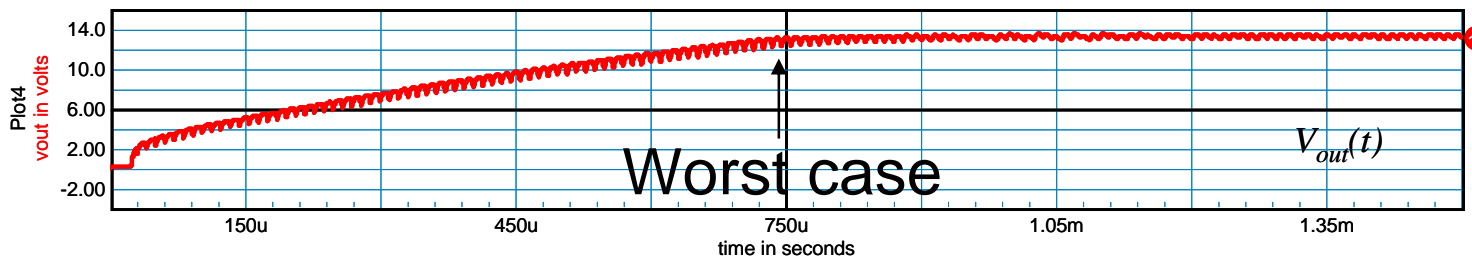


Output voltage



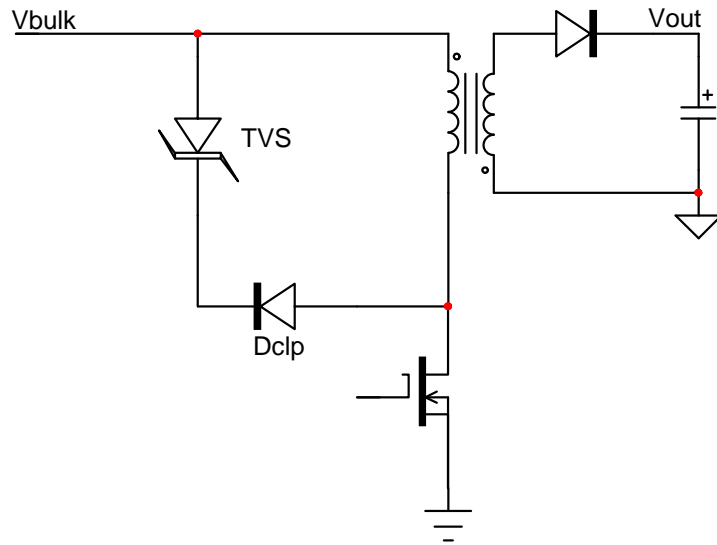
# A Zener or TVS to Hard Clamp the Voltage

- ❑ TVS do not suffer from voltage runaways in fault conditions


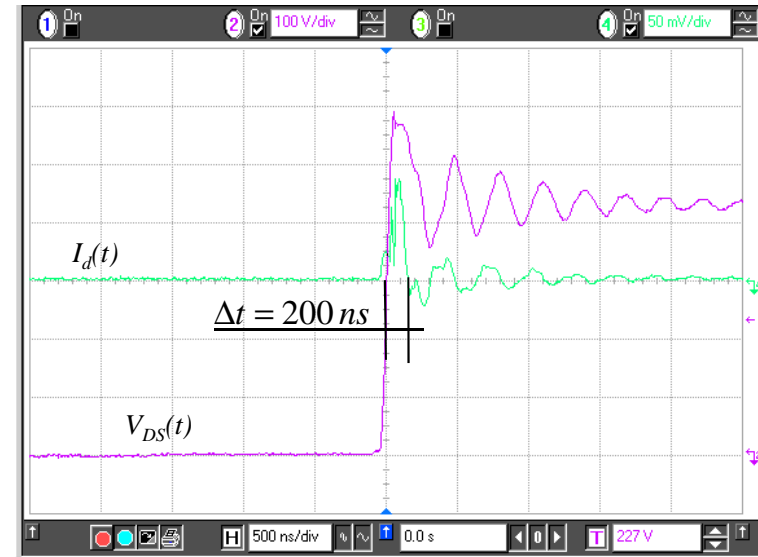
$$P_{TVS} = \frac{1}{2} F_{sw} I_{leak} I_{peak}^2 \frac{V_z}{V_z - \frac{(V_{out} + V_f)}{N}}$$



- ❑ The TVS improves the efficiency in standby but degrades EMI
- ❖ It costs around 5 cents...

---

# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme**
- Fixed or Variable Frequency?
- More Power than Needed
- The Frequency Response
- Compensating With the TL431




# What Control Scheme?

- ❑ Two control scheme coexist, current-mode and voltage-mode



Voltage-mode?

Current-mode?

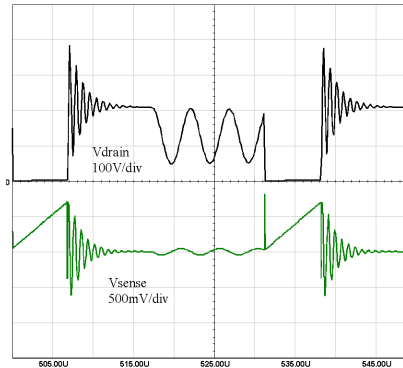


Operating waveforms are identical



Voltage-mode?

Current-mode?

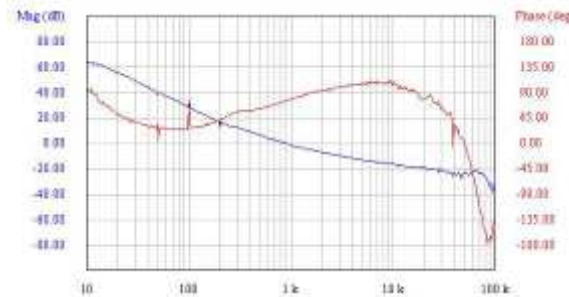


Ac-transfer functions differ


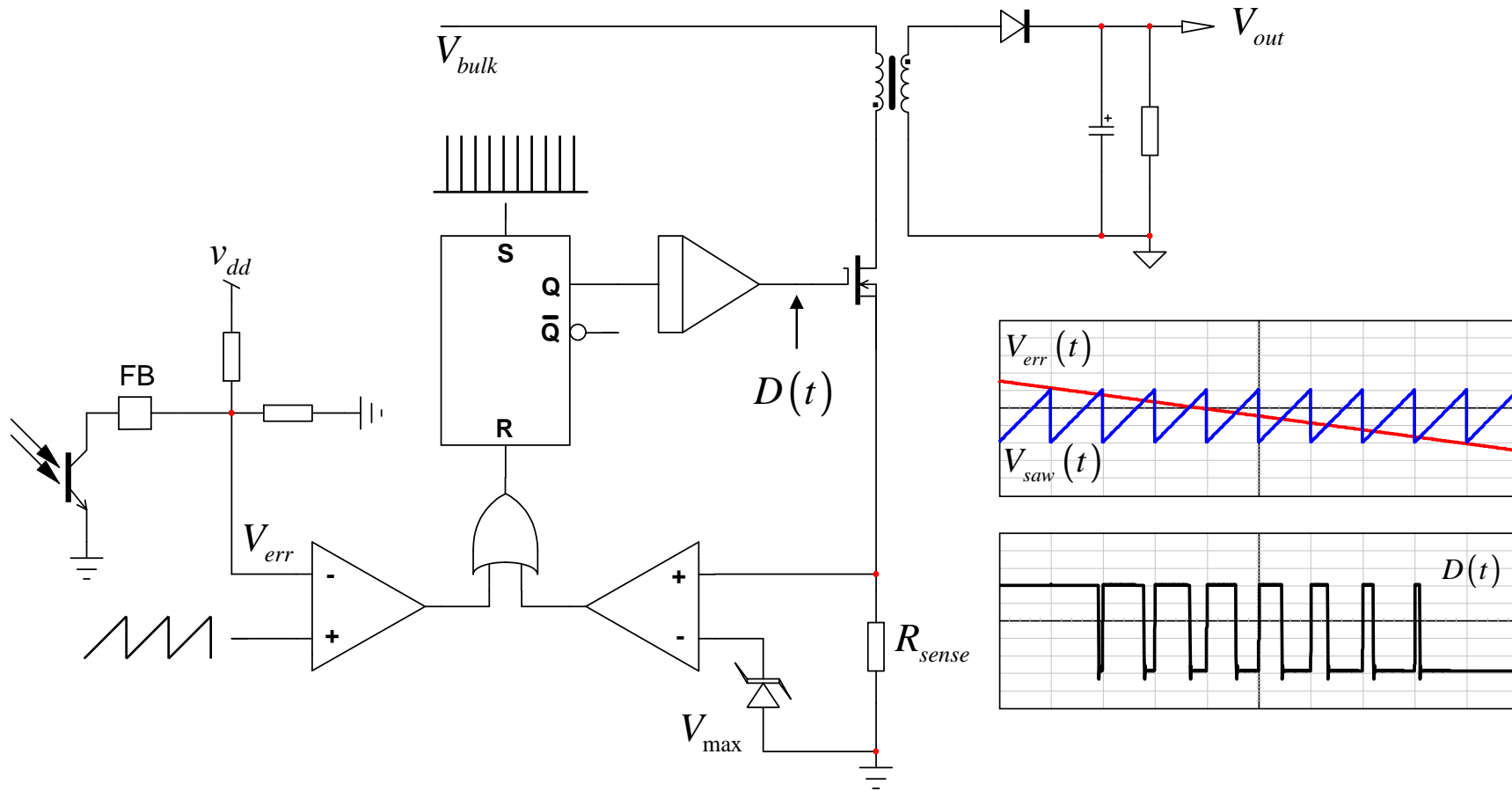
# Voltage-Mode Control

- ❑ Voltage mode uses a ramp to generate the duty-ratio
- ❑ The error voltage directly adjusts the duty-ratio



# Voltage-Mode Control

## PROs

- ❑ Does not need the inductor current information
- Can go to very small duty-ratio
- ❑ CCM operation without sub-harmonic instabilities
- No need for slope compensation, current limit unaffected


## CONs

- ❑ No inherent input line feedforward (weak audio susceptibility)
- Cannot use small bulk capacitor, bad ripple rejection
- ❑ 2<sup>nd</sup>-order system in CCM: mode transition can be a problem
- ❑ Limited integrated circuit offer


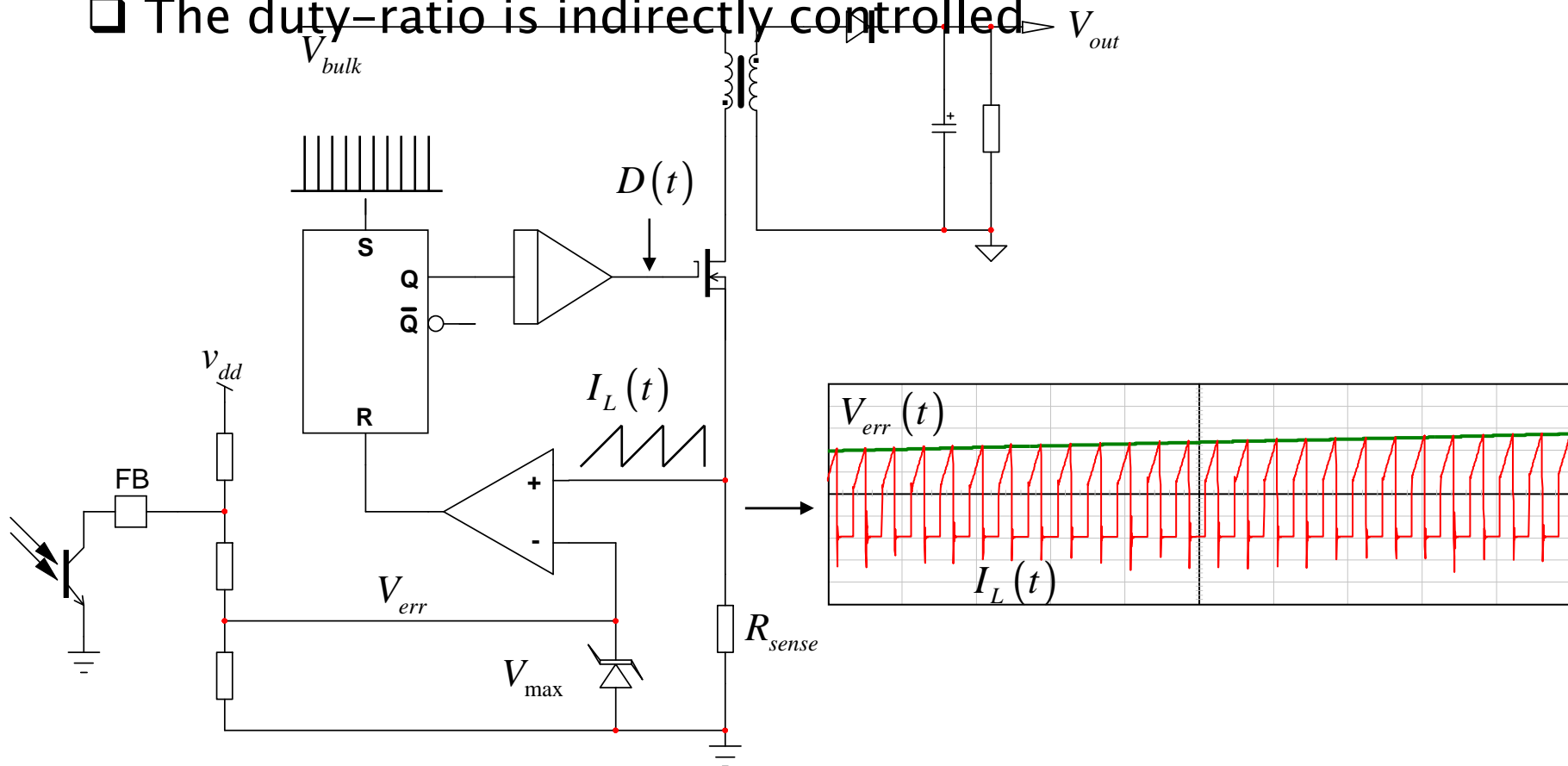
# Peak-Current-Mode Control

- ❑ Current mode uses the inductor current information as a ramp
- ❑ The error voltage adjusts the inductor peak current
- ❑ The duty-ratio is indirectly controlled



# Peak-Current-Mode Control

## PROs

- ❑ Inherent pulse-by-pulse current limitation
- ❑ Natural input line rejection
- ❑ Mode transition DCM to CCM is easy
- Converter remains a 1<sup>st</sup>-order system at low frequency
- ❑ Widest offer on the market: a really popular technique!

## CONs


- ❑ Leading Edge Blanking limits the minimum duty-ratio
- ❑ Requires slope compensation against sub-harmonic oscillations
- Additional ramp affects the available maximum peak current
- ❑ Current sense can sometimes be a problem (floating sense)






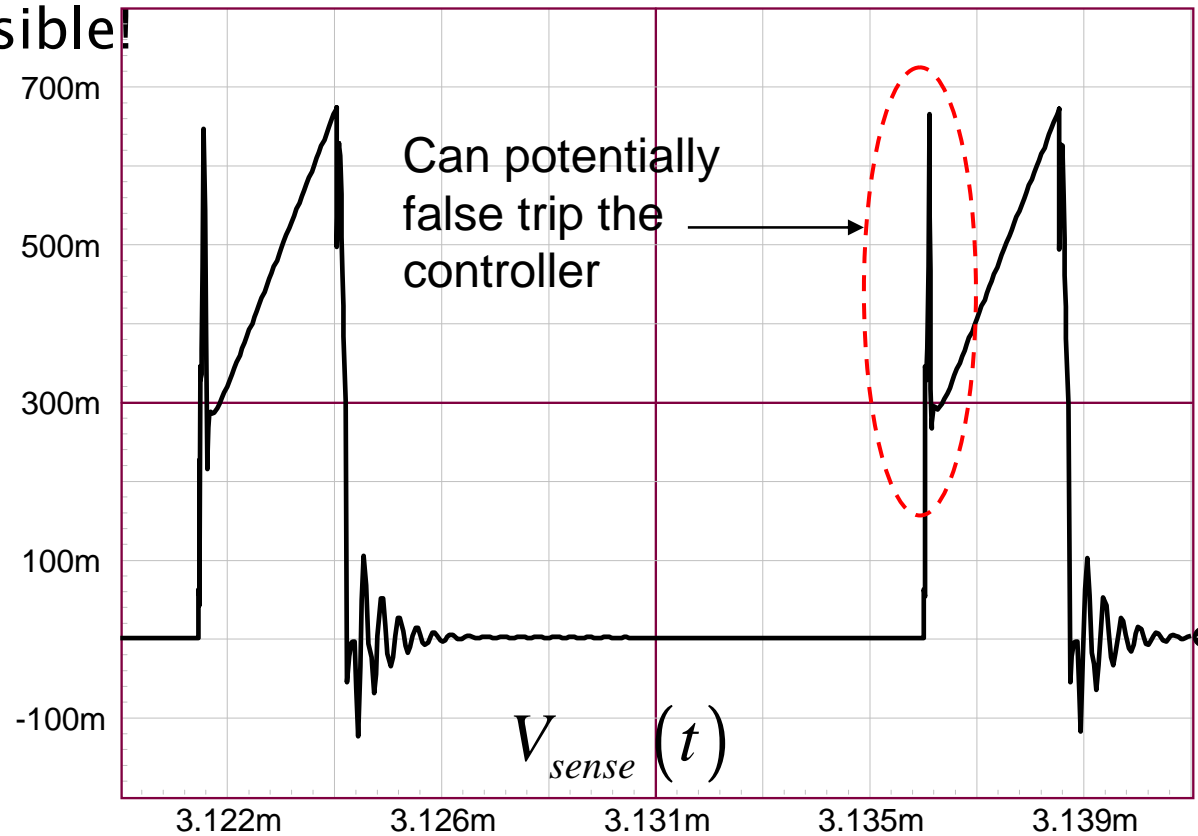
# A Dirty Inductor Current Signal

- ❑ The inductor current is sensed with a resistor, a transformer...
- ❑ This information is affected by parasitics: false tripping possible!



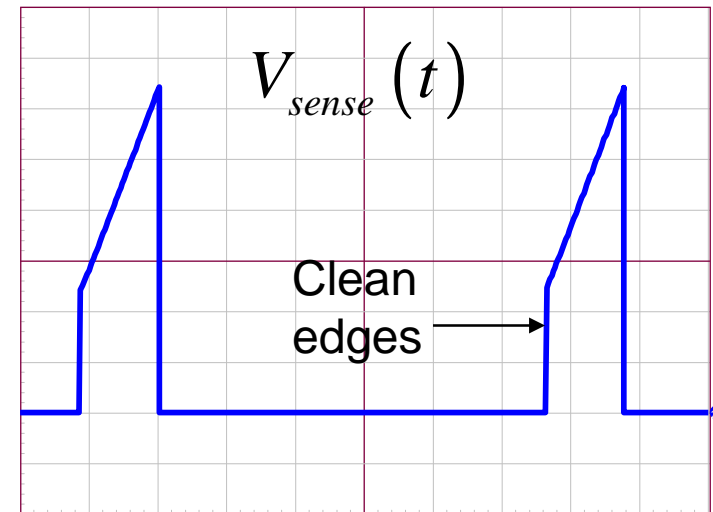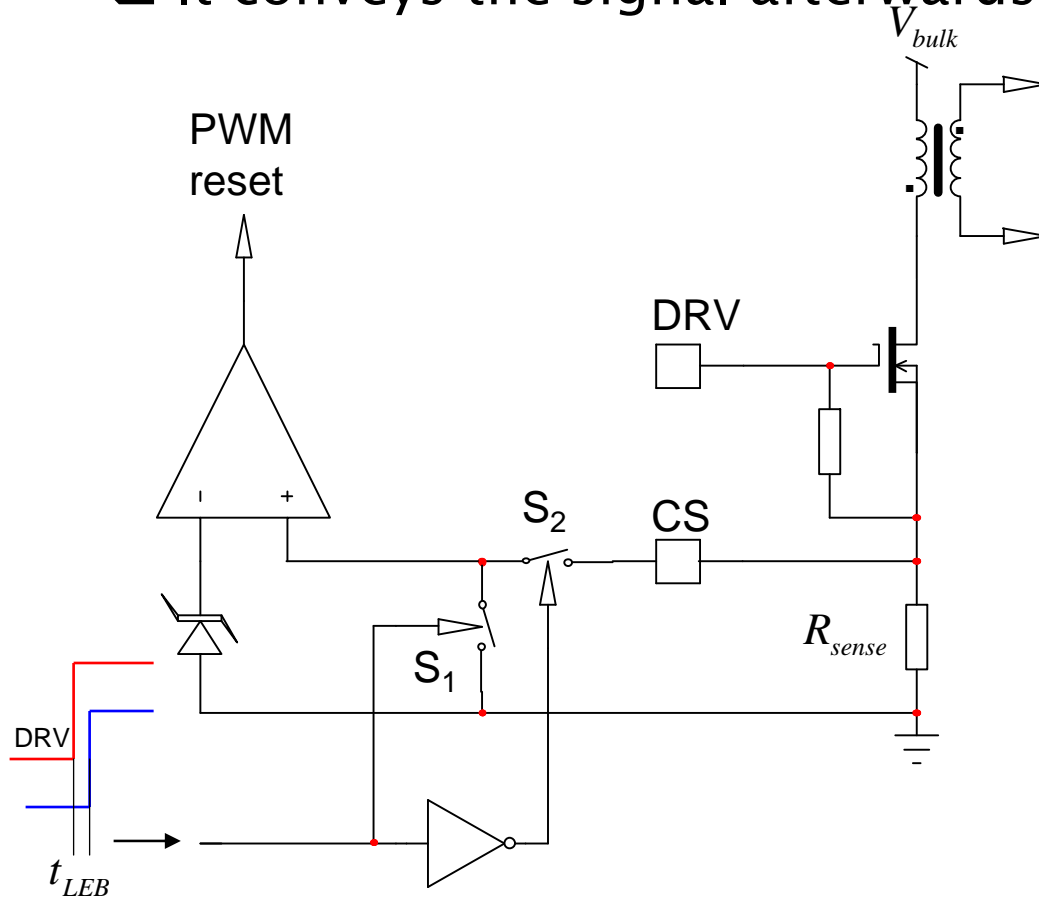
# The LEB Cleanses the Signal

- ❑ A circuit blinds the controller at turn-on for a small time ( $\approx 250$  ns)
- ❑ It conveys the signal afterwards: Leading Edge Blanking


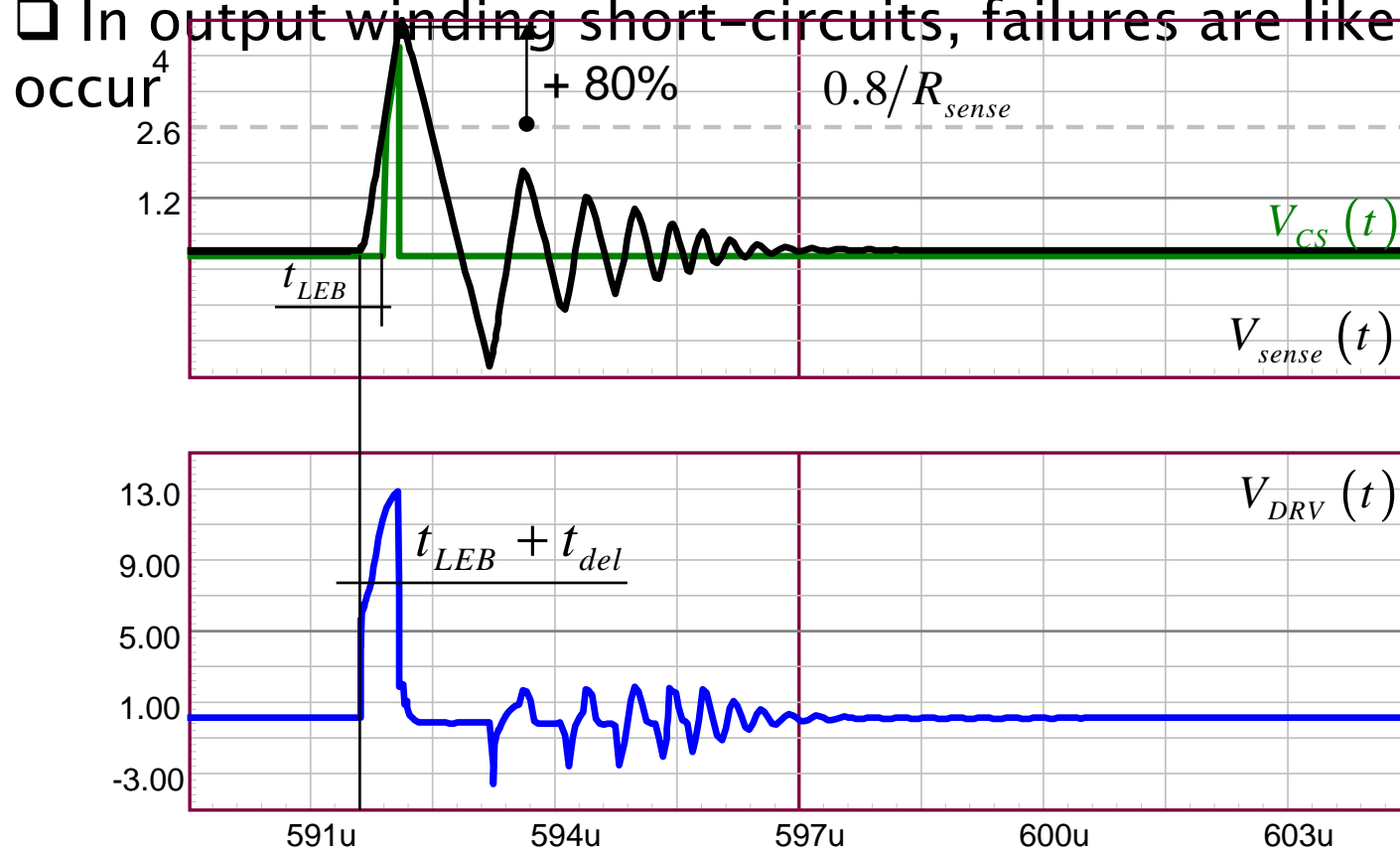
# It Limits the Minimum Duty-Ratio


- During the LEB duration, the controller is completely blind!
- In output winding short-circuits, failures are likely to occur



- $t_{LEB} + t_{del}$  sets the minimum duty-ratio: cannot go lower,  $t_{on,min}$
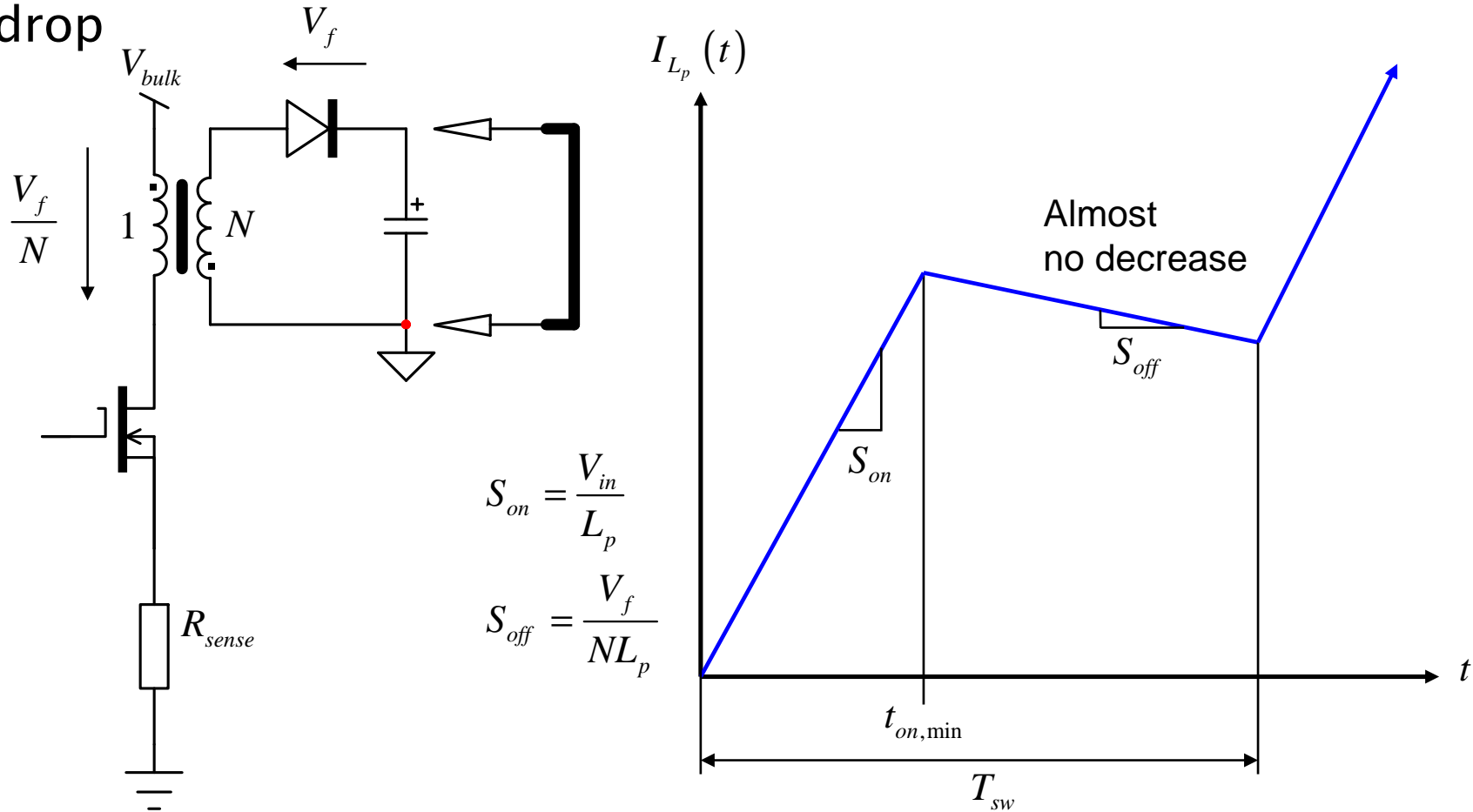
# If the Primary Inductor is too Low...


- ❑ In short-circuit situations, you reflect the diode forward drop




- ❑ If you hit the minimum on-time, you cannot limit the current!
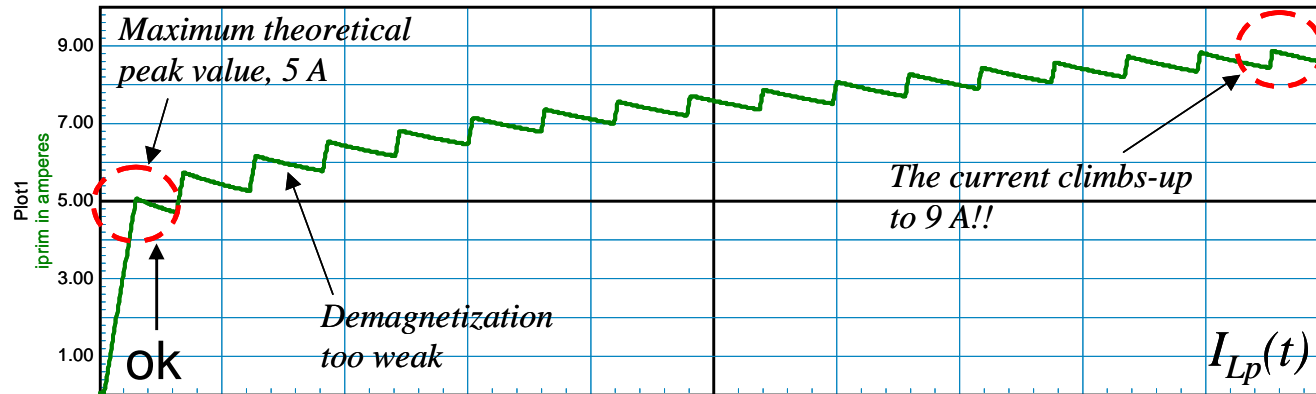
# The Primary Current Runs out of Control

- ❑ The current current climbs cycle by cycle until smoke appears!




Chris Basso first design...

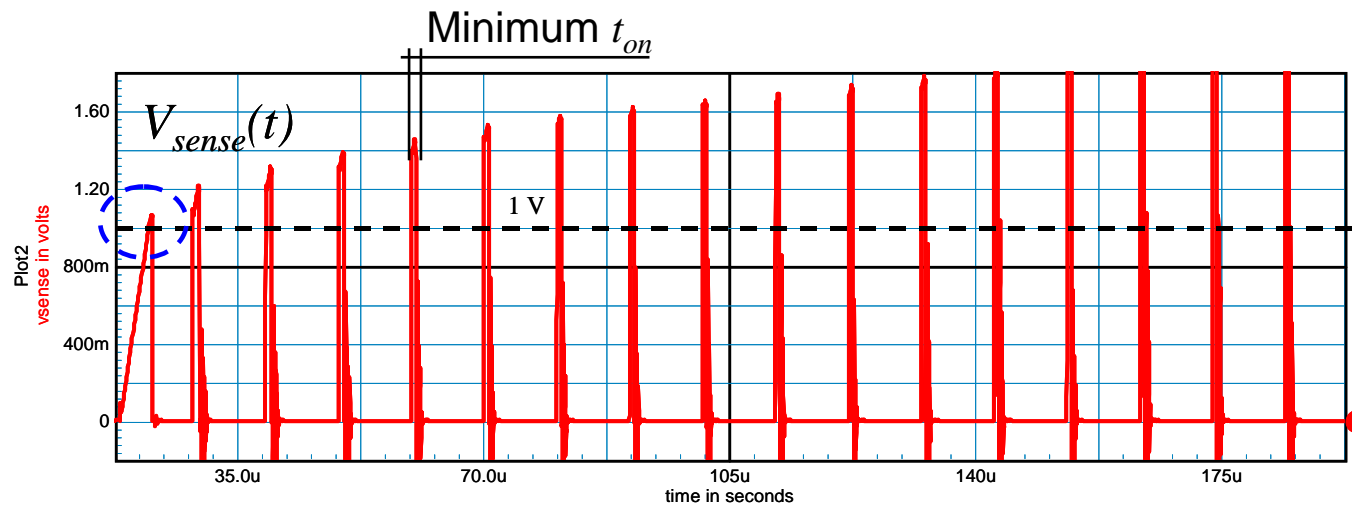
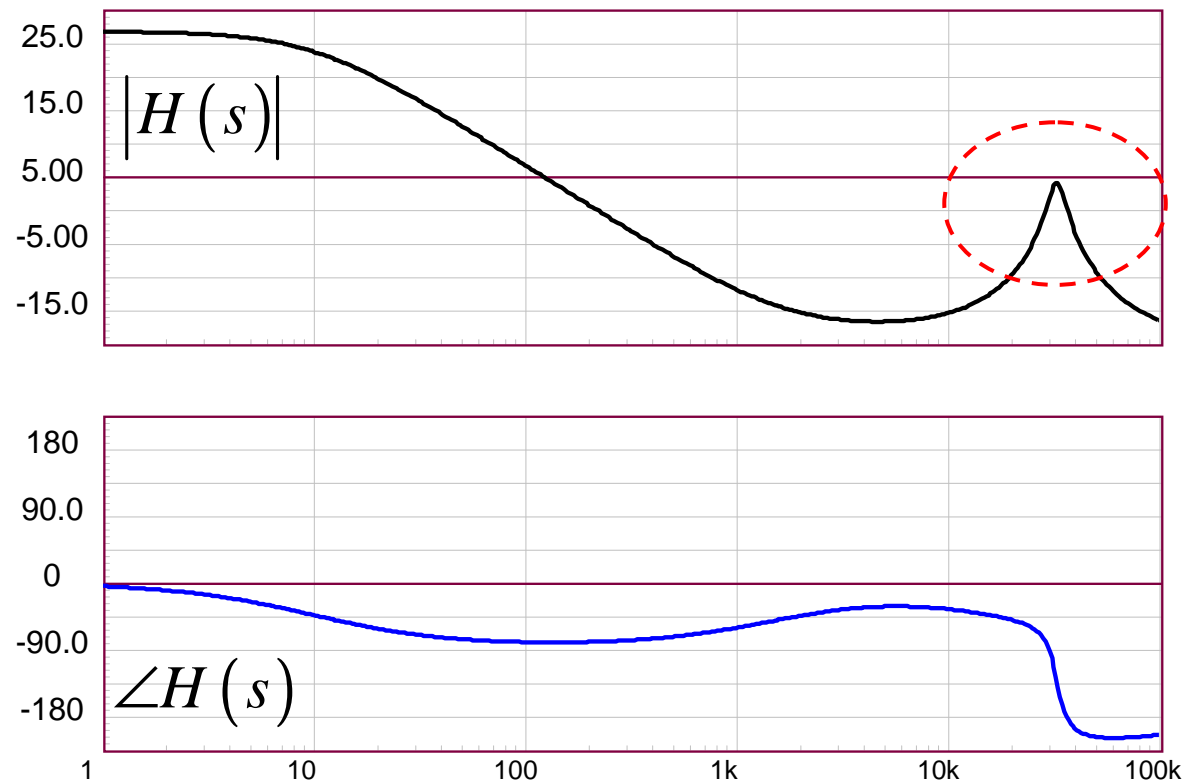
# Sub-Harmonic Oscillations


- ❑ Ac analysis shows a first-order system at  $f_c \ll F_{sw}/2$
- No  $LC$  peaking anymore as in CCM voltage mode
- But a subharmonic peaking at  $F_{sw}/2$  now appears



Flyback power stage in CCM
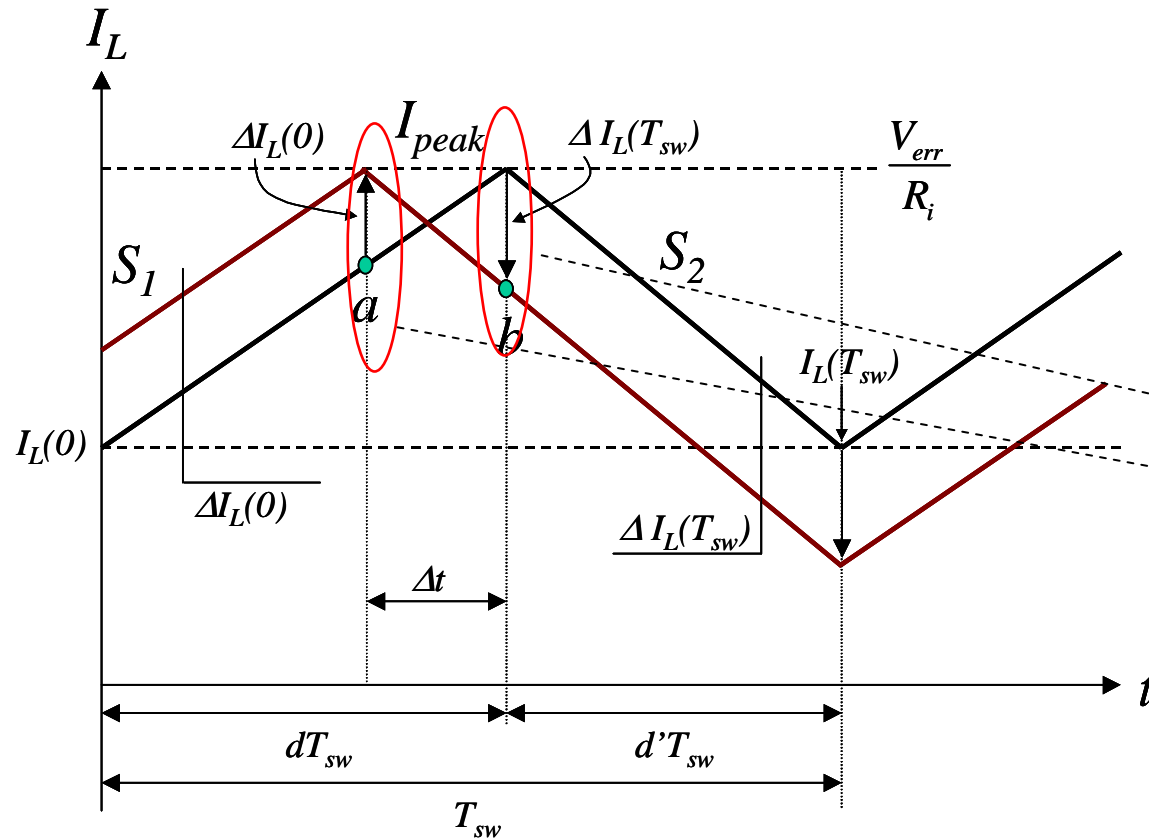
# Instability Depends on Duty-Ratio

- The condition for instability is: CCM operation + duty-ratio > 50%



$$I_{peak} = a + S_1 \Delta t$$

$$b = I_{peak} - S_2 \Delta t$$

Solving  
 $\Delta t$

$$\frac{I_{peak} - a}{S_1} = \frac{I_{peak} - b}{S_2}$$


$$\frac{\Delta I_L(0)}{S_1} = \frac{\Delta I_L(T_{sw})}{S_2}$$

$$\frac{S_2}{S_1} = \frac{d}{d'}$$


$$\Delta I_L(nT_{sw}) = \Delta I_L(0) \left( -\frac{d}{d'} \right)^n$$
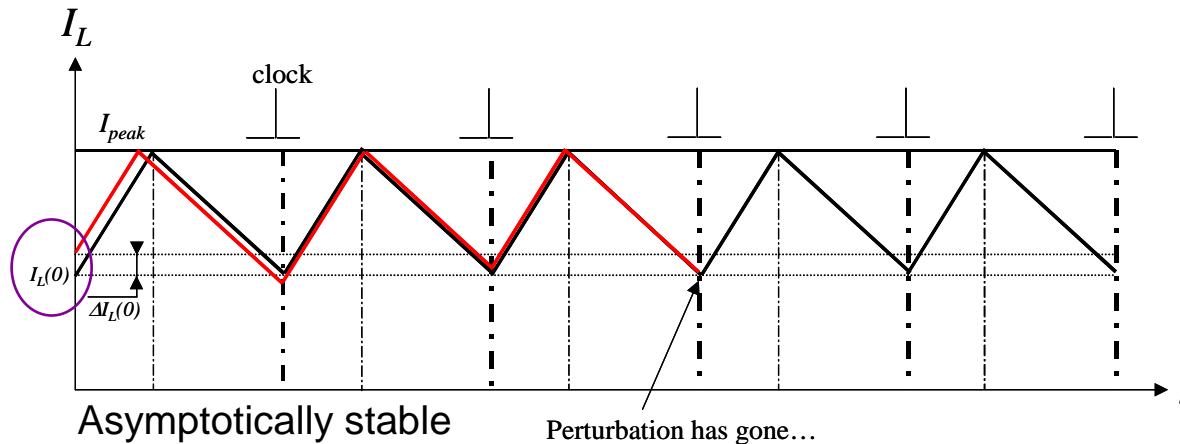
# Instability Depends on Duty-Ratio

- With a duty-ratio below 50%, perturbation naturally dies out ...



Duty-ratio < 50%

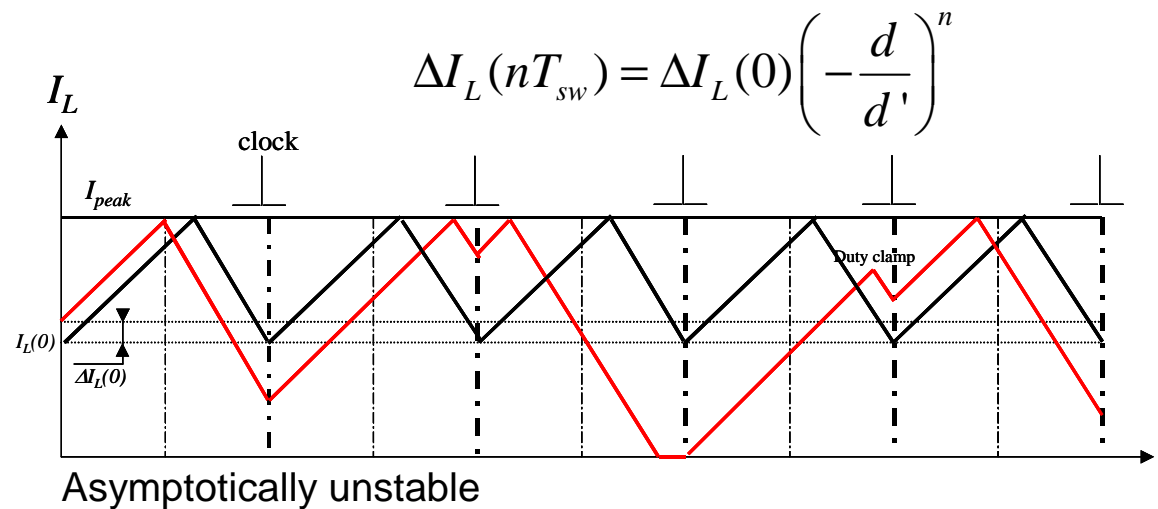


Duty-ratio > 50%



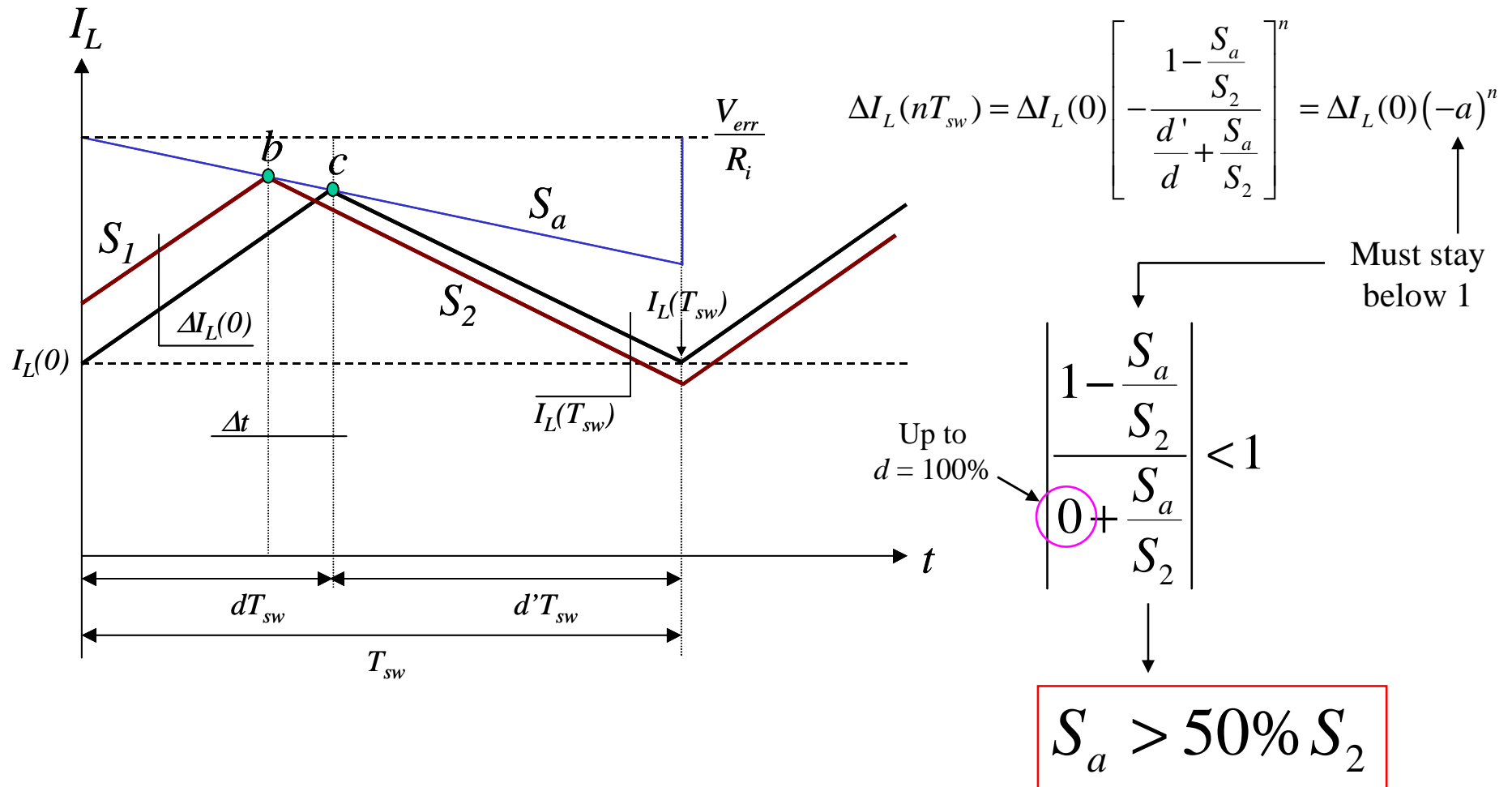
# The Cure is in the Ramp

- Injecting a ramp on the feedback signal, damping is obtained


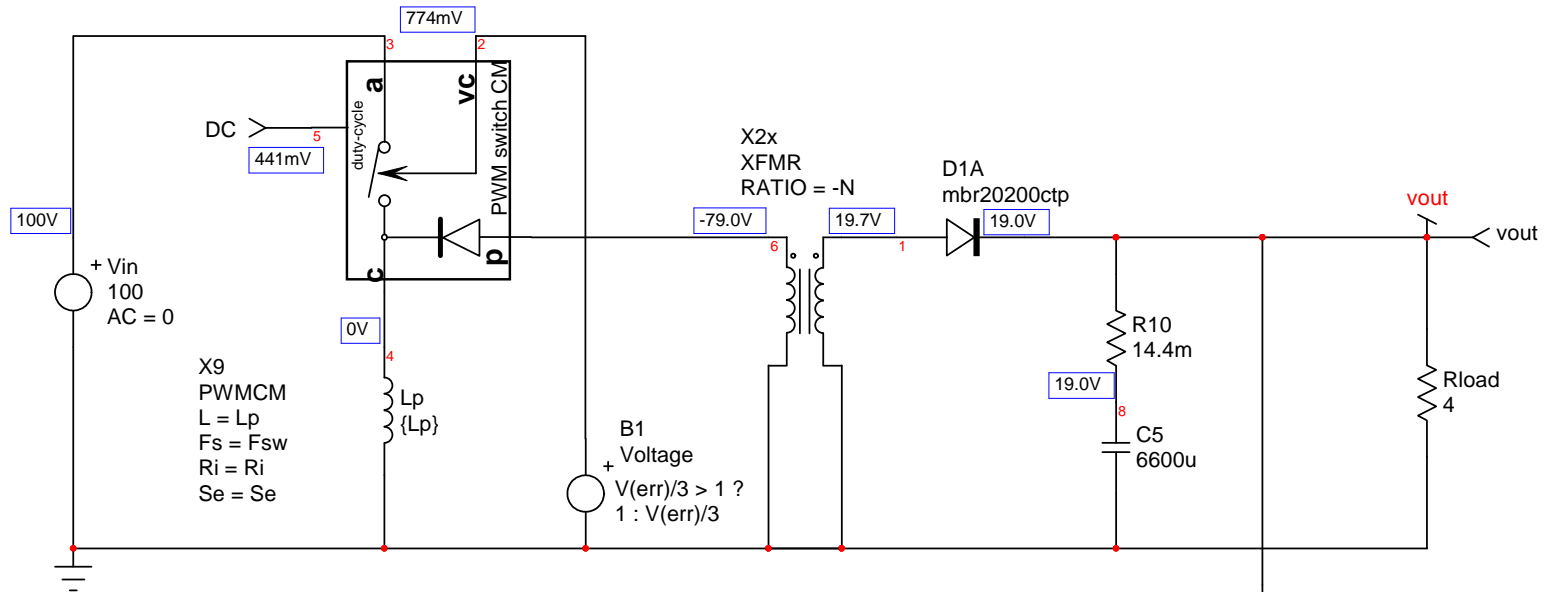
# A Model to Simulate a Flyback Converter


- ❑ A SPICE model can predict subharmonic instabilities



parameters


$V_{out}=19$   
 $S_{off}=(V_{out}/(N*L_p))*R_i$

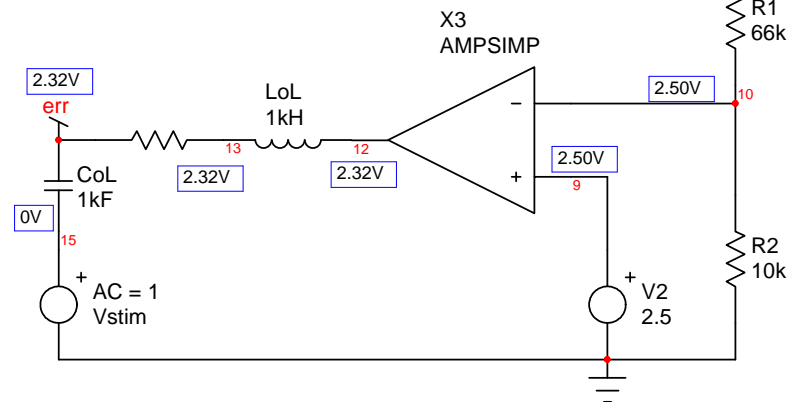$N=250m$   
 $F_{sw}=65k$   
 $L_p=350u$   
 $R_i=250m$   
 $A=0.5$   
 $S_e=A*S_{off}$



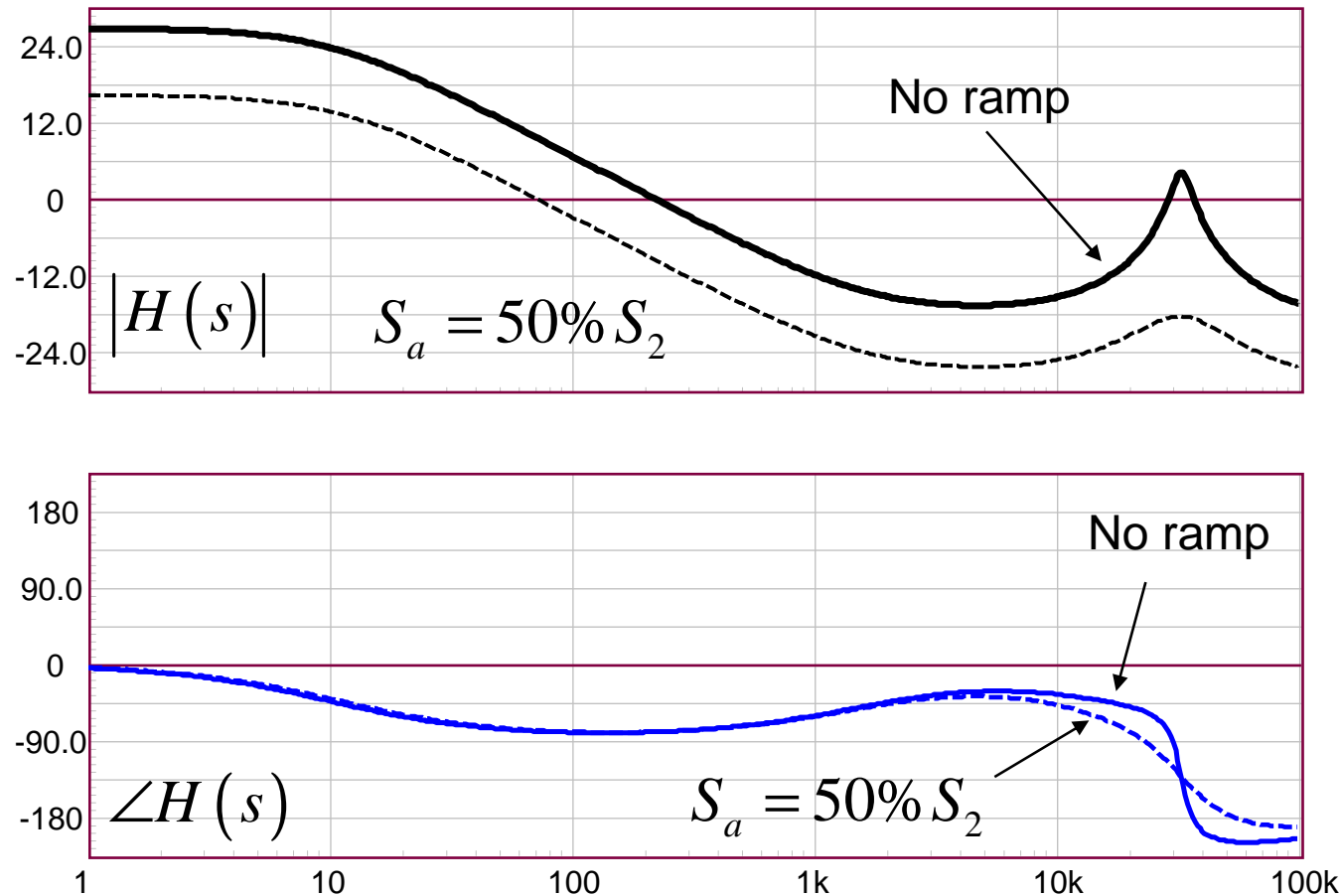
# Simulation Results of the CCM Flyback

- ❑ As ramp is injected, the double-pole  $Q$  is damped
- ❑ Injecting more ramp turns the converter into voltage-mode



# Modern Circuits Include Slope Compensation

- A simple resistor in series with current sense resistor does the job

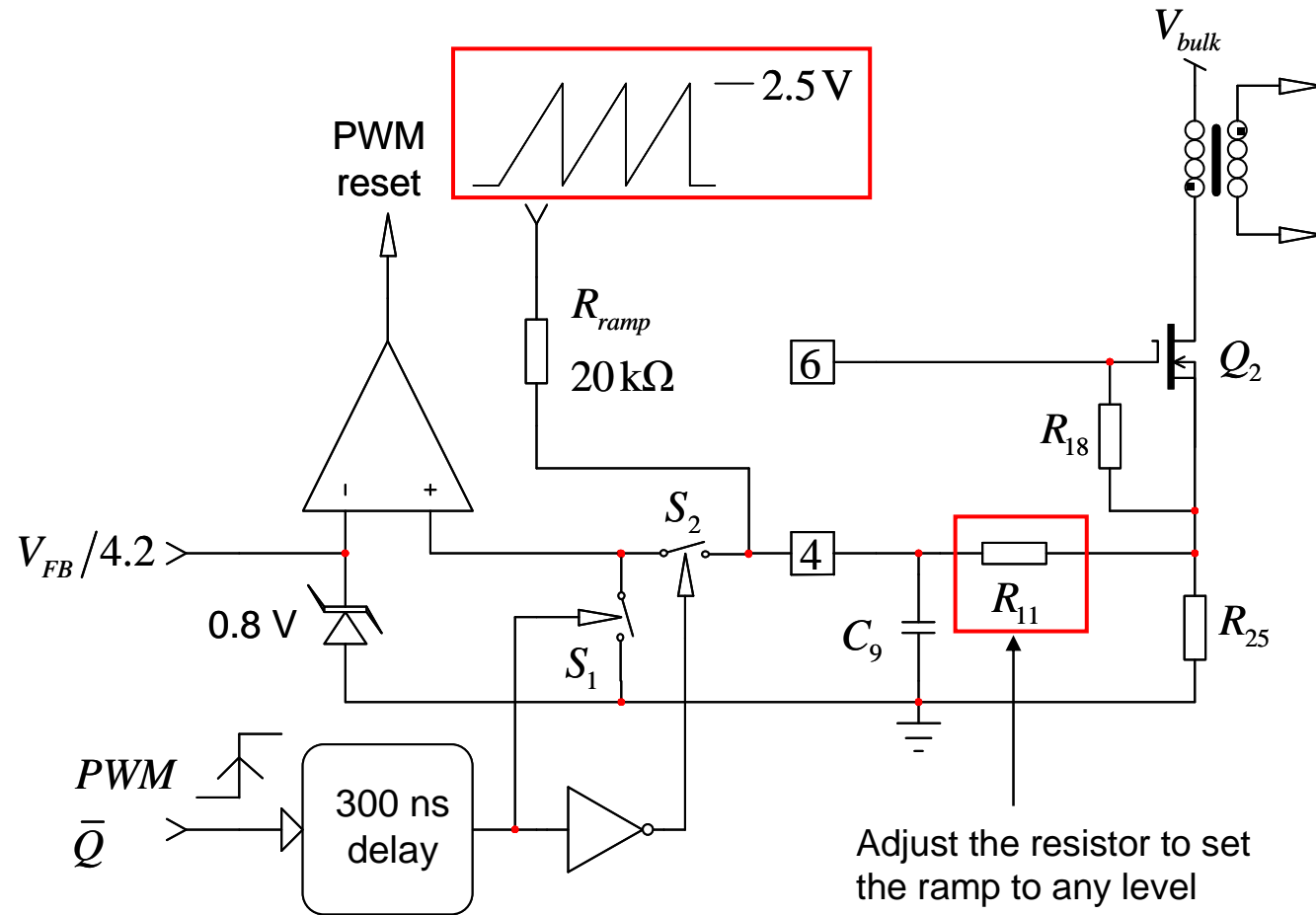

NCP1250

---


# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?**
- More Power than Needed
- The Frequency Response
- Compensating With the TL431



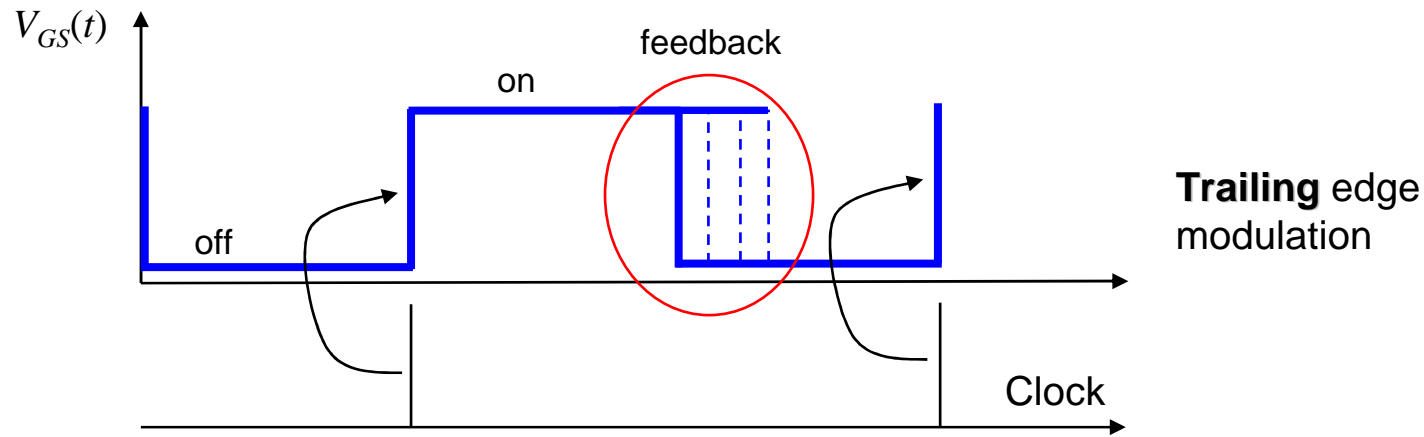
# Modulation Strategies

- The most popular modulation strategy is trailing-edge





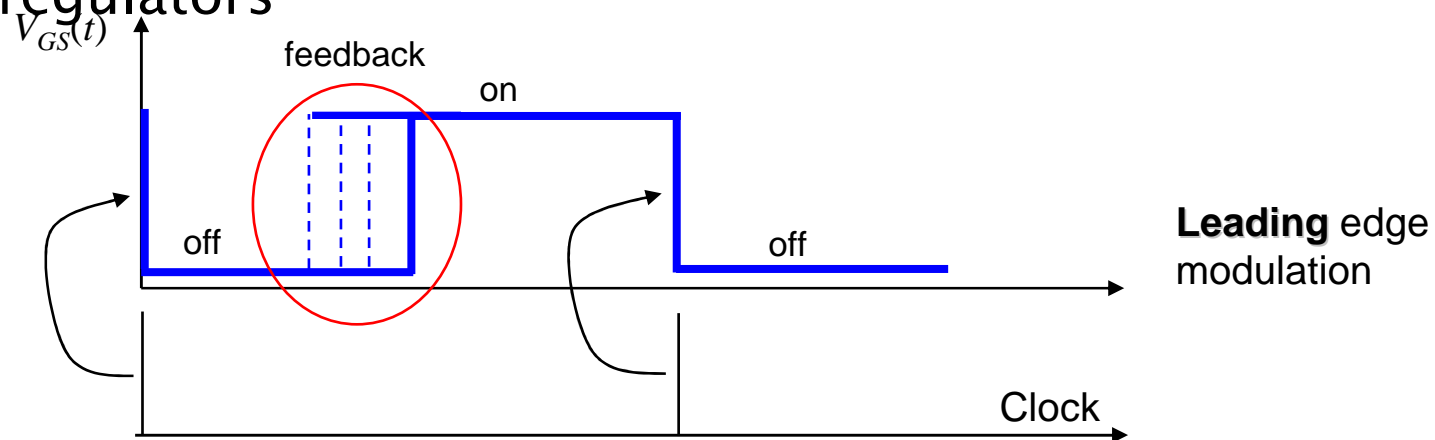- Leading-edge modulation often appears in post-regulators



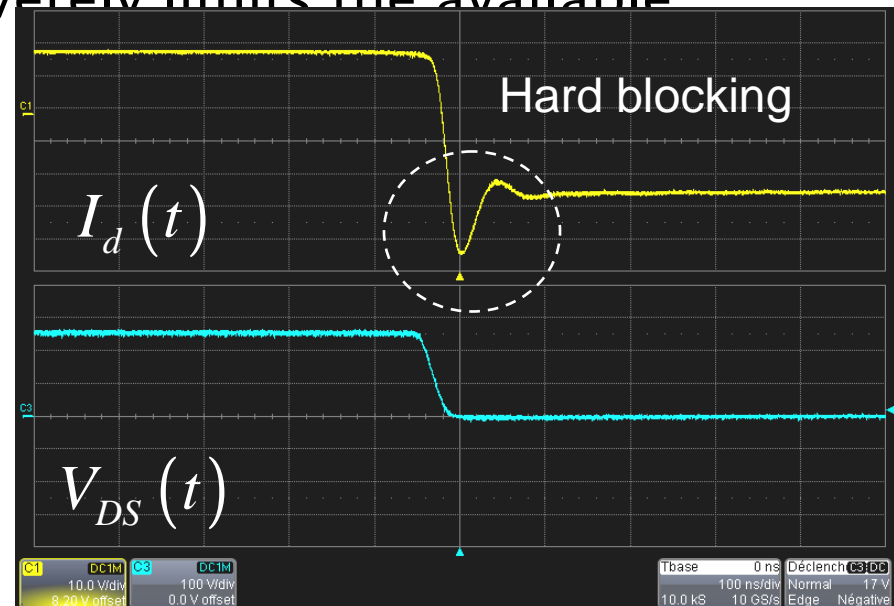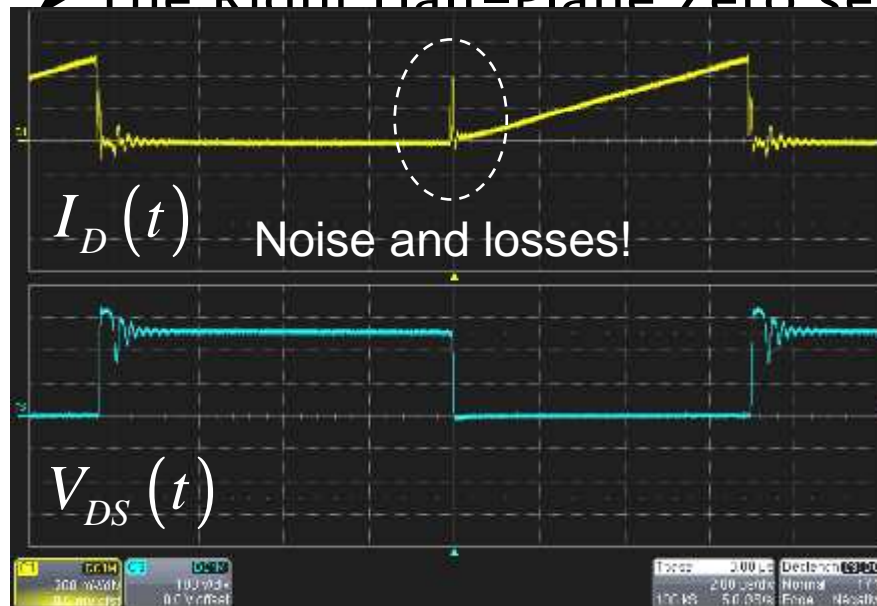
# Fixed Frequency Operation

- ❑ The vast majority of converters use fixed-frequency operation
  - Switching losses depend on frequency: high frequency, high losses!
  - Capacitive losses are a brake to efficiency improvement
  - CCM operation induces high losses on the secondary diode
  - Potential shoot-through hampers synchronous rectification
  - The Right Half-Plane Zero severely limits the available


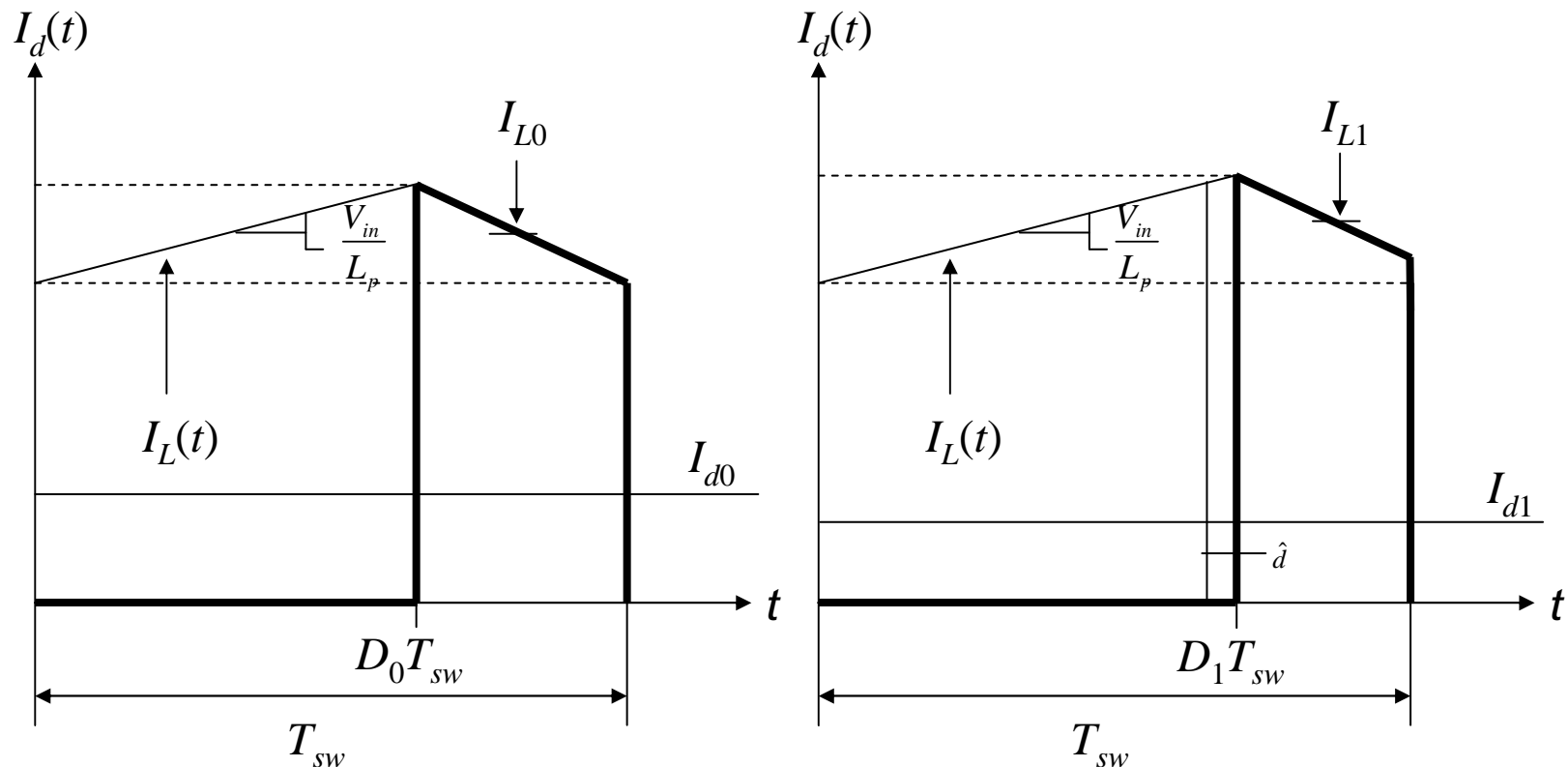
# The Right-Half-Plane Zero

- In a CCM flyback,  $I_{out}$  is delivered during the off-time:





- If  $D$  brutally increases,  $D'$  reduces and  $I_{out}$  drops!

- What matters is the inductor current slew-rate  $\longrightarrow \frac{d\langle V_L \rangle(t)}{dt}$



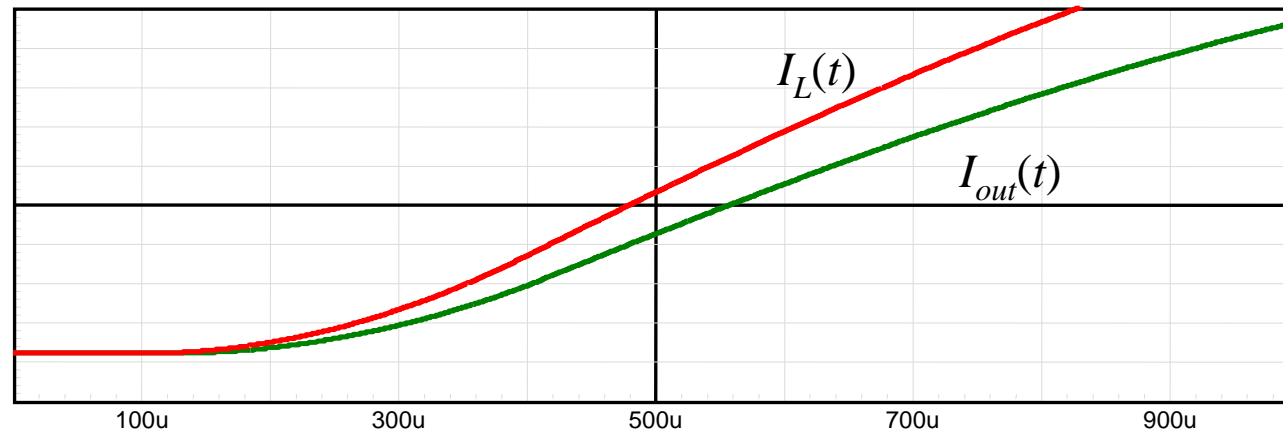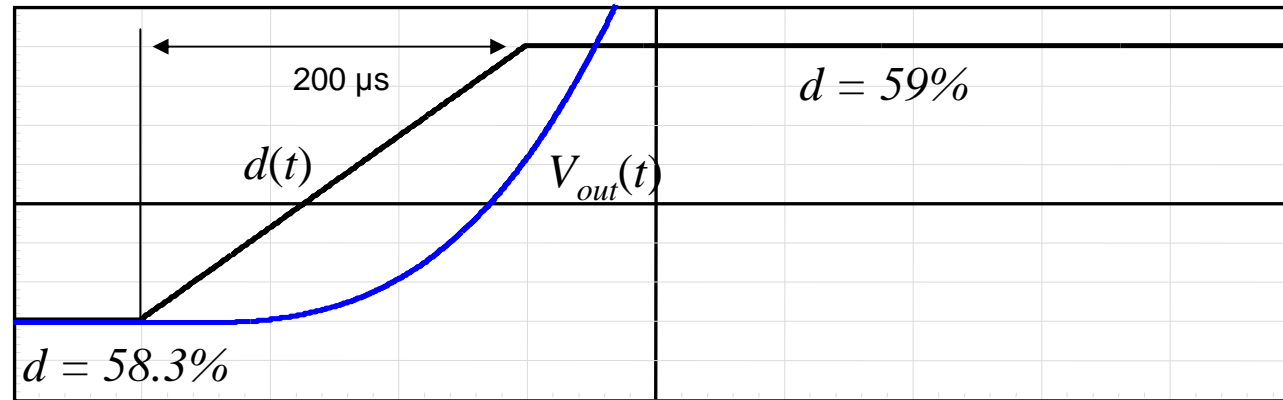
# Processing the Output Power Demand

- If  $I_L(t)$  can rapidly change,  $I_{out}$  increases when  $D$  goes up



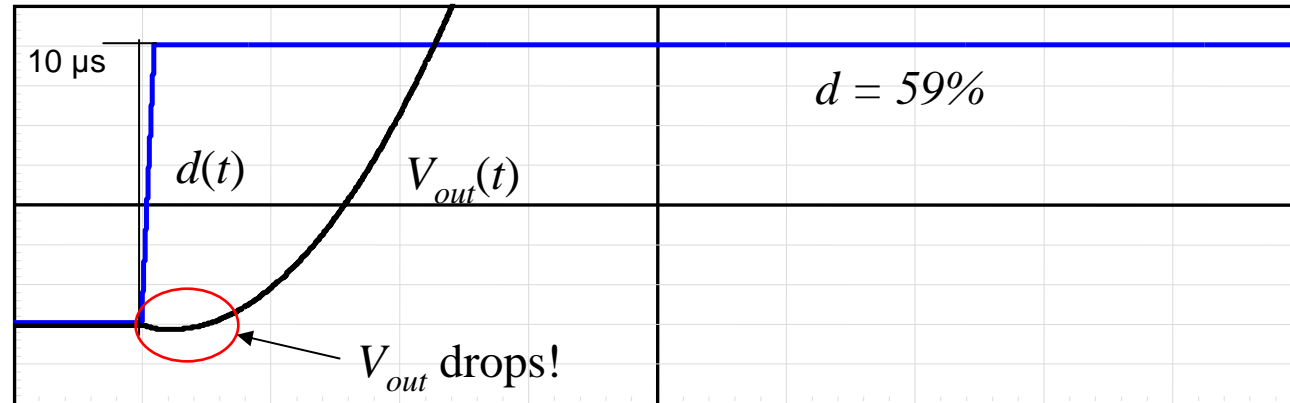
# Failing to Increase the Current in Time

- If  $I_L(t)$  is limited because of a big  $L_p$ ,  $I_{out}$  drops when  $D$  increases



$d = 58.3\%$

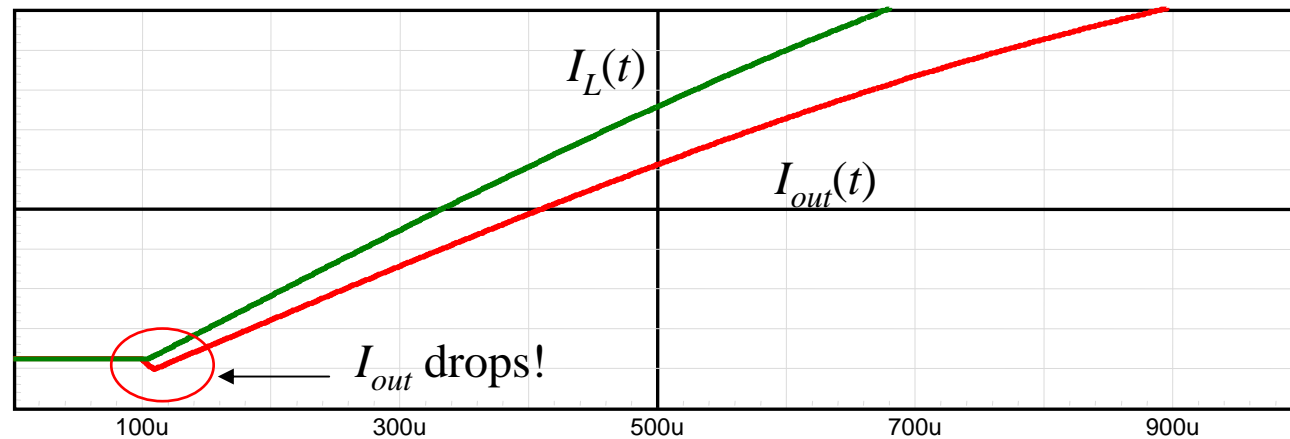

# The RHPZ is a Positive Root

- Small-signal equations can help us to formalize it

Voltage mode

$$\frac{\hat{v}_{out}(s)}{\hat{d}(s)} = G_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 - \frac{s}{\omega_{z2}}\right)}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

The negative sign indicates a positive root!

$$\omega_{z2} = \frac{R_{load} D'^2}{N^2 D L_p}$$

Current mode


$$\frac{\hat{v}_{out}(s)}{\hat{v}_c(s)} = G_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 - \frac{s}{\omega_{z2}}\right) \left(1 + \frac{s}{\omega_{z3}}\right)}{D(s)}$$

- Voltage mode or current mode, the RHPZ remains the same


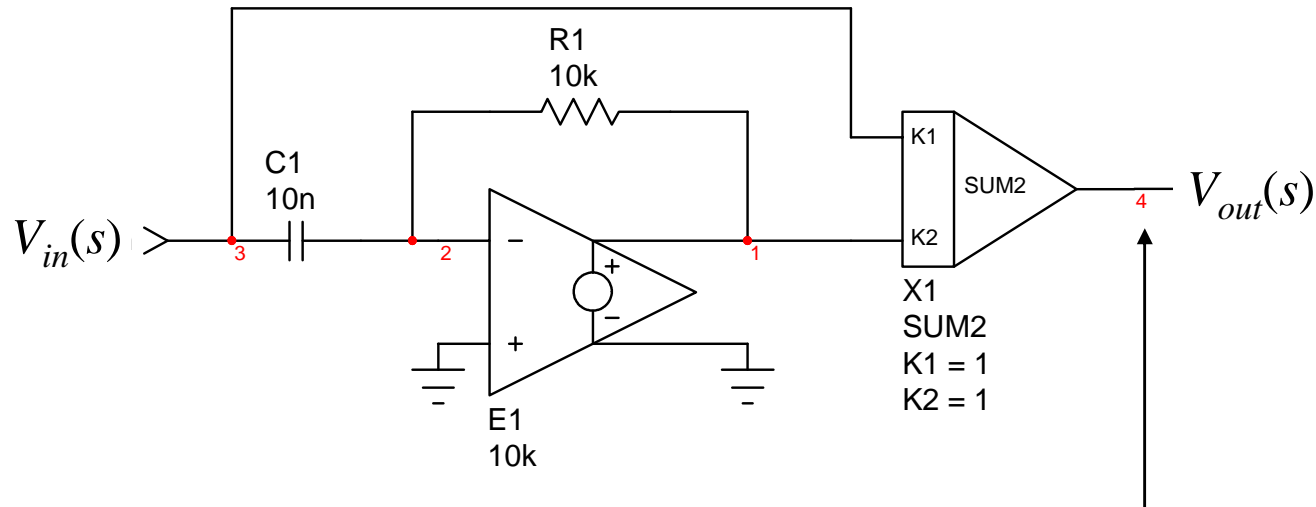
# Simulating the RHPZ


- ❑ To limit the effects of the RHPZ, limit the duty ratio slew-rate
- ❑ Choose a crossover frequency equal to 20-30% of RHPZ position
- A simple RHPZ can be easily simulated:



$$V_{out}(s) = V_{in}(s) - V_{in}(s) \frac{R_1}{1 + sC_1} = V_{in}(s) \left( 1 - \frac{s}{\omega_0} \right)$$
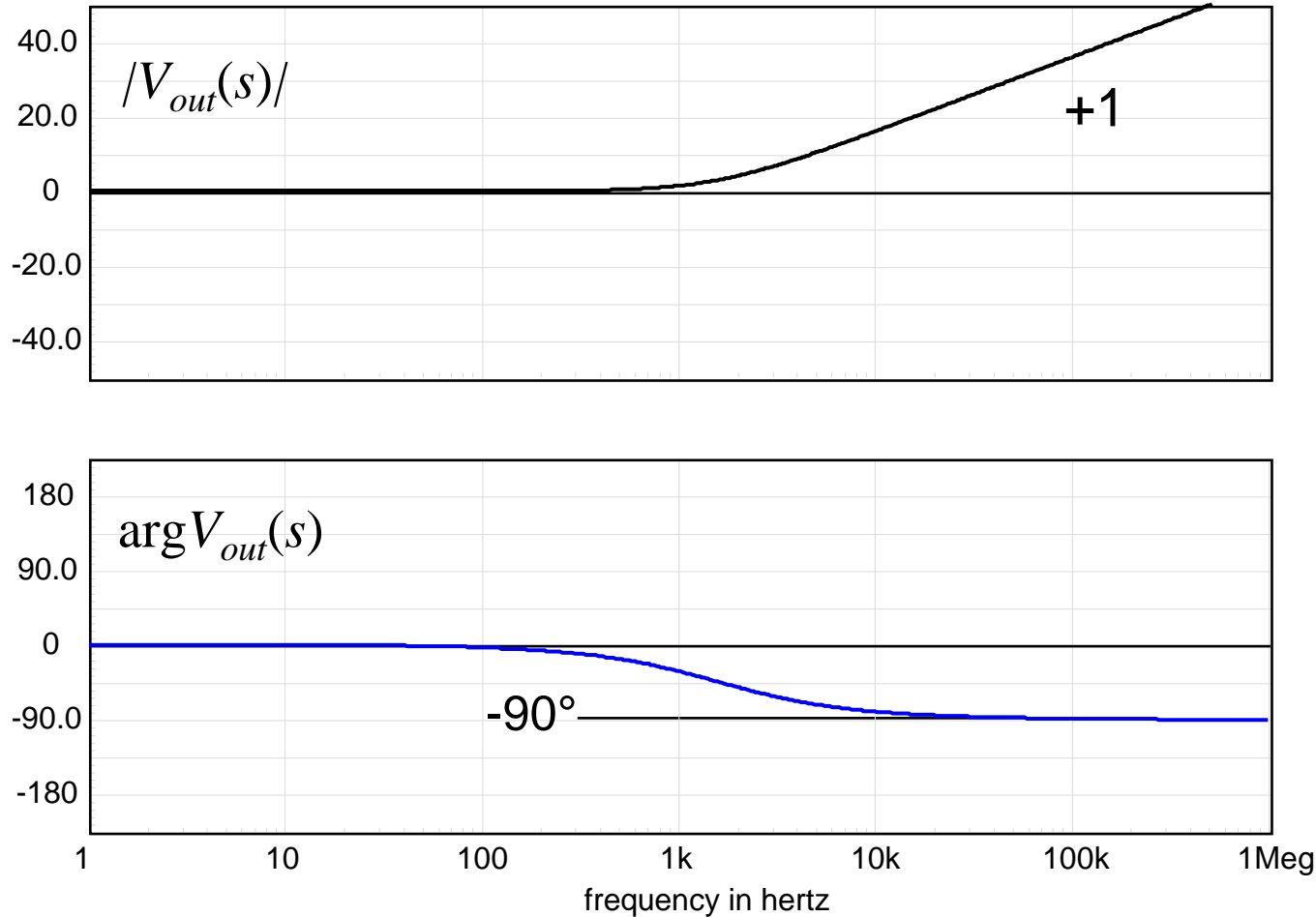
# A Zero Producing a Phase Lag

□ With a RHPZ we have a boost in gain but a lag in phase!



LHPZ

$$G(s) = 1 + \frac{s}{\omega_0}$$


RHPZ

$$G(s) = 1 - \frac{s}{\omega_0}$$


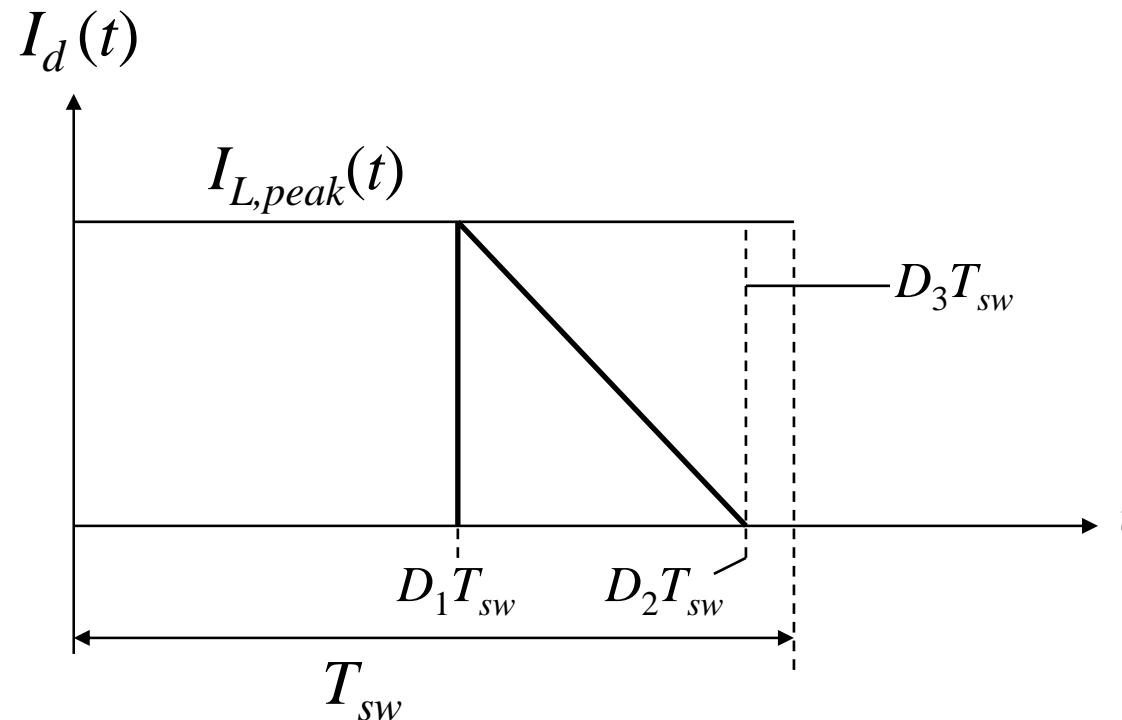
# Is There a RHPZ in DCM?


- A RHPZ also exists in DCM boost, buck-boost converters...



- When  $D_1$  increases,  $[D_1, D_2]$  stays constant but  $D_3$  shrinks
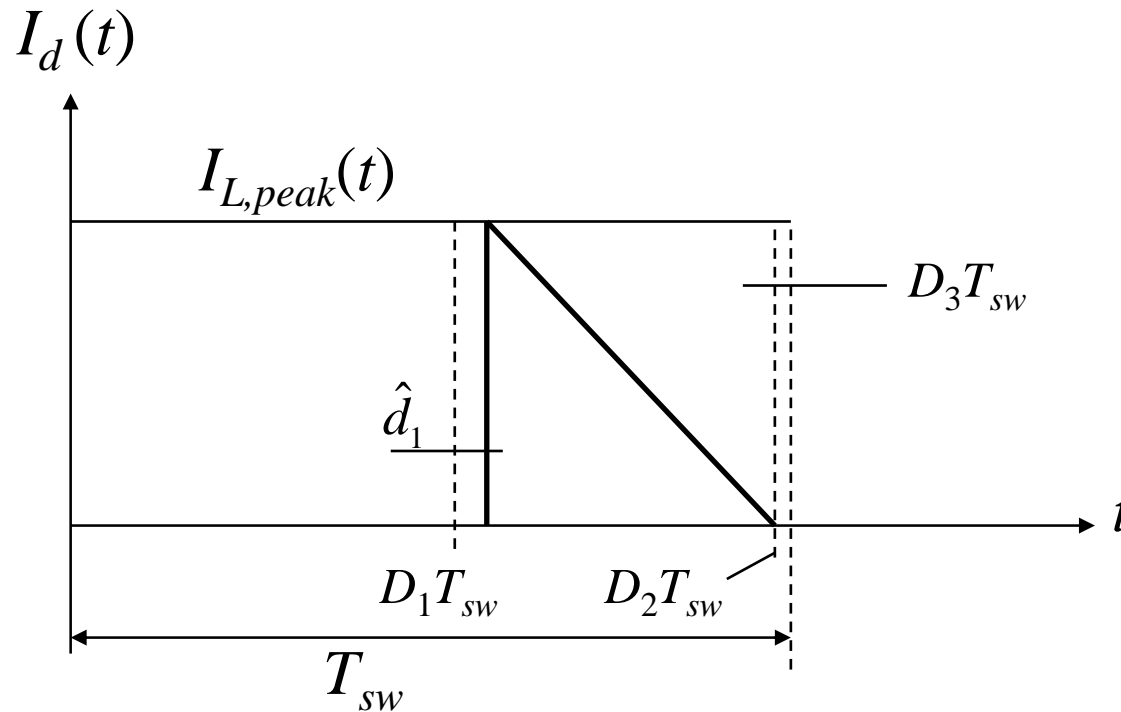
# Is There a RHPZ in DCM?




- The triangle is simply shifted to the right by  $\hat{d}_1$



- The refueling time of the capacitor is delayed and a drop occurs
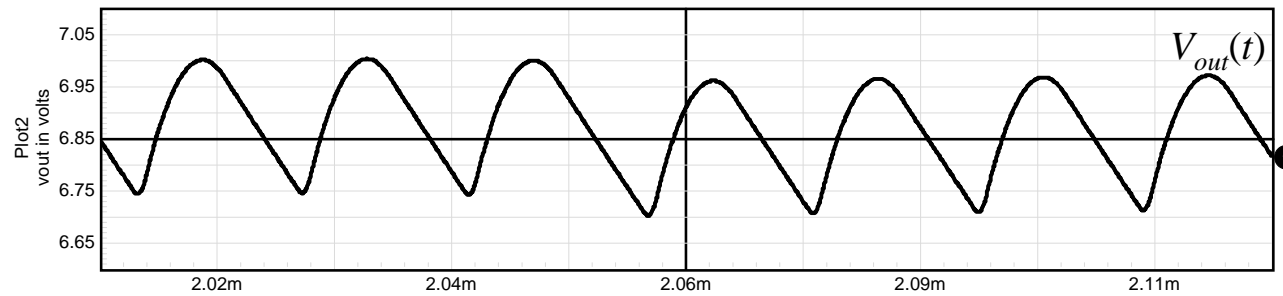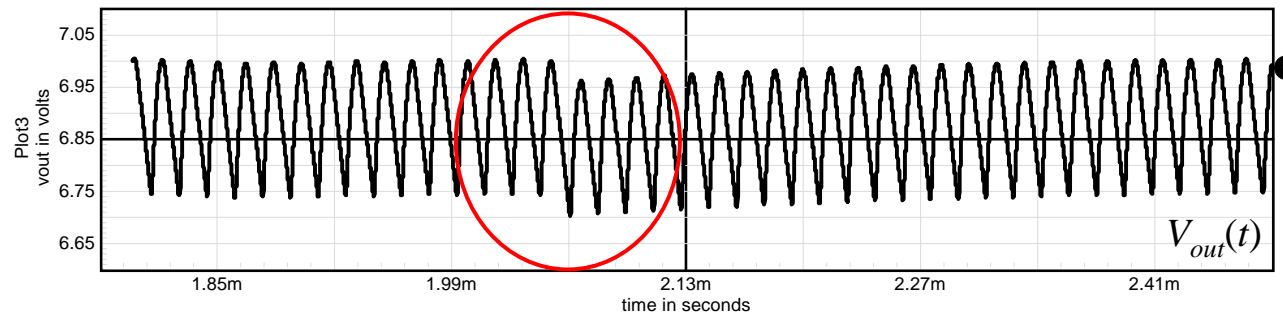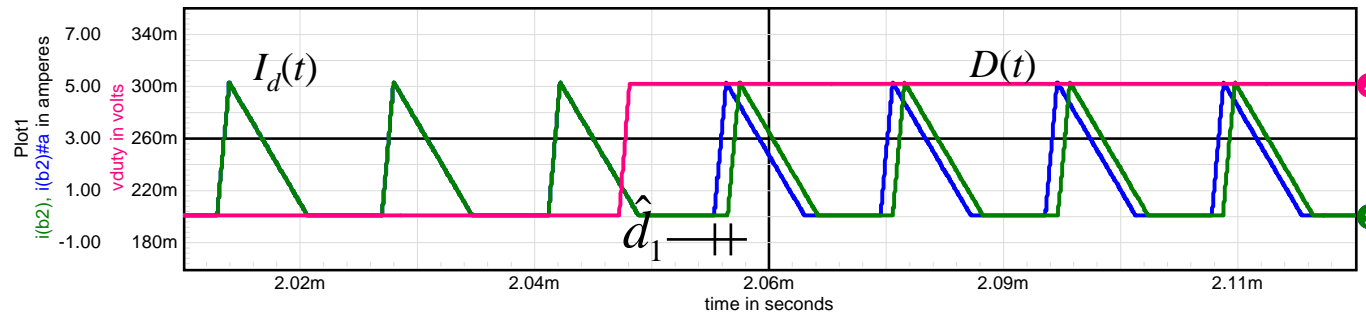
# Is There a RHPZ in DCM?


- If  $D$  increases, the diode current is delayed by  $\hat{d}_1$




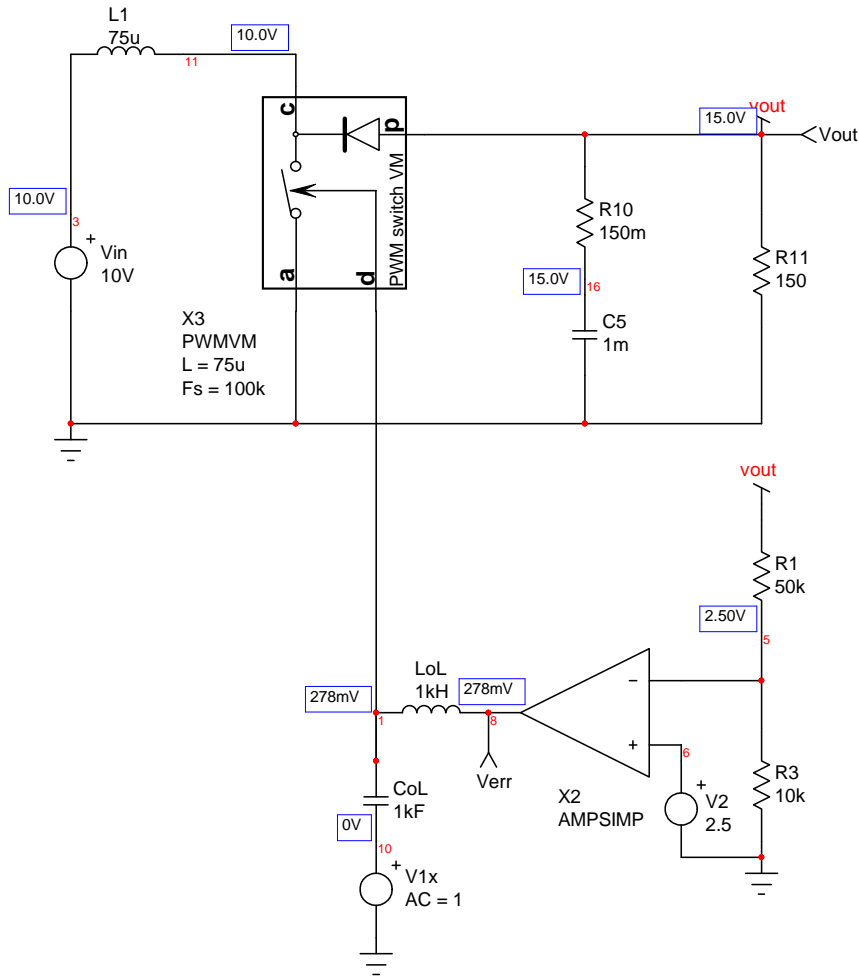
# A Large-Signal Model is Available

- Averaged models can predict the DCM RHPZ



$$\frac{\hat{v}_{out}(s)}{\hat{d}(s)} = H_d \frac{(1+s/s_{z1})(1-s/s_{z2})}{(1+s/s_{p1})(1+s/s_{p2})}$$

$$s_{z1} = \frac{1}{C_{out} R_{ESR}}$$

$$s_{z2} = \frac{R_{load}}{M^2 L}$$

$$s_{p1} = \frac{2M-1}{M-1} \frac{1}{C_{out} R_{ESR}}$$

$$s_{p2} = 2F_{sw} \left( \frac{1-1/M}{D} \right)^2$$


$$H_d = \frac{2V_{out}}{D} \frac{M-1}{2M-1}$$

Merci Vatché!


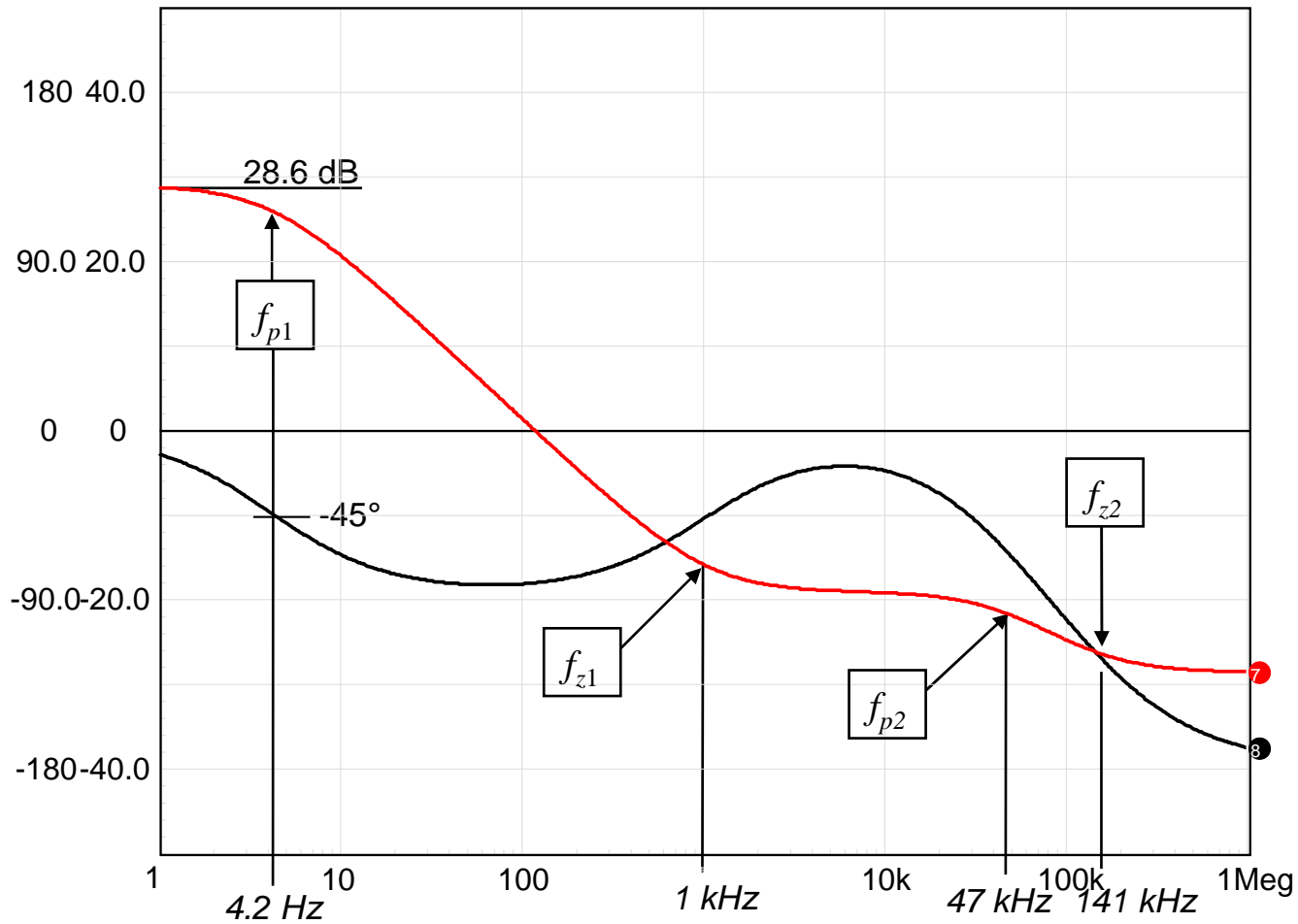
# The Model Predicts it!

□ Averaged models can predict the DCM RHPZ



$$H_d = 28.75 \text{ dB}$$

$$f_{z_1} = 1.06 \text{ kHz}$$

$$f_{z_2} = 141 \text{ kHz}$$



$$f_{p_1} = 4.2 \text{ Hz}$$

$$f_{p_2} = 47.1 \text{ kHz}$$


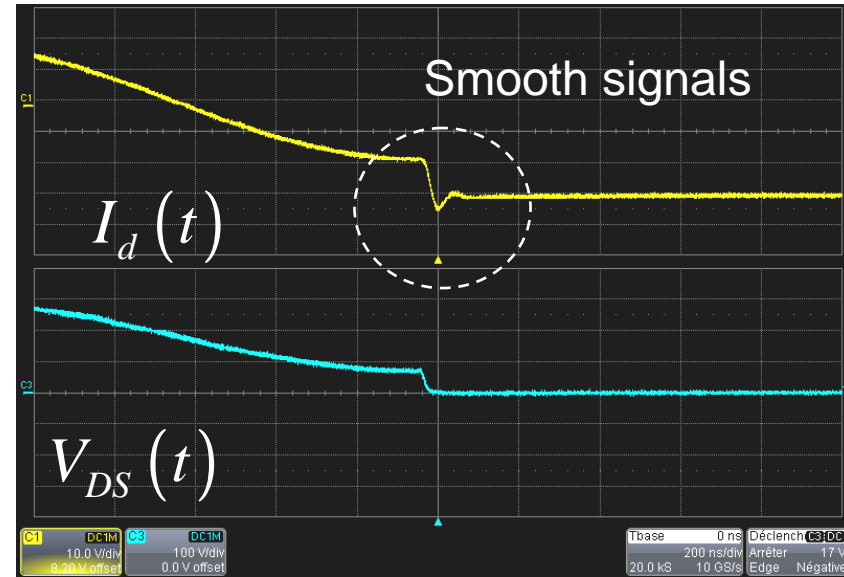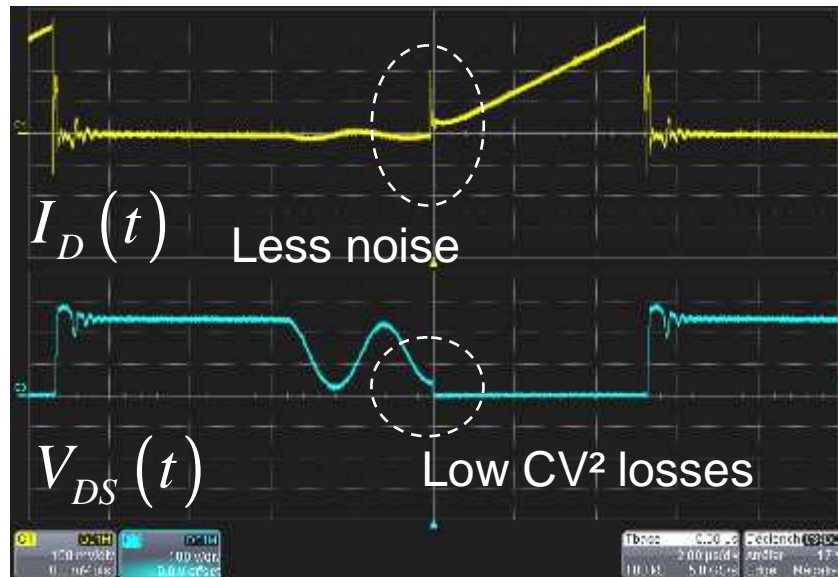
# Going to Variable Frequency


- ❑ More converters are using variable-frequency operation
- ❑ This is known as Quasi-Square Wave Resonant mode: QR
  - Valley switching ensures extremely low capacitive losses
  - DCM operation saves losses on the secondary diode
  - Easier synchronous rectification
  - The Right Half-Plane Zero is pushed to high frequencies



# What is the Principle of Operation?


- ❑ The drain–source signal is made of peaks and valleys
- ❑ A valley presence means:
  - The drain is at a minimum level, capacitors are naturally discharged
  - The converter is operating in the discontinuous conduction mode

Mode

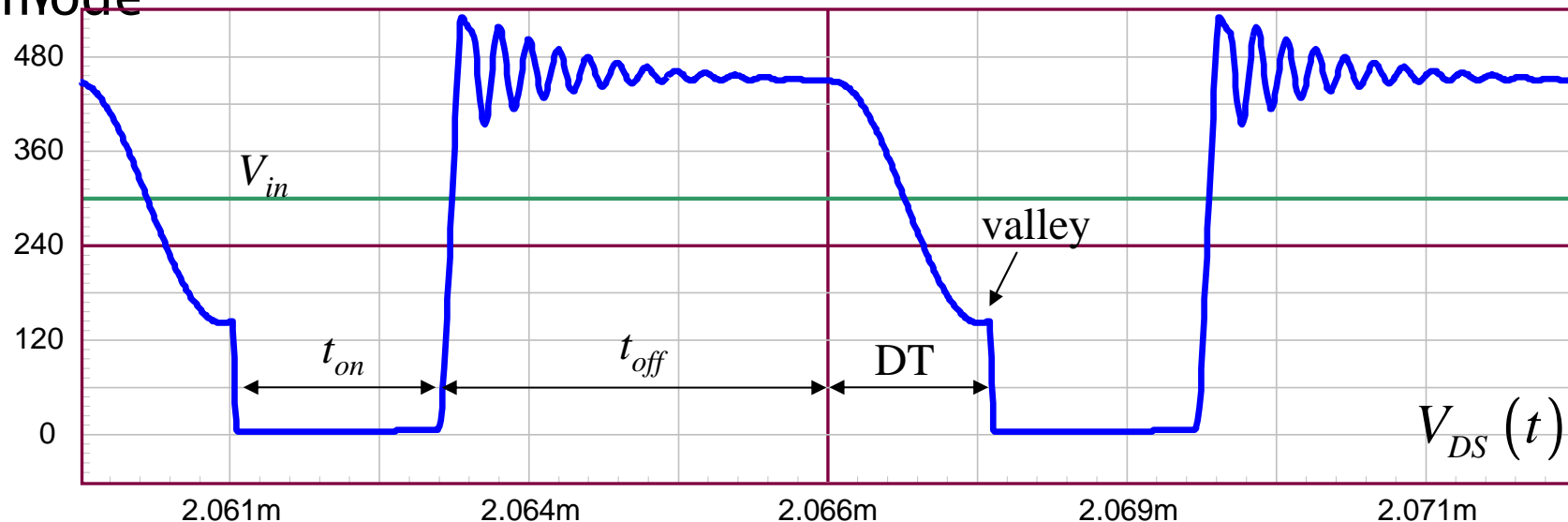


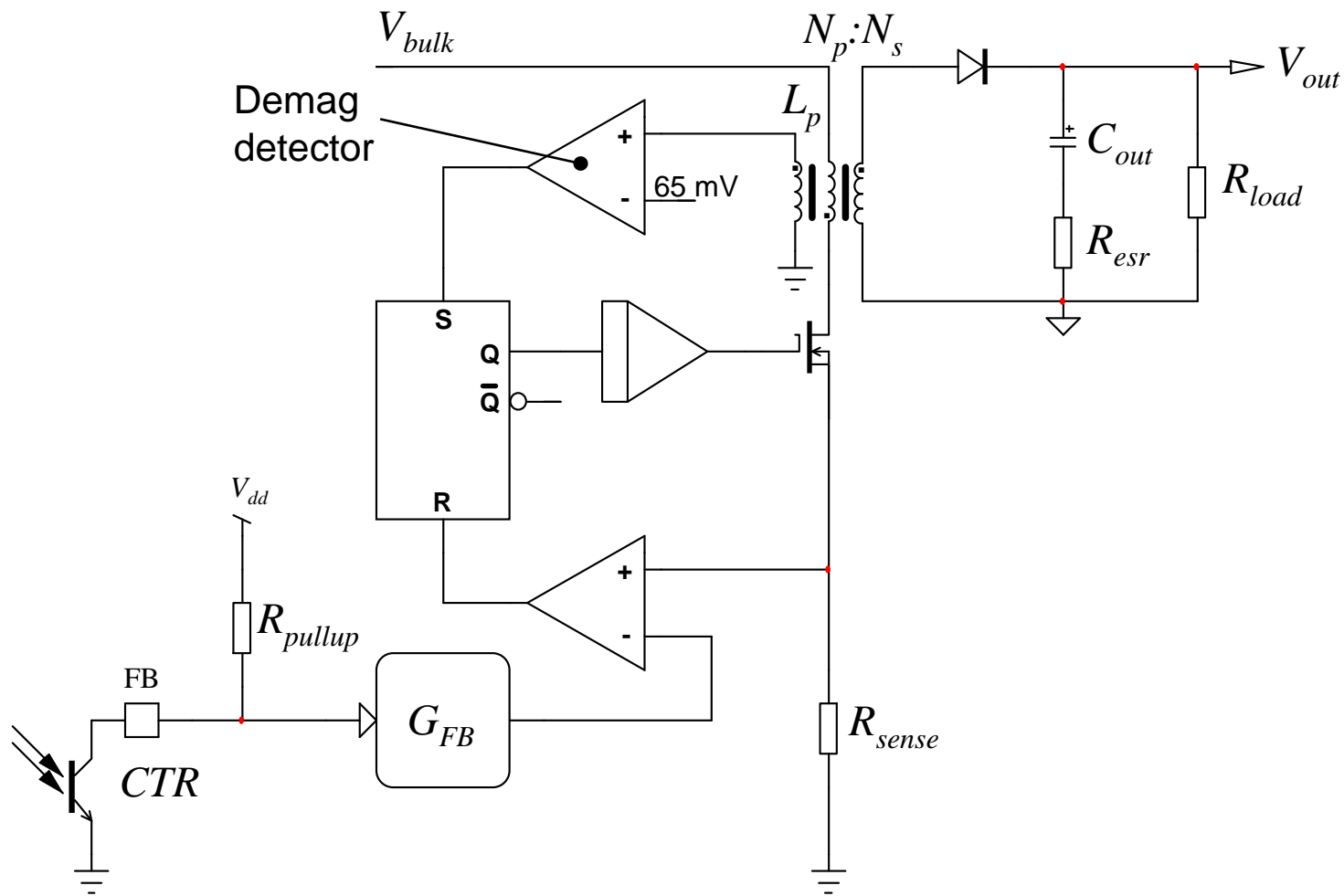
# A QR Circuit Does not Need a Clock

- The system is a self-oscillating current-mode converter



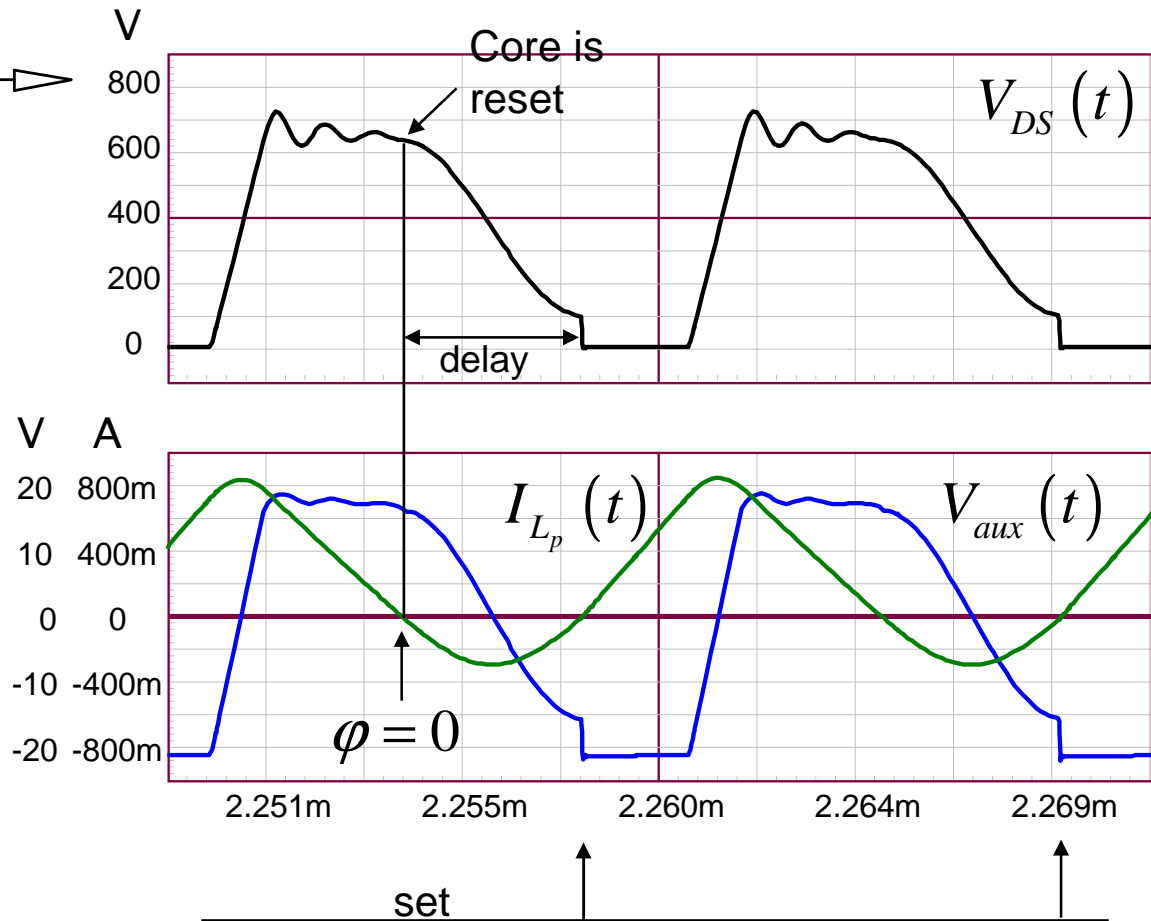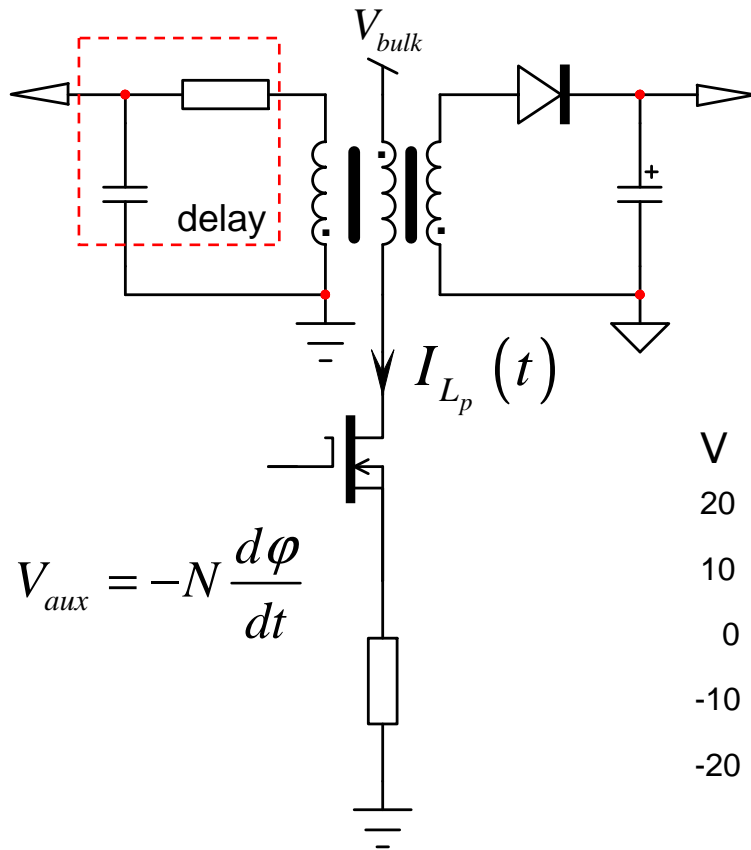
# A Winding is Used to Detect Core Reset

- ❑ When the flux returns to zero, the aux. voltage drops
- ❑ Discontinuous Mode is always maintained


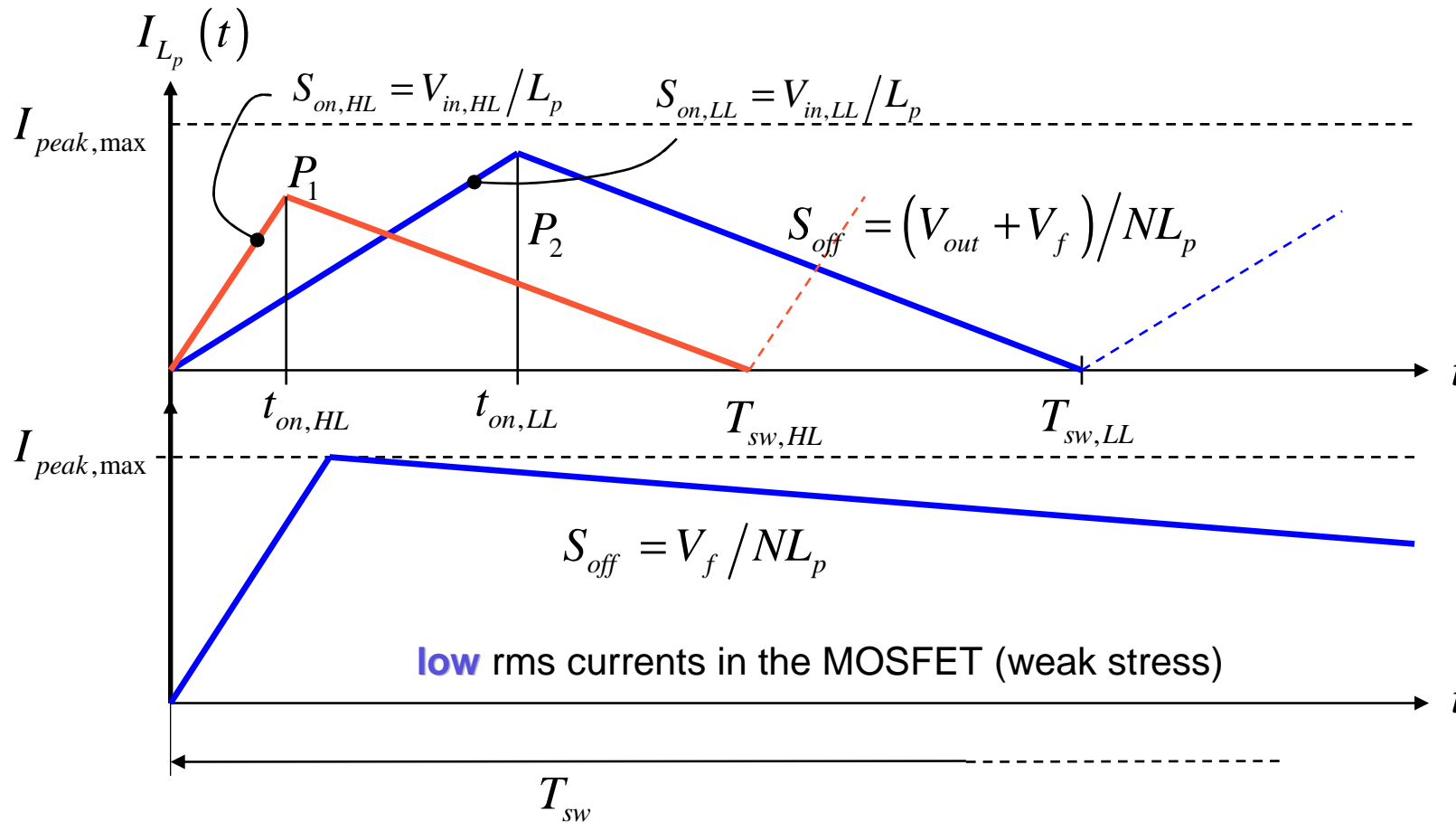
# The Frequency Linearly Changes



- As the peak current and the on-slope vary,  $T_{sw}$  changes



- Excellent behavior in short-circuit conditions!
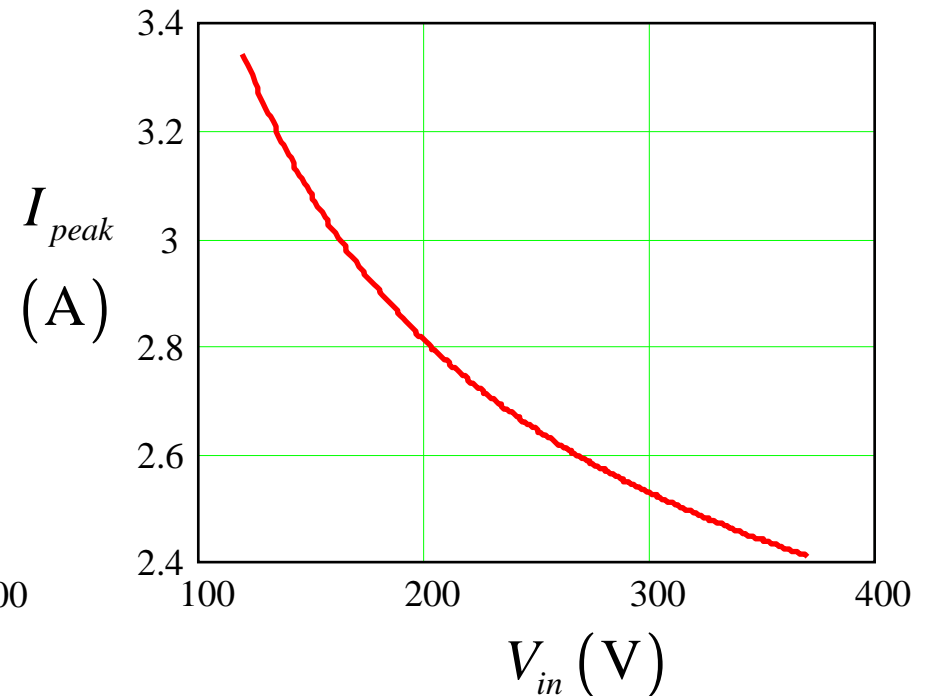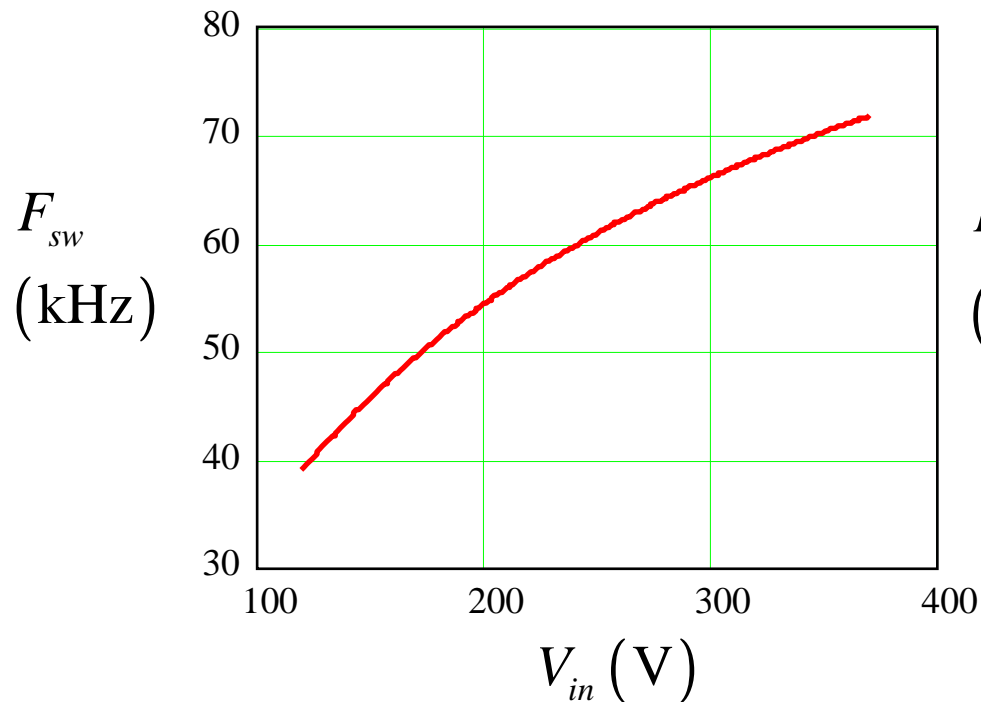
# The Excursion Can be Quite Large

- ❑ In heavy load low-line conditions,  $F_{sw}$  decreases
- ❑ In light-load and high-line operations,  $F_{sw}$  can go very high





- ❑ EMI and switching losses are at stake as  $F_{sw}$  goes up
- ❑ Standby power obviously suffers from this condition



# In a Bounded System Discrete Jumps


- ❑ As the load gets lighter, the frequency goes to the sky
- ❑ Modern controllers fold the frequency back with a VCO
- ❑ Problem, the only places to re-start are valleys: discrete jumps

Output  
current

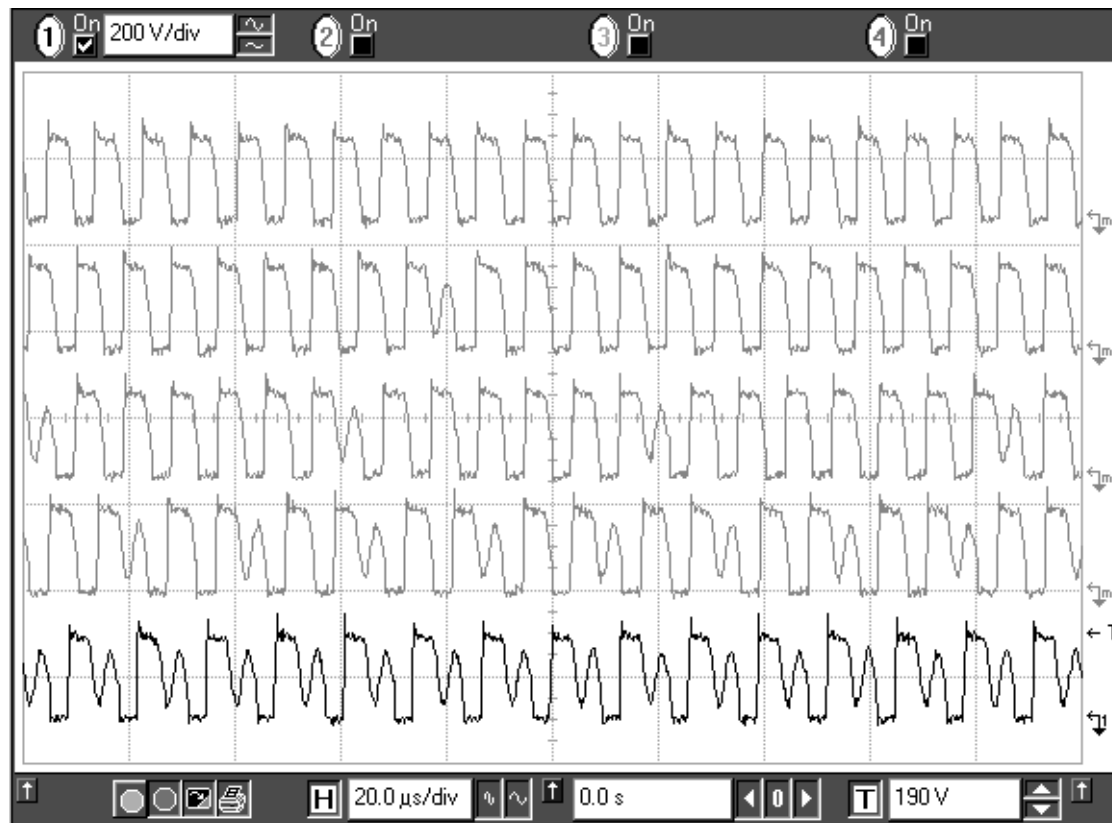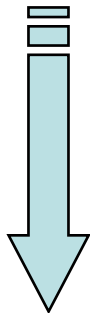
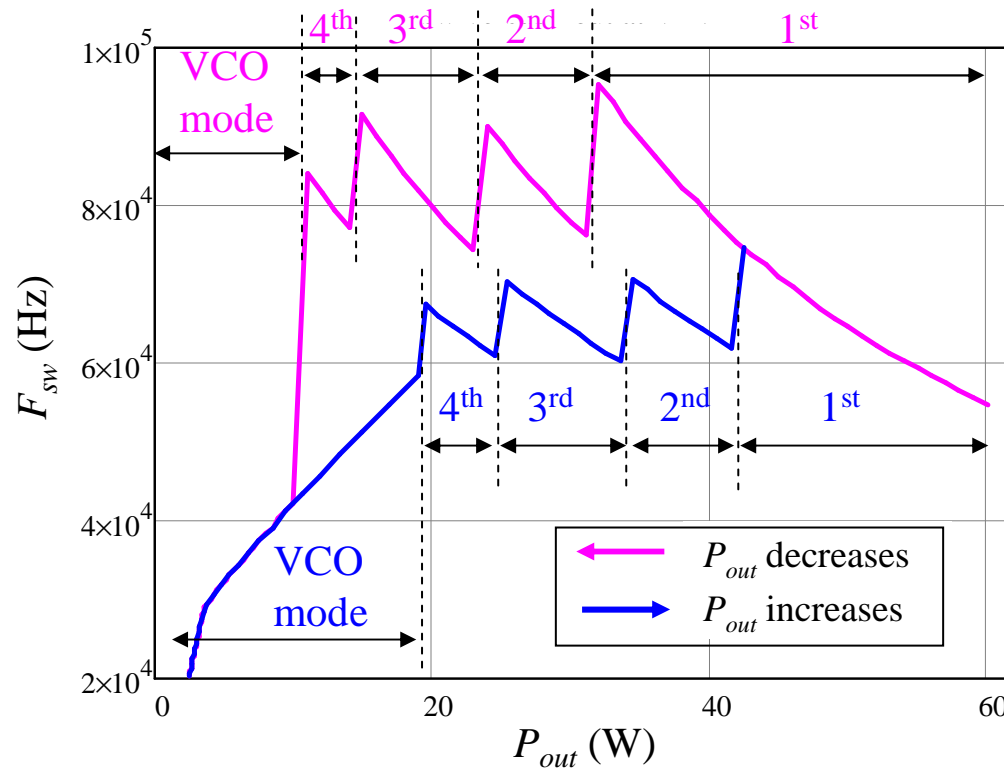
# New Controllers Lock in the Valleys

- ❑ To prevent the noise, the NCP1380 locks the valley
- ❑ The current is allowed to move within a certain limit
- ❑ When it exceeds this limit, the controller selects a new valley
- ❑ As the load gets lighter, a VCO takes over and reduce  $F_{sw}$



NCP1379/1380

---

# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?
- More Power than Needed**
- The Frequency Response
- Compensating With the TL431




# What is The Problem?

- ❑ A converter is designed to operate on wide mains – 85 to 265 V rms
- ❑ It can deliver a maximum power before protection trips
  - The maximum power delivered at high line is larger than that at low line



85 V rms to 265 V rms

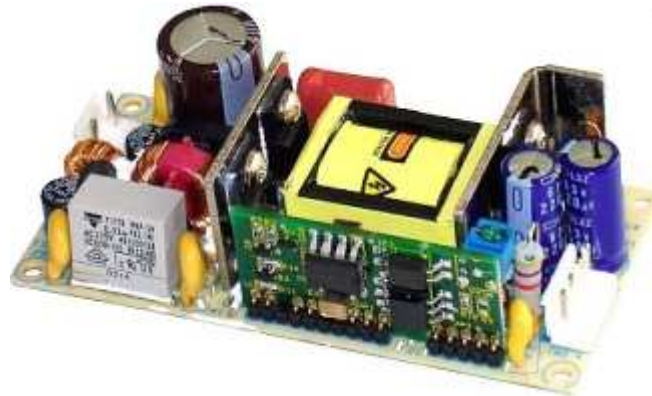

Increase load  
until protection  
trip.

# What Does the Standard Say?

- ❑ There is a test called Limited Power Source, LPS
- ❑ The maximum power the converter can deliver must be clamped
- ❑ If clamped, the manufacturer can use inferior fire proofing materials

Output Voltage $V_{out}$ (V)		Output Current $I_{out}$ (A)	Apparent Power $S$ (VA)
$V_{rms}$	$V_{dc}$		
$\leq 20$	$\leq 20$	$\leq 8$	$\leq 5 \cdot V_{out}$
$20 < V_{out} \leq 30$	$20 < V_{out} \leq 30$	$\leq 8$	$\leq 100$
-	$20 < V_{out} \leq 60$	$\leq 150/V_{out}$	$\leq 100$

19-V adapter,  $I_{out,max} = 5$  A




IEC950 safety standard


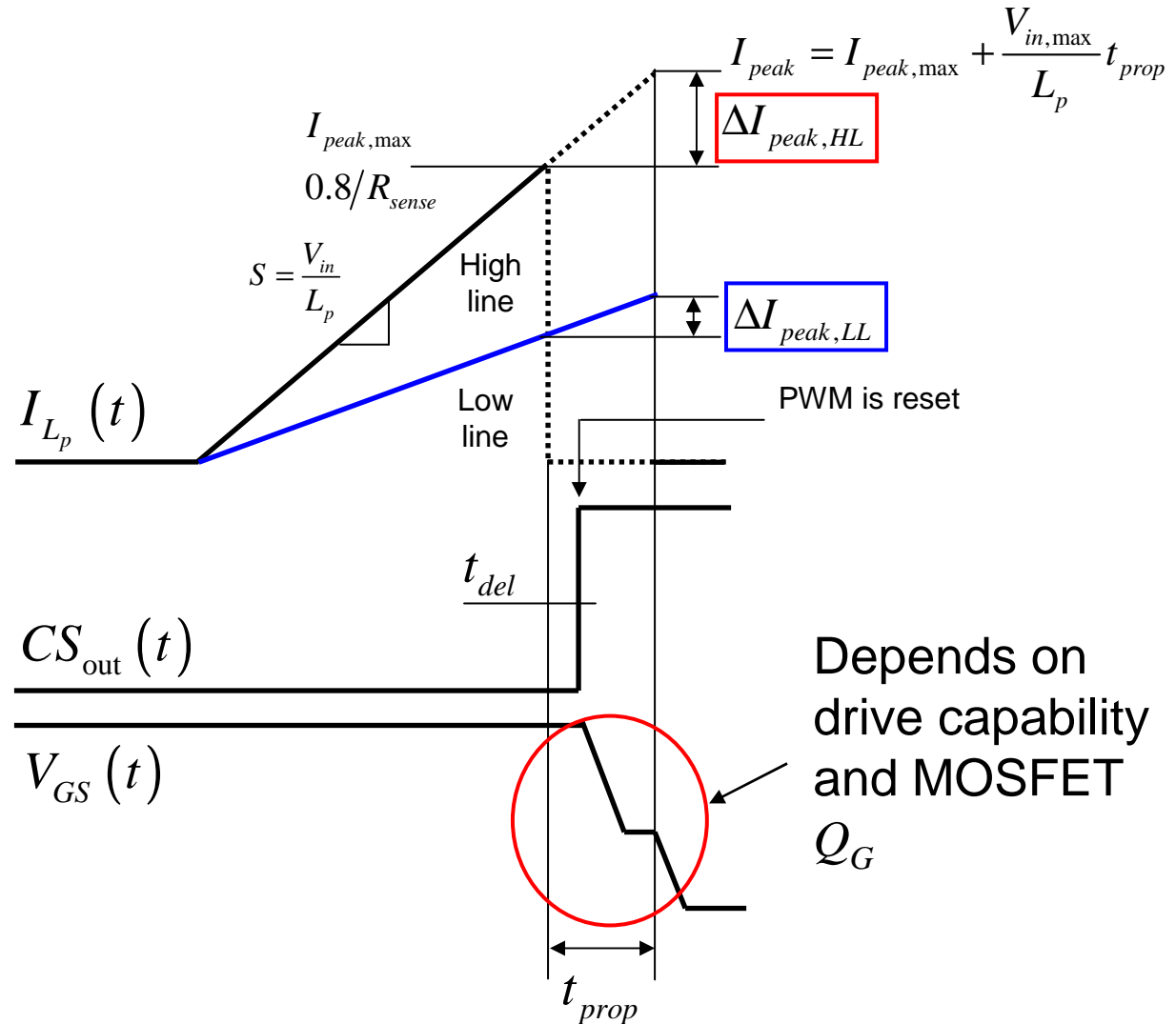
# Why the Power Runs Away in a Flyback?

- ❑ The inductor current slope increases at high line.
- ❑ The controller takes time to react to an overcurrent situation.
- ❑ The inductor current keeps growing until the MOSFET turns off.
- ❑ The overshoot is larger at higher slopes (High  $V_{in}$ )




# The Effect in a DCM Converter

□ A flyback converter operated in DCM obeys the formula:

$$P_{out} = \frac{1}{2} L_p I_{peak,max}^2 F_{sw} \eta$$

↑
↑
↑
↑

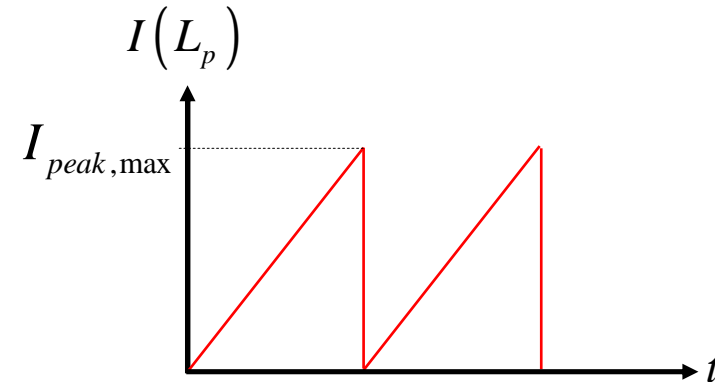Primary inductor    Max. peak current in fault    Switching frequency    Converter efficiency



□ As  $L_p$  and  $F_{sw}$  are fixed,  $I_{peak,max}$  changes with line input

$$I_{peak,max,LL} = \frac{V_{sense}}{R_{sense}} + \frac{V_{in,LL}}{L_p} t_{prop}$$

Low line

$$I_{peak,max,HL} = \frac{V_{sense}}{R_{sense}} + \frac{V_{in,HL}}{L_p} t_{prop}$$

High line

$$\frac{\Delta I_{peak}}{I_{peak,max,HL}} = \frac{V_{in,HL} - V_{in,LL}}{\frac{L_p V_{sense}}{t_{prop} R_{sense}} + V_{in,LL}}$$




$$(1.13)^2 = 1.28$$

A 13.5% overshoot translates in a 28% power increase  
( $\eta$  is considered constant over the range)


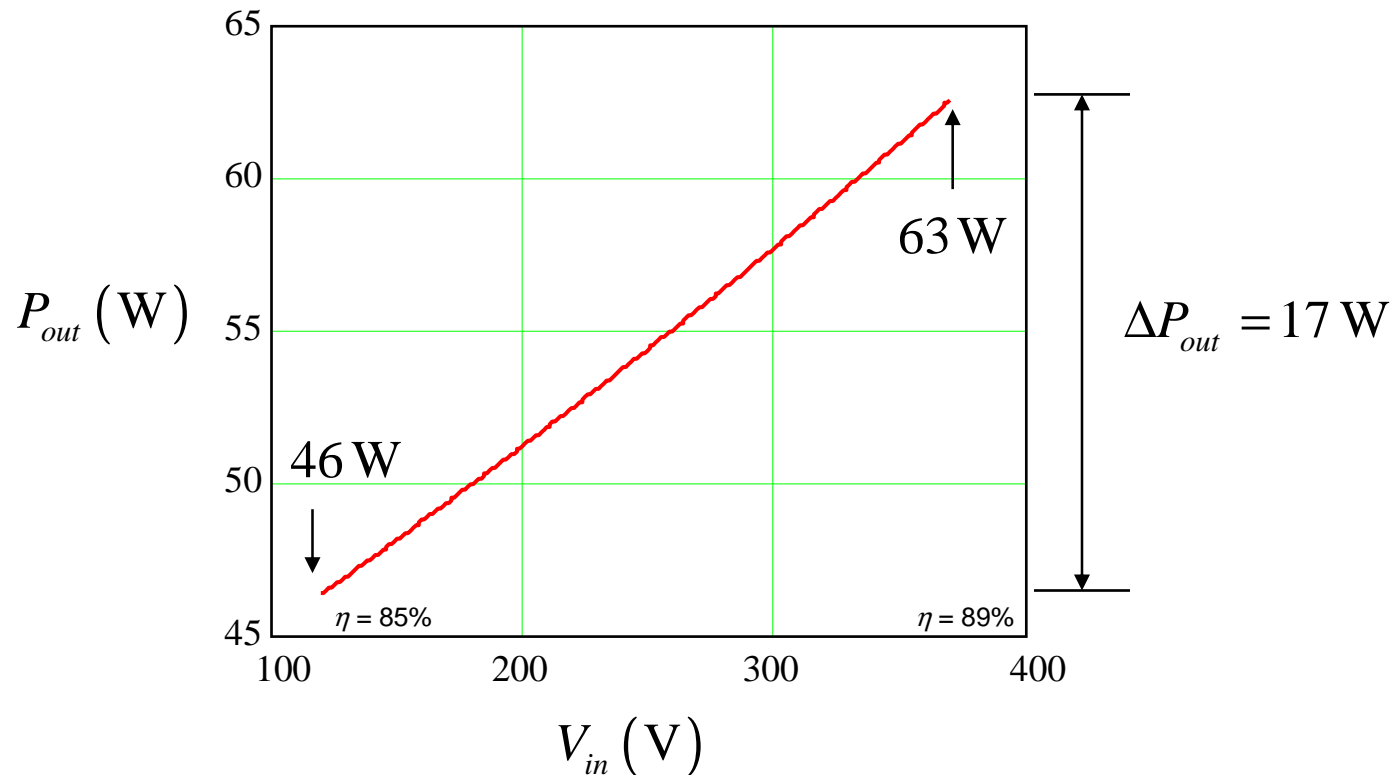
# The Power Increases at High Line

□  $L_p = 250 \mu\text{H}$ ,  $V_{sense} = 1 \text{ V}$ ,  $t_{prop} = 350 \text{ ns}$ ,  $V_{in,LL} = 120$ ,  $V_{in,HL} = 370 \text{ V}$ ,  $R_{sense} = 0.33 \Omega$ ,  $F_{sw} = 65 \text{ kHz}$



□ In this example, the converter stays DCM over the whole input range.




# How to Compensate the Runaway?

□ How do we compensate this excess of power?

➤ we reduce the maximum peak current at high line

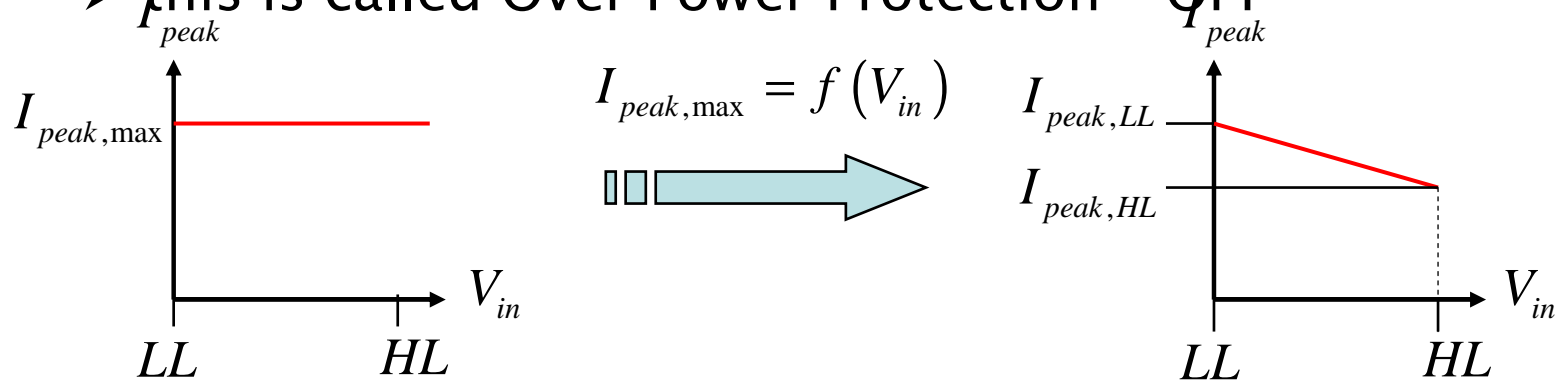➤ this is called Over Power Protection - OPP



□ How to calculate the compensated high-line current?

❖ Equate low-line power with high-line power and solve

for  $I_{peak}$

$$P_{out,max,HL} = \frac{1}{2} L_p I_{peak,max,HL}^2 F_{sw} \eta_{HL}$$

→ Solve for  $I_{peak}$



# Reducing the Peak Current

- The final inductor peak current must equal:

$$I_{peak,max,HL} = \sqrt{\frac{2P_{out,max,LL}}{L_p F_{sw} \eta_{HL}}}$$

- You must subtract the prop. delay to obtain the controller setpoint

$$\frac{V_{sense}}{R_{sense}} = I_{peak,max,HL} - \frac{V_{in,HL}}{L_p} t_{prop}$$


- The amplitude of the sensed voltage must reduce by:

$$\Delta V = V_{sense} - \left( I_{peak,max,HL} - \frac{V_{in,HL}}{L_p} t_{prop} \right) R_{sense}$$


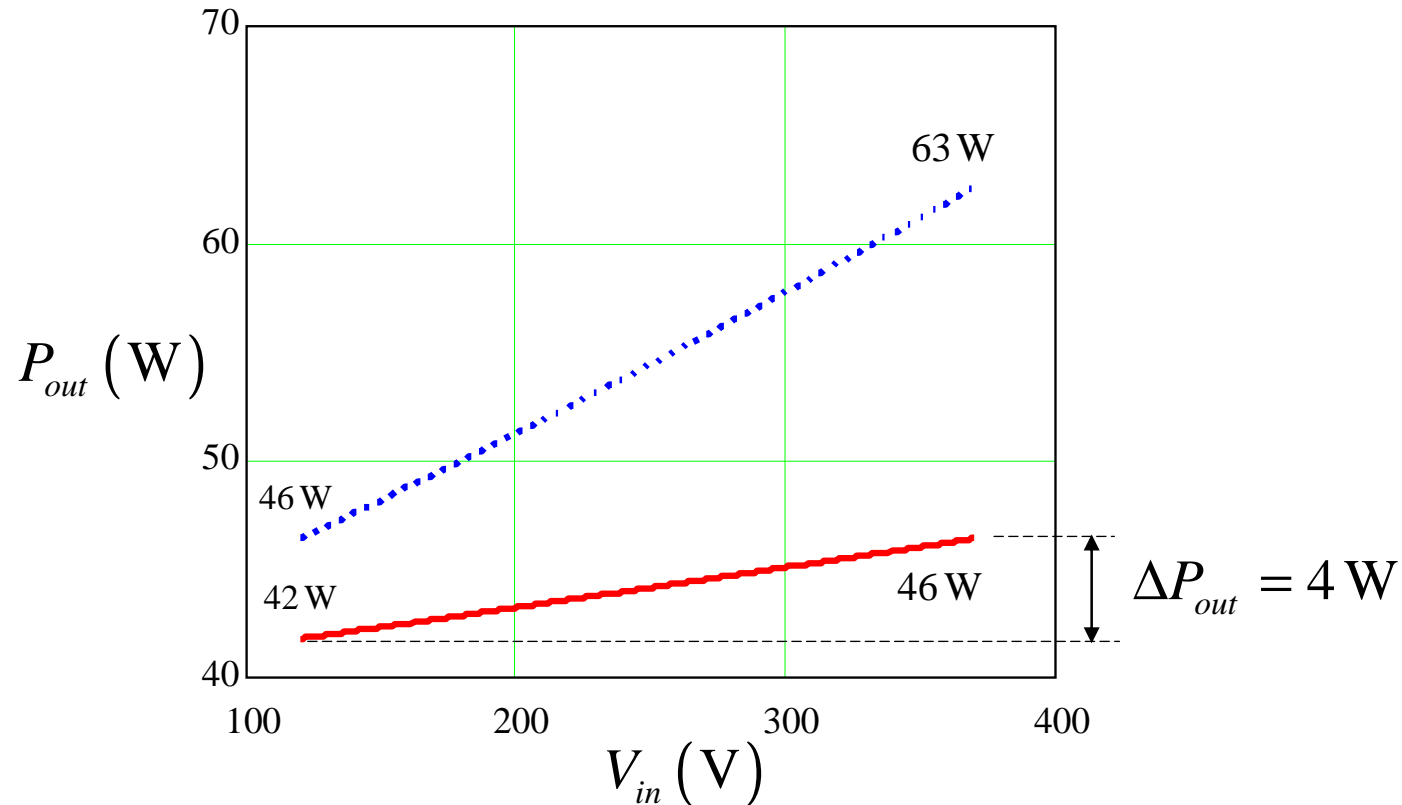
# For What Final Result?

- Thanks to the OPP, the power stays under control



# The CCM Case is a Different Picture


□ In DCM, the valley current is zero, the stored energy is:

$$E = \frac{1}{2} L_p I_{peak,max}^2$$

➤ The peak current runaway, alone, affects the transmitted power


□ In CCM, the valley current changes the formula:
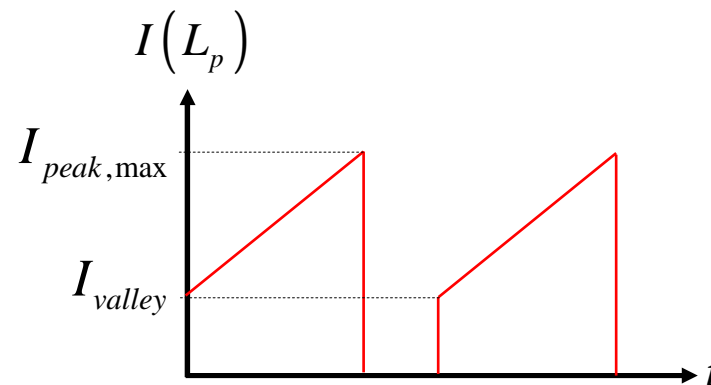
$$E = \frac{1}{2} L_p (I_{peak,max}^2 - I_{valley}^2)$$



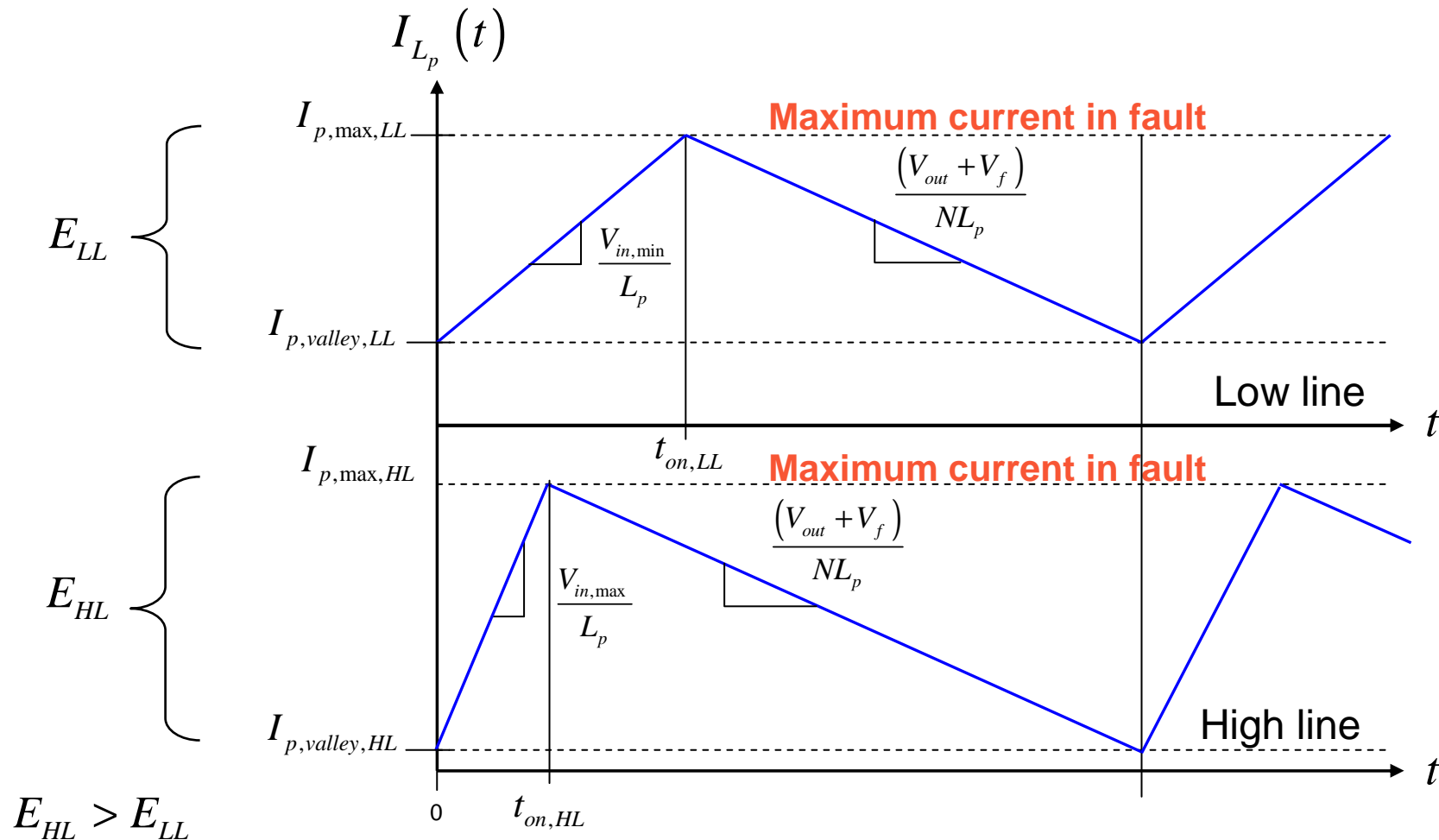
# The Converter Changes its Operating Mode

- ❑ In fault mode, the converter operates in deep CCM at low line
- ❑ As the input voltage increases, the valley current decreases


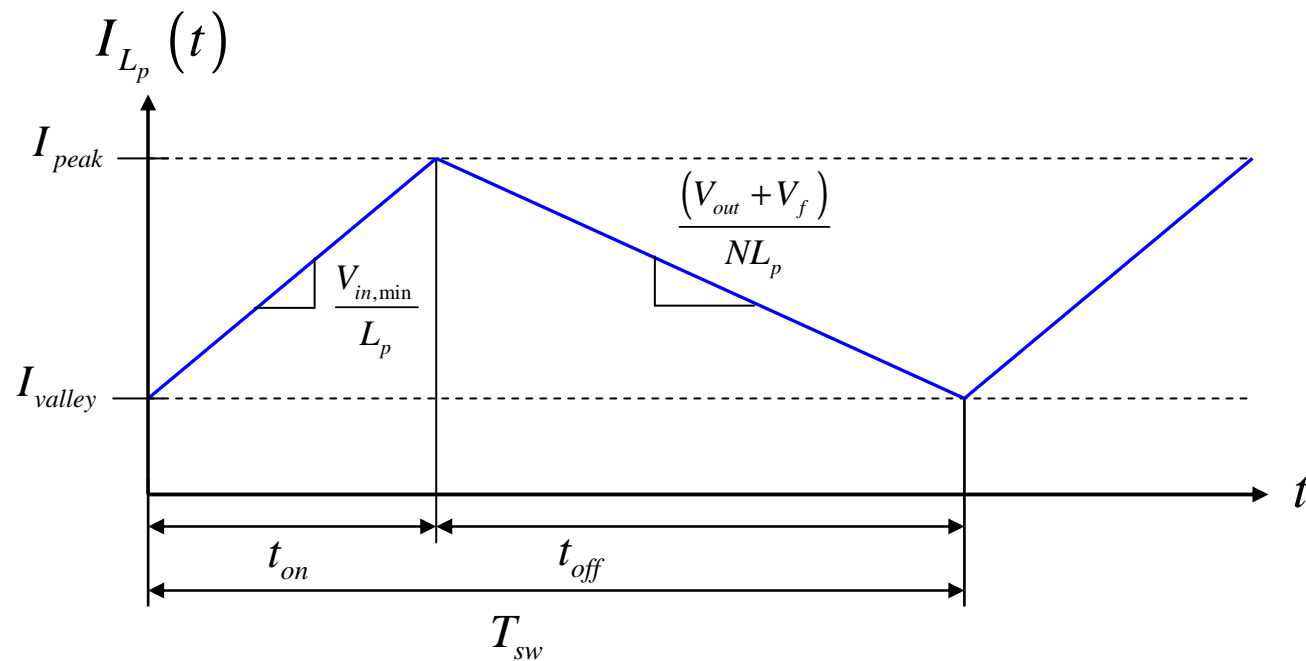
# Computing the Transmitted Power in CCM

- First, we write the  $t_{on}$  and  $t_{off}$  equations in CCM



$$I_{peak} = I_{valley} + \frac{V_{in}}{L_p} t_{on} \quad (1)$$

$$I_{valley} = I_{peak} - \frac{(V_{out} + V_f)}{NL_p} t_{off} \quad (2)$$

$$T_{sw} = t_{on} + t_{off} \quad (3)$$



# Solving for the Valley Current

- By combining the 3 equations, we have:

$$t_{on} = \frac{L_p (I_{peak} - I_{valley})}{V_{in}} \quad t_{off} = T_{sw} - t_{on} = T_{sw} - \frac{L_p (I_{peak} - I_{valley})}{V_{in}}$$

- Replace  $t_{off}$  in

(2):

$$I_{valley} = I_{peak} - \frac{(V_f + V_{out})(I_{valley} L_p - I_{peak} L_p + T_{sw} V_{in})}{L_p N V_{in}}$$

- Solve for  $I_{valley}$ :

$$I_{valley} = \boxed{I_{peak}} - \frac{T_{sw} V_{in} (V_f + V_{out})}{L_p (V_f + V_{out} + N V_{in})} \xrightarrow{\Delta I_L = I_{peak} - I_{valley}} \Delta I_L = \frac{T_{sw} V_{in} (V_f + V_{out})}{L_p (V_f + V_{out} + N V_{in})}$$

Inductor ripple current

$$\xrightarrow{\text{LL or HL}} I_{peak, \max} = \frac{V_{sense}}{R_{sense}} + \frac{V_{in}}{L_p} t_{prop}$$

Max fault current



# Identifying the Operating Mode

□ Having the ripple on hand, we can confirm the mode:

$$t_{on} = \frac{\Delta I_L}{V_{in}} L_p \quad t_{off} = \frac{N \Delta I_L}{(V_{out} + V_f)} L_p$$

$$t_{on} + t_{off} = T_{sw} \quad \longrightarrow \quad \text{CCM} \quad \longrightarrow$$


$$I_{valley} > 0$$

$$t_{on} + t_{off} = T_{sw} \quad \longrightarrow \quad \text{BCM} \quad \longrightarrow$$

$$I_{valley} = 0$$

$$t_{on} + t_{off} < T_{sw} \quad \longrightarrow \quad \text{DCM} \quad \longrightarrow$$

$$DT = T_{sw} - t_{off} - t_{on}$$

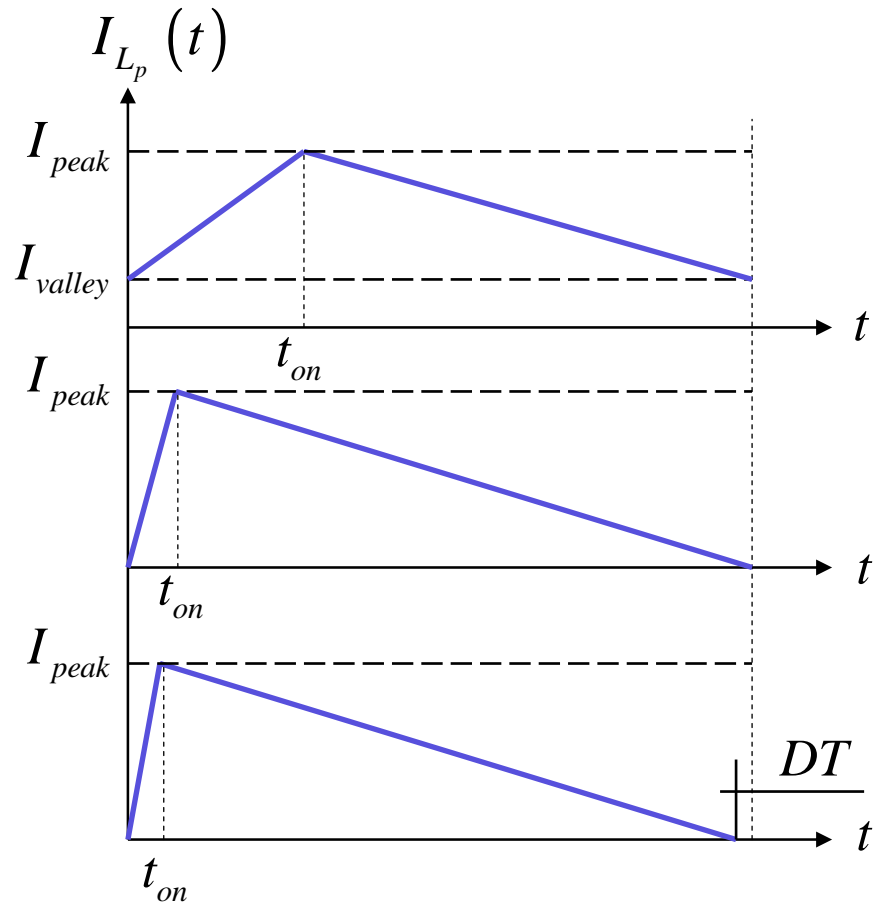




# Evaluating the Power in CCM

□  $L_p = 600 \mu\text{H}$ ,  $V_{sense} = 1 \text{ V}$ ,  $t_{prop} = 350 \text{ ns}$ ,  $V_{in,LL} = 120$ ,  $V_{in,HL} = 370 \text{ V}$ ,  $R_{sense} = 0.33 \Omega$ ,  $F_{sw} = 65 \text{ kHz}$


$$P_{\max,LL} = \frac{1}{2} L_p \left( I_{\text{peak,max,LL}}^2 - I_{\text{valley,LL}}^2 \right) F_{sw} \eta_{LL} \approx 76 \text{ W}$$
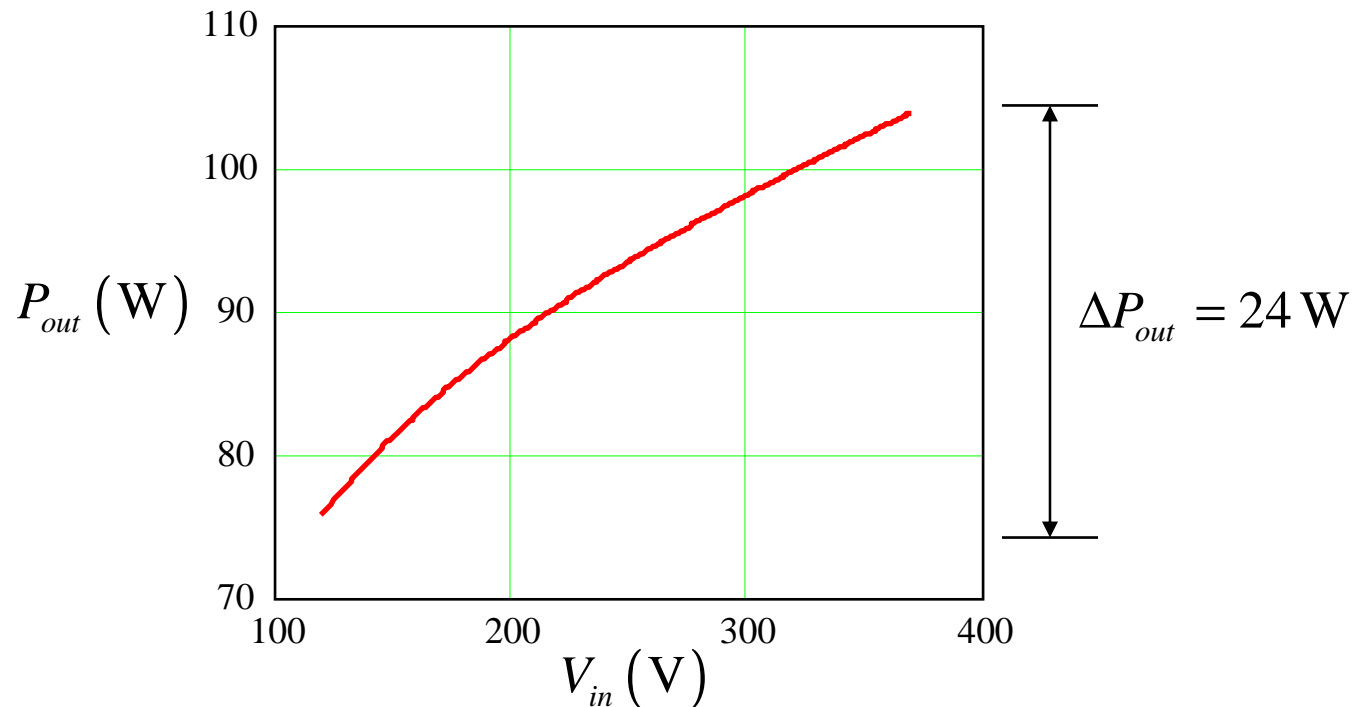
$$P_{\max,HL} = \frac{1}{2} L_p \left( I_{\text{peak,max,HL}}^2 - I_{\text{valley,HL}}^2 \right) F_{sw} \eta_{HL} = 104 \text{ W}$$


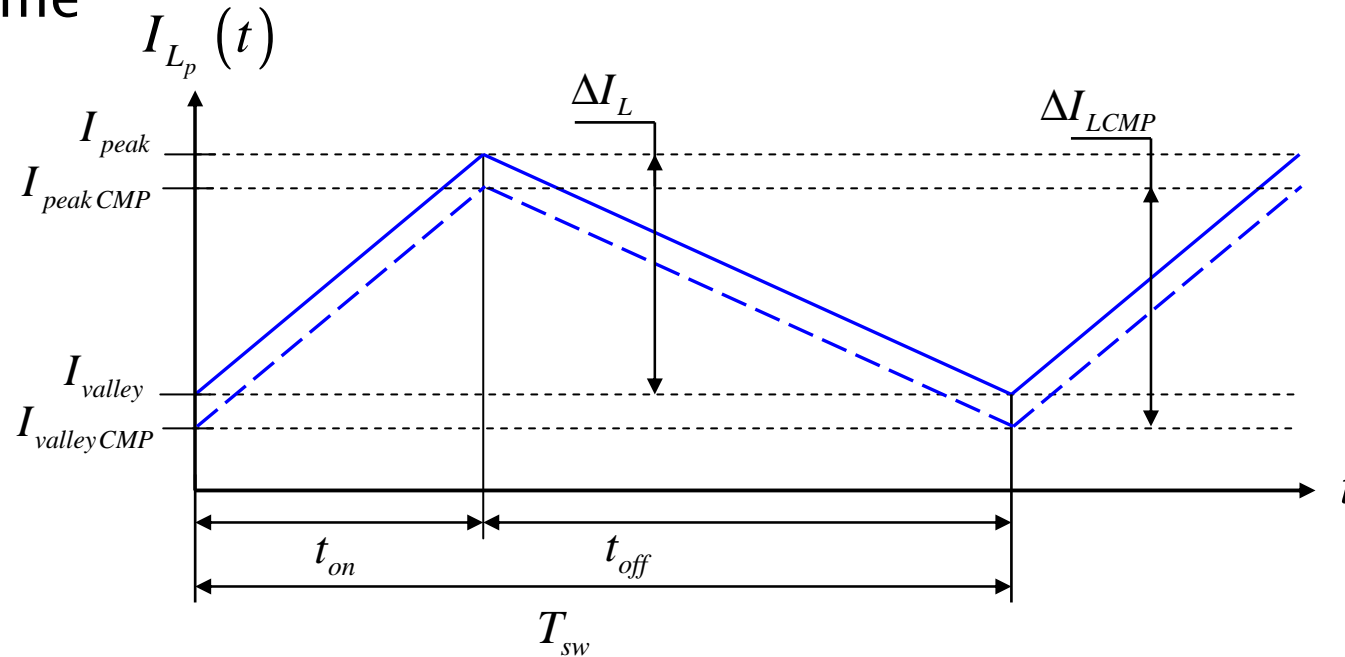
# Reducing the Peak Current at High Line

- If we lower the peak at high line, the ripple remains the same



- We can re-write the flyback power formula to include the ripple

$$P_{max,HL} = \frac{1}{2} L_p \left( I_{peak,max,HL}^2 - \underbrace{\left( I_{peak,max,HL} - \Delta I_{L,HL} \right)^2}_{0 \text{ in DCM}} \right) F_{sw} \eta_{HL}$$

# We Want to Limit the High-Line Power

- We can force the high-line power to match that of low line

$$P_{\max,LL} = \frac{1}{2} L_p \left( I_{\text{peak,max,HL}}^2 - \left( I_{\text{peak,max,HL}} - \Delta I_{L,HL} \right)^2 \right) F_{sw} \eta_{HL}$$

- From there, we can extract the compensated peak current value

$$I_{\text{peak,max,HL}} = \frac{F_{sw} L_p \eta_{HL} \Delta I_{L,HL}^2 + 2P_{\max,LL}}{2F_{sw} L_p \eta_{HL} \Delta I_{L,HL}}$$

- As this is the new setpoint, prop. delay contribution must be removed

$$\Delta V = V_{\text{sense}} - \left( I_{\text{peak,max,HL}} - \frac{V_{\text{in,HL}}}{L_p} t_{\text{prop}} \right) R_{\text{sense}}$$


- After compensation, the peak current setpoint at high line becomes

$$I_{\text{peak,max,HL}} = \frac{V_{\text{sense}} - \Delta V}{R_{\text{sense}}} + \frac{V_{\text{in,HL}}}{L_p} t_{\text{prop}}$$



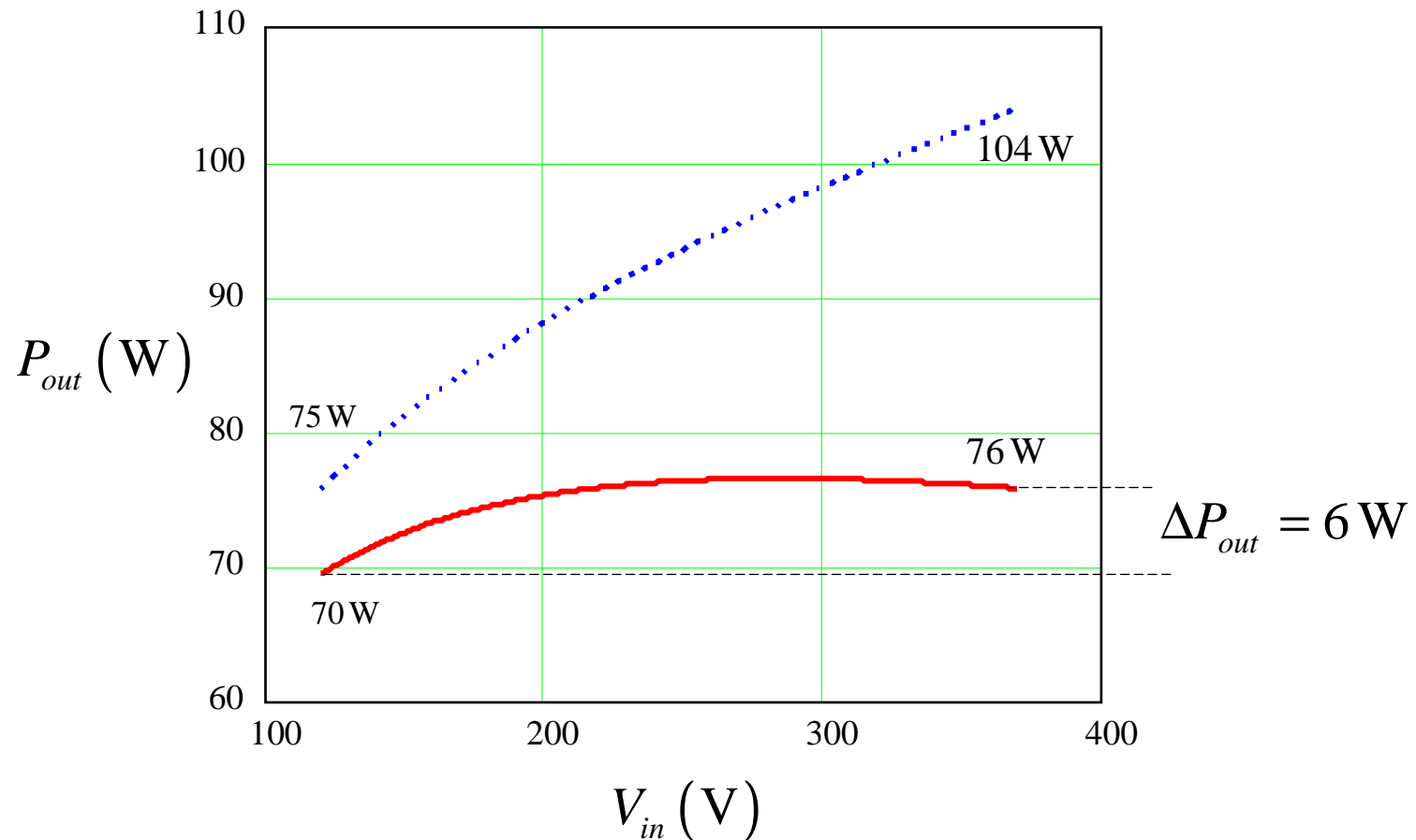
# What is the Final Result?

- The high line power now respects the LPS limit



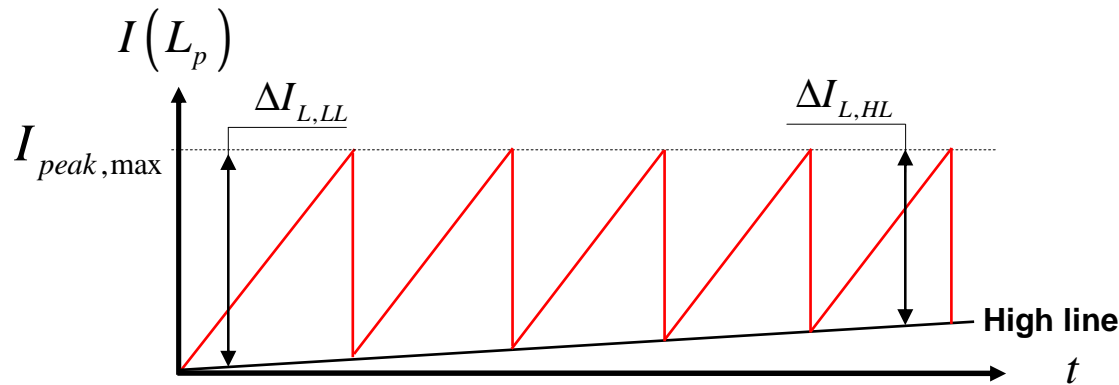
# What Practical Solutions?

- There are several possibilities to reduce the peak current
- 1. Offset the current sense signal in the CS pin:



- easy to do
- affects the no-load stand-by power
- affects light-load efficiency


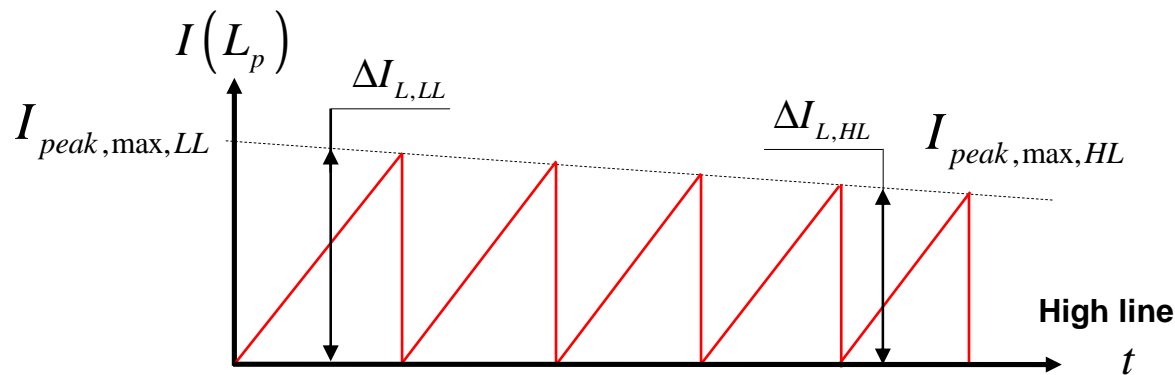
- 2. Reduce the peak limit as  $V_{in}$  increases



- implemented at IC level
- does not affect the no-load stand-by power
- does not affect light-load efficiency
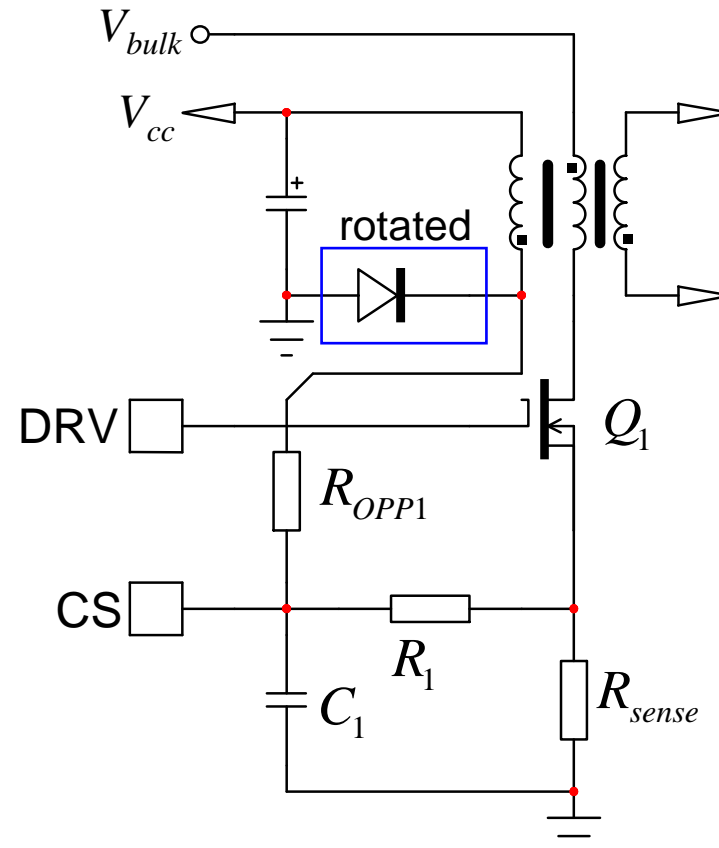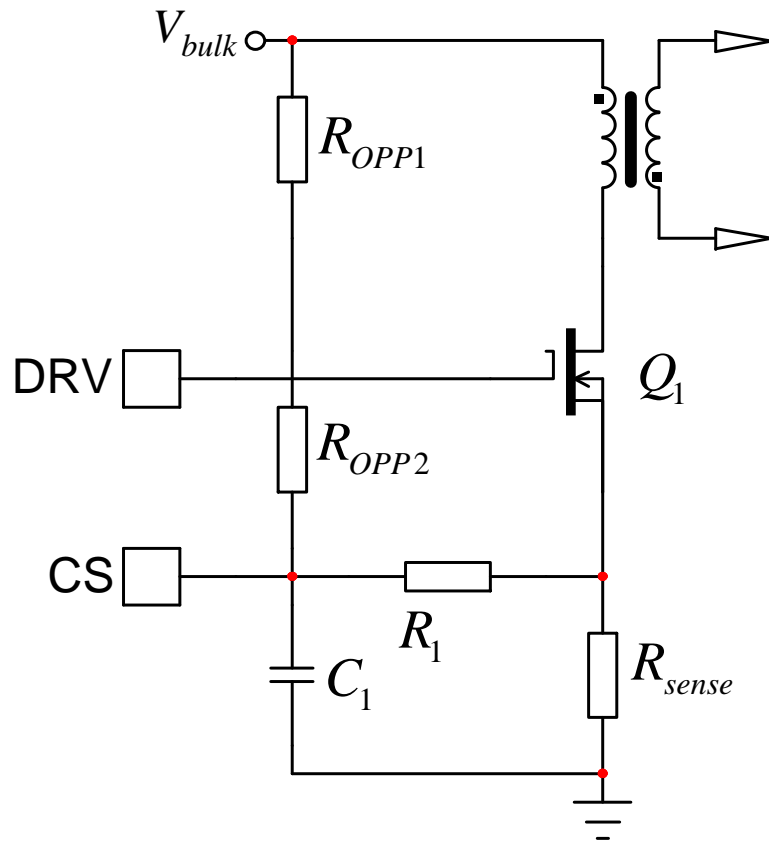
# Build an Offset on the CS Pin


- This offset must be proportional to the input voltage



- Both options degrade light-load operation because of the CS offset
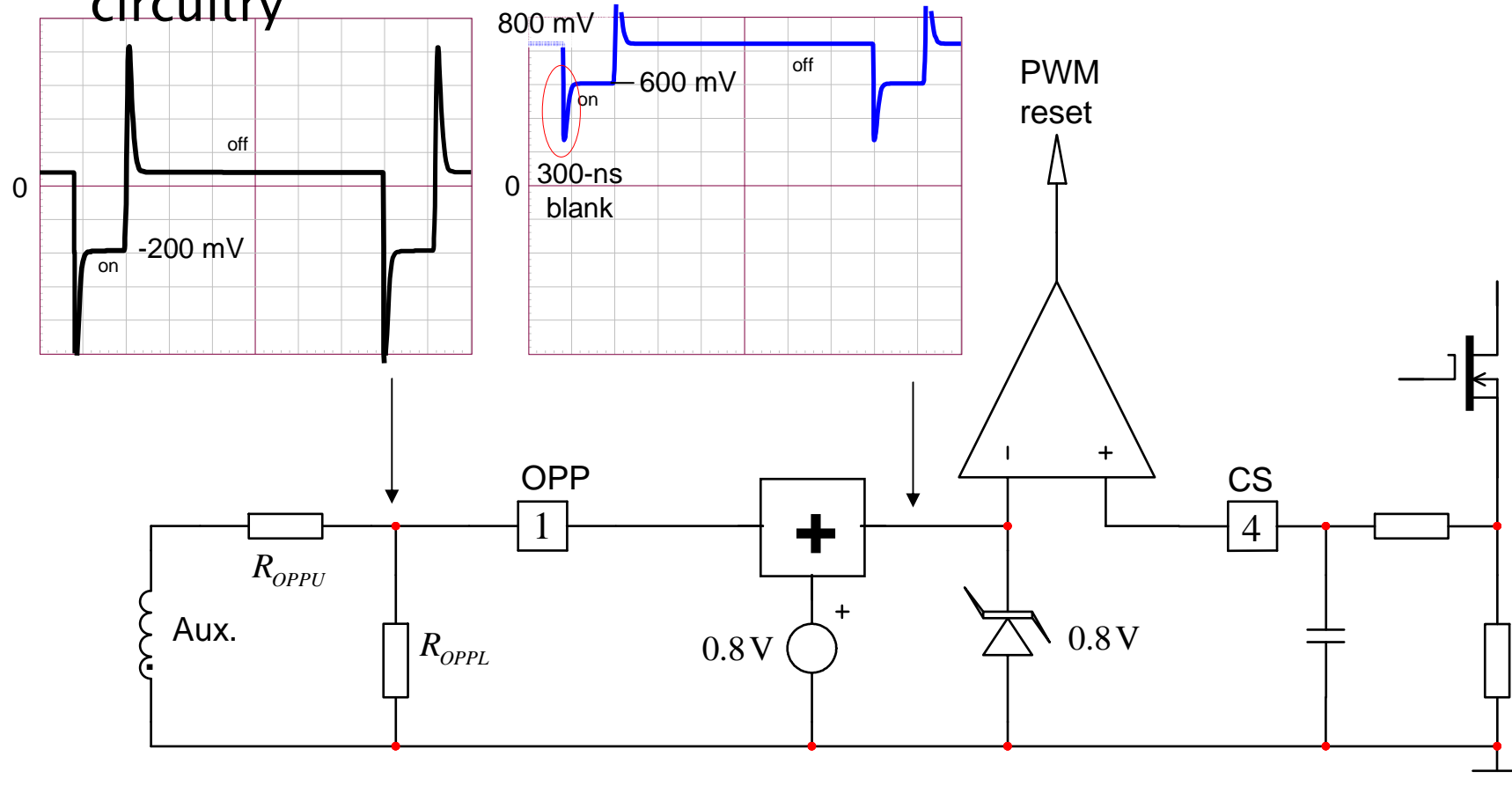
# OPP Implementation in the NCP1250

- The NCP1250 implement a non-dissipative OPP circuitry




- The auxiliary swings to  $-NV_{in}$  and reduces the setpoint  $\rightarrow$  OPP
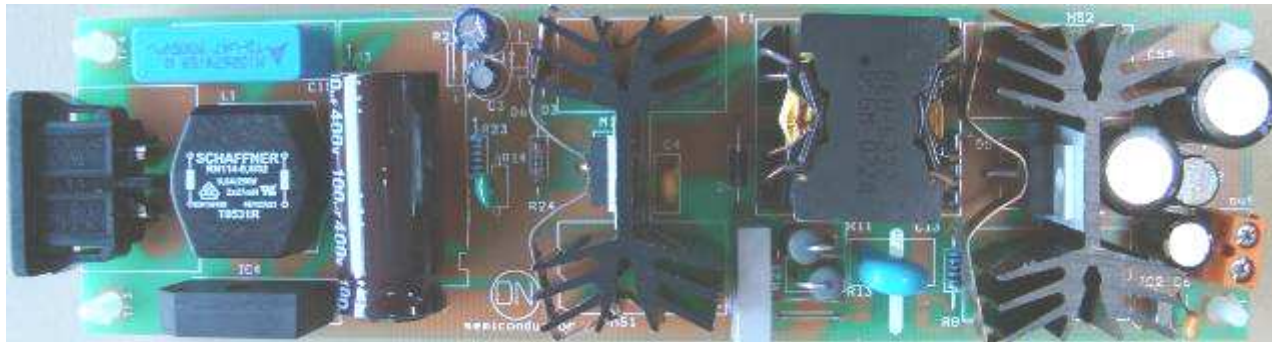
# Checking the Results

- Let us check on a real 19-V adapter built with the NCP1250

$$L_p = 600 \mu\text{H}, V_{sense} = 1 \text{ V}, t_{prop} = 350 \text{ ns}, V_{in,LL} = 120, V_{in,HL} = 370 \text{ V}$$
$$R_{sense} = 0.33 \Omega, F_{sw} = 65 \text{ kHz}, V_{clamp} = 90 \text{ V}, l_l = 2.2 \mu\text{H}, N = 0.25$$



- Without any OPP compensation, we have:

$$I_{out,max,LL} = 4.1 \text{ A} \quad I_{out,max,HL} = 5.7 \text{ A}$$

- Once OPP has been implemented:

$$P_{out,LL} \approx 72 \text{ W so } I_{out,LL} = 3.8 \text{ A} \quad P_{out,HL} \approx 78 \text{ W so } I_{out,HL} = 4.1 \text{ A}$$





---


# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?
- More Power than Needed
- The Frequency Response**
- Compensating With the TL431


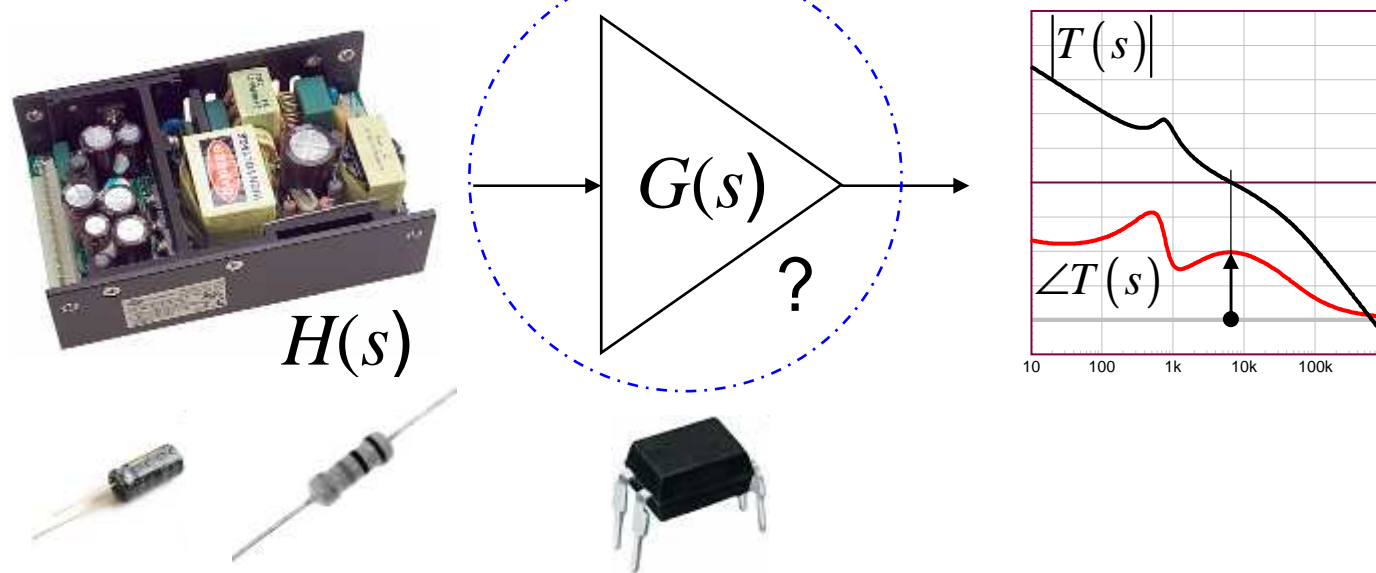
# Small-Signal Analysis

- ❑ Loop instability is a common issue in production
- ❑ Due to time pressure, designers often use trial and error
  - no indication on design margins
  - offenders are ignored, robustness is at stake



❖ Understand and counteract their variations when building  $G(s)$

# There are Two Options

- ❑ Analytical analysis of the power stage:
  - ✓ best to see where the offenders are hidden (ESR, opto pole etc.)
  - ✓ equations are complex but literature abounds
  - ❖ transfer function are for DCM or CCM
  - ❖ difficult to predict transient response
  
- ❑ SPICE models:
  - ✓ easy-to-implement averaged models
  - ✓ can work in ac or transient mode
  - ✓ easily transition between CCM and DCM
  - ❖ do not explicitly disclose the position of poles and zeros




**A measurement on the bench is mandatory, whatever you choose!**


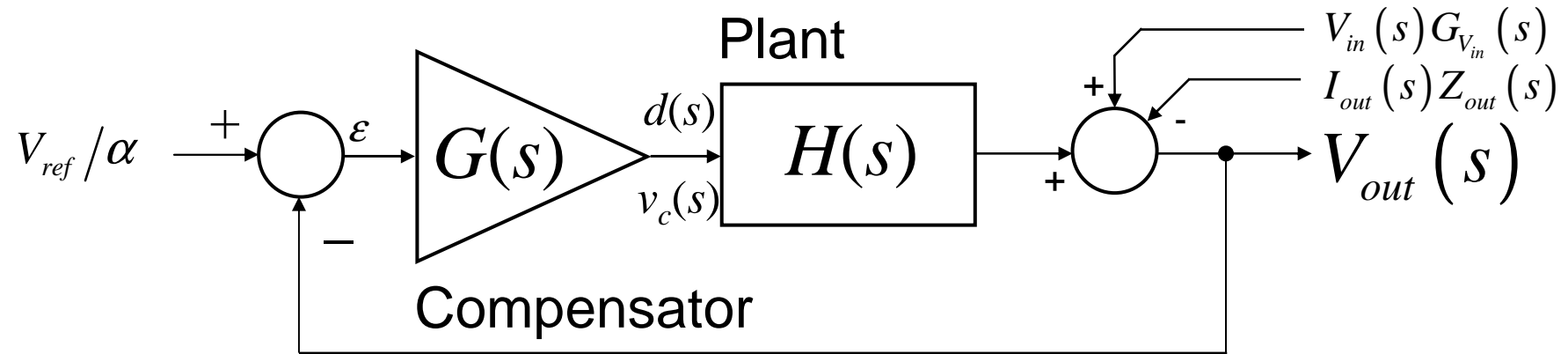
# Analytical Analysis

- ❑ You must first characterize the "plant" transfer function
  - what are your power stage ac characteristics?



$$H(s) = \frac{V_{out}(s)}{v_c(s)}$$

Current-mode  
control


$$H(s) = \frac{V_{out}(s)}{d(s)}$$

Voltage-mode  
control




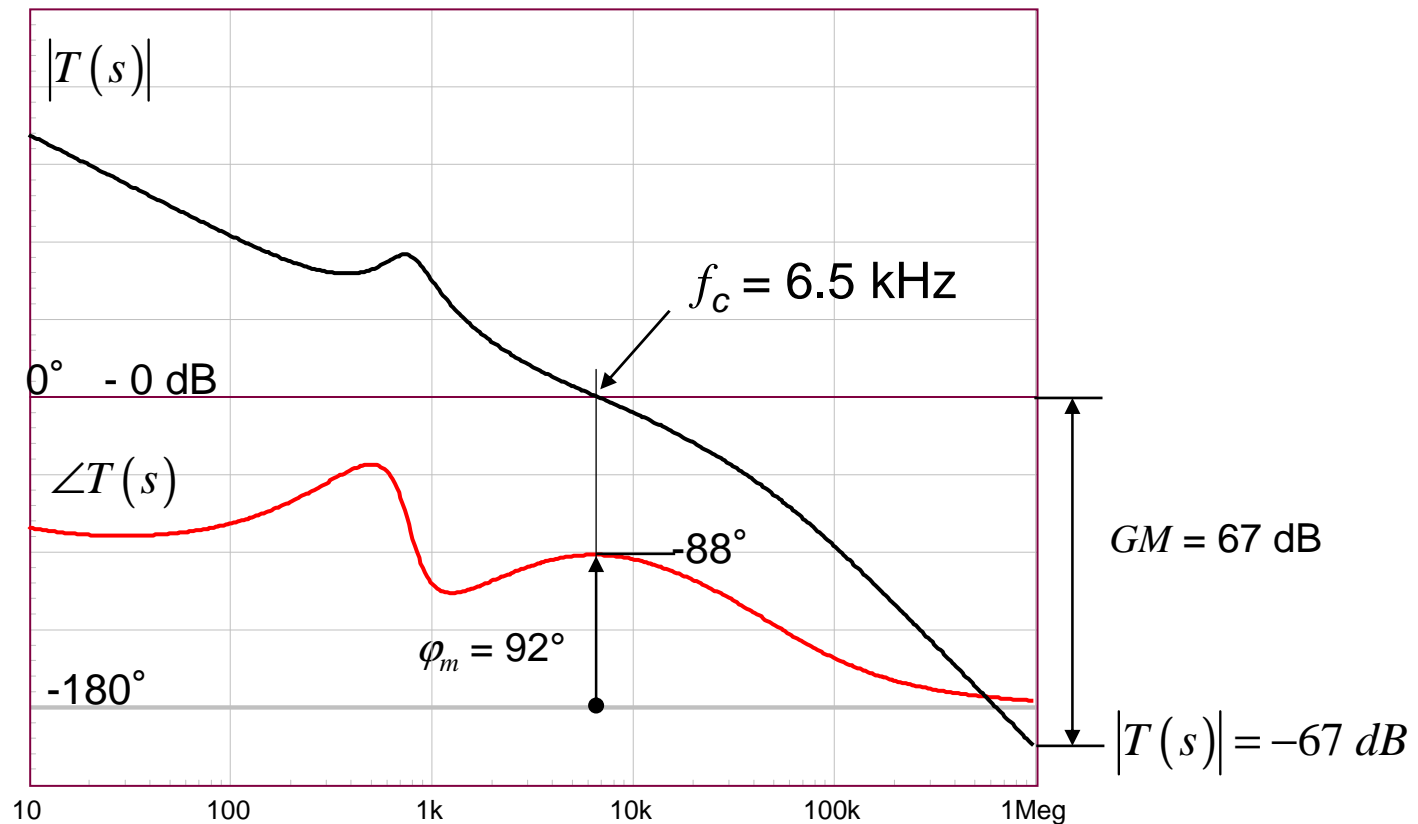
# How do we Stabilize a Converter?

- ❑ We need a high gain at dc for a low static error
- ❑ We want a sufficiently high crossover frequency for response speed
- Shape the compensator  $G(s)$  to build phase and gain margins!


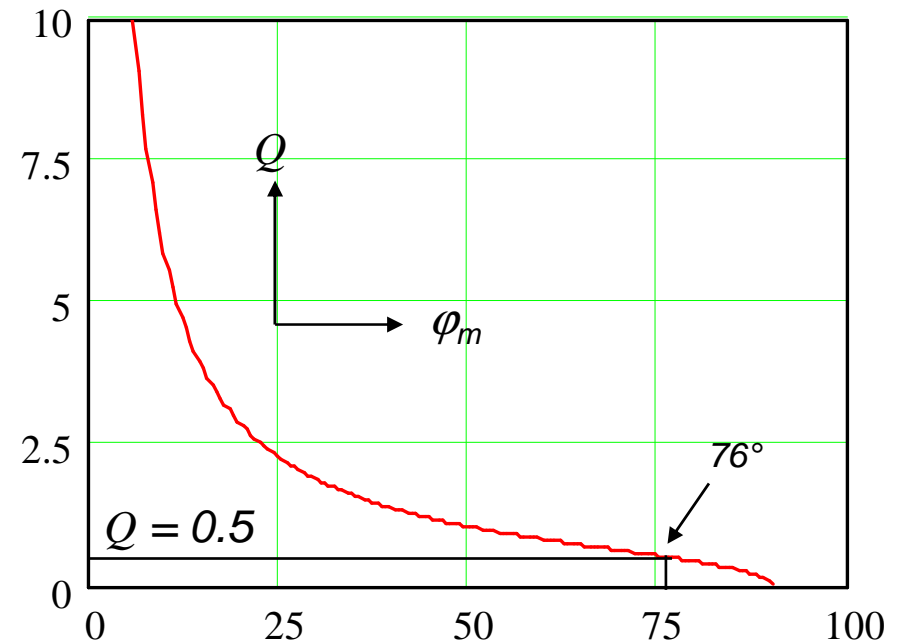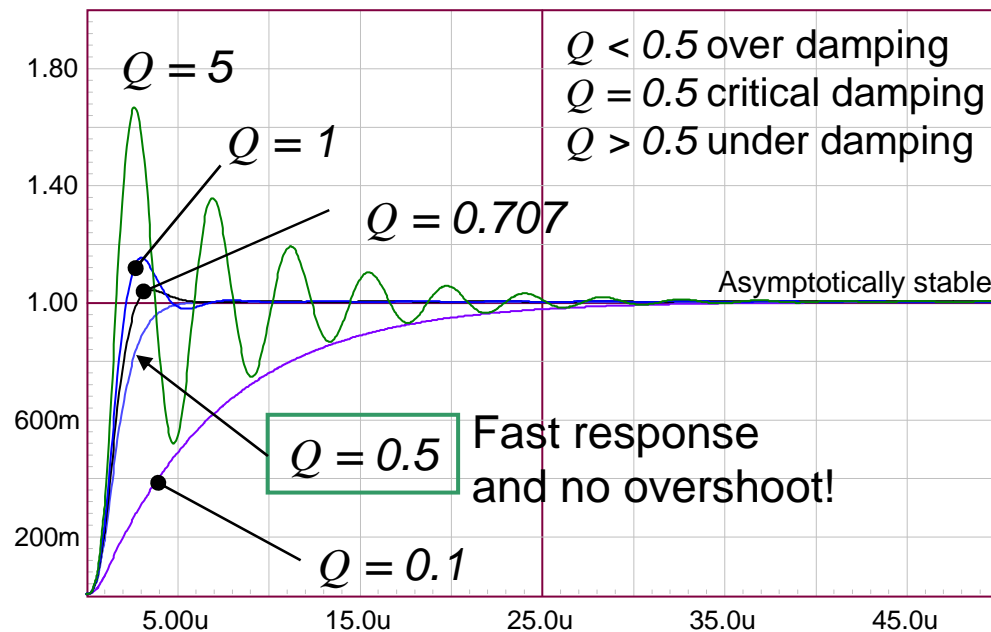
# How much phase margin to chose?


- ❑ a  $Q$  factor of 0.5 (critical response) implies a  $\phi_m$  of  $76^\circ$
- ❑ a  $45^\circ$   $\phi_m$  corresponds to a  $Q$  of 1.2: oscillatory response!



- ❑ phase margin depends on the needed response: fast, no overshoot...
- ❑ good practice is to shoot for  $60^\circ$  and make sure  $\phi_m$  always  $> 45^\circ$


# What Compensator Types do we Need?

- There are basically 3 compensator types:
  - type 1, 1 pole at the origin, no phase boost
  - type 2, 1 pole at the origin, 1 zero, 1 pole. Phase boost up to  $90^\circ$
  - type 3, 1 pole at the origin, 1 zero pair, 1 pole pair. Boost up to  $180^\circ$

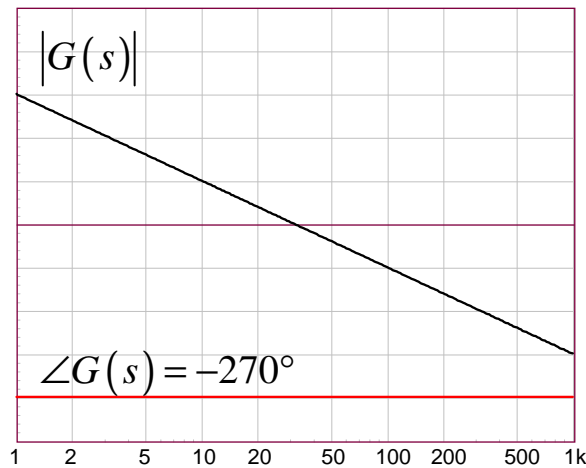


Type 1

Boost = 0

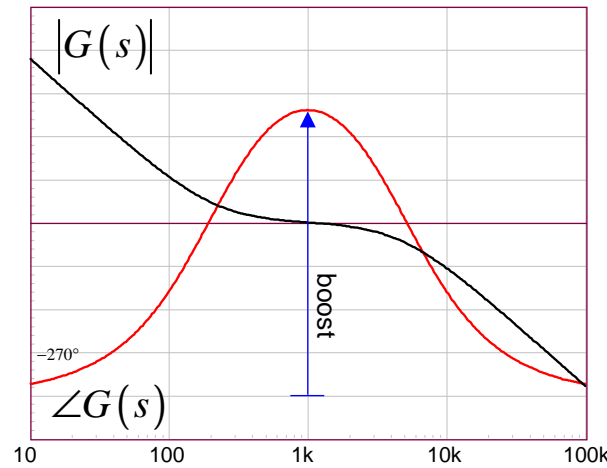

Type 2

Boost up to  $90^\circ$

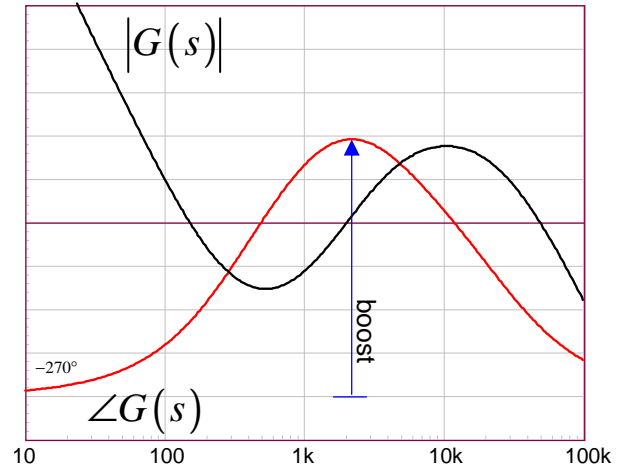

Type 3

Boost up to  $180^\circ$

# Fixed-Frequency Current-Mode

- First, check the operating mode, CCM or DCM?

$$L_{p,crit} = \frac{R_{load}}{2F_{sw}N^2} \left( \frac{V_{in}}{V_{in} + \frac{V_{out}}{N}} \right)^2 \quad L_p > L_{p,crit} ? \text{ Yes, CCM else DCM}$$

- Assume CCM, compute the duty-ratio:

$$D = \frac{V_{out}}{V_{out} + NV_{in}}$$

- Compute  $M$  and  $\tau_L$   $M = \frac{V_{out}}{NV_{in}} \quad \tau_L = \frac{2L_p N^2}{R_{load} T_{sw}}$

- Evaluate the dc gain and poles/zeros positions:

$$G_0 = \frac{R_{load}}{R_{sense} G_{FB} N} \frac{1}{\frac{(1-D)^2}{\tau_L} + 2M + 1}$$





# Fixed-Frequency Current-Mode

- Compute the poles/zeros positions:

$$f_{z_1} = \frac{1}{2\pi R_{ESR} C_{out}} \quad f_{z_2} = \frac{(1-D)^2 R_{load}}{2\pi D L_p N^2} \quad f_{p_1} = \frac{(1-D)^3}{2\pi R_{load} C_{out}} + 1 + D$$

- Check the quality coefficient at  $F_{sw}/2$

$$S_n = \frac{V_{in}}{L_p} R_{sense} \quad S_e = (M_c - 1) S_n \quad Q_p = \frac{1}{\pi (M_c (1-D) - 0.5)}$$

↓  
1 = no compensation

- Apply to formula to plot the ac response:

$$H(s) \approx G_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \left(1 - \frac{s}{\omega_{z2}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_n Q_p} + \frac{s^2}{\omega_n^2}\right)}$$

3<sup>rd</sup> order →

$$M_c = 1 + \frac{S_e}{S_n} \quad \omega_n = \frac{\pi}{T_{sw}}$$



# Fixed-Frequency Current-Mode

- Extract the magnitude and the argument definitions

$$|H(f)| = 20 \log_{10} \left[ G_0 \frac{\sqrt{1 + \left(\frac{f}{f_{z1}}\right)^2} \sqrt{1 + \left(\frac{f}{f_{z2}}\right)^2}}{\sqrt{1 + \left(\frac{f}{f_{p1}}\right)^2} \sqrt{\left(1 - \left(\frac{f}{f_n}\right)^2\right)^2 + \left(\frac{f}{f_n Q_p}\right)^2}} \right]$$

$$\arg H(f) = \tan^{-1}\left(\frac{f}{f_{z1}}\right) - \tan^{-1}\left(\frac{f}{f_{z2}}\right) - \tan^{-1}\left(\frac{f}{f_{p1}}\right) - \tan^{-1}\left(\frac{f}{f_n Q_p} \frac{1}{1 - \left(\frac{f}{f_n}\right)^2}\right)$$


$\uparrow$   
 RHPZ

- Plot them with Mathcad® for instance.


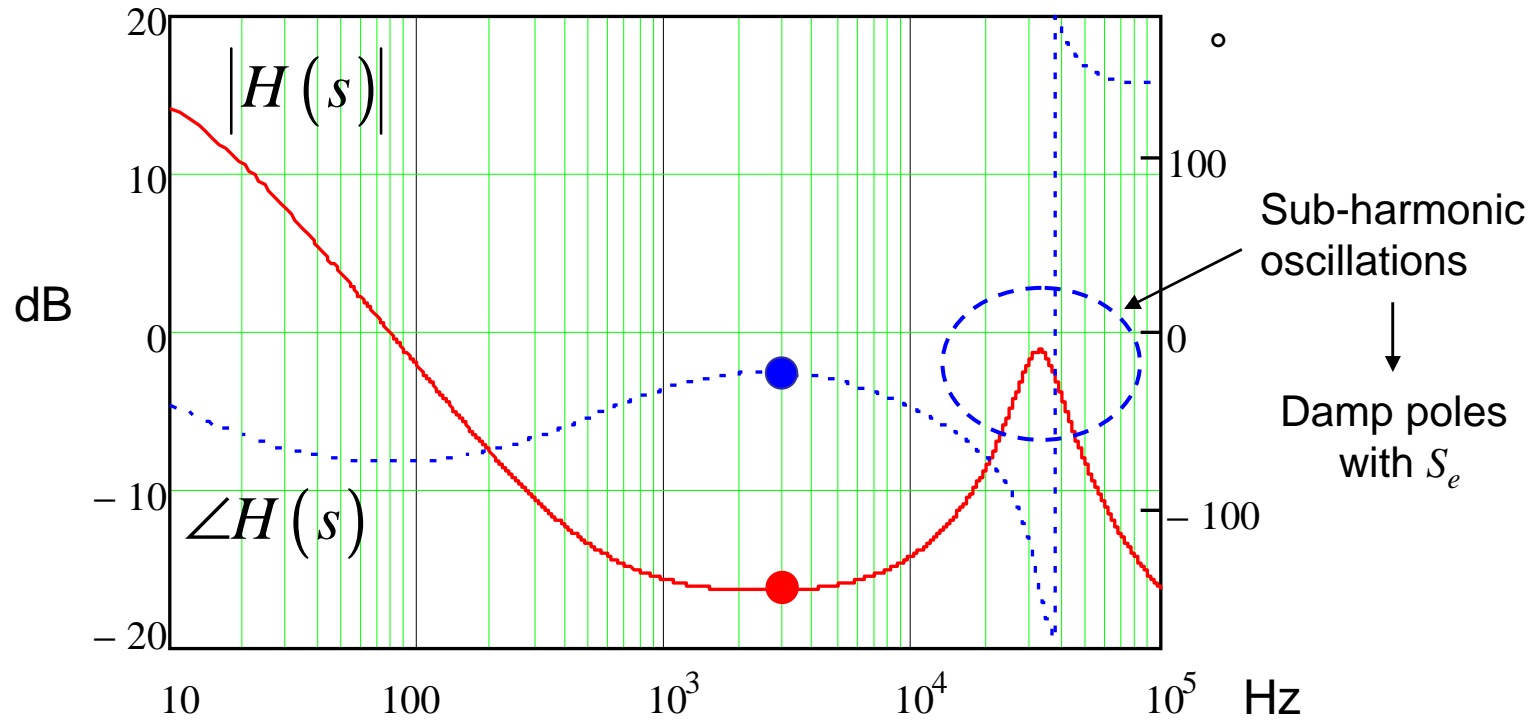
# Fixed-Frequency Current-Mode

- Extract the information at the selected crossover frequency



$$|H(3 \text{ kHz})| = -16.3 \text{ dB}$$

$$\arg H(3 \text{ kHz}) = -23^\circ$$

Low line, high power

# Fixed-Frequency Current-Mode

□ The compensation strategy is the following:

▪ compensate the gain loss at  $f_c$  so that  $|G(3\text{kHz})| = +16.3\text{dB}$

▪ evaluate the boost in phase at  $f_c$  to get phase 70° margin:

$$\text{Boost} = \text{PM} - \arg H(f_c) - 90 = 3.15^\circ$$

→ Boost = 0 select type 1 – origin pole  
→ Boost < 90° select type 2 – origin pole, 1 pole, 1 zero

□  $k$ -factor can be used to place the pole and the zero

$$k = \tan\left(\frac{\text{boost}}{2} + 45\right) \approx 1 \longrightarrow \text{poles and zeros are coincident}$$


$$f_{pk1} = kf_c = 1 \times 3k = 3 \text{ kHz}$$

$$f_{zk1} = \frac{f_c}{k} = \frac{3k}{1} = 3 \text{ kHz}$$



# Fixed-Frequency Current-Mode

- Plot the compensator transfer function

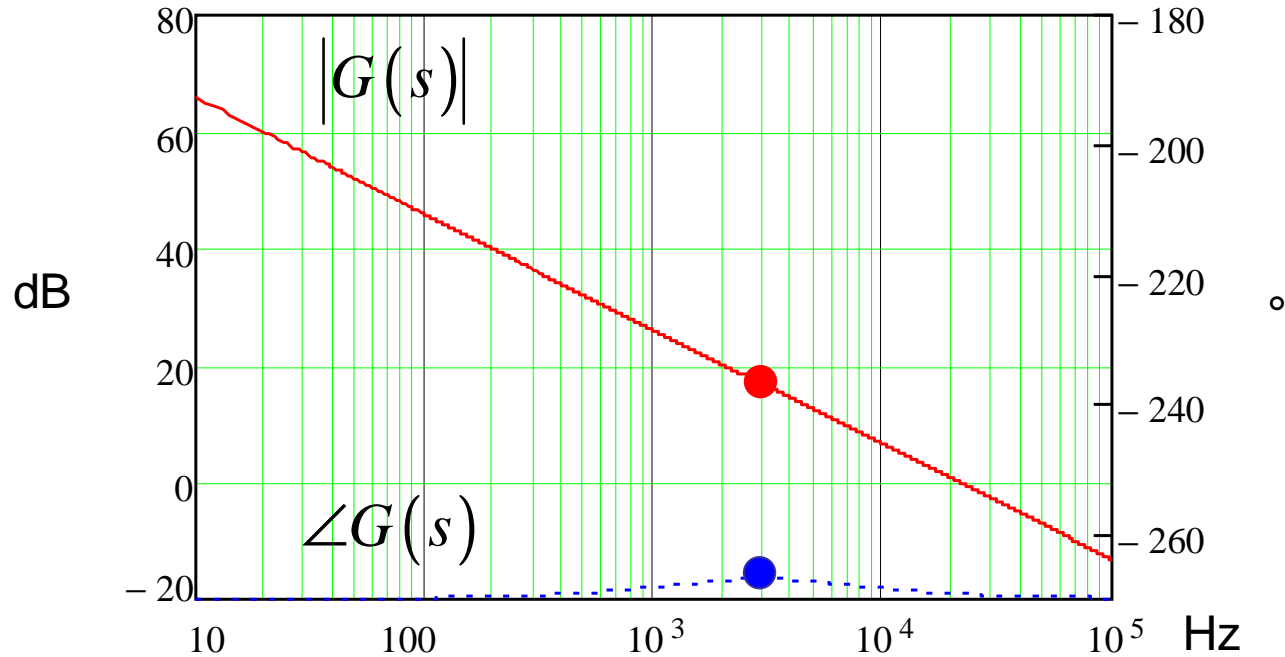


$$|G(f)| = 20 \log_{10} \left[ G \frac{\sqrt{1 + \left(\frac{f}{f_{zk1}}\right)^2}}{\frac{f}{f_{pk0}} \sqrt{1 + \left(\frac{f}{f_{pk1}}\right)^2}} \right]$$

$$boost = \left( \tan^{-1} \left( \frac{f}{f_{zk1}} \right) - \tan^{-1} \left( \frac{f}{f_{pk1}} \right) \right) \frac{180}{\pi}$$
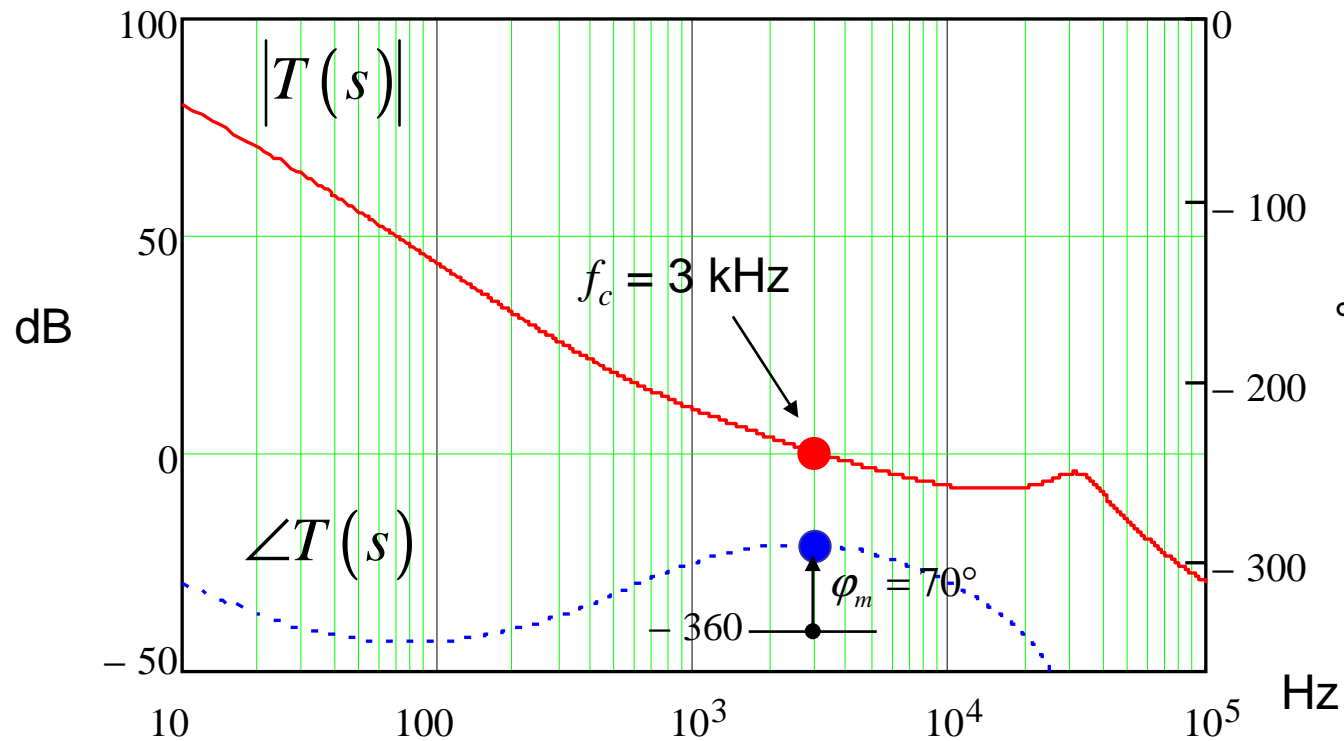
# Fixed-Frequency Current-Mode

- Plot the loop gain transfer function  $G(s)H(s)$  and check the margin




- Sweep ESR,  $C_{out}$ ,  $R_{load}$  and verify the results

Low line, high power
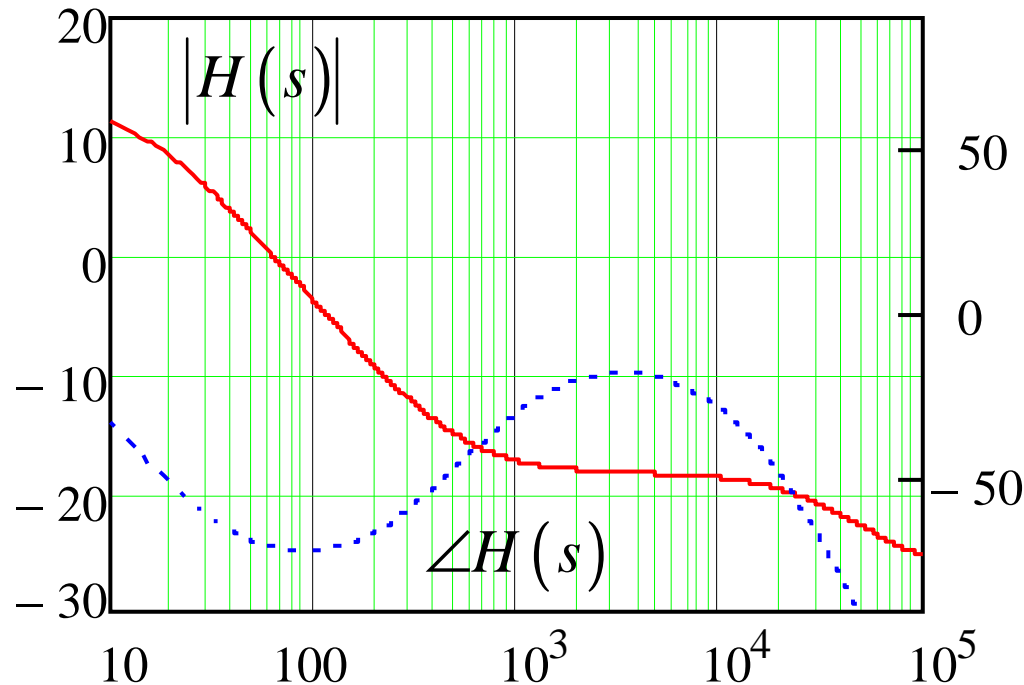
# Fixed-Frequency Current-Mode

- ❑ In case the converter transitions to DCM, update the equation




$$H(s) = G_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 - \frac{s}{\omega_{z_2}}\right)}{\left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)}$$

- Yes, analytical analysis is long and tedious.
- But, it teaches where the threats are and how to deal with!



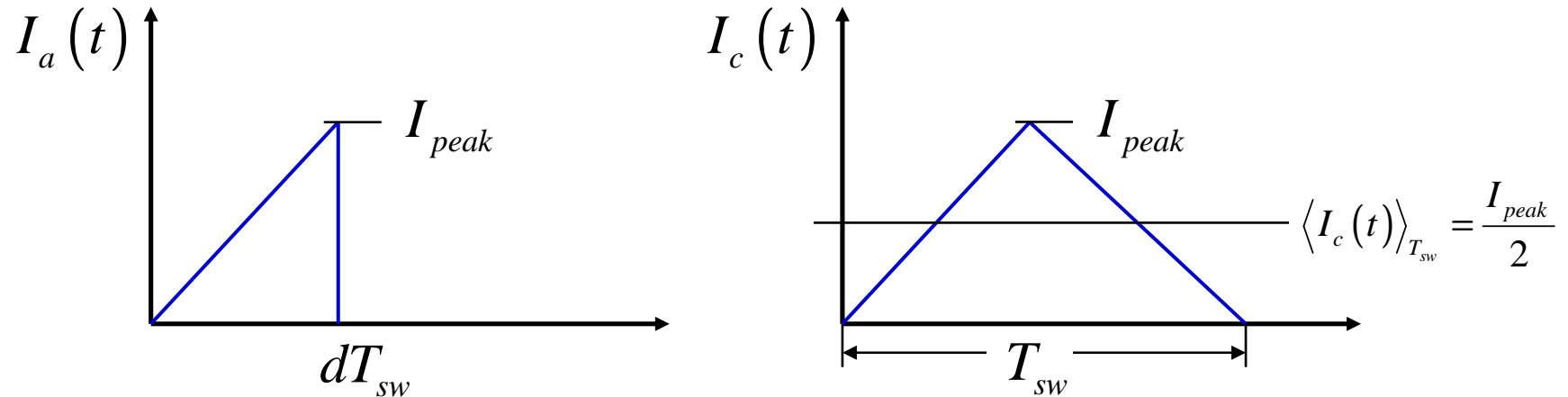
# Variable-Frequency Current-Mode

- Observing the waveforms helps us to derive an average mode



- It gives birth to a large-signal model

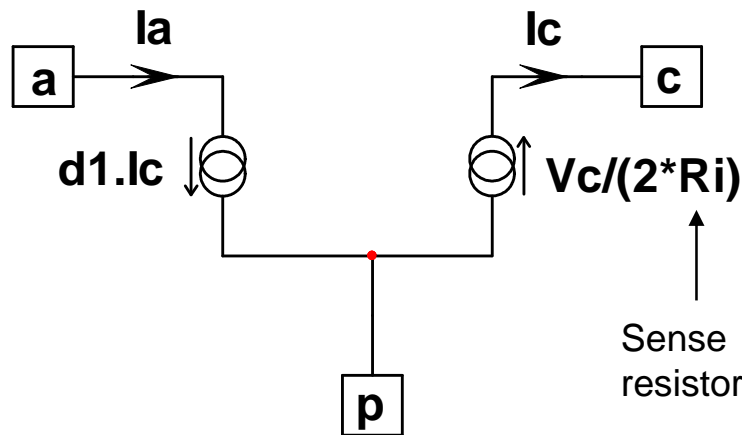

$$V_c = \frac{2R_i P_{out} (V_{out} + NV_{in})}{V_{in} V_{out}}$$

$$T_{sw} = \frac{V_c L_p}{R_i} \left( \frac{1}{V_{in}} + \frac{N}{V_{out}} \right)$$


$$d_1 = \frac{2P_{out} R_i}{V_c V_{in}}$$




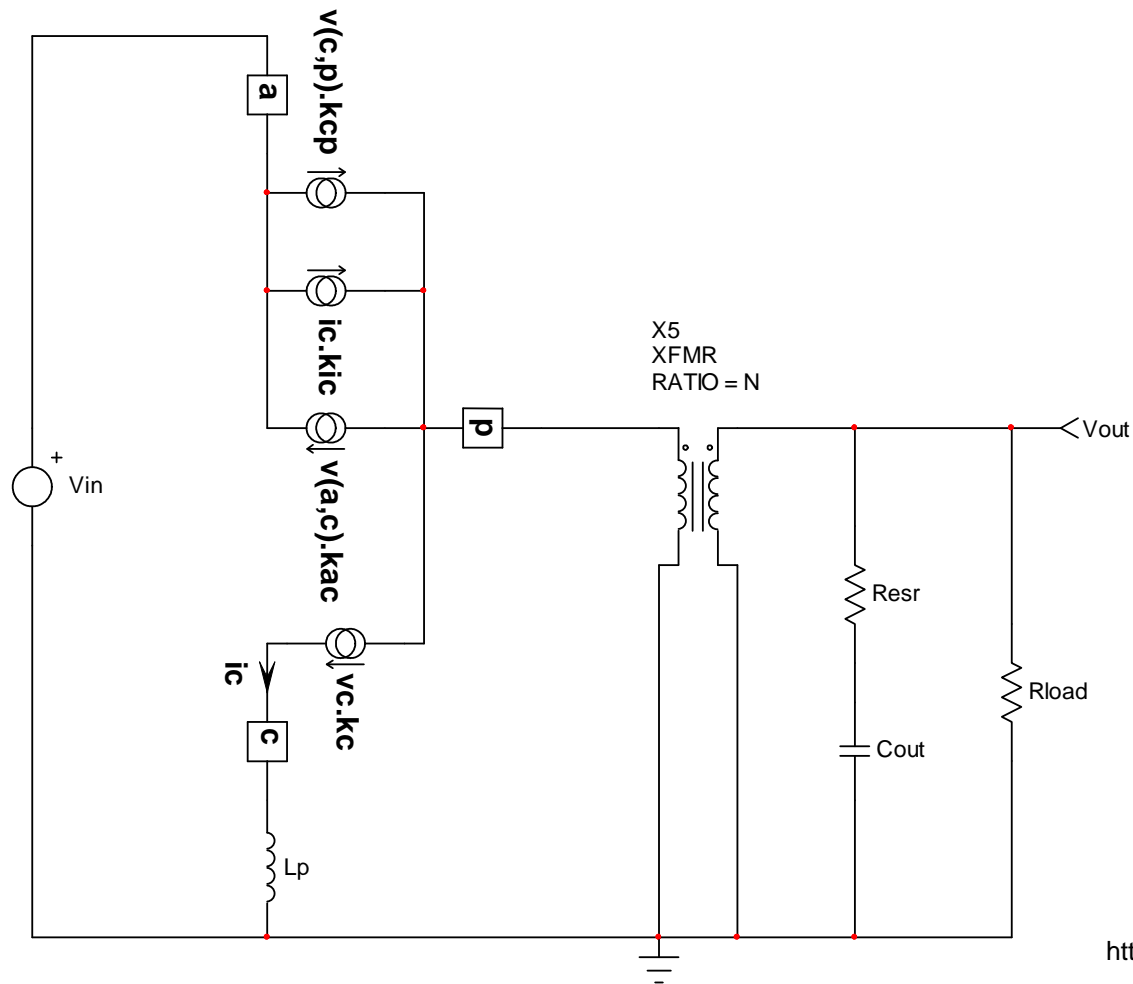
# Variable-Frequency Current-Mode

- ❑ Linearization is needed to get a small-signal model
- ❑ Implement this small-signal model in a flyback configuration



<http://cbasso.pagesperso-orange.fr/Spice.htm>

# Variable-Frequency Current-Mode

- Derive the transfer function and isolate poles and zeros

$$\frac{\hat{v}_{out}(s)}{\hat{v}_c(s)} = G_0 \frac{\left(1 + \frac{s}{s_{z1}}\right) \left(1 - \frac{s}{s_{z2}}\right)}{\left(1 + \frac{s}{s_{p1}}\right)}$$

1<sup>st</sup> order  $\longrightarrow$



$$G_0 = \frac{R_{load} Div}{2NR_i \left(\frac{2V_{out}}{NV_{in}} + 1\right)}$$

$$f_{p1} = \frac{1}{2\pi R_{load} C_{out}} \frac{2M+1}{M+1}$$

$$f_{z1} = \frac{1}{2\pi R_{ESR} C_{out}}$$

$$f_{z2} = \frac{R_{load}}{2\pi N^2 L_p} \frac{1}{M(1+M)}$$

- Then plot the function

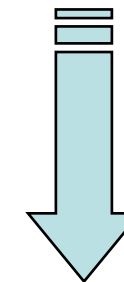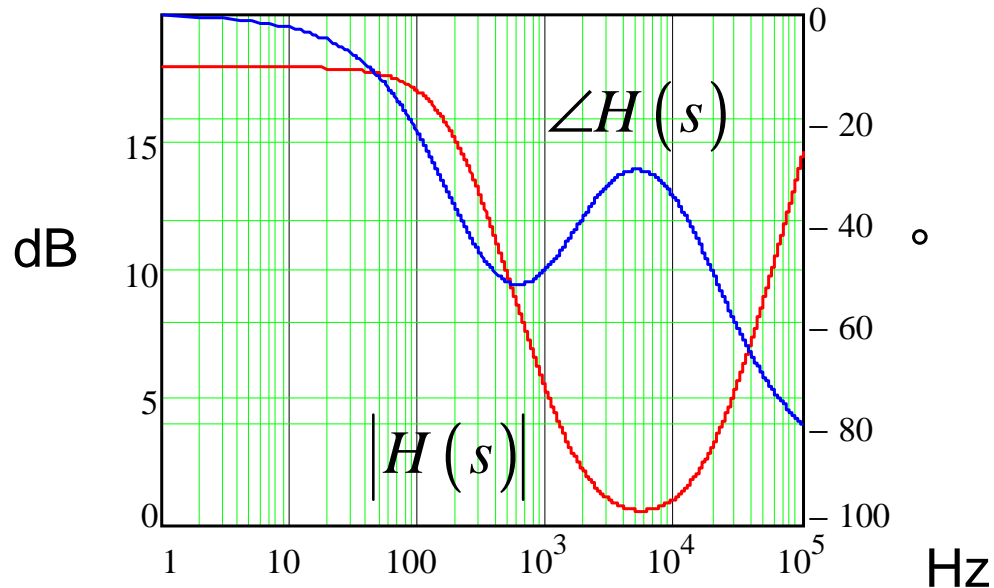

Tailor  $G(s)$  to get the desired  $f_c$

# Use a SPICE Model to Stabilize the Converter

parameters

Vout=19

Ibridge=250u  
 Rlower=2.5/Ibridge  
 Rupper=(Vout-2.5)/Ibridge

Lp=600u  
 Fs=70k  
 Rsense=0.5  
 Se=0

fc=1k  
 pm=60  
 Gfc=-21  
 pfc=-88


$G=10^{-(Gfc/20)}$   
 boost=pm-(pfc)-90  
 pi=3.14159  
 $K=\tan((boost/2+45)*\pi/180)$

Fzero=fc/k  
 Fpole=k\*fc

Rpulldown=4.7k  
 RLED=CTR\*Rpulldown/G  
 $Czero=1/(2*\pi*Fzero*Rupper)$   
 $Cpole=1/(2*\pi*Fpole*Rpulldown)$

CTR=0.9  
 Pole=15k


Automate the compensation!

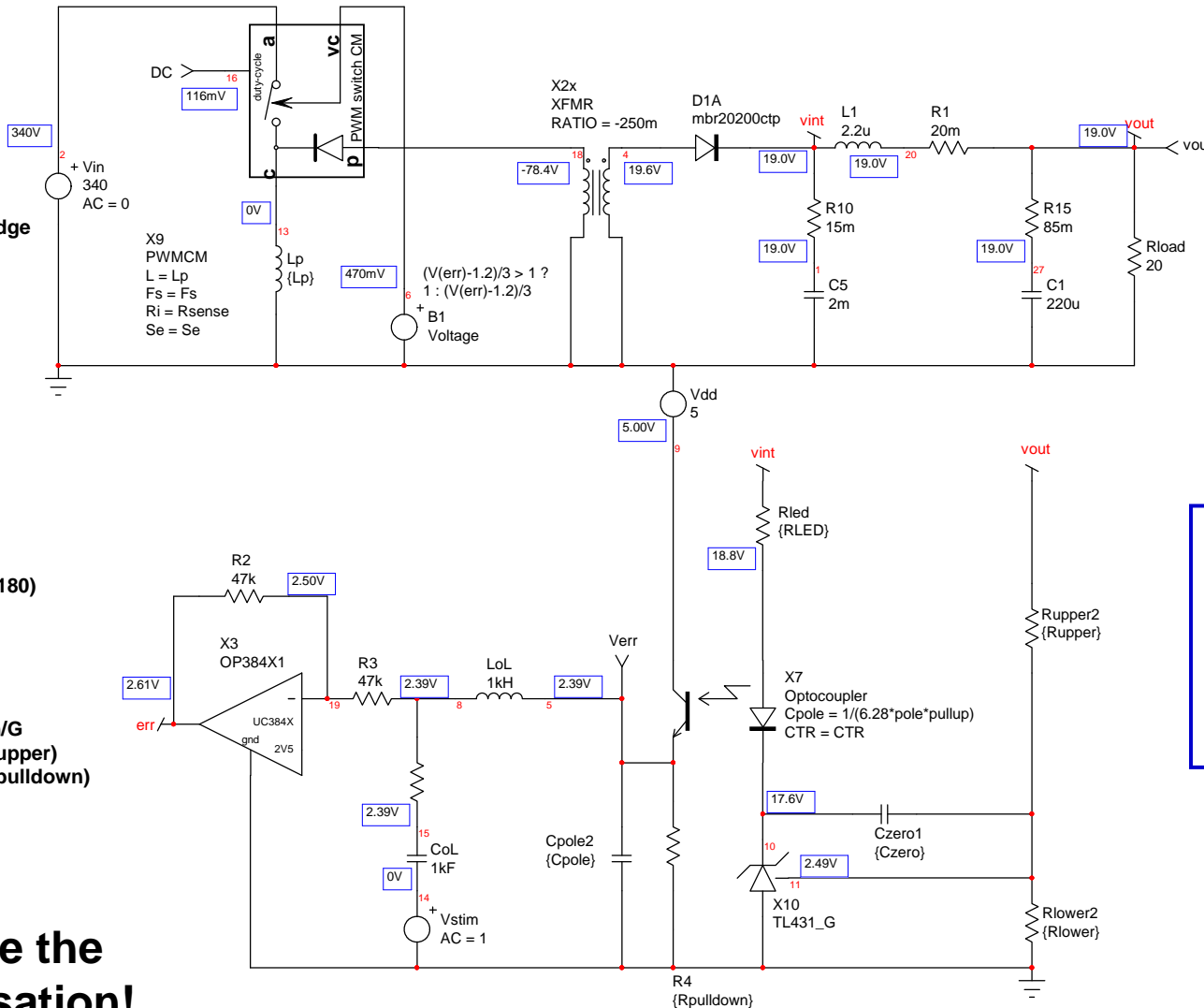

Cannot be beaten for simplicity and speed!


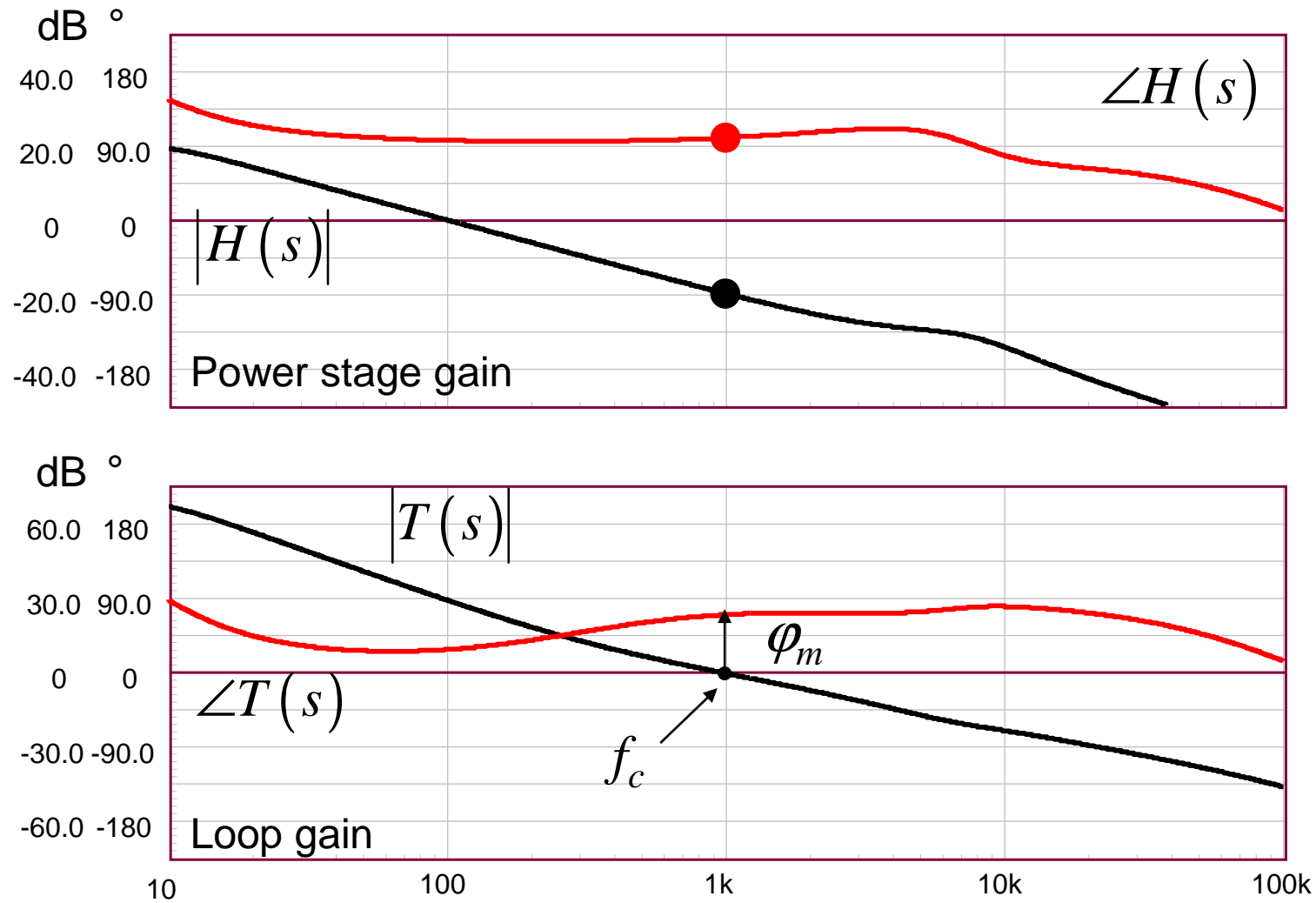
# Unveil the Transfer Function in a Second



---




# Course Agenda

- The Flyback Converter
- The Parasitic Elements
- How These Parasitics Affect your Design?
- Current-Mode is the Most Popular Scheme
- Fixed or Variable Frequency?
- More Power than Needed
- The Frequency Response
- Compensating With the TL431**



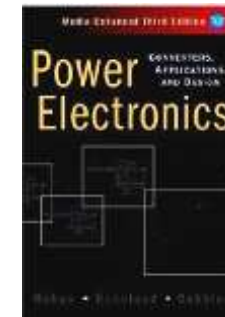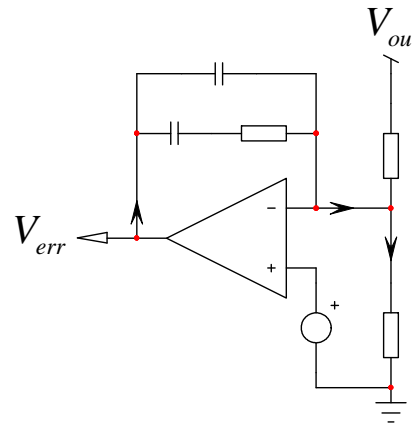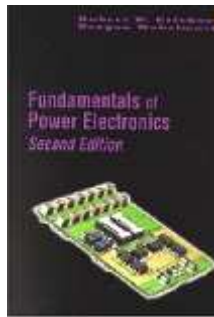
# How is regulation performed?


- ❑ Text books only describe op amps in compensators...





- ❑ The market reality is different: the TL431 rules!

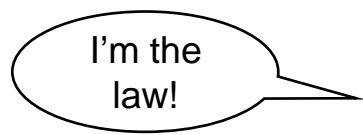

TL431



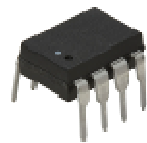


optocoupler

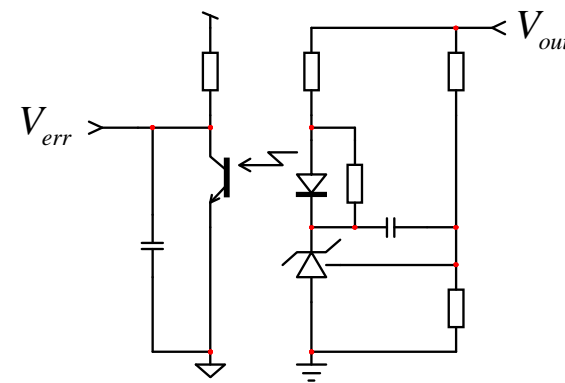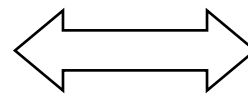
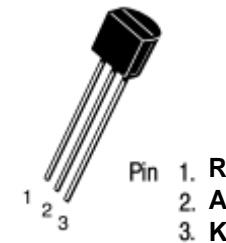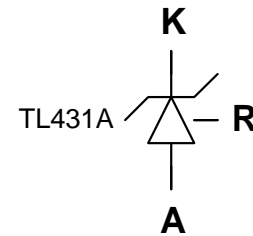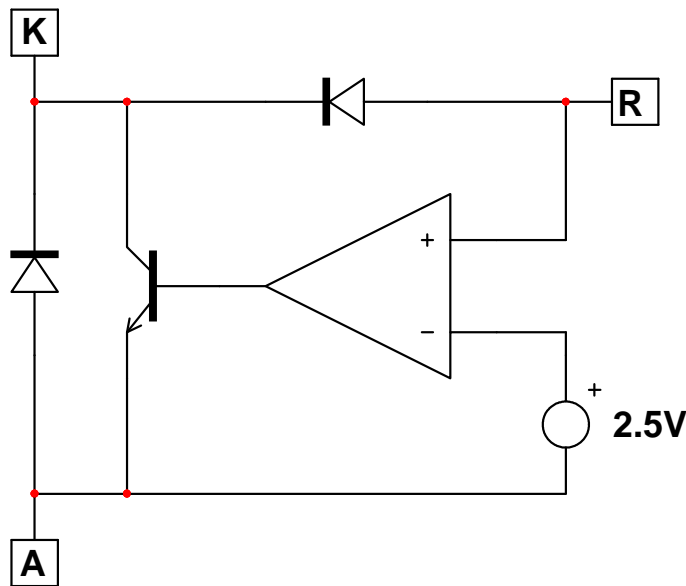
# The TL431 Programmable Zener



- ❑ The TL431 is the most popular choice in nowadays designs
- ❑ It associates an open-collector op amp and a reference voltage
- ❑ The internal circuitry is self-supplied from the cathode current
- ❑ When the R node exceeds 2.5 V, it sinks current from its cathode



- ❑ The TL431 is a shunt regulator
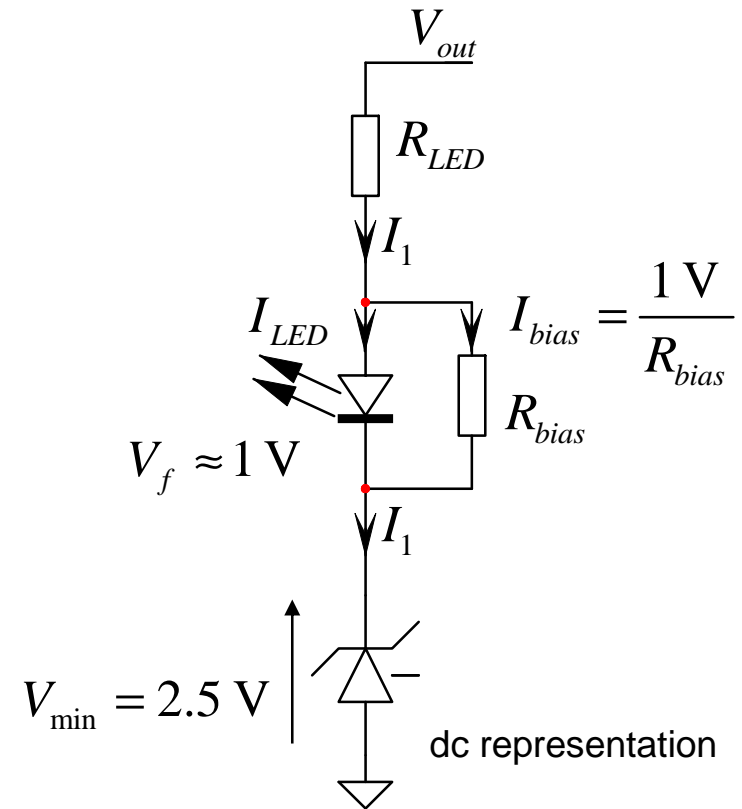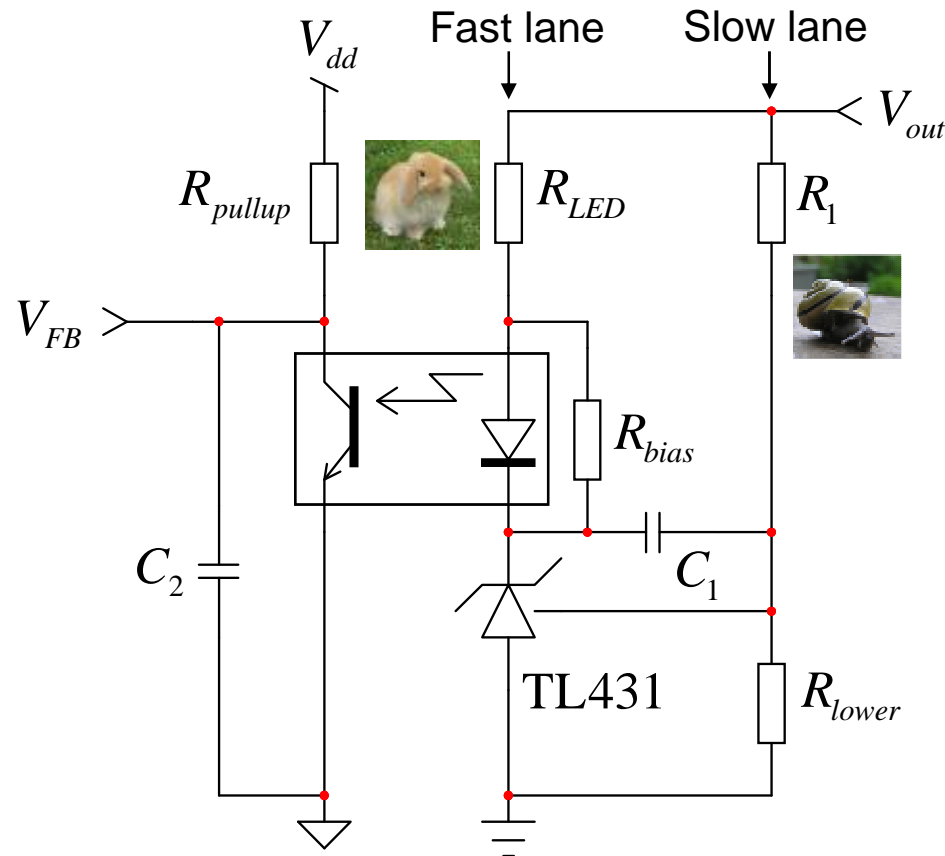
# A Rabbit and a (French) Snail...

- The TL431 lends itself very well to optocoupler control



- $R_{LED}$  must leave enough headroom over the TL431: upper limit!




# Understanding the Fast Lane Drawback

- This LED resistor is a design limiting factor in low output voltages:

$$R_{LED,max} \leq \frac{V_{out} - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min} R_{pullup}} R_{pullup} CTR_{min}$$

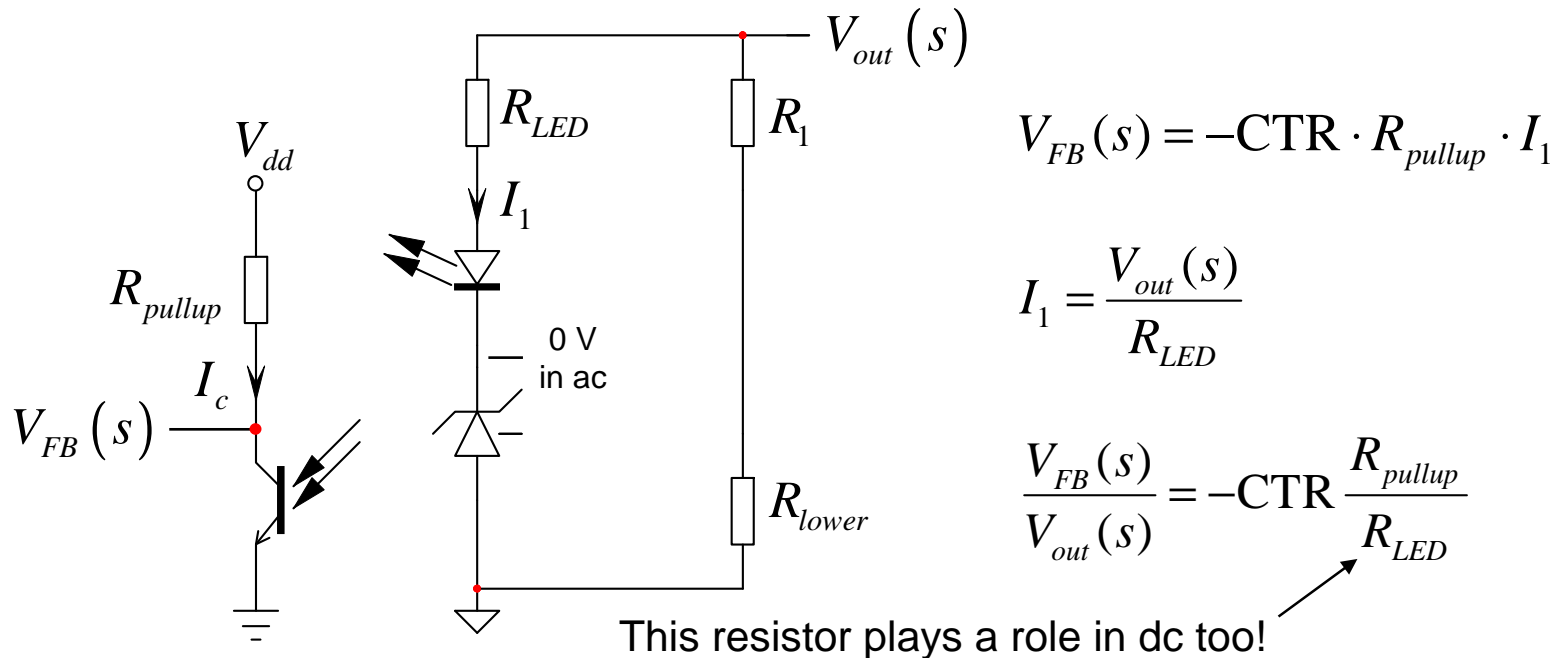- When the capacitor  $C_1$  is a short-circuit,  $R_{LED}$  fixes the fast lane gain



# The Static Gain Limit

□ Let us assume the following design:

$$V_{out} = 5 \text{ V}$$

$$V_f = 1 \text{ V}$$

$$V_{TL431,min} = 2.5 \text{ V}$$

$$V_{dd} = 4.8 \text{ V}$$


$$V_{CE,sat} = 300 \text{ mV}$$

$$I_{bias} = 1 \text{ mA}$$


$$CTR_{min} = 0.3$$

$$R_{pullup} = 20 \text{ k}\Omega$$
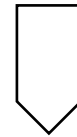
$$R_{LED,max} \leq \frac{5 - 1 - 2.5}{4.8 - 0.3 + 1m \times 0.3 \times 20k} \times 20k \times 0.3$$



$$R_{LED,max} \leq 857 \Omega$$

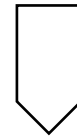

$$G_0 > CTR \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{0.857} > 7 \text{ or } \approx 17 \text{ dB}$$


□ In designs where  $R_{LED}$  fixes the gain,  $G_0$  cannot be below 17 dB

⇒ You cannot “amplify” by less than 17 dB




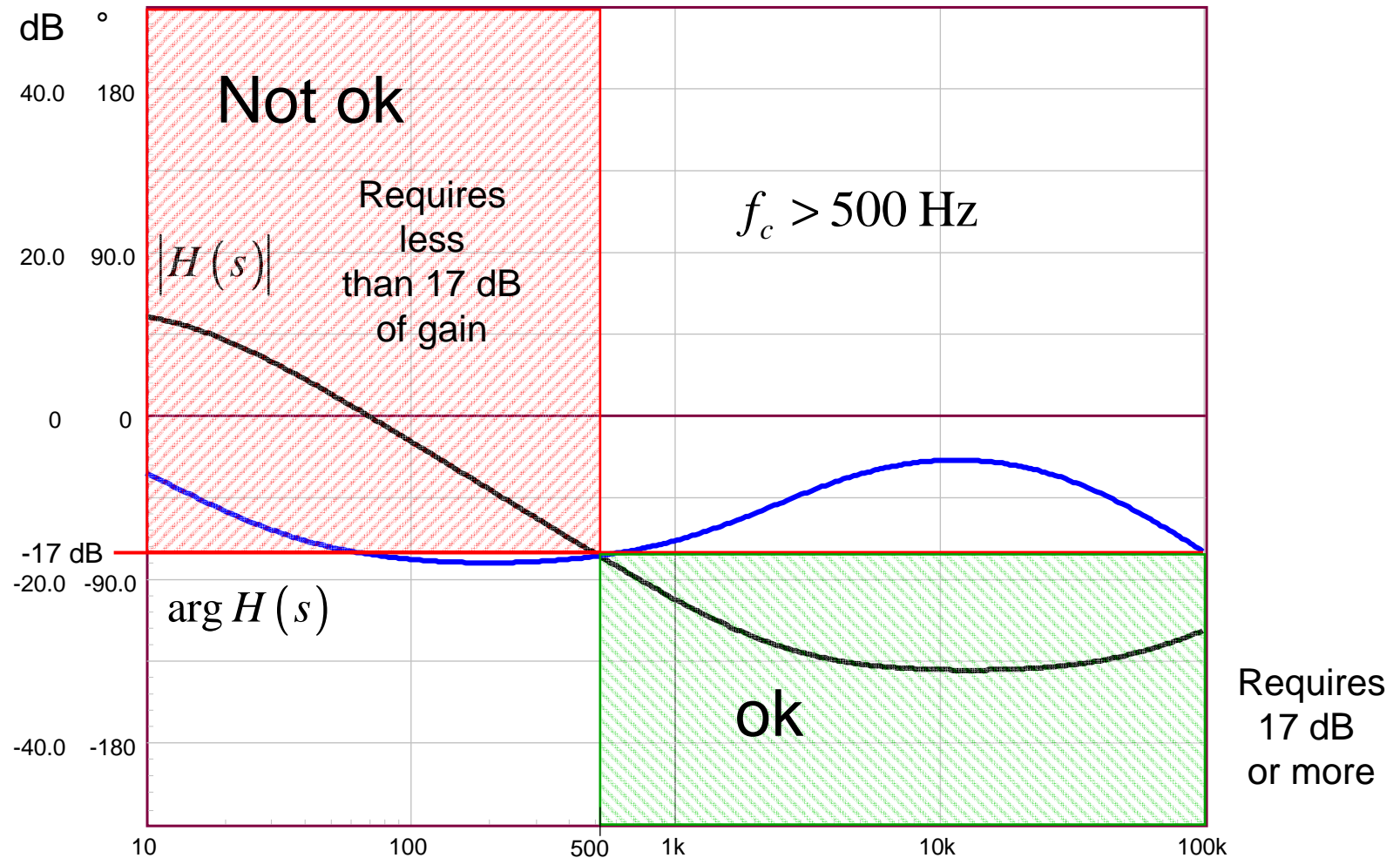
# Forbidden Compensation Areas

- ❑ You must identify the areas where compensation is possible


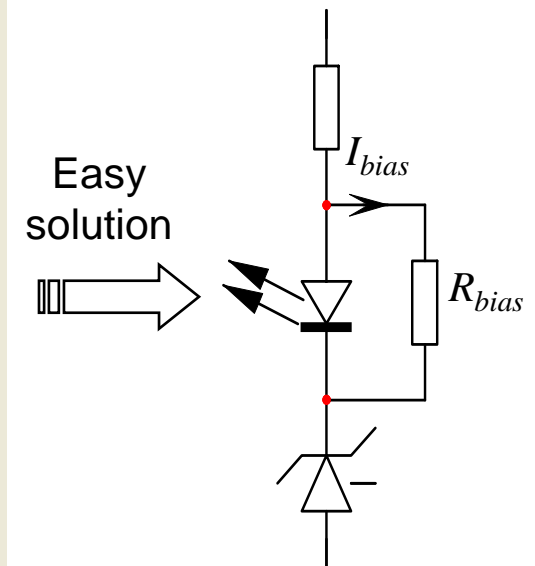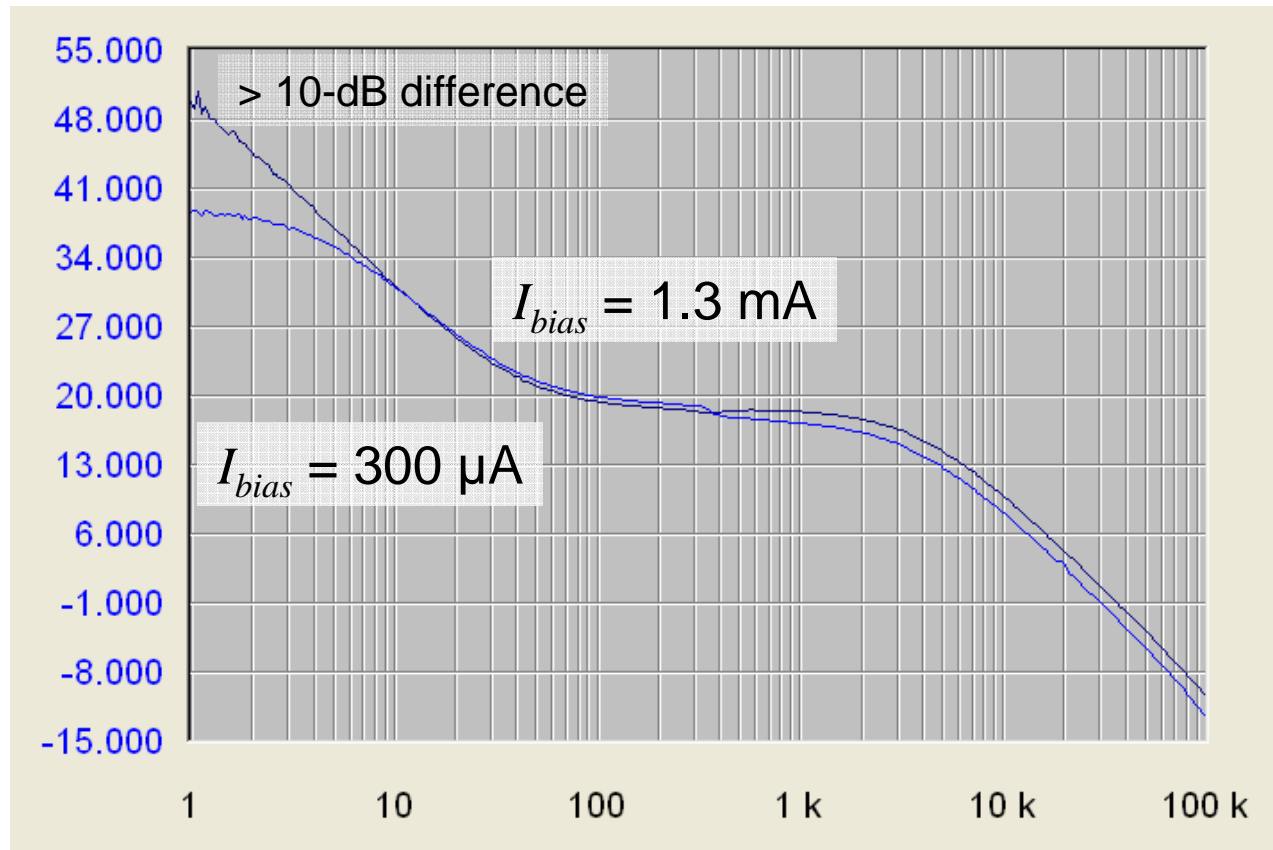
# Injecting Bias Current


- ❑ Make sure enough current always biases the TL431
- ❑ If not, open-loop gain suffers – a 10-dB difference can be observed!



$$R_{bias} = \frac{1}{1m} = 1 \text{ k}\Omega$$
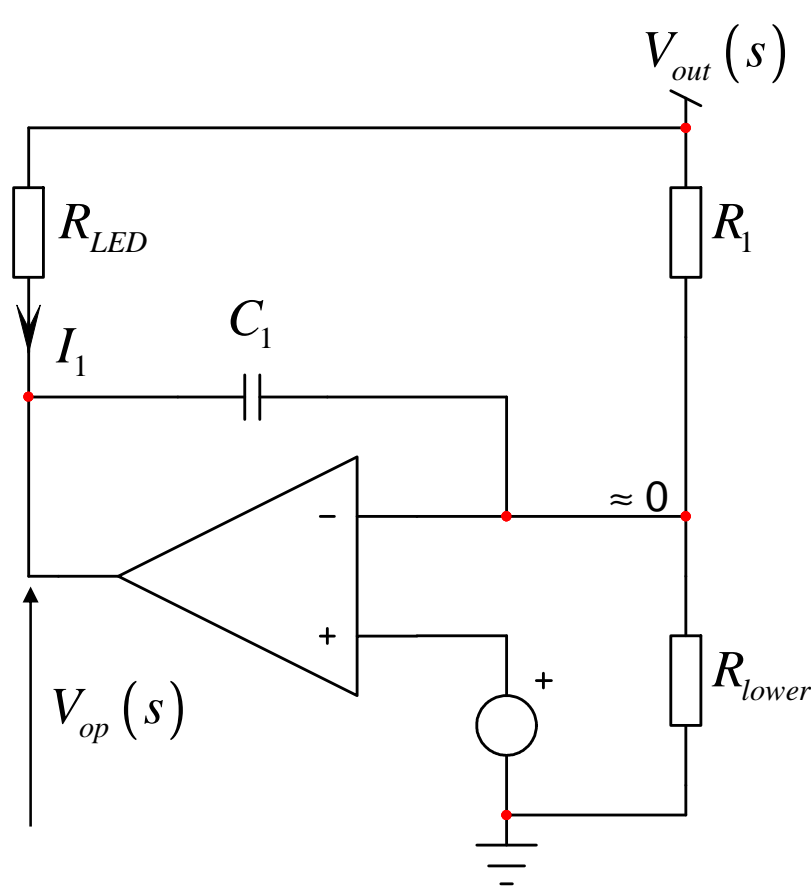
# Small-Signal Analysis

- ❑ The TL431 is an open-collector op amp with a reference voltage
- ❑ Neglecting the LED dynamic resistance, we have:



$$I_1(s) = \frac{V_{out}(s) - V_{op}(s)}{R_{LED}}$$

$$V_{op}(s) = -V_{out}(s) \frac{sC_1}{R_{upper}} = -V_{out}(s) \frac{1}{sR_{upper}C_1}$$

$$\frac{I_1(s)}{V_{out}(s)} = \frac{1}{R_{LED}} \left[ \frac{1 + sR_{upper}C_1}{sR_{upper}C_1} \right]$$

We know that:  $V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup} CTR}{R_{LED}} \left[ \frac{1 + sR_{upper}C_1}{sR_{upper}C_1} \right]$$

# Creating a High-Frequency Pole


❑ In the previous equation we have:

✓ a static gain  $G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}}$

✓ a 0-dB origin pole frequency  $\omega_{p_0} = \frac{1}{C_1 R_{\text{upper}}}$


✓ a zero  $\omega_{z_1} = \frac{1}{R_{\text{upper}} C_1}$

❑ We are missing a pole for the type 2!

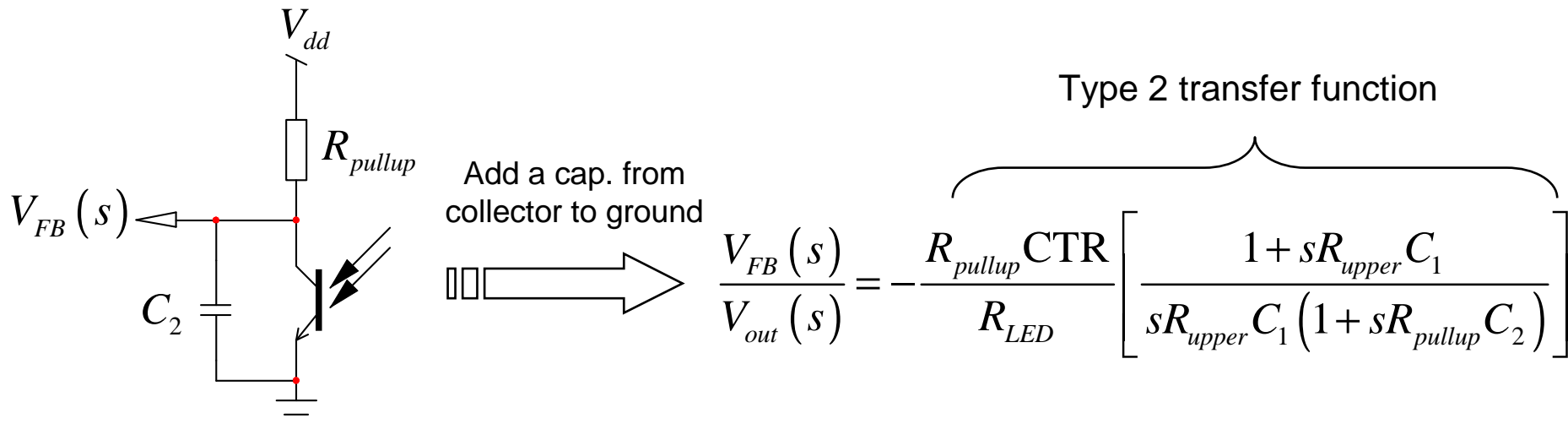


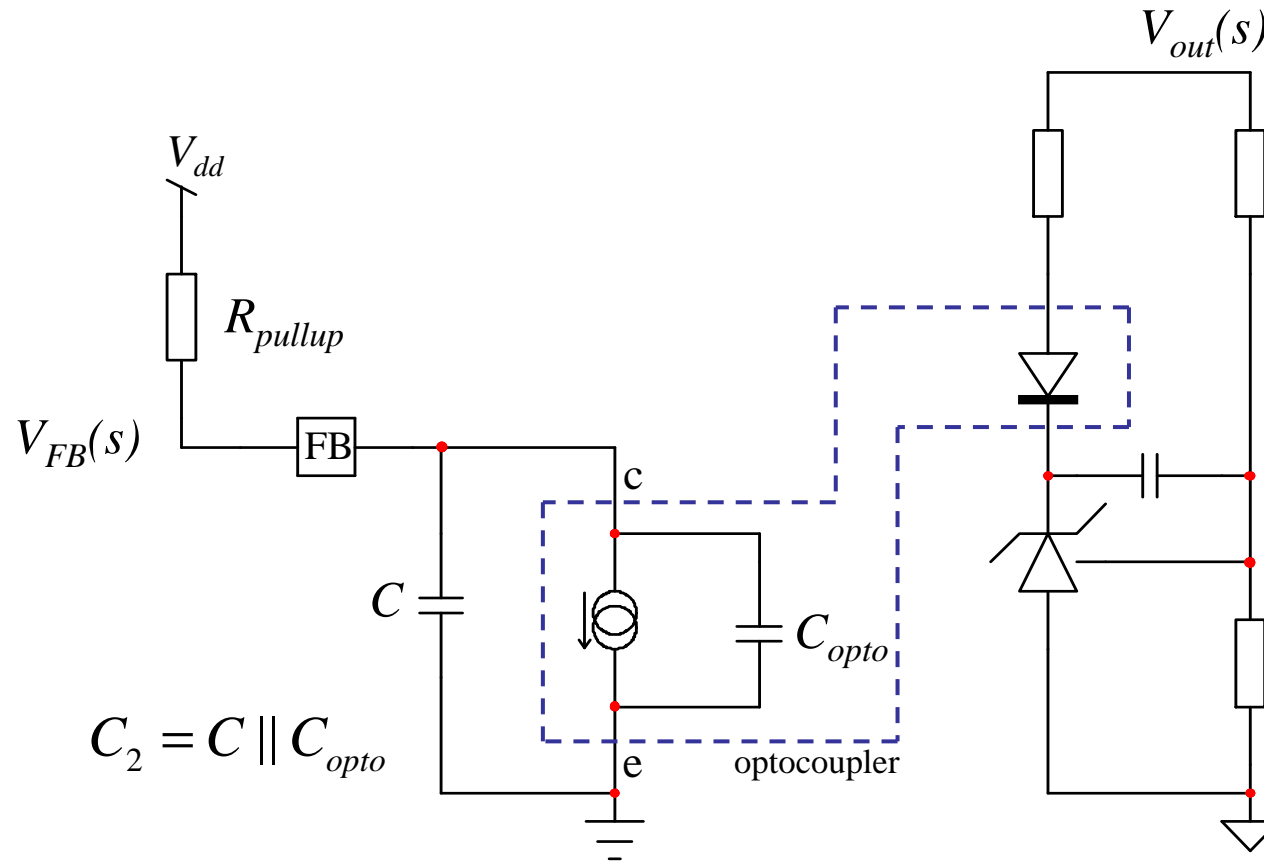
# Understanding the Optocoupler Pole

- ❑ The optocoupler also features a parasitic capacitor
  - it comes in parallel with  $C_2$  and must be accounted for


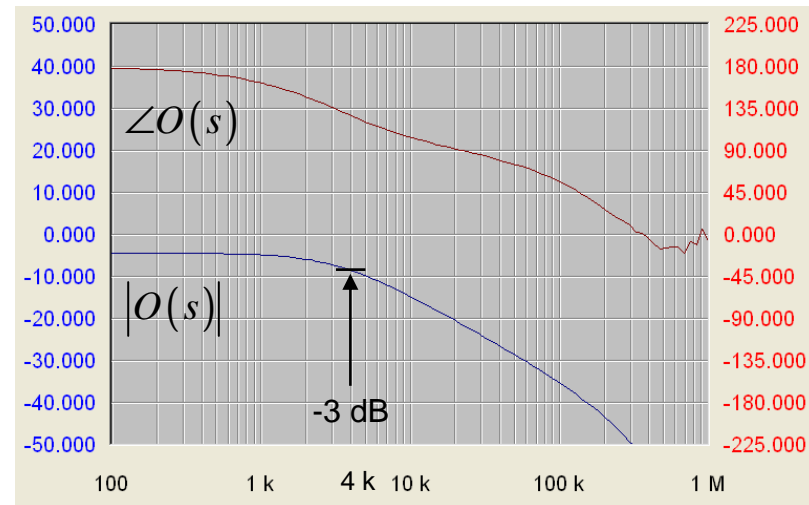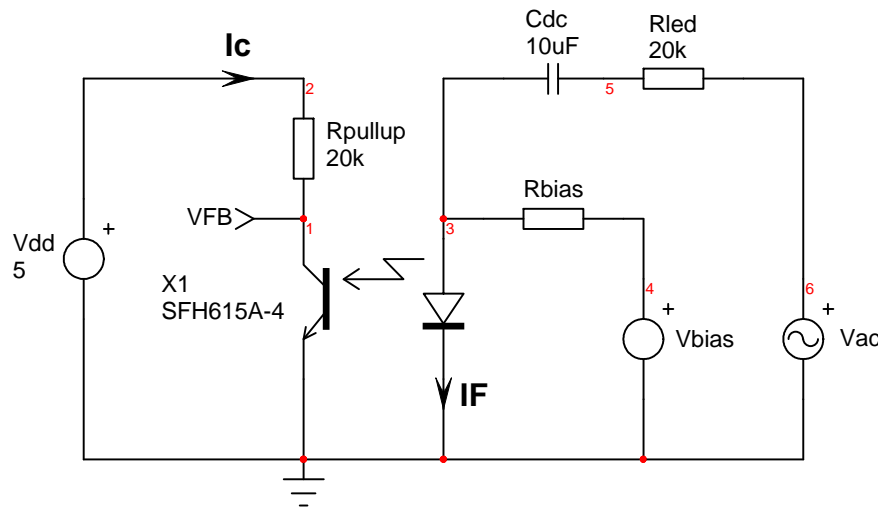
# Extracting the Pole

- The optocoupler must be characterized to know where its pole is



- Adjust  $V_{bias}$  to have  $V_{FB}$  at 2-3 V to be in linear region, then ac-sweep
- The pole in this example is found at 4 kHz

$$C_{opto} = \frac{1}{2\pi R_{pullup} f_{pole}} = \frac{1}{6.28 \times 20k \times 4k} \approx 2 \text{ nF} \quad \Rightarrow \quad \text{Another design constraint!}$$



# The TL431 in a Type 1 Compensator

- To make a type 1 (origin pole only) neutralize the zero and the pole

$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup} CTR}{R_{LED}} \left[ \frac{1 + sR_{upper} C_1}{sR_{upper} C_1 (1 + sR_{pullup} C_2)} \right]$$

$$sR_{upper} C_1 = sR_{pullup} C_2 \quad \Rightarrow \quad C_1 = \frac{R_{pullup}}{R_{upper}} C_2 \quad \xrightarrow{\text{substitute}} \quad \omega_{p_o} = \frac{1}{\frac{R_{upper} R_{LED}}{R_{pullup} CTR} C_1}$$

$$\omega_{p_o} = \frac{CTR}{C_2 R_{LED}} \quad \Rightarrow \quad C_2 = \frac{CTR}{2\pi f_{p_o} R_{LED}}$$

- Once neutralized, you are left with an integrator

$$G(s) = \frac{1}{s} \quad \xrightarrow{\omega_{p_o}} \quad |G(f_c)| = \frac{f_{p_o}}{f_c} \quad \rightarrow \quad f_{p_o} = G_{f_c} f_c \quad \Rightarrow \quad C_2 = \frac{CTR}{2\pi G_{f_c} f_c R_{LED}}$$



# A Type 1 Design Example

- We want a 5-dB gain at 5 kHz to stabilize the 5-V converter

$$V_{out} = 5 \text{ V}$$

$$V_f = 1 \text{ V}$$

$$V_{TL431,min} = 2.5 \text{ V}$$

$$V_{dd} = 4.8 \text{ V}$$

$$V_{CE,sat} = 300 \text{ mV}$$

$$I_{bias} = 1 \text{ mA}$$

$$CTR_{min} = 0.3$$

$$R_{pullup} = 20 \text{ k}\Omega$$

Apply 15%  
margin


$$R_{LED,max} \leq 857 \Omega \longrightarrow R_{LED} = 728 \Omega$$

$$G_{fc} = 10^{\frac{5}{20}} = 1.77$$

$$f_c = 5 \text{ kHz}$$

$$C_2 = \frac{CTR}{2\pi G_{fc} f_c R_{LED}} = \frac{0.3}{6.28 \times 1.77 \times 5k \times 728} \approx 7.4 \text{ nF}$$

$$C_{opto} = 2 \text{ nF}$$

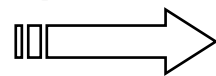

$$C = 7.4n - 2n = 5.4 \text{ nF} \quad C_1 = \frac{R_{pullup}}{R_{upper}} C_2 \approx 14.7 \text{ nF}$$



# Simulation of the Type 1

- ❑ SPICE can simulate the design – automate elements calculations...

parameters

Vout=5

Vf=1

Vref=2.5

VCEsat=300m

Vdd=4.8

Ibias=1m

$A = V_{out} - V_f - V_{ref}$

$B = V_{dd} - V_{CEsat} + I_{bias} * CTR * R_{pullup}$

$R_{max} = (A/B) * R_{pullup} * CTR$

$R_{upper} = (V_{out} - 2.5) / 250u$

fc=5k

Gfc=-5

$G = 10^{(-G_{fc}/20)}$

pi=3.14159

Fpo=G\*fc

Rpullup=20k

RLED=Rmax\*0.85

$C1 = C_{pole1} * R_{pullup} / R_{upper}$


$C_{pole1} = CTR / (2 * pi * F_{po} * R_{LED})$

$C_{pole} = C_{pole1} - C_{opto}$

Fopto=4k


$C_{opto} = 1 / (2 * pi * F_{opto} * R_{pullup})$

CTR = 0.3

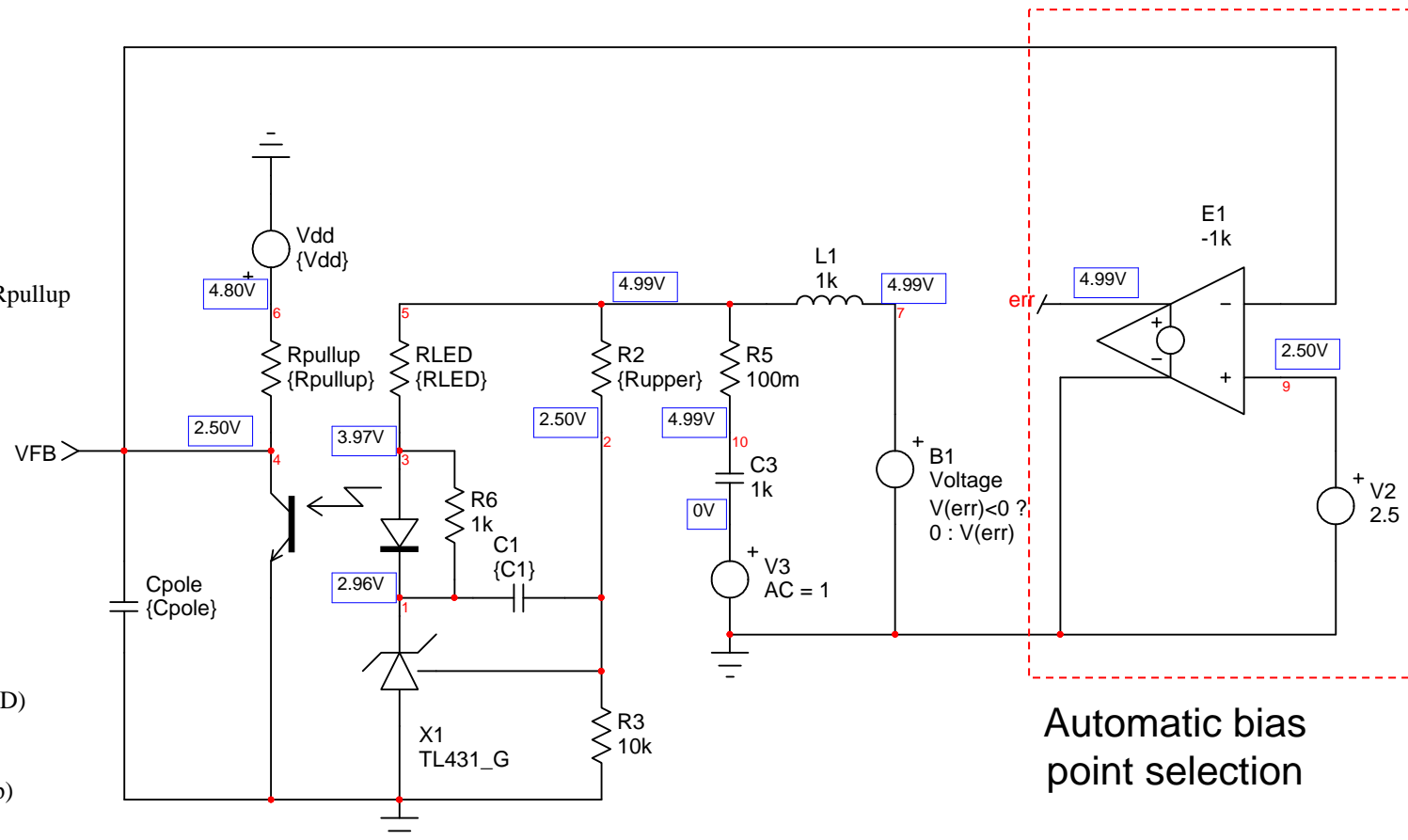

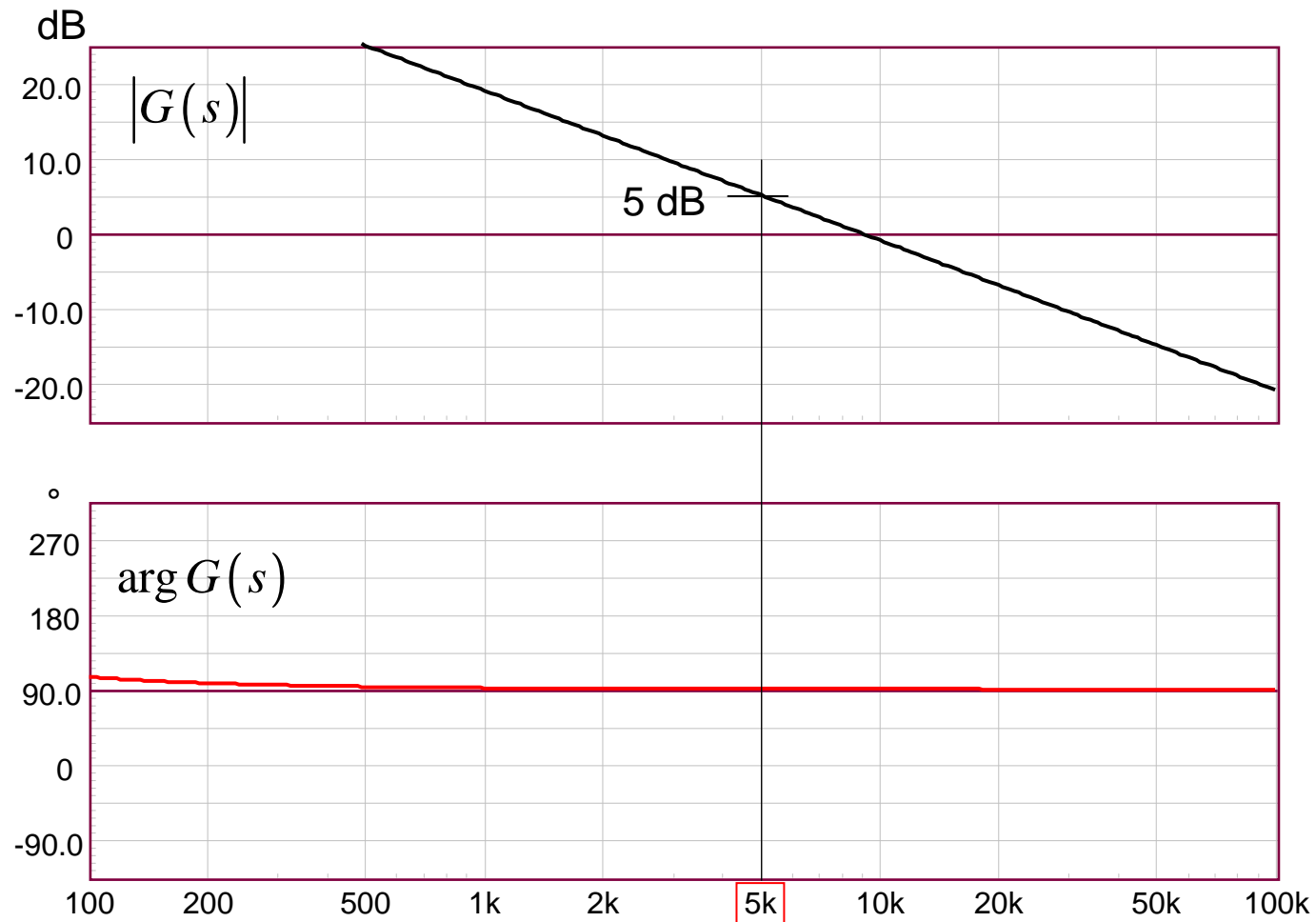
# Type 1 Simulation Results

- The pullup resistor is 1 kΩ and the target now reaches 5 dB


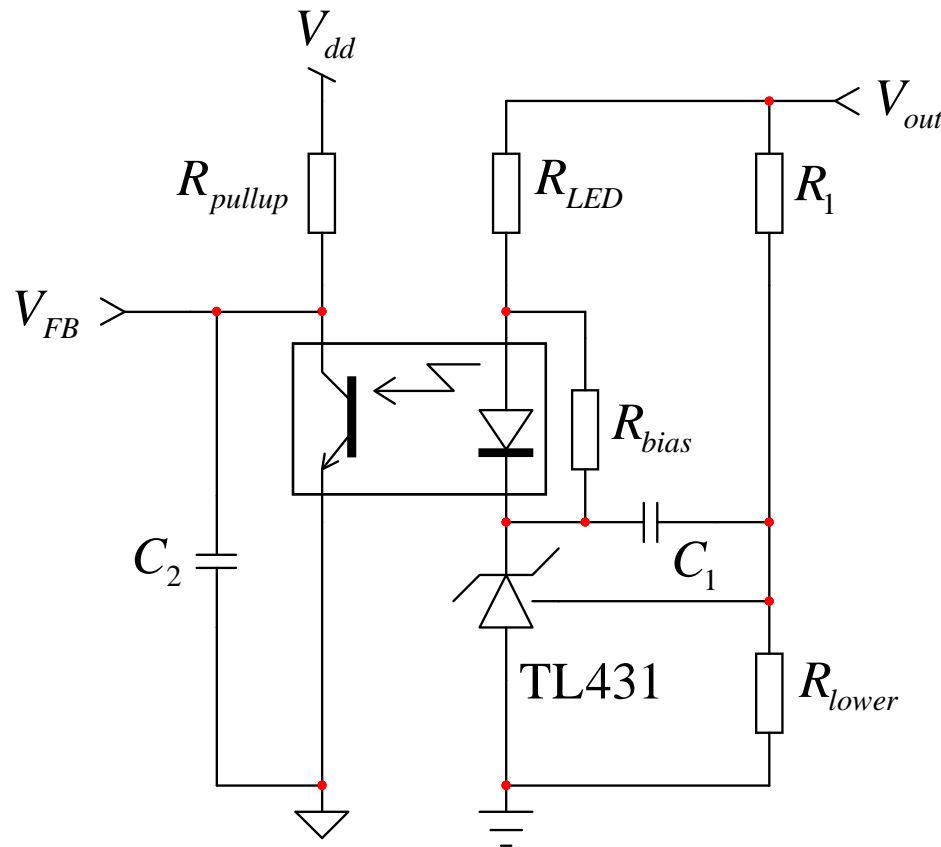
# The TL431 in a Type 2 Compensator

- Our first equation was already a type-2 definition, we are all set!



$$G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}}$$

$$\omega_{z_1} = \frac{1}{R_1 C_1}$$

$$\omega_{p_1} = \frac{1}{R_{\text{pullup}} C_2}$$

- Just make sure the optocoupler contribution is involved...

# Deriving Component Values for the Type 2

- You need to provide a 15-dB gain at 5 kHz with a 50° boost

$$f_p = \left[ \tan(\text{boost}) + \sqrt{\tan^2(\text{boost}) + 1} \right] f_c = 2.74 \times 5k = 13.7 \text{ kHz}$$

$$f_z = f_c^2 / f_p = 25k / 13.7k \approx 1.8 \text{ kHz} \quad G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}} = 10^{15/20} = 5.62$$

- With a 250-μA bridge current, the divider resistor is made of:

$$R_{\text{lower}} = 2.5 / 250\mu = 10 \text{ k}\Omega \quad R_1 = (12 - 2.5) / 250\mu = 38 \text{ k}\Omega$$

- The pole and zero respectively depend on  $R_{\text{pullup}}$  and  $R_1$ :

$$C_2 = 1 / 2\pi f_p R_{\text{pullup}} = 581 \text{ pF} \quad C_1 = 1 / 2\pi f_z R_1 = 2.3 \text{ nF}$$

- The LED resistor depends on the needed mid-band gain:

$$R_{\text{LED}} = \frac{R_{\text{pullup}} \text{CTR}}{G_0} = 1.06 \text{ k}\Omega \quad \xrightarrow{\text{ok}} \quad R_{\text{LED,max}} \leq 4.85 \text{ k}\Omega$$



# Checking the Optocoupler Contribution

- The optocoupler is still at a 4-kHz frequency:

$$C_{pole} \approx 2 \text{ nF} \quad \text{Already above!}$$

- Type 2 pole capacitor calculation requires a 581-pF cap.!

 The bandwidth cannot be reached, reduce  $f_c$ !

- For noise purposes, we want a minimum of 100 pF for  $C$
- With a total capacitance of 2.1 nF, the highest pole can be:

$$f_{pole} = \frac{1}{2\pi R_{pullup} C} = \frac{1}{6.28 \times 20k \times 2.1n} = 3.8 \text{ kHz}$$

- For a 50° phase boost and a 3.8-kHz pole, the crossover must be:

$$f_c = \frac{f_p}{\tan(\text{boost}) + \sqrt{\tan^2(\text{boost}) + 1}} \approx 1.4 \text{ kHz}$$

# Placing the Zero in the Transfer Function

- The zero is then simply obtained:

$$f_z = \frac{f_c^2}{f_p} = 516 \text{ Hz}$$

- We can re-derive the component values and check they are ok

$$C_2 = 1/2\pi f_p R_{pullup} = 2.1 \text{ nF} \quad C_1 = 1/2\pi f_z R_1 = 8.1 \text{ nF}$$

- Given the 2-nF optocoupler capacitor, we just add 100 pF

- In this example,  $R_{LED,max}$  is 4.85 k $\Omega$

$$G_0 > \text{CTR} \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{4.85} > 1.2 \text{ or } \approx 1.8 \text{ dB}$$


- You cannot use this type 2 if an attenuation is required at  $f_c$ !





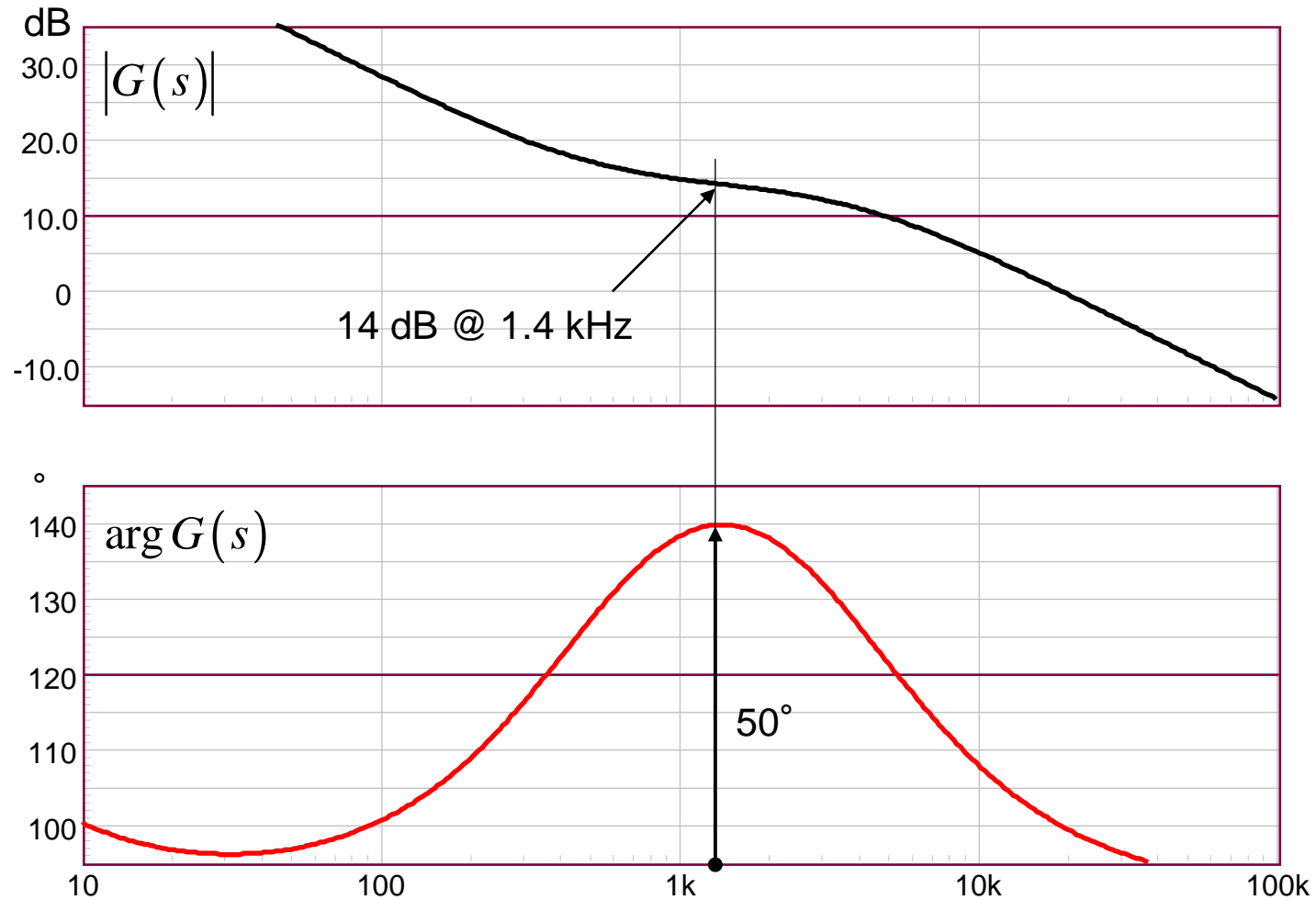
# TL431 type 2 Design Example

- The 1-dB gain difference is linked to  $R_d$  and the bias current



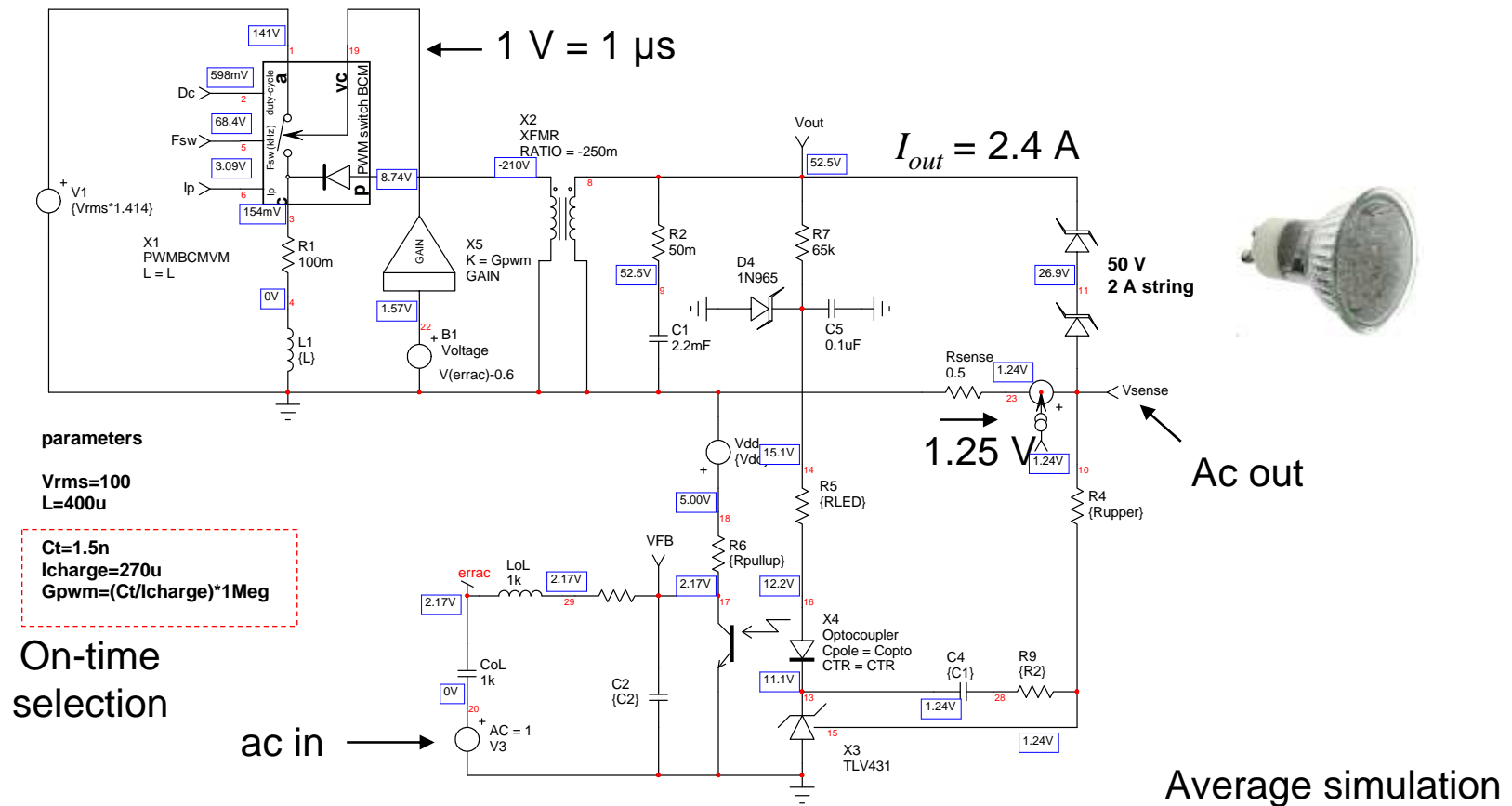
# Design Example 1 – a Single-Stage PFC

- ❑ The single-stage PFC is often used in LED applications
- ❑ It combines isolation, current-regulation and power factor correction
- ❑ Here, a constant on-time BCM controller, the **NCL30000**, is used




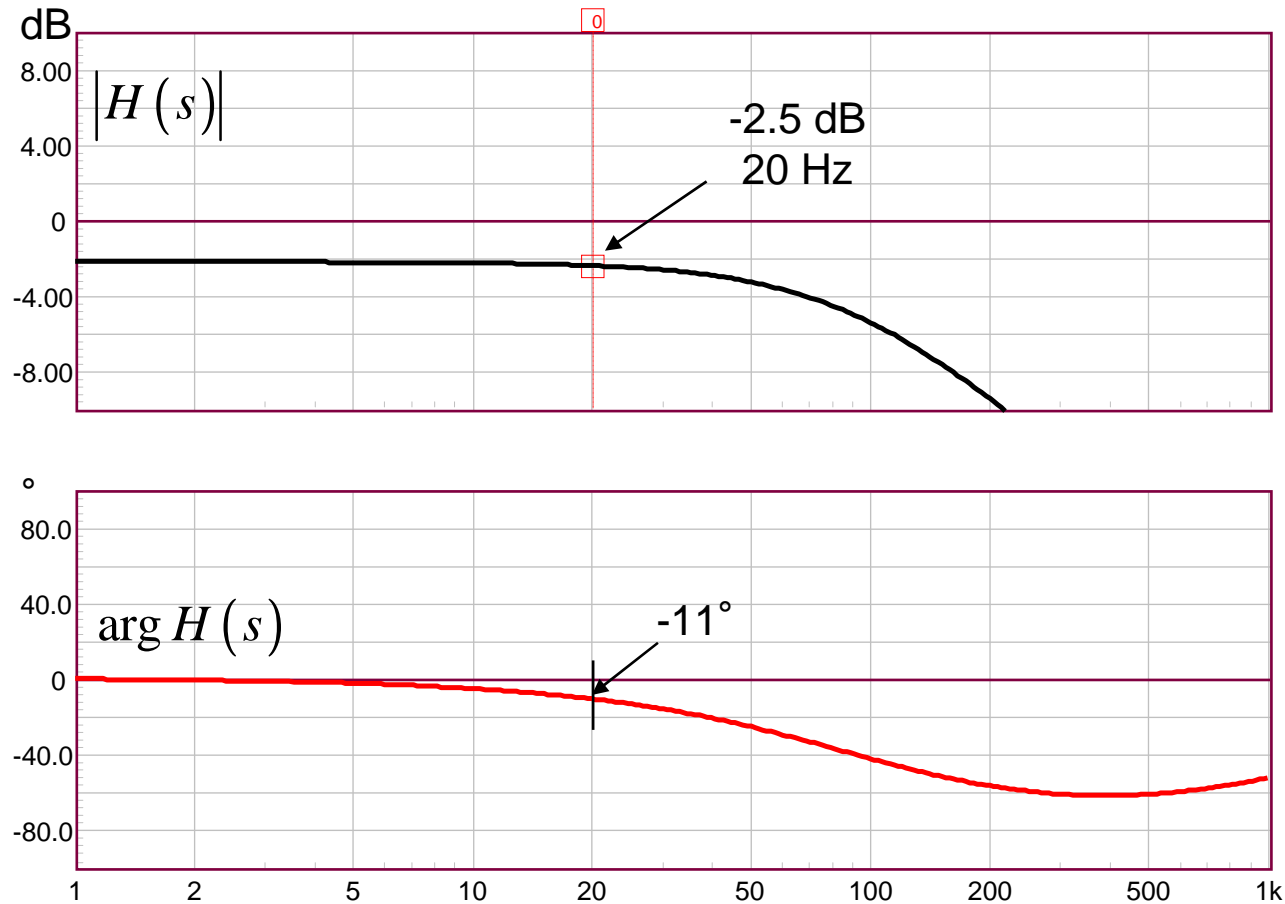
# Design Example 1 – a Single-Stage PFC

- Once the converter elements are known, ac-sweep the circuit
- Select a crossover low enough to reject the ripple, e.g. 20 Hz



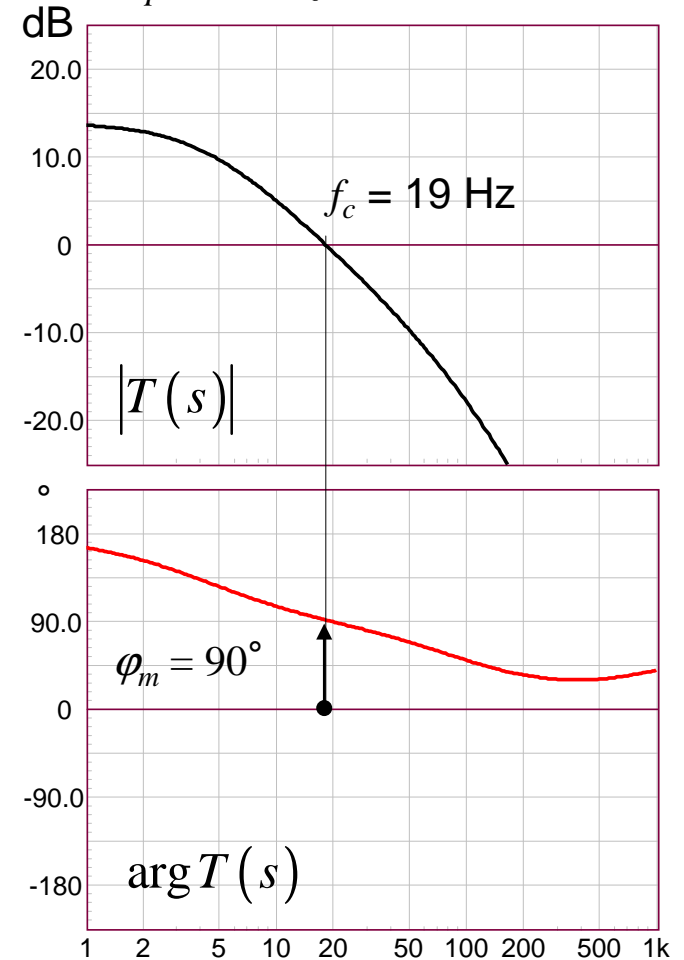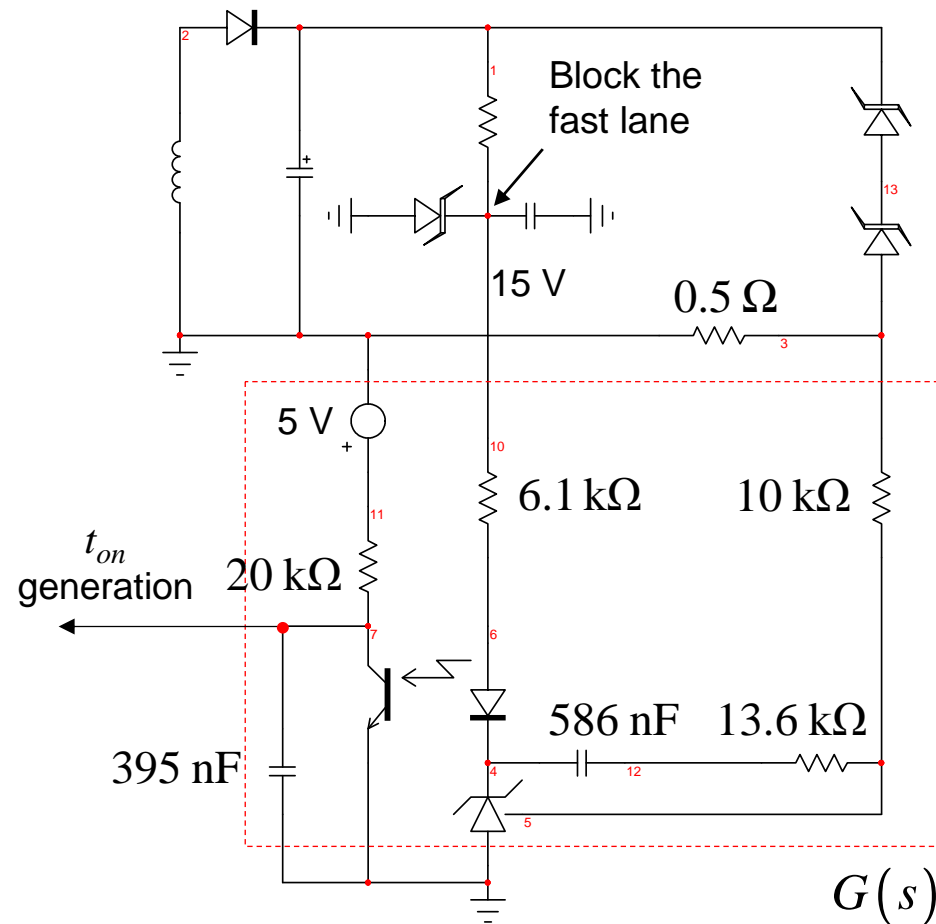
# Design Example 1 – a Single-Stage PFC

- Given the low phase lag, a type 1 can be chosen
- Use the type 2 with fast lane removal where  $f_p$  and  $f_z$  are coincident


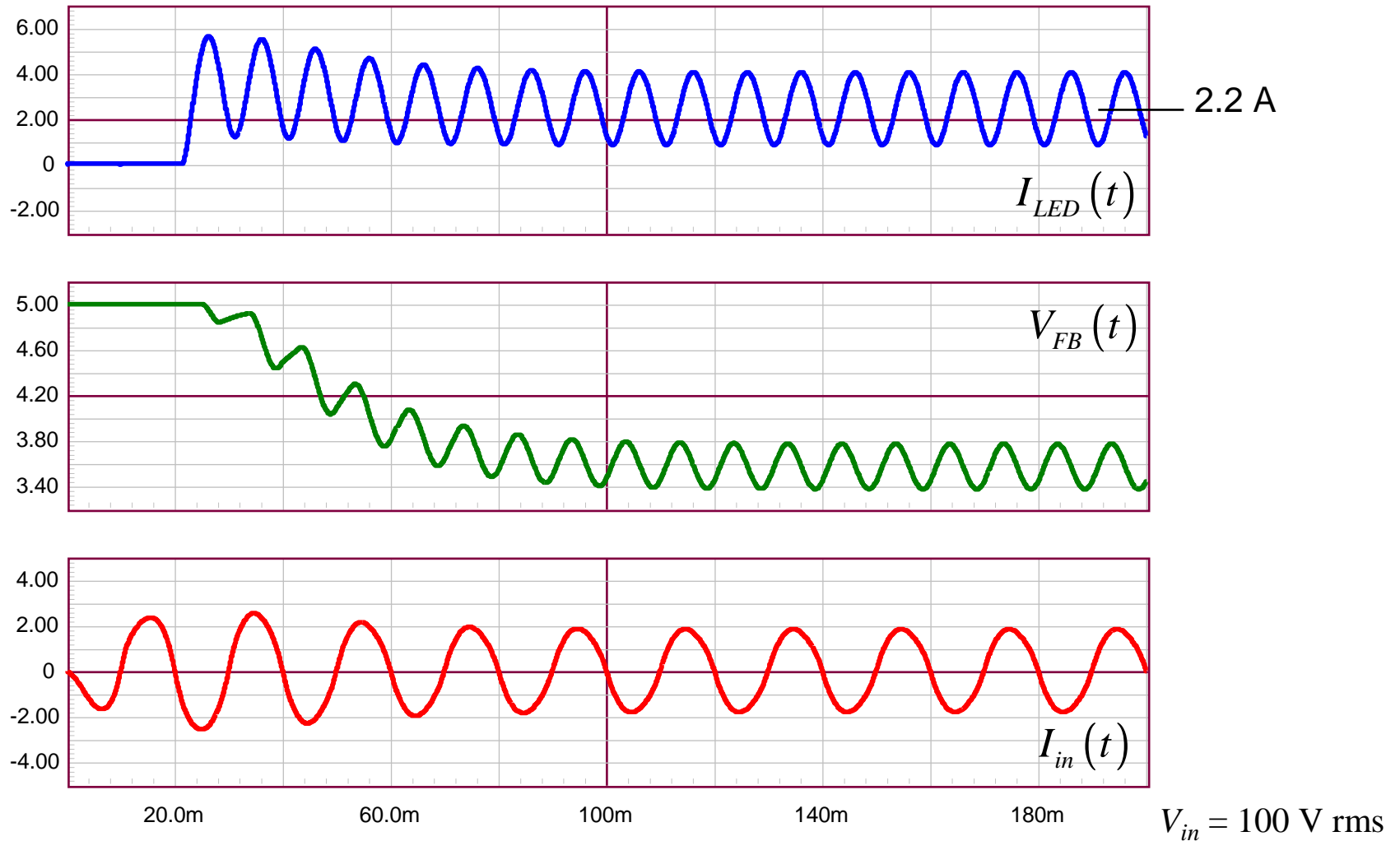
# Design Example 1 – a Single-Stage PFC

- A transient simulation helps to test the system stability




## Design Example 2 – a DCM Flyback Converter

- ❑ We want to stabilize a 20-W DCM adapter
  - ❑  $V_{in} = 85$  to  $265$  V rms,  $V_{out} = 12$  V/1.7 A
  - ❑  $F_{sw} = 65$  kHz,  $R_{pullup} = 20$  k $\Omega$
  - ❑ Optocoupler is SFH-615A, pole is at 6 kHz
  - ❑ Crossover target is 1 kHz
  - ❑ Selected controller: NCP1216
1. Obtain a power stage open-loop Bode plot,  $H(s)$
  2. Look for gain and phase values at crossover
  3. Compensate gain and build phase at crossover,  $G(s)$
  4. Run a loop gain analysis to check for margins,  $T(s)$
  5. Test transient responses in various conditions


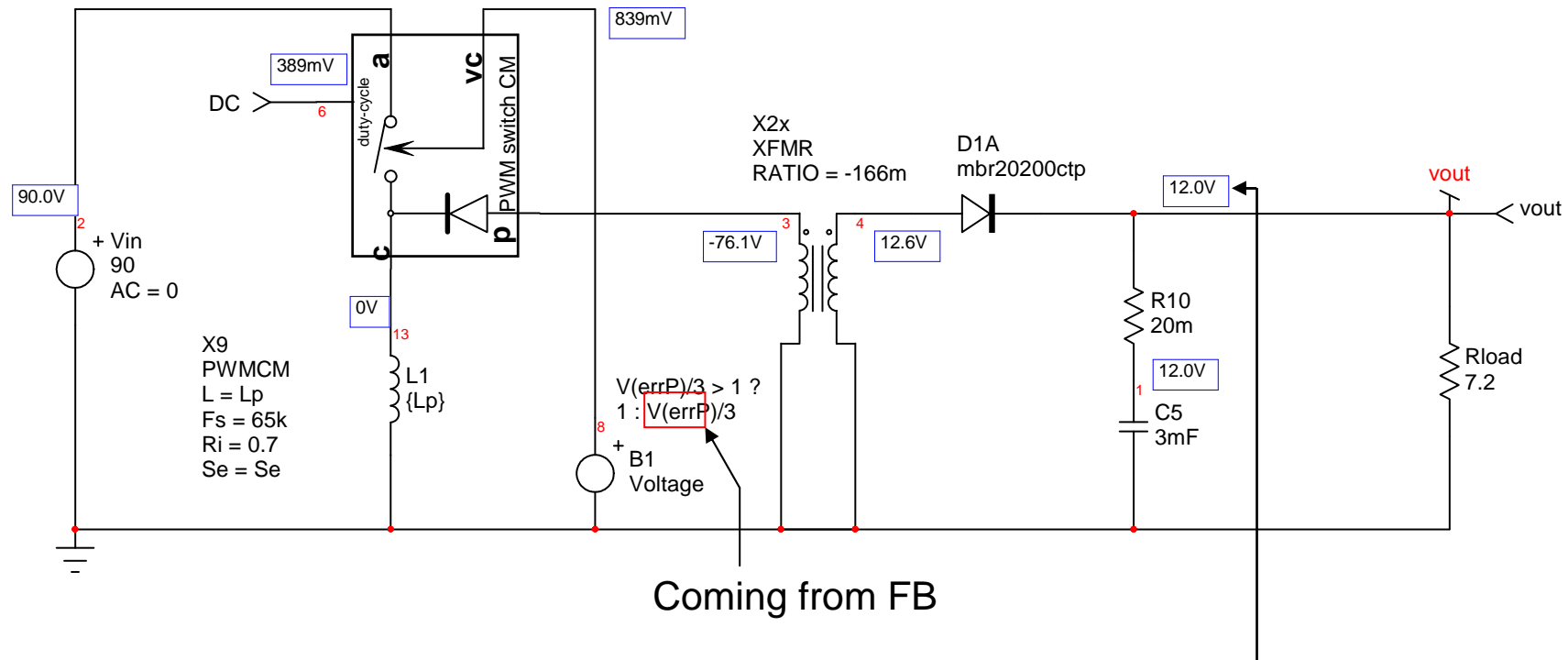
# Design Example 2 – a DCM Flyback Converter


- Capture a SPICE schematic with an averaged model



- Look for the bias points values:  $V_{out} = 12\text{ V}$ , ok
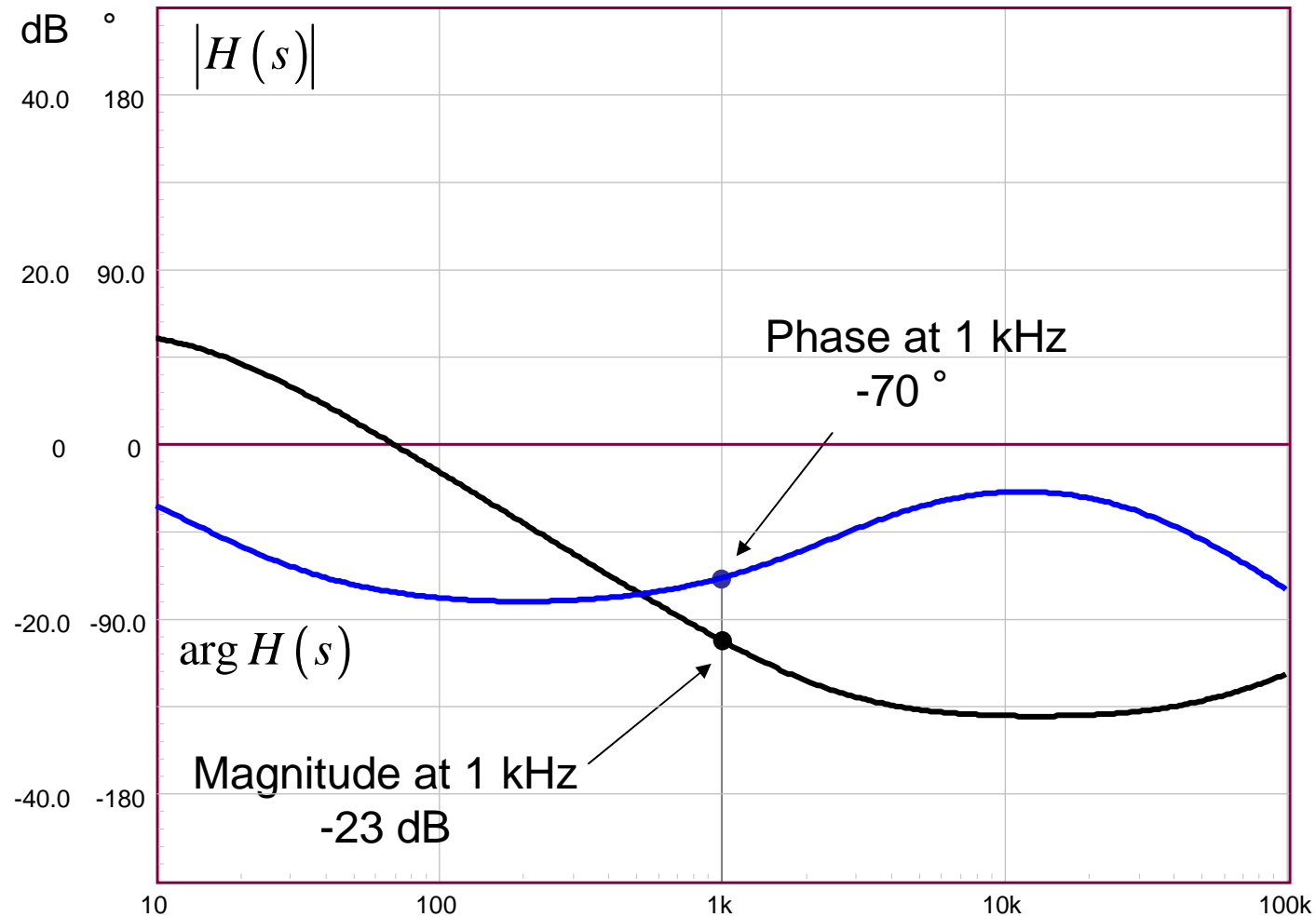
# Design Example 2: a DCM Flyback Converter


- Observe the open-loop Bode plot and select  $f_c$ : 1 kHz





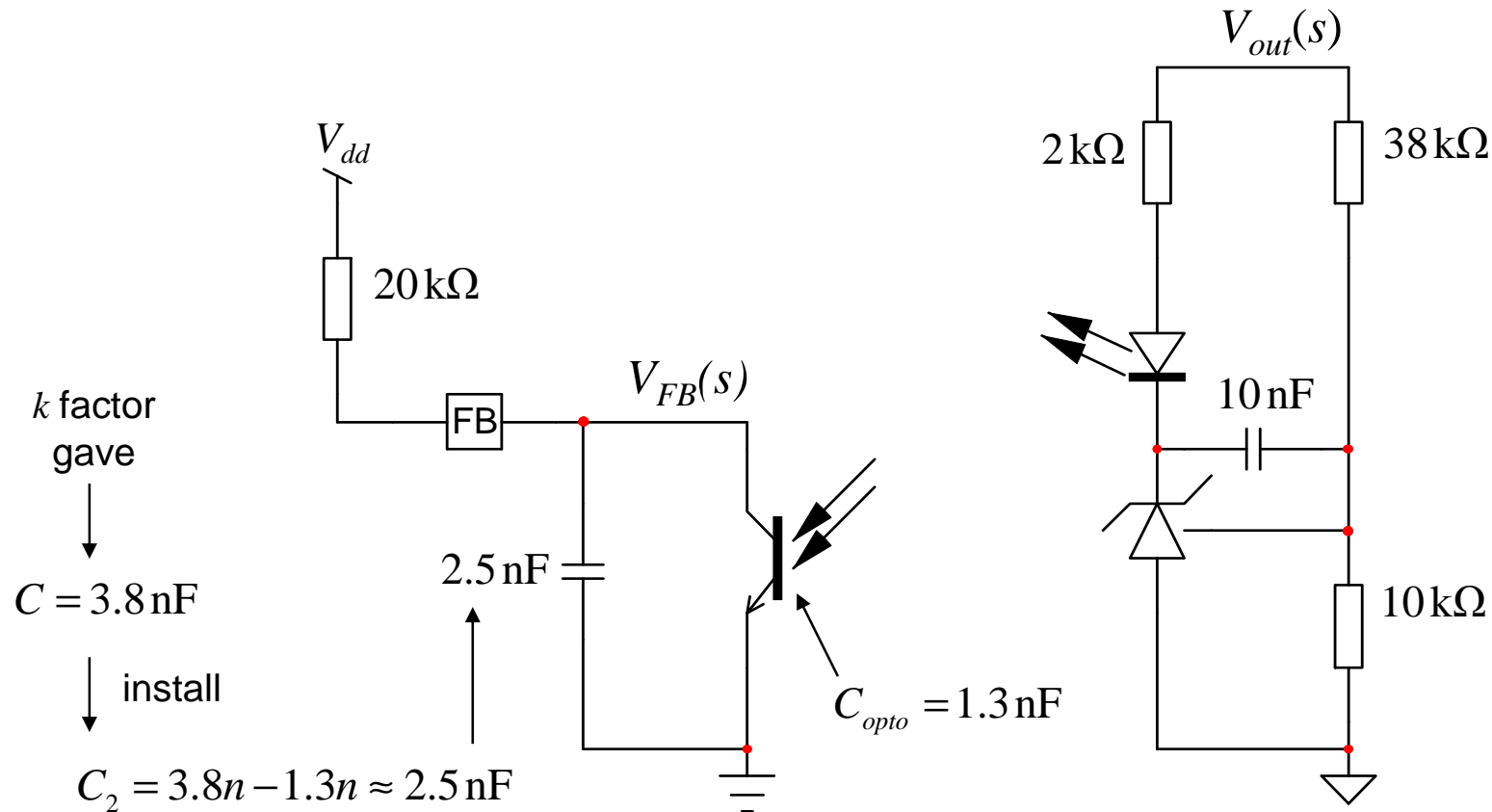
# Design example 2: a DCM flyback converter

- Apply  $k$  factor or other method, get  $f_z$  and  $f_p$
- $f_z = 3.5 \text{ kHz}$   $f_p = 4.5 \text{ kHz}$



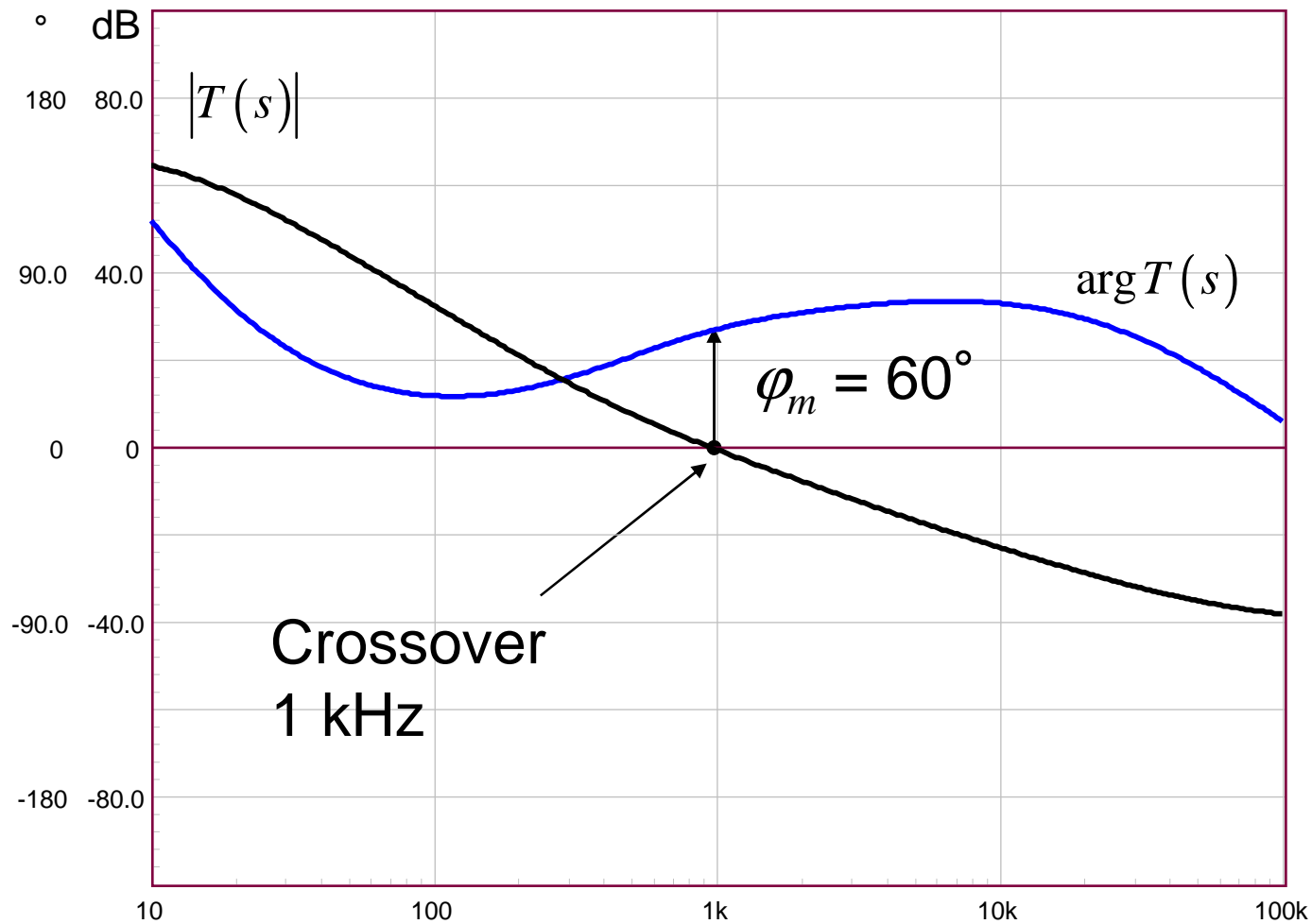
# Design example 2: a DCM Flyback Converter

- Check loop gain and watch phase margin at  $f_c$




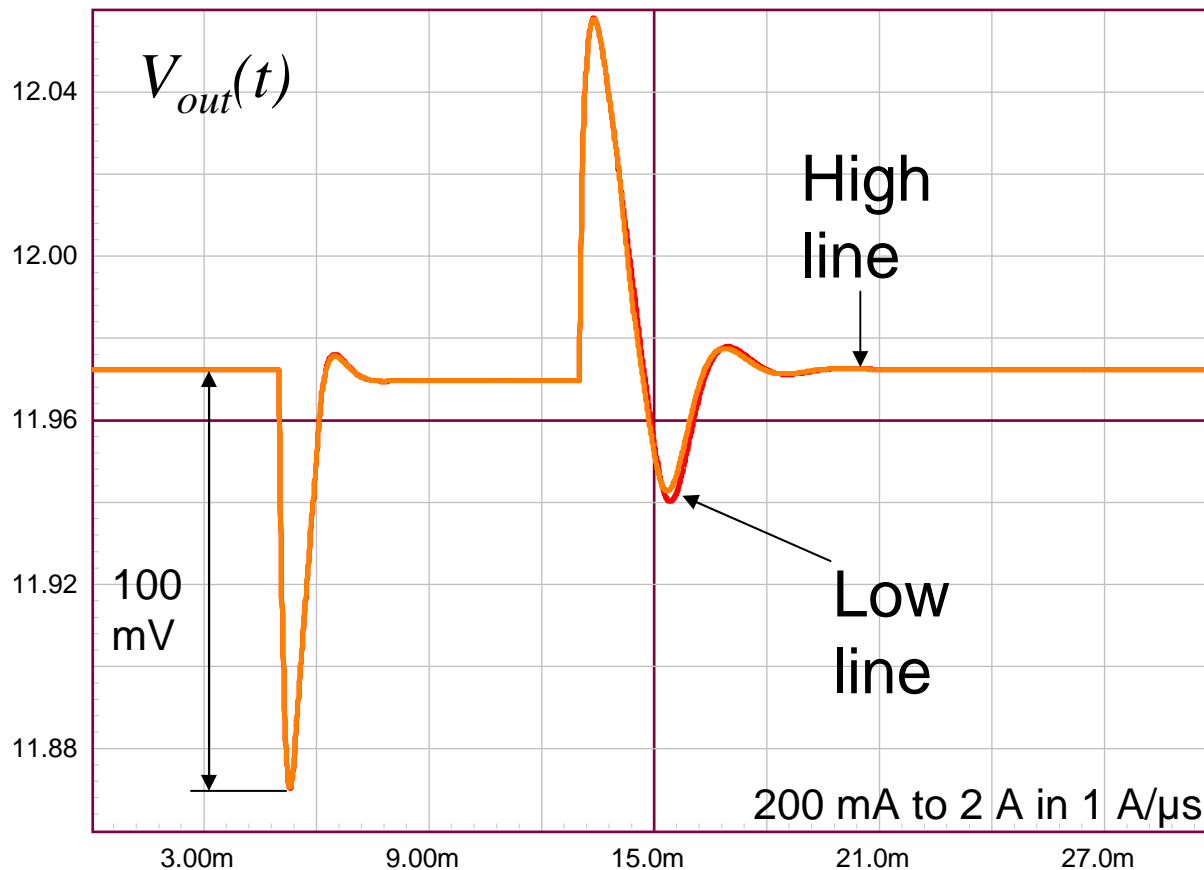
# Design Example 2: a DCM Flyback Converter

- Sweep ESR values and check margins again


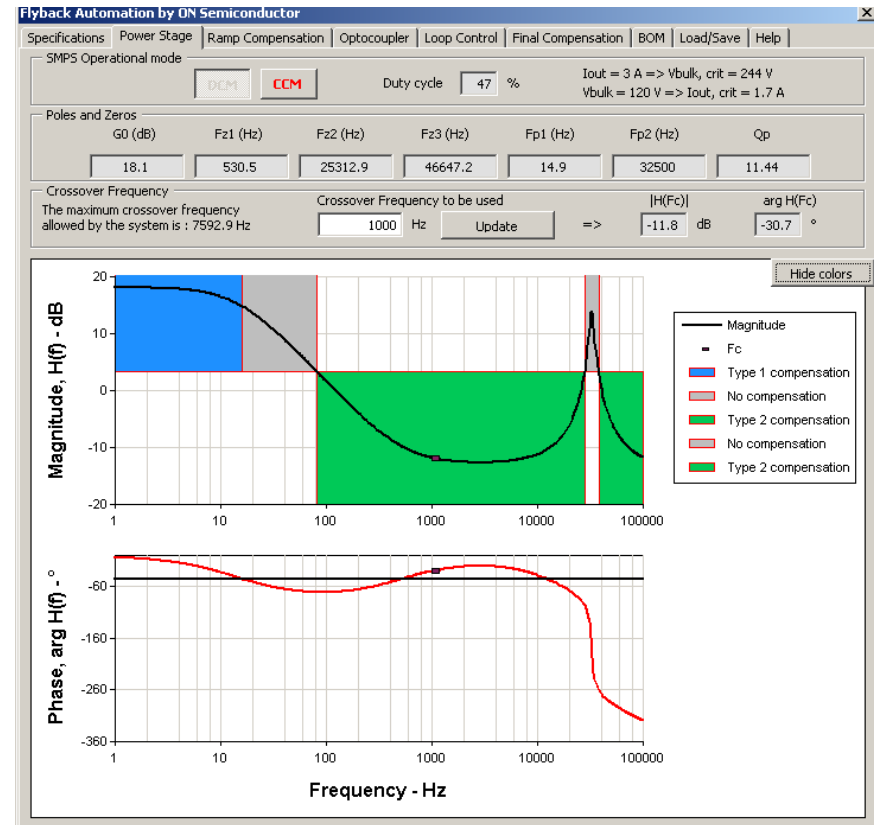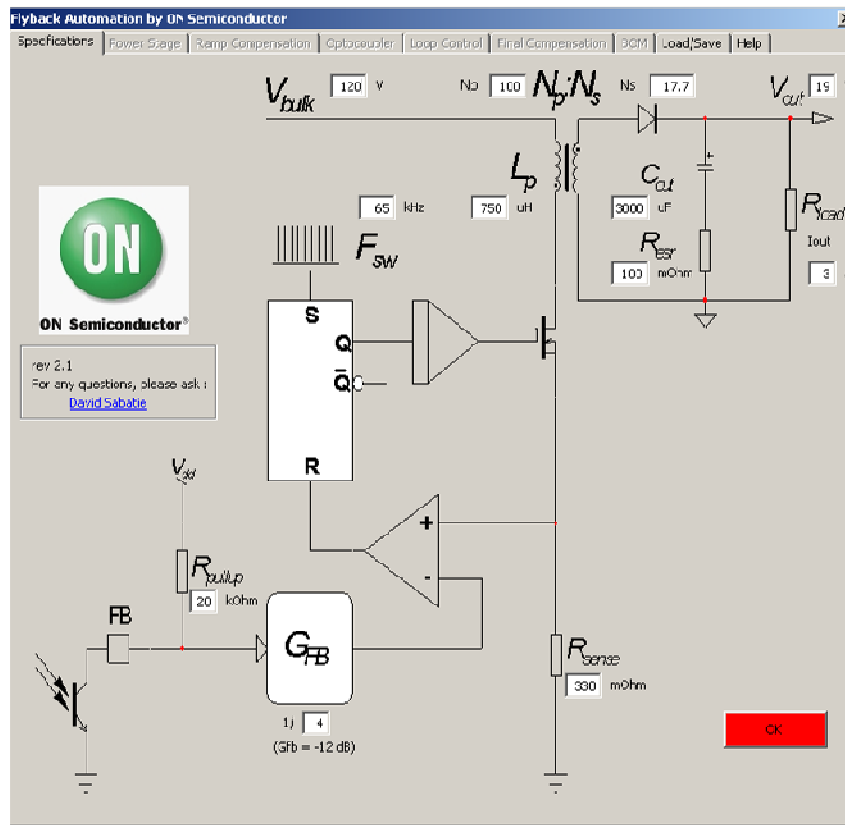
# No Time to Compute? Check EXCEL!

- ❑ An automated spreadsheet does the calculations for you
- ❑ Download a version from [www.onsemi.com](http://www.onsemi.com)



# Conclusion

- ❑ The flyback converter hides several parasitic elements
- ❑ Understanding where they hide and how they move is key!
- ❑ Despite CM presence, QR designs gain in popularity
- ❑ CM fixed-frequency is a 3<sup>rd</sup>-order type whereas QR is 1<sup>st</sup> order
- ❑ TL431 lends itself well for compensation, watch the optocoupler!
- ❑ SPICE eases and speed-up the design
- ❑ Always check theoretical assumptions with bench measurement



Merci !  
Thank you!  
Xiè-xie!

