

Evaluate power level based on User's Guide

$$V_{cst_max} := 0.825V$$

$$R_{17} := 1\text{ohm}$$

$$R_{18} := 0.18\text{ohm}$$

$$R_{cs} := \frac{R_{17} \cdot R_{18}}{R_{17} + R_{18}}$$

$$R_{cs} = 0.153\ \Omega \quad \text{Current Sense Resistance}$$

$$I_{pk} := \frac{V_{cst_max}}{R_{cs}} = 5.408\text{ A}$$

$$N_{ps} := 5.5 \quad \text{Transformer turns ratio used in the UCC28780 65W reference design}$$

Transformer should be set based on volt second balance. The following is an estimate of how the transformer turns ratio could be set.

$$V_{inmin} := 72V \quad V_{out} := 20V$$

$$V_{rdson} := 0.20V \quad \text{Estimate of synchronous rectifier } R_{dson} \text{ voltage drop on secondary and primary FET.}$$

$$N_{ps} = \frac{(V_{inmin} - V_{rdson}) \cdot D_{max}}{(V_{out} + V_{rdson})(1 - D_{max})}$$

D_{max} can be calculated based on N_{ps} and estimates for

$$D_{max} := \frac{N_{ps} \cdot V_{out} + N_{ps} \cdot V_{rdson}}{V_{inmin} - V_{rdson} + N_{ps} \cdot V_{out} + N_{ps} \cdot V_{rdson}} = 0.607$$

Based on conservation of energy, N_{ps} and D_{max} the maximum output power during PCL can be calculated. For this design I estimated that it can deliver 116.7 W for 160 ms.

$$\frac{V_{in}}{V_{out}} = N_{ps} = \frac{I_{out}}{I_{in}}$$

$$I_{in} := \frac{I_{pk} \cdot D_{max}}{2}$$

$$I_{out} := \frac{I_{pk} \cdot N_{ps} \cdot (1 - D_{max})}{2} = 5.839\text{ A}$$

$$P_{out_max} := I_{out} \cdot V_{out} = 116.772\text{ W}$$

Calculate OPP trip point at 72 V input to the flyback converter


First you need to calculate the IVSL current at 72 V input.

$N_{pa} := 4.4$ The primary to aux turns ratio.

$R_{vs1} := 69.8 \cdot 10^3 \text{ ohm}$

$$I_{vsl_72V} := \frac{V_{inmin}}{N_{ps} \cdot R_{vs1}} = 1.875 \times 10^{-4} \text{ A}$$

 This design uses a Ropp of zero ohms, so figure 5 from the data sheet can be used calculate the VCST(OPP) trip point at the CS pin base on IVSL. At a IVSL = 187.5 uA the CS trip point for VCST(OPP) is 600 mV.



Based on a Vcst(opp) of 0.6V the OPP trip point will be roughly 85W.

$V_{cst_opp} := 0.6V$

$$P_{opp} := \frac{V_{cst_opp} \cdot N_{ps} \cdot (1 - D_{max}) \cdot V_{out}}{R_{cs} \cdot 2} = 84.925 \text{ W}$$

So what this means is if the converter is delivering more 85W for a 160 ms or more the converter will initiate a VDD UVLO restart (VDD(off) to VDD(on)). Please refer to the following figure for details.

 


Figure 35. Timing Diagram of OPP

Please note that $V_{CST(OPP)}$ changes with IVLS current and is a delayed over power protection. In this design and may vary with line depending R_{vs1} and N_{pa} . $V_{opp1} = 600\text{ mV}$ and $V_{opp4} = 425\text{mV}$ in regards to figure 34.

Figure 34 comes from the data sheet and shows the OPP, PCL and OCP trip points.

- 1.) The first trip point $V_{cst(opp)}$ needs to see the peak current limit consecutively triggered for 160 ms before shutting down.
- 2.) The PCL is a cycle by cycle peak current limit that can be delivered for 160 ms this is more power than OPP.
- 3.) The OCP will only be seen in the case of transformer saturation or output short circuit. This will be seen when the CS voltage is above V_{OCP} (1.2V).

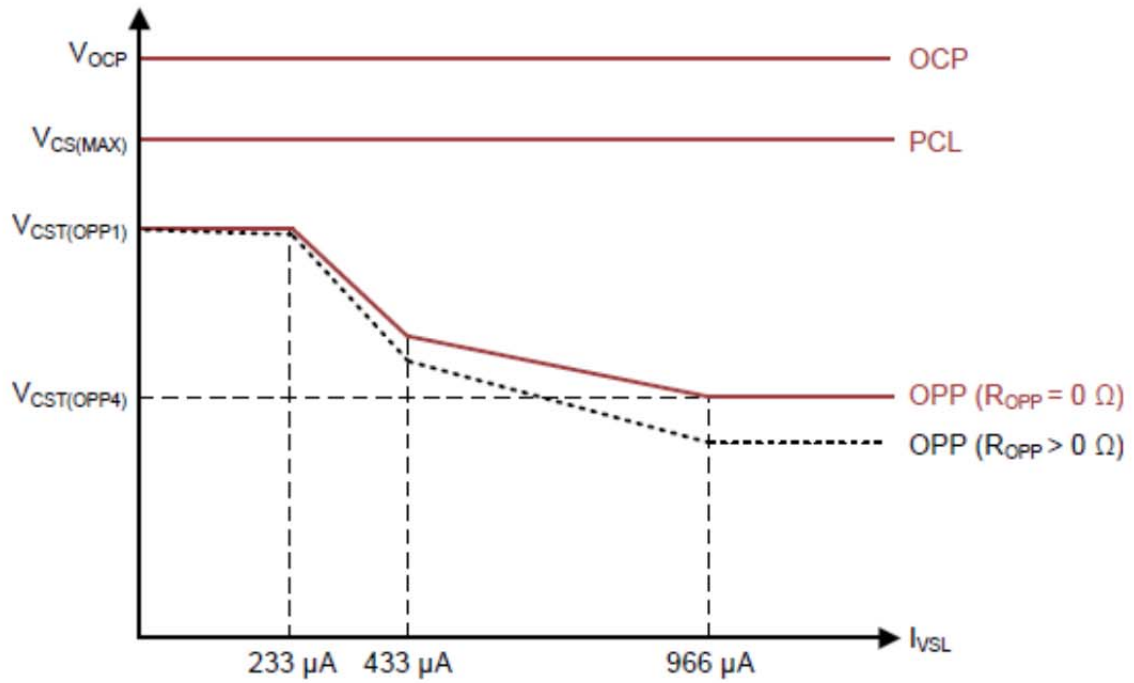


Figure 34. CS-Pin Related Faults

PARAMETER		TEST CONDITION	MIN	TYP	MAX	UNIT
PROTECTION						
V_{OVP}	Over-voltage threshold	V_{VS} increasing	4.4	4.5	4.6	V
V_{OCP}	Over-current threshold	V_{CS} increasing	0.97	1.2	1.35	

Regards,

Mike