



[Maxim](#) > [Design Support](#) > [Technical Documents](#) > [Application Notes](#) > [Battery Management](#) > APP 123

Keywords: Li+, li-ion, li-polymer, battery monitor, DS2438, battery pack, Li+ safety, ESD protection, lithium ion

APPLICATION NOTE 123

Recommended ESD Protection and Circuit Placement for the DS2438 in Li-Ion Cell Pack Master

May 07, 2001

Abstract: This application note presents to the reader a recommended Li-Ion/polymer battery pack circuit reference design using the Dallas Semiconductor DS2438 battery monitor. Special emphasis is placed on placement of the DS2438 in the battery pack with respect to the battery cell and the Li-Ion protection circuitry. It is explained why this must be addressed to assure proper and safe operation of the battery pack. Additionally, considerations and component selection for ESD protection are addressed and described in detail.

Overview

This application note addresses the implementation of a DS2438-based Lithium-Ion battery pack with low-side n-channel safety FETs. A reference design is presented that focuses on Li+ cell safety and ESD-hardness. ESD protection components are recommended for applications where the DS2438 is connected directly across a cell and where protection FETs are present in the circuit and it is possible for device ground to be floating. Considerations on how the protection circuitry will affect the operation range and A/D accuracy of the DS2438 are also presented.

Li+ Safety Considerations

Safety will be considered first. Dallas recommends that no circuit should exist on the Li+ cell side of the safety FETs. Such a connection could compromise overall safety of the battery pack by potentially bypassing the safety FETs. An example of such a case is illustrated in **Figure 1**.

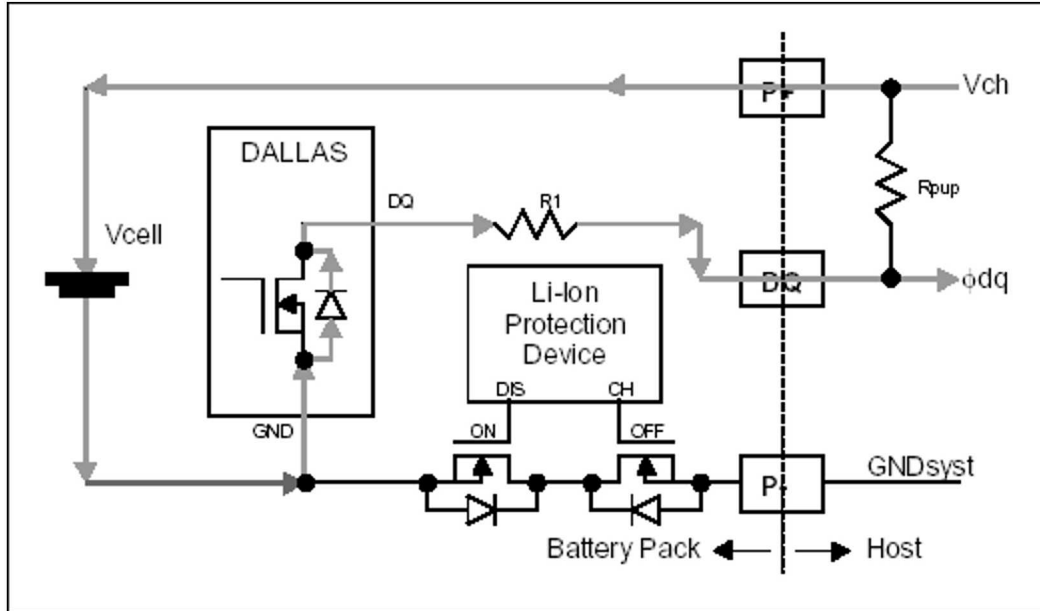


Figure 1. Potential charging path that bypasses safety FETs if Dallas chip is on the cell side.

The drain-to-body diode of the n-channel open-drain DQ output driver of the DS2438 could provide a charging path (highlighted in Figure 1) through the device that will bypass the protection FETs. This conduction path will exist only if the potential difference between V_{CH} and Φ_{DQ} is more than a diode drop greater than the sum of V_{CELL} and the voltage drop across R1. While such a condition is unlikely, it does illustrate a possible way to bypass the safety circuit if the DS2438 is connected on the cell side of the safety FETs. Dallas thus recommends connecting the DS2438 on the terminal side of the safety FETs, unless otherwise recommended by the Li+ cell manufacturer.

Dallas Reference Design

Figure 2 below illustrates the recommended implementation of the DS2438 with respect to the low-side n-channel safety FETs. Additionally, Dallas recommends passive devices that primarily serve to protect the DS2438 from ESD damage. The protection offered by each device is described below:

 


Figure 2. Recommended schematic for single-cell Li+ pack with low-side n-channel protection FETs.

1. The capacitor C1 on V_{CC} is simply a high-frequency bypass cap. 0.1 μF is recommended.
2. The Zener diode D1 on V_{CC} serves two purposes. It clamps at the Zener voltage so that ESD and switching transients cannot damage the Dallas chip through V_{CC} . In the forward bias region, it clamps around 0.7 volts, thereby disallowing V_{CC} from falling more than 0.7 volts below GND, which is possible when both the CHarge and DIScharge FETs are high impedance. Choose a Zener voltage that is larger than the maximum cell(s) voltage for the application, but lower than the 10.0 volts rating of the DS2438. A Zener value between 5.1 volts and 10.0 volts would be ideal for the circuit in Figure 2.
3. The resistor R1 in series with V_{CC} limits current through the device and the protection Zener D1. A minimum R1 value of 510 Ω is recommended to protect during conditions when ground is floating (CHarge and DIScharge disabled). If the circuit does not have charge protection and GND will never be in a floating state, an R1 value of at least 330 Ω is recommended. Since the maximum active current of the DS2438 is 100 μA , this represents a 50 mV drop worst case.
4. The Zener diode D2 performs the same function for DQ as D1 does for V_{CC} . Choose a Zener value larger than the communication logic high level for the application, but lower than the 5.5 volts maximum rating for DQ. If the application does not allow for a floating ground condition, this component is not required.
5. The resistor R2 in series with DQ limits current through the large ESD protection diode internally connected between DQ and GND and through the external protection diode D2. An R2 value of at least 330 Ω is recommended (100 Ω if ground will never be floating), but consider the size of the pullup on DQ (which is generally installed in the host system) and the I/O specs of DQ and the host processor before setting this value.
6. The resistor R3 in series with VAD limits current through another possible ESD path from V_{CC} . A value of at least 510 Ω for R3 is recommended. Please take into consideration the possible voltage drop and resulting A/D inaccuracy when selecting an R3 value.

In summary, this application note considered an application of the DS2438 in a Lithium-Ion based cell pack with the common implementation of low side n-channel safety FETs. Dallas recommends that the DS2438 be connected on the terminal side of the safety FETs so that no potential charging paths exist that bypass the FETs. A reference design is recommended, including passive components that increase the ESD-hardness of the battery pack to meet the requirements of the IEC1000-4-2 model ($\pm 8\text{kV}$ direct contact, $\pm 15\text{kV}$ air).

Related Parts

[DS2438](#) Smart Battery Monitor

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 123: <http://www.maximintegrated.com/an123>

APPLICATION NOTE 123, AN123, AN 123, APP123, Appnote123, Appnote 123

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>