

Proposed Worst-case IC Power Dissipation Calculation

$$\mathbf{IC_Pd = P_{COND_Mos} + P_{SW} + P_{GD} + P_{IQ}}$$

*Take the value in
Webench simulation result*

$$P_{HIGH_COND} + P_{LOW_COND}$$

*can be considered as
constant in the entire
temperature range*

$$V_{IN} * I_Q$$

Mosfet Conduction losses

- High-side FET conduction loss

$$P_{HS_{cond}} = RDS_{onHS} * (I_o^2) * D * \left(1 + \frac{1}{12} \left(\frac{L_{Ipp}}{I_o}\right)^2\right)$$

- Low-side FET conduction loss

$$P_{LS_{cond}} = RDS_{onLS} * (I_o^2) * (1 - D) * \left(1 + \frac{1}{12} \left(\frac{L_{Ipp}}{I_o}\right)^2\right)$$

$P_{HS_{cond}}$: high-side FET conduction loss

$P_{LS_{cond}}$: low-side FET conduction loss

* R_{DSonHS} : high-side FET on-state resistance

* R_{DSonLS} : low-side FET on-state resistance

I_o : output current

D : duty cycle (V_{out} / V_{in})

L_{Ipp} : inductor peak-peak ripple current

- *for worst case analysis, use the max on-state resistance indicated in the datasheet*
- *take the calculated duty cycle and inductor peak-peak current ripple in Webench simulation result*

reference: <https://www.ti.com/lit/an/slvaeq9/slvaeq9.pdf?ts=1665007621996>

Calculate $P_{SW} + P_{GD}$

- Application condition

- $V_{in} = 3.3V$
- $V_{out} = 1.8V$
- $I_{out} = 1.0A$

$$P_{HS_{cond}} = RDS_{onHS} * (I_o^2) * D * \left(1 + \frac{1}{12} \left(\frac{L_{Ipp}}{I_o} \right)^2 \right)$$

$$P_{LS_{cond}} = RDS_{onLS} * (I_o^2) * (1 - D) * \left(1 + \frac{1}{12} \left(\frac{L_{Ipp}}{I_o} \right)^2 \right)$$

- Calculate for $P_{SW} + P_{GD}$ at $T_{amb} = 30 \text{ }^\circ\text{C}$

- $IC_{Pd} = \underline{148.39 \text{ mW}}$ (from Webench)
- $P_{HS_{cond}} = 37\text{m}\Omega * (1A)^2 * (0.37) * (1 + 1/12 (1.103A)^2) = \underline{15.08\text{mW}}$
- $P_{LS_{cond}} = 15\text{m}\Omega * (1A)^2 * (1 - 0.37) * (1 + 1/12 (1.103A)^2) = \underline{10.41\text{mW}}$
- $P_{IQ} = 5.0V * 15\mu A = \underline{75\mu W}$

- $P_{SW} + P_{GD} = IC_{Pd} + (P_{HS_{cond}} + P_{LS_{cond}}) + P_{IQ} = 148.39\text{mW} - 10.41\text{mW} - 15.08\text{mW} - 75\mu W$
- $P_{SW} + P_{GD} = \underline{122.675\text{mW}}$

Worst-case calculation sample

- $P_{SW} + P_{GD} = \underline{122.675mW}$
- $P_{HS_cond} = 60m\Omega * (1A)^2 * (0.37) * (1 + 1/12 (1.103A)^2)$
 $= \underline{24.45mW}$ (wc on-state resistance)
- $P_{LS_cond} = 35m\Omega * (1A)^2 * (1 - 0.37) * (1 + 1/12 (1.103A)^2)$
 $= \underline{24.28mW}$ (wc on-state resistance)
- $P_{IQ} = 5.0V * 30mA = \underline{150\mu W}$

- $IC_Pd = P_{COND_Mos} + P_{SW} + P_{GD} + P_{IQ}$
- $IC_Pd = (24.45mW + 24.28mW) + (122.675mW) + 150\mu W$
- **$IC_Pd = 171.55mW$**

Important notice and disclaimer

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES “AS IS” AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI’s products are provided subject to [TI’s Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI’s provision of these resources does not expand or otherwise alter TI’s applicable warranties or warranty disclaimers for TI products.