

Starting from the specifications in [Table 2](#), a step-by-step design procedure and some design hints to obtain a symmetrical layout are given below.

**Table 2. Push-pull converter specifications**

Specification	Symbol	Value
Nominal input voltage	$V_{in}$	24 V
Maximum input voltage	$V_{inmax}$	28 V
Minimum input voltage	$V_{inmin}$	20 V
Nominal output power	$P_{out}$	1000 W
Nominal output voltage	$V_{out}$	350 V
Target efficiency	$\eta$	> 90%
Switching frequency	$f$	100 kHz

A switching frequency of  $f = 100$  kHz was chosen to minimize passive components size and weight, then the following step-by-step calculation was done:

- Switching period:

**Equation 2**

$$T = \frac{1}{f} = \frac{1}{10^5} = 10 \mu s$$

- Maximum duty cycle

The theoretical maximum on time for each phase of the push-pull converter is:

**Equation 3**

$$t_{on}^* = 0.5T = 5 \mu s$$

Since deadtime has to be provided in order to avoid simultaneous device conduction, it is better to choose the maximum duty cycle of each phase as:

**Equation 4**

$$D_{max} = 0.9 \frac{t_{on}^*}{T} = 0.45$$

This means a total deadtime of  $1 \mu s$  at maximum duty cycle, occurring for minimum input voltage operation.

- Input power

Assuming 90% efficiency the input power is:

**Equation 5**

$$P_{in} = \frac{P_{out}}{0.9} = 1111 W$$

- Maximum average input current:

**Equation 6**

$$I_{in} = \frac{P_{in}}{V_{inmin}} = \frac{1111}{20} = 55.55 \text{ A}$$

- Maximum equivalent flat topped input current:

**Equation 7**

$$I_{pft} = \frac{I_{in}}{2D_{max}} = \frac{55.55}{0.9} = 61.72 \text{ A}$$

- Maximum input RMS current:

**Equation 8**

$$I_{inRMS} = I_{pft} \sqrt{2D_{max}} = 58.55 \text{ A}$$

- Maximum MOSFET RMS current:

**Equation 9**

$$I_{MosRMS} = I_{pft} \sqrt{D_{max}} = 41.4 \text{ A}$$

- Minimum MOSFET breakdown voltage:

**Equation 10**

$$V_{BrkMos} = 1.3 \cdot 2 \cdot V_{inMax} = 72.8 \text{ V}$$

- Transformer turns ratio:

**Equation 11**

$$N = \frac{N_2}{N_1} = \frac{V_{out}}{2V_{inmin} D_{max}} = 19$$

- Minimum duty cycle value:

**Equation 12**

$$D_{min} = \frac{V_{out}}{2NV_{inmax}} = 0.32$$

- Duty cycle at nominal input voltage:

**Equation 13**

$$D_{min} = \frac{V_{out}}{2NV_{in}} = 0.38$$

- Maximum average output current:

**Equation 14**

$$I_{out} = \frac{P_{out}}{V_{out}} = 2.86 \text{ A}$$

- Secondary maximum RMS current

Assuming that the secondary top flat current value is equal to the average output value the rms secondary current is:

#### Equation 15

$$I_{\text{secRMS}} = I_{\text{out}} \sqrt{D_{\text{max}}} = 1.91 \text{ A}$$

- Rectifier diode voltage:

#### Equation 16

$$V_{\text{diode}} = N V_{\text{inMax}} = 532 \text{ V}$$

- Output filter inductor value:

#### Equation 17

$$L_{\text{min}} \geq \left( \frac{N_2}{N_1} V_{\text{in}} - V_{\text{out}} \right) \frac{t_{\text{onMax}}}{\Delta I}$$

Assuming a ripple current value  $\Delta I = 15\% I_{\text{out}} = 0.43 \text{ A}$ , the minimum value for the output filter inductance is:

#### Equation 18

$$L_{\text{min}} = 1.109 \text{ mH}$$

With this value of inductance continuous current mode (CCM) operation is guaranteed for a minimum output current of:

#### Equation 19

$$I_{\text{outMin}} = \frac{\Delta I}{2} = 0.215 \text{ A}$$

which means a minimum load of 75 W is required for CCM operation. The chosen value for this design is  $L = 1.5 \text{ mH}$ .

- Output filter capacitor value:

#### Equation 20

$$C = \frac{1}{8} \frac{\Delta I_L}{\Delta V_0} T_s$$

Considering a maximum output ripple value equal to:

#### Equation 21

$$\Delta V_0 = 0.1\% V_{\text{out}} = 0.35 \text{ V}$$

the minimum value of capacitance is:

**Equation 22**

$$C_{\min} = 1.53 \mu\text{F}$$

and the equivalent series resistance (ESR) has to be lower than:

**Equation 23**

$$\text{ESR}_{\max} = \frac{\Delta V_0}{\Delta I_L} = 0.81 \Omega$$

- Input capacitor:

**Equation 24**

$$C_{\text{in}} = I_{\text{C}_{\text{rms}}} \frac{\Delta T_{\text{onMax}}}{\Delta V_{\text{in}}}$$

where  $I_{\text{C}_{\text{rms}}}$  is the RMS capacitor current value given by:

**Equation 25**

$$I_{\text{C}_{\text{rms}}} = \sqrt{I_{\text{inRms}}^2 - I_{\text{in}}^2} = 19\text{A}$$

and

**Equation 26**

$$\Delta V_{\text{in}} = 0.1\% V_{\text{inMax}} = 0.028\text{V}$$

then

**Equation 27**

$$C_{\text{in}} = I_{\text{C}_{\text{rms}}} \frac{\Delta T_{\text{onMax}}}{\Delta V_{\text{in}}} = 3053 \mu\text{F}$$