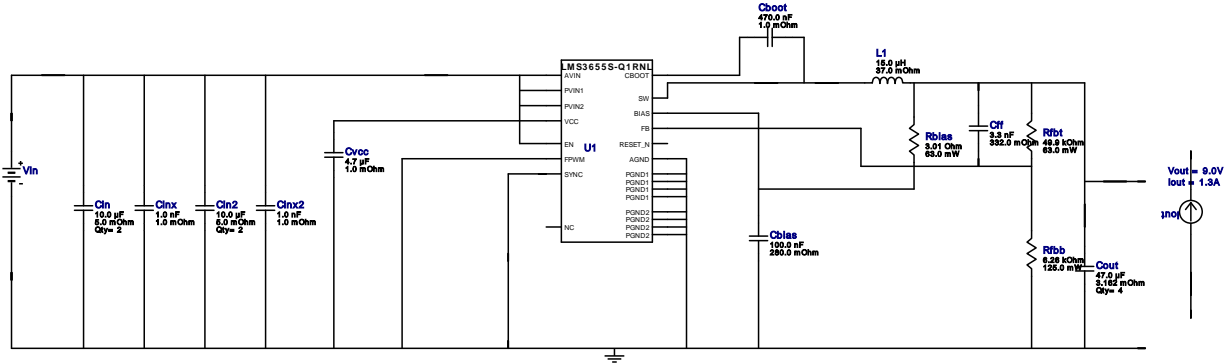


VinMin = 20.0V
 VinMax = 30.0V
 Vout = 9.0V
 Iout = 1.3A

Device = LMS3655SQRNLRQ1
 Topology = Buck
 Created = 2023-02-27 03:03:20.802
 BOM Cost = \$6.73
 BOM Count = 19
 Total Pd = 0.5W

WEBENCH® Design Report

Design : 26 LMS3655SQRNLRQ1
 LMS3655SQRNLRQ1 20V-30V to 9.00V @ 1.3A



1. The input capacitor included in the BOM only contains a small filter capacitor that should be placed near the IC. Depending on where the power supply is laid out in the system additional bulk capacitance may need to be added to filter the line ripple.
2. If there is no VinTyp specified, WEBENCH will use the VinMax value. To change the VinTyp value, click on the "Change Design Inputs" button under the Optimization Tuning knob. In some applications, while the design requires the input voltage to be a wide range, for a majority of the time, it is operating at a much lower voltage than the maximum input voltage. Sizing the inductor based on the maximum input voltage may yield an inductance much larger than typically needed, causing a larger footprint for the overall design. At the same time, components such as the input capacitor must be rated based on the maximum input voltage. WEBENCH now supports the use of this additional input voltage specification.
3. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.

Design Alerts



Component Selection Information







The LMS3655S-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application.







Electrical BOM




Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbias	AVX	08053C104KAT2A Series= X7R	Cap= 100.0 nF ESR= 280.0 mOhm VDC= 25.0 V IRMS= 0.0 A	1	\$0.01	0805 7 mm ²
Cboot	MuRata	GRM155R60J474KE19D Series= X5R	Cap= 470.0 nF ESR= 1.0 mOhm VDC= 6.3 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
Cff	Kemet	C0805C332K5RACTU Series= X7R	Cap= 3.3 nF ESR= 332.0 mOhm VDC= 50.0 V IRMS= 319.0 mA	1	\$0.01	0805 7 mm ²
Cin	Samsung Electro-Mechanics	CL32B106KBJNNWE Series= X7R	Cap= 10.0 uF ESR= 5.0 mOhm VDC= 50.0 V IRMS= 0.0 A	2	\$0.17	1210_270 15 mm ²
Cin2	Samsung Electro-Mechanics	CL32B106KBJNNWE Series= X7R	Cap= 10.0 uF ESR= 5.0 mOhm VDC= 50.0 V IRMS= 0.0 A	2	\$0.17	1210_270 15 mm ²

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cinx	MuRata	GRM1555C1H102JA01D Series= C0G/NP0	Cap= 1.0 nF ESR= 1.0 mOhm VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
Cinx2	MuRata	GRM1555C1H102JA01D Series= C0G/NP0	Cap= 1.0 nF ESR= 1.0 mOhm VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	0402 3 mm ²
Cout	TDK	CGA9N3X7R1C476M230KB Series= X7R	Cap= 47.0 uF ESR= 3.162 mOhm VDC= 16.0 V IRMS= 5.1344 A	4	\$0.67	2220_250 54 mm ²
Cvcc	MuRata	GRM155R61A475MEAAD Series= X5R	Cap= 4.7 uF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.02	0402_065 3 mm ²
L1	Bourns	SRU1038-150Y	L= 15.0 µH 37.0 mOhm	1	\$0.49	SRU1038 144 mm ²
Rbias	Vishay-Dale	CRCW04023R01FKED Series= CRCW..e3	Res= 3.01 Ohm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rfbb	Yageo	RT0805BRD076K26L Series= ?	Res= 6.26 kOhm Power= 125.0 mW Tolerance= 0.1%	1	\$0.06	0805 7 mm ²
Rfbt	Vishay-Dale	CRCW040249K9FKED Series= CRCW..e3	Res= 49.9 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
U1	Texas Instruments	LMS3655SQRNLRQ1	Switcher	1	\$2.73	RNL0022A 42 mm ²

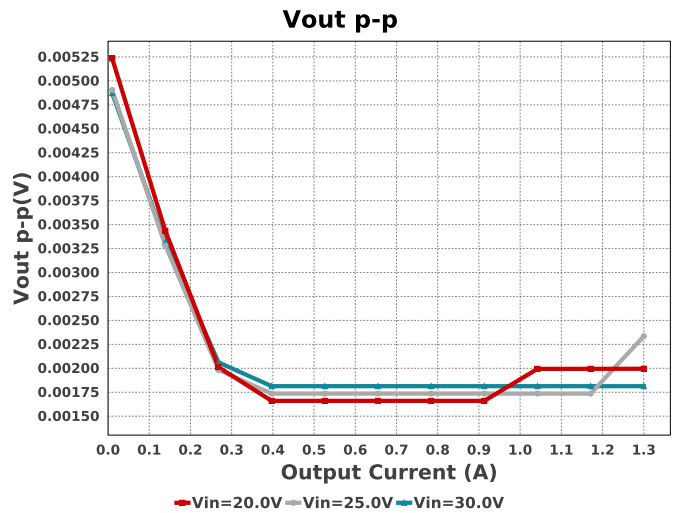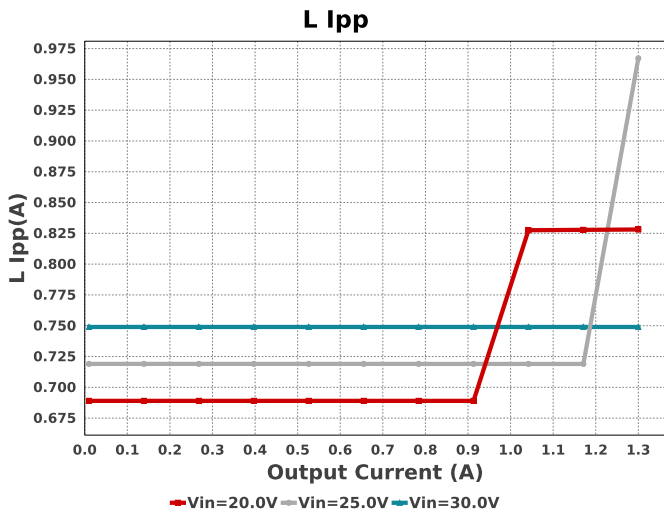

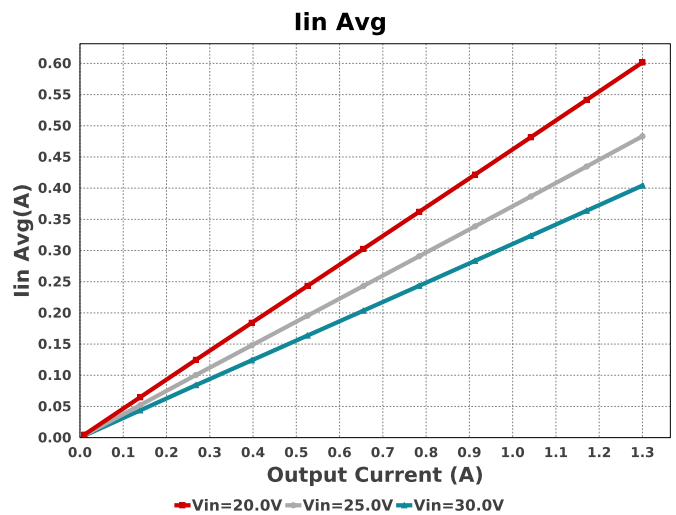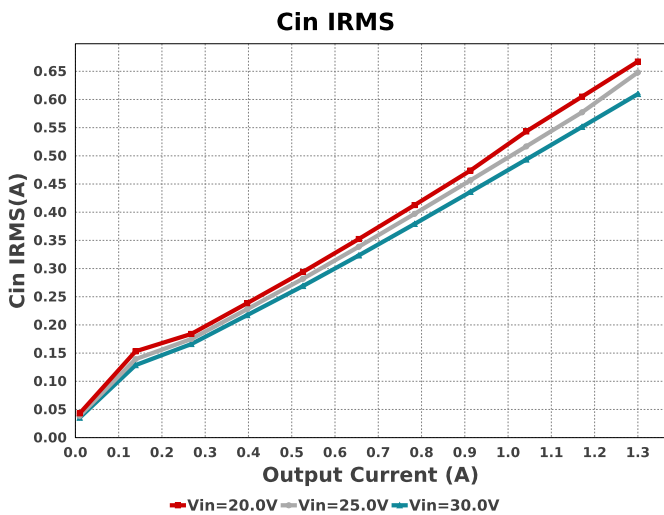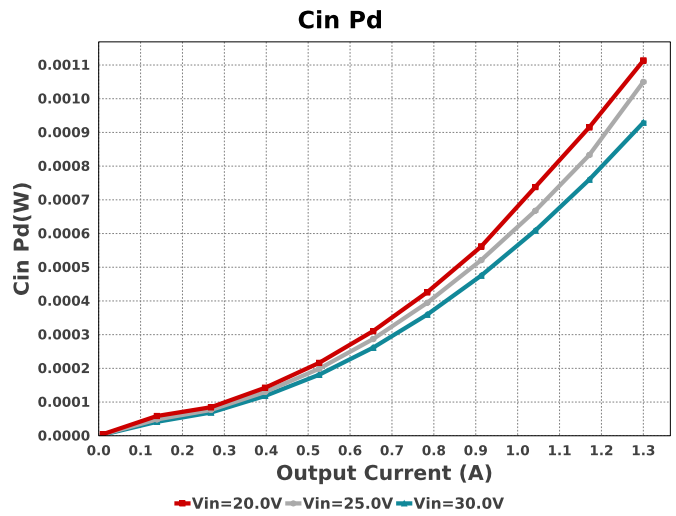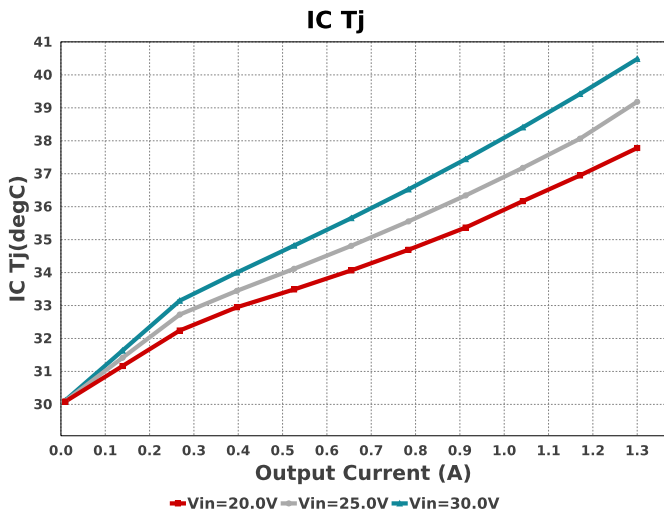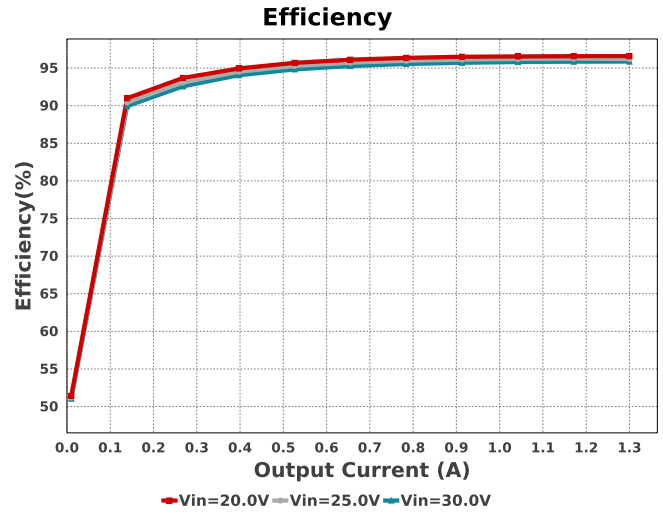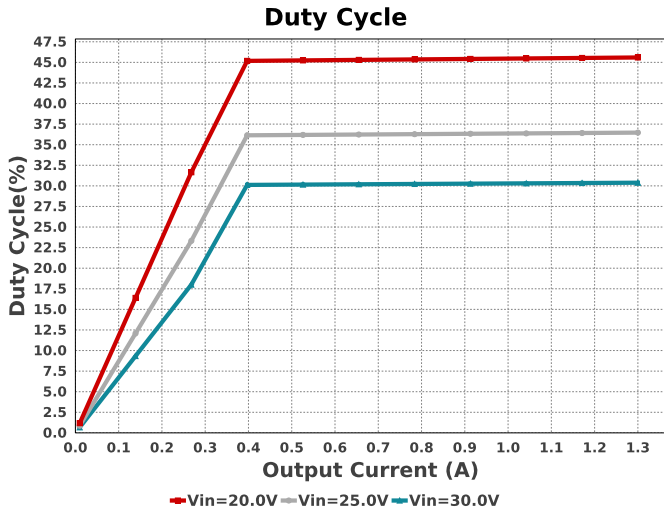

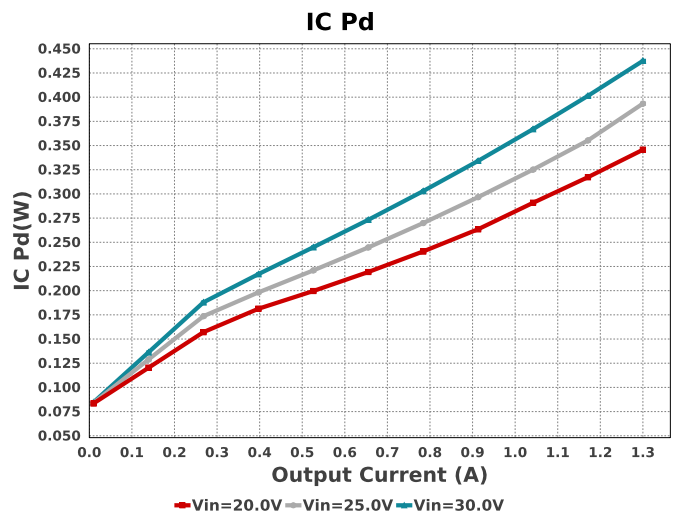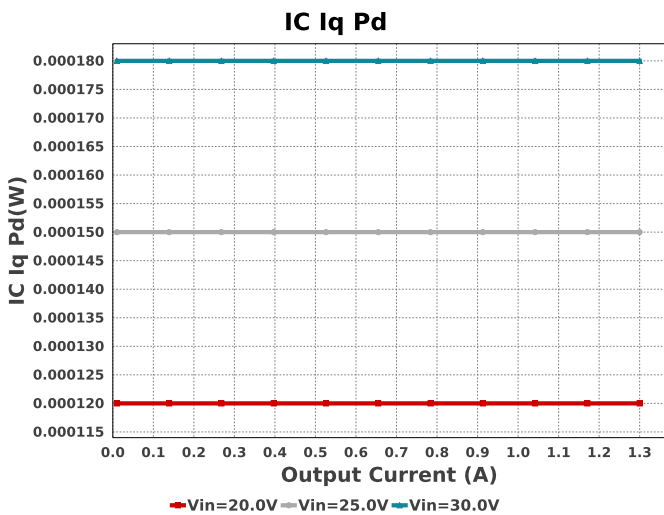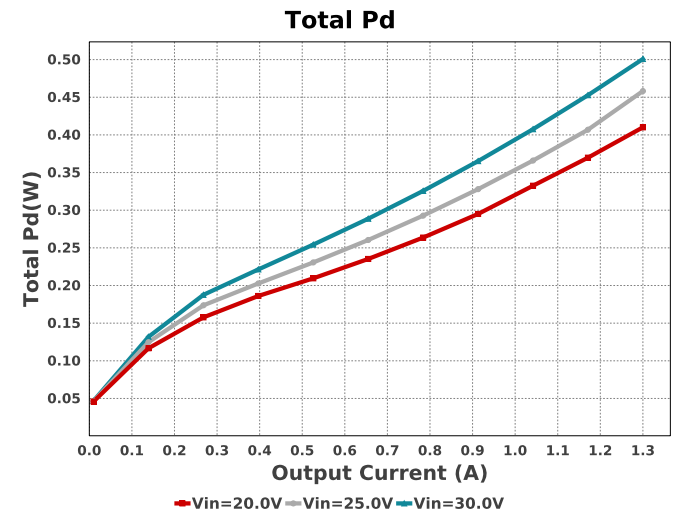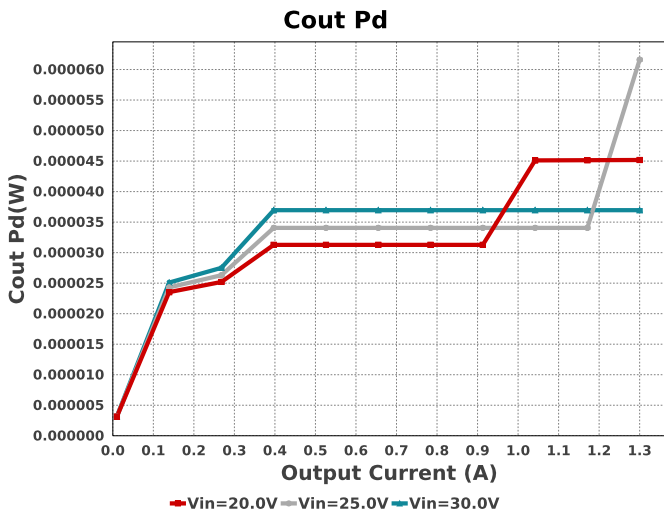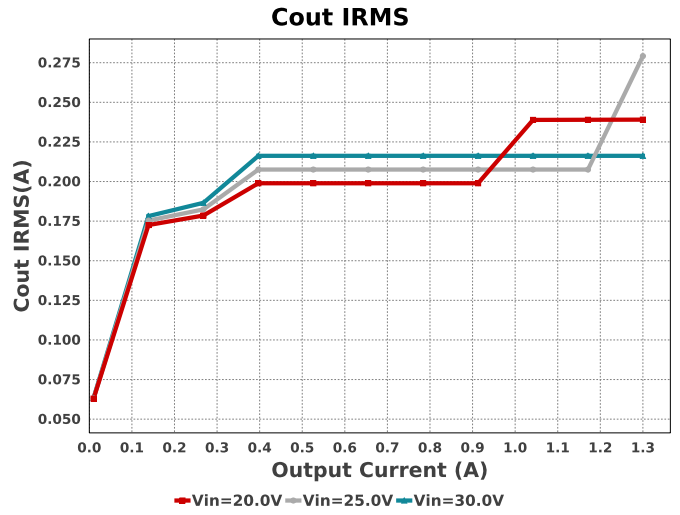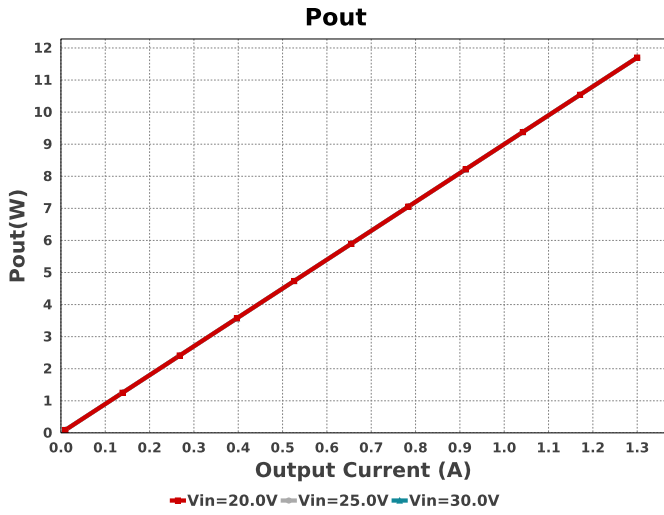

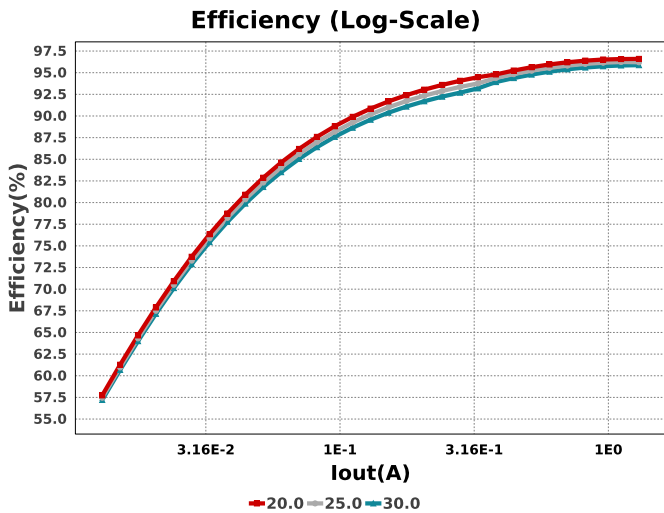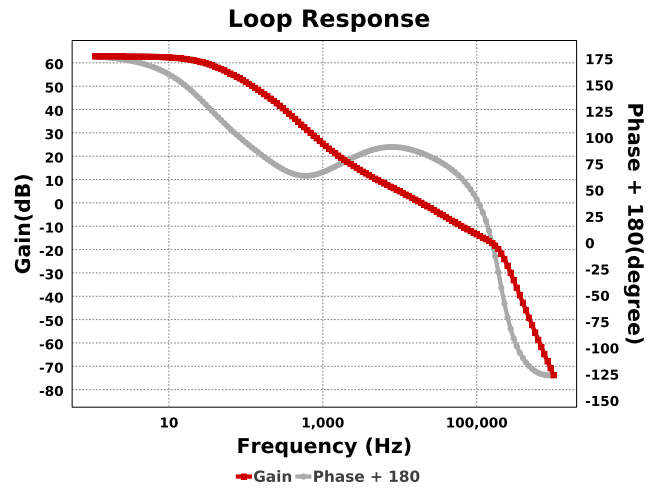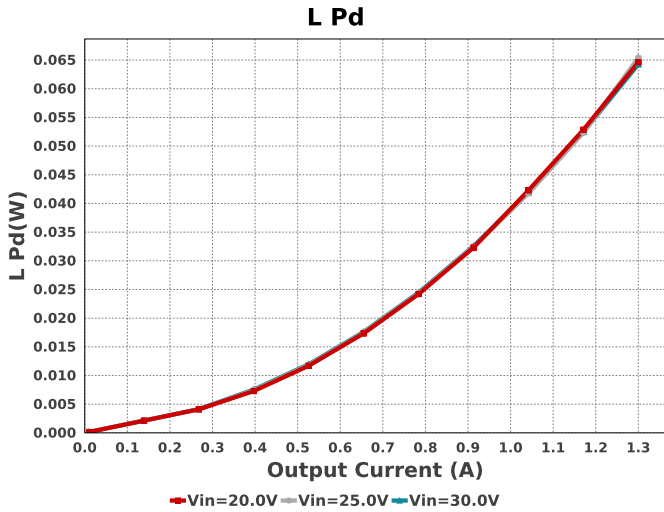

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	19		Total Design BOM count
2.	Total BOM	\$6.73		Total BOM Cost
3.	Cin IRMS	609.65 mA	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	929.18 μW	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	216.213 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	36.954 μW	Capacitor	Output capacitor power dissipation
7.	IC Iq Pd	180.0 μW	IC	IC Iq Pd
8.	IC Pd	437.52 mW	IC	IC power dissipation
9.	IC Tj	40.483 degC	IC	IC junction temperature
10.	ICThetaJA	29.4 degC/W	IC	IC junction-to-ambient thermal resistance
11.	Iin Avg	404.11 mA	IC	Average input current
12.	L Ipp	748.985 mA	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	64.26 mW	Inductor	Inductor power dissipation
14.	Cin Pd	929.18 μW	Power	Input capacitor power dissipation
15.	Cout Pd	36.954 μW	Power	Output capacitor power dissipation
16.	IC Pd	437.52 mW	Power	IC power dissipation
17.	L Pd	64.26 mW	Power	Inductor power dissipation
18.	Total Pd	500.814 mW	Power	Total Power Dissipation
19.	Cross Freq	18.981 kHz	System	Bode plot crossover frequency
20.	Duty Cycle	30.384 %	System	Duty cycle
21.	Efficiency	95.869 %	System	Steady state efficiency
22.	FootPrint	499.0 mm ²	System	Total Foot Print Area of BOM components
23.	Frequency	400.0 kHz	System	Switching frequency
24.	Gain Marg	-17.264 dB	System	Bode Plot Gain Margin
25.	Iout	1.3 A	System	Iout operating point

#	Name	Value	Category	Description
26.	Low Freq Gain	62.728 dB	System Information	Gain at 1Hz
27.	Mode	CCM	System Information	Conduction Mode
28.	Phase Marg	86.071 deg	System Information	Bode Plot Phase Margin
29.	Pout	11.7 W	System Information	Total output power
30.	Vin	30.0 V	System Information	Vin operating point
31.	Vout	9.0 V	System Information	Operational Output Voltage
32.	Vout Actual	8.971 V	System Information	Vout Actual calculated based on selected voltage divider resistors
33.	Vout Tolerance	1.988 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
34.	Vout p-p	1.813 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	1.3	Maximum Output Current
VinMax	30.0	Maximum input voltage
VinMin	20.0	Minimum input voltage
Vout	9.0	Output Voltage
base_pn	LMS3655S-Q1	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 20.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



Design Assistance

1. The LMS3655S-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application.
2. Master key : AF780BC098447727[v1]
3. **LMS3655S-Q1** Product Folder : <http://www.ti.com/product/LMS3655%2DQ1> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.