

$$m := 10^{-3} \quad k := 10^3 \quad u := 10^{-6} \quad n := 10^{-9}$$

▼ Load conditions

$$V_{\text{out}} := 12$$

$$I_{\text{out}} := 2.1$$

$$V_{\text{Bias}} := 22$$

$$I_{\text{bias}} := 0.1$$

▲ Load conditions

▼ I/O Spec of UCC28700

I/O Specifications:

$$85\sqrt{2} = 120.208$$

$$264\sqrt{2} = 373.352$$

Input Voltage:

$$V_{\text{in}_{\text{min}}} := 80$$

$$V_{\text{in}_{\text{max}}} := 375$$

Switching Frequency:

$$F_{\text{sw}} := 57\text{k}$$

$$V_{\text{in}} := (V_{\text{in}_{\text{min}}} - 10), V_{\text{in}_{\text{min}}} + \frac{V_{\text{in}_{\text{max}}} - V_{\text{in}_{\text{min}}}}{10} .. V_{\text{in}_{\text{max}}}$$

▲ I/O Spec of UCC28700

Turns Ratio:

Assumed Diode Drop: $V_d := 0.6 \text{ V}$ $D_{\max} := 1 - \left(\frac{F_{\text{sw}}}{2 \cdot 500\text{k}} \right) - 0.425$ $D_{\max} = 0.518$ From datasheet


$N_{p2s} := \frac{V_{\text{in_min}} \cdot D_{\max}}{(V_{\text{out}} + V_d)(1 - D_{\max})}$ $N_{p2s} = 6.823$ Maximum Primary to Secondary Turns Ratio - Limited by Dmax

Primary Turns: $N_p := 40$ $13 \cdot \frac{10}{3} = 43.333$

$N_s := \frac{N_p}{N_{p2s}}$ $N_s = 5.862$

Secondary Turns: $N_s := 7$ $12 \cdot \frac{5}{20} = 3$ $\frac{1}{4.2} = 0.238$
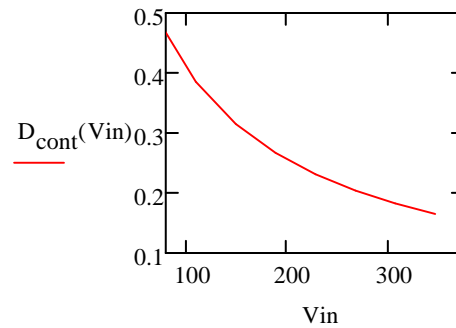
$$D_{\text{cont}}(V_{\text{in}}) := \frac{V_{\text{out}} \cdot \frac{N_p}{N_s}}{V_{\text{in}} + \frac{V_{\text{out}} \cdot N_p}{N_s}}$$



Determine Current Sense Resistance:

$V_{CCR} := 0.33$ From Datasheet: constant current regulation voltage

$I_{OCC} := 2.3$ Output over current level.

$\eta_{XFMR} := 0.9$ Estimated transformer efficiency

$$R_{CS} := \frac{V_{CCR} \cdot \frac{N_p}{N_s}}{2 \cdot I_{OCC}} \cdot \sqrt{\eta_{XFMR}}$$

$R_{CS} = 0.389$

Current sense resistance should be equal or less than this value.

$R_{CS} := 0.375$

Determine Primary Inductance:

$P_{out} := V_{out} \cdot I_{out}$ $P_{out} = 25.2$ W

Maximum Output Power

Output Power at DCM Boundary (Low Line):

$P_{out_boundary} := 28$ W

To ensure a DCM Flyback operation.

$$L_{dis} := \frac{V_{in_min}^2 \cdot D_{cont} \cdot (V_{in_min})^2}{2 \cdot P_{out_boundary} \cdot F_{sw}}$$

$L_{dis} = 427.103$ u H

Maximum Inductance to Remain Discontinuous

$V_{CST_max} := 0.78$ From Datasheet

$$I_{pp_max} := \frac{V_{CST_max}}{R_{CS}}$$

$I_{pp_max} = 2.08$

$$L_p := \frac{2 \cdot (V_{out} + V_d) \cdot I_{OCC}}{\eta_{XFMR} \cdot I_{pp_max}^2 \cdot F_{sw}}$$

$L_p = 261.147$ u

Actual Inductance:

$$L_{\text{act}} := 250 \mu \text{ H}$$

$$P_{\text{out, boundary}}(\text{Vin}) := \frac{\text{Vin}^2 \cdot D_{\text{cont}}(\text{Vin})^2}{2 \cdot L_{\text{act}} \cdot F_{\text{sw}}}$$

$$D_{\text{DCM}}(\text{Vin}) := \sqrt{\frac{2 \cdot P_{\text{out}} \cdot L_{\text{act}} \cdot F_{\text{sw}}}{\text{Vin}^2}}$$

DCM Duty cycle

$$D_{\text{CCM}}(\text{Vin}) := \frac{N_p \cdot V_{\text{out}}}{N_s \cdot \text{Vin} + N_p \cdot V_{\text{out}}}$$

CCM Duty cycle

$$\text{CCM}(\text{Vin}) := (D_{\text{DCM}}(\text{Vin}) > D_{\text{CCM}}(\text{Vin}))$$

$$D(\text{Vin}) := \text{if}(\text{CCM}(\text{Vin}), D_{\text{CCM}}(\text{Vin}), D_{\text{DCM}}(\text{Vin}))$$

$$V_{\text{us}}(\text{Vin}) := \frac{\text{Vin} \cdot D(\text{Vin})}{F_{\text{sw}}} \quad T_{\text{on}}(\text{Vin}) := \frac{D(\text{Vin})}{F_{\text{sw}}}$$

$$I_{\text{pri_pkpk}}(\text{Vin}) := \frac{\text{Vin} \cdot D(\text{Vin})}{L_{\text{act}} \cdot F_{\text{sw}}}$$

Peak to peak primary current

$$I_{\text{pri_le}}(\text{Vin}) := \text{if}\left(\text{CCM}(\text{Vin}), \frac{P_{\text{out}}}{\text{Vin} \cdot D(\text{Vin})} - \frac{I_{\text{pri_pkpk}}(\text{Vin})}{2}, 0\right)$$

Leading edge primary current

$$I_{\text{pri_te}}(\text{Vin}) := \text{if}\left(\text{CCM}(\text{Vin}), \frac{P_{\text{out}}}{\text{Vin} \cdot D(\text{Vin})} + \frac{I_{\text{pri_pkpk}}(\text{Vin})}{2}, I_{\text{pri_pkpk}}(\text{Vin})\right)$$

Trailing edge primary current

$$t := 0, \left(\frac{1}{10^3 \cdot F_{sw}} \right) \cdot \frac{1}{F_{sw}}$$

$$I_{pri}(V_{in}, t) := \text{if} \left[t \leq \frac{D(V_{in})}{F_{sw}}, \left(\frac{I_{pri_pkpk}(V_{in}) \cdot F_{sw}}{D(V_{in})} \cdot t + I_{pri_le}(V_{in}) \right), 0 \right]$$

Instantaneous Primary Current

$$I_{pri_rms}(V_{in}) := \sqrt{F_{sw} \int_0^{\frac{D(V_{in})}{F_{sw}}} I_{pri}(V_{in}, t)^2 dt}$$

RMS Primary Current

Primary MOSFET:

On resistance: $R_{ds_qpri} := 2.9 \quad \Omega$

Gate charge: $Q_{gate_qpri} := 9.9n \quad C$

Rise time: $Trise_qpri := 17n \quad S$

Bias voltage: $V_{bias} := 12 \quad V$

$$V_{ds}(V_{in}) := V_{in} + (V_{out} + V_d) \cdot \left(\frac{N_p}{N_s} \right)$$

Primary Drain Voltage

$$P_{drv_qpri} := Q_{gate_qpri} \cdot F_{sw} \cdot V_{bias} \quad P_{drv_qpri} = 6.772m \quad W$$

Driving Losses

$$P_{cond_qpri}(V_{in}) := I_{pri_rms}(V_{in})^2 \cdot R_{ds_qpri}$$

Conduction Losses

$$P_{off_qpri}(V_{in}) := \frac{1}{4} \cdot V_{ds}(V_{in}) \cdot I_{pri_te}(V_{in}) \cdot Trise_qpri \cdot F_{sw}$$

Turn-off Losses

$$P_{tot_qpri}(V_{in}) := P_{cond_qpri}(V_{in}) + P_{off_qpri}(V_{in})$$

Total MOSFET Losses
excluding driving losses

Diode Rectifier (Regulated Output):

Forward Drop:

$$V_{fwd} := 0.8$$

$$L_{sec} := L_{act} \cdot \frac{N_s^2}{N_p^2}$$

Secondary inductance

$$I_{sec_pkpk}(Vin) := I_{pri_pkpk}(Vin) \cdot \frac{N_p}{N_s}$$

Secondary peak current

$$T_{diode}(Vin) := \text{if} \left(\text{CCM}(Vin), \frac{1 - D(Vin)}{F_{sw}}, L_{sec} \cdot \frac{I_{sec_pkpk}(Vin)}{V_{out}} \right)$$

Diode conduction time

$$I_{sec}(Vin, t) := \text{if} \left[t \geq \frac{D(Vin)}{F_{sw}}, \text{if} \left[t < T_{diode}(Vin) + \frac{D(Vin)}{F_{sw}}, I_{pri_te}(Vin) \cdot \frac{N_p}{N_s} - \frac{I_{sec_pkpk}(Vin)}{T_{diode}(Vin)} \cdot \left(t - \frac{D(Vin)}{F_{sw}} \right), 0 \right], 0 \right]$$

Instantaneous secondary current

$$I_{sec_rms}(Vin) := \sqrt{F_{sw} \cdot \int_{\frac{D(Vin)}{F_{sw}}}^{\frac{1}{F_{sw}}} I_{sec}(Vin, t)^2 dt}$$

Secondary RMS current

$$V_{ds_qsec}(Vin) := V_{out} + Vin \cdot \frac{N_s}{N_p}$$

Reverse voltage

$$P_{cond_qsec} := I_{out} \cdot V_{fwd}$$

$$P_{cond_qsec} = 1.68$$

W

Voltage Sense:

Desired Bias Voltage:

$$V_b := 12$$

$$N_B := N_s \cdot \frac{V_b + 1}{V_{out} + V_{fwd}}$$

$$N_B = 7.109$$

Actual Bias Turns:

$$N_B := 11$$

Turn On Voltage(DC):

$$V_{en} := 85$$

From Datasheet:

$$I_{VSLRUN} := 220\mu$$

$$R_{S1} := \frac{N_B}{N_p} \cdot \frac{V_{en}}{I_{VSLRUN}}$$

$$R_{S1} = 106.25\text{k}$$

Actual resistance:

$$R_{S1} := 75\text{k}$$

From Datasheet:

$$V_{VSR} := 4.05$$

$$R_{S2} := \frac{V_{VSR}}{\frac{(V_{out} + V_{fwd}) \cdot \frac{N_B}{N_s} - V_{VSR}}{R_{S1}}}$$

$$R_{S2} = 18.908\text{k}$$

Actual resistance:

$$R_{S2} := 19.6\text{k}$$

$$V_{out_verify} := \left(1 + \frac{R_{S1}}{R_{S2}}\right) \cdot V_{VSR} \cdot \frac{N_s}{N_B} - V_{fwd} \quad V_{out_verify} = 11.639$$

Current Sense:

From Datasheet:

$$K_{LC} := 25$$

From Datasheet:

$$t_D := 50\text{n}$$

$$R_{LC} := \frac{K_{LC} \cdot R_{S1} \cdot R_{CS} \cdot t_D \cdot \frac{N_p}{N_B}}{L_{act}}$$

$$R_{LC} = 511.364$$

$$I_{OCCact} := \frac{V_{CCR} \cdot \frac{N_p}{N_s}}{2 \cdot R_{CS}} \cdot \eta_{XFMR}$$


$$I_{OCCact} = 2.263$$

$$P_{limit} := \frac{1}{2} \cdot L_{act} \left(\frac{0.71}{R_{CS}} \right)^2 \cdot F_{sw}$$

$$P_{limit} = 25.541$$

$$P_{CS}(V_{in}) := I_{pri_{rms}}(V_{in})^2 \cdot R_{CS}$$

Current sense losses

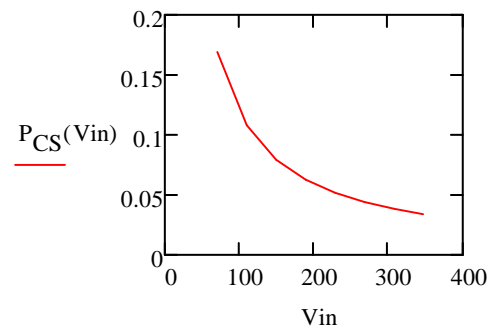

VDD Capacitor calculation:

From datasheet: $I_{\text{RUN}} := 2\text{m}$

$V_{\text{OCC}} := 8.5$

$V_{\text{DDon}} := 21$

$V_{\text{DDoff}} := 8.5$

$I_{\text{START}} := 2.1\text{m}$ Start-up bias supply current

$I_{\text{tran}} := 3$ Assumed load transient current

$dV_{\text{tran}} := 0.36$ Allowed voltage difference during transient.

$f_{\text{min}} := 30\text{k}$ Minimum switching frequency.

Minimum output capacitance required:

$$C_{\text{OUT}} := \frac{I_{\text{tran}} \cdot \left(\frac{1}{f_{\text{min}}} + 150\text{u} \right)}{dV_{\text{tran}}} \quad C_{\text{OUT}} = 1.528 \times 10^3 \text{ u}$$

$$C_{\text{OUT}} := 2200\text{u}$$

Target lowest converter output voltage in CC regulation:

$T_{\text{STR}} := 2$ converter start-up time requirement

$$C_{\text{Vdd}} := \frac{(I_{\text{RUN}} + 1\text{m}) \cdot \frac{C_{\text{OUT}} \cdot V_{\text{OCC}}}{I_{\text{OCC}}}}{(V_{\text{DDon}} - V_{\text{DDoff}}) - 1} \quad C_{\text{Vdd}} = 2.121 \text{ u}$$


Start up resistor:

$$R_{STR} := \frac{\sqrt{2} \cdot V_{in_min}}{I_{START} + \frac{V_{DDon} \cdot C_{Vdd}}{T_{STR}}} \quad R_{STR} = 5.331 \times 10^4$$


▲ UCC28700

▼ Plots for UCC28710

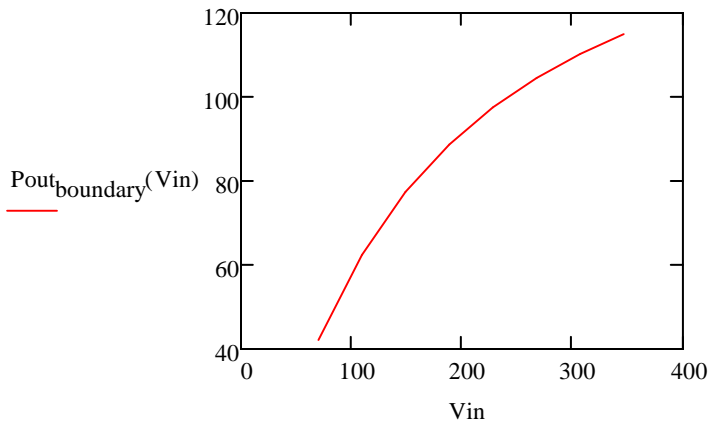Output power for the current Flyback coupled inductor setting to operate at boundary mode:




Instantaneous primary current:

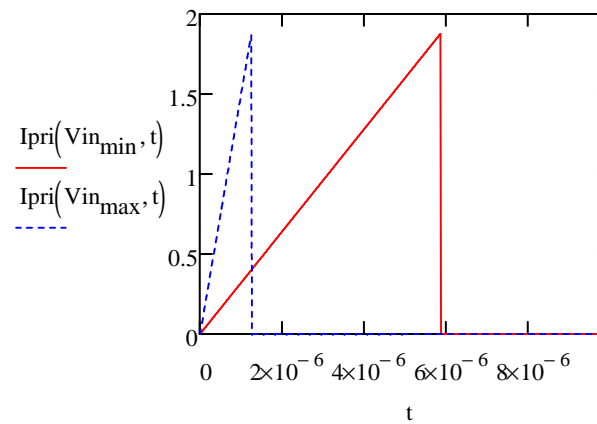


Need to make sure if the minimum on time @ V_{in_max} is greater than 400nS. If and only if $T_{on_min} > 400nS$, the design is valid!


Primary MOSFET on time:

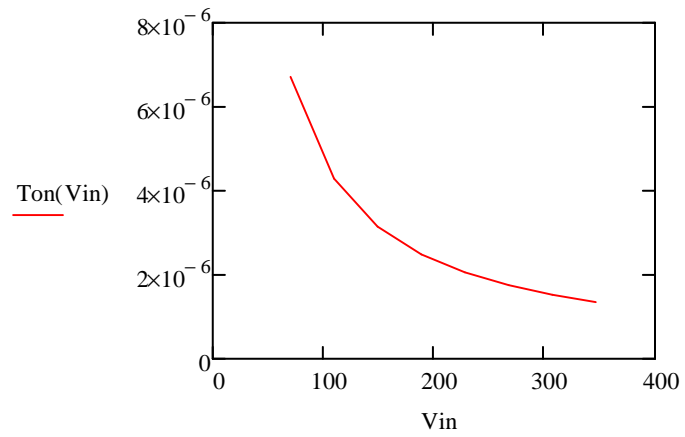


Duty cycle:

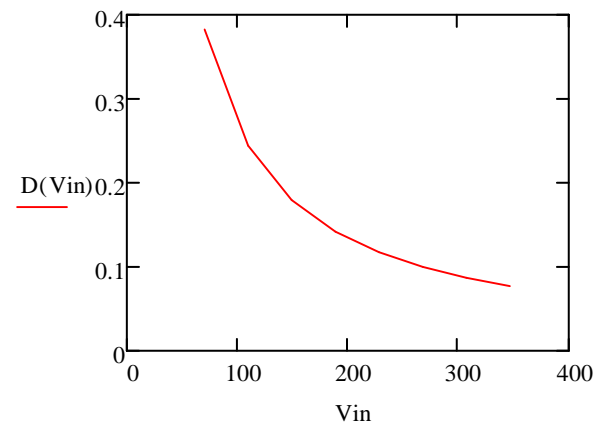


Primary MOSFET current:

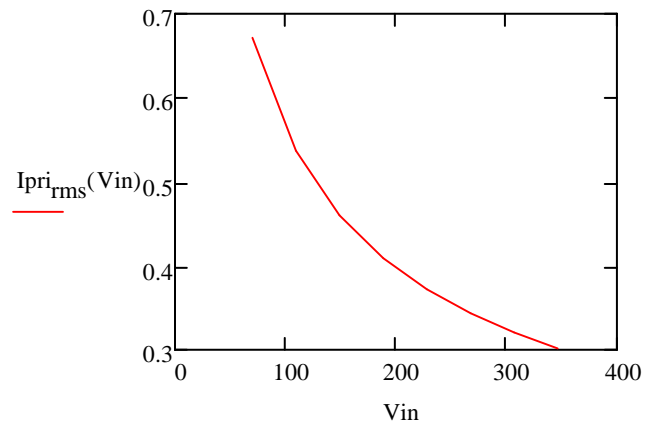


Voltage second:

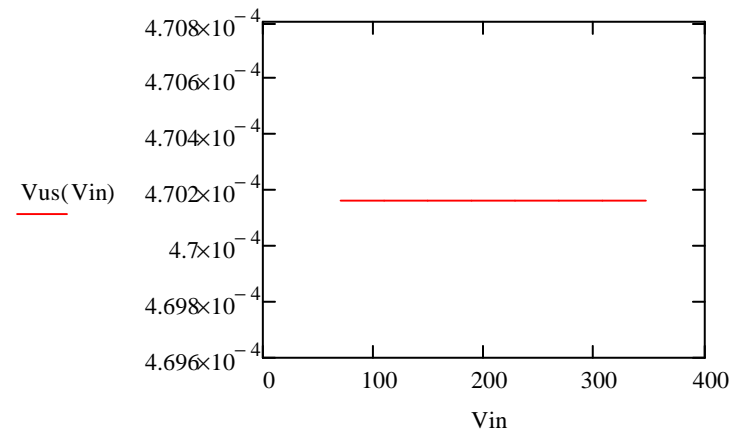


MOSFET losses:

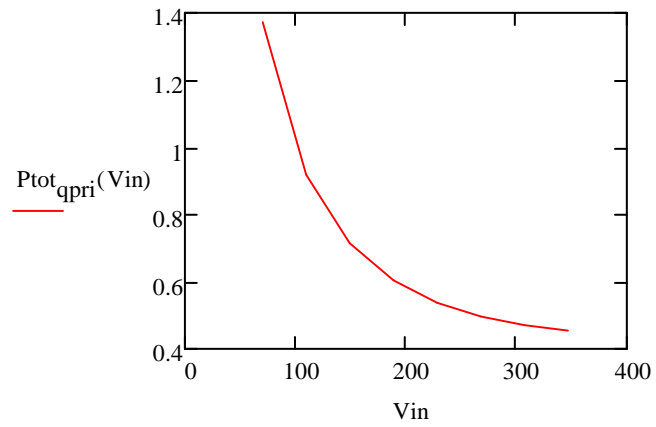


Voltage stress:

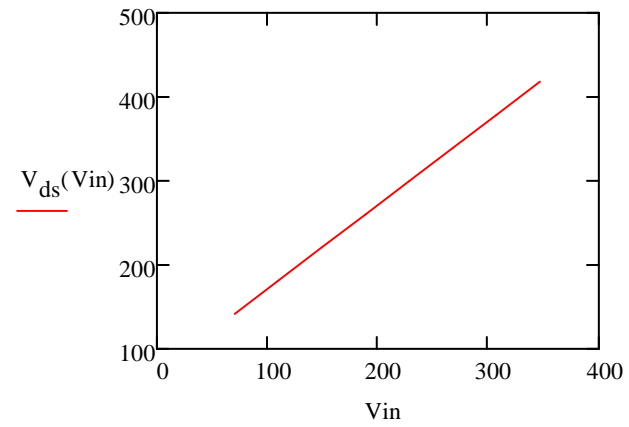

Instantaneous secondary current:

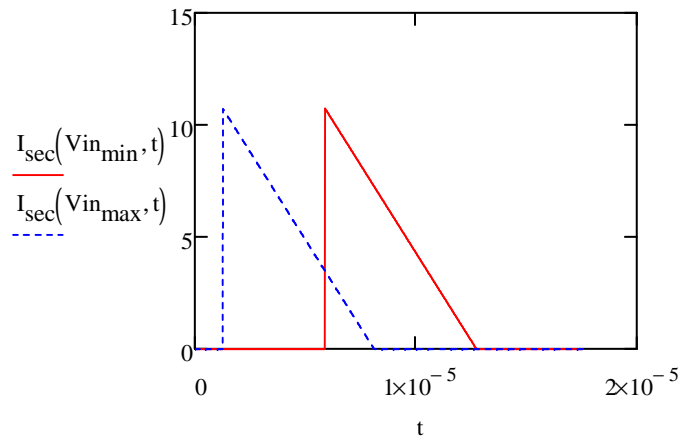

Secondary RMS current:

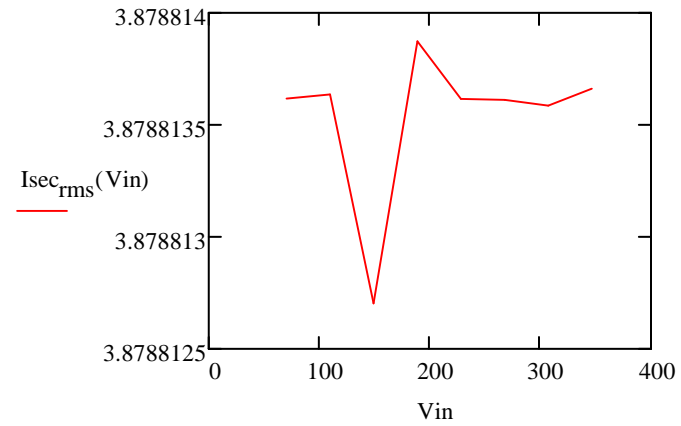

Instantaneous secondary voltage:

