

Predefinition of variables

$$\mu_0 := 4\pi \cdot 10^{-7} \cdot \frac{\text{H}}{\text{m}}$$

$$j := \sqrt{-1}$$

$$P_o := 0\text{W}, 100\text{W}.. 1100\text{W}$$

$$V_{\text{pfc}} := 395\text{V}$$

$$f_s := 0\text{kHz}, 1\text{kHz}.. 500\text{kHz}$$

$$n := \frac{22}{30}$$

1. Calculation of main circuit parameter

$$L_m := 72\mu\text{H}$$

$$L_r := 24\mu\text{H}$$

$$C_r := 94\text{nF}$$

$$f_r := \frac{1}{2\pi \cdot \sqrt{L_r \cdot C_r}} = 105.962 \cdot \text{kHz}$$

$$f_{r-} := \frac{1}{2\pi \cdot \sqrt{(L_r + L_m) \cdot C_r}} = 52.981 \cdot \text{kHz}$$

Output Voltage $V_o := 360\text{V}$

The output current is: $I_o(P_o) := \frac{P_o}{V_o}$ $I_o(1100\text{W}) = 3.056 \text{ A}$

The output equivalent load resistance is: $R_o(P_o) := \frac{V_o}{I_o(P_o)}$ $R_o(1100\text{W}) = 117.818 \Omega$

The equivalent load resistance on primary side of transformer can be described as:

$$R_{e(P_o)} := \frac{8}{\pi^2} \cdot n^2 \cdot R_o(P_o) \quad R_e(1100\text{W}) = 51.358 \Omega$$

The Q value of resonant tank is:

$$Q_e(P_o) := \frac{\sqrt{\frac{L_r}{C_r}}}{\left(\frac{8}{\pi^2} \cdot n^2 \cdot R_o(P_o)\right)} \quad Q_e(1100W) = 0.311$$

Frequency Margin for max load and max voltage


The voltage gain of DCDC converter (considering the turn ratio is 1:1) is

$$M(f_s, P_o) := \frac{0.5}{\sqrt{\left[1 + \frac{L_r}{L_m} \left[1 - \left(\frac{f_r}{f_s}\right)^2\right]^2\right]^2 + Q_e(P_o)^2 \cdot \left(\frac{f_s}{f_r} - \frac{f_r}{f_s}\right)^2}}$$

The output voltage function is:

$$V_{out}(f_s, P_o) := \frac{V_{pfc}}{n} \cdot M(f_s, P_o) - 1V \quad \text{where } 1V \text{ is forward voltage drop on output diode, but with SR, the actually voltage drop is less than } 1V$$

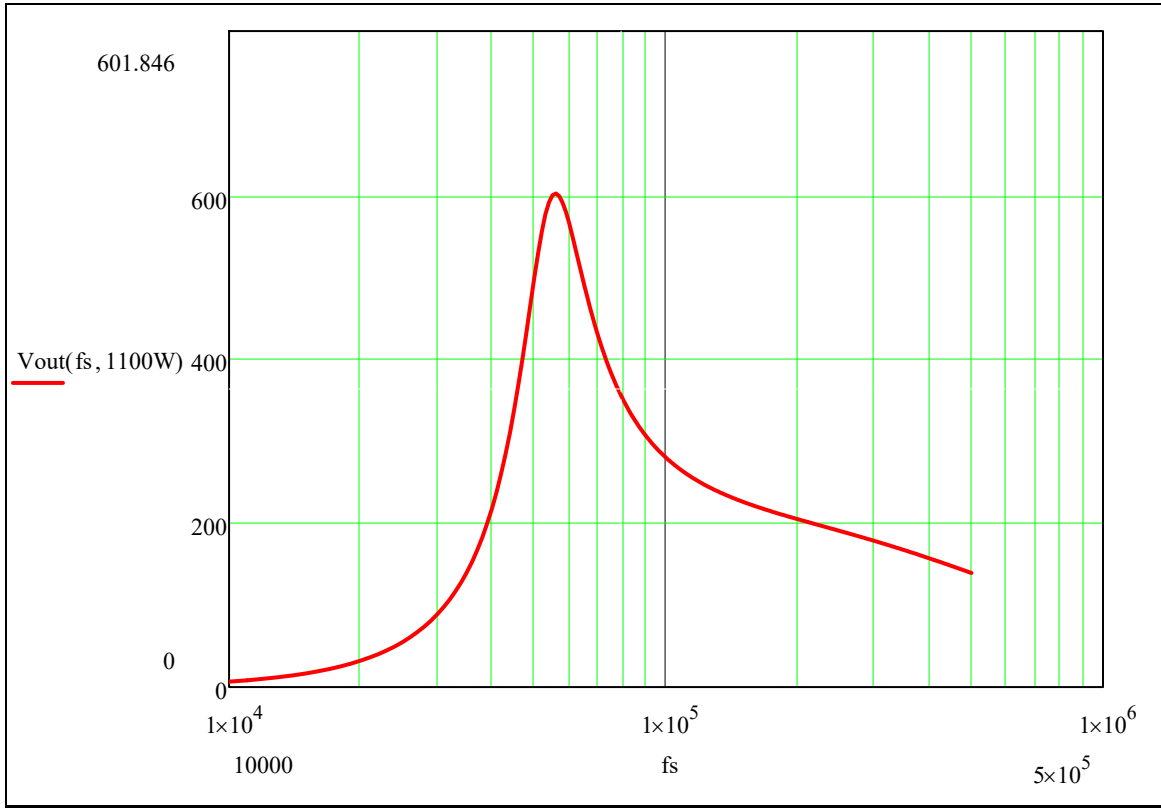Then we can get the curve of oupput voltage vs switching frequency as follow:



|