 




WHITEPAPER

Gate drive configurations for GaN power transistors

Bernhard Zojer, Infineon Technologies Austria AG

Edition: v1.0
Date: 04/2024

www.infineon.com



Table of contents

1	Introduction	3
2	Overview of standard GaN gate drive solutions	4
2.1	RC interface	4
2.1.1	RC interface for GIT	4
2.1.2	RC interface for SGT	6
2.2	Bipolar driver supply voltage	7
2.3	Direct drive	8
3	General dimensioning guidelines	9
3.1	Supply voltage V_{DD}	9
3.2	Coupling capacitance C_c	9
3.3	Resistor R_{SS}	9
3.4	Resistors R_{on} , R_{off}	10
4	Application examples	12
4.1	Universal gate driving circuit for GIT and SGT half-bridge with unipolar supply voltage and dual-channel gate driver IC	12
4.2	Universal gate driving circuit for GIT and SGT half-bridge with bipolar supply voltage and single-channel gate driver ICs	13
5	Summary	14
Appendix		15
	GaN half-bridge switching dynamics	15
6	References	17

1 Introduction

A proper gate control is crucial for system performance. This is valid for all power switches, and it is valid for gallium nitride (GaN) switches, too. Among the different GaN technologies available on the market, Infineon's portfolio comprises both common enhancement-mode (normally-off) concepts. They utilize a p-doped gate to shift the threshold voltage from the inherently negative value (normally-on) to a positive value. Depending on the realization of the gate contact, the resulting devices are either referred to as "gate injection transistor" (GIT) with an ohmic gate contact or as "Schottky gate transistor" (SGT) with an isolated gate structure similar to that of MOSFETs. While GITs are exclusively used in high-voltage applications (up to 700 V), SGTs cover a broader voltage range from 100 to 700 V. Essentially, the gate drive considerations discussed in this document are valid for all voltage classes.

All GaN switches are characterized by low terminal capacitances, and this results in a gate charge that is almost an order of magnitude lower than that of their silicon counterparts. Thus the driving capability of standard MOSFET drivers is usually more than sufficient for driving GaN transistors. However, there is a parameter typical for enhancement-mode (e-GaN) switches that significantly influences gate drive concepts. It is the low threshold voltage of the p-GaN gate, typically only slightly above +1 V. This has severe consequences:

- a relatively small gate current for switch-off at zero gate voltage
- an increased sensitivity with respect to cross-conduction in half-bridge applications

Both these effects can be mitigated by using a negative gate drive voltage. But there are also drawbacks associated with this measure, as a negative gate drive causes an increased voltage-drop in reverse (third quadrant) operation and thus higher conduction losses during dead-time. The optimum gate drive thus always depends on basic application conditions (hard/soft-switching, power class, switching voltage, frequency, etc.).

This whitepaper gives a compact overview of the recommended gate drive concepts for both GIT and SGT product families. A versatile standard drive (RC interface) can be easily adapted to both technologies. The document also provides basic gate drive dimensioning guidelines and some typical application examples.

2 Overview of standard GaN gate drive solutions

These solutions are characterized by utilizing standard gate drivers, acting as low impedance voltage sources to drive the GaN gate. In general, a passive interface then adapts the gate driver to specific GaN requirements.

2.1 RC interface

Although the RC interface is a natural solution for driving a GIT, it can also be adapted to drive an SGT. The main advantage in both cases is the generation of a well-defined negative gate drive voltage.

2.1.1 RC interface for GIT

The GIT is characterized by a non-isolated gate with a diode-like input characteristic. In the equivalent circuit of [Figure 1](#) this is indicated by the diode located between the gate and source, with a forward voltage drop V_F of about 3.5 V.

 


Figure 1 Equivalent circuit of CoolGaN™ GIT and a standard gate drive with RC interface

It is evident that the GIT gate structure is not compatible with standard MOSFET driving schemes, because a low-impedance voltage drive would cause unacceptably high current through the gate diode. But the standard way to drive a GIT is nevertheless simple. As shown in [Figure 1](#), an interface consisting of a coupling capacitance C_C and resistors R_{on} , R_{off} , and R_{SS} is added to a standard gate driver supplied with voltage V_{DD} . A gate driver from Infineon's EiceDRIVER™ product family [\[6\]](#) or a comparable one can in most applications be regarded as “quasi-ideal”, i.e., it has only a small or even negligible influence on the switching behavior which is mainly controlled by the external components. The ideal driver is characterized by:

- low-impedance outputs with high current capability
- true rail-to-rail operation
- a low input-to-output delay with very small random variations
- a galvanic input-to-output isolation (up to 8 kV)

In the steady “on”-state, the best way to drive a GIT's gate is by a small, constant gate current I_{ss} . This ensures stable operating conditions, independent of temperature, load current, or parameter variations. I_{ss} is defined by the driver-supply V_{DD} and the relatively high R_{SS} . A low-impedance path in parallel, formed by R_{on}/C_C for turn-on and R_{off}/C_C for turn-off, provides the higher current needed during fast-switching transitions. [Figure 2](#), left, shows the resulting current waveform.

 


Figure 2 Typical gate current and gate voltage waveforms for GIT

As a very valuable feature of this approach, the coupling capacitance C_C not only provides the high-current path, but also generates a negative gate drive voltage V_N in the “off”-state. This is possible because during the preceding “on”-state (S_1 closed), C_C is charged to the difference of the driver supply V_{DD} and gate diode clamping voltage V_F . By switching to the “off”-state (closing S_2), C_C acts as a charge pump, driving the gate to a negative voltage with an initial value of $-V_N$ that is defined by the total gate charge Q_{Gtot} (corresponds to Q_G in the datasheet), gate driver supply voltage V_{DD} , and coupling capacitance C_C , according to the relation

$$-V_N = -\frac{C_C \cdot (V_{DD} - V_F) - Q_{Gtot}}{C_C + C_{GS}} \quad (1)$$

While for soft-switching systems, usually a $-V_N$ value of -2 V to -3 V is sufficient, a value of -3 V to -5 V is a good choice in most hard-switching applications. After the “off”-transition $-V_N$ decays at a time constant given by C_C and R_{SS} (Figure 2b). This time constant is typically in the range of a few microseconds; it is essentially defined by the switch parameters (gate charge and steady-state gate current).

A negative gate drive voltage not only enables the usually intended fast switching “off”, but it is also beneficial during hard commutations in a half-bridge to protect the passive device from turning “on” and causing cross-conduction. Details of this very important mechanism, sometimes also referred to as “spurious turn-on” or “shoot-through”, are explained in the [Appendix](#).

In many cases the hard commutation occurs soon after switching “off” the passive device. In other words, the dead-time with both switches in the “off”-state is short (complementary switching). The initial V_N is sufficiently large to prevent cross-conduction, and the following decay of V_N is even beneficial, as any negative gate drive increases the voltage drop in diode operation. The tradeoff of reduced cross-conduction versus increased dead-time losses is inevitably associated with negative gate drive.

In certain applications, however, both switches in a half-bridge can be in the “off”-state for a longer period (non-complementary switching). Then, due to the discharging of C_C (decay of V_N), the RC interface may no longer guarantee sufficient suppression of cross-conduction. In this case the use of a bipolar supply voltage can be an option (Section 2.2).

Figure 1 also shows a separate source connection SK (Kelvin source) as the reference for the gate driver IC. Using the SK pin, any influence from the source inductance L_S on the gate loop is avoided. All discrete switches in Infineon’s GIT portfolio offer such a Kelvin source connection. It is not available in integrated power stages (IPS) that combine two GaN switches in half-bridge configuration with dedicated gate drivers in a common package.

2.1.2 RC interface for SGT

A GaN switch with a Schottky gate contact lacks the internal gate diode. Thus the equivalent circuit looks very similar to that of a MOSFET, and basically can be driven like a MOSFET, by applying a driving voltage to the gate via a low-impedance driver plus a gate resistor. Nevertheless, specific GaN aspects have to be considered. For a Schottky gate GaN switch, the optimum gate voltage range in the “on”-state is relatively small (typically 5 V to 6 V). And again, due to the low threshold, a negative gate drive can be beneficial to allow fast switching “off” and to avoid cross-conduction, particularly in hard-switched applications at higher voltage and power levels.

 


Figure 3 Equivalent circuit of CoolGaN™ SGT and gate drive with RC interface and clamping diodes

Figure 3 shows a gate drive concept for a Schottky gate GaN transistor, similar to the RC drive described in [Section 2.1.1](#). The gate voltage clamping function inherent to a GIT is taken over here by external components. Thus two Zener diodes ZD1 and ZD2 are added to the RC interface, clamping the gate voltage for both polarities (for ZD2 a standard diode also can be used). ZD1 typically is a 5.3 V Zener diode, resulting in a gate drive voltage of ~6 V. If VDD is chosen sufficiently high (e.g., VDD = 9 V), a negative gate drive voltage $-V_N$, according to equation 1, will be generated in the “off”-state. This is illustrated in the respective gate voltage and current waveforms of [Figure 4](#).

 


Figure 4 Typical gate current and gate voltage waveforms for SGT

With the proposed circuitry, the gate is driven at an approximately constant voltage close to 6 V. However, the effective gate drive varies not only with temperature, but also with the load current; this is caused by the fact that for a lateral transistor like GaN, a part of the channel resistance $R_{DS(on)}$ is situated within the gate drive loop (**Figure 3**). The voltage drop across this resistor obviously reduces the effective driving voltage.

In general, the coupling capacitance of the RC interface generates a negative gate voltage in the “off”-state with a starting value $-V_N$ that then decays at a time constant $R_{SS} \cdot C_C$. The negative gate voltage is required in hard switched half-bridges to avoid significant cross-conduction. Most applications use complementary control signals, with the switching transient happening within a short dead-time (typically < 100 ns) after having switched “off” the passive transistor. The generated negative voltage thus remains nearly unchanged and no further measures are needed to avoid cross-conduction.

Figure 5 shows the solutions for both an SGT and a GIT. While for an SGT a simple resistive interface is sufficient (**Figure 5a**), the GIT still needs the RC interface to provide the required two gate current paths (**Figure 5b**).



7
04/2024

3 General dimensioning guidelines

The dimensioning of the RC interface is relatively uncritical if a few basic relations are fulfilled. Further restrictions may result from specific application requirements.

3.1 Supply voltage V_{DD}

For a GIT, the intended high-impedance gate driver requires a supply voltage that is significantly larger than the gate diode clamping voltage V_F . The recommended driving voltage ranges between 8 V and 12 V (higher voltages are possible, but at the expense of increased third quadrant and driving losses).

For an SGT, the optimum gate voltage range is relatively small (typically 5 V to 6 V) to avoid reliability issues. Thus, an SGT driver is typically supplied with 9 V, if one of the recommended options with negative gate drive is chosen; a direct-driven SGT ideally utilizes a 6 V supply.

Generally, the negative gate drive voltage V_N calculated from Equation (1) should never be higher than needed, as this would only increase losses in third quadrant operation without providing any benefit.

3.2 Coupling capacitance C_c

Equation (1) is the key relation for dimensioning the RC interface. It is evident that the gate drive voltage in “off”-state must never become positive. According to Equation (1) this is fulfilled if the charge in the coupling capacitor in the “on”-state is larger than the total gate charge. To safely guarantee this under all possible conditions, the steady-state charge in C_c under nominal conditions should be two to three times the total gate charge, resulting in a simple relation for C_c ,

$$C_c \geq (2 \dots 3) \cdot Q_{Gtot} / (V_{DD} - V_F) \quad (\text{unipolar supply}) \quad (2a)$$

Although this slightly increases the dynamic gate drive power dissipation, the overall effect on losses is usually negligible.

With the use of a bipolar supply voltage, a reduction of C_c is recommended to avoid a high negative gate drive. As a rule of thumb,

$$C_c = Q_{Gtot} / (V_{DD} - V_F) \quad (\text{bipolar supply}) \quad (2b)$$

If SGTs are used with the RC interface, the possible range for the coupling capacitor is larger, because the difference between the supply and clamping voltages can be lower. This also increases the range for the discharging time constant.

3.3 Resistor R_{SS}

For GITs, the required steady-state gate current I_{SS} is directly set by R_{SS} according to the relation:

$$I_{SS} = (V_{DD} - V_F) / R_{SS} \quad (3)$$

A steady-state current of typically 10 mA is recommended for the 55 m Ω GIT. For different $R_{DS(on)}$ values, I_{SS} should be scaled inversely proportionally (e.g., half the I_{SS} for double the $R_{DS(on)}$).

With $V_{DD} = 8\text{ V}$, an I_{SS} of 10 mA causes an additional 40 mW of gate drive power (assuming a 50% duty-cycle). In many applications, this will be negligible. If it is of concern, I_{SS} can be further reduced. However, a minor increase in $R_{DS(on)}$ will be the consequence. Respective characterization data are given in the switch datasheets.

The average current through the Zener diodes in the RC drive for an SGT can be even smaller ($< 1\text{ mA}$) as the effect on the dissipated power is definitely negligible.

3.4 Resistors R_{on} , R_{off}

In general, a decrease in R_{on} causes a faster voltage transient and reduced switching losses (shorter voltage/current overlap period). A lower limit of R_{on} is usually given by the fact that faster switching leads to higher inductive overvoltages. The resulting drain-source voltage stress for the switch, however, has to be limited due to reliability reasons.

In soft-switching systems, R_{on} is rather uncritical and a larger value can be chosen without significant impact. Switching “off” should normally happen as fast as possible. However, there exists another lower limit on the gate resistors, which arises from the fact that the gate loop is essentially a series RLC circuit. It can be shown that a damping resistor with a minimum value

$$R_{min} = 1.5 \cdot \sqrt{L_G / C_G} \quad (4)$$

results in adequate gate voltage waveforms. Assuming, for example, a total gate loop inductance L_G of 10 nH (discrete HV switch), an effective capacitance C_G of around 0.5 nF (C_{iss} in series with C_c) and considering the gate driver output resistance and internal gate resistance, we can conclude that a minimum external gate resistor of a few ohms is required for R_{off} (usually the R_{on} value resulting from switching speed limitations is anyway higher).

Table 1 summarizes typical component values for the 55 mΩ GIT, taking into account these guidelines.

Table 1 Typical RC interface component values for 55/140 mΩ CoolGaN™ GIT

V_{DDO} [V]	$C_{c,soft}$ [nF]	$C_{c,hard}$ [nF]	R_{SS} [kΩ]	R_{on} [Ω]	R_{off} [Ω]
8	2.2/1.5	3.9/3.3	0.41/1.2	4.7–22/10–47	2.2/4.7
10	1.5/1.2	2.2/1.8	0.68/1.8	6.8–27/12–56	2.2/4.7
12	1/0.8	1.8/1	0.82/2.2	10–33/22–68	2.2/4.7

It should be noted that different C_c values are proposed for hard-switching and soft-switching topologies. This is because in hard-switched half-bridges, a higher negative gate drive is required to optimize the tradeoff between cross-conduction effects and increased reverse conduction losses. The minimum R_{on} depends on the total power loop inductance due to a further fundamental tradeoff between switching speed and voltage stress. The low R_{on} values require a total power loop inductance of a few nH only; the higher this inductance, the higher the R_{on} value should be. Similar considerations are valid for the typical values/ranges of the RC interface components for an SG switch as given in **Table 2**; for ZD1 a 5.3 V Zener diode is chosen.

Table 2 Typical RC interface component values for 50/150 mΩ CoolGaN™ SGT

V_{DD} [V]	C_c [nF]	R_{SS} [kΩ]	R_{on} [Ω]	R_{off} [Ω]
9	3.3–4.7	10	4.7–22/10–47	2.2/4.7
12	1.2–4.7	20	6.8–33/15–68	2.2/4.7

With the high C_C values of [Table 2](#), V_N stays nearly constant and is equal to the difference of supply voltage and Zener clamp voltage. The variation of V_{DD} then allows an easy control of V_N .

4 Application examples

4.1 Universal gate driving circuit for GIT and SGT half-bridge with unipolar supply voltage and dual-channel gate driver IC

Figure 7 shows a standard solution for a universal GaN half-bridge gate drive circuit. The two isolated output stages of the dual-channel EiceDRIVER™ 2EDB7259Y drive the respective switch via the RC interface, as described in sections 2.1 and 2.2. In case of an SGT, two Zener diodes are added to the RC interface, clamping the gate voltage for both polarities. The component values for the RC interface should be dimensioned following the guidelines in Section 3. As the dual-channel gate driver ICs do not provide separate source and sink outputs, a diode must be added to the standard interface if different values for R_{on} and R_{off} are required (in many applications, particularly soft-switching ones, a single resistor is sufficient). The circuit in **Figure 7** is typical for hard-switched topologies, with the driver connected to the Kelvin source SK. Two separate power supplies generate the driver output supplies (e.g., 8 V).

The dual-channel isolated EiceDRIVER™ 2EDB7259Y [7] is offered in a DSO-14 150 mil package with 3.3 mm channel-to-channel creepage and features a 3 kV_{rms} single protection isolation rating according to the UL 1577 standard. Furthermore, it ensures a minimum of 150 V/ns common-mode transient immunity (CMTI) robustness, which exceeds the requirements for even very fast switching GaN applications. With a stable propagation delay ($-5/+9$ ns) over both temperature and production variations, EiceDRIVER™ 2EDB7259Y ensures accurate timing and reliable operation over the full temperature range. More detailed information including measurement data is available in [1] and [2].

 


Figure 7 Universal gate driving circuit for GIT and SGT based on RC interface

4.2 Universal gate driving circuit for GIT and SGT half-bridge with bipolar supply voltage and single-channel gate driver ICs

Figure 8 shows a similar universal GaN half-bridge configuration utilizing a bipolar gate drive supply voltage. Instead of a dual-channel, it implements two single-channel EiceDRIVER™ 1EDB7275F with separate source and sink outputs. This can be beneficial in achieving a more compact PCB layout.

 


Figure 8 Universal gate driving circuit for GIT and SGT with bipolar driver supply

As indicated in Figure 8, again the same PCB can easily be adapted to drive either an SGT with an interface consisting of two gate resistors only, or to drive a GIT with the appropriately dimensioned RC interface.

The gate driver ICs have non-inverting and inverting inputs (IN+ and IN-) that can be connected as shown in Figure 8 to implement shoot-through protection. This feature provides an additional safety layer and therefore significantly improves system robustness. More detailed information including measurement data is available in [3]–[5].

5 Summary

[Table 3](#) and [Table 4](#) summarize the discussed gate drive configurations for a GIT and an SGT. As shown in [Section 4](#), a “universal” gate driving circuit compatible with both GaN technologies can be designed using the standard RC interface and populating accordingly the components on the PCB [\[1\]](#).

Table 3 Gate drive configurations for GIT

Driving voltage	Gate driver	Interface	Pros	Cons	Application
unipolar +8 V to +12 V	standard	RC	negative gate drive	larger gate loop	soft-switching hard-switching (complementary)
bipolar +9 V/-3 V (typical)	standard isolated	RC (reduced C_C)	negative gate drive	no bootstrapping	hard-switching (non-complementary)

Table 4 Gate drive configurations for SGT

Driving voltage	Gate driver	Interface	Pros	Cons	Application
unipolar +5 V to +6 V	standard	R_{on} only “direct” drive	like MOSFET	requires very low gate loop inductance (<1 nH)	medium voltage (100 V)
unipolar +8 V to +12 V	standard	RC plus clamping diode	similar to standard GIT drive large discharging time-constant range	additional components (Zener diodes)	soft-switching hard-switching
bipolar +6 V/-3 V (typical)	standard isolated	R_{on} , R_{off}	negative gate drive	no bootstrapping	soft-switching hard-switching

In these tables, the “standard” driver refers to fast low-impedance gate driver ICs with a current capability above 1 A. Input-to-output isolation is always required with bipolar supply and for high-side operation [\[3\]](#). For low-side operation, differential-input drivers are available; see [\[4\]](#) and [\[5\]](#). More information about the recommended EiceDRIVER™ gate driver ICs for driving GaN switches is available in [\[6\]](#).

Appendix

GaN half-bridge switching dynamics

Stacking two GaN/driver combinations and applying a (high) voltage V_+ results in the most important building block of a majority of power topologies: the half-bridge, consisting of a high-side (hs) and a low-side (ls) switch. The connection point is the switching node SW that is either connected to V_+ (hs “on”) or to ground (ls “on”), or exhibits high impedance (both switches “off”). It is evident that the two switches must never be in “on” state at the same time. If, except for a short dead-time, high- and low-side switches are always in opposite states, we talk about complementary switching. Such a situation is shown in Figure 9 (the equivalent circuit here has been reduced to comprise only the most important elements; power and gate loop inductance components have been lumped into L_L and L_{GG} , respectively.)

 


Figure 9 Hard-switched GaN half-bridge in boost configuration: equivalent circuit for hard switching transition (a) and symbolic voltage waveforms (b)

The constant load current I_L flowing into the switching node SW defines the role of the switches: if the low-side switch is “off”, V_{SW} is high and I_L flows through the upper switch in the reverse direction. Switching “on” the ls switch at time t_2 then causes the high-to-low transition of V_{SW} (“hard switching”). The opposite transition starts when switching “off” the low-side (t_3), as then the switching node is pulled up by the load current, and the high-side can be switched “on” at zero V_{DS} (“soft switching”). Thus, in the chosen “boost” configuration, the low-side is the active switch, whereas the high-side acts as the free-wheeling diode.

The qualitative (not to scale) waveforms in [Figure 9b](#) illustrate a few important effects associated with half-bridges. We start with the ls switch in the “off” state and V_{SW} at a level slightly higher than the supply voltage V_+ , as the hs switch is operated in reverse mode with a small negative V_{DS} ($R_{DS(on)} * I_L$). At time t_1 the hs switch is switched “off” (S_2 closed), and the charge in C_C causes a negative V_{GS} with an initial value of $-V_{Ni}$. To further allow current flow in reverse direction, V_{SW} has to exceed V_+ by V_{Ni} plus the GaN threshold V_{th} . This explains the small step in the V_{SW} waveform at time t_1 . After a short dead-time t_d , the ls switch is switched “on” at time t_2 , causing the “hard” negative transition of V_{SW} . Due to the associated Q_{GD} , this transition finally leads to a hs gate voltage increase from $-V_{Ni}$ to $-V_N$ according to

$$V_{Ni} - V_N = Q_{GD} / (C_C + C_{GS}) \quad (5)$$

V_N then slowly decays during the “off”-phase at a typical time constant $R_{SS} * C_C$, reaching a final value $-V_{Nf}$ at the end of the “off”-phase. It is evident that this Q_{GD} -induced gate voltage step has to be carefully considered for switching transitions occurring when C_C is uncharged (e.g., for non-complementary signals, during start-up or in burst mode operation).

The indicated undershoot of the switch node voltage after the switch-“on” event (V_{SW-}) is equivalent to a V_{DS} peak for the hs switch. It is caused by the power loop inductance L_L and depends on the switching speed that is essentially controlled by R_{on} . After the “on”-phase, the low-side is switched “off” at t_3 , and I_L again pulls V_{SW} up. The high-side has to conduct in reverse direction, and the required gate current causes the negative V_{GS} peak (V_{Gn} , [Figure 9b](#)) at time t_3 . Usually, the switching “off” process is sufficiently fast, and the overshoot of V_{SW} caused by L_L (V_{SW+}) then mainly depends on I_L . In most applications V_{SW+} is lower than V_{SW-} . After another dead-time the hs switch is switched “on” at t_4 , reducing V_{DS} again to its $R_{DS(on)}$ -defined value.

The most important effect associated with hard-switching, however, is caused by the switches’ gate-to drain capacitance C_{GD} . This is one of the components causing an interaction between the gate and the power loop (the other one being the common source inductance). As indicated in [Figure 9a](#), the falling V_{SW} is equivalent to an increase in the drain-to-gate voltage for the passive (hs) switch; this causes a current I_{GD} flowing into C_{GD} . Obviously I_{GD} has to be sunk by the gate driver, and the non-zero gate loop impedance leads to a peak in V_{GS} (V_{Gp}). If V_{Gp} exceeds the threshold voltage, both transistors are conducting simultaneously (cross-conduction or “spurious turn-on” (STO)). As the threshold concept is of course a simplification and approximation of real switch characteristics, STO effects also are not digital in nature, but may vary from “negligible” over “increased switching power” to even “destructive”. For GaN switches, a reduction through the negative V_{GS} is usually required in high-voltage applications with hard-switching voltage transitions. However, the trade-off with the increased reverse voltage drop during dead-time ($t_1 - t_2$ and $t_3 - t_4$) has to be taken into account.

6 References

- [1] C. Menditti, A. Laneve, and D. Varajao, “Universal Isolated Gate Driving Platform for 650 V GaN HEMTs Half-Bridge with Dead-Time Control and Integrated Bias Supply”, PCIM Europe 2023, Nuremberg, Germany, 2023
- [2] C. Menditti Matrisciano, “Half-bridge evaluation board designed with CoolGaN™ GIT HEMTs and EiceDRIVER™ 2EDB8259Y”, Infineon Technologies AG, AN_2210_PL21_2211_151906, 2023
- [3] C. Menditti Matrisciano, “Isolated Gate Driver IC with a configurable floating bipolar auxiliary supply for GaN MOSFETs”, Infineon Technologies AG, AN_2210_PL21_2211_152313, 2023
- [4] A. Laneve, “CoolGaN™ hybrid driving evaluation board with EiceDRIVER™ 1EDB7275F and 1EDN7550B”, Infineon Technologies AG, AN_2308_PL21_2309_151257, 2023
- [5] D. Varajao, T. Ferianz, V. Zhang, and C. Matrisciano, “Driving GaN HEMT High-Voltage Half-Bridge with a Single-Channel Non-Isolated Gate Driver with Truly Differential Inputs”, PCIM Europe 2020; International Exhibition and Conference for Power Electronics, Intelligent Motion, Renewable Energy and Energy Management, Nuremberg, Germany, 2020, pp. 1-8
- [6] Infineon Technologies AG, “Gate Driver ICs for GaN HEMTs,” 2024. [Online]. Available: <https://www.infineon.com/driver-gan>
- [7] Infineon Technologies AG, “Infineon GaN power transistors portfolio”, 2024. [Online]. Available: <https://www.infineon.com/gan>
- [8] Infineon Technologies AG, “EiceDRIVER™ 2EDB7259Y webpage”, 2024. [Online]. Available: <https://www.infineon.com/cms/en/product/power/gate-driver-ics/2edb7259y/>



www.infineon.com

Published by
Infineon Technologies AG
Am Campeon 1-15, 85579 Neubiberg
Germany

© 2023 Infineon Technologies AG
All rights reserved.

Public

Date: 04/2024

Please note!

This Document is for information purposes only and any information given herein shall in no event be regarded as a warranty, guarantee or description of any functionality, conditions and/or quality of our products or any suitability for a particular purpose. With regard to the technical specifications of our products, we kindly ask you to refer to the relevant product data sheets provided by us. Our customers and their technical departments are required to evaluate the suitability of our products for the intended application.

We reserve the right to change this document and/or the information given herein at any time.

Additional information

For further information on technologies, our products, the application of our products, delivery terms and conditions and/or prices, please contact your nearest Infineon Technologies office (www.infineon.com).

Warnings

Due to technical requirements, our products may contain dangerous substances. For information on the types in question, please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by us in a written document signed by authorized representatives of Infineon Technologies, our products may not be used in any life-endangering applications, including but not limited to medical, nuclear, military, life-critical or any other applications where a failure of the product or any consequences of the use thereof can result in personal injury.