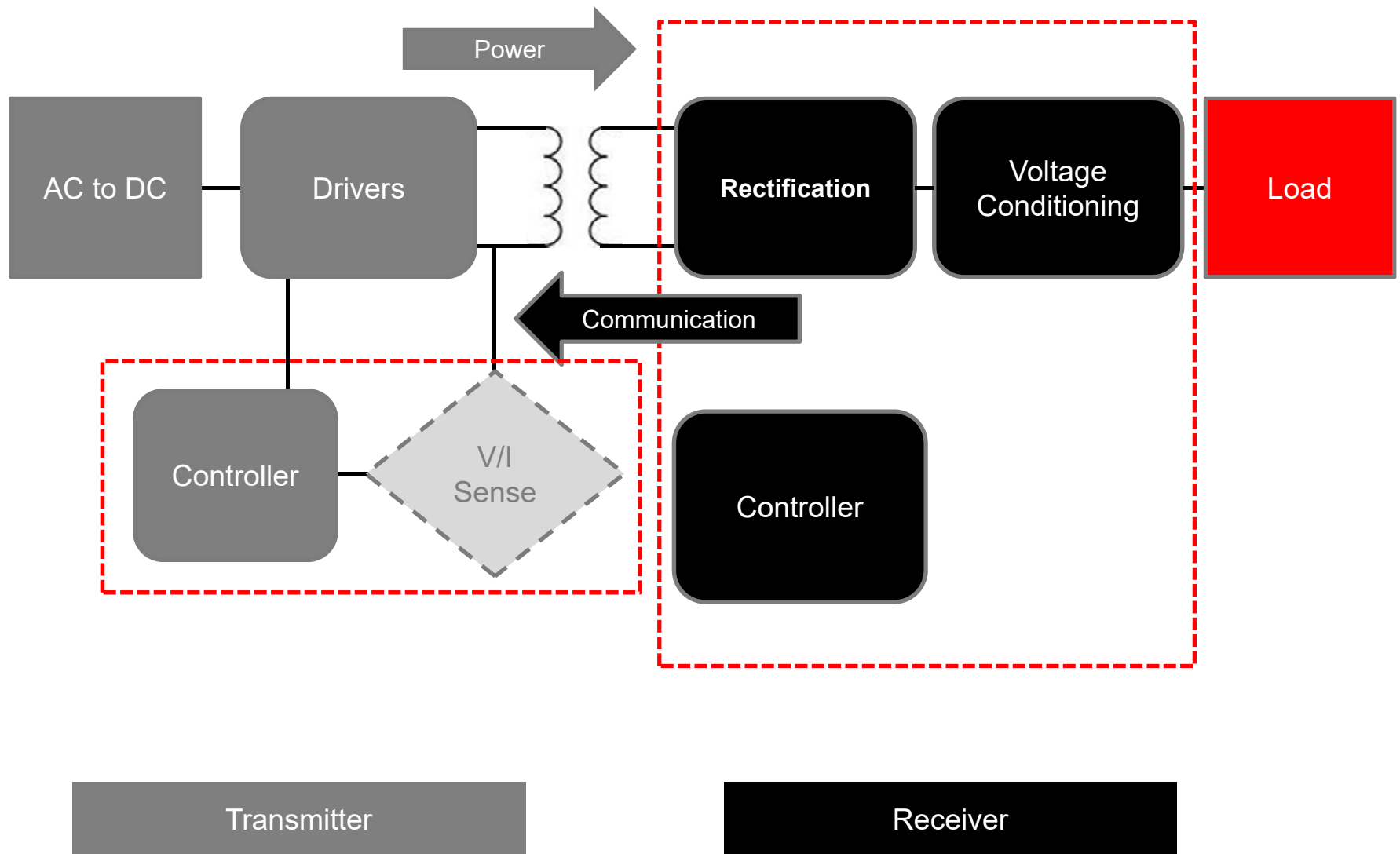


Wireless Power Receiver RX Coil Tuning Guide


Version 1.0

April 2022


bqTESLA Wireless Solutions for WPC



Wireless Power System Diagram

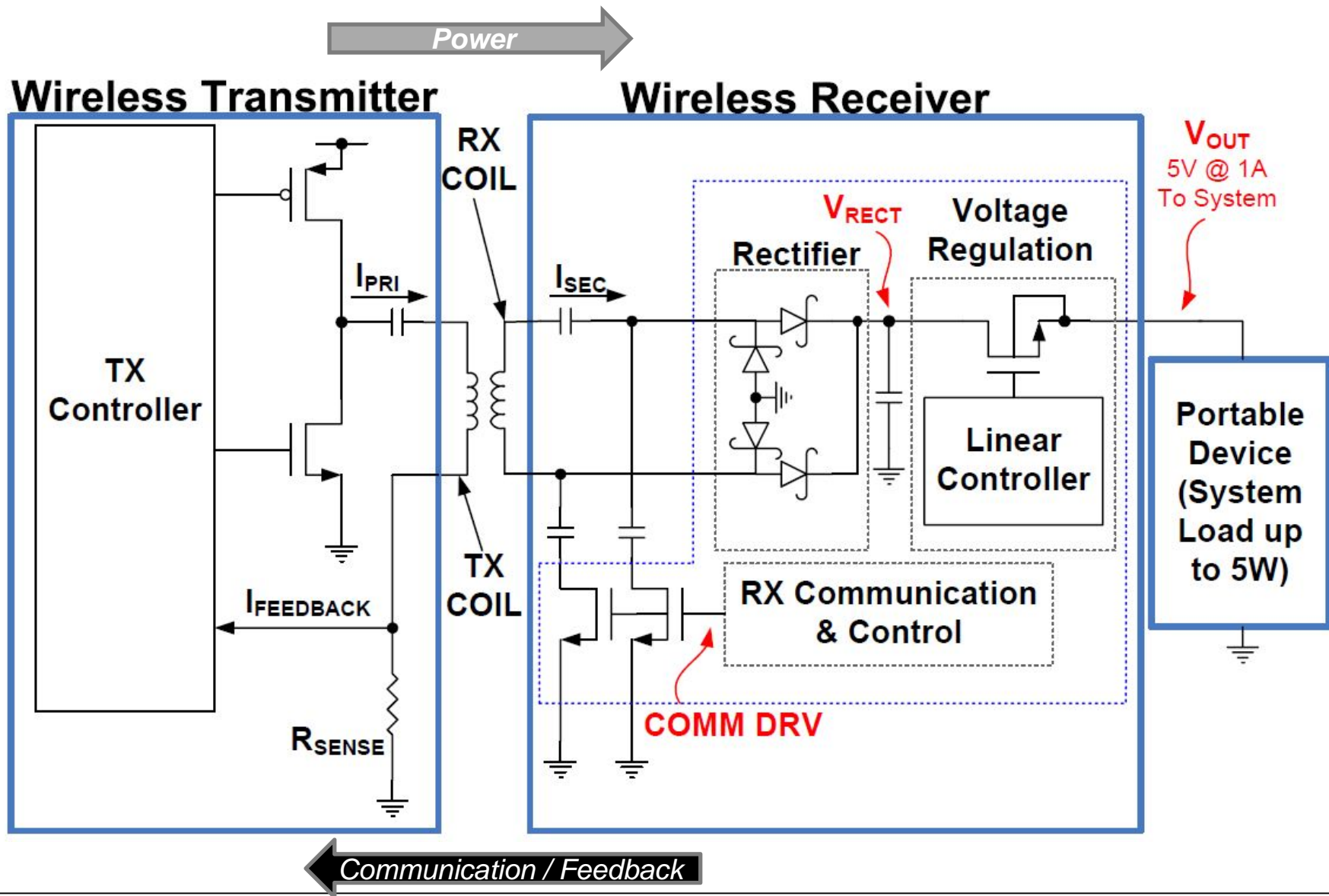


BQ510XX EVM/Reference Design

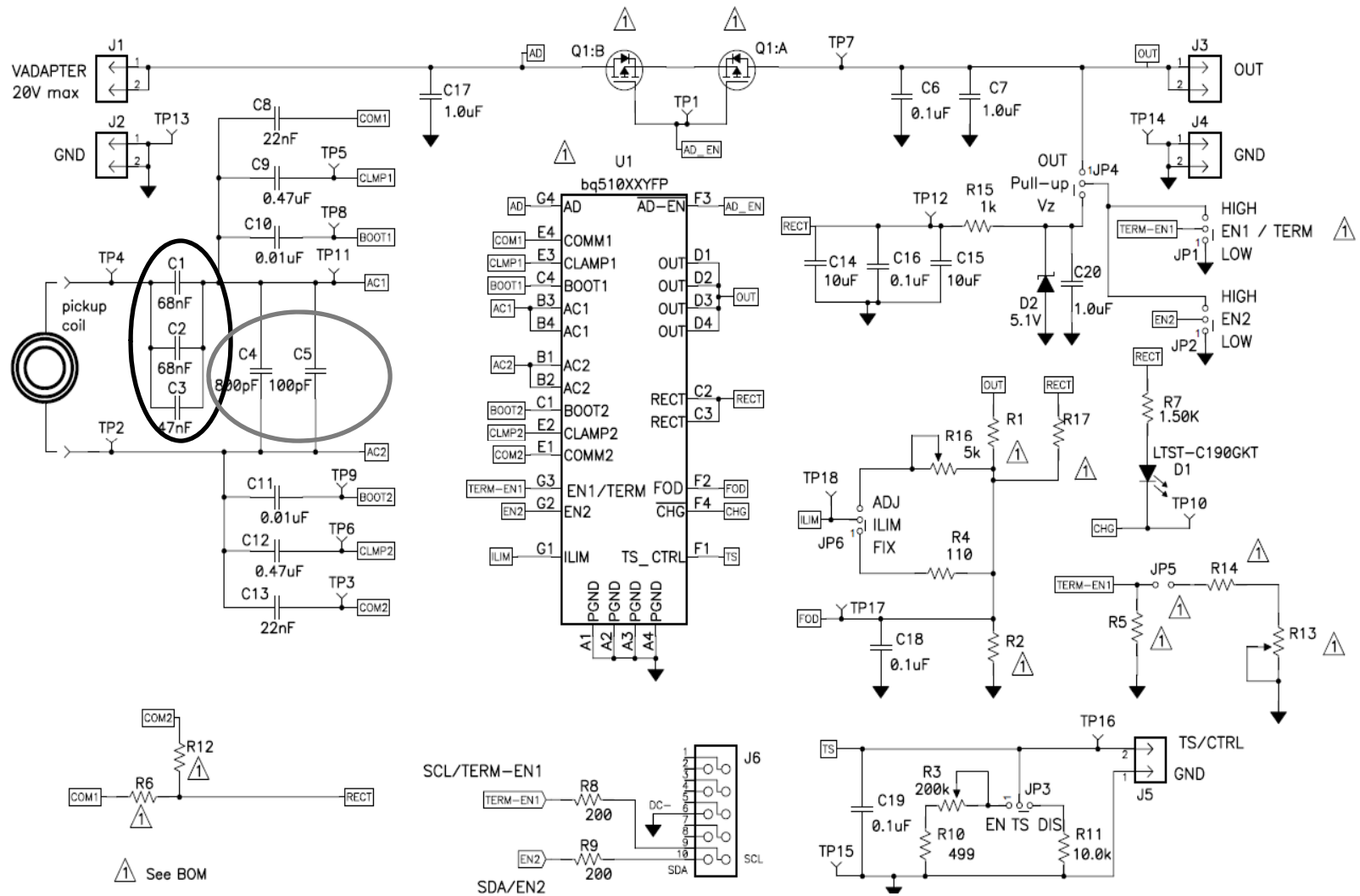

Series and Parallel Resonant Capacitor and Coil Inductor

Series and Parallel Resonant Capacitor and Coil Inductor

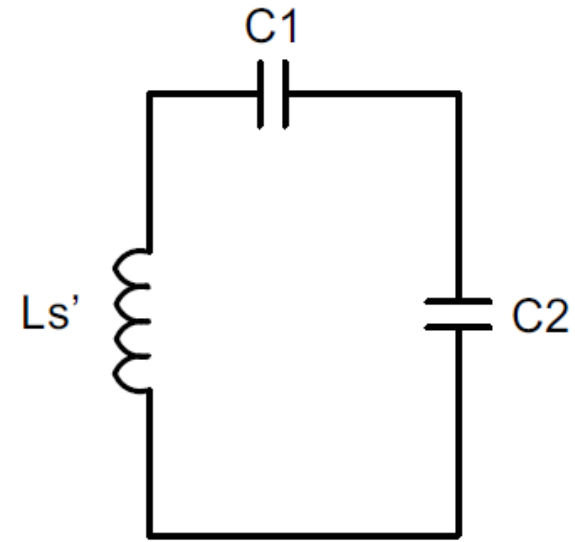- The capacitors C1 (series) and C2 (parallel) make up the dual resonant circuit with the receiver coil
- These two capacitors must be sized correctly
- L_s is the coil inductor on the receiver
- L_s and L_s' need to be measured



Series and Parallel Resonant Capacitors Calculation


$$C1 = \left[(f_s \times 2\pi)^2 \times L'_s \right]^{-1} \quad \text{Equation (01)}$$

$$C2 = \left[(f_D \times 2\pi)^2 \times L_s - \frac{1}{C1} \right]^{-1} \quad \text{Equation (02)}$$

- Equation (01): Calculates C1 using the measured value of L_s'
- Equation (02): Calculates C2 using the measured value of L_s and the calculated value of C1
- f_s : is 100KHz +5%/-10%
- f_D : is 1MHz \pm 10%

Ls Coil Measurements

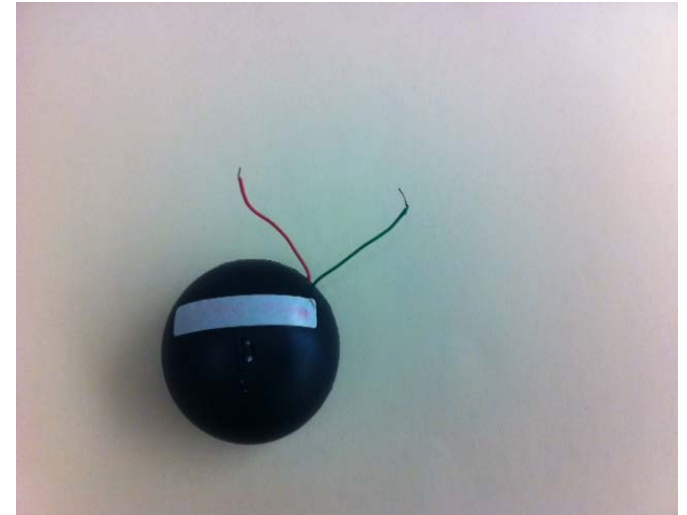
- Ls or the free-space inductance:
Inductance of the secondary coil away from transmitter pad
- Inductance will change with distance and other objects around the coil.
- Measurement of coil inductance should be made in final configuration inside the case with shields and battery in place.
- RX coil is tuned to 100kHz
- Inductance is to be measured at 1-V RMS



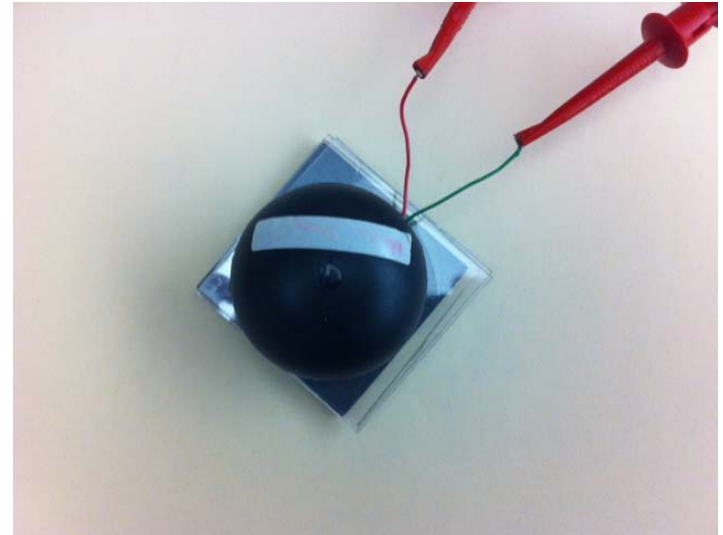Example: Inductance of the secondary coil away from transmitter pad and made in final configuration inside the case with shields and battery in place.


Ls' Coil Measurements

- Ls': Inductance of the secondary coil when placed on transmitter pad.
- The primary shield is to be 50 mm x 50 mm x 1 mm of Ferrite material PC44 from TDK Corp.
- The gap dz is to be 3.4 mm.
- The center of the Secondary Coil and the center of the primary Shielding shall be aligned.
- Inductance will change with distance and other objects around the coil.
- Measurement of coil inductance should be made in final configuration inside the case with shields and battery in place.
- RX coil is tuned to 100kHz
- Inductance is to be measured at 1-V RMS



Example: Secondary coil (made in final configuration inside the case with shields and battery in place) when placed on transmitter pad. Secondary Coil and the center of the primary Shielding shall be aligned.

The Primary Shielding

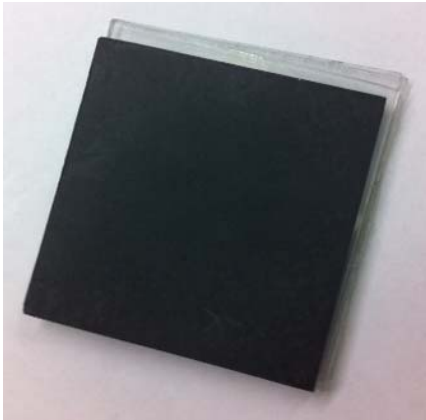

The primary shield is to be 50 mm x 50 mm x 1 mm of Ferrite material PC44 from TDK Corp.



The distance from the Receiver Interface Surface to the primary Shielding is 3.4 mm.

Example on Tuning Receiver Coil

Example: Step by Step Tuning Receiver Coil




Step 01: Set the tuning frequency to 100KHz



Step 02: Set the tuning voltage to 1-V RMS

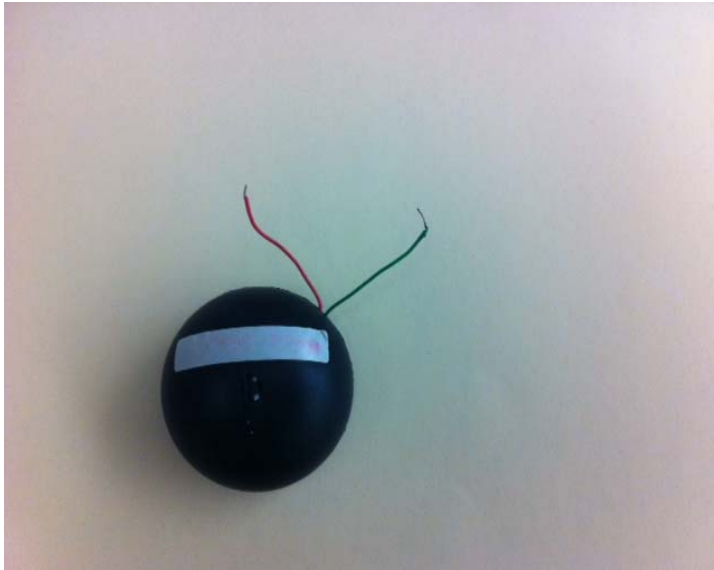Example: Step by Step Tuning Receiver Coil




Step 03: Measure the inductance of the secondary coil away from transmitter pad and made in final configuration inside the case with shields and battery in place.



Step 04: Record $L_s = 10.791 \mu\text{H}$

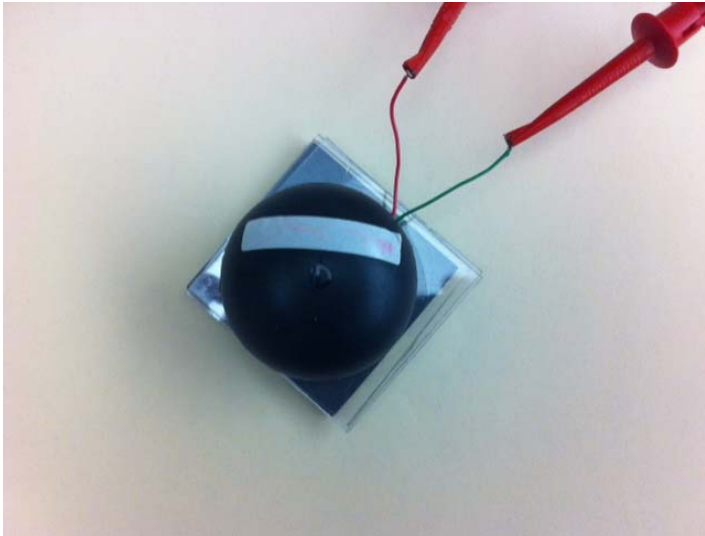Example: Step by Step Tuning Receiver Coil



Step 05: Measure the inductance of the secondary (made in final configuration inside the case with shields and battery in place) when placed on transmitter pad. Secondary Coil and the center of the primary Shielding shall be aligned.



Step 06: Record $L_s' = 15.606 \mu\text{H}$

Example: Step by Step Tuning Receiver Coil

$$C1 = \left[(f_s \times 2\pi)^2 \times L'_s \right]^{-1}$$

Equation (01)

Step 07: Use Equation (01) and calculated C1 Max and C1 Min.

f_s is 100KHz +5%/-10%

$$C1(\min) = 1 / ((105\text{kHz} \times 2\pi)^2 \times 15.606\mu\text{H})$$

$$C1(\min) = 147.22\text{nF}$$

$$C1(\max) = 1 / ((90\text{kHz} \times 2\pi)^2 \times 15.606\mu\text{H})$$

$$C1(\max) = 200.38\text{nF}$$

Step 08: chose a value between 147.22nF and 200.38nF

For this example we chose a standard values

$$2 \times 68\text{nF} + 1 \times 47\text{nF} = 183\text{nF}$$

$$(68\text{nF} // 68\text{nF} // 47\text{nF})$$

$$\mathbf{C1 = 183\text{nF}}$$

Example: Step by Step Tuning Receiver Coil

$$C2 = \left[(f_D \times 2\pi)^2 \times L_S - \frac{1}{C1} \right]^{-1}$$

Equation (02)

Step 09: Use Equation (02) and value of C1 calculated in previous step and calculate C2 Max and C2 Min.

f_D : is 1MHz $\pm 10\%$

$$C2(\min) = 1 / ((1.1\text{MHz} \times 2\pi)^2 \times 10.791\mu\text{H} - 1/183\text{nF})$$

$$C2(\min) = 1.96\text{nF}$$

$$C2(\min) = 1 / ((0.9\text{MHz} \times 2\pi)^2 \times 10.791\mu\text{H} - 1/183\text{nF})$$

$$C2(\max) = 2.94\text{nF}$$

Step 10: chose a value between 1.96nF and 2.94nF

For this example we chose a standard values

$$1800\text{pF} + 560\text{pF} = 2.36\text{nF}$$

$$(1800\text{pF} // 560\text{pF})$$

$$\mathbf{C2 = 2.36nF}$$

END