

Designed with TPSM84824

12V input,

0.95V, 15A output.

1. Output required for TPSM84824

	min		typ	max	
Input Voltage	-5.000 %	11.400 V	12.000 V	12.600 V	5.000 %
Output Voltage	-2.778 %	3.500 V	3.600 V	3.700 V	2.778 %
Output Current	-	-	-	5.000 A	-

2. Design plan for output accuracy

R_{fbt}=10kohm, ±0.1%

R_{fb}=2kohm, ±0.1%

DC accuracy (T _a = 0 ~ 40 °C)	±0.835 %	
Line Regulation	±0.028 %	;0.1mV/A*8A+a=0.2
Load Regulation	±0.910 %	;0.8mV/V*3.6+a,a=0.4
Output voltage ripple	±0.722 %	;16mV+a,a=10mV
Total accuracy	±2.495 %	

	min		typ	max	
Output Voltage	-2.495 %	3.510 V	3.600 V	3.690 V	2.495 %

I think it meets the required accuracy.

3. Designed files


The following materials are available.

- Schematic
- Bills of materials
- WEBNCH Summary Report

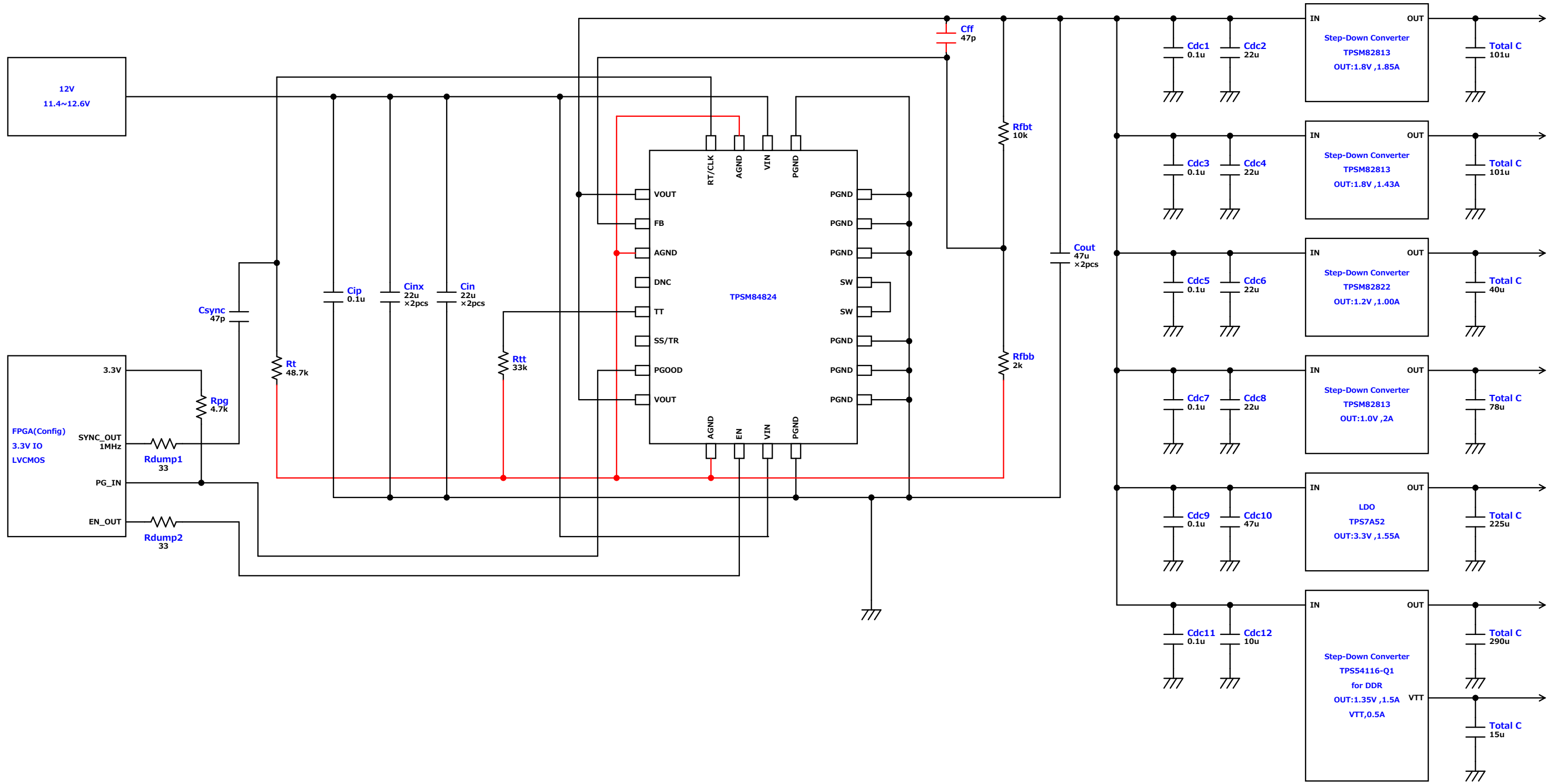4. Comment

This power supply drops 12V to 3.6V and supplies it to the IO power supply (6 power supplies) of the FPGA. Fill in the Schematic. Since LDO3.3V is used, it is set to 3.6V.


An external 1MHz clock is used to synchronize with TPSM82813 (2MHz) and TPS54116-Q1 (1MHz). This is to avoid beat noise.



Part	Manufacturer	Part Number	Quantity	Description
Rt	KOA	RK73H1ETTP4872F	1	Resistance: 48.7 kΩ Tolerance: 1.0% Power: 100 mW Package: 0402
Rfbb	KOA	RN73R1ETTP2001B25	1	Resistance: 2 kΩ Tolerance: 1.0% Power: 63 mW Package: 0402
Rfbt	KOA	RN73H1ETTP1002B25	1	Resistance: 10 kΩ Tolerance: 0.1% Power: 63 mW Package: 0402
Rtt	KOA	RK73H1ETTP3302F	1	Resistance:33 kΩ Tolerance: 1.0% Power: 100 mW Package: 0402
Cff	MuRata	GRM0335C1H470JA01D	1	Cap: 47 pF Total Derated Cap: 47 pF VDC: 50 V ESR: 120 mΩ Package: 0201
U1	Texas Instruments	TPSM84824MOLR	1	
Cin	MuRata	GRM21BR61E226ME44L	2	Cap: 22 μF Total Derated Cap: 7.4 μF VDC: 25 V ESR: 2 mΩ Package: 0805
Cin1	MuRata	GRM21BR61E226ME44L	2	Cap: 22 μF Total Derated Cap: 7.4 μF VDC: 25 V ESR: 2 mΩ Package: 0805
Cout	MuRata	GRM31CR61C476ME44L	2	Cap: 47 μF Total Derated Cap: 32 μF VDC: 16 V ESR: 1 mΩ Package: 1206
Csync	MuRata	GRM0335C1H470JA01D	1	Cap: 47 pF Total Derated Cap: 47 pF VDC: 50 V ESR: 120 mΩ Package: 0201
Rdump1	KOA	RK73H1ETTP33R0F	1	Resistance:33 Ω Tolerance: 1.0% Power: 100 mW Package: 0402
Rdump2	KOA	RK73H1ETTP33R0F	1	Resistance:33 Ω Tolerance: 1.0% Power: 100 mW Package: 0402
Cip	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc1	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc2	MuRata	GRM21BR61E226ME44L	1	Cap: 22 μF Total Derated Cap: 13,6 μF VDC: 25 V ESR: 2 mΩ Package: 0805
Cdc3	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc4	MuRata	GRM21BR61E226ME44L	1	Cap: 22 μF Total Derated Cap: 13,6 μF VDC: 25 V ESR: 2 mΩ Package: 0805
Cdc5	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc6	MuRata	GRM21BR61E226ME44L	1	Cap: 22 μF Total Derated Cap: 13,6 μF VDC: 25 V ESR: 2 mΩ Package: 0805
Cdc7	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc8	MuRata	GRM21BR61E226ME44L	1	Cap: 22 μF Total Derated Cap: 13,6 μF VDC: 25 V ESR: 2 mΩ Package: 0805
Cdc9	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc10	MuRata	GRM31CR61C476ME44L	1	Cap: 47 μF Total Derated Cap: 32 μF VDC: 16 V ESR: 1 mΩ Package: 1206
Cdc11	MuRata	GRM033R61E104KE14D	1	Cap: 0.1 μF Total Derated Cap: 0..068 μF VDC: 25 V ESR: 30 mΩ Package: 0201
Cdc12	MuRata	GRM188R61E106KA73D	1	Cap: 10 μF Total Derated Cap: 5.58 μF VDC: 25 V ESR: 3 mΩ Package: 0603







WEBENCH® Design Report






 
Design : 62 TPSM84824MOLR
 TPSM84824MOLR 11.4V-12.6V to 3.60V @ 8A







Electrical BOM

Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cin	MuRata	GRM21BR61E226ME44L Series= X7R	Cap= 3.74 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.87 A	2	\$0.10	0805 7 mm ²
Cin1	MuRata	GRM21BR61E226ME44L Series= X7R	Cap= 3.76 uF ESR= 2.0 mOhm VDC= 25.0 V IRMS= 3.87 A	2	\$0.10	0805 7 mm ²
Cout	MuRata	GRM31CR61C476ME44L Series= X7R	Cap= 32.0 uF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 3.2 A	7	\$0.10	1210 11 mm ²
Rfbb	Vishay-Dale	CRCW04021K96FKED Series= CRCW..e3	Res= 1.96 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	0402 3 mm ²
Rfbt	Yageo	RC0201FR-0710KL Series= ?	Res= 10.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	0201 2 mm ²
Rt	KOA	RK73H1ETTP4872F Series= CRCW..e3	Res= 48.7 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.10	0402 3 mm ²
Rtt	MuRata	RK73H1ETTP3302F Series= CRCW..e3	Res= 33.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.10	0402 3 mm ²
U1	Texas Instruments	TPSM84824MOLR	Switcher	1	\$5.00	MOL0024A 90 mm ²

      

      

    

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	16		Total Design BOM count
2.	Total BOM	\$6.32		Total BOM Cost
3.	Cin IRMS	1.842 A	Capacitor	Input capacitor RMS ripple current
4.	Cin Pd	3.391 mW	Capacitor	Input capacitor power dissipation
5.	Cout IRMS	893.51 mA	Capacitor	Output capacitor RMS ripple current
6.	Cout Pd	114.05 μW	Capacitor	Output capacitor power dissipation
7.	IC Ipk	9.548 A	IC	Peak switch current in IC
8.	IC Iq Pd	7.151 mW	IC	IC Iq Pd
9.	IC Pd	2.571 W	IC	IC power dissipation
10.	IC Tj	109.0 degC	IC	IC junction temperature
11.	ICThetaJA Effective	21.0 degC/W	IC	Effective IC Junction-to-Ambient Thermal Resistance
12.	Iin Avg	2.491 A	IC	Average input current
13.	L Ipp	3.095 A	Inductor	Peak-to-peak inductor ripple current
14.	L Pd	485.99 mW	Inductor	Inductor power dissipation
15.	Cin Pd	3.391 mW	Power	Input capacitor power dissipation
16.	Cout Pd	114.05 μW	Power	Output capacitor power dissipation
17.	IC Pd	2.571 W	Power	IC power dissipation
18.	L Pd	485.99 mW	Power	Inductor power dissipation
19.	Total Pd	2.58 W	Power	Total Power Dissipation
20.	Duty Cycle	29.844 %	System	Duty cycle
21.	Efficiency	91.78 %	Information	Steady state efficiency
22.	FootPrint	231.0 mm ²	System	Total Foot Print Area of BOM components
23.	Frequency	995.676 kHz	Information	Switching frequency
24.	Iout	8.0 A	System	Iout operating point
25.	Mode	CCM	Information	Conduction Mode

#	Name	Value	Category	Description
26.	Pout	28.8 W	System Information	Total output power
27.	Vin	12.6 V	System Information	Vin operating point
28.	Vout	3.6 V	System Information	Operational Output Voltage
29.	Vout Actual	3.661 V	System Information	Vout Actual calculated based on selected voltage divider resistors
30.	Vout Tolerance	3.384 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
31.	Vout p-p	1.768 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	8.0	Maximum Output Current
SoftStart	1.2 ms	Soft Start Time (ms)
VinMax	12.6	Maximum input voltage
VinMin	11.4	Minimum input voltage
Vout	3.6	Output Voltage
base_pn	TPSM84824	Base Product Number
source	DC	Input Source Type
Ta	55.0	Ambient temperature
UserFsw	1000.0 k	Customer Selected Frequency
1. Vout Sch	3.6	Output voltage selected

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 11.4V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

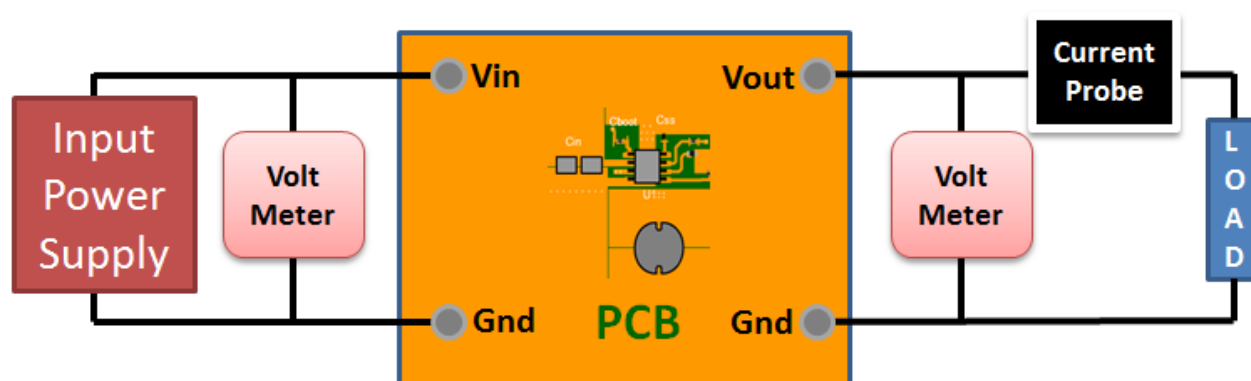


WEBENCH® Electrical Simulation Report

Design Id = 62



sim_id = 1

Simulation Type = Startup

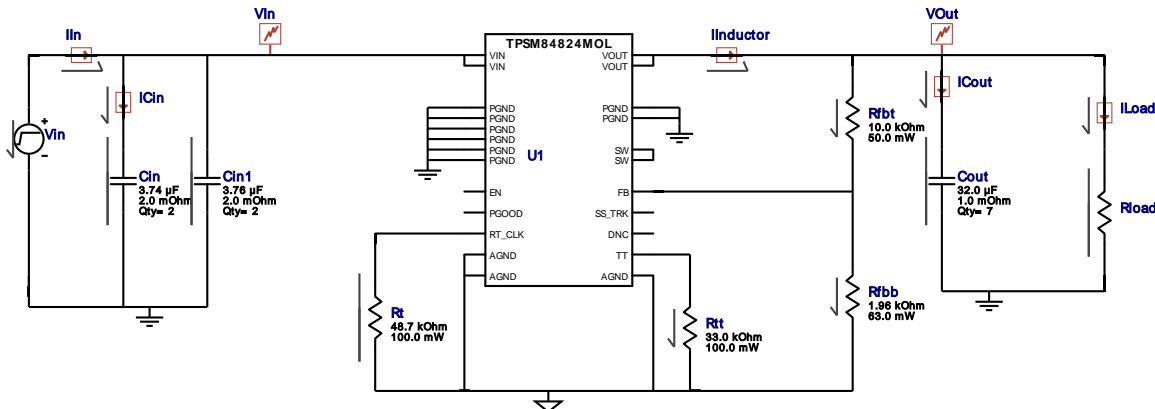

Simulation Parameters


#	Name	Parameter Name	Description	Values
1.	Rload	R	Load Resistance	0.45 Ohm

  

Design Id = 62


sim_id = 2

Simulation Type = Load Transient

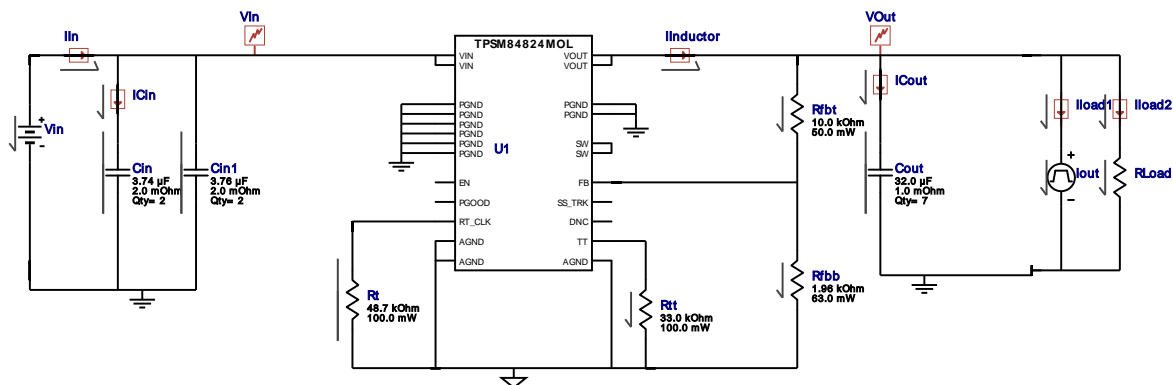

Simulation Parameters


#	Name	Parameter Name	Description	Values
1.	Cin	IC	Initial Voltage	12.0 V
2.	Cout	IC	Initial Voltage	3.6 V
3.	Iout	signal_type	Signal Type	PULSE
		I1	Initial Load Current	0 A
		I2	Minimum Load Current	-7.2 A
		Td	Initial Time Delay	0.2m s
		Tf	Fall Time	10u s
		Tr	Rise Time	10u s
		Pw	Pulse Width	0.3m s
4.	Rload	R	Load Resistance	0.45 Ohm

 

Design Id = 62



sim_id = 3

Simulation Type = Input Transient

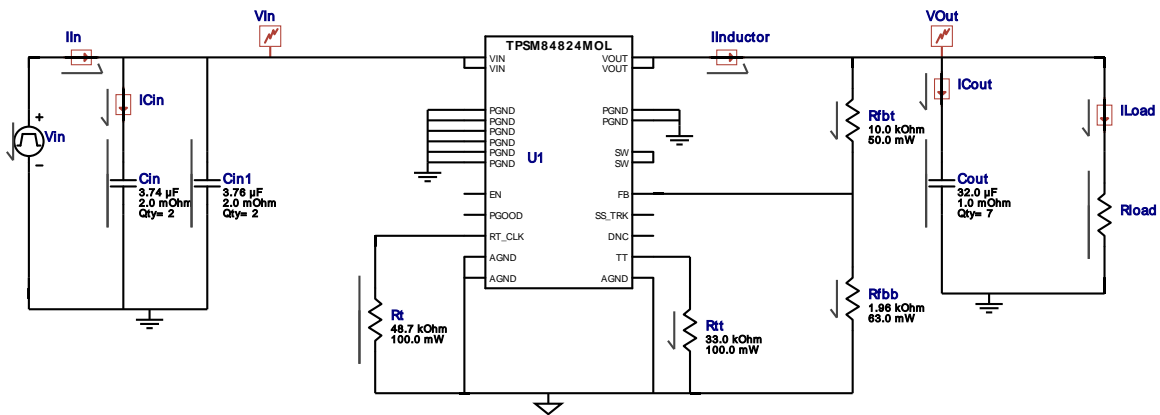

Simulation Parameters


#	Name	Parameter Name	Description	Values
1.	Cin	IC	Initial Voltage	12.0 V
2.	Cout	IC	Initial Voltage	3.6 V
3.	Rload	R	Load Resistance	0.45 Ohm

  

Design Id = 62


sim_id = 4

Simulation Type = Steady State

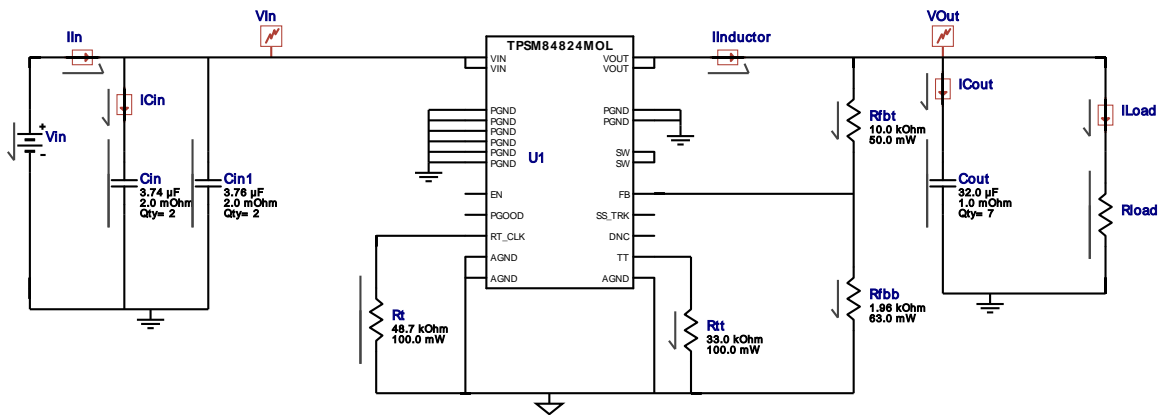

Simulation Parameters

#	Name	Parameter Name	Description	Values
1.	Cin	IC	Initial Voltage	12.0 V
2.	Cout	IC	Initial Voltage	3.6 V
3.	Rload	R	Load Resistance	0.45 Ohm

 

Design Assistance

1. Master key : 4B22EECAC03607DD[v1]

2. **TPSM84824** Product Folder : <http://www.ti.com/product/TPSM84824> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.