Load detect with split power path


bqMaximo
Willy Massoth

TI Information – Selective Disclosure



Split power path

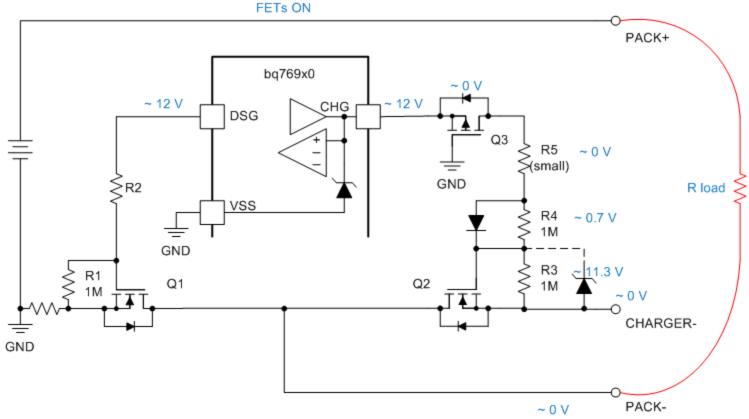- Charge through discharge FET for protection
- Discharge bypassing charge FET




2

Load detect inoperable with split path

- R load does not pull up CHARGER-, FET leakage typically too low
- Need ~ 1V/750k = 1.4 uA into CHG pin to sense load

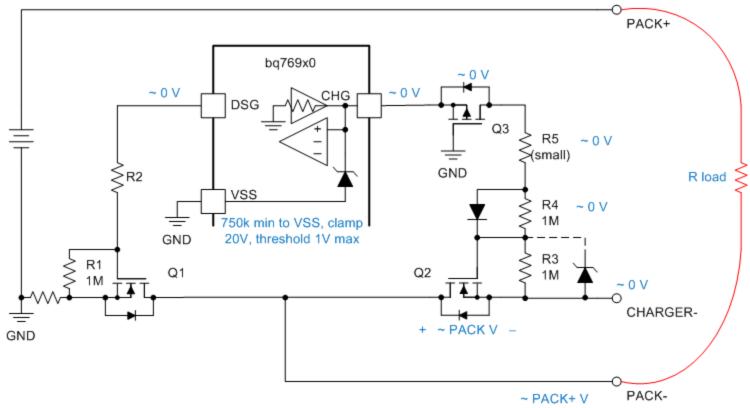
Load Detect inoperable with split charge path



TI Information – Selective Disclosure


Load detect resistor needed

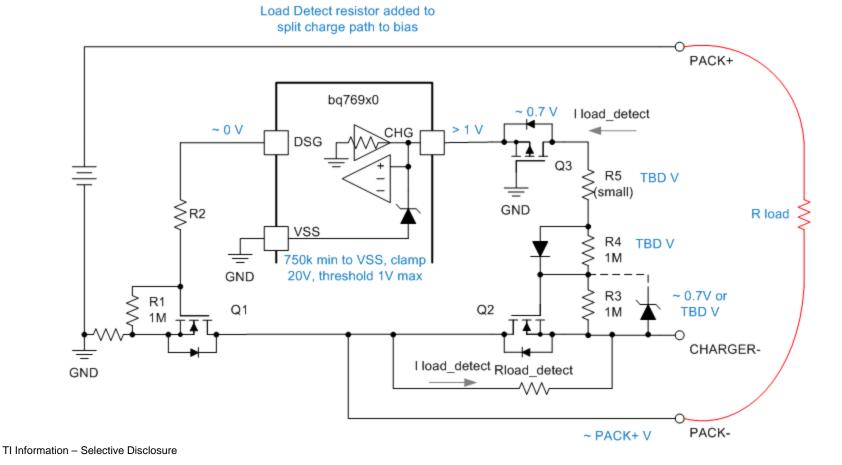 Select Rload_detect to provide voltage through divider with minimum allowed PACK+, minimum load for detection and circuit option (zener)



Rload_detect allows charger leakage

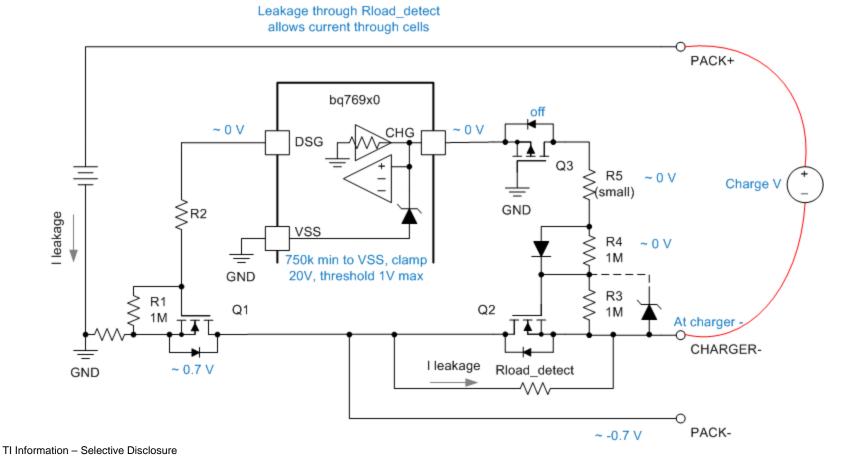
 Resistor will allow continued charge current when charger is off. Be sure this is acceptable; ~ (Charge Vmax – Cells Vmin)/Rload_detect



5

Alternate load detect by microcontroller

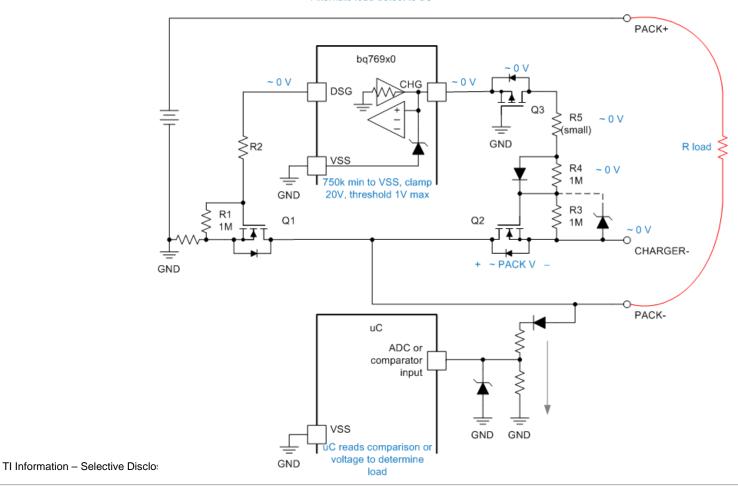 May be preferred. Divider will allow continued discharge after protection unless switched. Diode blocks charge current



6