


UCC28070

StartUp behaviour

Design Root Cause Analysis



Introduction

 - Observe spurious PWM signal at Startup.
- There is a delay of some ms before normal operation starts
- The behavior was confirmed on the TI evm.
- TI Design
 - Ran simulations to reproduce the behavior.
 - Analyzed the design implementation to confirm the IC behavior.




Root Cause Analysis - silicon

- The waveforms on Current Amplifier Output A (CAOA) and CAOB explain the behavior:
 - The switching is inhibit until $CAOA/B < 0.7V$, see circuit below
 - Once $CAOA/B$ rises above $0.7V$, at the first rising/falling edge of the clock GDA/GDB are turned on
 - After the first switching cycle $CAOA/B$ decrease going below $0.7V$, inhibiting any other switching cycle
 - The switching will restart again once $CAOA/B$ goes again above $0.7V$

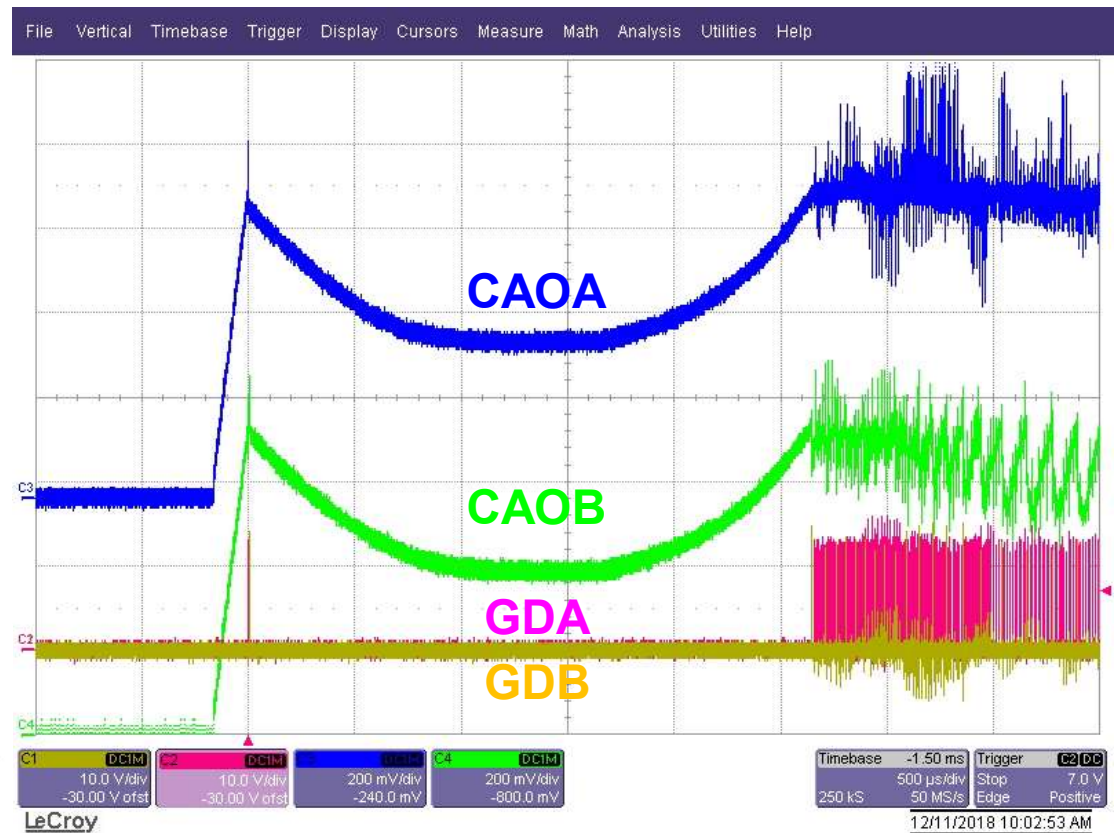 


Root Cause Analysis - simulation

- Simulation confirmed the analysis:
 1. A first packet of switching cycle is observed
 2. Then there is no switching for few ms
 3. The switching starts again later
- The first packet of switching cycles starts when CAOA and CAOB rise above 0.7V
- Around the middle of this packet of switching cycles CAOA and CAOB start to fall
- When CAOA and CAOB goes below 0.7V the switching stops
- The switching restarts when CAOA and CAOB go again above 0.7V

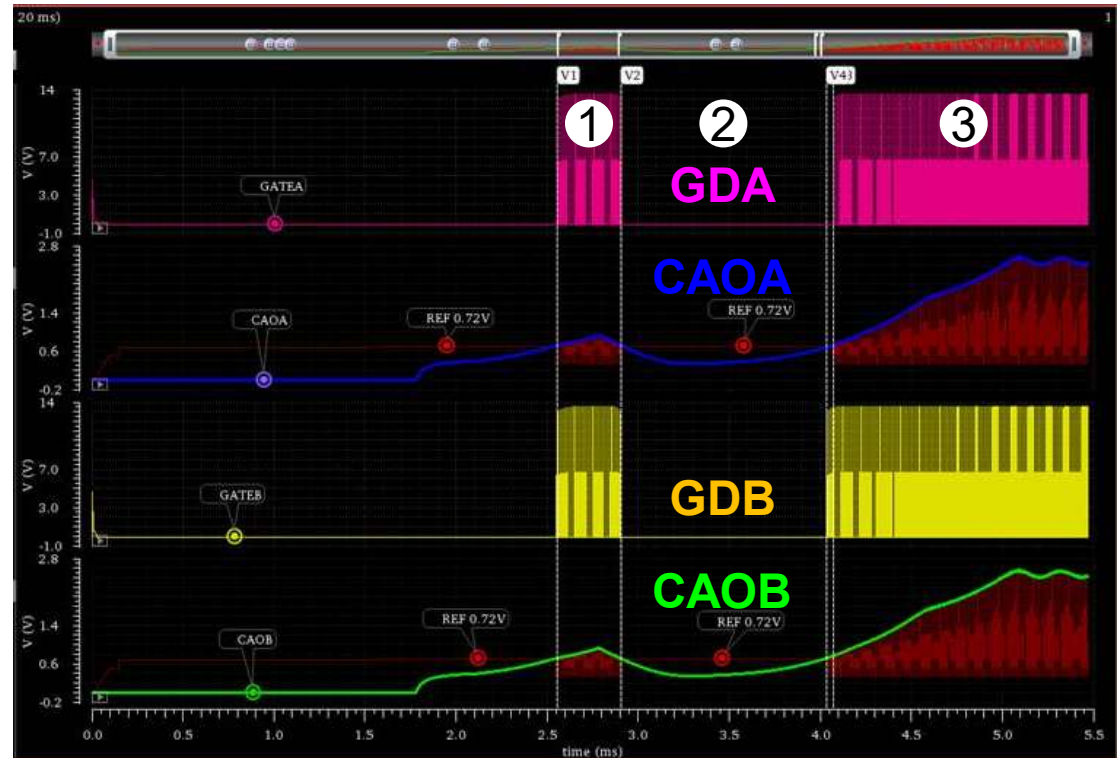

Why do CAO/A/B change Slope

- Simulation shows that a negative shift on the positive input (IN+) of the current error amplifier occurs, on both phases, after some switching cycles
 - When IN+ is above IN- , CAO rises
 - When the negative shift occurs, IN+ drops below IN- and CAO changes slope starting to decrease
 - IN+ has an increasing trend that will take some time to compensate for the negative step and move IN+ again above IN- , to make CAO rise again
- This negative shift occurs in IN+ signal due to a change in bias current when the Current Synthesizer circuit is enabled. This is part of the normal startup process.

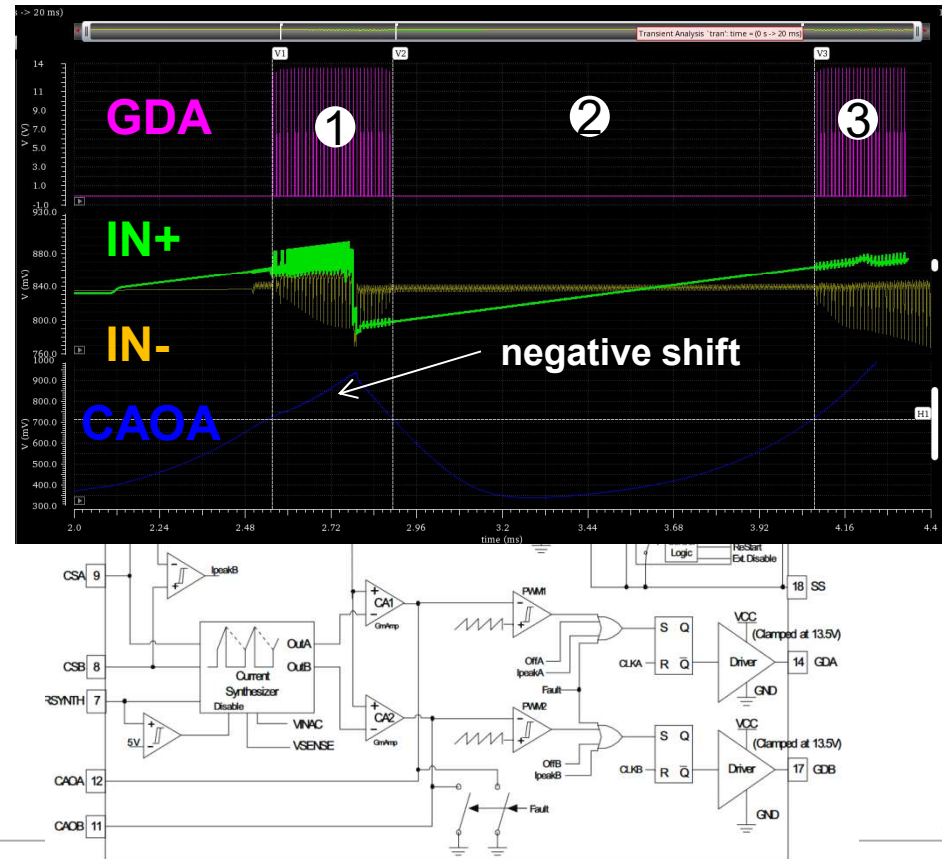

Root Cause Analysis – conclusion

- At power-up the switching is determined by the CAO/A/B level:
 - $V(\text{CAO/A/B}) > 0.7\text{V}$ switching allowed
 - $V(\text{CAO/A/B}) < 0.7\text{V}$ switching inhibited
- CAO/A/B initially rises but after the first switching cycles it starts to fall
- The change in the slope is due to a shift on one input of the current error amplifier, that will cause the plus input to become lower than the minus input
- The negative shift occurs when the Current Synthesizer circuit starts to work
- The behavior is in line with the IC design implementation