

Technical Note TN16081101

Spikes on 175063A

Created by Jürg Schneider, TN16081101_Spikes_on_175063A.docx

Version: A Release 0

Copyright © 2016

Creation date: 11.August 16 15:59

Print date: 12.August 16 14:01

Versions and Releases:

Version A: None

Technical Note.....	1
1. Setup.....	3
1.1 Used devices	3
2. Comparison of measuring methodes.....	4
2.1 GND connection of the probe	4
2.1.1 Conclusion.....	6
2.2 Normal probe vs. Sapphire SI-9001.....	7
2.2.1 Conclusion.....	7
3. Initial assembly.....	8
3.1 Spikes.....	8
4. With snubber 4R7 / 10nF.....	13
4.1 Spikes.....	13
5. History	16

1. Setup

1.1 Used devices

Scope: waveRunner 44Xi

Probes: 10x

BW limited to 20MHz

Galvanic separated probe: Sapphire SI-9001

2. galvanic separated probe: Sapphire SI-9101

DRAFT / PRERELEASE

2. Comparison of measuring methodes

2.1 GND connection of the probe



Figure 1, spring contact



Figure 2, wired GND connection

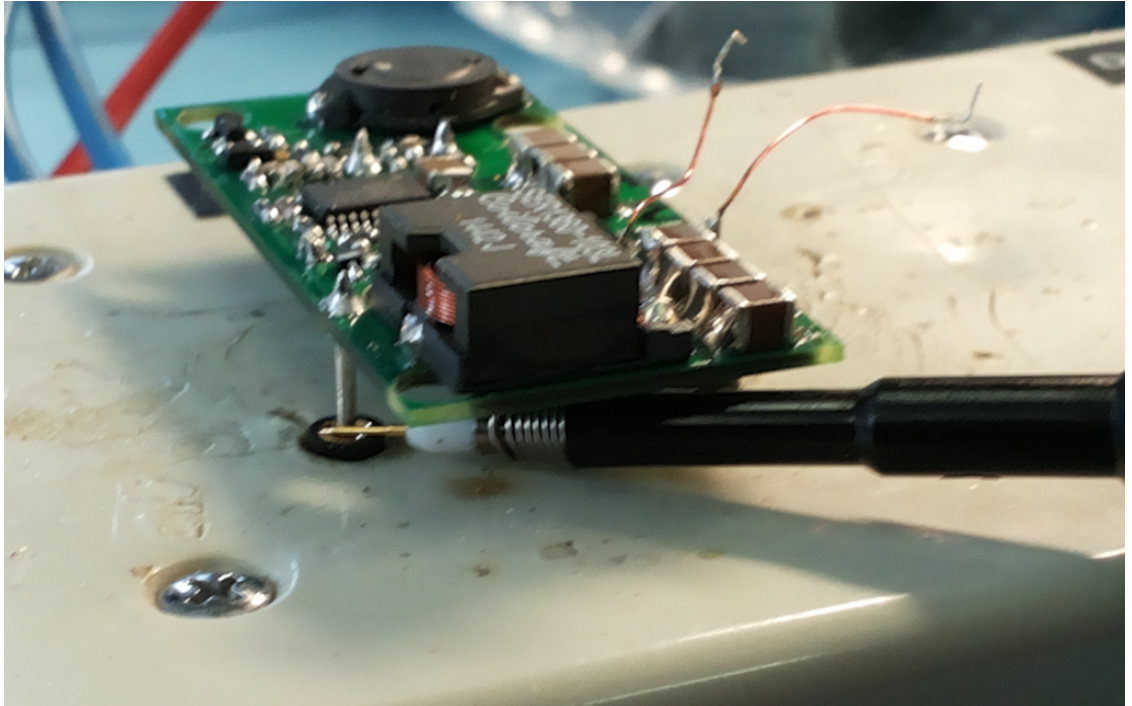


Figure 3, spring contact across the pins

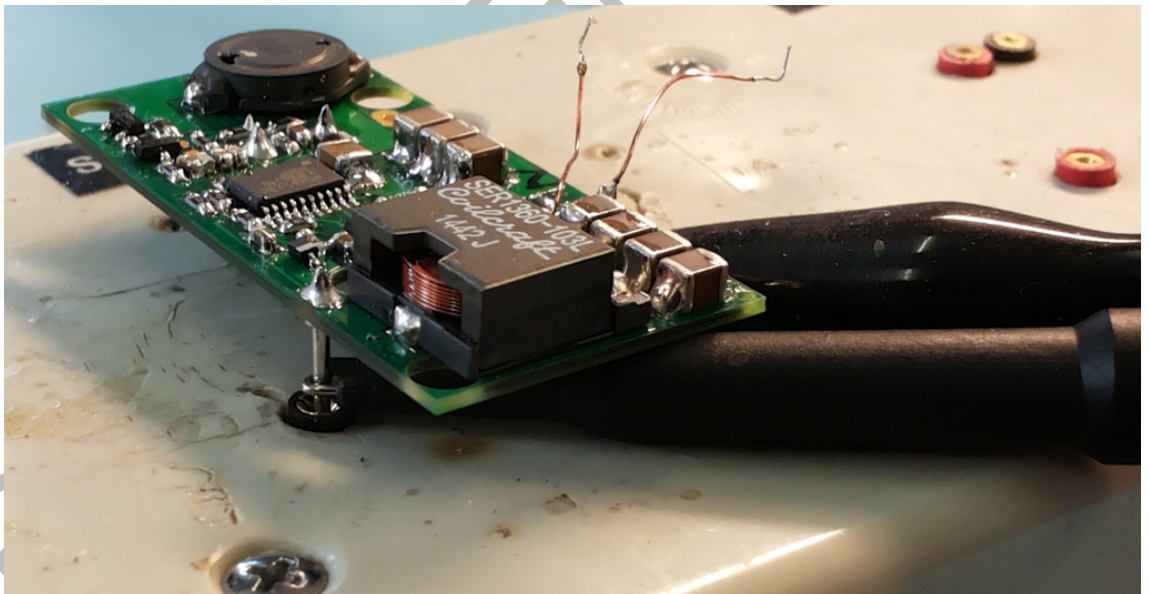


Figure 4, wired GND connection across the pins

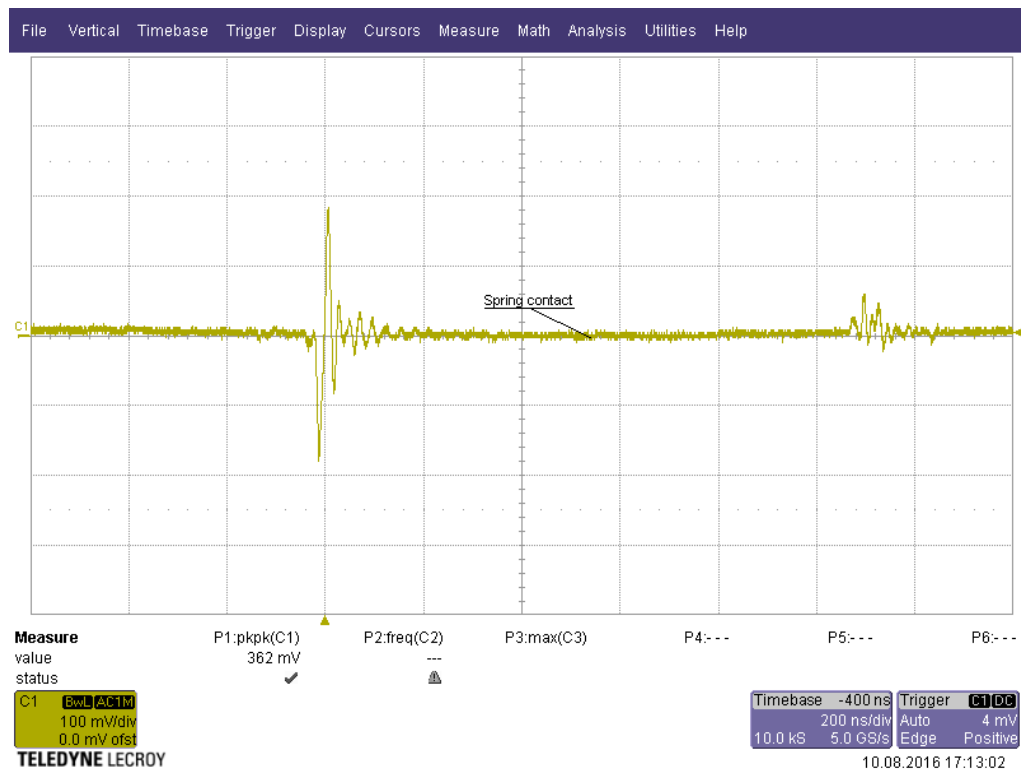


Figure 5, HF spikes with spring contact across the pins

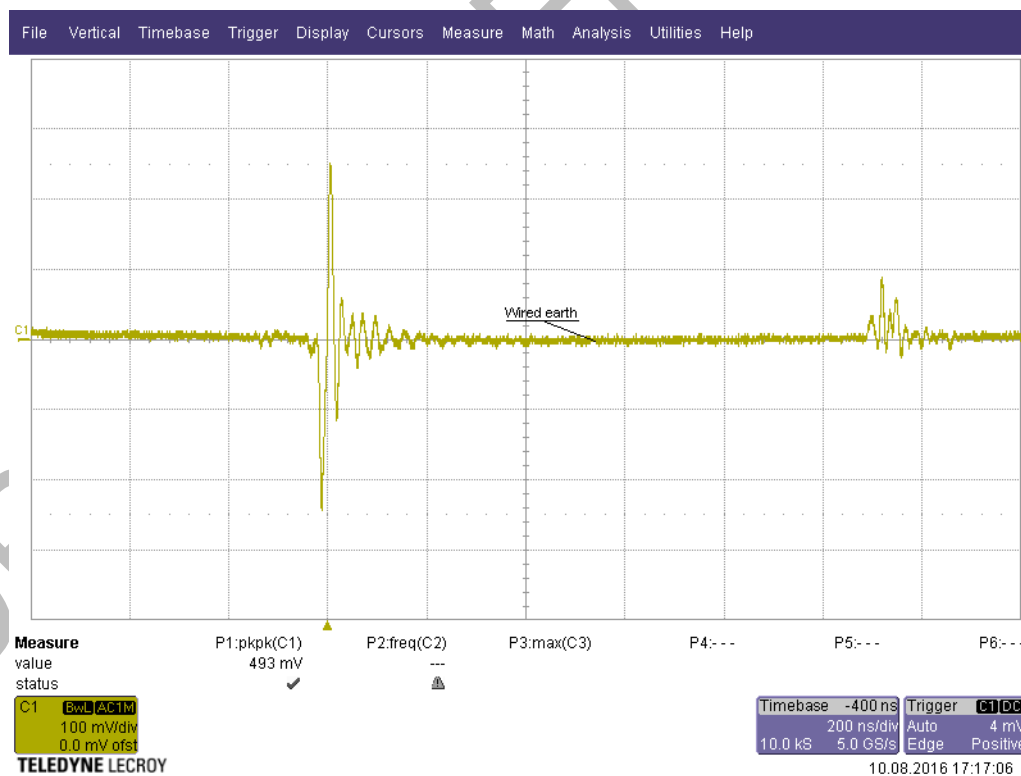


Figure 6, HF spikes with wired GND connection across the pins

2.1.1 Conclusion

With wired GND connection the values are little worse, but this is not the cause.

2.2 Normal probe vs. Sapphire SI-9001

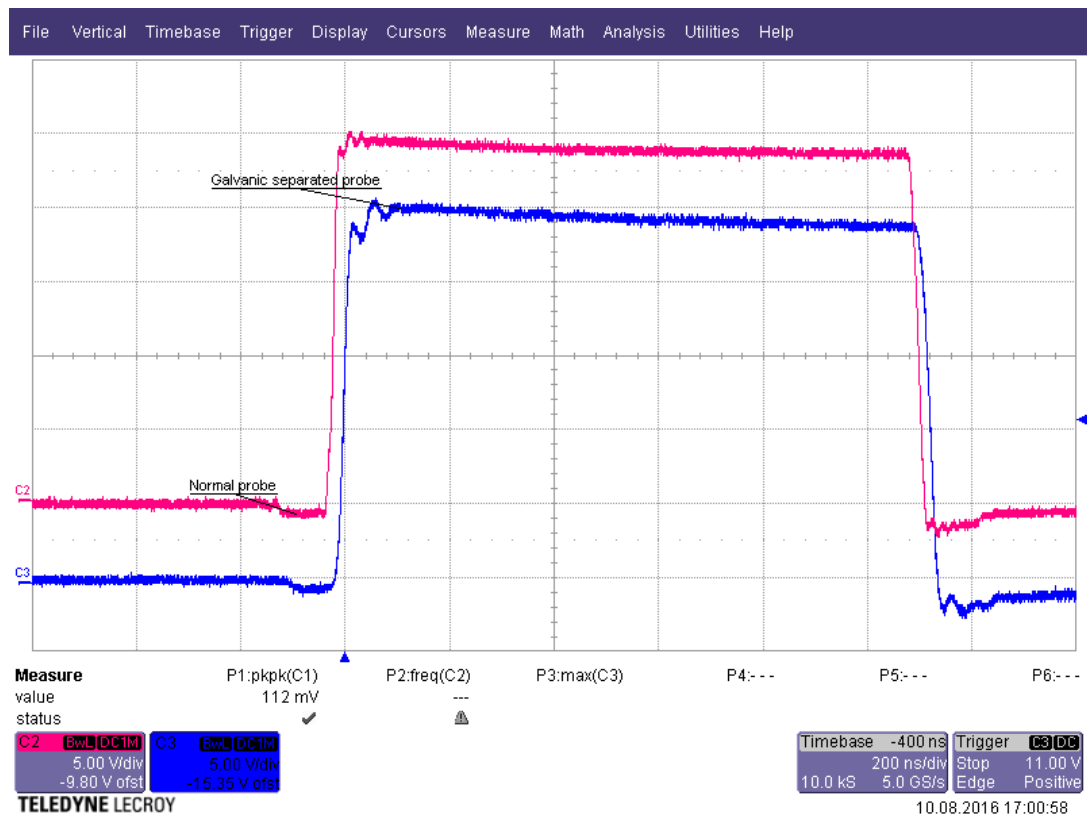


Figure 7, Sapphire SI-9001 in comparison

2.2.1 Conclusion

The differences seems marginal, the Sapphire probe has a little delay.

Further measurments are made with the wired probe (HF spikes) and Sapphire probe (others).

3. Initial assembly

3.1 Spikes

Yello: The spikes on Uout.

Blue: The switching node.

Green: Inductor current.

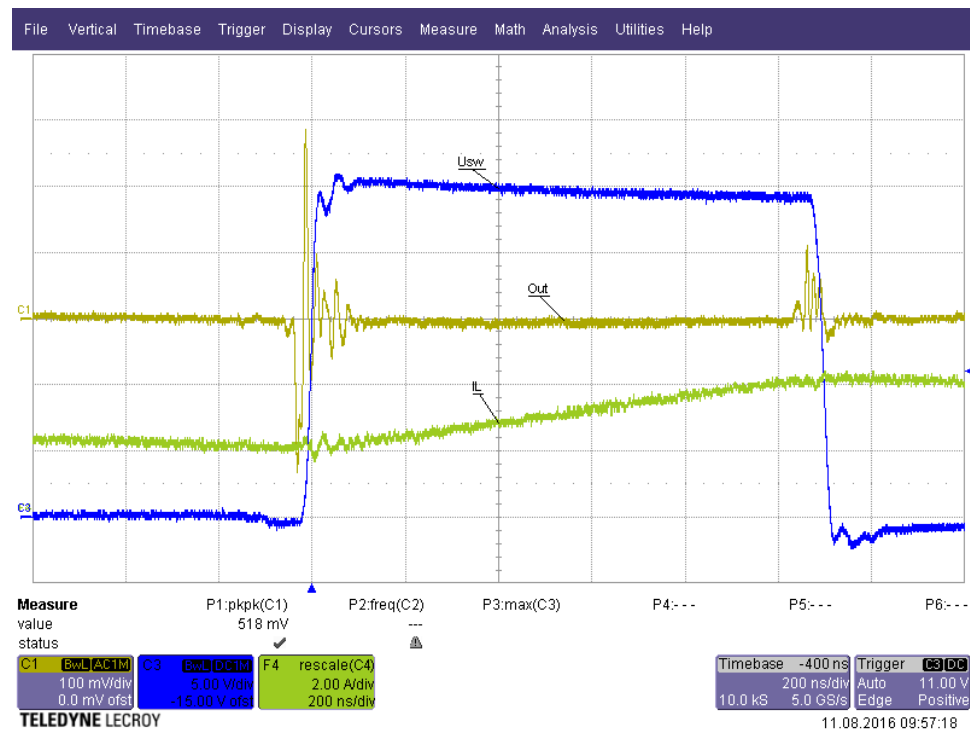
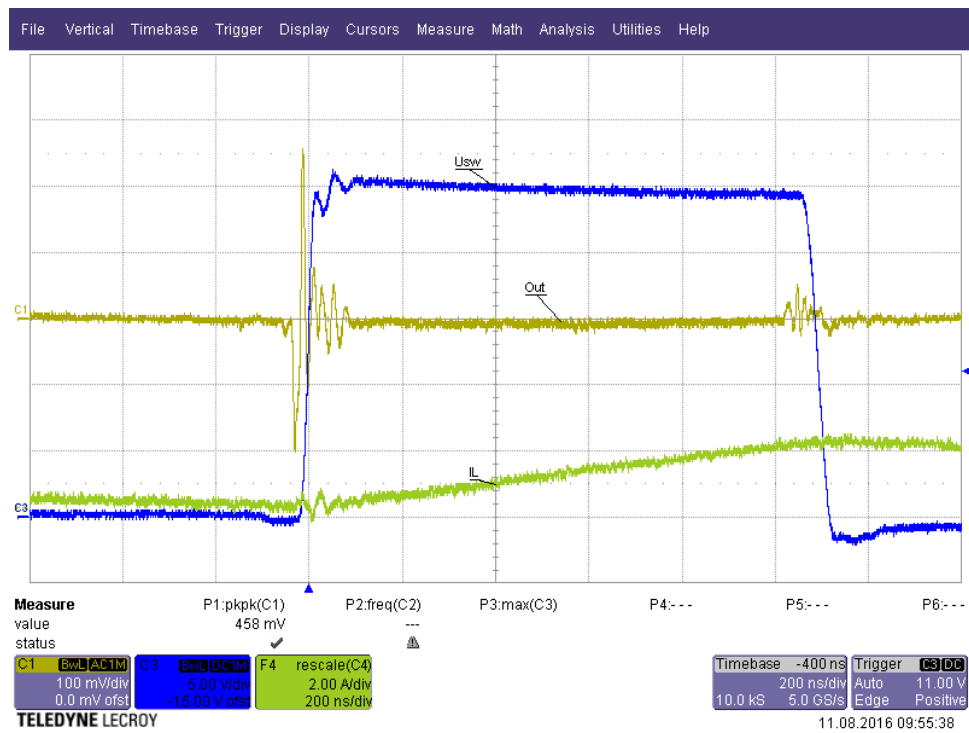
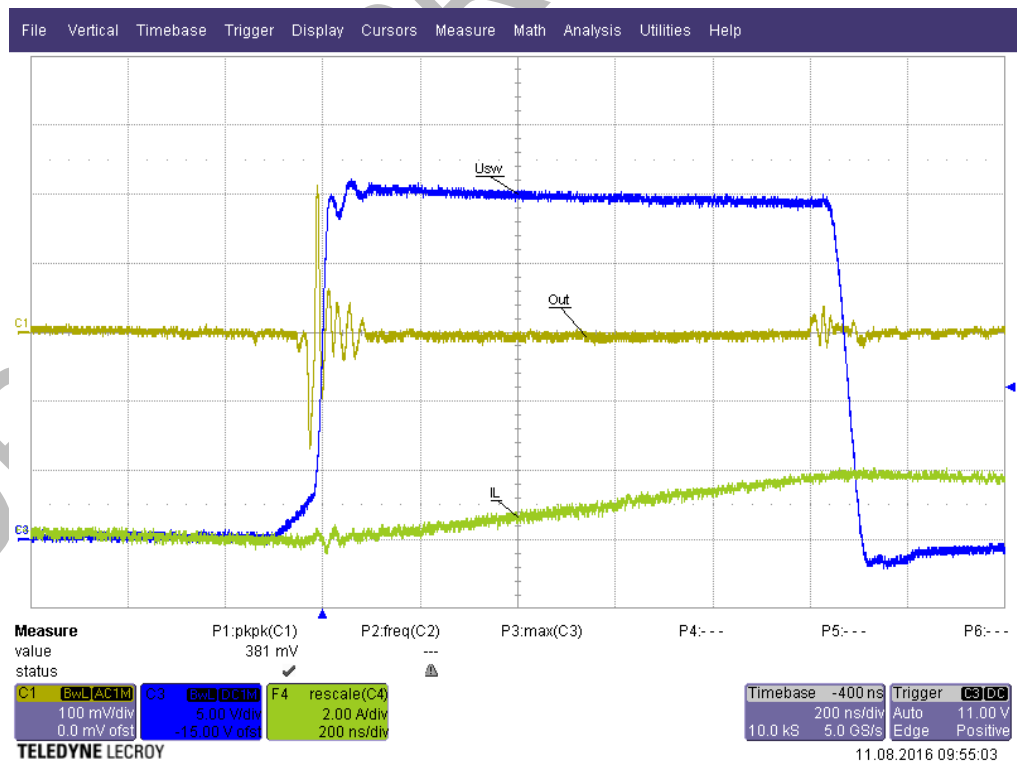
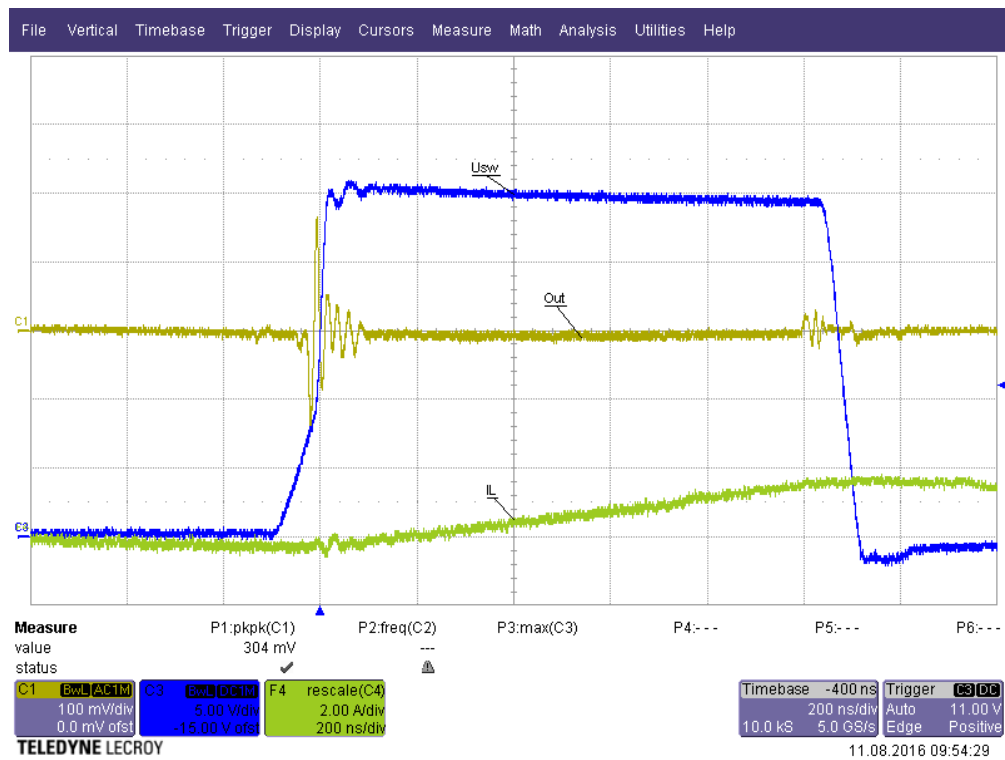
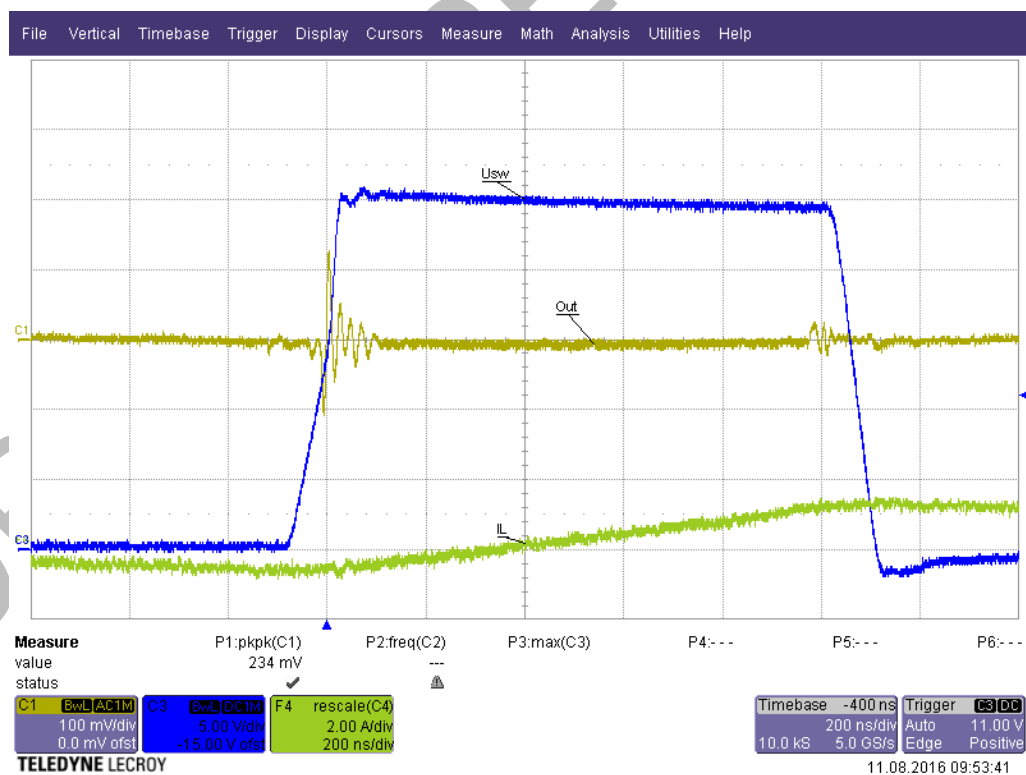


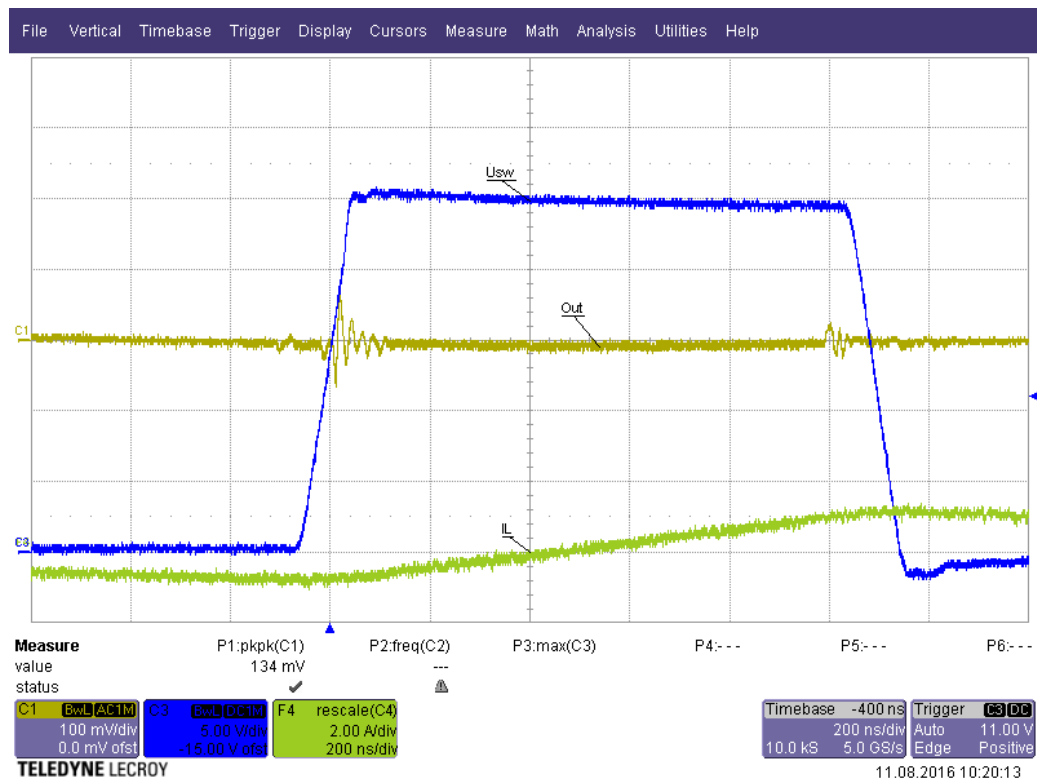
Figure 8, Spikes, $U_{in} = 24V$, $I_{out} = 3A$

Figure 9, Spikes, $U_{in} = 24V$, $I_{out} = 1.2A$

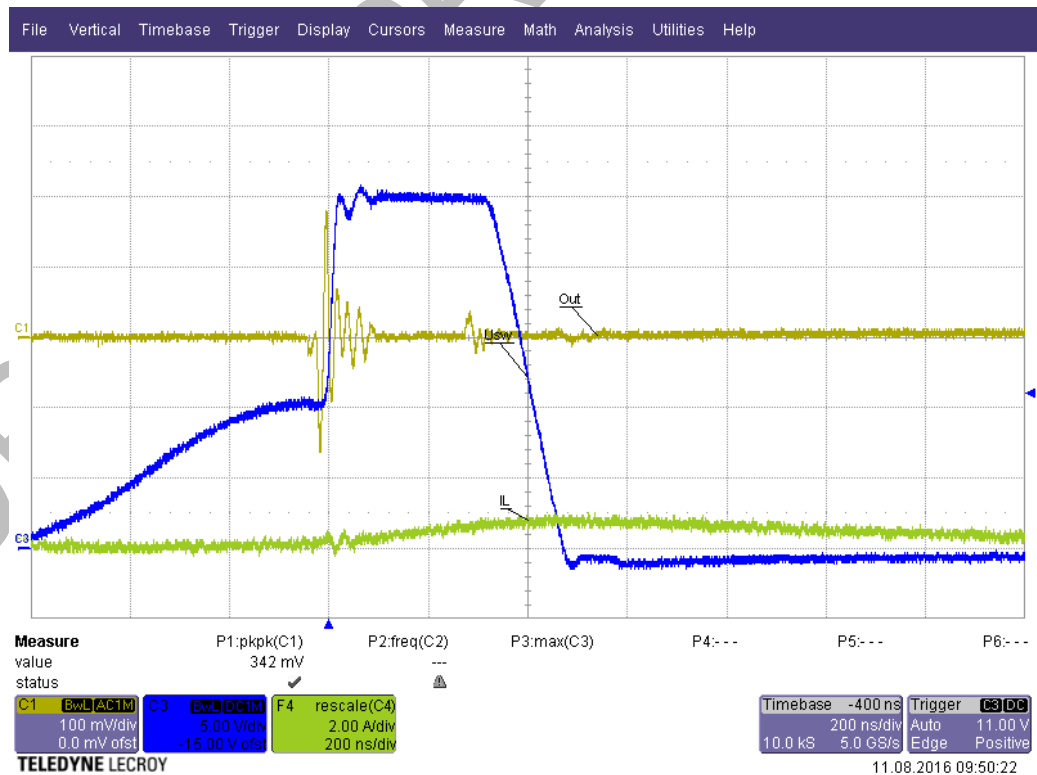
The inductor becomes empty:

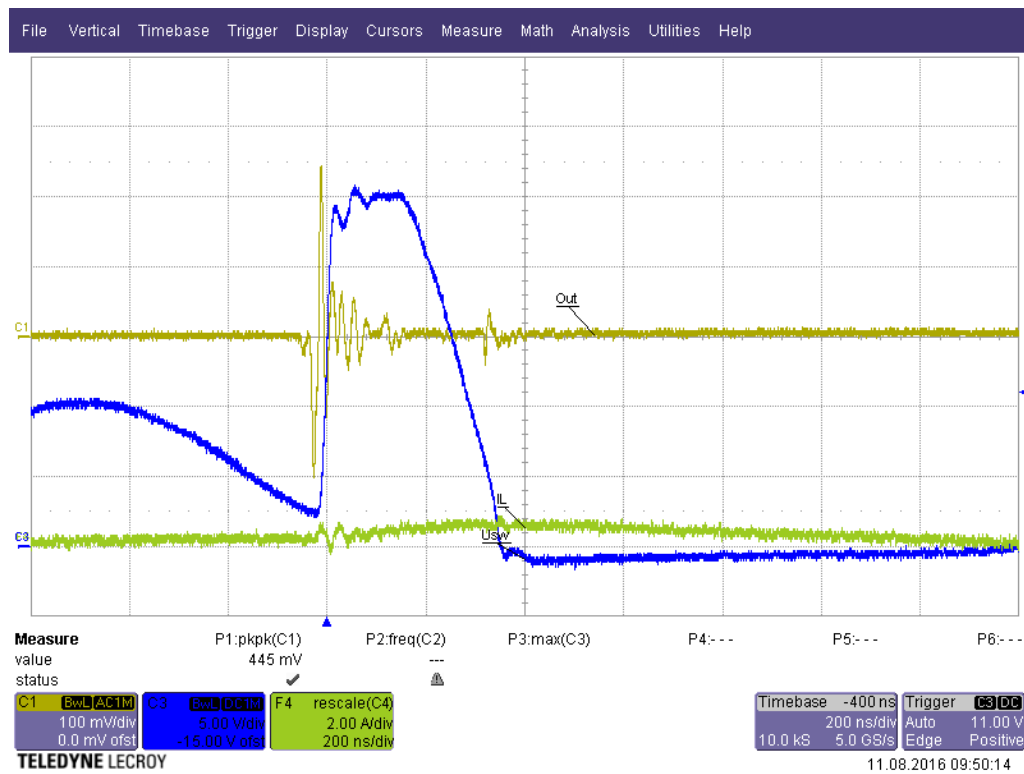
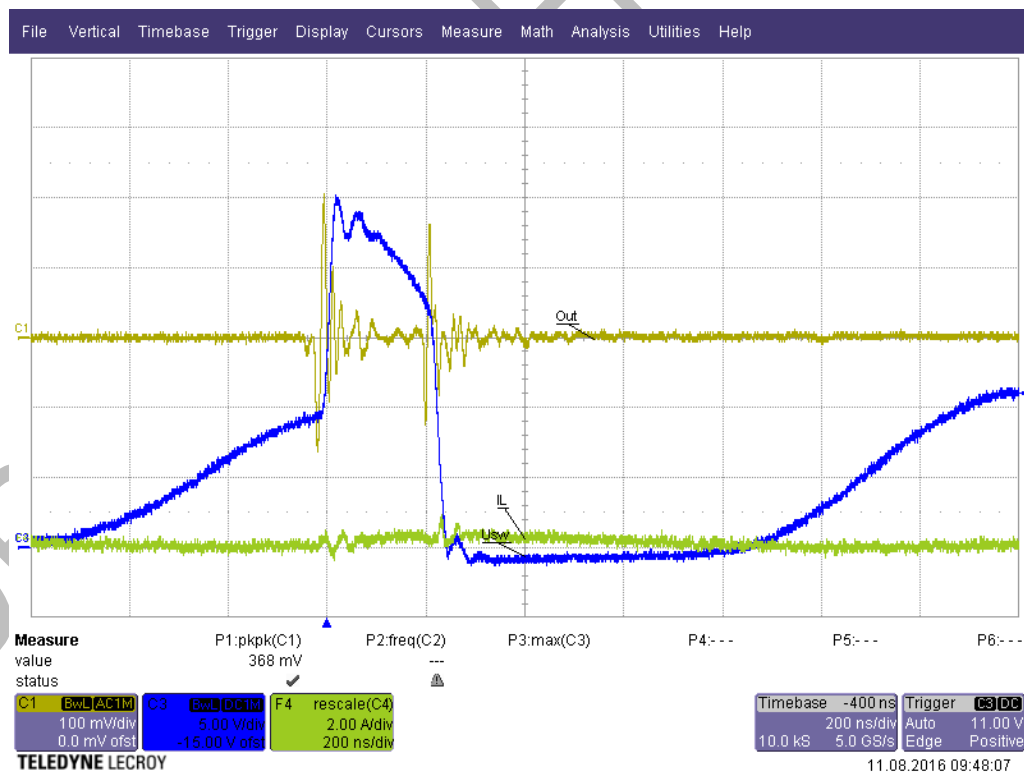
Figure 10, Spikes, $U_{in} = 24V$, $I_{out} = 0.8A$

Figure 11, Spikes, $U_{in} = 24V$, $I_{out} = 0.5A$ Figure 12, Spikes, $U_{in} = 24V$, $I_{out} = 0.2A$

Figure 13, Spikes, $U_{in} = 24V$, $I_{out} = 0A$

In case of hard load jumps the controller switches to diode emulation:

Figure 14, Spikes, $U_{in} = 24V$, $I_{out} = 0.12A$

Figure 15, Spikes, $U_{in} = 24V$, $I_{out} = 0.065A$ Figure 16, Spikes, $U_{in} = 24V$, $I_{out} = 0A$

4. With snubber 4R7 / 10nF

4.1 Spikes

With snubber the controller works at light loads always in diode emulation:

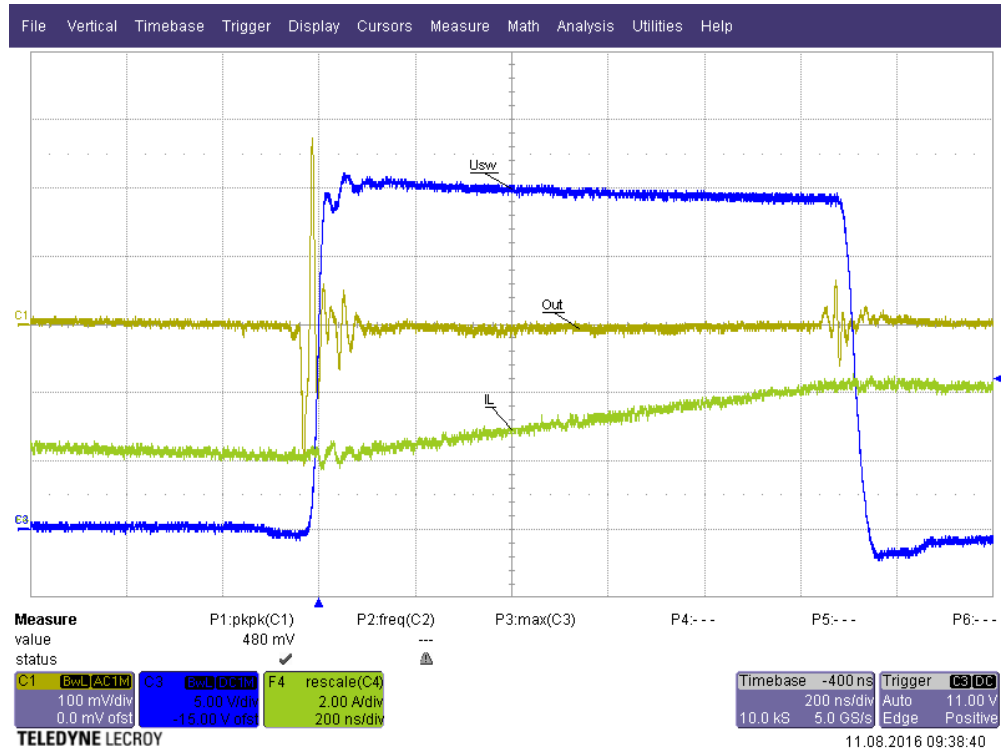


Figure 17, Spikes, $U_{in} = 24V$, $I_{out} = 3A$

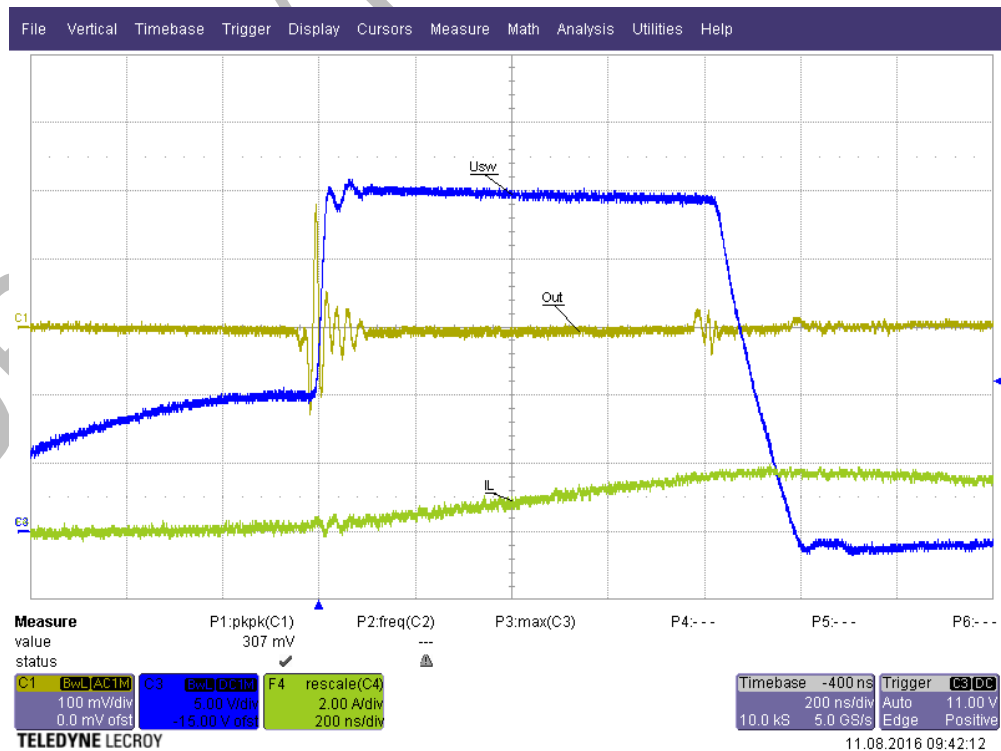
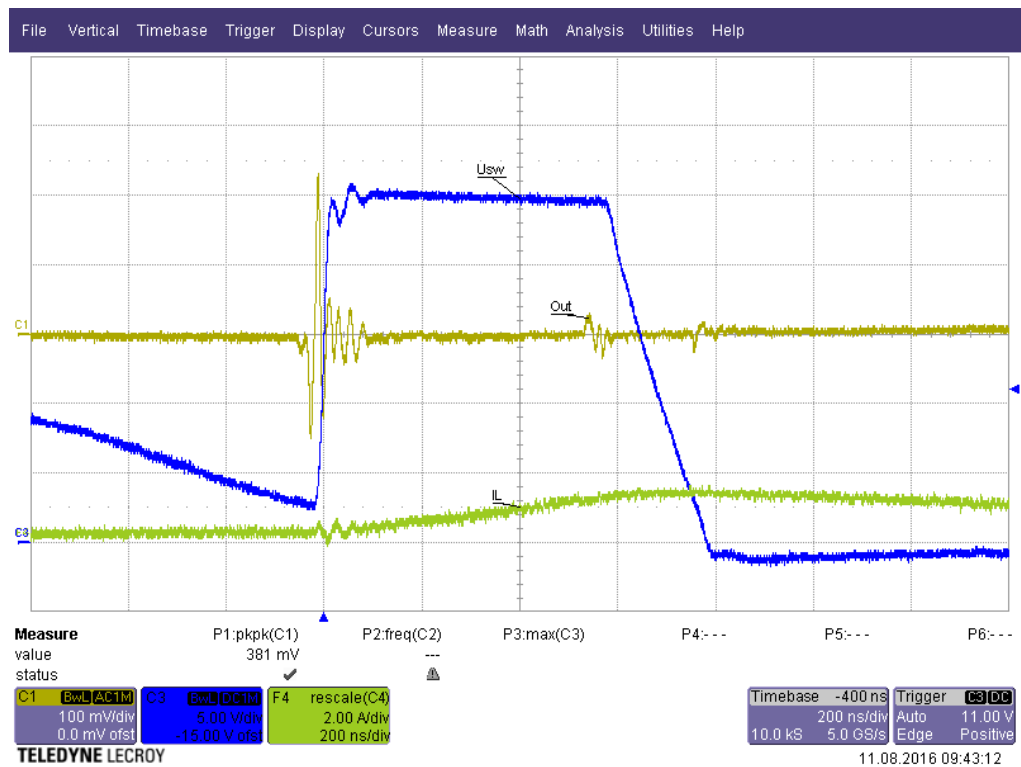
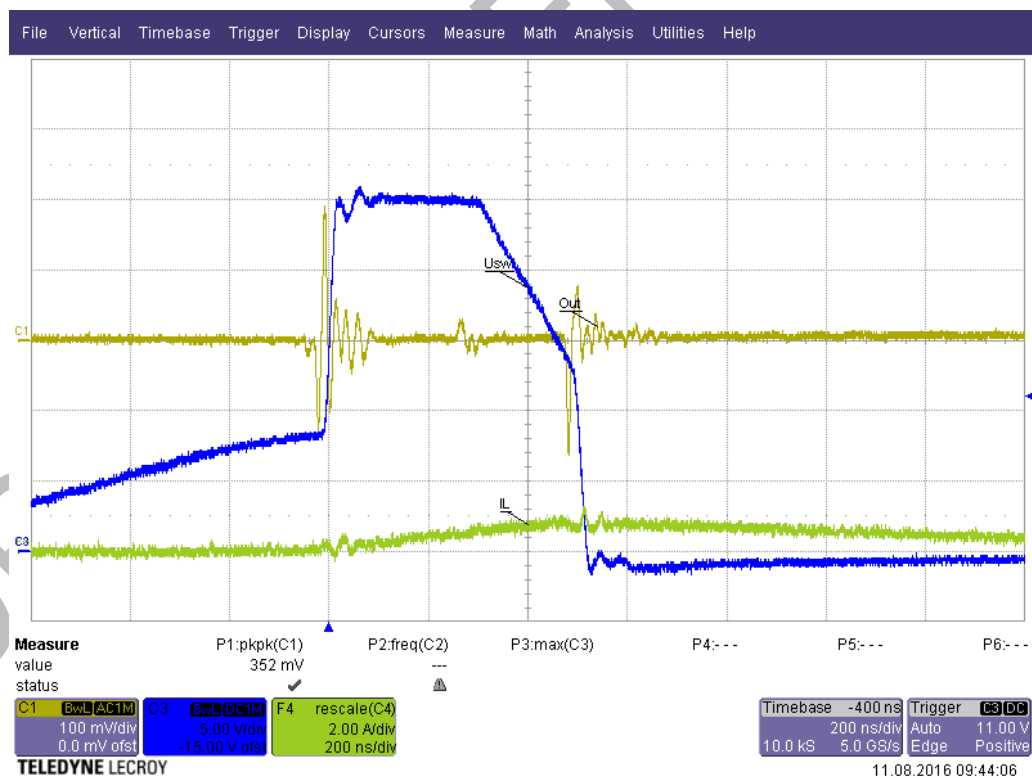
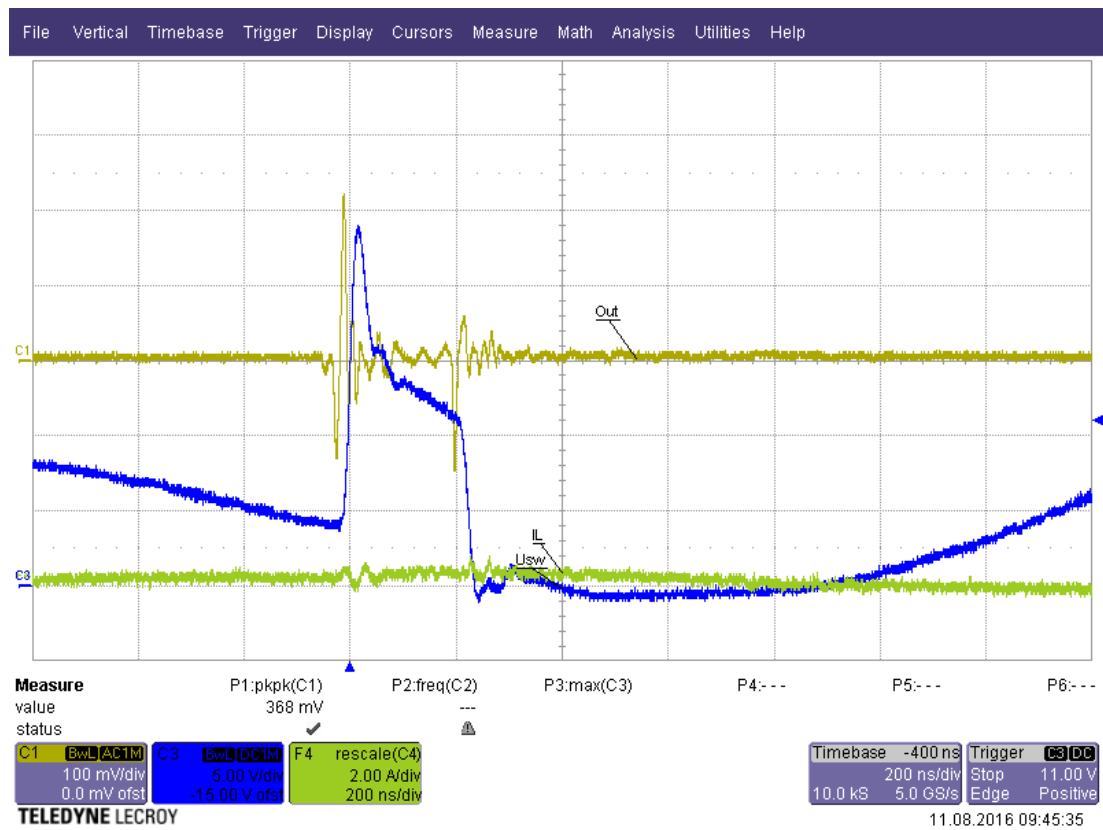


Figure 18, Spikes, $U_{in} = 24V$, $I_{out} = 0.62A$

Figure 19, Spikes, $U_{in} = 24V$, $I_{out} = 0.43A$ Figure 20, Spikes, $U_{in} = 24V$, $I_{out} = 0.12A$

Figure 21, Spikes, $U_{in} = 24V$, $I_{out} = 0A$

The snubber doesn't solve the issue.

5. History

Issue	Date	Remarks
Draft.		

DRAFT / PRERELEASE