


Target Circuit


12V

3.3V#0

3.3V#1

Application Diagram

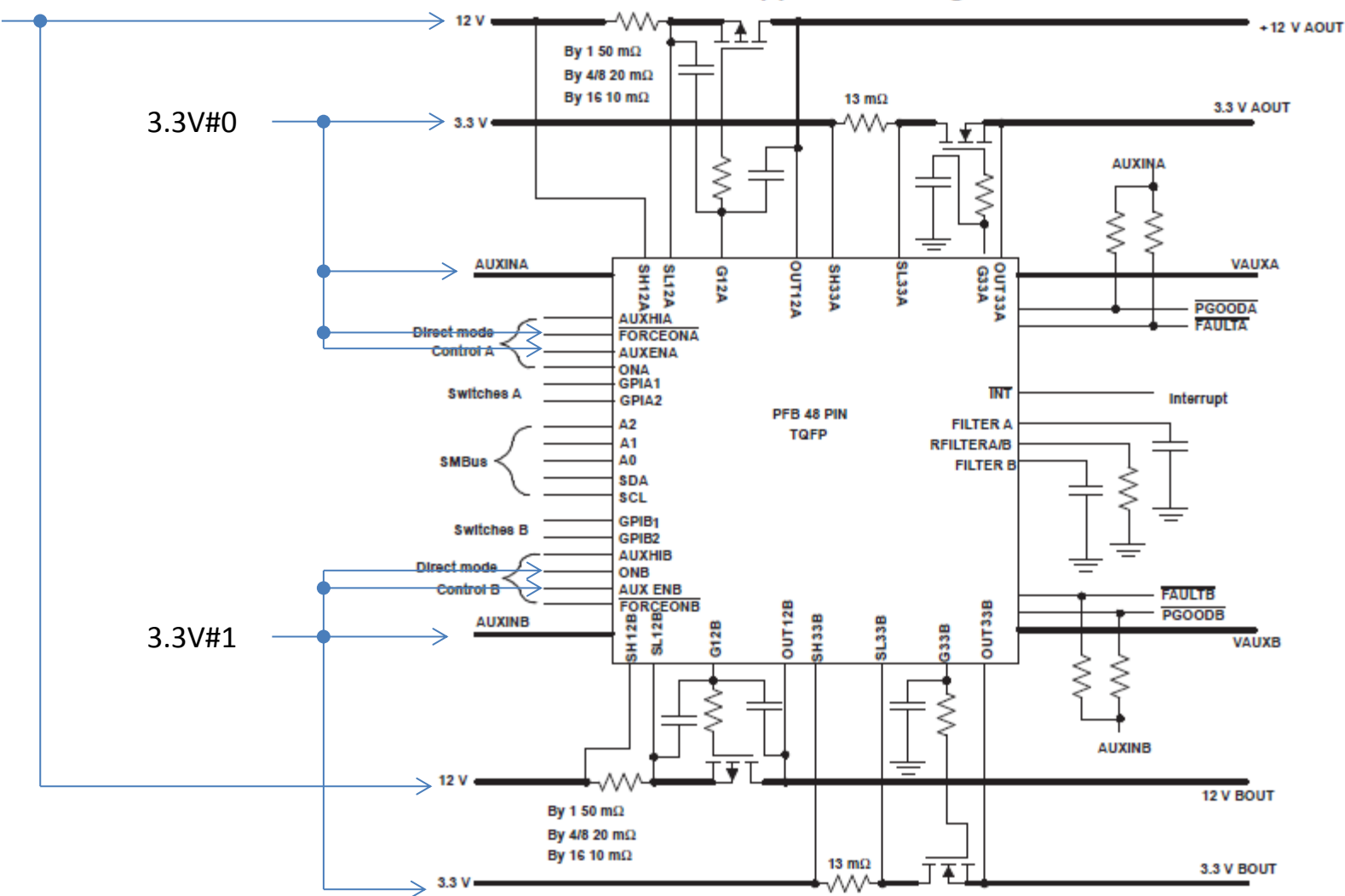

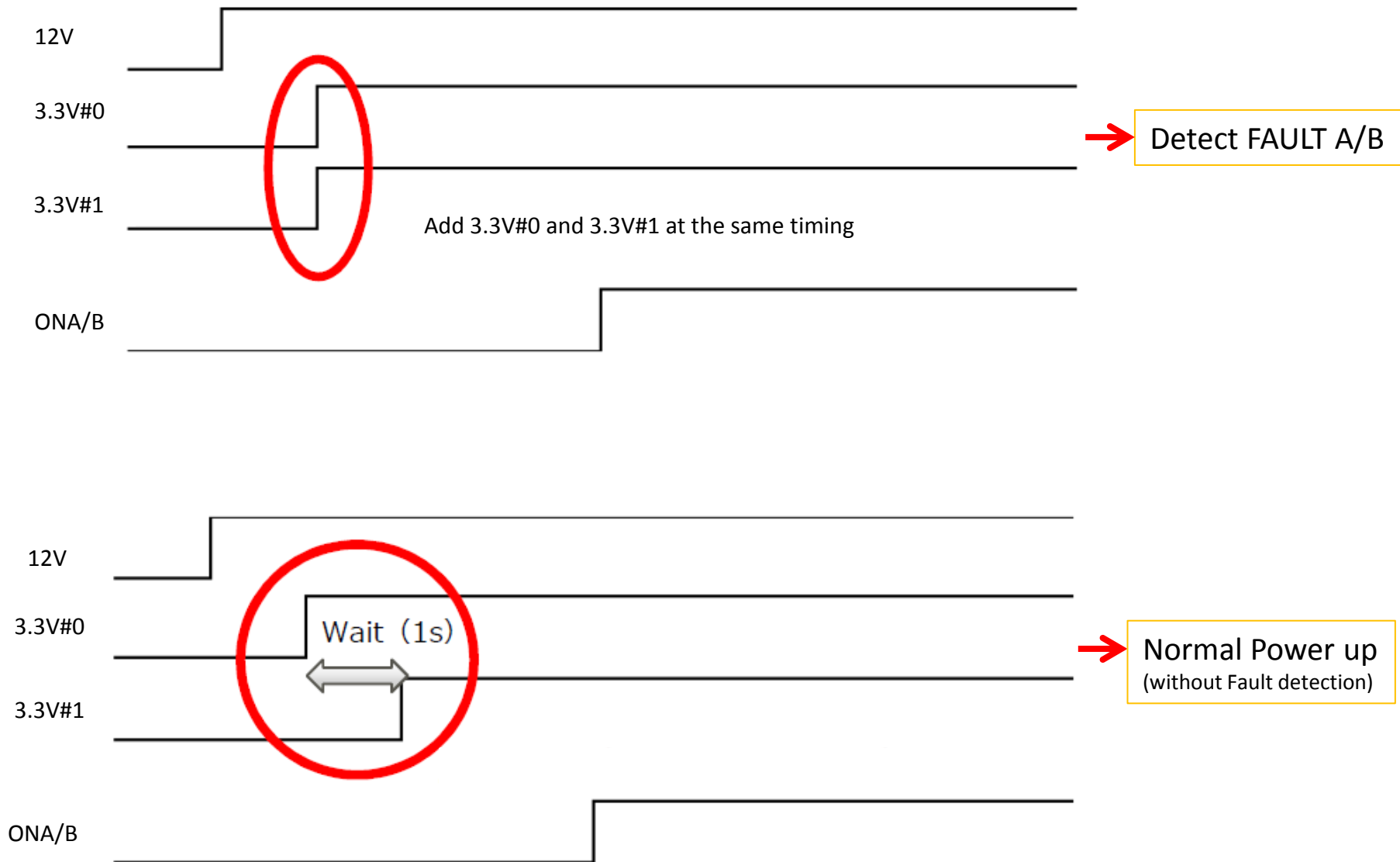



Another Circuit

12V

3.3V#2

Application Diagram

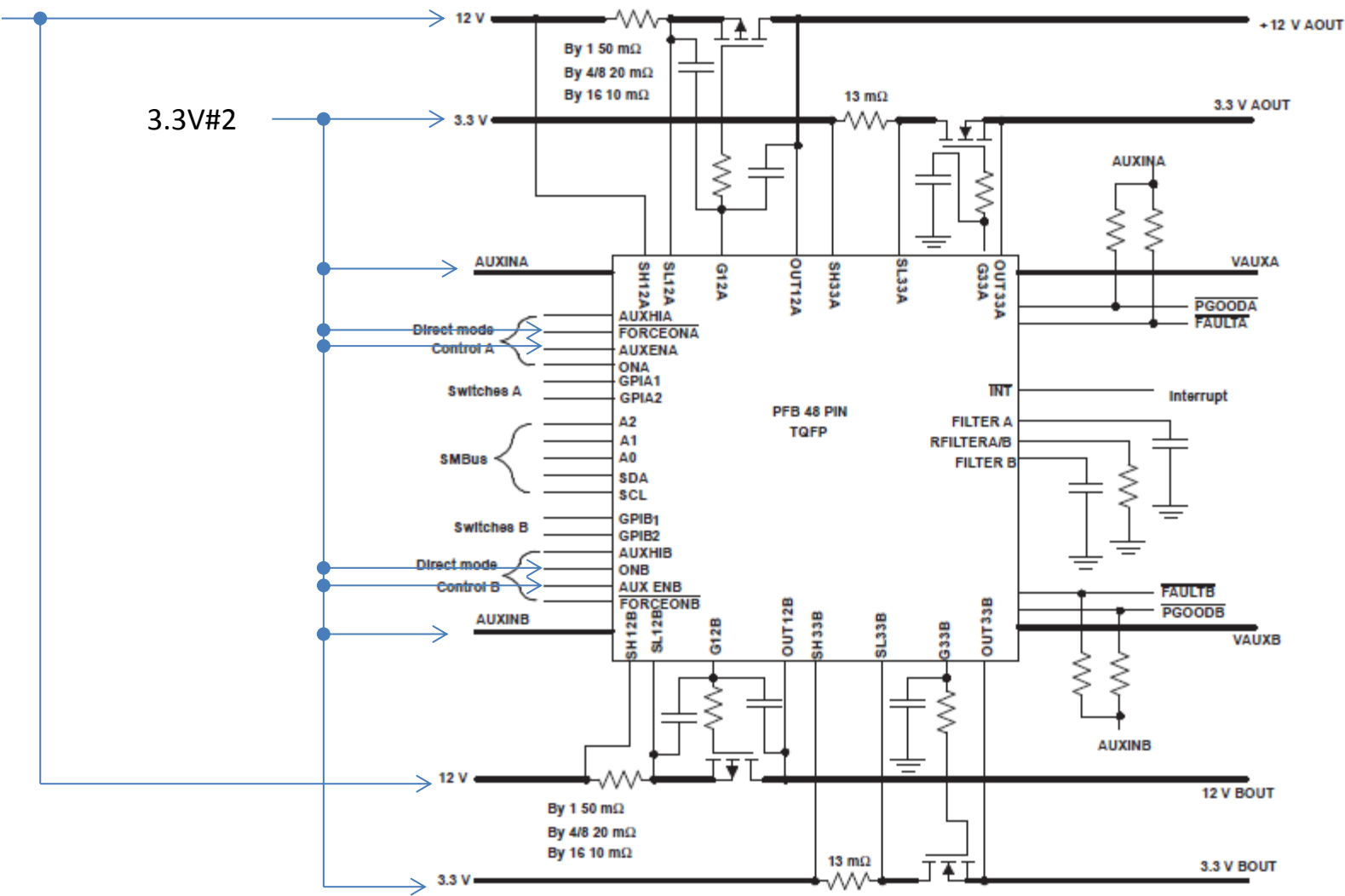

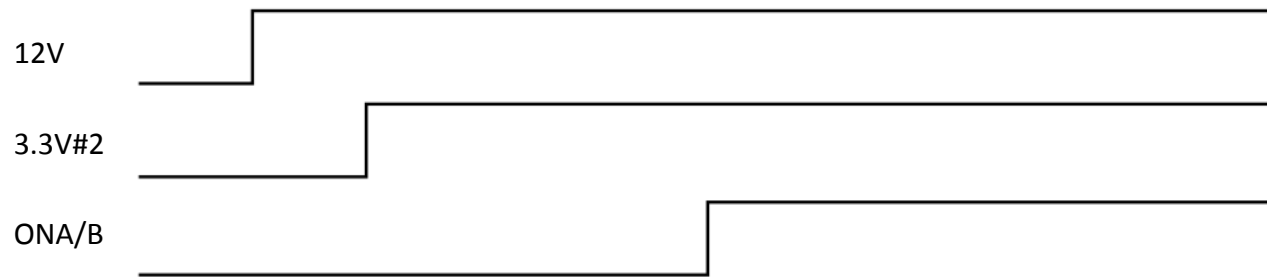

Normal Power up
(without Fault detection)